

- 1.1 A lightning bolt carrying 30,000 A lasts for 50 micro-seconds. If the lightning strikes an airplane flying at 20,000 feet, what is the charge deposited on the plane?

---

**SOLUTION:**

$$I = 30,000 \text{ A}, \Delta t = 50 \mu\text{s}$$

$$Q = I \Delta t$$

$$Q = 30,000 (50 \mu)$$

$$Q = 1.5 \text{ C}$$

- 1.2 If a 12-V battery delivers 100 J in 5 s, find (a) the amount of charge delivered and (b) the current produced.

---

**SOLUTION:**

$$V = 12 \text{ V}, \Delta W = 100 \text{ J in } 5 \text{ s}$$

$$\text{a) } \Delta Q = \frac{\Delta W}{V} = \frac{100}{12}$$

$$\Delta Q = 8.33 \text{ C}$$

$$\text{b) } I = \frac{\Delta Q}{\Delta t} = \frac{8.33}{5}$$

$$I = 1.67 \text{ A}$$



- 1.3** The current in a conductor is 3.5 A. How many coulombs of charge pass any point in a time interval of 2.5 min?

---

**Solution:**

$$1.3 \quad I = 3.5 \text{ A} \quad \Delta t = 2.5 \text{ min} = 150 \text{ s}$$

$$Q = I(\Delta t) \quad \boxed{Q = 525 \text{ C}}$$

1.4 If 90 C of charge pass through an electric conductor in 30 seconds, determine the current in the conductor.

---

**Solution:**

$$1.4 \quad Q = 90 \text{ C} \quad \Delta t = 30 \text{ s}$$

$$I = \frac{Q}{\Delta t} = \frac{90}{30} \quad \boxed{I = 3 \text{ A}}$$

- 1.5 Determine the number of coulombs of charge produced by a 12-A battery charger in an hour.

---

**SOLUTION:**

$$I = 12\text{ A}, \quad \Delta t = 1\text{ hr} = 60\text{ min}$$
$$\Delta t = 3600\text{ s}$$

$$Q = I\Delta t = 12(3600)$$

$$Q = 43.2\text{ kC}$$

1.6 Five coulombs of charge pass through the element in Fig. P1.6 from point A to point B. If the energy absorbed by the element is 150 J, determine the voltage across the element.


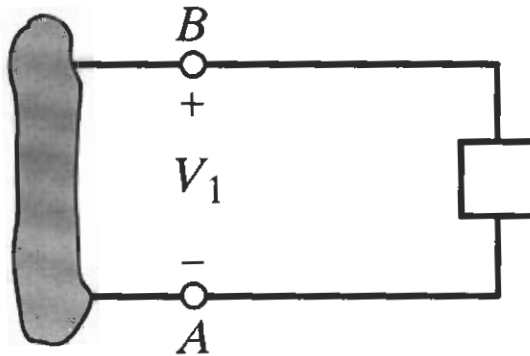


Figure P1.6

Solution:

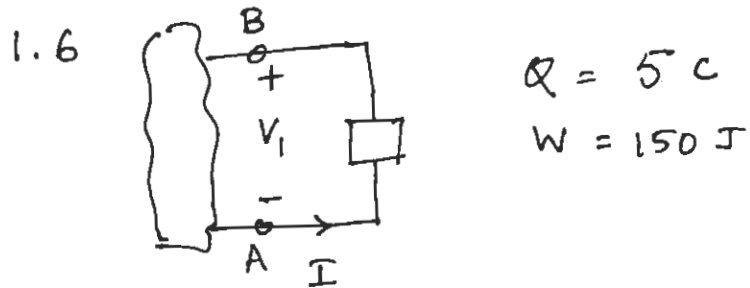

For passive sign convention:  $W = -V_1 Q$

$$V_1 = -\frac{W}{Q}$$

$V_1 = -30 \text{ V}$

1.7 The charge entering an element is shown in Fig. P1.7

Find the current in the element in the time interval

$0 \leq t \leq 0.5$  s. [Hint: The equation for  $q(t)$  is

$q(t) = 1 + (1/0.5)t$ ,  $t \geq 0$ .]

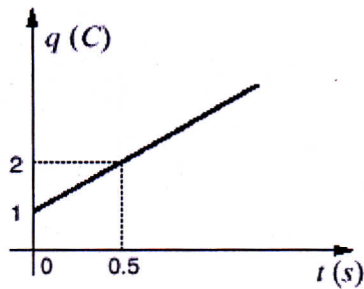


Figure P1.7

**SOLUTION:**

$$q(t) = 1 + 2t, \quad 0 \leq t \leq 0.5 \text{ s}$$

$$i(t) = \frac{dq(t)}{dt}$$

$$i(t) = 2 \text{ A}, \quad 0 \leq t \leq 0.5 \text{ s}$$

- 1.8 The current that enters an element is shown in Fig. P1.8. Find the charge that enters the element in the time interval  $0 < t < 20$  s.

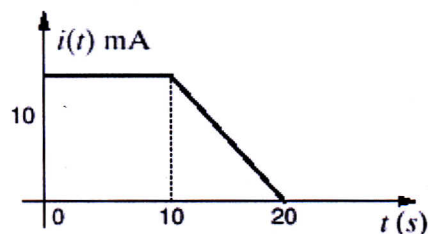


Figure P1.8

**SOLUTION:**

$$i(t) = m_1 t + b$$

$$m_1 = \frac{10 - 0}{10 - 20} = -1$$

$$i(t) = -t + b$$

$$10 = -10 + b$$

$$b = 20$$

$$i(t) = -t + 20 \text{ mA}$$

$$q(t) = \int_0^{20} i(t) dt$$

$$q(t) = \int_0^{10} 10 \times 10^{-3} dt + \int_{10}^{20} \frac{20-t}{1000} dt$$

$$q(t) = 10 \times 10^{-3} t \Big|_0^{10} + \frac{1}{1000} \left[ 20t - \frac{t^2}{2} \right]_{10}^{20}$$

$$q(t) = 0.1 + \frac{1}{1000} \left[ 20(20) - \frac{(20)^2}{2} - 20(10) + \frac{(10)^2}{2} \right]$$

$$q(t) = 0.1 + \frac{1}{1000} [200 - 200 + 50]$$

$$q(t) = 0.15 \text{ C}$$

- 1.9 The charge entering the positive terminal of an element is  $q(t) = -30e^{-4t}$  mC. If the voltage across the element is  $120e^{-2t}$  V, determine the energy delivered to the element in the time interval  $0 < t < 50$  ms.

**SOLUTION:**

$$q(t) = 30e^{-4t} \text{ mC}$$

$$v(t) = 120e^{-2t} \text{ V}$$

$$W = \int_{t_1}^{t_2} P dt = \int_{t_1}^{t_2} vi dt$$

$$i(t) = \frac{dq(t)}{dt} = -4(-30)e^{-4t} \text{ mA}$$

$$i(t) = 120e^{-4t} \text{ mA}$$

$$W = \int_{t_1}^{t_2} (120e^{-2t})(120e^{-4t} \text{ m}) dt$$

$$W = 14.4 \int_0^{50\text{m}} e^{-6t} dt$$

$$W = 14.4 \left[ \frac{e^{-6t}}{-6} \right]^{50\text{m}}$$

$$W = 14.4 \left[ \frac{e^{-6(50\text{m})}}{-6} + \frac{e^{-6(0)}}{6} \right]$$

$$W = 622.04 \text{ mJ}$$

- 1.10 The charge entering the positive terminal of an element is given by the expression  $q(t) = -12e^{-2t}$  mC. The power delivered to the element is  $p(t) = 2.4e^{-3t}$  W. Compute the current in the element, the voltage across the element, and the energy delivered to the element in the time interval  $0 < t < 100$  ms.

**SOLUTION:**

$$q(t) = -12 e^{-2t} \text{ mC}$$

$$p(t) = 2.4 e^{-3t} \text{ W}$$

$$i(t) = \frac{dq(t)}{dt}$$

$$i(t) = 2(-12)e^{-2t} \text{ m}$$

$$i(t) = 24 e^{-2t} \text{ mA}$$

$$W = \int_{t_1}^{t_2} p(t) dt = \int_0^{100\text{m}} 2.4 e^{-3t} dt$$

$$W = \left[ \frac{2.4}{-3} e^{-3t} \right]_0^{100\text{m}}$$

$$W = \frac{2.4}{-3} \left[ e^{-3(100\text{m})} - e^{-3(0)} \right]$$

$$W = 207.35 \text{ mJ}$$

$$V(t) = \frac{P(t)}{i(t)}$$

$$V(t) = \frac{2.4 e^{-3t}}{24 e^{-2t} \text{ m}}$$

$$V(t) = 100 e^{-t} \text{ V}$$



- 1.11 The voltage across an element is  $12e^{-2t}$  V. The current entering the positive terminal of the element is  $2e^{-2t}$  A. Find the energy absorbed by the element in 1.5 s starting from  $t = 0$ .

**SOLUTION:**

$$V(t) = 12e^{-2t} \text{ V}$$

$$i(t) = 2e^{-2t} \text{ A}$$

$$W = ? , 0 - 1.5 \text{ s}$$

$$W = \int_{t_1}^{t_2} Vi \, dt$$

$$W = \int_0^{1.5} (12e^{-2t})(2e^{-2t}) \, dt$$

$$W = \int_0^{1.5} 24e^{-4t} \, dt$$

$$W = \frac{24e^{-4t}}{-4} \Big|_0^{1.5}$$

$$W = -6e^{-4t} \Big|_0^{1.5} = -6e^{-4(1.5)} + 6e^{-4(0)}$$

$$W = 5.99 \text{ J}$$

- 1.12 The waveform for the current flowing into a circuit element is shown in Fig. P1.12. Calculate the amount of charge which enters the element between (a) 0 and 3 seconds, (b) 1 and 5 seconds, and (c) 0 and 6 seconds.

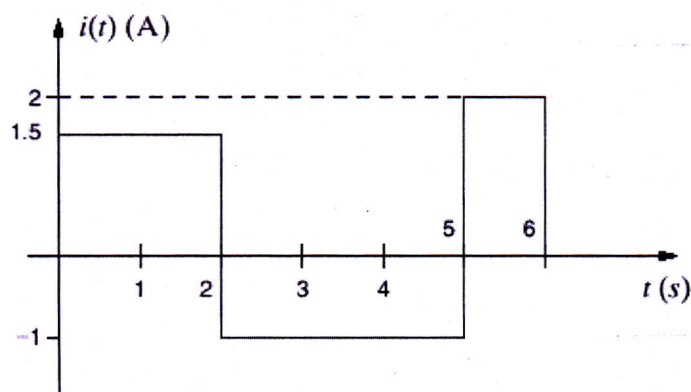


Figure P1.12

**SOLUTION:**

$$a) \quad q(t) = \int_{-\infty}^t i(x) dx$$

$$q(t) = \int_0^3 i(x) dx$$

$$q(t) = \int_0^2 1.5 dx + \int_2^3 -1 dx$$

$$q(t) = 1.5x \Big|_0^2 + -x \Big|_2^3$$

$$q(t) = 1.5(2) + [(-3) - (-2)]$$

$$q(t) = 3 - 3 + 2 = 2C$$

$$b) \quad q(t) = \int_1^5 i(x) dx$$

$$q(t) = \int_1^2 1.5 dx + \int_2^5 -1 dx$$

$$q(t) = 1.5x \Big|_1^2 + (-x) \Big|_2^5$$

$$q(t) = [1.5(2) - 1.5(1)] + [-5 - (-2)]$$

$$q(t) = 1.5 - 5 + 2 = 1.5C$$

$$c) \quad q(t) = \int_0^6 i(x) dx$$

$$q(t) = \int_0^2 1.5 dx + \int_2^5 -1 dx + \int_5^6 2 dx$$

$$q(t) = 1.5x \Big|_0^2 + (-x) \Big|_2^5 + 2x \Big|_5^6$$

$$q(t) = 1.5(2) + [-5 - (-2)] + [2(6) - 2(5)]$$

$$q(t) = 3 - 3 + 12 - 10$$

$$q(t) = 2C$$

- 1.13 The current flowing into a box is given by the waveform shown in Fig. P1.13. Calculate the following quantities: (a) the amount of charge which has entered the box at  $t = 1$  s,  $t = 3$  s, and  $t = 4.5$  s, (b) the power absorbed by the box at  $t = 1$  s, 2.5 s, 4.5 s, and 5.5 s and (c) the amount of energy absorbed by the box between 0 and 6 s.

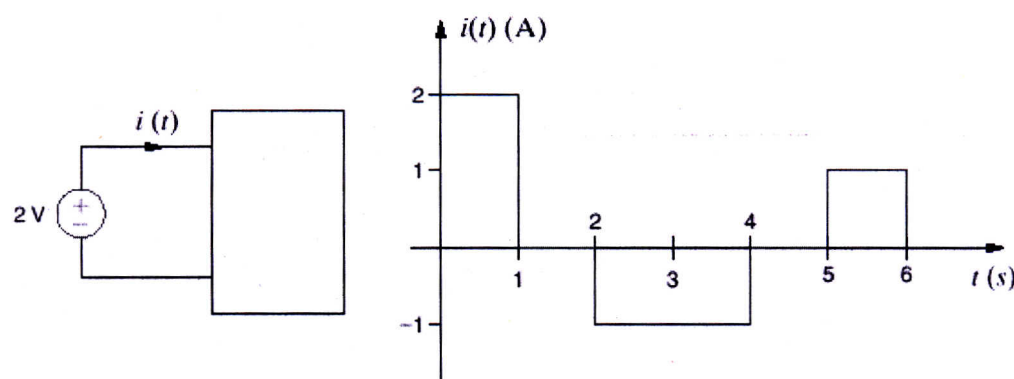


Figure P1.13.

**SOLUTION:**

$$a) \quad q(t) = \int_{-\infty}^t i(x) dx$$

$$q(t) = \int_0^t 2 dx = 2t \Big|_0^t = 2t$$

$$q(1) = 2C$$

$$q(t) = \int_0^1 2 dx + \int_2^t -1 dx$$

$$q(t) = 2 - x \Big|_2^t$$

$$q(t) = 2 + [-t + 2]$$

$$q(t) = -t + 4$$

$$q(3) = 1C$$

By counting the areas:

$$q(4.5) = 2(1) + 2(-1)$$

$$q(4.5) = 0C$$

b) At  $t = 1s$

$$v(t) \cdot i(t) = 2 \cdot 2 = 4W$$

At  $t = 2.5s$

$$v(t) \cdot i(t) = 2 \cdot (-1) = -2W \text{ (power is given out by the box)}$$

At  $t = 4.5s$

$$i(t) = 0 \Rightarrow \text{Power} = 0W$$

At  $t = 5.5s$

$$v(t) \cdot i(t) = 2 \cdot 1 = 2W$$

c)  $W = \int_1 v(t) i(t) dt$

$$W = \int_0^1 2(2) dt + \int_2^4 2(-1) dt + \int_5^6 2(1) dt$$

$$W = 4t \Big|_0^1 - 2t \Big|_2^4 + 2t \Big|_5^6$$

$$W = 4 - 2[2] + 2[6 - 5]$$

$$W = 4 - 4 + 2 = 2J$$

- 1.14 The charge flowing into the box is shown in the graph in Fig. P1.14. Sketch the power absorbed by the box.

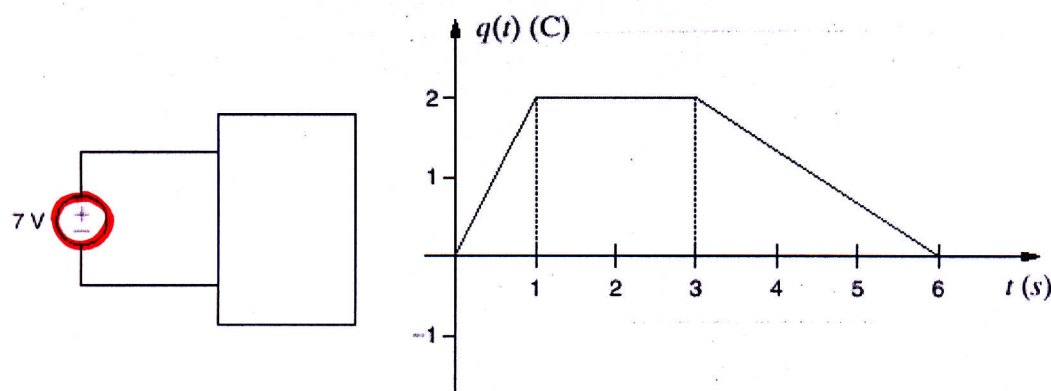


Figure P1.14

**SOLUTION:**

$$p(t) = v(t) i(t)$$

$$i(t) = \frac{dq(t)}{dt}$$

$$q(t) = m_1 t + b_1$$

$$m_1 = \frac{2-0}{1-0} = 2$$

$$q(t) = 2(t) + b_1$$

$$b_1 = 0$$

$$q(t) = 2t, \quad 0 \leq t \leq 1$$

$$q(t) = 2, \quad 1 \leq t \leq 3$$

$$q(t) = m_2 t + b_2$$

$$m_2 = \frac{0-2}{6-3} = -2/3$$

$$q(t) = -2/3 t + b_2$$


$$0 = -2/3(6) + b_2$$

$$b_2 = 4$$

$$q(t) = -2/3 t + 4, \quad 3 \leq t \leq 6$$

$$i(t) = \begin{cases} 2A & 0 \leq t \leq 1 \\ 0A & 1 \leq t \leq 3 \\ -2/3A & 3 \leq t \leq 6 \end{cases}$$
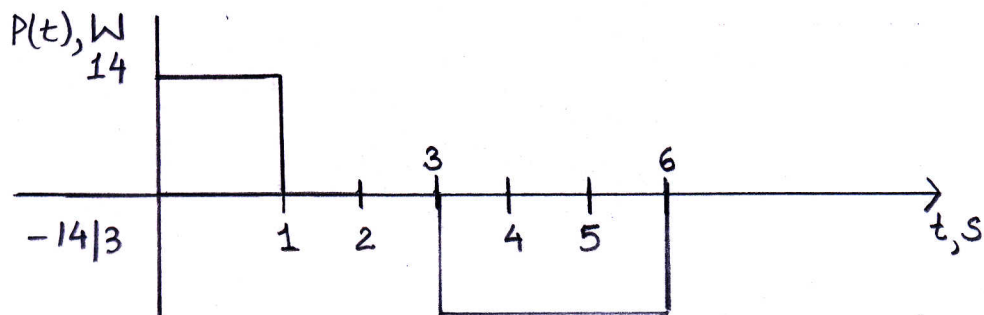
$$p(t) = \begin{cases} 14W & , 0 \leq t \leq 1s \\ 0W & , 1 \leq t \leq 3s \\ -\frac{14}{3}W & , 3s \leq t \leq 6s \end{cases}$$



- 1.15 The charge that enters a BOX is shown in Fig. P1.15. Calculate and sketch the current flowing into and the power absorbed by the BOX between 0 and 9 milliseconds. Also calculate the energy absorbed by the BOX between 0 and 9 milliseconds.

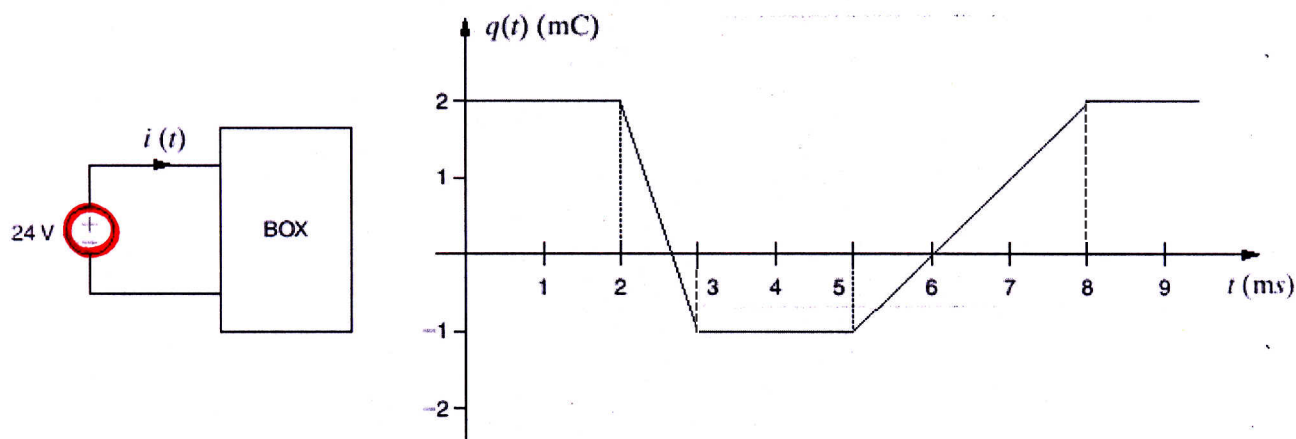


Figure P1.15

**SOLUTION:**

$$i(t) = \frac{dq(t)}{dt}$$

$$q(t) = 2, \quad 0 \leq t \leq 2 \text{ ms}$$

$$m = \frac{-1 - 2}{3 - 2} = \frac{-3}{1} = -3$$

$$q(t) = m(t) + b$$

$$q(t) = -3t + b$$

$$2 = -3(2) + b$$

$$b = 8$$

$$q(t) = -3t + 8, \quad 2 \text{ ms} \leq t \leq 3 \text{ ms}$$

$$q(t) = -1, \quad 3 \text{ ms} \leq t \leq 5 \text{ ms}$$

$$q(t) = mt + b$$

$$m = \frac{2 + 1}{8 - 5} = 1$$

$$q(t) = t + b$$


$$2 = 8 + b$$

$$b = -6$$



$$q(t) = t - 6, \quad 5\text{ms} \leq t \leq 8\text{ms}$$
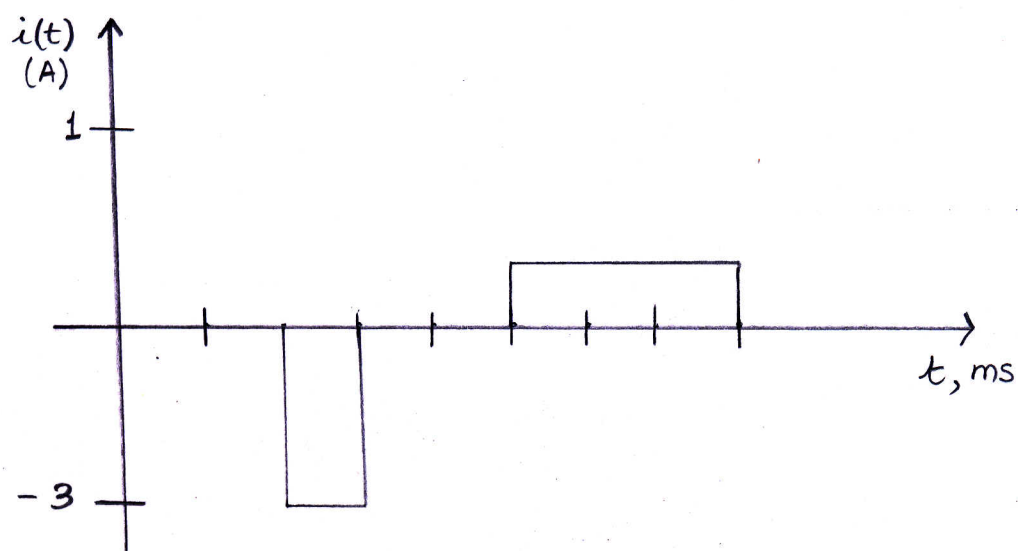
$$q(t) = 2, \quad 8\text{ms} \leq t \leq 9\text{ms}$$



$$i(t) = \begin{cases} 0 & , \quad 0 \leq t \leq 2\text{ms} \\ -3 & , \quad 2\text{ms} \leq t \leq 3\text{ms} \\ 0 & , \quad 3\text{ms} \leq t \leq 5\text{ms} \\ 1 & , \quad 5\text{ms} \leq t \leq 8\text{ms} \end{cases}$$

$$p(t) = v(t) i(t)$$

$$p(t) = \begin{cases} 0 \text{ W} & , \quad 0 \leq t \leq 2\text{ms} \\ -72 \text{ W} & , \quad 2\text{ms} \leq t \leq 3\text{ms} \\ 0 \text{ W} & , \quad 3\text{ms} \leq t \leq 5\text{ms} \\ 24 \text{ W} & , \quad 5\text{ms} \leq t \leq 8\text{ms} \end{cases}$$

$$W(t) = \int_0^t p(t) dt$$

$$= 0 + (-72) \times 1 + 0 + 24 \times 3 = 0 \text{ J}$$

**1.16** Determine the amount of power absorbed or supplied by the element in Fig. P1.16 if

- (a)  $V_1 = 5 \text{ V}$  and  $I = 6 \text{ A}$ .
- (b)  $V_1 = 5 \text{ V}$  and  $I = -7 \text{ A}$ .
- (c)  $V_1 = -14 \text{ V}$  and  $I = 6 \text{ A}$ .
- (d)  $V_1 = -14 \text{ V}$  and  $I = -7 \text{ A}$ .

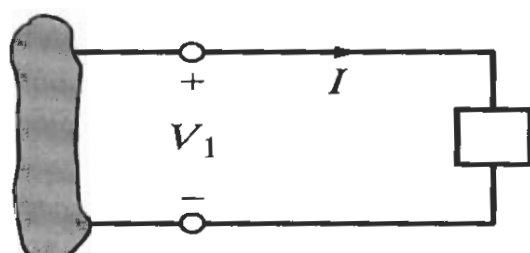


Figure P1.16

**Solution:**

1.16 a)  $V_1 = 5 \text{ V}$ ,  $I = 6 \text{ A}$

For passive sign convention,

$P = V_1 I$  is power absorbed.

$$P = V_1 I = 5(6) = 30 \text{ W absorbed}$$

$$P = 30 \text{ W absorbed}$$

b)  $V_1 = 5 \text{ V}$ ,  $I = -7 \text{ A}$

$$P = 5(-7) = -35 \text{ W}$$

$$P = 35 \text{ W supplied}$$

c)  $V_1 = -14 \text{ V}$ ,  $I = 6 \text{ A}$


$$P = -84 \text{ W}$$

$$P = 84 \text{ W supplied}$$

d)  $V_1 = -14 \text{ V}$ ,  $I = -7 \text{ A}$

$$P = 98 \text{ W}$$

$$P = 98 \text{ W absorbed}$$

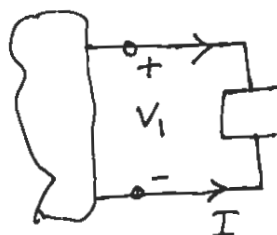

1.17 Determine the missing quantity in the circuits in Fig. P 1.17.

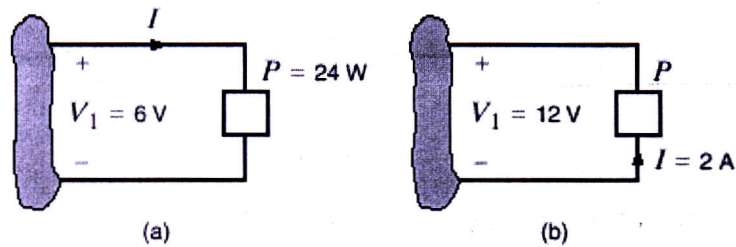


Figure P 1.17

**SOLUTION:**

$$a) I = \frac{P}{V} = \frac{24}{6} = 4\text{ A}$$

$$b) P = VI = (-12)(2) = -24\text{ W}$$

$P = 24\text{ W}$  supplied

1.18 Repeat Problem 1.17 for the circuits in Fig. P1.18.

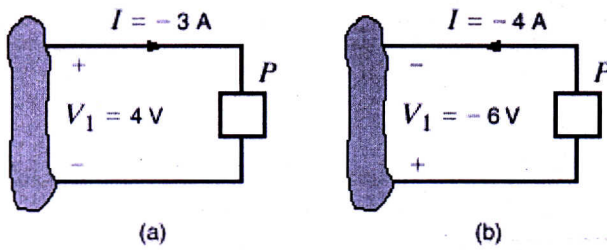


Figure P 1.18

**SOLUTION:**

a)  $P = VI$   
 $P = 4(-3)$   
 $P = -12\text{ W}$   
 $P = 12\text{ W supplied}$

b)  $P = -6(-4)$   
 $P = 24\text{ W absorbed}$

- 1.19 Determine the power supplied to the elements in Fig. P1.19.

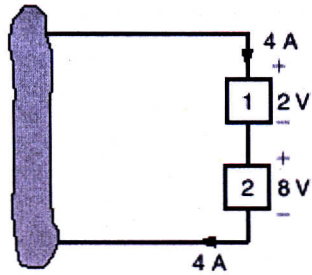


Figure P 1.19

**SOLUTION:**

$$P_1 = V_1 I = 2(4) = 8 \text{ W}$$

$$P_2 = V_2 I = 8(4) = 32 \text{ W}$$

- 1.20 Determine the power supplied to the elements in Fig. P1.20.

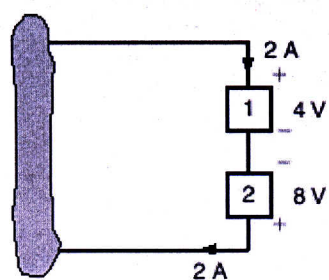


Figure P 1.20

**SOLUTION:**

$$P_1 = V_1 I = 4(2) = 8 \text{ W}$$

$$P_2 = V_2 I = (-8)(2)$$

$$P_2 = -16 \text{ W}$$

- 1.21 (a) In Fig. P1.21 (a),  $P_1 = 42 \text{ W}$ . How much power is element 2 absorbing?
- (b) In Fig. P1.21 (b),  $P_2 = -72 \text{ W}$ . How much power is element 1 absorbing?


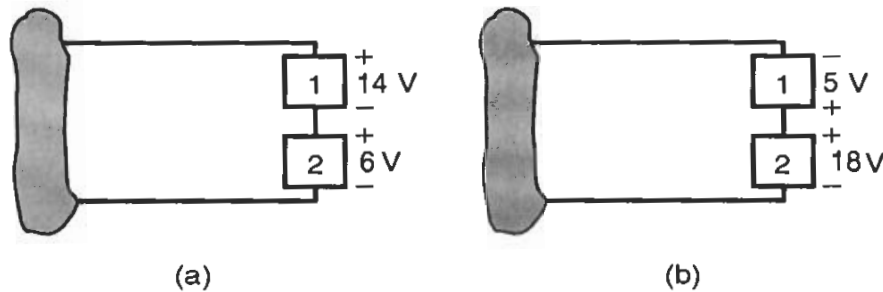


Figure P1.21

Solution:

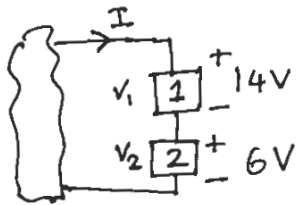1.21 a)  $P_1 = 42 \text{ W}$ . By default, using passive sign convention, since  $P_1$  is positive,  $I$  flows as shown in the circuit diagram.




$$P_1 = V_1 I \quad I = P_1 / V_1 = 42 / 14 = 3 \text{ A}$$

$$I = 3 \text{ A}$$

For element 2,  $V_2$  and  $I$  are defined in passive sign convention:  $P_2 = V_2 I = 6(3) = 18 \text{ W}$

$$P_2 = 18 \text{ W absorbed}$$

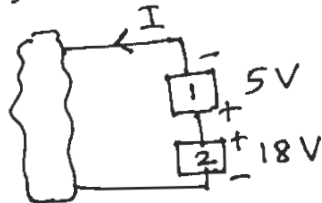b)  $P_2 = -72 \text{ W}$ . Again passive sign convention is the default. Since  $P_2 < 0$ , element 2 supplies power and  $I$  flows as shown.



$$P_2 = -V_2 I = -18 I \quad I = \frac{-72}{-18} = 4 \text{ A}$$

For element 1,  $V_1$  and  $I$  are defined in passive sign convention. Power absorbed is  $P_1 = V_1 I = 5(4) = 20 \text{ W}$

$$P_1 = 20 \text{ W absorbed}$$

- 1.22 Two elements are connected in series, as shown in Fig. P 1.22. Element 1 supplies 24 W of power. Is element 2 absorbing or supplying power, and how much?

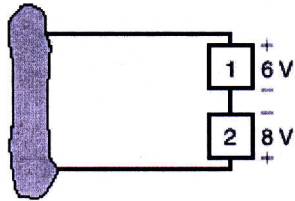


Figure P 1.22

**SOLUTION:**

$$P_1 = 24 \text{ W}$$

$$I = \frac{P_1}{V_1}$$

$$I = \frac{24}{6}$$

$$I = 4 \text{ A}$$

$$P_2 = V_2 I$$

$$P_2 = 8(4)$$

$$P_2 = 32 \text{ W absorbed}$$



- 1.23 Two elements are connected in series, as shown in Fig. P1.23. Element 1 supplies 24 W of power. Is element 2 absorbing or supplying power, and how much?

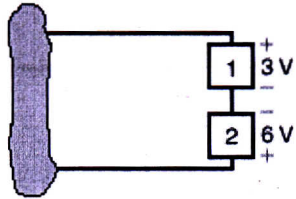


Figure P 1.23

**SOLUTION:**

$$P_1 = 24 \text{ W}$$


$$I = \frac{P_1}{V_1} = \frac{24}{3}$$

$$I = 8 \text{ A}$$

$$P_2 = V_2 I = 6(8)$$

$$P_2 = 48 \text{ absorbed}$$


- 1.24** Two elements are connected in series, as shown in Fig. P 1.24. Element 1 absorbs 45 W of power. Is element 2 absorbing or supplying power, and how much?

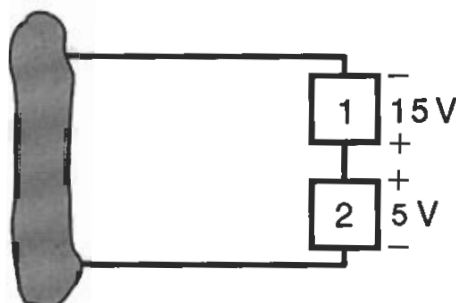

**Figure P1.24**

**Solution:**

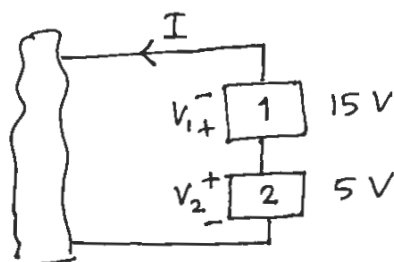- 1.24 Element 1 absorbs 45 W. For absorbing power,  $I$  must flow as shown in the diagram.



$$P_1 = V_1 I, \quad I = \frac{P_1}{V_1} = \frac{45}{15} = 3 \text{ A}$$

$$I = 3 \text{ A}$$

For element 2,  $V_2$  and  $I$  are defined in active sign convention. Power supplied is

$$P_2 = V_2 I = 5(3) = 15 \text{ W}$$

$$P_2 = 15 \text{ W supplied}$$

- 1.25 Choose  $I_s$  such that the power absorbed by element 2 in Fig. P 1.25 is 7 W.

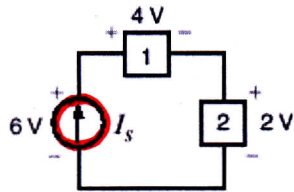


Figure P 1.25

**SOLUTION:**

$$P_2 = 7 \text{ W absorbed}$$

$$P_2 = V_2 I_s$$

$$I_s = \frac{P_2}{V_2} = \frac{7}{2}$$

$$I_s = 3.5 \text{ A}$$

- 1.26 Determine the power that is absorbed or supplied by the circuit elements in Fig. P 1.26.

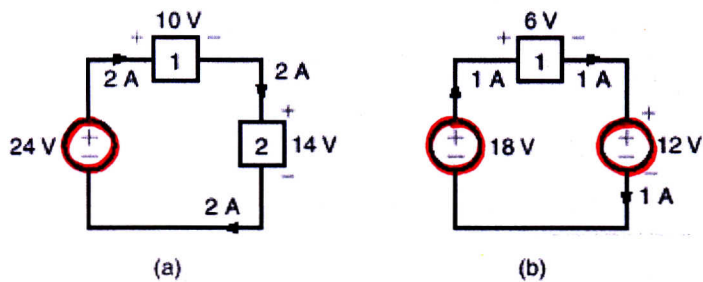


Figure P 1.26

**SOLUTION:**

$$a) P_{24V} = (-24)(2) = -48W$$

$$P_{24W} = 48W \text{ supplied}$$

$$P_1 = 10(2) = 20W \text{ absorbed}$$

$$P_2 = 14(2) = 28W \text{ absorbed}$$

$$b) P_{18V} = (-18)(1) = -18W$$

$$P_{18V} = 18W \text{ supplied}$$

$$P_1 = 6(1) = 6W \text{ absorbed}$$

$$P_{12V} = 12(1) = 12W \text{ absorbed}$$

- 1.27 Find the power that is absorbed or supplied by the circuit elements in Fig. P 1.27.

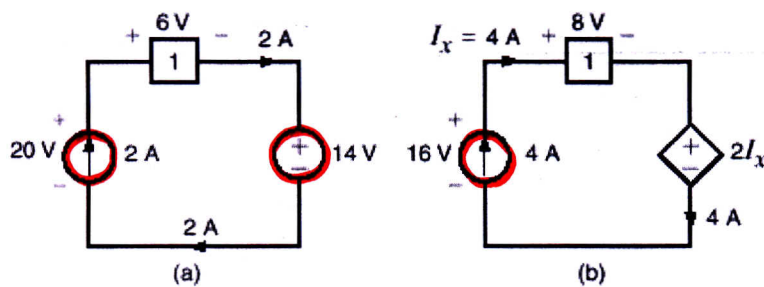


Figure P 1.27

**SOLUTION:**


$$\begin{aligned} a) \quad P_{2A} &= -20(2) \\ P_{2A} &= -40 \text{ W} \\ P_{2A} &= 40 \text{ W supplied} \end{aligned}$$

$$\begin{aligned} P_1 &= 6(2) = 12 \text{ W absorbed} \\ P_{14V} &= 14(2) = 28 \text{ W absorbed} \end{aligned}$$


$$\begin{aligned} b) \quad P_{4A} &= 16(-4) = -64 \text{ W} \\ P_{4A} &= 64 \text{ W supplied} \\ P_1 &= 8(4) = 32 \text{ W absorbed} \\ P_{2I_x} &= (2I_x)(4) = 2(4)(4) \\ P_{2I_x} &= 32 \text{ W absorbed} \end{aligned}$$

**1.28** Determine the power that is absorbed or supplied by the circuit elements in Fig. P1.28.

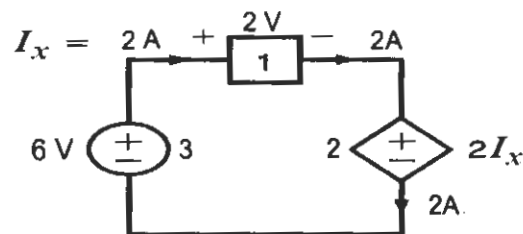- (a) Power of element 1 at figure (a).
- (b) Power of element 2 at figure (a).
- (c) Power of element 3 at figure (a).
- (d) Power of element 1 at figure (b).
- (e) Power of element 2 at figure (b).
- (f) Power of element 3 at figure (b).
- (g) Power of element 4 at figure (b).



(a)

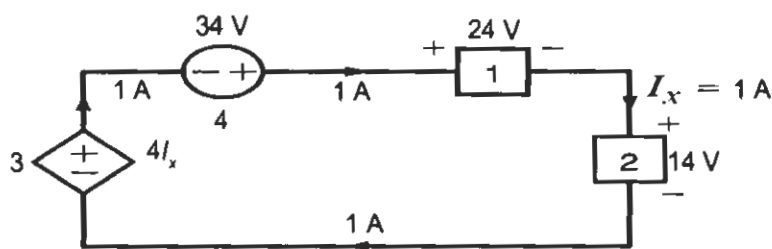

(b)

**Figure P1.28**

**Solution:** See next page.

1.28 a) Voltage and current for element 1 in Fig. (a) are defined in the passive sign convention.

Power supplied by element 1 in Fig. (a) is

$$P_1 = -V_1 I_x = -2(2) = -4 \text{ W}$$

$$P_1 = -4 \text{ W supplied.}$$

b) Voltage and current for element 2 in Fig. (a) are defined in the passive sign convention.

Power supplied by element 2 in Fig. (a) is

$$P_2 = -(2I_x) = -4(2) = -8 \text{ W}$$

$$P_2 = -8 \text{ W supplied}$$

c) For element 3 in Fig. (a)  $V$  and  $I$  are defined in active sign convention.

Power supplied by element 3 in Fig. (a) is

$$P_3 = 6 I_x = 6(2) = 12 \text{ W}$$

$$P_3 = 12 \text{ W supplied}$$

d)  $V$  and  $I$  are defined in the passive sign convention for element 1 in Fig. (b).

Power supplied by element 1 in Fig. (b) is

$$P_1 = -V_1 I_x = -24(1) = -24 \text{ W}$$

$$P_1 = -24 \text{ W supplied}$$

e)  $V$  and  $I$  are defined in the passive sign convention for element 2 in Fig. (b).

Power supplied by element 2 in Fig. (b) is

$$P_2 = -V_2 I_x = -14(1) = -14\text{ W}$$

$$P_2 = -14\text{ W supplied}$$

f)  $V$  and  $I$  are defined in the active sign convention for element 3 in Fig. (b).

Power supplied by element 3 in Fig. (b) is

$$P_3 = (4 I_x) I_x = 4\text{ W}$$

$$P_3 = 4\text{ W supplied}$$

g)  $V$  and  $I$  are defined in the active sign convention for element 4 in Fig. (b).

Power supplied by element 4 in Fig. (b) is

$$P_4 = 34(I_x) = 34\text{ W supplied}$$

$$P_4 = 34\text{ W supplied}$$



- 1.29 Compute the power that is absorbed or supplied by the elements in the network in Fig. P 1.29.

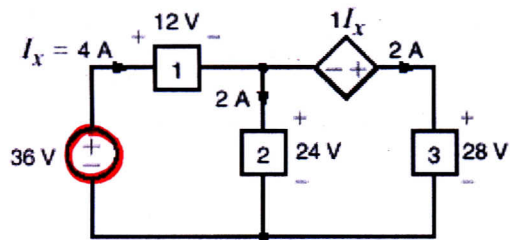


Figure P 1.29

**SOLUTION:**

$$P_{36V} = -36(4) = -144 \text{ W}$$

$$P_{36V} = 144 \text{ W supplied}$$

$$P_1 = 12(4) = 48 \text{ W absorbed}$$

$$P_2 = 24(2) = 48 \text{ W absorbed}$$

$$P_{1I_x} = (-I_x)(2) = -4(2) = -8 \text{ W}$$

$$P_{1I_x} = 8 \text{ W supplied}$$

$$P_3 = 28(2) = 56 \text{ W absorbed}$$

- 1.30 Calculate the power absorbed by each element in the circuit in Fig. P1.30.

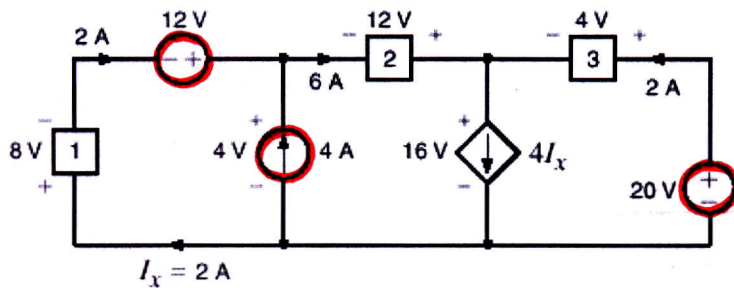


Figure P 1.30

**SOLUTION:**

$$P_{12V} = -12(2) = -24 \text{ W}$$

$$P_{12V} = 24 \text{ W supplied}$$

$$P_{4A} = 4(-4) = -16 \text{ W}$$

$$P_{4A} = 16 \text{ W supplied}$$

$$P_2 = -12(6) = -72 \text{ W}$$

$$P_2 = 72 \text{ W supplied}$$

$$P_3 = 4(2) = 8 \text{ W absorbed}$$

$$P_{20V} = -20(2) = -40 \text{ W}$$

$$P_{20V} = 40 \text{ W supplied}$$

$$P_1 = 8(2) = 16 \text{ W absorbed}$$

$$\text{KCL: } 6 + 2 = 4I_x$$

$$I_x = 2 \text{ A}$$

$$P_{4I_x} = 4I_x (16)$$

$$P_{4I_x} = 4(2)(16)$$

$$P_{4I_x} = 128 \text{ W absorbed}$$

1.31 Find  $V_x$  in the network in Fig. P 1.31 using Tellegen's theorem.

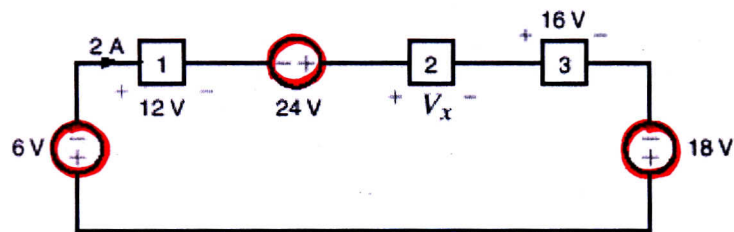


Figure P 1.31

### SOLUTION:

$$P_1 = 12(2) = 24\text{ W absorbed}$$

$$P_2 = V_x(2) = 2V_x \text{ absorbed}$$

$$P_3 = 16(2) = 32\text{ W absorbed}$$

$$P_{6V} = 6(2) = 12\text{ W absorbed}$$

$$P_{24V} = 24(-2) = -48\text{ W}$$

$$P_{24V} = 48\text{ W supplied}$$

Power supplied = Power absorbed

$$P_{24V} + P_{18V} = P_1 + P_2 + P_3$$

$$48 + 36 = 24 + 2V_x + 32$$

$$V_x = 8\text{ V}$$

1.32 Find  $V_x$  in the network in Fig. P1.32.

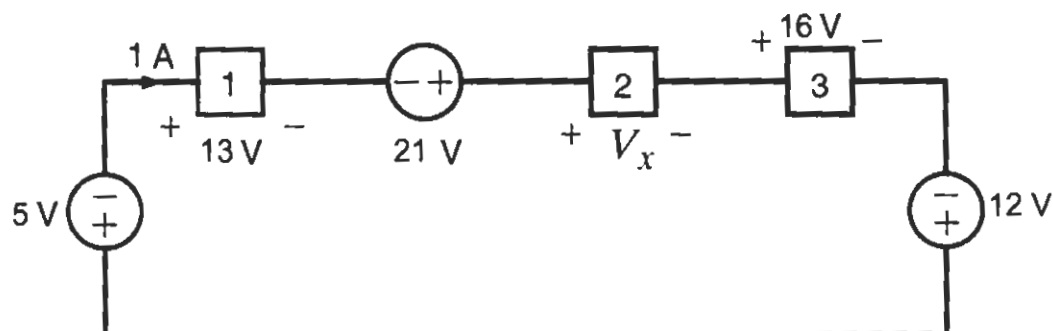


Figure P1.32

**Solution:**

1.32 Passive sign convention: Elements 1, 2, 3 and the 5V source.

Active sign convention: 21V and 12V source.

Power balance:  $P_{21V} + P_{12V} = P_1 + P_2 + P_3 + P_{5V}$

$$21I + 12I = 13I + V_x I + 16I + 5I$$

$$33 = 34 + V_x$$

$$V_x = -1V$$

1.33 Find  $V_x$  in the network in Fig. P1.33 using Tellegen's theorem.

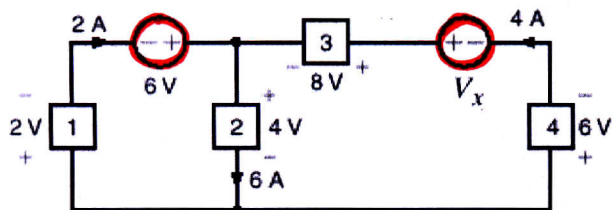


Figure P 1.33

**SOLUTION:**

$$\text{Power supplied} = \text{Power absorbed}$$

$$P_{6V} + P_{V_x} = P_1 + P_2 + P_3 + P_4$$

$$P_1 = 2(2) = 4\text{W absorbed}$$

$$P_2 = 4(6) = 24\text{W absorbed}$$

$$P_3 = 8(4) = 32\text{W absorbed}$$

$$P_4 = 6(4) = 24\text{W absorbed}$$

$$P_{6V} = 6(-2) = -12\text{W}$$

$$P_{6V} = 12\text{W supplied}$$

$$P_{6V} + P_{V_x} = P_1 + P_2 + P_3 + P_4$$

$$12 + P_{V_x} = 4 + 24 + 32 + 24$$

$$P_{V_x} = -4V_x$$

$$P_{V_x} = 4V_x \text{ supplied}$$

$$12 + 4V_x = 4 + 24 + 32 + 24$$

$$V_x = 18\text{V}$$

1.34 Find  $I_x$  in the circuit in Fig. P1.34.


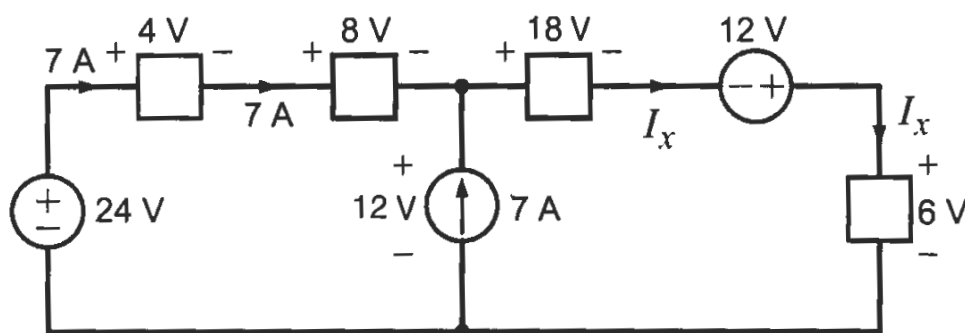


Figure P1.34

Solution:

1.34

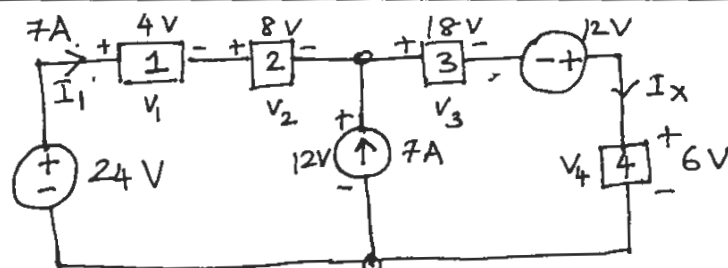

Passive sign convention: elements 1, 2, 3, 4

$$P_1 = V_1 I_1 = 4(7) = 28 \text{ W absorbed}$$

$$P_2 = V_2 I_1 = 8(7) = 56 \text{ W absorbed}$$

$$P_3 = V_3 I_x = 18 I_x \text{ absorbed}$$

$$P_4 = V_4 I_x = 6 I_x \text{ absorbed}$$

$$P_{24V} = 24 I_1 = 168 \text{ W supplied}$$

$$P_{7A} = 12(7) = 84 \text{ W supplied}$$

$$P_{12V} = 12 I_x \text{ supplied}$$

Power supplied = Power absorbed

$$P_{24V} + P_{7A} + P_{12V} = P_1 + P_2 + P_3 + P_4$$

$$12 I_x = 168$$

$$I_x = 14 \text{ A}$$

- 1.35 Is the source  $V_s$  in the network in Fig. P1.35 absorbing or supplying power, and how much?

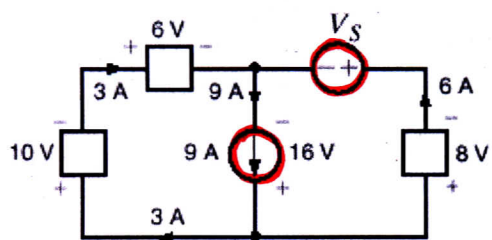


Figure P 1.35

**SOLUTION:**

$$P_{10V} = 10(3) = 30W \text{ absorbed}$$

$$P_{6V} = 6(3) = 18W \text{ absorbed}$$

$$P_{9A} = 16(-9) = -144W$$

$$P_{9A} = 144W \text{ supplied}$$

$$P_{V_s} = V_s(6) = 6V_s \text{ absorbed}$$

$$P_{8V} = 8(6) = 48W \text{ absorbed}$$

Power supplied = Power absorbed

$$P_{9A} = P_{10V} + P_{6V} + P_{V_s} + P_{8V}$$

$$144 = 30 + 18 + 6V_s + 48$$

$$144 = 96 + 6V_s$$

$$24 = 16 + V_s$$

$$V_s = 8V$$

$$P_{V_s} = 8(6) = 48W \text{ absorbed}$$

- 1.36 Find  $V_x$  in the network in Fig. P1.36 using Tellegen's theorem.

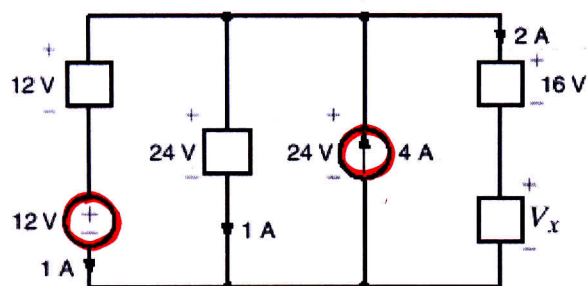


Figure P1.36

**SOLUTION:**

$$P_1 = 12(1) = 12\text{ W absorbed}$$

$$P_{12V} = 12(1) = 12\text{ W absorbed}$$

$$P_2 = 24(1) = 24\text{ W absorbed}$$

$$P_{4A} = 24(-4) = -96\text{ W}$$

$$P_{4A} = 96\text{ W supplied}$$

$$P_3 = 16(2) = 32\text{ W absorbed}$$

$$P_4 = V_x(2) = 2V_x$$

Power supplied = Power absorbed

$$P_{4A} = P_1 + P_{12V} + P_2 + P_3 + P_4$$

$$96 = 12 + 12 + 24 + 32 + 2V_x$$

$$V_x = 8\text{ V}$$



- 1.37 Find  $I_o$  in the network in Fig. P1.37 using Tellegen's theorem.

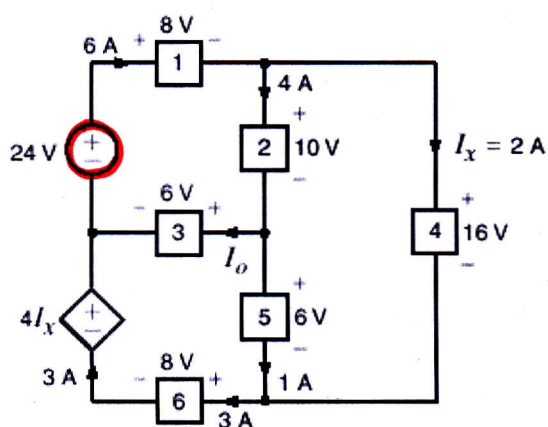


Figure P 1.37

### SOLUTION:

$$P_{24V} = 24(-6) = -144 \text{ W}$$

$$P_{24V} = 144 \text{ W supplied}$$

$$P_1 = 8(6) = 48 \text{ W absorbed}$$

$$P_2 = 10(4) = 40 \text{ W absorbed}$$

$$P_3 = 6I_o \text{ ABSORBED}$$

$$P_4 = 16(2) = 32 \text{ W absorbed}$$

$$P_5 = 6(1) = 6 \text{ W absorbed}$$

$$P_6 = 8(3) = 24 \text{ W absorbed}$$

$$P_{4I_x} = 4I_x(-3) = -12(2) = -24 \text{ W}$$

$$P_{4I_x} = 24 \text{ W supplied}$$

$$\text{Power supplied} = \text{Power absorbed}$$

$$P_{24V} + P_{4I_x} = P_1 + P_2 + P_3 + P_4 + P_5 + P_6$$

$$144 + 24 = 48 + 40 + 6I_o + 32 + 6 + 24$$

$$I_o = 3 \text{ A}$$

1.38 Find  $V_x$  in the network in Fig. P1.38.


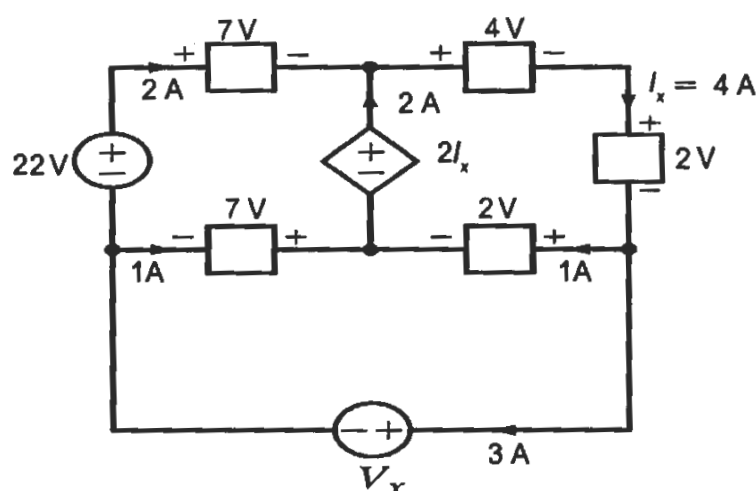


Figure P 1.38

Solution: 1-38

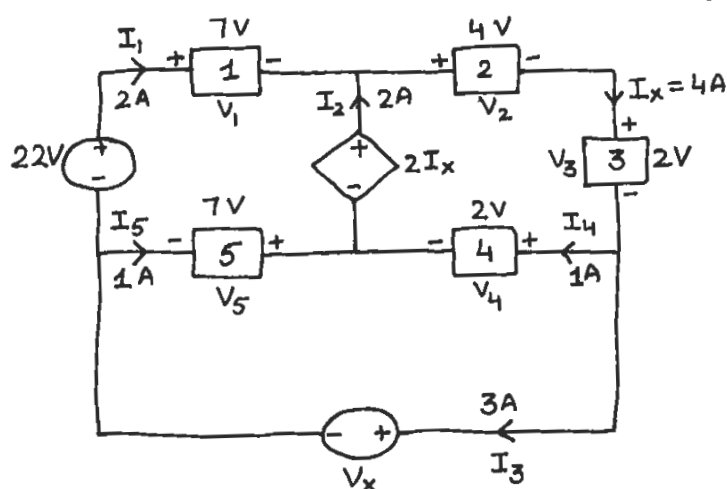Passive sign convention elements 1, 2, 3, 4,  $V_x$



$$\begin{aligned}
 P_1 &= V_1 I_1 = 7(2) = 14 \text{ W absorbed} \\
 P_2 &= V_2 I_2 = 4(4) = 16 \text{ W absorbed} \\
 P_3 &= V_3 I_3 = 2(4) = 8 \text{ W absorbed} \\
 P_4 &= V_4 I_4 = 2(1) = 2 \text{ W absorbed} \\
 P_{V_x} &= V_x I_3 = 3V_x \text{ absorbed} \\
 P_{22V} &= 22 I_1 = 22(2) \\
 &= 44 \text{ W supplied} \\
 P_5 &= V_5 I_5 = 7 \text{ W supplied} \\
 P_{2I_x} &= 2 I_x I_2 = 16 \text{ W supplied}
 \end{aligned}$$

$$\begin{aligned}
 P_{\text{supplied}} &= P_{\text{absorbed}} \\
 P_{22V} + P_5 + P_{2I_x} &= P_1 + P_2 + P_3 + P_4 + P_{V_x} \\
 44 + 7 + 16 &= 14 + 16 + 8 + 2 + 3V_x \\
 27 &= 3V_x \Rightarrow \boxed{V_x = 9 \text{ V}}
 \end{aligned}$$

2.1 Determine the current and power dissipated in the resistors in Fig. P2.1.

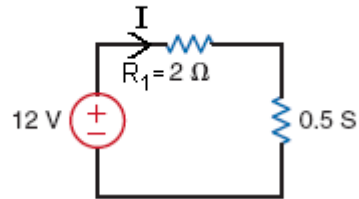


Figure P2.1

**SOLUTION:**

$$R_2 = \frac{1}{0.5} = 2\ \Omega$$

$$I = \frac{12}{2+2}$$

$$I = 3\text{A}$$

$$P_{R_1} = I^2 R_1 = (3)^2 (2)$$

$$P_{R_1} = 18\text{W}$$

$$P_{R_2} = I^2 R_2 = (3)^2 (2)$$

$$P_{R_2} = 18\text{W}$$

2.2 Determine the voltage across the resistor in Fig. P2.2 and the power dissipated.

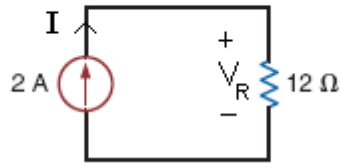


Figure P2.2

**SOLUTION:**

$$V_R = I R$$

$$V_R = 2(12) = 24 \text{ V}$$

$$P_R = I^2 R = 2^2(12)$$

$$P_R = 48 \text{ W}$$

2.3 Given the circuit in Fig. P2.3, find the voltage across each resistor and the power dissipated in each.

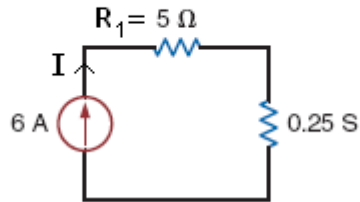


Figure P2.3

**SOLUTION:**

$$R_2 = \frac{1}{0.25} = 4 \Omega$$

$$V_{R_1} = IR_1$$

$$V_{R_1} = 6(5) = 30 \text{ V}$$

$$V_{R_2} = IR_2 = 6(4) = 24 \text{ V}$$

$$P_{R_1} = \frac{V_{R_1}^2}{R_1} = \frac{(30)^2}{5}$$

$$P_{R_1} = 180 \text{ W}$$

$$P_{R_2} = \frac{V_{R_2}^2}{R_2} = \frac{(24)^2}{4}$$

$$P_{R_2} = 144 \text{ W}$$

2.4 In the network in Fig. P2.4, the power absorbed by  $R_x$  is 20 mW. Find  $R_x$ .

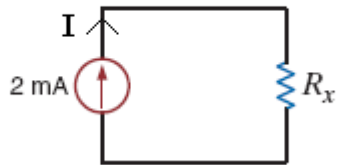


Figure P2.4

**SOLUTION:**


$$P_{Rx} = 20 \text{ mW}$$

$$P_{Rx} = I^2 R_x$$

$$R_x = \frac{P_{Rx}}{I^2} = \frac{20 \text{ m}}{(2 \text{ m})^2} = \frac{20 \times 10^{-3}}{(2 \times 10^{-3})^2} = \frac{20 \times 10^{-3}}{4 \times 10^{-6}}$$

$$R_x = 5 \text{ k}\Omega$$

**2.5** In the network in the accompanying Figure, the power absorbed by  $G_x$  is 60 mW, Find  $G_x$ .

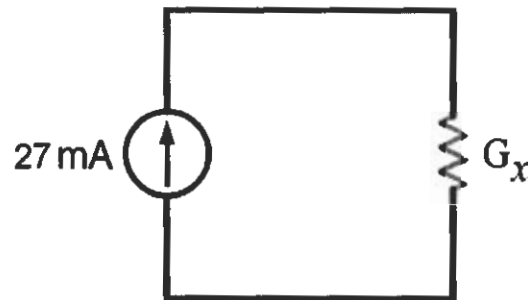

**Figure P2.5**

**Solution:** 2.5

$$\begin{aligned} P_G &= 60 \text{ mW} \quad ; \quad I = 27 \times 10^{-3} \text{ A} \\ P_G &= R_x I^2 \\ 60 \times 10^{-3} &= \frac{1}{G_x} I^2 \quad \left( \because R_x = \frac{1}{G_x} \right) \\ \Rightarrow G_x &= \frac{(27 \times 10^{-3})^2}{60 \times 10^{-3}} \\ \boxed{G_x} &= 12.15 \text{ mS} \end{aligned}$$

- 2.6 A model for a standard two D-cell flashlight is shown in Fig. P2.6. Find the power dissipated in the lamp.

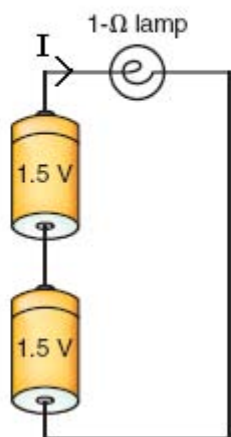


Figure P2.6

**SOLUTION:**

$$I = \frac{V}{R}$$

$$I = \frac{1.5 + 1.5}{1}$$

$$I = 3\text{ A}$$

$$P_{\text{lamp}} = I^2 R = 3^2(1)$$

$$P_{\text{lamp}} = 9\text{ W}$$



- 2.7 An automobile uses two halogen headlights connected as shown in Fig. P2.7. Determine the power supplied by the battery if each headlight draws 3 A of current.

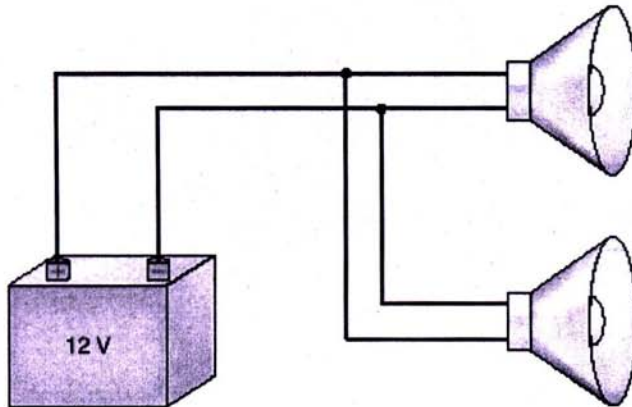


Figure P2.7

**SOLUTION:**

$$I_1 = I_2 = 3\text{ A}$$

$$I = I_1 + I_2 = 6\text{ A}$$

$$P_{12\text{V}} = VI = 12(6)$$

$$P_{12\text{V}} = 72\text{ W}$$

2.8 Many years ago a string of Christmas tree lights was manufactured in the form shown in Fig. P2.8a. Today the lights are manufactured as shown in Fig. P2.8b. Is there a good reason for this change?

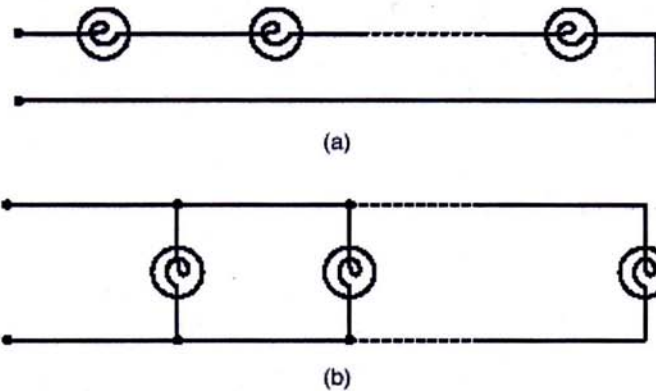


Figure P2.8

**SOLUTION:**

When Christmas tree lights are connected in series as shown in Figure 2.8a, an open circuit bulb failure will cause all bulbs to turn off (no current flows.)

If the bulbs are connected in parallel as shown in Figure 2.8b, an open circuit bulb failure will only cause one bulb to turn off. The other bulbs will still function when connected in parallel.

2.9 Find  $I_1$  in the network in Fig. P2.9.

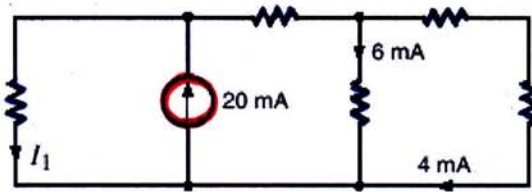


Figure P2.9

**SOLUTION:**

$$\begin{aligned}\text{KCL at node B: } I_2 &= 6\text{ m} + 4\text{ m} \\ I_2 &= 10\text{ m A}\end{aligned}$$

$$\begin{aligned}\text{KCL at node A: } I_1 + I_2 &= 20\text{ m} \\ I_1 &= 20\text{ m} - 10\text{ m} \\ I_1 &= 10\text{ m A}\end{aligned}$$

2.10 Find  $I_1$  in the network in Fig. P2.10

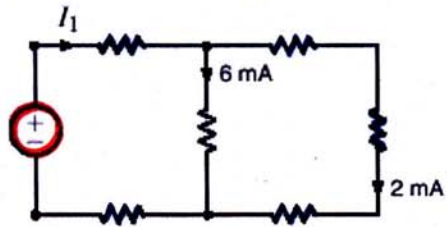


Figure P2.10

**SOLUTION:**

KCL at node A:  $I_1 = 6\text{ m} + 2\text{ m}$   
 $I_1 = 8\text{ mA}$

2.11 Find  $I_1$  and  $I_2$  in the circuit in Fig. P2.11.


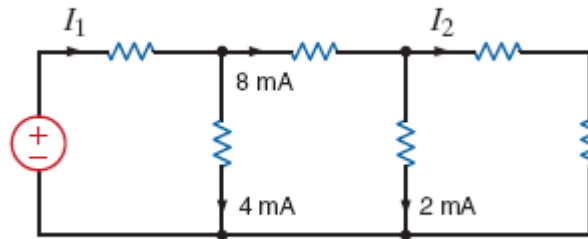


Figure P2.11

**SOLUTION:**

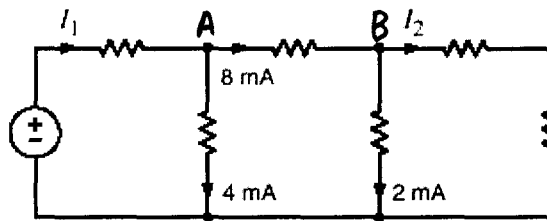

KCL at node A:  $I_1 = 4\text{m} + 8\text{m}$   
 $I_1 = 12\text{mA}$

KCL at node B:  $8\text{m} = 2\text{m} + I_2$   
 $I_2 = 6\text{mA}$

2.12 Find  $I_1$  in the circuit in Fig. P2.12.


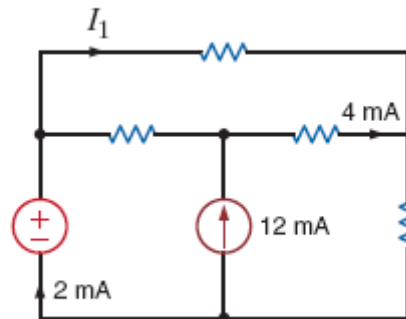


Figure P2.12

**SOLUTION:**

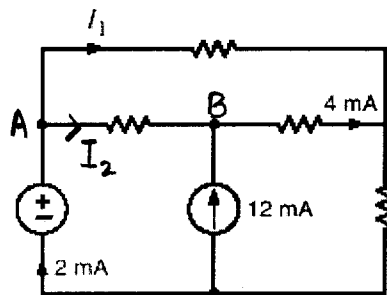

$$\text{KCL at node B: } I_2 + 12\text{m} = 4\text{m}$$

$$I_2 = -8\text{mA}$$

$$\text{KCL at node A: } 2\text{m} = I_1 + I_2$$

$$I_1 = 10\text{mA}$$

2.13 Find  $I_x$  in the circuit in Fig. P2.13.

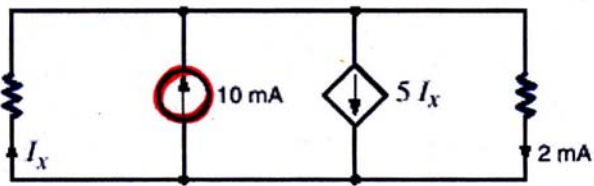


Figure P2.13

**SOLUTION:**

$$\begin{aligned} \text{KCL: } I_x + 10\text{m} &= 5I_x + 2\text{m} \\ 4I_x &= 8\text{m} \\ I_x &= 2\text{mA} \end{aligned}$$

2.14 Determine  $I_L$  in the circuit in Fig. P2.14.

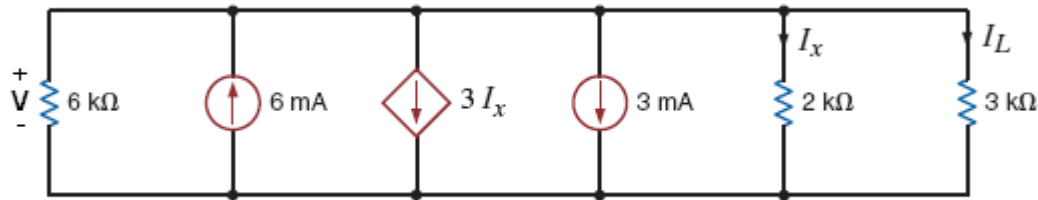


Figure P2.14

**SOLUTION:**

$$6\text{ m} = \frac{V}{6\text{ k}} + 3I_x + 3\text{ m} + I_x + I_L$$

$$\frac{V}{6\text{ k}} + 4I_x + I_L = 3\text{ m}$$

$$I_x = \frac{V}{2\text{ k}} \text{ and } I_L = \frac{V}{3\text{ k}}$$

$$\frac{V}{6\text{ k}} + 4\left(\frac{V}{2\text{ k}}\right) + \frac{V}{3\text{ k}} = 3\text{ m}$$

$$V + 12V + 2V = 18$$

$$15V = 18$$

$$V = \frac{18}{15} \text{ V}$$

$$I_L = \frac{18}{15(3\text{ k})}$$

$$I_L = 0.4\text{ mA}$$



2.15 Find (a)  $I_o$  and (b)  $I_1$  in the circuit in the Figure.


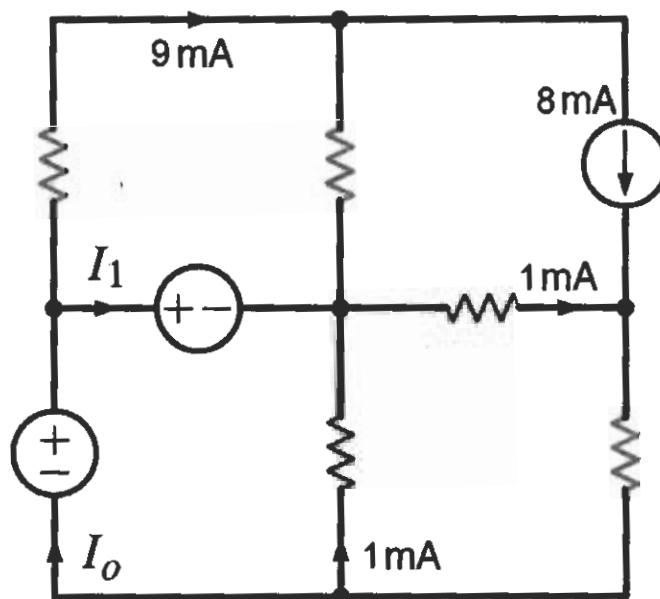


Figure P2.15

Solution: 2.15

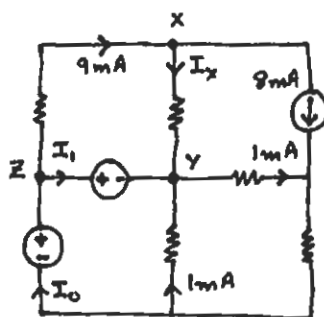

KCL: Currents enter + Currents exit = 0

KCL at x:

$$9 \times 10^{-3} - 8 \times 10^{-3} - I_x = 0$$

$$\Rightarrow I_x = 1 \text{ mA}$$

KCL at y:

$$I_1 + I_x + 1 \times 10^{-3} - 1 \times 10^{-3} = 0$$

$$\Rightarrow \boxed{I_1 = -1 \text{ mA}}$$

KCL at z:

$$I_o - I_1 - 9 \times 10^{-3} = 0$$

$$\Rightarrow \boxed{I_o = 8 \text{ mA}}$$

2.16 Find  $I_x$ ,  $I_y$ , and  $I_z$  in the network in Fig. P2.16.

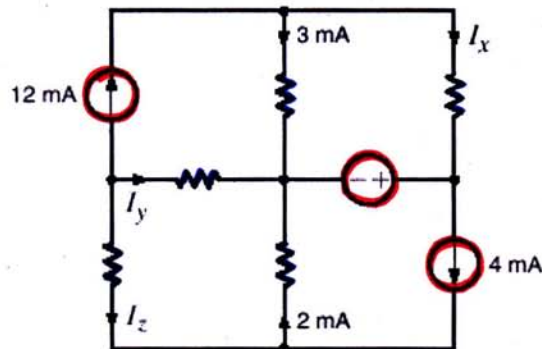


Figure P2.16

**SOLUTION:**

$$\begin{aligned}\text{KCL at A: } 12\text{ m} &= 3\text{ m} + I_x \\ I_x &= 9\text{ mA}\end{aligned}$$

$$\begin{aligned}\text{KCL at B: } I_z + 4\text{ m} &= 2\text{ m} \\ I_z &= -2\text{ mA}\end{aligned}$$

$$\begin{aligned}\text{KCL at C: } 12\text{ m} + I_y + I_z &= 0 \\ I_y &= 2\text{ m} - 12\text{ m} \\ I_y &= -10\text{ mA}\end{aligned}$$

2.17 Find  $V_{bd}$  in the circuit in Fig. P2.17.

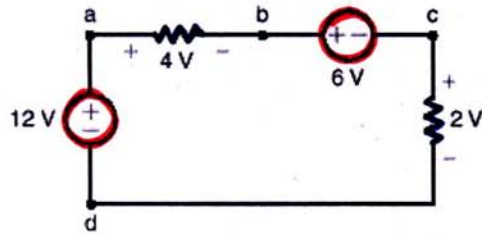


Figure P2.17

**SOLUTION:**

$$V_{bd} = V_{bc} + V_{cd}$$

$$V_{bd} = 6 + 2 = 8\text{ V}$$

2.18 Find  $V_{ad}$  in the network in Fig. P2.18.

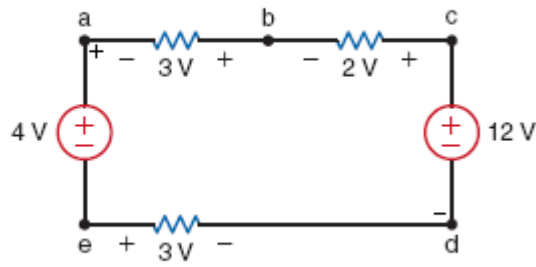


Figure P2.18

**SOLUTION:**

$$V_{ad} + 3 + 2 = 12$$

$$V_{ad} = 7V$$

2.19 Find  $V_{fb}$  and  $V_{ec}$  in the circuit in Fig. P2.19.

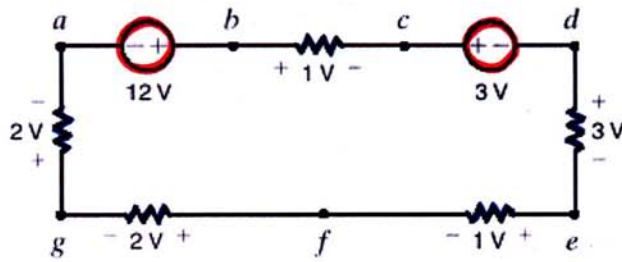


Figure P2.19

**SOLUTION:**

KVL around  $fbcd$  :

$$V_{fb} + 1 + 3 + 3 + 1 = 0$$

$$V_{fb} = -8V$$

KVL around  $ecde$  :

$$V_{ec} + 3 + 3 = 0$$

$$V_{ec} = -6V$$

2.20 Find  $V_{ae}$  and  $V_{cf}$  in the circuit in Fig. P2.20.

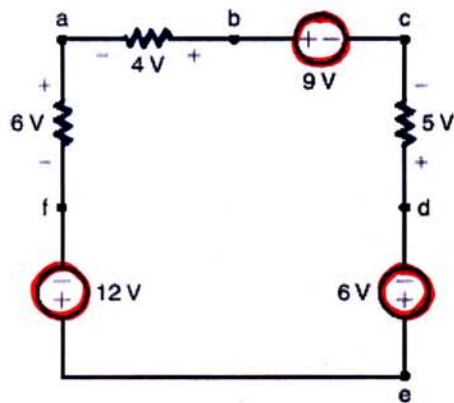


Figure P2.20

**SOLUTION:**

KVL around  $aef$  :

$$V_{ae} + 12 = 6$$

$$V_{ae} = -6 \text{ V}$$

KVL around  $cfedc$  :

$$V_{cf} + 5 + 6 = 12$$

$$V_{cf} = 1 \text{ V}$$

2.21 Given the circuit diagram in Fig. P2.21, find the following voltages:  $V_{da}$ ,  $V_{bh}$ ,  $V_{gc}$ ,  $V_{di}$ ,  $V_{fa}$ ,  $V_{ac}$ ,  $V_{ai}$ ,  $V_{hf}$ ,  $V_{fb}$ , and  $V_{dc}$ .

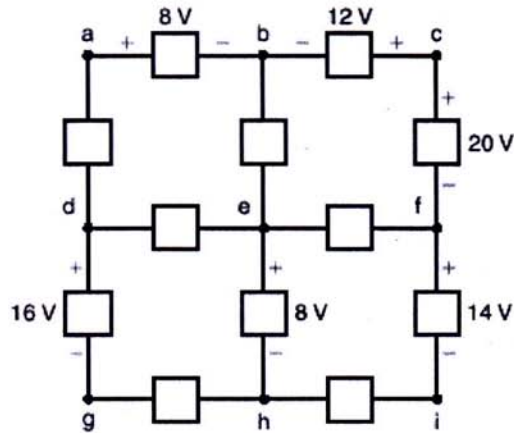


Figure P2.21

**SOLUTION:**

$$\text{KVL: } V_{eh} = V_{ef} + V_{fi} + V_{ih}$$

$$V_{eh} = 8 - 14 - 4$$

$$V_{eh} = -10\text{ V}$$

$$\text{KVL: } V_{de} + V_{ef} + V_{fi} + V_{ih} = V_{dg} + V_{gh}$$

$$V_{de} = 16 + 12 - (-10) - 14 - 4$$

$$V_{de} = 20\text{ V}$$

$$\text{KVL: } V_{ef} + V_{be} + V_{eb} = V_{ef}$$

$$V_{be} = 20 - (-10) - 12$$

$$V_{be} = 18\text{ V}$$

$$\text{KVL: } V_{de} = V_{da} + V_{ab} + V_{be}$$

$$V_{da} = 20 - 8 - 18$$

$$V_{da} = -6\text{ V}$$

$$V_{bh} = V_{be} + V_{eh} = 18 + 8$$

$$V_{bh} = 26\text{ V}$$

$$\text{KVL : } V_{gh} = V_{gc} + V_{in} + V_{fi} + V_{cf}$$

$$V_{gc} = 12 - 4 - 14 - 20$$

$$\boxed{V_{gc} = -26 \text{ V}}$$

$$\text{KVL : } V_{di} + V_{in} = V_{dg} + V_{gh}$$

$$V_{di} = -4 + 16 + 12$$

$$\boxed{V_{di} = 24 \text{ V}}$$

$$\text{KVL : } V_{fa} + V_{ab} + V_{cf} = V_{cb}$$

$$V_{fa} = 12 - 8 - 20$$

$$\boxed{V_{fa} = -16 \text{ V}}$$

$$\text{KVL : } V_{ac} + V_{cb} = V_{ab}$$

$$V_{ac} = 8 - 12$$

$$V_{ac} = -4 \text{ V}$$

$$\text{KVL : } V_{cf} + V_{fi} + V_{ia} + V_{ab} = V_{cb}$$

$$V_{ia} = 12 - 14 - 8 - 20$$

$$V_{ia} = -30 \text{ V}$$

$$\text{KVL : } V_{hf} + V_{fi} + V_{in} = 0$$

$$V_{hf} = -14 - 4$$

$$\boxed{V_{hf} = -18 \text{ V}}$$



$$\text{KVL : } V_{fb} + V_{cf} = V_{cb}$$


$$V_{fb} = 12 - 20$$

$$V_{fb} = -8 \text{ V}$$

$$\text{KVL : } V_{dc} + V_{cf} = V_{ef} + V_{de}$$

$$V_{dc} = -10 + 20 - 20$$

$$V_{dc} = -10 \text{ V}$$

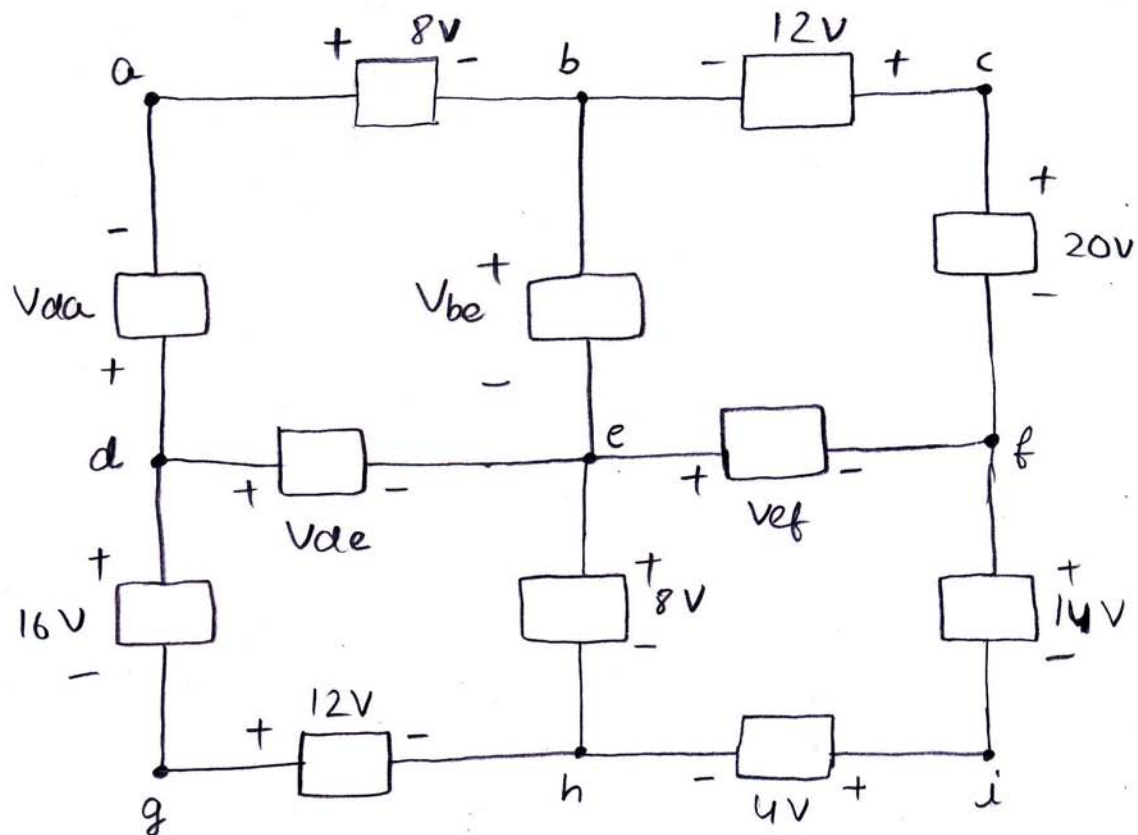

2.22 Find  $V_{ac}$  in the circuit in Fig. P2.22.

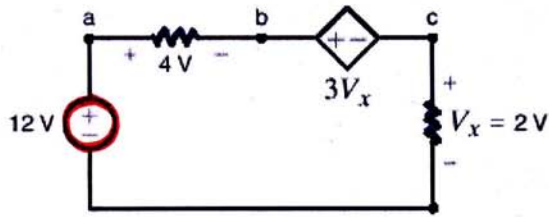


Figure P2.22

**SOLUTION:**

$$V_{ac} = 4 + 3V_x$$

$$V_{ac} = 4 + 3(2)$$

$$V_{ac} = 10\text{V}$$

2.23 Find  $V_{ad}$  and  $V_{ce}$  in the circuit in Fig. P2.23.

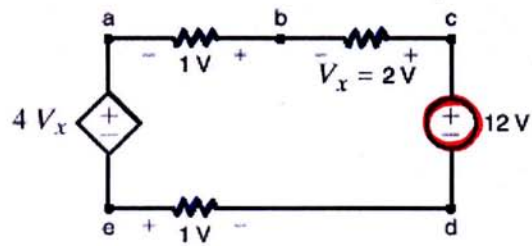


Figure P2.23

**SOLUTION:**

$$V_{ad} = 4V_x + 1 = 4(2) + 1$$

$$V_{ad} = 9V$$

$$12 = 1 + V_{ce}$$

$$V_{ce} = 11V$$

2.24 Find  $V_o$  in the network in the accompanying Figure.


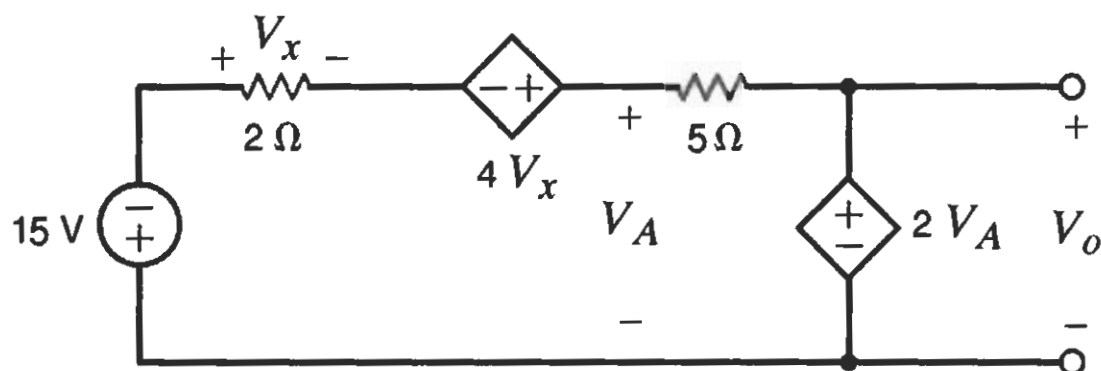


Figure P2.24

Solution: 2.24

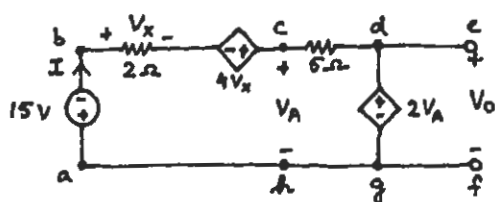

$$\text{KVL for 'abcdgha': } 15 + V_x - 4V_x + 5I + 2V_A = 0 \quad (1)$$

$$V_x = 2I \quad (2)$$

$$\text{KVL for 'cdghc': } V_A = 5I + 2V_A \Rightarrow V_A = -5I \quad (3)$$

$$\text{KVL for 'defgd': } V_o - 2V_A = 0 \Rightarrow V_o = 2V_A \quad (4)$$

$$\text{Substituting (2) + (3) in (1): } 15 + 2I - 4(2I) + 5I + 2(-5I) = 0$$

$$15 - 11I = 0 \Rightarrow I = \frac{15}{11} \text{ A} \quad (5)$$

$$\text{Substituting (5) in (3): } V_A = (-5) \frac{15}{11} \Rightarrow V_A = -\frac{75}{11} \text{ V} \quad (6)$$

$$\text{Substituting (6) in (4): } V_o = 2 \left( -\frac{75}{11} \right) \Rightarrow \boxed{V_o = -13.64 \text{ V}}$$

(Value rounded off to 2 significant digits.)

2.25 Find  $V_o$  in the circuit in Fig. P2.25.

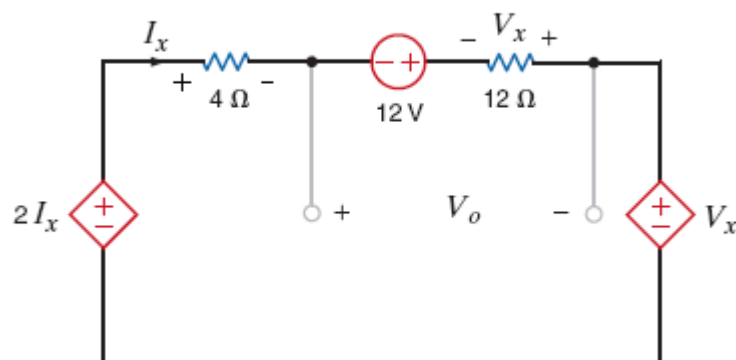


Figure P2.25

**SOLUTION:**

KVL:

$$V_o + 12 + V_x = 0$$

$$V_o = -V_x - 12$$

$$V_x = -12I_x$$

KVL around outer loop:

$$2I_x + 12 + V_x = 4I_x + V_x$$

$$2I_x + 12 + 12I_x = 4I_x + 12I_x$$

$$2I_x = 12$$


$$I_x = 6A$$

$$V_x = -12(6) = -72V$$

$$V_o = -(-72) - 12$$


$$V_o = 60V$$

**2.26** The 10-V source absorbs 2.500 mW of power. Calculate (a)  $V_{ba}$  and (b) the power absorbed by the dependent voltage source in the Figure.

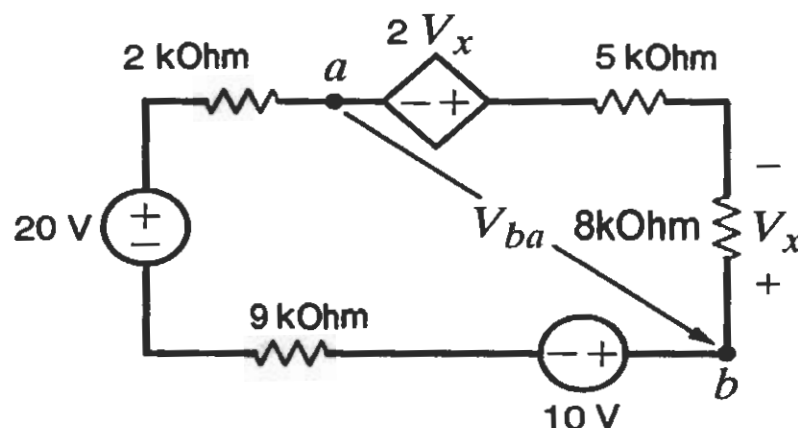

**Figure P2.26**

**Solution:** 2.26

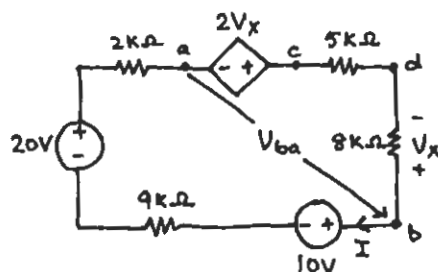

$$P_{10V} = 2.50 \text{ mW absorbed}$$

$$P_{10V} = 10I$$

$$\Rightarrow I = \frac{P_{10V}}{10} = 250 \mu\text{A}$$

$$\text{KVL for 'bacdb': } V_{ba} - V_{ca} - V_{dc} - V_{bd} = 0$$

$$\Rightarrow V_{ba} = V_{ca} + V_{dc} + V_{bd} \quad \text{--- (1)}$$

$$V_{bd} = -I(8 \times 10^3) = -(250 \times 10^{-6})(8 \times 10^3)$$

$$\Rightarrow V_{bd} = -2 \text{ V} \quad \text{--- (2)}$$

$$V_{dc} = -I(5 \times 10^3) \Rightarrow V_{dc} = -1.25 \text{ V} \quad \text{--- (3)}$$

$$V_x = V_{bd} = -2 \text{ V}$$

$$V_{ca} = 2V_x = -4 \text{ V} \quad \text{--- (4)}$$

$$\text{Substituting (2), (3), (4) in (1): } \boxed{V_{ba} = -7.25 \text{ V}}$$

$$P_{DS} = -2V_x I = -2(-2)(250 \times 10^{-6})$$

$$\Rightarrow \boxed{P_{DS} = 1 \text{ mW}}$$

2.27 Find  $V_{bd}$  in the network in Fig. P2.27.

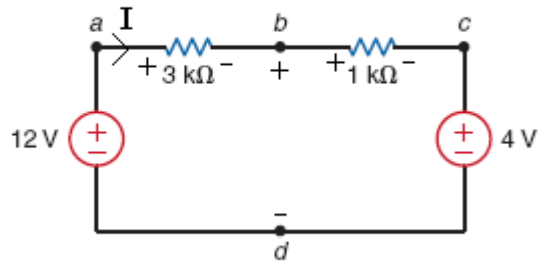


Figure P2.27

**SOLUTION:**

$$\text{KVL: } 12 = 3KI + 1KI + 4$$

$$4KI = 8$$

$$I = 2\text{mA}$$

$$\text{KVL left loop: } 12 = 3KI + V_{bd}$$

$$V_{bd} = 12 - 3K(2\text{m})$$

$$V_{bd} = 6\text{V}$$

2.28 Find  $V_x$  in the circuit in Fig. P2.28.

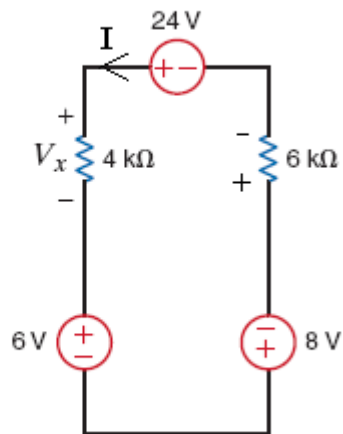


Figure P2.28

**SOLUTION:**

KVL:

$$24 = 4kI + 6 + 8 + 6kI$$

$$10kI = 10$$

$$I = 1mA$$

$$V_x = I(4k) = (1m)(4k)$$

$$V_x = 4V$$



2.29 Find  $V_{ab}$  in the network in Fig. P2.29.

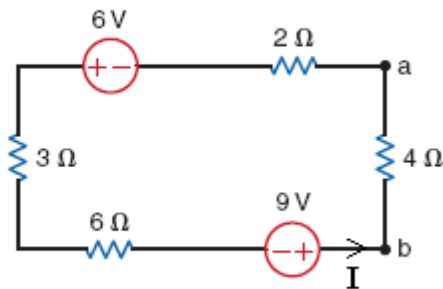


Figure P2.29

**SOLUTION:**

$$V_{ab} = -4I$$

$$\text{KVL: } 6 + 9 = 4I + 2I + 3I + 6I$$

$$15I = 15$$

$$I = 1\text{ A}$$

$$V_{ab} = -4(1)$$

$$V_{ab} = -4\text{ V}$$

2.30 If  $V_o = 3\text{ V}$  in the circuit in Fig P2.30, find  $V_S$ .

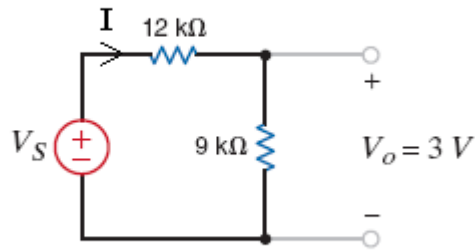


Figure P2.30

**SOLUTION:**

$$V_o = 9\text{ k}\Omega I$$

$$I = \frac{V_o}{9\text{ k}} = \frac{3}{9\text{ k}}$$

$$I = \frac{1}{3}\text{ mA}$$

KVL:

$$V_S = 12\text{ k}\Omega I + 9\text{ k}\Omega I$$

$$V_S = 21\text{ k}\left(\frac{1}{3}\text{ mA}\right)$$

$$V_S = 7\text{ V}$$

- 2.31 Find the power supplied by each source in the circuit in Fig. P2.31.

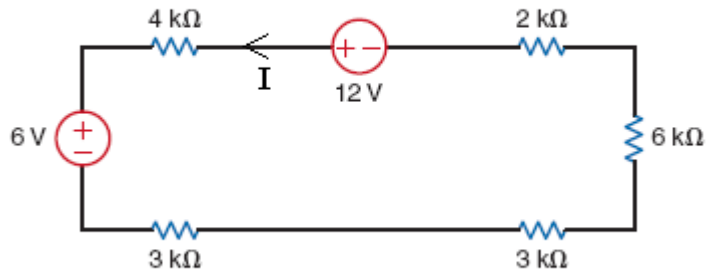


Figure P2.31

**SOLUTION:**

$$\begin{aligned}\text{KVL: } 4kI + 6 + 3kI + 3kI + 6kI + 2kI &= 12 \\ 18kI &= 6 \\ I &= \frac{1}{3} \text{ mA}\end{aligned}$$

$$\begin{aligned}P_{12V} &= 12I = 12\left(\frac{1}{3} \text{ m}\right) \\ P_{6V} &= 4 \text{ mW (supplied)}\end{aligned}$$

$$P_{6V} = -6I = -6\left(\frac{1}{3} \text{ m}\right) = -2 \text{ mW (absorbed)}$$

- 2.32 Find  $V_x$  and the power supplied by the 15-V source in the circuit in Fig. P2.32.

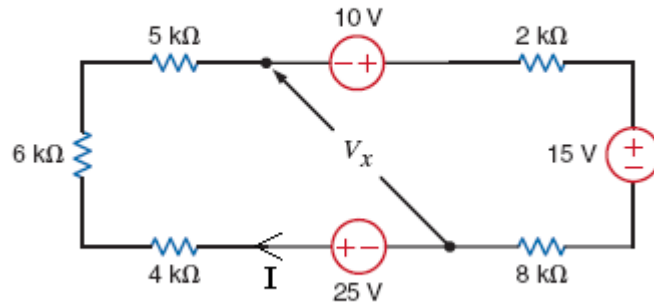


Figure P2.32


**SOLUTION:**

$$\begin{aligned}\text{KVL : } 25 + 10 &= 4KI + 6KI + 5KI + 2KI + 15 + 8KI \\ 25KI &= 20 \\ I &= 0.8 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{KVL : } V_x + 10 &= 2KI + 15 + 8KI \\ V_x &= 5 + 10K(0.8 \text{ m}) \\ V_x &= 13 \text{ V}\end{aligned}$$


$$\begin{aligned}P_{15\text{V}} &= VI = 15(0.8 \text{ m}) \\ P_{15\text{V}} &= 12 \text{ mW (absorbed)}\end{aligned}$$

2.33 Find  $V_1$  in the network in the accompanying Figure.

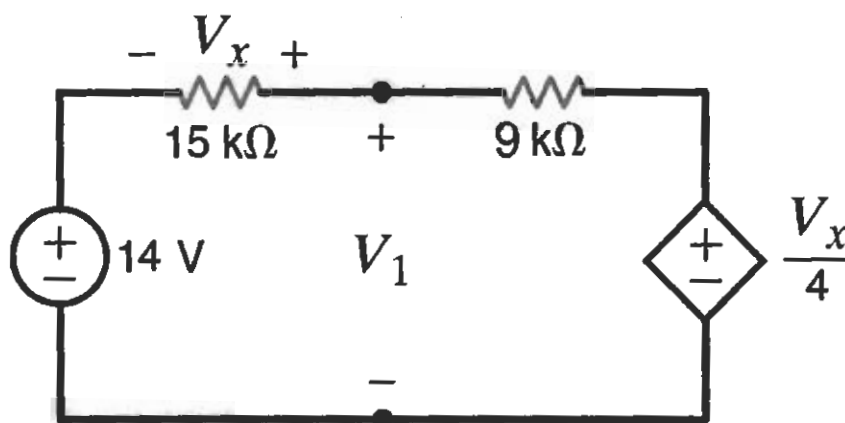

**Figure P2.33**

**Solution: 2.33**

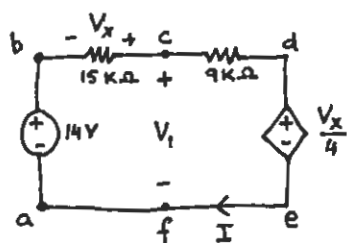

$$V_x = -I(15 \times 10^3)$$

$$\text{KVL for 'abcdefa': } -V_x + I(9 \times 10^3) + \frac{V_x}{4} - 14 = 0$$

$$I(15 \times 10^3) + I(9 \times 10^3) - \frac{I}{4}(15 \times 10^3) = 14$$

$$I(10^3) \left( 15 + 9 - \frac{15}{4} \right) = 14$$

$$\Rightarrow I = 691.36 \mu\text{A}$$

$$\text{KVL for 'cfabc': } V_1 - 14 - V_x = 0$$

$$\Rightarrow V_1 = 14 + V_x$$

$$= 14 + (-I)(15 \times 10^3)$$

$$= 14 - (691.36 \times 10^{-6})(15 \times 10^3)$$

$$\Rightarrow \boxed{V_1 = 3.63 \text{ V}}$$

(Value rounded off to 2 significant digits.)

2.34 Calculate the power absorbed by the dependent source in the circuit in Fig. P2.34.

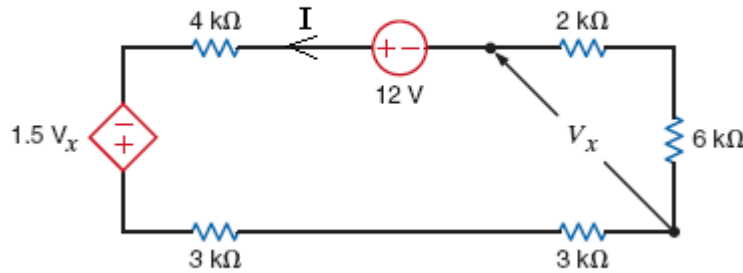


Figure P2.34

**SOLUTION:**

$$\text{KVL: } 12 + 1.5V_x = (4\text{K} + 3\text{K} + 3\text{K} + 2\text{K})I$$

$$I = \frac{12}{18\text{K}} + \frac{1.5}{18\text{K}}V_x$$

$$\text{KVL: } 2\text{KI} + 6\text{KI} = V_x$$

$$V_x = -8\text{KI}$$

$$I = \frac{12}{18\text{K}} + \frac{1.5}{18\text{K}}(-8\text{KI})$$

$$I = 0.4\text{mA}$$

$$P = 1.5V_x(I)$$

$$P = 1.5V_x(0.0004)$$

$$P = 1.5(8\text{K})(0.0004)(0.0004)$$

$$P = 1.92\text{mW}$$

2.35 Find the power absorbed by the dependent voltage source in the circuit in Fig. P2.35.

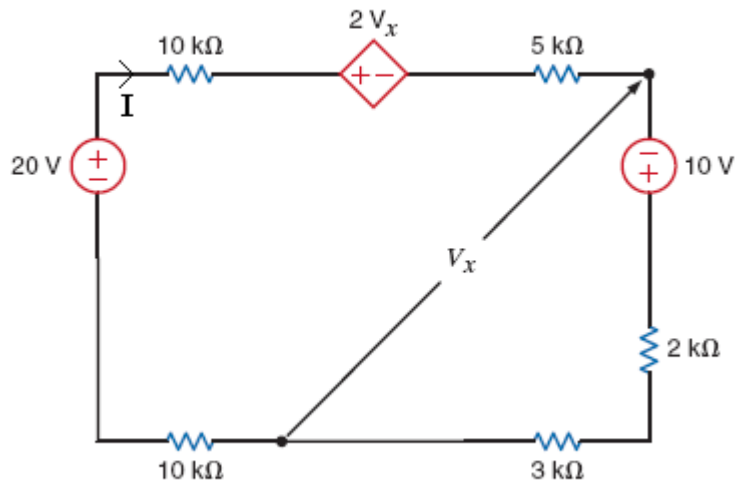


Figure P2.35

**SOLUTION:**

$$\text{KVL: } 20 + 10 = 10kI + 2V_x + 5kI + 2kI + 3kI + 10kI$$

$$30 = 30kI + 2V_x$$

$$I = 1m - \frac{1}{15}m V_x$$

$$\text{KVL: } V_x + 10 = 2kI + 3kI$$

$$V_x = 5k \left( 1m - \frac{1}{15}m V_x \right) - 10$$

$$V_x = 5 - \frac{1}{3} V_x - 10$$

$$3V_x = 15 - V_x - 30$$

$$4V_x = -15$$

$$V_x = -3.75 \text{ V}$$

$$I = 1m - \frac{1}{15}m (-3.75)$$

$$I = 1.25 \text{ mA}$$

$$P = 2V_x(I)$$

$$P = 2(-3.75)(1.25 \text{ m})$$

$$P = -9.375 \text{ mW}$$



2.36 Find the power absorbed by the dependent source in the circuit in Fig. P2.36.

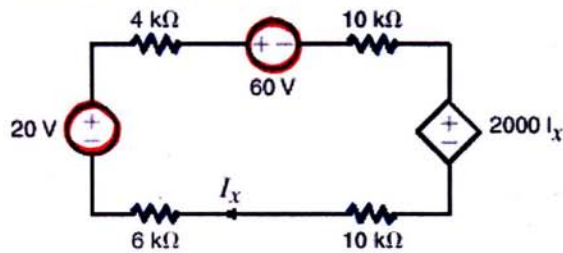


Figure P2.36

**SOLUTION:**

KVL:

$$20 = 6kI_x + 4kI_x + 60 + 10kI_x + 2kI_x + 10kI_x$$

$$32kI_x = -40$$

$$I_x = -1.25 \text{ mA}$$

$$P = (2000I_x)(I_x)$$

$$P = \{2000(-1.25 \text{ m})\}(-1.25 \text{ m})$$

$$P = 3.125 \text{ mW}$$

2.37 Find  $I_o$  in the network in Fig. P2.37.


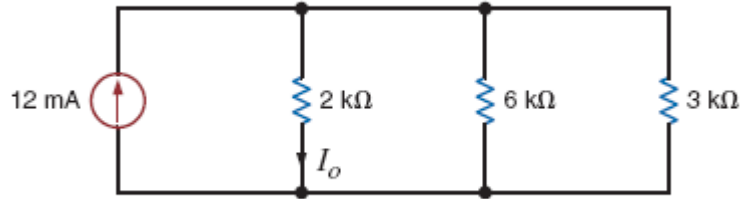


Figure P2.37

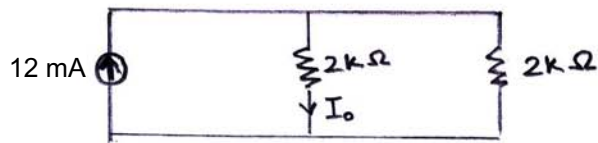**SOLUTION:**

$$6\text{ k}\Omega \parallel 3\text{ k}\Omega = 2\text{ k}\Omega$$



$$I_o = \left( \frac{2\text{ k}\Omega}{2\text{ k}\Omega + 2\text{ k}\Omega} \right) (12\text{ mA})$$

$$I_o = 6\text{ mA}$$

2.38 Find  $I_o$  in the network in Fig. P2.38.


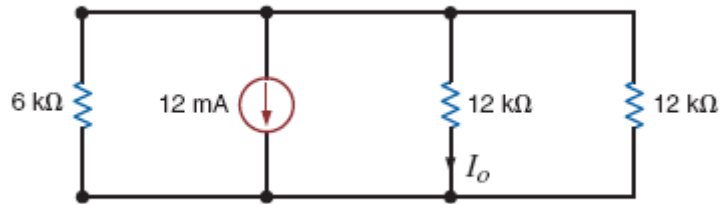


Figure P2.38

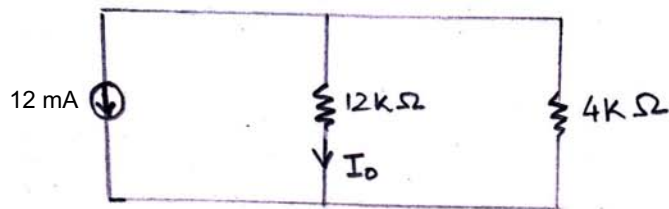**SOLUTION:**

$$6\text{ k}\Omega \parallel 12\text{ k}\Omega = 4\text{ k}\Omega$$



$$I_o = \left( \frac{4\text{ k}}{4\text{ k} + 12\text{ k}} \right) (-12\text{ mA})$$

$$I_o = -3\text{ mA}$$

2.39 Find the power supplied by each source in the circuit in Fig. P2.39.


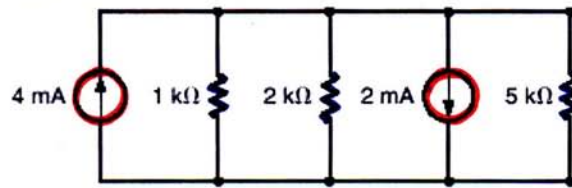



Figure P2.39

**SOLUTION:**

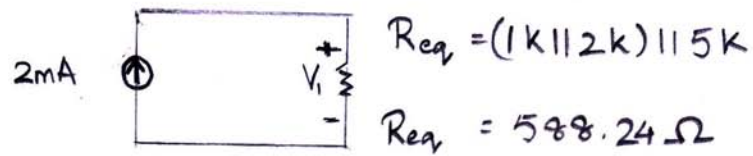

$$V_1 = 2m(588.24)$$

$$V_1 = 1.18 V$$

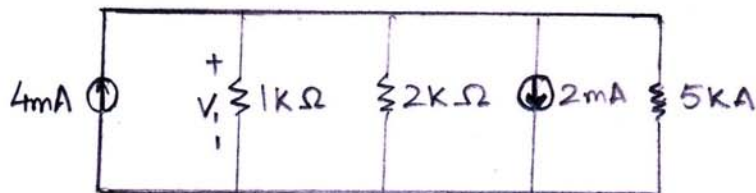

$$P_{4mA} = 4m(1.18)$$

$$P_{4mA} = 4.72 mW$$

$$P_{2mA} = (-2m)(1.18)$$

$$P_{2mA} = -2.36 mW$$

2.40 Find the current  $I_A$  in the circuit in Fig. P2.40.


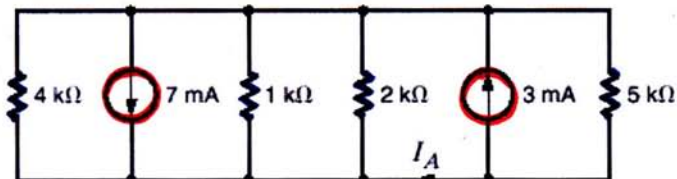
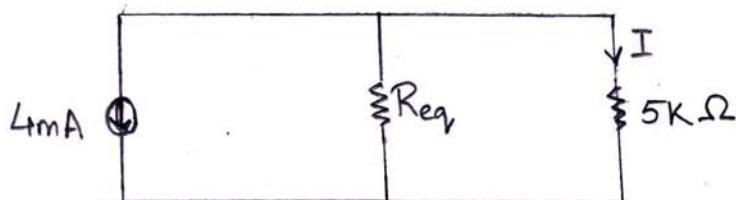


Figure P2.40

**SOLUTION:**

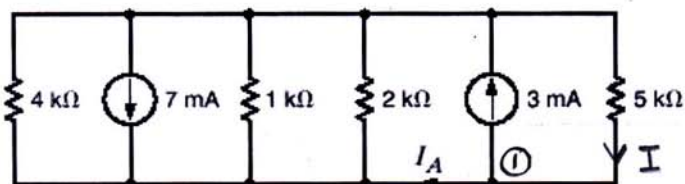

$$I = \left( \frac{R_{eq}}{R_{eq} + 5k} \right) (-4m)$$

$$I = -0.41mA$$

KCL at ① :

$$I = 3m + I_A$$

$$I_A = -0.41m - 3m$$

$$\boxed{I_A = -3.41mA}$$

2.41 Find  $I_o$  in the network in the accompanying Figure.


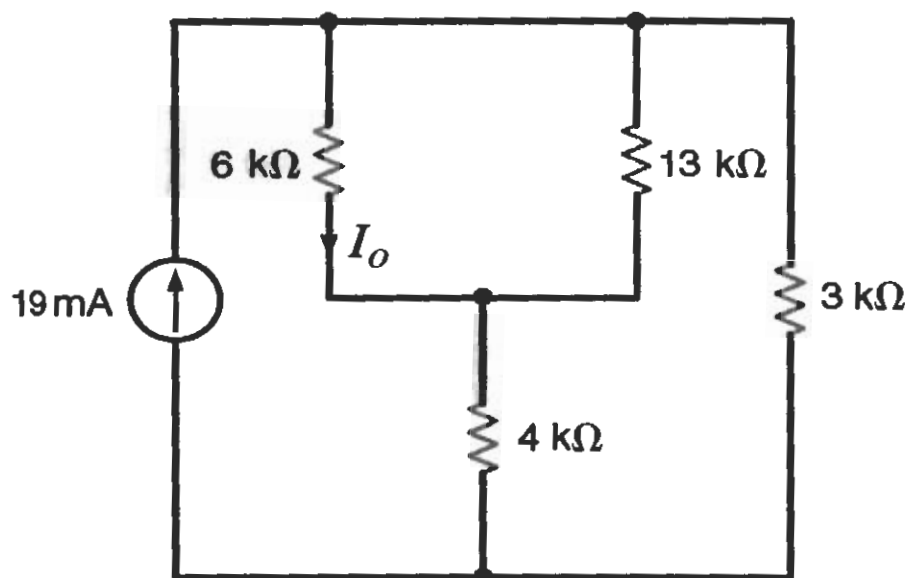


Figure P2.41

Solution: 2.41

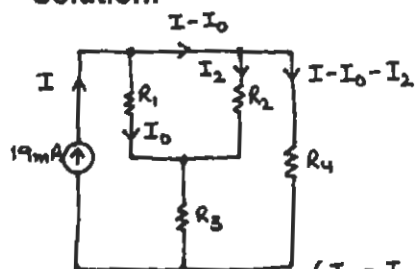

$$R_1 = 6 \text{ k}\Omega, R_2 = 13 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, R_4 = 3 \text{ k}\Omega$$

$$R_{EQ} = \frac{R_1 R_2}{R_1 + R_2} + R_3 = \frac{6(13)}{6+13} + 4$$

$$\Rightarrow R_{EQ} = 8.11 \text{ k}\Omega$$



$$(I_1 = I_o + I_2) \quad I_1 = 19 \times 10^{-3} \left[ \frac{R_4}{R_{EQ} + R_4} \right]$$

$$= 19 \times 10^{-3} \left[ \frac{3}{8.11 + 3} \right] = 5.13 \text{ mA}$$

$$I_o = I_1 \left[ \frac{R_2}{R_1 + R_2} \right]$$

$$= 5.13 \times 10^{-3} \times \frac{13}{19}$$
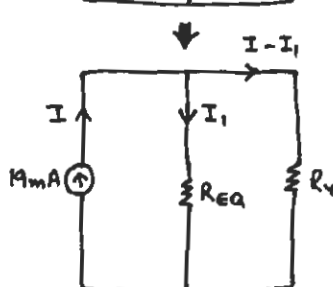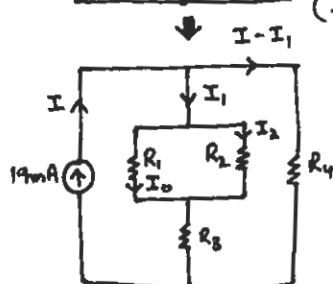
$$\Rightarrow \boxed{I_o = 3.51 \text{ mA}}$$



(Value rounded off to two significant digits.)

2.42 Find  $I_0$  in the network in Fig. P2.42.

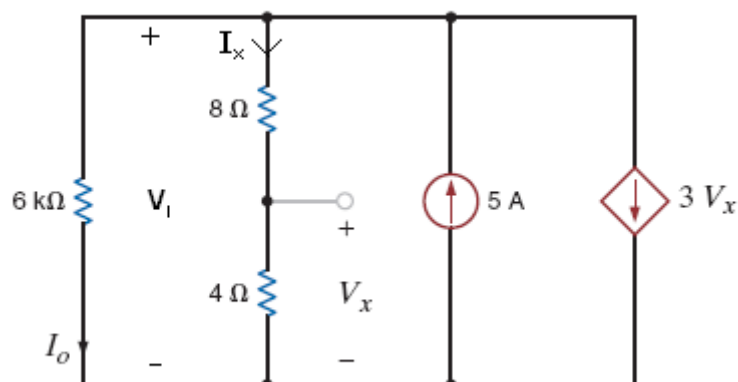


Figure P2.42

**SOLUTION:**

$$\text{KCL: } 5 = \frac{V_1}{6} + \frac{V_1}{8+4} + 3V_x$$

$$V_x = \left( \frac{4}{4+8} \right) (V_1)$$

$$V_x = \frac{V_1}{3}$$

$$5 = \frac{V_1}{6} + \frac{V_1}{12} + 3\left(\frac{V_1}{3}\right)$$

$$60 = 2V_1 + V_1 + 12V_1$$

$$15V_1 = 60$$

$$V_1 = 4 \text{ V}$$

$$V_1 = 6I_0$$

$$I_0 = \frac{V_1}{6}$$

$$I_o = \frac{4}{6}$$

$$I_o = \frac{2}{3} \text{ A}$$



2.43 Calculate the power absorbed by the dependent source in the circuit in Fig. P2.43.


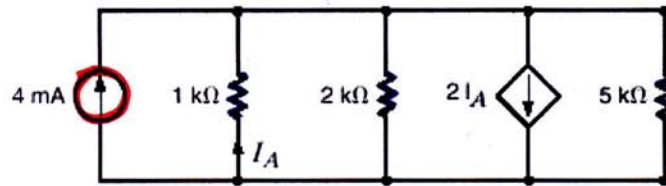


Figure P2.43

**SOLUTION:**

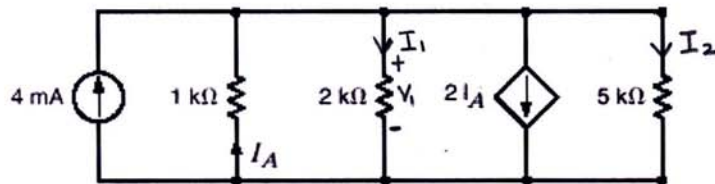

$$\text{KCL: } 4\text{m} + I_A = I_1 + I_2 + 2I_A$$

$$I_A = -\frac{V_1}{1\text{k}}$$

$$4\text{m} - \frac{V_1}{\text{k}} = I_1 + I_2 + 2\left(-\frac{V_1}{1\text{k}}\right)$$

$$I_1 = \frac{V_1}{2\text{k}} \text{ and } I_2 = \frac{V_1}{5\text{k}}$$

$$4\text{m} - \frac{V_1}{1\text{k}} = \frac{V_1}{2\text{k}} + \frac{V_1}{5\text{k}} + 2\left(-\frac{V_1}{1\text{k}}\right)$$

$$40 - 10V_1 = 5V_1 + 2V_1 - 20V_1$$

$$V_1 = -\frac{40}{3} \text{ V}$$


$$I_A = \frac{-(-\frac{40}{3})}{1\text{k}} = 13.33\text{mA}$$

$$P_{2I_A} = V_1 (2I_A) = \left(-\frac{40}{3}\right) (2) (13.33\text{m})$$

$$P_{2I_A} = \left(-\frac{40}{3}\right) (2) \left(\frac{40}{3}\right)$$

$$= -355.55\text{mW}$$

2.44 Determine  $I_L$  in the circuit in the Figure.

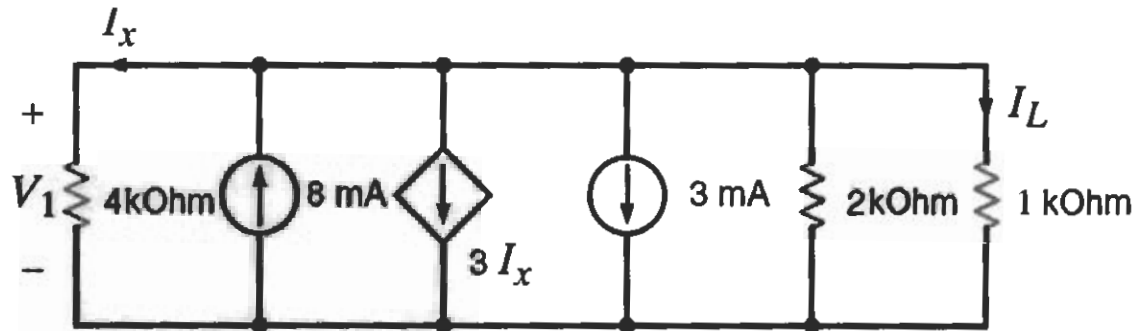

**Figure P2.44**

**Solution:** 2.44

$$I_x = \frac{V_1}{4000}$$

$$\text{KCL : } I_x - 8 \times 10^{-3} + 3I_x + 3 \times 10^{-3} + \frac{V_1}{2000} + \frac{V_1}{1000} = 0$$

$$\frac{V_1}{4000} - 8 \times 10^{-3} + \frac{3V_1}{4000} + 3 \times 10^{-3} + \frac{V_1}{2000} + \frac{V_1}{1000} = 0$$

$$\frac{V_1}{1000} \left[ \frac{1}{4} + \frac{3}{4} + \frac{1}{2} + 1 \right] = 5 \times 10^{-3}$$

$$\Rightarrow V_1 = 2 \text{ V}$$

$$I_L = \frac{V_1}{1000} \Rightarrow I_L = 2 \text{ mA}$$

2.45 Find the power absorbed by the dependent source in the network in Fig. P2.45.


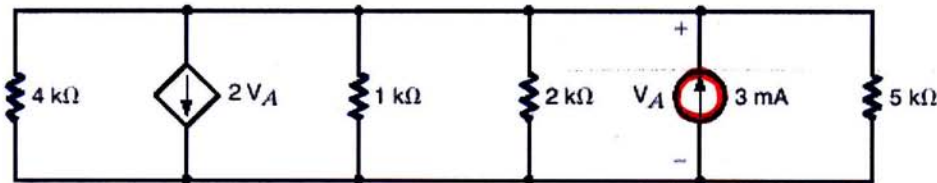


Figure P2.45

**SOLUTION:**

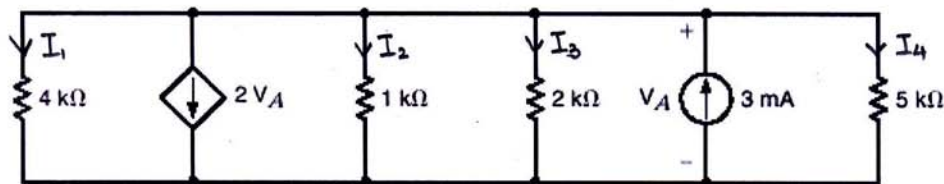

$$\text{KCL: } 3\text{m} = I_1 + 2V_A + I_2 + I_3 + I_4$$

$$I_1 = \frac{V_A}{4\text{k}}, I_2 = \frac{V_A}{1\text{k}}, I_3 = \frac{V_A}{2\text{k}}, \text{ and } I_4 = \frac{V_A}{5\text{k}}$$

$$3\text{m} = \frac{V_A}{4\text{k}} + 2V_A + \frac{V_A}{1\text{k}} + \frac{V_A}{2\text{k}} + \frac{V_A}{5\text{k}}$$

$$60 = 5V_A + 40\text{k}V_A + 20V_A + 10V_A + 4V_A$$

$$V_A = 1.5\text{mV}$$

$$P_{2V_A} = V_A I = V_A (2V_A)$$

$$P_{2V_A} = 1.5\text{m}(2)(1.5\text{m})$$

$$P_{2V_A} = 4.5\mu\text{W}$$

2.46 Find  $R_{AB}$  in the circuit in the accompanying Figure.


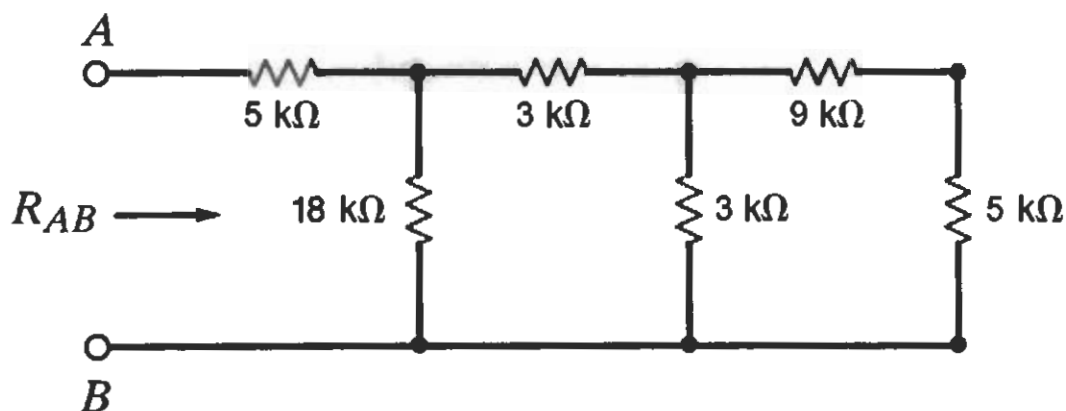


Figure P2.46

Solution: 2.46

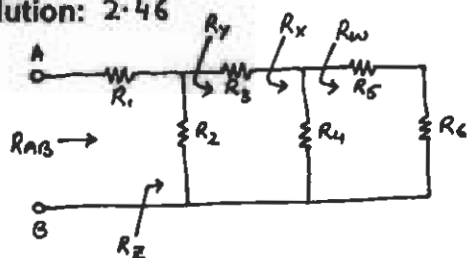

$$R_1 = 5 \text{ k}\Omega, R_2 = 18 \text{ k}\Omega, R_3 = 3 \text{ k}\Omega, \\ R_4 = 3 \text{ k}\Omega, R_5 = 9 \text{ k}\Omega, R_6 = 5 \text{ k}\Omega$$

$$R_W = R_5 + R_6 = 14 \text{ k}\Omega$$

$$R_X = R_4 \parallel R_W = \frac{3(14)}{3+14} = 2.47 \text{ k}\Omega$$

$$R_Y = R_3 + R_X = 5.47 \text{ k}\Omega$$


$$R_Z = R_2 \parallel R_Y = \frac{18(5.47)}{18+5.47} = 4.20 \text{ k}\Omega$$

$$R_{AB} = R_1 + R_Z = 9.20 \text{ k}\Omega$$

$$\Rightarrow \boxed{R_{AB} = 9.20 \text{ k}\Omega}$$


(Value rounded off to 2 significant digits.)

**2.47** Find  $R_{AB}$  in the network in the accompanying Figure.

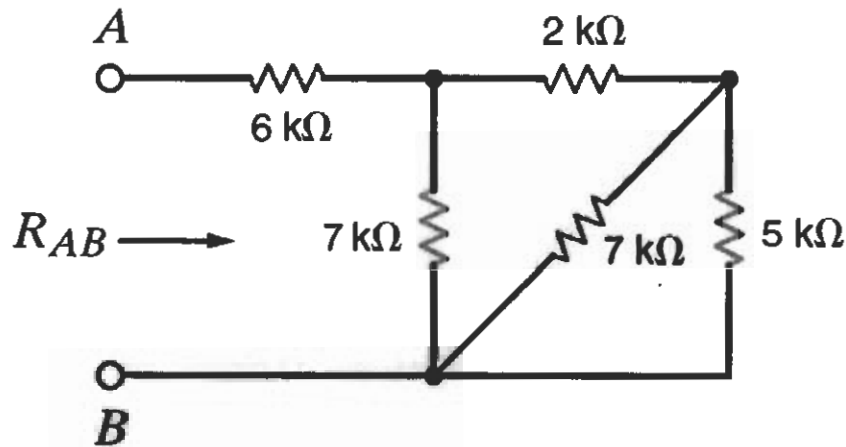

**Figure P2.47**

**Solution:** 2.47

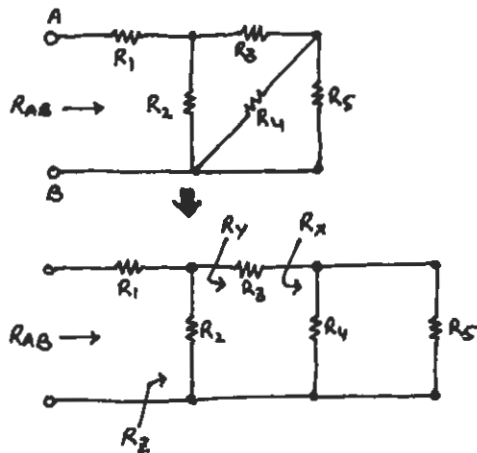

$$R_1 = 6 \text{ k}\Omega, R_2 = 7 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega, \\ R_4 = 7 \text{ k}\Omega, R_5 = 5 \text{ k}\Omega$$

$$R_x = R_4 \parallel R_5 = \frac{7(5)}{12} = 2.92 \text{ k}\Omega$$

$$R_y = R_3 + R_x = 4.92 \text{ k}\Omega$$

$$R_z = R_2 \parallel R_y = \frac{7(4.92)}{11.92} = 2.89 \text{ k}\Omega$$

$$R_{AB} = R_1 + R_z = 8.89 \text{ k}\Omega$$

$$\Rightarrow \boxed{R_{AB} = 8.89 \text{ k}\Omega}$$

(Value rounded off to 2 significant digits.)

2.48 Find  $R_{AB}$  in the circuit in the accompanying Figure.


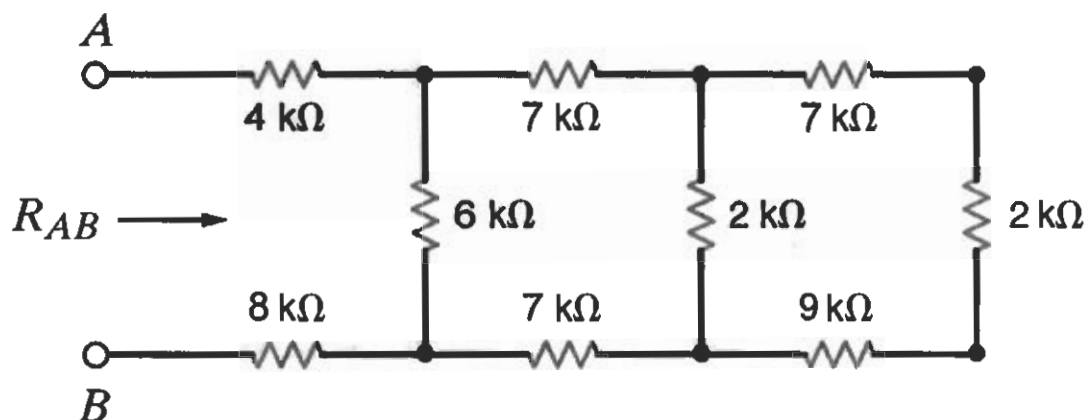


Figure P2.48

Solution: 2.48

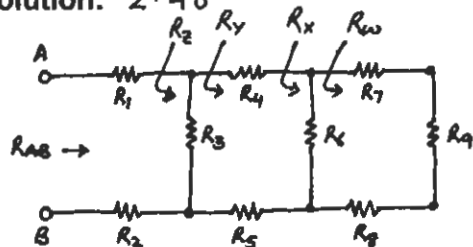

$$\begin{aligned} R_1 &= 4 \text{ k}\Omega, \quad R_2 = 8 \text{ k}\Omega, \quad R_3 = 6 \text{ k}\Omega, \\ R_4 &= 7 \text{ k}\Omega, \quad R_5 = 7 \text{ k}\Omega, \quad R_6 = 2 \text{ k}\Omega, \\ R_7 &= 7 \text{ k}\Omega, \quad R_8 = 9 \text{ k}\Omega, \quad R_9 = 2 \text{ k}\Omega \end{aligned}$$

$$R_W = R_7 + R_8 + R_9 = 18 \text{ k}\Omega$$

$$R_x = R_6 \parallel R_W = \frac{2(18)}{2+18} = 1.8 \text{ k}\Omega$$

$$R_y = R_4 + R_x + R_5 = 15.8 \text{ k}\Omega$$

$$R_z = R_3 \parallel R_y = \frac{6(15.8)}{6+15.8} = 4.35 \text{ k}\Omega$$

$$R_{AB} = R_1 + R_2 + R_z$$

$$\Rightarrow R_{AB} = 16.35 \text{ k}\Omega$$

(Value rounded off to 2 significant digits.)

2.49 Find  $R_{AB}$  in the network in Fig. P2.49.

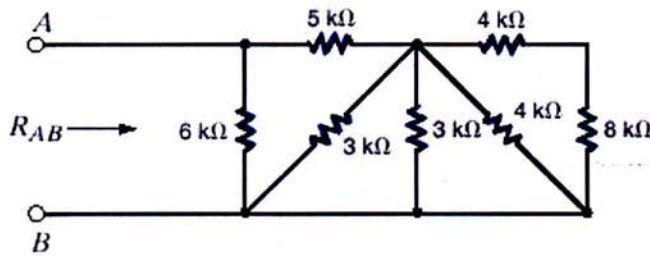



Figure P2.49

**SOLUTION:**

$$R_1 = [(4k + 8k) \parallel 4k] \parallel 3k$$

$$R_1 = \left( \frac{12k(4k)}{12k + 4k} \right) \parallel 3k$$

$$R_1 = 1.5k \Omega$$

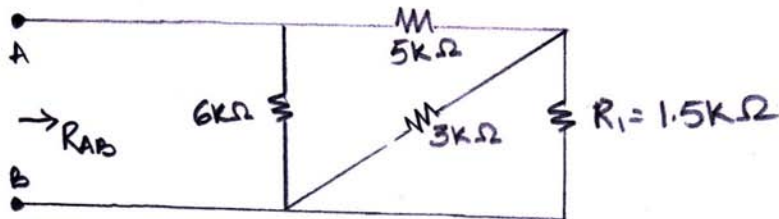


$$R_{AB} = [(1.5k \parallel 3k) + 5k] \parallel 6k$$

$$R_{AB} = \left( \frac{1.5k(3k)}{1.5k + 3k} + 5k \right) \parallel 6k$$

$$R_{AB} = 3k \Omega$$



2.50 Find  $R_{AB}$  in the circuit in Fig. P2.50.

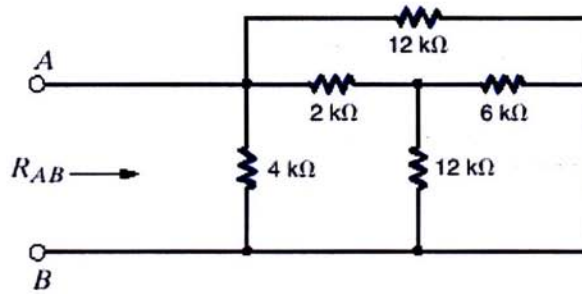


**Figure P2.50**

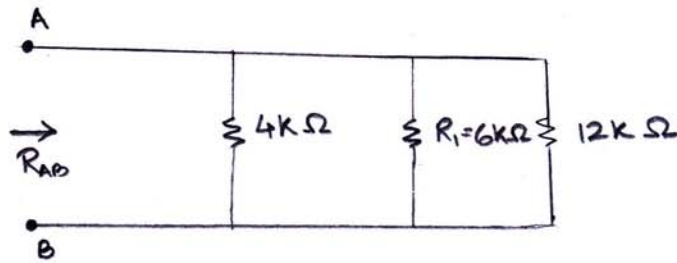**SOLUTION:**

$$R_1 = (12k \parallel 6k) + 2k$$

$$R_1 = 6k\Omega$$



$$R_{AB} = (4k \parallel 6k) \parallel 12k$$

$$R_{AB} = 2.4K \parallel 12K$$

$$R_{AB} = 2k\Omega$$

2.51 Find  $R_{AB}$  in the network in Fig. P2.51.


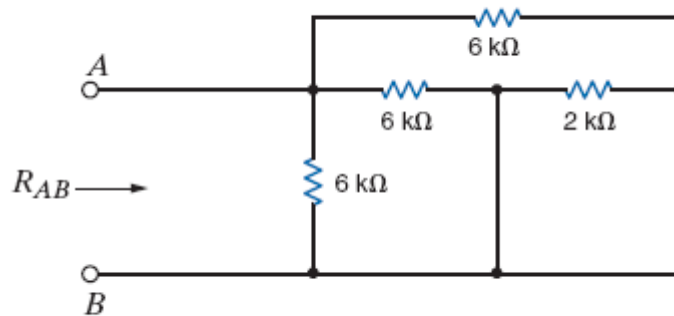


Figure P2.51

**SOLUTION:**

$$R_1 = (2k \parallel 6k) + 6k$$

$$R_1 = 6k \Omega$$

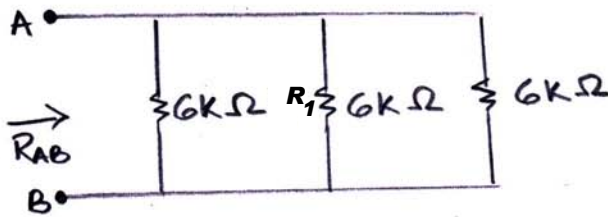

$$R_{AB} = (6k \parallel 6k) \parallel 6k$$

$$R_{AB} = 3k \parallel 6k$$

$$R_{AB} = 2k \Omega$$

2.52 Find  $R_{AB}$  in the circuit in Fig. P2.52.


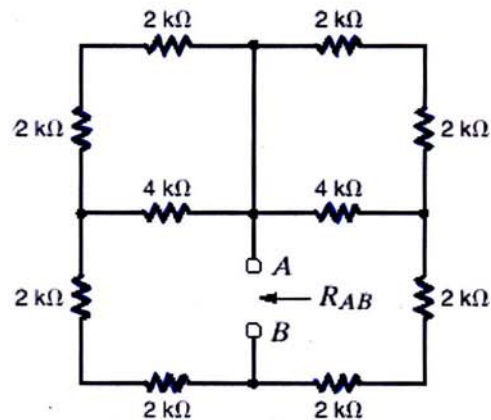
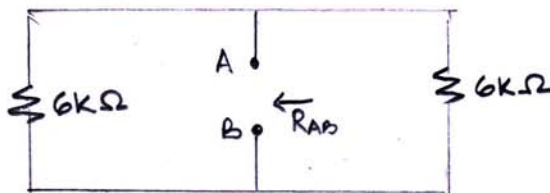


Figure P2.52

**SOLUTION:**

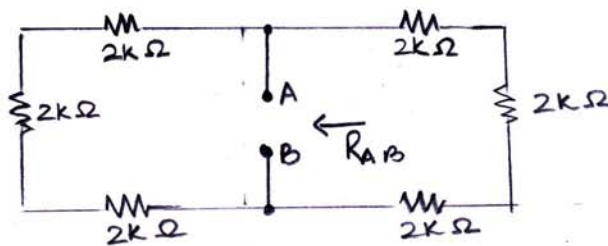

$$R_{AB} = 6k \parallel 6k$$

$$R_{AB} = 3k \Omega$$

2.53 Find the equivalent resistance,  $R_{eq}$ , in the network in Fig. P2.53.


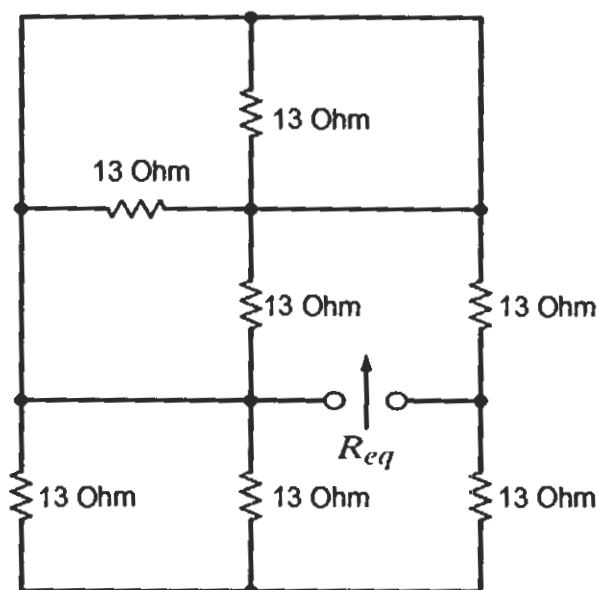


Figure P2.53

Solution: 2.53

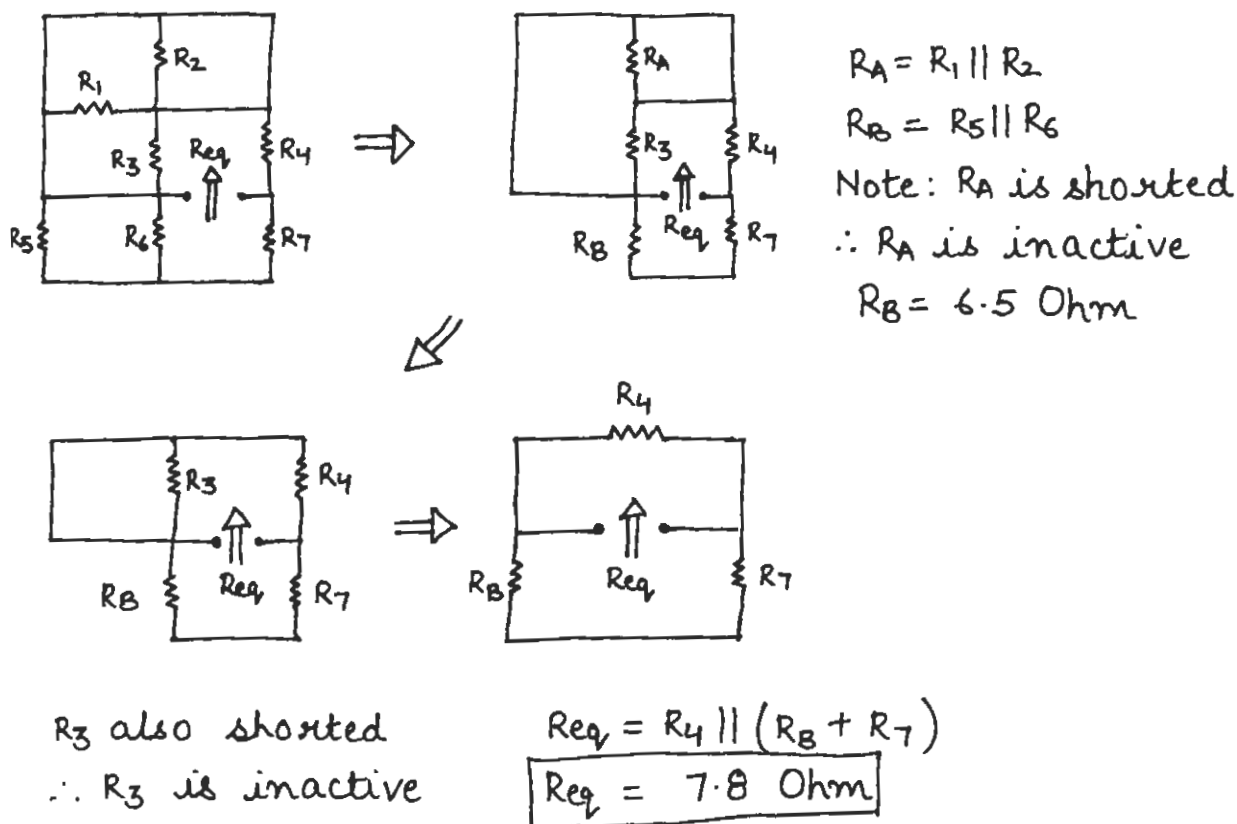

2.54 Find the equivalent resistance looking in at terminals a-b in the circuit in Fig. P2.54.


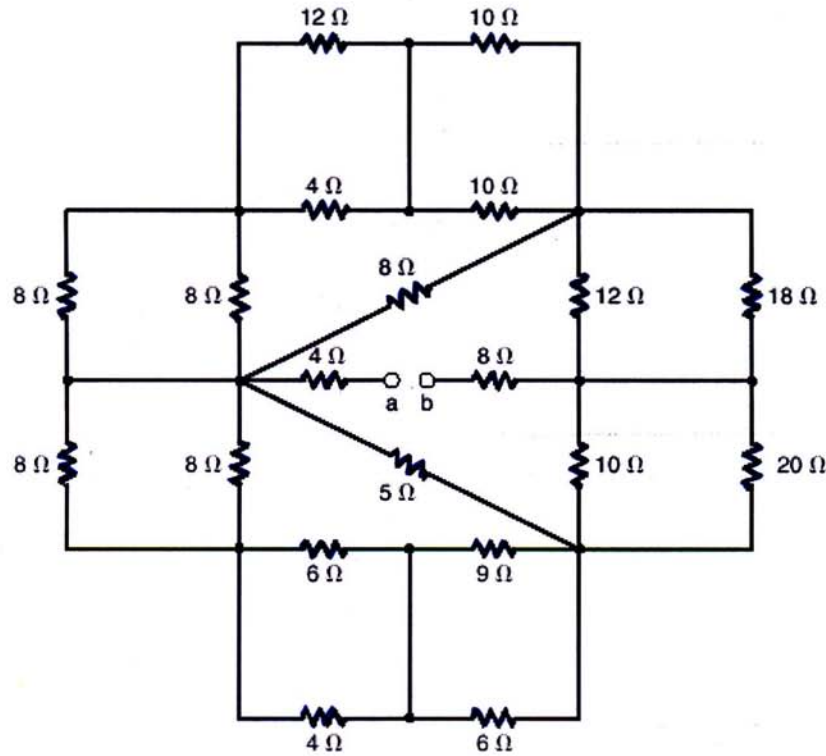


Figure P2.54

**SOLUTION:**

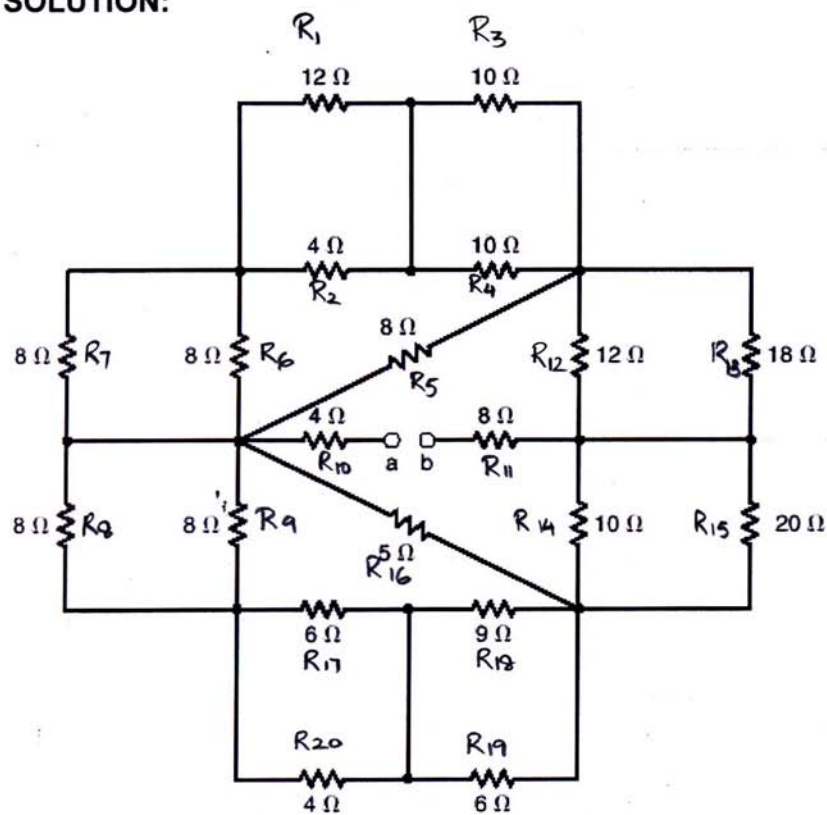

$$R_a = R_1 \parallel R_2 = 12 \parallel 4 = 3 \Omega$$

$$R_b = R_3 \parallel R_4 = 10 \parallel 10 = 5 \Omega$$

$$R_c = R_7 \parallel R_6 = 8 \parallel 8 = 4 \Omega$$

$$R_d = R_{12} \parallel R_{13} = 12 \parallel 18 = 7.2 \Omega$$

$$R_e = R_8 \parallel R_9 = 8 \parallel 8 = 4 \Omega$$

$$R_f = R_{14} \parallel R_{15} = 10 \parallel 20 = 6.67 \Omega$$


$$R_g = R_{17} \parallel R_{20} = 6 \parallel 4 = 2.4 \Omega$$

$$R_h = R_{18} \parallel R_{19} = 9 \parallel 6 = 3.6 \Omega$$

$$R_z = (R_x + R_d) \parallel (R_y + R_f)$$

$$R_z = (4.8 + 7.2) \parallel (3.33 + 6.67)$$

$$R_z = 12 \parallel 10 = 5.45 \Omega$$

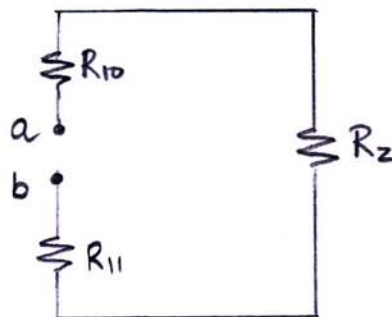

$$R_{ab} = R_{10} + R_{11} + R_2 = 4 + 8 + 5.45$$

$$R_{ab} = 17.45 \, \Omega$$

- 2.55 Given the resistor configuration shown in Fig. P2.55, find the equivalent resistance between the following sets of terminals: (1) a and b, (2) b and c, (3) a and c, (4) d and e, (5) a and e, (6) c and d, (7) a and d, (8) c and e, (9) b and d, and (10) b and e.


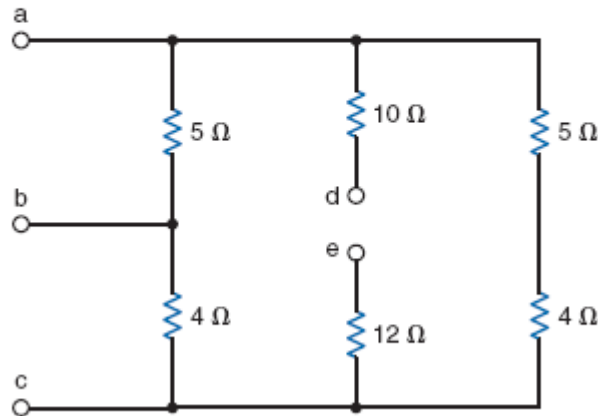


Figure P2.55


**SOLUTION:**

1.)

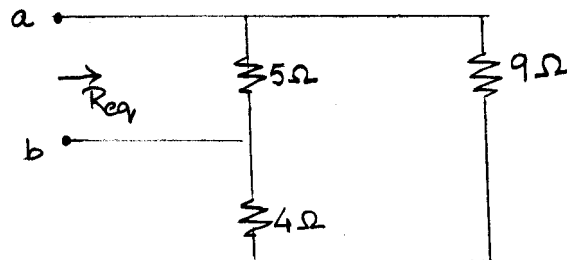

$$R_{eq} = (9 + 4) \parallel 5 = 3.61 \Omega$$


2.)

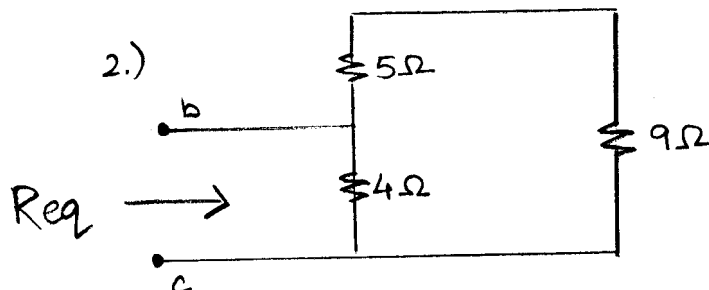

$$R_{eq} = 14 \parallel 14 = 3.11 \Omega$$




3.)

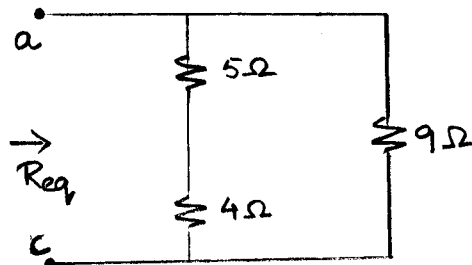


$$R_{eq} = 9 \parallel 9 = 4.5 \Omega$$

4.)

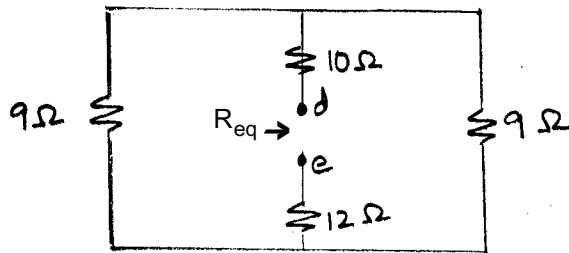


$$R_{eq} = (9 \parallel 9) + 10 + 12 = 26.5 \Omega$$

5.)

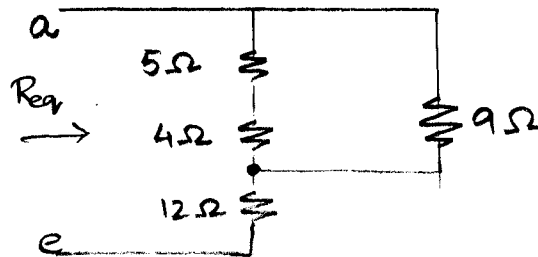



$$R_{eq} = [9 \parallel (5 + 4)] + 12 = (9 \parallel 9) + 12 = 16.5 \Omega$$

6.)

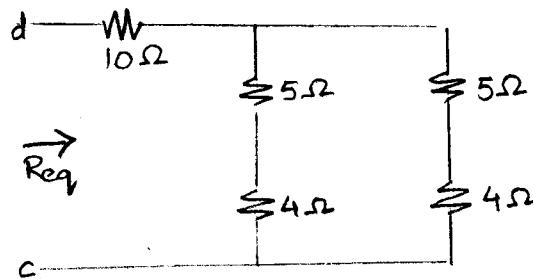


$$R_{eq} = (9 \parallel 9) + 10$$


$$R_{eq} = 14.5 \Omega$$

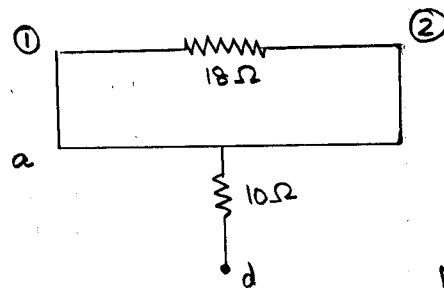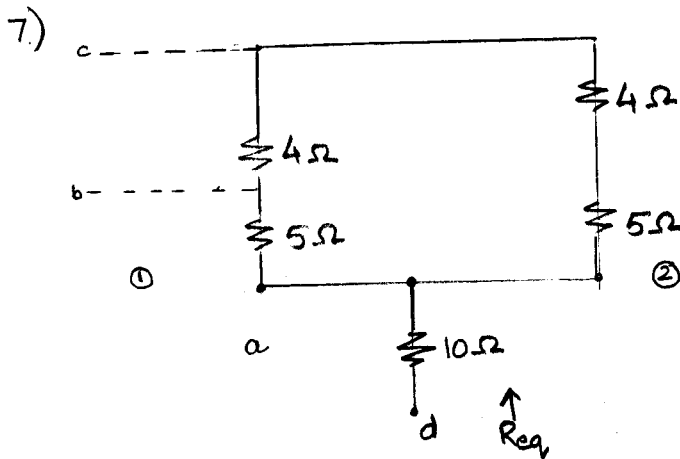

Node ① and ② are shorted.

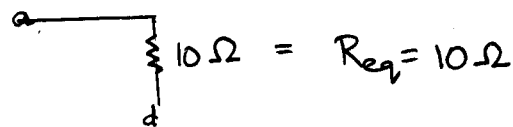


8.)

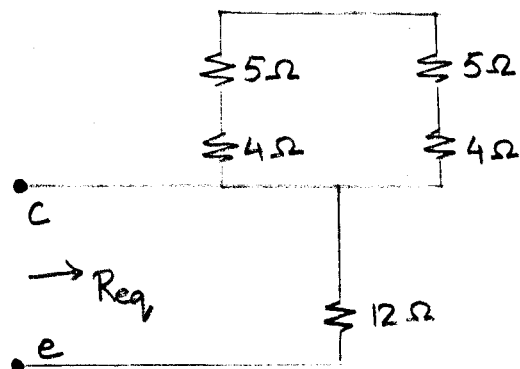


$$R_{eq} = 12 \Omega$$

9.)

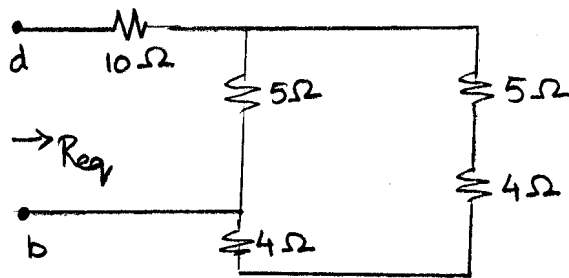

$$R_{eq} = (13 \parallel 5) + 10 = 13.61\ \Omega$$

10.)

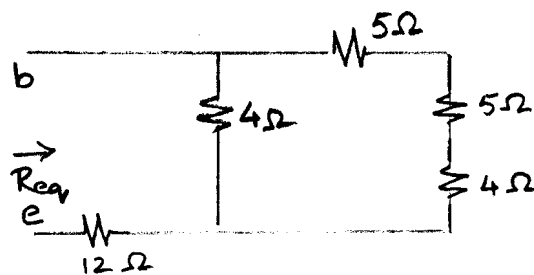

$$R_{eq} = (14 \parallel 4) + 12$$


$$R_{eq} = \frac{4(14)}{4+14} + 12$$

$$R_{eq} = 15.11\ \Omega$$


- 2.56 Seventeen possible equivalent resistance values may be obtained using three resistors. Determine the seventeen different values if you are given resistors with standard values:  $47\ \Omega$ ,  $33\ \Omega$ , and  $15\ \Omega$ .

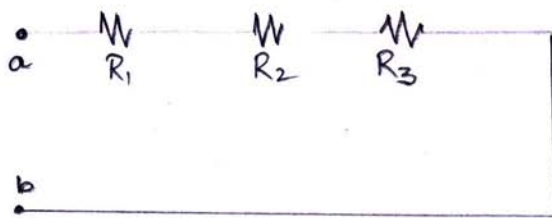**SOLUTION:**

$$R_1 = 47\ \Omega, R_2 = 33\ \Omega, \text{ and } R_3 = 15\ \Omega$$



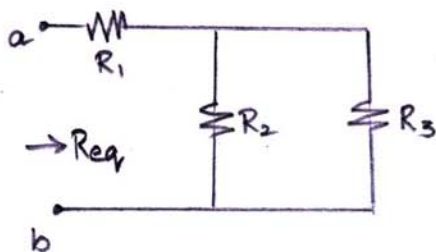
$$R_{eq} = R_1 + R_2 + R_3 = 95\ \Omega$$




$$R_{eq} = R_1 + (R_2 \parallel R_3) = 47 + \frac{33(15)}{33+15}$$

$$R_{eq} = 57.31\ \Omega$$

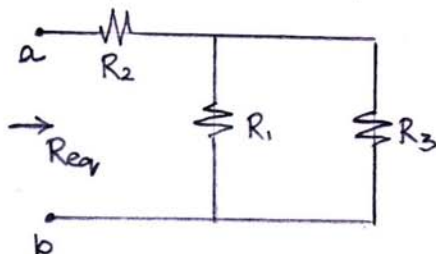

$$R_{eq} = R_2 + (R_1 \parallel R_3) = 33 + \frac{47(15)}{47+15}$$

$$R_{eq} = 44.37\ \Omega$$

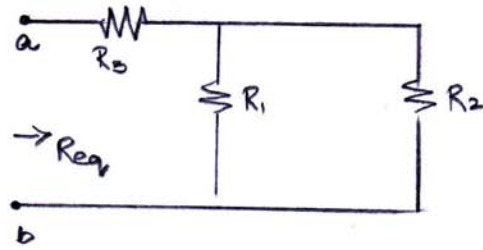

$$R_{eq} = R_3 + (R_1 \parallel R_2) = 15 + \frac{47(33)}{47+33}$$


$$R_{eq} = 34.39 \Omega$$




$$R_{eq} = R_1 \parallel R_2 \parallel R_3 = 47 \parallel 33 \parallel 15$$

$$R_{eq} = \frac{47(33)}{47+33} \parallel 15$$

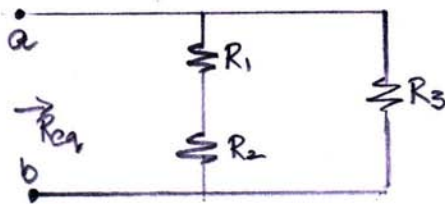
$$R_{eq} = 19.39 \parallel 15 = 8.46 \Omega$$


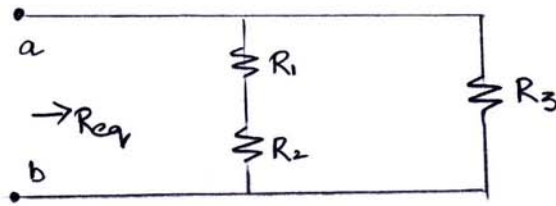
$$R_{eq} = (R_1 + R_2) \parallel R_3 = 80 \parallel 15 = 12.63 \Omega$$



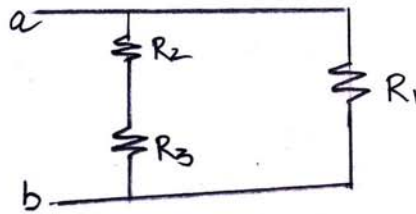
$$R_{eq} = (R_1 + R_3) \parallel R_2 = 62 \parallel 33 = 21.54 \Omega$$




$$R_{eq} = (R_2 + R_3) \parallel R_1 = 48 \parallel 47$$

$$R_{eq} = 23.75 \Omega$$

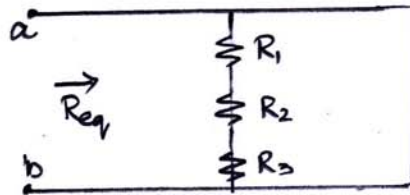


$$R_{eq} = (R_1 + R_2 + R_3) \parallel 0$$

$$R_{eq} = 0 \Omega$$

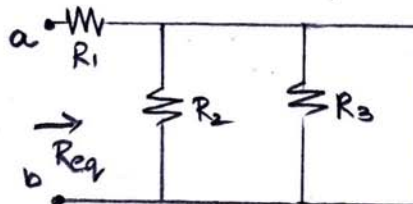


$$R_{eq} = R_1 + (R_2 \parallel R_3 \parallel 0)$$

$$R_{eq} = R_1 = 47 \Omega$$

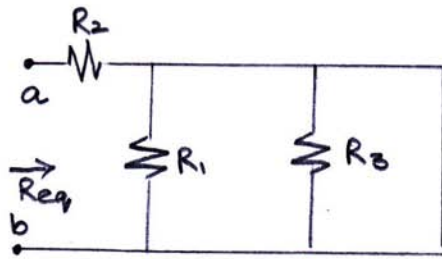


$$R_{eq} = R_2 + (R_1 \parallel R_3 \parallel 0)$$

$$R_{eq} = R_2 = 33 \, \Omega$$

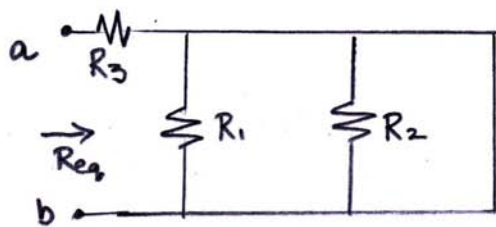


$$R_{eq} = R_3 + (R_1 \parallel R_2 \parallel 0)$$

$$R_{eq} = R_3 = 15 \, \Omega$$

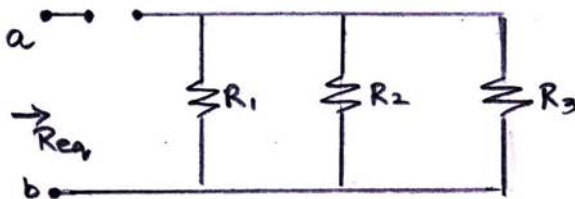

$$R_{eq} = \infty$$

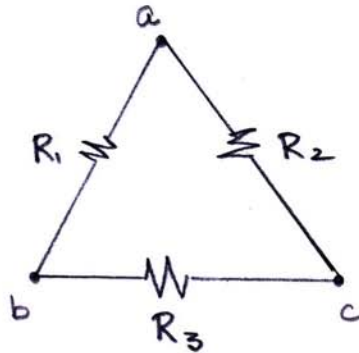


$$R_{ab} = \frac{R_2 (R_1 + R_3)}{R_2 + R_1 + R_3} = \frac{33(47+15)}{33+47+15} = 21.53 \Omega$$

$$R_{bc} = \frac{R_3 (R_1 + R_2)}{R_3 + R_1 + R_2} = \frac{15(47+33)}{15+47+33} = 12.63 \Omega$$
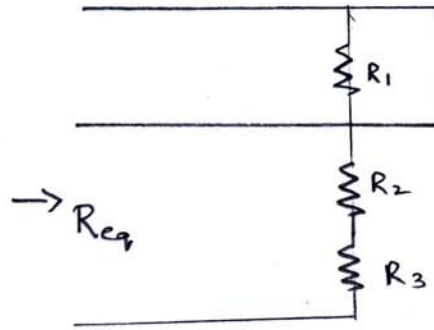
$$R_{ca} = \frac{R_1 (R_2 + R_3)}{R_1 + R_2 + R_3} = \frac{47(33+15)}{47+33+15} = 23.75 \Omega$$





$$(R_1 || 0) + R_2 + R_3$$

$$= R_2 + R_3$$

**2.57** Find the range of resistance for the following resistors.

1.  $1\text{ k}\Omega$  with a tolerance of 5% [(a)  $R_{\min}$  and (b)  $R_{\max}$ ]
2.  $670\ \Omega$  with a tolerance of 2% [(c)  $R_{\min}$  and (d)  $R_{\max}$ ]
3.  $12\text{ k}\Omega$  with a tolerance of 10% [(e)  $R_{\min}$  and (f)  $R_{\max}$ ]

---

**Solution:** 2.57

1.  $R = 1\text{ k}\Omega @ \pm 5\%$

$$R_{\min} = R(1 - \text{tol}) = 1000(0.95) = 950\ \Omega$$

$$R_{\max} = R(1 + \text{tol}) = 1000(1.05) = 1050\ \Omega$$

2.  $R = 670\ \Omega @ \pm 2\%$

$$R_{\min} = 670(0.98) = 656.60\ \Omega$$

$$R_{\max} = 670(1.02) = 683.40\ \Omega$$

3.  $R = 12\text{ k}\Omega @ \pm 10\%$

$$R_{\min} = 12 \times 10^3(0.9) = 10.8\text{ k}\Omega$$

$$R_{\max} = 12 \times 10^3(1.1) = 13.2\text{ k}\Omega$$

2.58 Given the network in Fig. P2.58, find the possible range of values for the current and power dissipated by the following resistors.

1.  $180\Omega$  with a tolerance of 1% [(a)  $I_{\min}$ , and (b)  $I_{\max}$ , (c)  $P_{\min}$ , and (d)  $P_{\max}$ ]
2.  $660\Omega$  with a tolerance of 2% [(e)  $I_{\min}$ , and (f)  $I_{\max}$ , (g)  $P_{\min}$ , and (h)  $P_{\max}$ ]

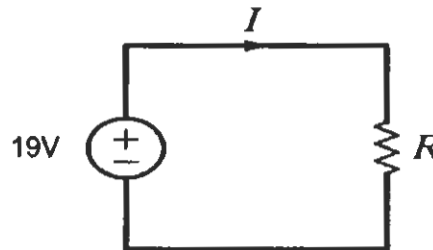


Figure P2.58

Solution: 2.58

1.  $R = 180\Omega @ 1\%$

$$I = \frac{19}{R} \quad I_{\max} = \frac{19}{R_{\min}} \quad I_{\min} = \frac{19}{R_{\max}}$$

$$R_{\min} = 180(0.99) = 178.2\Omega$$

$$R_{\max} = 180(1.01) = 181.8\Omega$$

$$(a) I_{\min} = \frac{19}{181.8} = 104.51 \text{ mA} = 105 \text{ mA}$$

$$(b) I_{\max} = \frac{19}{178.2} = 106.62 \text{ mA} = 107 \text{ mA}$$

$$(c) P_{\min} = 19(I_{\min}) = 19(104.51) = 1985.69 = 1986 \text{ mW}$$

$$(d) P_{\max} = 19(I_{\max}) = 19(106.62) = 2025.78 = 2026 \text{ mW}$$

$$I_{\min} = 105 \text{ mA}$$

$$P_{\min} = 1986 \text{ mW}$$

$$I_{\max} = 107 \text{ mA}$$

$$P_{\max} = 2026 \text{ mW}$$

$$2. \quad R = 660 \, \Omega @ \pm 2\%$$

$$R_{\min} = 660(0.98) = 646.8 \, \Omega$$

$$R_{\max} = 660(1.02) = 673.2 \, \Omega$$

$$(e) \quad I_{\min} = \frac{19}{673.2} = 28.22 \, \text{mA}$$

$$(f) \quad I_{\max} = \frac{19}{646.8} = 29.38 \, \text{mA}$$

$$(g) \quad P_{\min} = 19(28.22) = 536.18 \, \text{mW} = 536 \, \text{mW}$$

$$(h) \quad P_{\max} = 19(29.4) = 558.6 \, \text{mW} = 558 \, \text{mW}$$

$$I_{\min} = 28.2 \, \text{mA}$$

$$P_{\min} = 536 \, \text{mW}$$

$$I_{\max} = 29.4 \, \text{mA}$$

$$P_{\max} = 558 \, \text{mW}$$

2.59 Find  $I_1$  and  $V_o$  in the circuit in Fig. P2.59.


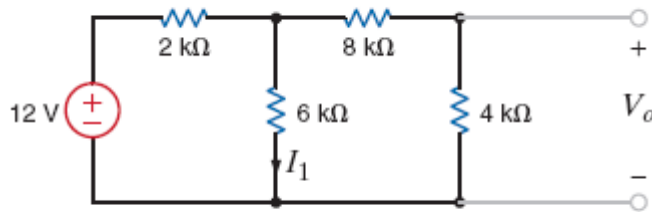



Figure P2.59

**SOLUTION:**

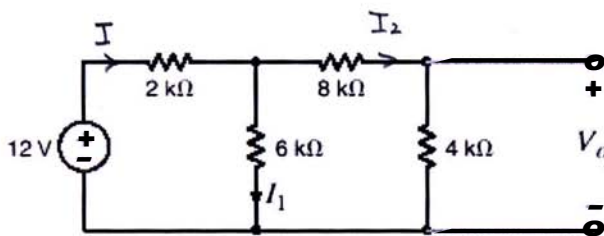

$$R = 12\text{ k} \parallel 6\text{ k}$$

$$R = 4\text{ k} \Omega$$

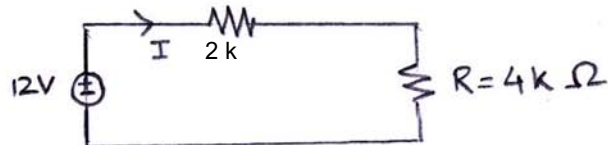

$$I = \frac{12}{2\text{ k} + 4\text{ k}}$$

$$I = 2\text{ mA}$$

$$I_1 = \left( \frac{8\text{ k} + 4\text{ k}}{8\text{ k} + 4\text{ k} + 6\text{ k}} \right) (2\text{ m})$$

$$I_1 = 1.33\text{ mA}$$

KCL:

$$I = I_1 + I_2$$

$$I_2 = 2\text{m} - 1.33\text{m}$$

$$I_2 = 0.667\text{mA}$$

$$V_o = I_2(4\text{k})$$

$$V_o = 0.667(4\text{k})$$

$$V_o = 2.67\text{V}$$

2.60 Find  $I_1$  and  $V_o$  in the circuit in Fig. P2.60.


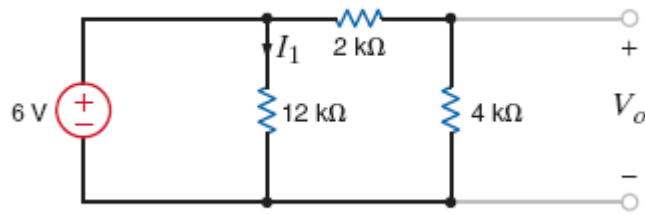


Figure P2.60

**SOLUTION:**

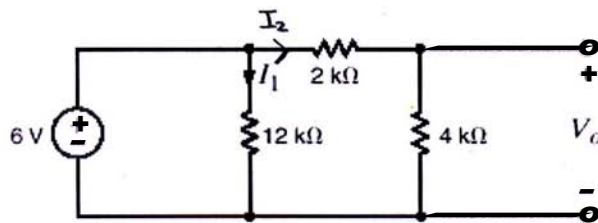

$$I_1 = \frac{6}{2k} = 0.5 \text{ mA}$$

$$I_2 = \frac{6}{2k+4k} = 1 \text{ mA}$$

$$V_o = I_2 (4k) = 1\text{m}(4k)$$

$$V_o = 4 \text{ V}$$

2.61 Find  $V_{ab}$  and  $V_{dc}$  in the circuit in Fig. P2.61.


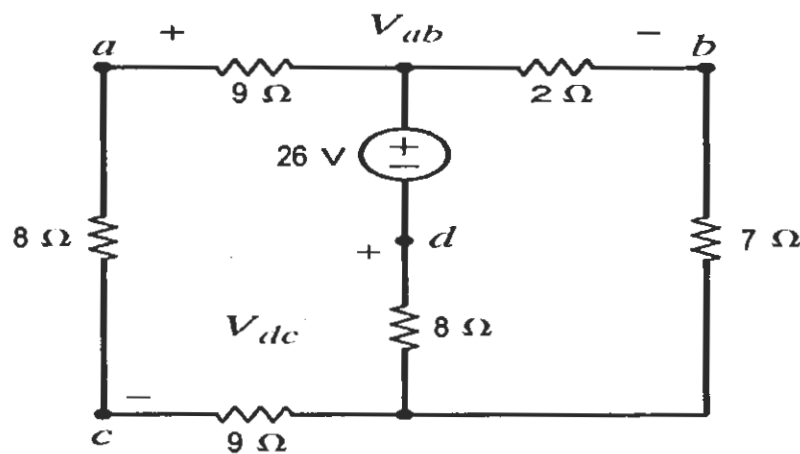



Figure P2.61

Solution: 2.61

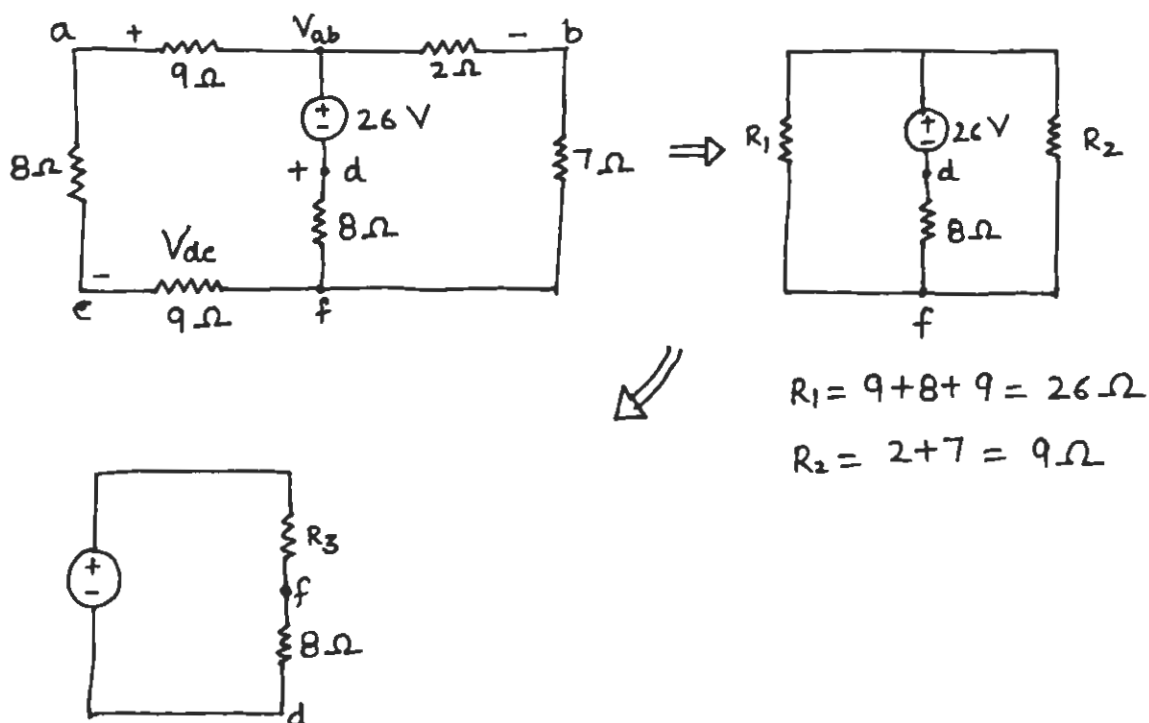



Now we have

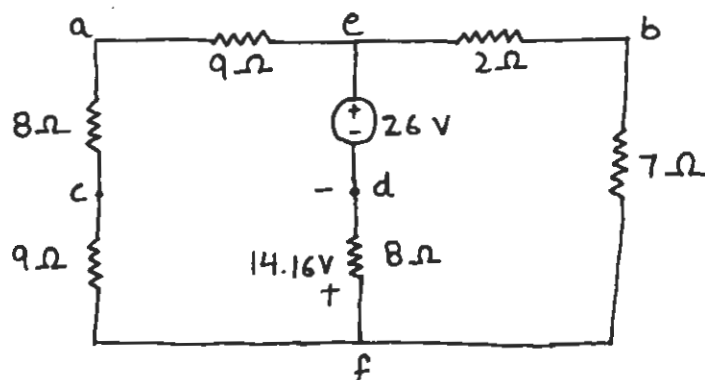

$$V_{ef} = (26 - 14.16) = 11.84 \text{ V}$$

$$V_{ea} = V_{ef} \left[ \frac{9}{9 + 8 + 9} \right] = 4.098 \text{ V}$$

$$V_{eb} = V_{ef} \left[ \frac{2}{2 + 7} \right] = 2.63 \text{ V}$$

$$V_{ab} = V_{ae} + V_{eb} = -4.098 + 2.63 = -1.468 \text{ V}$$

$$\boxed{V_{ab} = -1.47 \text{ V}}$$

$$V_{ef} = V_{ef} \left[ \frac{9}{9 + 8 + 9} \right] = 4.098 \text{ V}$$

$$V_{de} = V_{df} + V_{fe} = -14.16 + (-4.098) = -18.26 \text{ V}$$

$$\boxed{V_{de} = -18.3 \text{ V}}$$

2.62 Find  $V_1$  and  $I_A$  in the network in Fig P2.62.


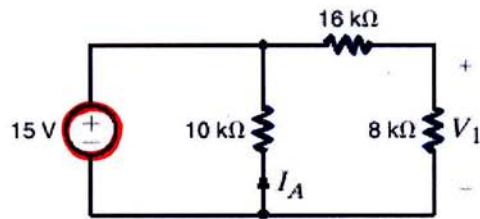


Figure P2.62

**SOLUTION:**

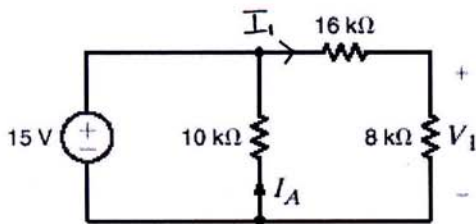

$$I_A = -\frac{15}{10K}$$

$$I_A = -1.5\text{mA}$$

$$I_1 = \frac{15}{16K+8K}$$

$$I_1 = 0.625\text{mA}$$

$$V_1 = I_1(8K) = (0.625\text{m})(8K)$$

$$V_1 = 5V$$

2.63 Find  $I_o$  in the network in Fig P2.63.


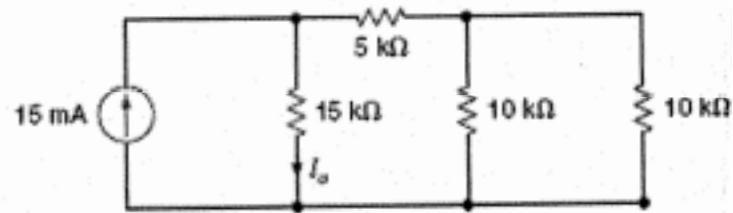


Figure P2.63

Solution: 2.63

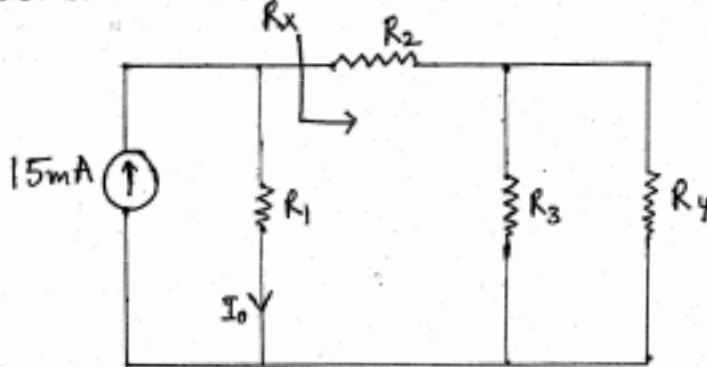

$$R_1 = 15 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 10 \text{ k}\Omega, R_4 = 10 \text{ k}\Omega$$

$$R_x = R_2 + (R_3 \parallel R_4) = 10 \text{ k}\Omega$$

$$I_o = 15 \times 10^{-3} \left[ \frac{R_x}{R_1 + R_x} \right]$$

$$\boxed{I_o = 6 \text{ mA}}$$

2.64 Determine  $I_o$  in the circuit in Fig. P2.64.


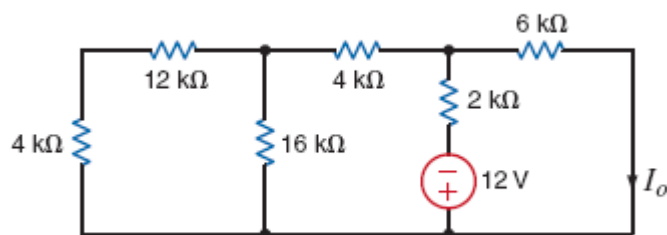



Figure P2.64

**SOLUTION:**

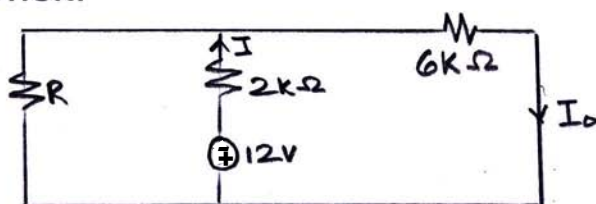

$$R = [(4k + 12k) \parallel 16k] + 4k$$

$$R = 8k + 4k = 12k \Omega$$

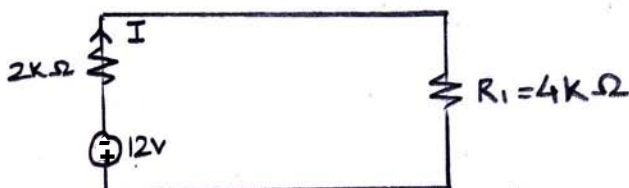

$$R_1 = 12k \parallel 6k$$

$$R_1 = 4k \Omega$$

$$I = \frac{-12}{2k + 4k} = -2 \text{ mA}$$

Current division:

$$I_o = \left( \frac{12k}{12k + 6k} \right) (-2 \text{ mA})$$

$$I_o = -1.33 \text{ mA}$$

2.65 Find  $V_1$  in the network in Fig P2.65.


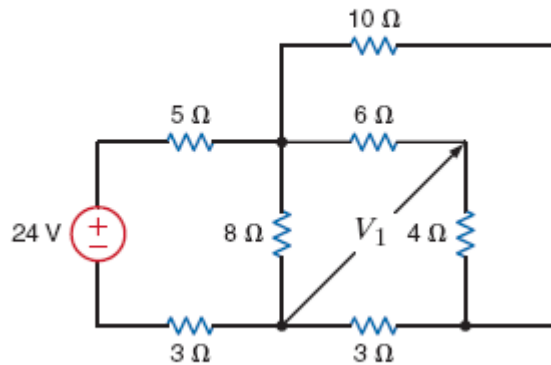



Figure P2.65

**SOLUTION:**

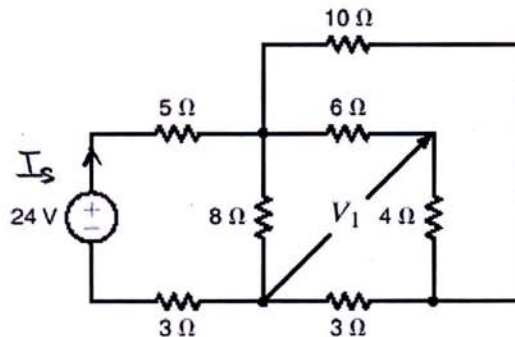


$$R_{eq} = \{ [10 \parallel (6+4)] + 3 \} \parallel 8$$
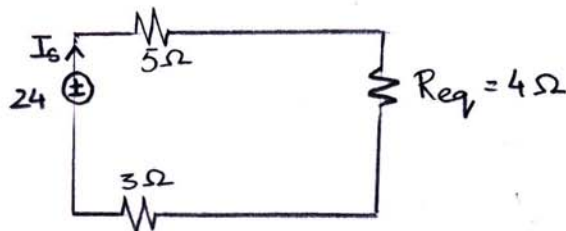
$$R_{eq} = (5+3) \parallel 8 = 4 \Omega$$



$$I_s = \frac{24}{5+4+3} = 2A$$

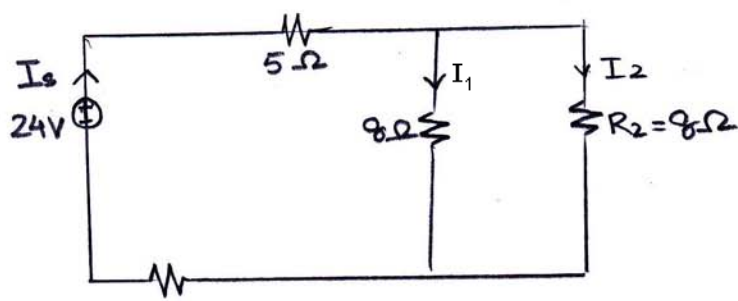


$$R_2 = [10 \parallel (6+4)] + 3$$

$$R_2 = 8\Omega$$

$$I_1 = \left(\frac{8}{8+8}\right)(2) = 1A$$

$$I_2 = I_1 = 1A$$

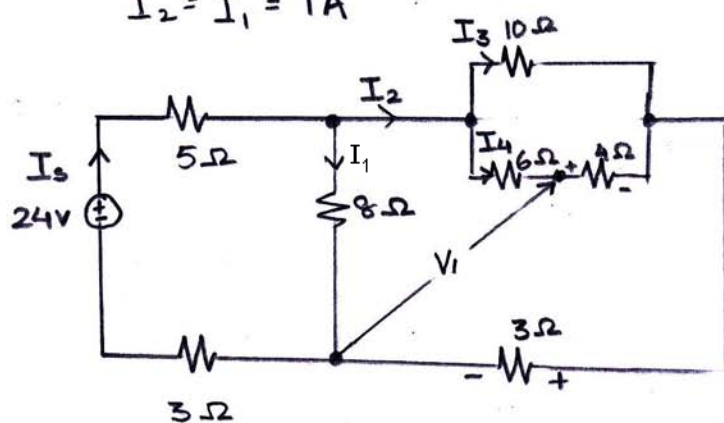

$$I_3 = \left(\frac{6+4}{6+4+10}\right) I_2$$

$$I_3 = 0.5A$$

$$I_4 = I_3 = 0.5A$$

KVL:

$$V_1 = I_4(4) + I_2(3)$$

$$V_1 = 0.5(4) + (1)(3)$$

$$V_1 = 5V$$

2.66 Determine  $V_o$  in the network in Fig. P2.66.


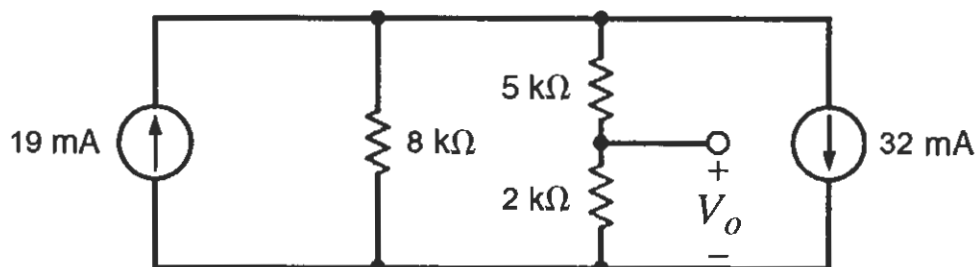


Figure P2.66

Solution: 2.66

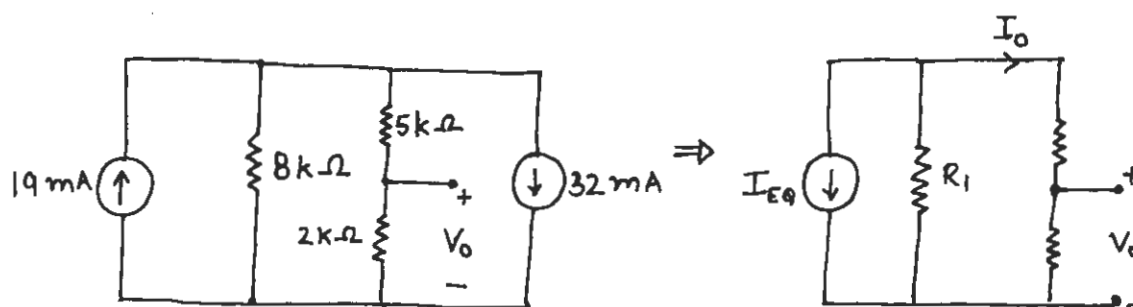

$$R_1 = 8 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega$$

$$I_{Eq} = (32 - 19) = 13 \text{ mA}$$

$$-I_o = I_{Eq} \left[ \frac{R_1}{R_1 + (R_2 + R_3)} \right] \Rightarrow I_o = -6.93 \text{ mA}$$

$$\begin{aligned} V_o &= I_o R_3 \\ &= -13.86 \text{ V} \end{aligned}$$

$$\boxed{V_o = -13.9 \text{ V}}$$

2.67 Find  $V_{ab}$  in the circuit in Fig P2.67.


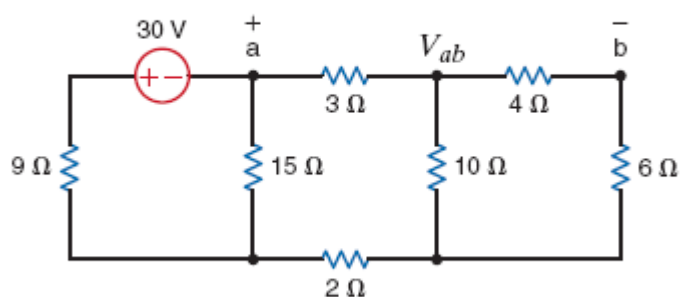



Figure P2.67

**SOLUTION:**

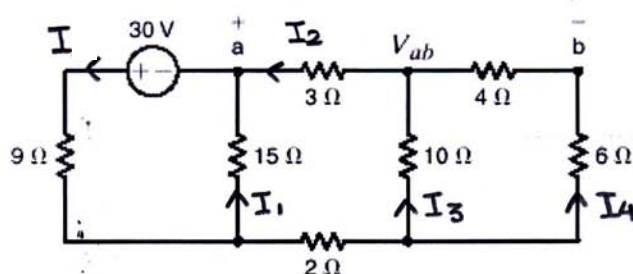

$$R_{eq} = \{[(4+6) \parallel 10] + 3 + 2\} \parallel 15$$
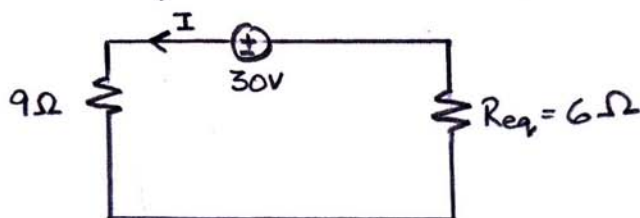
$$R_{eq} = (5+5) \parallel 15 = 6 \Omega$$



$$I = \frac{30}{9+6} = 2A$$

KVL around original circuit:

$$30 = 9I + 15I_1$$



$$15I_1 = 12$$

$$I_1 = \frac{4}{5} \text{ A}$$

KCL:

$$I = I_1 + I_2$$

$$I_2 = 2 - \frac{4}{5}$$

$$I_2 = \frac{6}{5} \text{ A}$$

$$I_4 = \left( \frac{10}{10+4+6} \right) (I_2)$$

$$I_4 = \frac{3}{5} \text{ A}$$

KVL:

$$V_{ab} + 3I_2 + 4I_4 = 0$$

$$V_{ab} = -3\left(\frac{6}{5}\right) - 4\left(\frac{3}{5}\right)$$

$$V_{ab} = -6 \text{ V}$$

2.68 Find  $V_{ab}$  in the network in Fig P2.68.


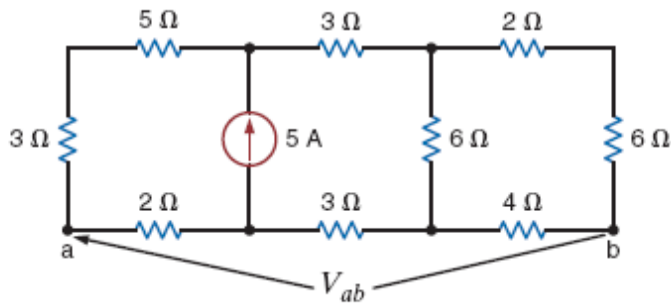



Figure P2.68

**SOLUTION:**

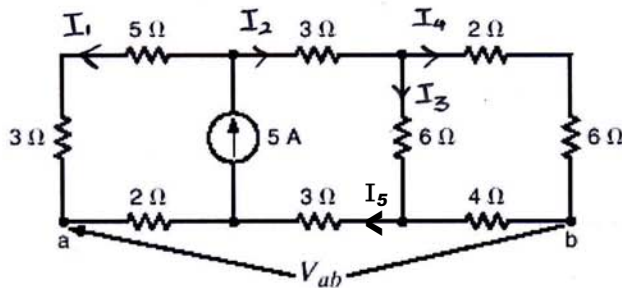

$$R_{eq} = (2 + 6 + 4 \parallel 6) + 6$$

$$R_{eq} = 10 \Omega$$

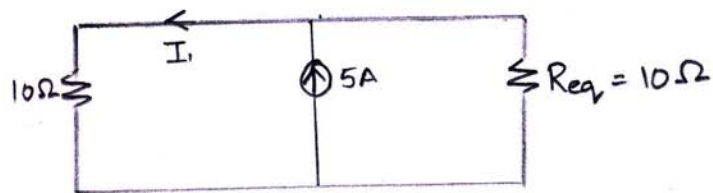

$$I_1 = \left( \frac{10}{10 + 10} \right) (5) = 2.5 \text{ A}$$

$$I_2 = I_1 = 2.5 \text{ A}$$

$$I_4 = \left( \frac{6}{6 + 2 + 6 + 4} \right) (I_2)$$

$$I_4 = 0.833 \text{ A}$$

$$I_5 = 2.5 \text{ A}$$

$$I_3 = I_5 - I_4$$

$$I_3 = 2.5 - 0.833$$

$$I_3 = 1.67 \text{ A}$$

KVL:

$$2I_1 = 3I_5 + 4I_4 + V_{ab}$$

$$V_{ab} = 2(2.5) - 3(2.5) - 4(0.833)$$

$$V_{ab} = -5.83 \text{ V}$$

2.69 Find  $I_1$ ,  $I_2$  and  $V_1$  in the circuit in Fig P2.69.



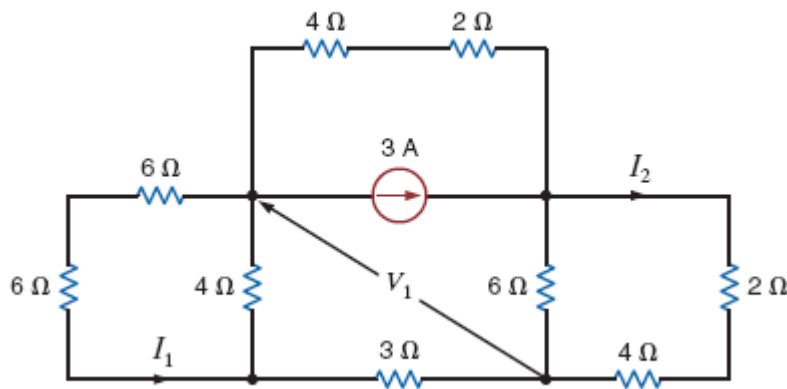


Figure P2.69

**SOLUTION:**

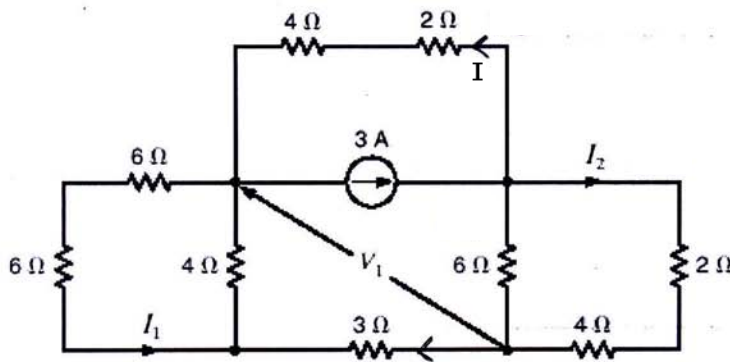
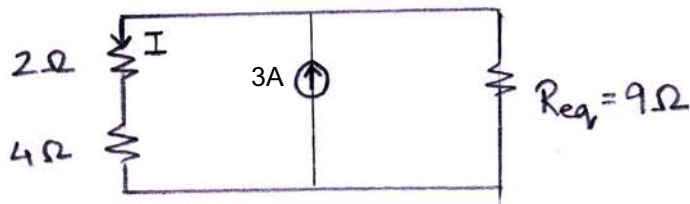
$$R_1 = [(2+4) \parallel 6] + 3 + [(6+6) \parallel 4] = 3 + 3 + 3 = 9 \Omega$$



$$I = \left( \frac{9}{9+2+4} \right) (3) = 1.8 \text{ A}$$

$$I_2 = \left( \frac{6}{6+2+4} \right) (3-I)$$

$$I_2 = 0.6 \text{ A}$$

$$I_1 = \left( \frac{4}{4+6+6} \right) (-3 + I)$$

$$I_1 = -0.3 \text{ A}$$

KVL:

$$2I + 4I + V_1 = 2I_2 + 4I_2$$

$$V_1 = 6I_2 - 6I$$

$$V_1 = 6(0.6) - 6(1.8)$$

$$V_1 = -7.2 \text{ V}$$

2.70 If  $V_o = 4\text{ V}$  in the network in Fig. P2.70, find  $V_s$ .

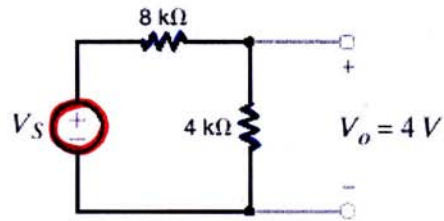


Figure P2.70

**SOLUTION:**

$$V_o = \left( \frac{4\text{ k}}{4\text{ k} + 8\text{ k}} \right) V_s$$

$$V_s = \left( \frac{4}{\frac{4\text{ k}}{4\text{ k} + 8\text{ k}}} \right) = 12\text{ V}$$

- 2.71 If the power absorbed by the 4-k $\Omega$  resistor in the circuit in Fig. P2.71 is 36 mW, find  $V_S$ .


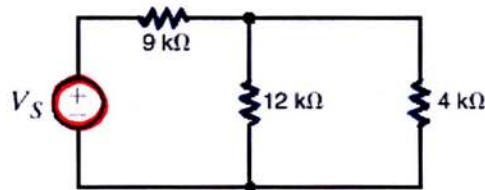


Figure P2.71

**SOLUTION:**

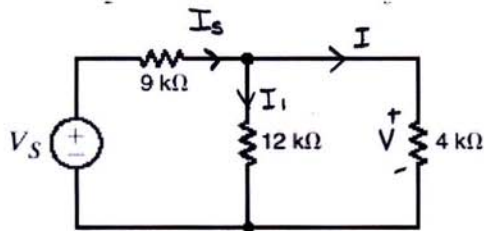

$$P_{4k} = 36\text{ mW}$$

$$P_{4k} = \frac{V^2}{R}$$

$$V = \sqrt{P_{4k} R}$$

$$V = 12\text{ V}$$

$$I_1 = \frac{V}{12k} = \frac{12}{12k}$$

$$I_1 = 1\text{ mA}$$

KCL:

$$I_S = I_1 + I$$

$$I_S = 1\text{ m} + 3\text{ m}$$

$$P_{4k} = I^2 R$$

$$I = \sqrt{\frac{P_{4k}}{R}}$$

$$I = \sqrt{\frac{36\text{ m}}{4k}} = 3\text{ mA}$$

$$I_s = 4\text{mA}$$

KVL:

$$V_s = I_s(9\text{k}) + V$$

$$V_s = 4\text{m}(9\text{k}) + 12$$

$$V_s = 48\text{V}$$



2.72 If  $I_o = 5 \text{ mA}$  in the circuit in Fig. P2.72, find  $I_s$ .


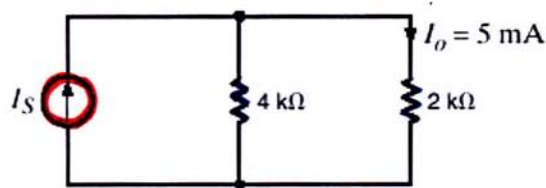


Figure P2.72

**SOLUTION:**

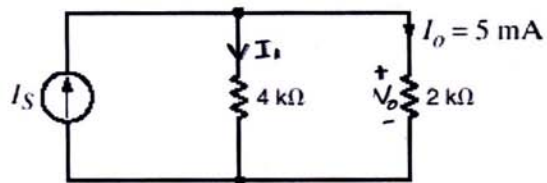

$$V_o = I_o(2\text{k}) = 5\text{m}(2\text{k}) = 10\text{V}$$

$$I_1 = \frac{10}{4\text{k}}$$

$$I_1 = 2.5\text{mA}$$

KCL:

$$I_s = I_1 + I_o$$

$$I_s = 2.5\text{m} + 5\text{m}$$

$$I_s = 7.5\text{mA}$$

2.73 If  $I_o = 2 \text{ mA}$  in the circuit in Fig. P2.73, find  $V_s$ .


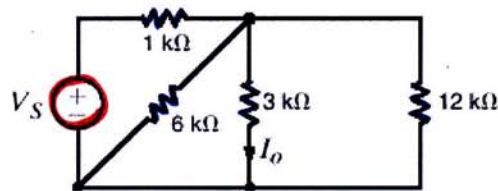


Figure P2.73

**SOLUTION:**

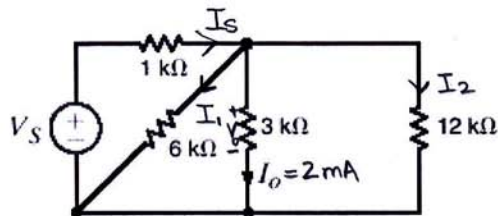

$$V_o = I_o (3\text{k}) = 2\text{m}(3\text{k}) = 6\text{V}$$

$$I_1 = \frac{6}{6\text{k}} = 1\text{mA}$$

$$I_2 = \frac{6}{12\text{k}} = 0.5\text{mA}$$

KCL:

$$I_s = I_1 + I_o + I_2 = 1\text{m} + 2\text{m} + 0.5\text{m}$$

$$I_s = 3.5\text{mA}$$

KVL:

$$V_s = 1\text{k}I_s + V_o$$

$$V_s = 1\text{k}(3.5) + 6$$

$$V_s = 9.5\text{V}$$

2.74 Find the value of  $V_s$  in the network in Fig. P2.74 such that the power supplied by the current source is 0.


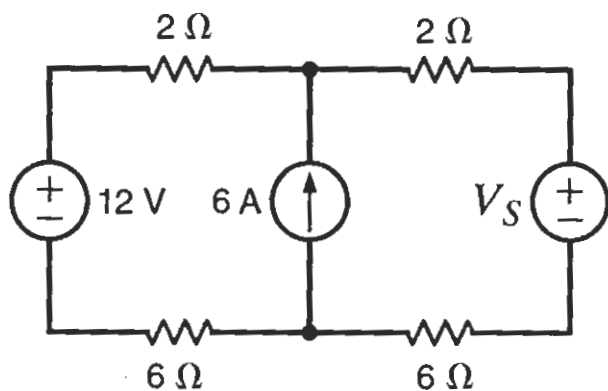


Figure P2.74

Solution: 2.74

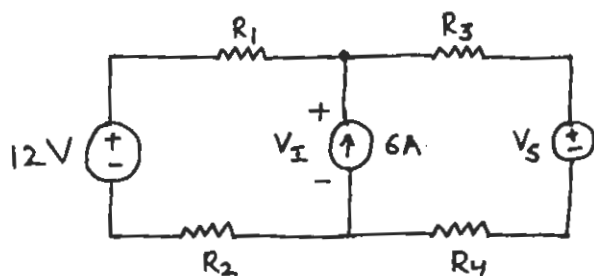

$$R_1 = 2\ \Omega, R_2 = 6\ \Omega, R_3 = 2\ \Omega, R_4 = 6\ \Omega$$

$$P_{I_s} = 6 V_I = 0 \Rightarrow V_I = 0$$

$$\text{KCL : } \frac{12}{R_1 + R_2} + \frac{V_s}{R_3 + R_4} + 6 = 0$$

$$\frac{12}{8} + \frac{V_s}{8} + 6 = 0$$

$$\boxed{V_s = -60.0\ \text{V}}$$

2.75 In the network in Fig. P2.75,  $V_1 = 12\text{ V}$ . Find  $V_s$ .



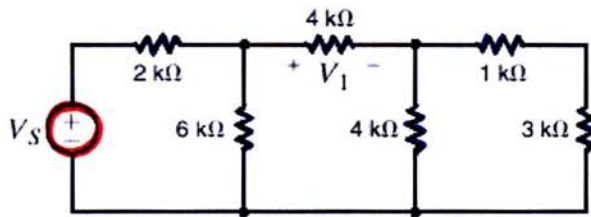


Figure P2.75

**SOLUTION:**

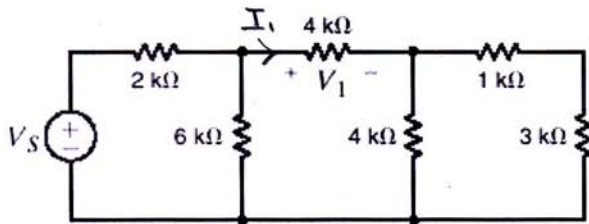
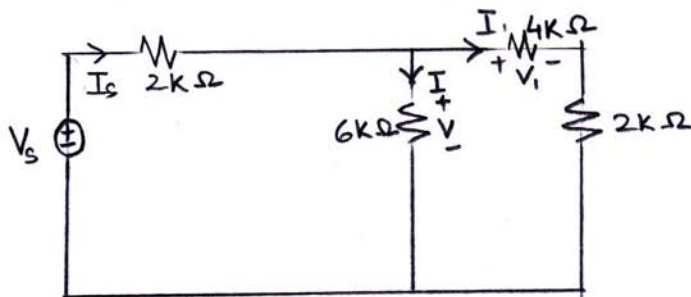
$$I_1 = \frac{V_1}{4\text{ k}} = \frac{12}{4\text{ k}} = 3\text{ mA}$$



$$R_2 = (1\text{ k} + 3\text{ k}) \parallel 4\text{ k}$$

$$R_2 = 2\text{ k}\Omega$$

$$V = I_1 (4\text{ k} + 2\text{ k}) = 3\text{ m}(6\text{ k}) = 18\text{ V}$$

$$I = \frac{V}{6\text{ k}} = \frac{18}{6\text{ k}} = 3\text{ mA}$$

KCL:

$$I_s = I + I_1 = 3\text{ m} + 3\text{ m} = 6\text{ mA}$$

KVL:

$$V_s = I_s (2\text{ k}) + V$$

$$V_s = 6m(2k) + 18$$

$$V_s = 30V$$

2.76 In the network in Fig. P2.76,  $V_o = 8\text{ V}$ . Find  $I_s$ .


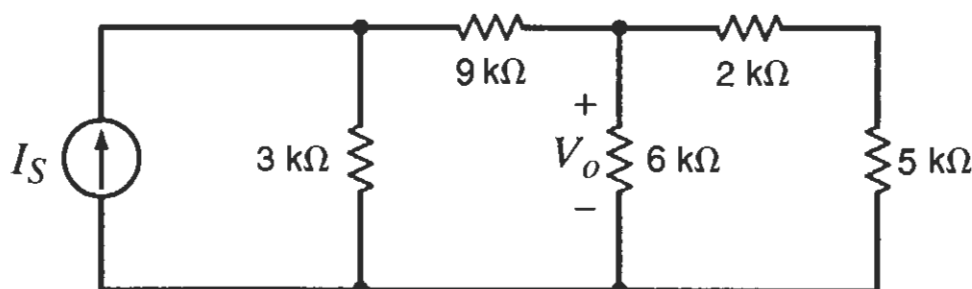


Figure P2.76

Solution: 2.76

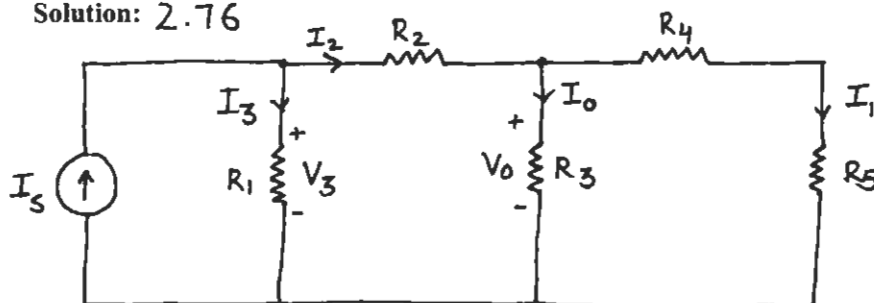

$$R_1 = 3\text{ k}\Omega, R_2 = 9\text{ k}\Omega, R_3 = 6\text{ k}\Omega, R_4 = 2\text{ k}\Omega, R_5 = 5\text{ k}\Omega$$

$$I_0 = V_o / R_3 = 8 / 6 = 1.33\text{ mA}$$

$$I_1 = \frac{V_o}{R_4 + R_5} = \frac{8}{7} = 1.143\text{ mA}$$

$$I_2 = I_0 + I_1 = (1.33 + 1.143)\text{ mA} = 2.473\text{ mA}$$

$$V_3 = I_2 R_2 + V_o = (2.473 \times 9) + 8 = 30.257\text{ V}$$

$$I_3 = \frac{V_3}{R_1} = 10.087\text{ mA}$$

$$I_s = I_2 + I_3 = 2.473 + 10.087 = 12.56\text{ mA}$$

$$\boxed{I_s = 12.6\text{ mA}}$$

2.77 In the circuit in Fig. P2.77,  $V_o = 2$  V. Find  $I_s$ .


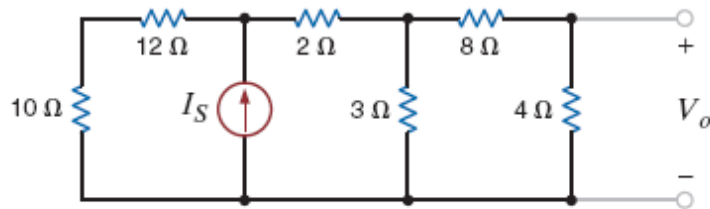


Figure P2.77

**SOLUTION:**

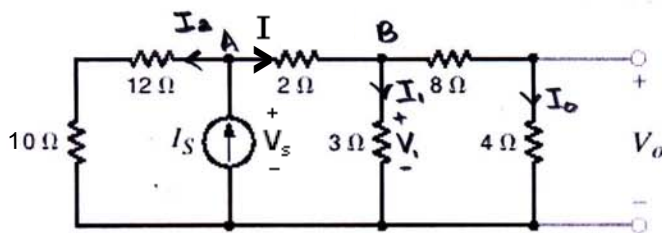

$$I_o = \frac{V_o}{4} = \frac{2}{4} = 0.5 \text{ A}$$

$$V_1 = I_o(12) = 0.5(12) = 6 \text{ V}$$

$$I_1 = \frac{V_1}{3} = \frac{6}{3} = 2 \text{ A}$$

KCL at B:

$$I = I_1 + I_o$$

$$I = 2 + 0.5 = 2.5 \text{ A}$$

KVL:

$$V_s = I(2) + V_1$$

$$V_s = 2.5(2) + 6$$

$$V_s = 11 \text{ V}$$

$$I_2 = \frac{V_s}{10+12} = \frac{11}{22} = 0.5A$$

KCL at A:

$$I_s = I + I_2 = 2.5 + 0.5$$

$$I_s = 3A$$



2.78 Find the value of  $V_1$  in the network in Fig. P2.78 such that  $V_a = 0$ .


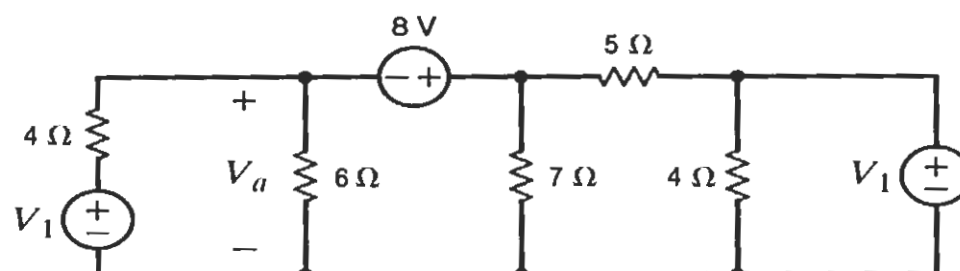


Figure P2.78

Solution: 2.78

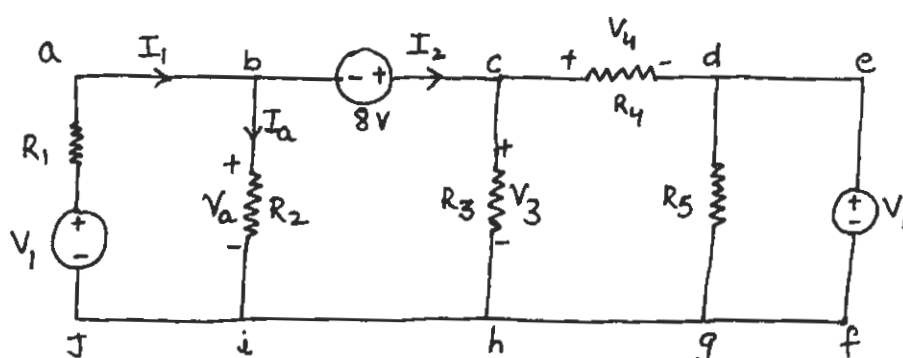

$$R_1 = 4\ \Omega, R_2 = 6\ \Omega, R_3 = 7\ \Omega, R_4 = 5\ \Omega, R_5 = 4\ \Omega$$

$$I_1 = I_a + I_2 \Rightarrow I_1 = I_2 \quad (\text{By Ohm's law, if } V_a = 0, I_a = 0)$$

$$I_1 = \frac{V_1}{R_1} = \frac{V_1}{4}$$

$$I_2 = \frac{V_3}{R_3} + \frac{V_4}{R_4} = \frac{V_3}{7} + \frac{V_4}{5}$$

Applying KVL in loop bchib

$$8 + 0 - V_3 = 0$$

$$V_3 = 8\text{ V}$$

Applying KVL in loop cdefghc

$$-V_3 + V_4 + V_1 = 0$$

$$V_4 = 8 - V_1$$

$$\text{So, } I_2 = \frac{8}{7} + \frac{8 - V_1}{5}$$

$$I_1 = I_2 = \frac{8}{7} + \frac{8 - V_1}{5}$$

$$\text{So, } \frac{V_1}{4} = \frac{8}{7} + \frac{8 - V_1}{5}$$

$$V_1 = 6.095 \text{ V}$$

$$\boxed{V_1 = 6.10 \text{ V}}$$

2.79 If  $V_1 = 3\text{V}$  in the circuit in Fig. P2.79, find  $I_s$ .


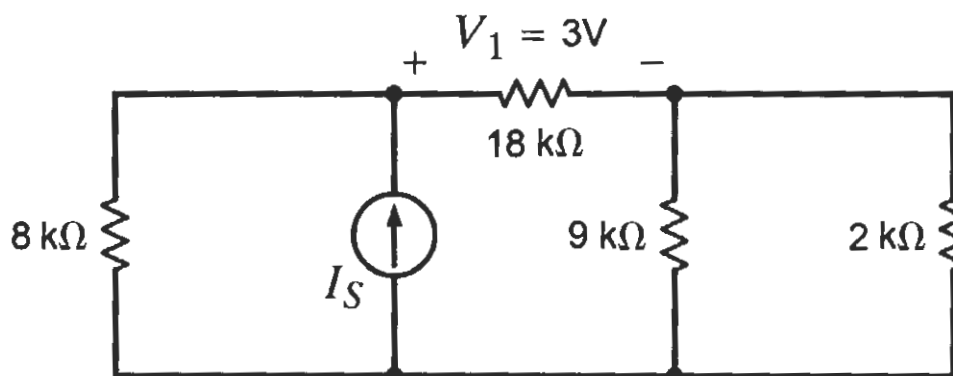


Figure P2.79

Solution: 2.79

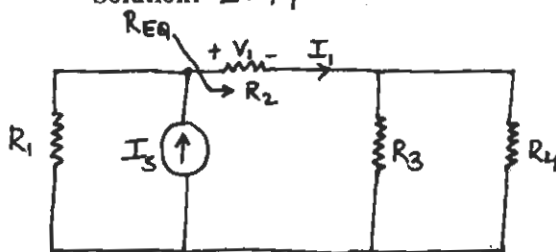

$$R_1 = 8\text{ k}\Omega, R_2 = 18\text{ k}\Omega, R_3 = 9\text{ k}\Omega, R_4 = 2\text{ k}\Omega$$

$$V_1 = 3\text{V}$$

$$R_{EQ} = R_2 + (R_3 \parallel R_4) = 19.636 = 19.64\text{ k}\Omega$$

$$I_1 = \frac{V_1}{R_2} = \frac{3}{18} = \frac{1}{6}\text{ mA}$$

$$I_1 = I_s \left[ \frac{R_1}{R_1 + R_{EQ}} \right]$$

$$I_s = 0.576\text{ mA}$$

2.80 In the network in Fig. P2.80,  $V_1 = 16$  V. Find  $V_S$ .


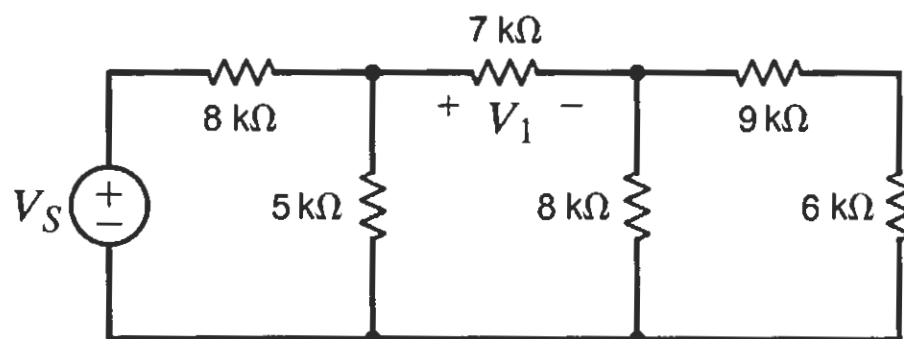


Figure P2.80

Solution: 2.80

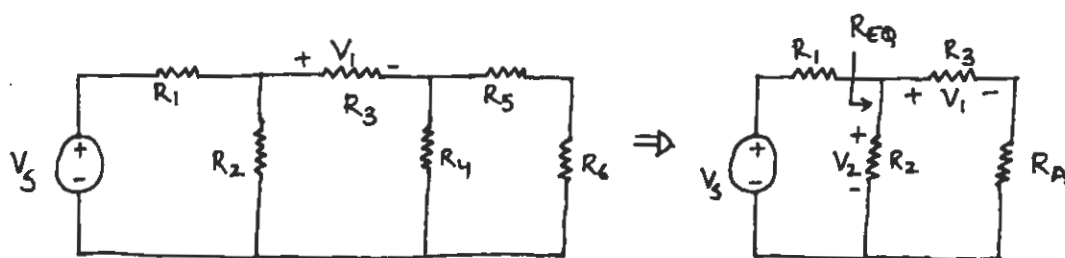

$$V_1 = 16 \text{ V}, R_1 = 8 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 7 \text{ k}\Omega, R_4 = 8 \text{ k}\Omega, \\ R_5 = 9 \text{ k}\Omega, R_6 = 6 \text{ k}\Omega$$

$$R_A = R_4 \parallel (R_5 + R_6) = 5.217 \text{ k}\Omega$$

$$R_{EQ} = R_2 \parallel (R_3 + R_A) = 3.548 \text{ k}\Omega$$

$$V_1 = V_2 \left[ \frac{R_3}{R_3 + R_A} \right] \Rightarrow V_2 = 27.925 \text{ V}$$

$$V_2 = V_S \left[ \frac{R_{EQ}}{R_{EQ} + R_1} \right] \Rightarrow V_S = 90.89 \text{ V}$$

$$\boxed{V_S = 90.9 \text{ V}}$$

2.81 Given that  $V_o = 4\text{ V}$  in the network in Fig. P2.81, find  $V_S$ .


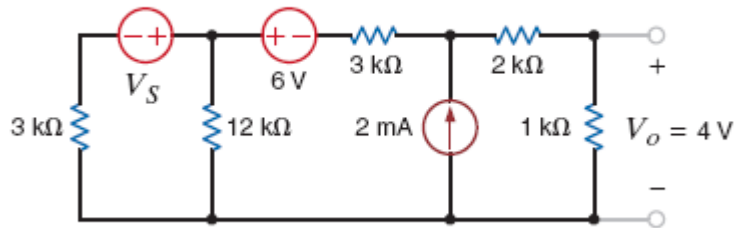


Figure P2.81

**SOLUTION:**

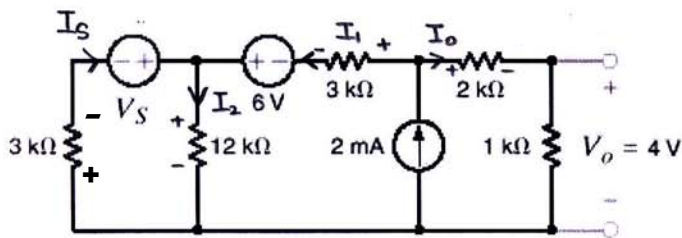

$$I_o = \frac{V_o}{1k} = \frac{4}{1k} = 4\text{ mA}$$

$$I_1 + I_o = 2\text{ m}$$

$$I_1 = 2\text{ m} - 4\text{ m}$$

$$I_1 = -2\text{ mA}$$

KVL:

$$4 + I_o(2k) + 6 = I_1(3k) + I_2(12k)$$

$$(12k)I_2 = 4 + 4\text{ m}(2k) + 6 - (-2\text{ m})(3k)$$

$$I_2 = 2\text{ mA}$$

KCL:

$$I_s + I_1 = I_2$$

$$I_s = I_2 - I_1$$

$$I_s = 2\text{m} - (-2\text{m})$$

$$I_s = 4\text{mA}$$

KVL:

$$V_s = 3\text{K}I_s + 12\text{K}I_2$$

$$V_s = 3\text{K}(4\text{m}) + 12\text{K}(2\text{m})$$

$$V_s = 36\text{V}$$

- 2.82 Given that  $I_x = 4$  A, find  $R$ ,  $V_{ab}$ , and the power supplied by the 10-A current source in the network in Fig. P2.82.


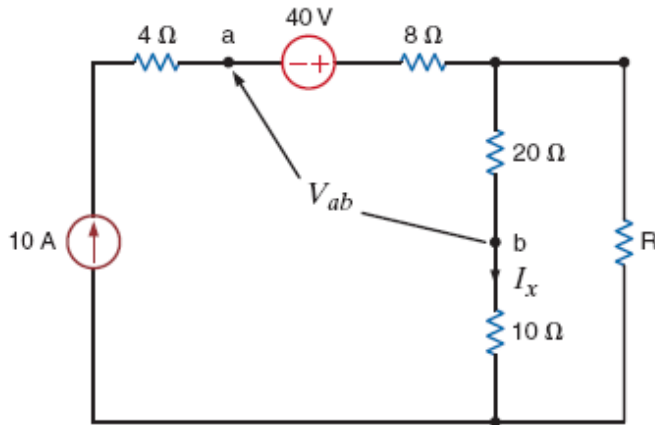


Figure P2.82

**SOLUTION:**

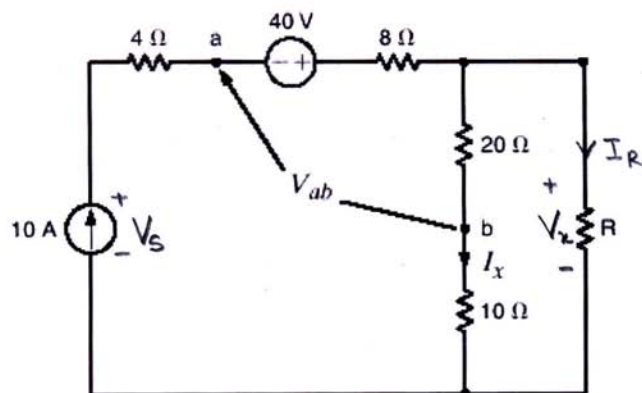

$$V_R = I_x(20 + 10) = 4(20 + 10)$$

$$V_R = 120\text{ V}$$

KCL:

$$10 = I_x + I_R$$

$$I_R = 10 - 4$$

$$I_R = 6\text{ A}$$

$$V_x = I_R R$$

$$R = \frac{V_x}{I_R}$$

$$R = \frac{120}{6}$$

$$R = 20\Omega$$

KVL:

$$V_{ab} + 40 = 10(8) + I_x(20)$$

$$V_{ab} = 80 - 40 + (4)(20)$$

$$V_{ab} = 120V$$

KVL:

$$V_s + 40 = 10(4) + 10(8) + I_R R$$

$$V_s = -40 + 40 + 80 + 6(20)$$

$$V_s = 200V$$

$$P_{10A} = V_s(10) = 200(10)$$

$$P_{10A} = 2KW$$



2.83 Find, the value of  $V_x$  in the network in Fig. P2.83 such that the 8-A current source supplies 48 W.


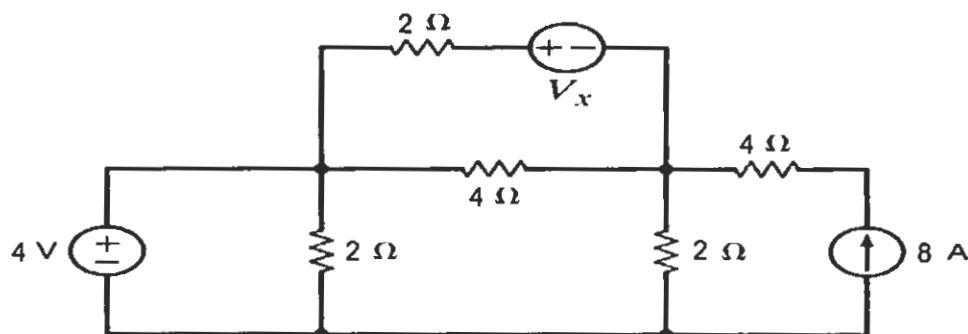


Figure P2.83

Solution: 2.83

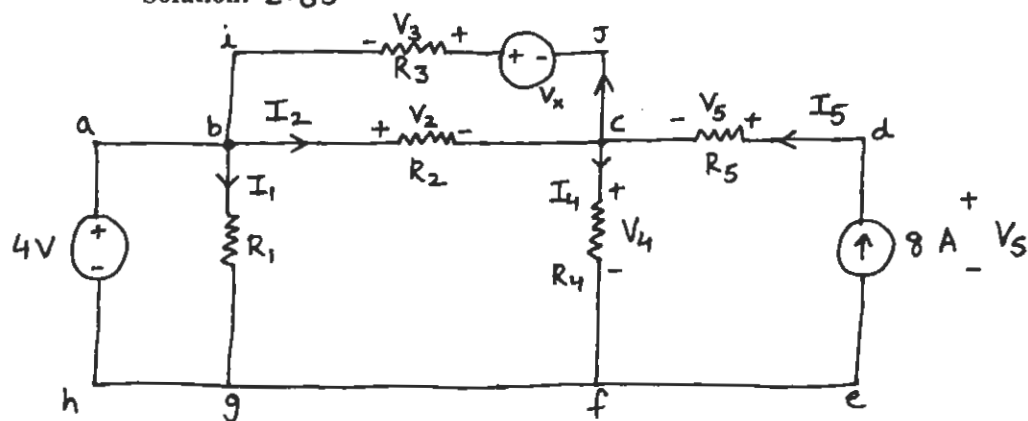

$$R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 2\Omega, R_4 = 2\Omega, R_5 = 4\Omega$$

$$P_{8A} = (V_5)(8) = 48 \Rightarrow V_5 = 6V$$

$$V_5 = R_5 I_5 = 32V$$

$$V_5 = V_5 + V_4 \Rightarrow V_4 = -V_5 + V_5 \Rightarrow V_4 = -26V$$

$$I_4 = \frac{V_4}{R_4} = -13A$$

KVL for loop a b c f g h a

$$-4 + V_2 + V_4 = 0$$

$$V_2 = 4 - V_4 = 30V$$

$$I_2 = \frac{V_2}{R_2} = 7.5A$$

KCL at node c:

$$I_2 + I_5 = I_3 + I_4$$

$$\therefore I_3 = I_2 + I_5 - I_4$$

$$= 7.5 + 8 + 13$$

$$I_3 = 28.5 \text{ A}$$

$$V_3 = R_3 I_3 = 57 \text{ V}$$

$$\begin{aligned} V_x &= V_3 + V_2 \\ &= 57 + 30 \\ &= 87 \text{ V} \end{aligned}$$

$$\boxed{V_x = 87 \text{ V}}$$

- 2.84 If the power absorbed by the 6-A current source in the circuit in Fig. P2.84 is 144 W, find  $V_S$  and the power supplied by the 24-V voltage source.


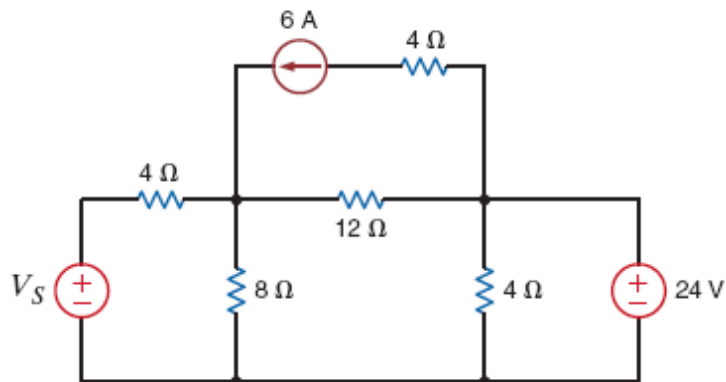


Figure P2.84

**SOLUTION:**

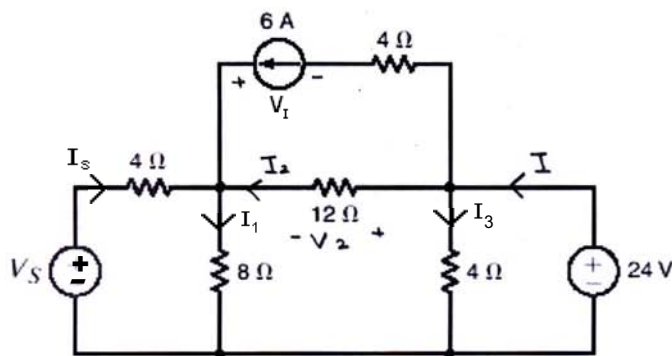

$$P_{6A} = V_1(6)$$

$$V_1 = \frac{P_{6A}}{6} = \frac{144}{6} = 24 \text{ V}$$

$$V_1 = 24 \text{ V}$$

$$V_1 - 6A(4) = I_2(12)$$

$$I_2(12) = 0$$

$$I_2 = 0 \text{ A}$$

KVL:

$$24 + V_1 = 6(4) + 8I_1$$

$$8I_1 = 24 + 24 - 24$$

$$I_1 = 3A$$

KCL:

$$I_s + 6 = I_1$$

$$I_s = 3 - 6$$

$$I_s = -3A$$

KVL:

$$V_s = I_s(4) + I_1(8)$$

$$V_s = -3(4) + (3)(8)$$

$$V_s = 12V$$

KVL:

$$V_2 + V_1 = 4(6)$$

$$V_2 = 0V$$

$$V_2 = I_2(12)$$

$$I_2 = 0A$$

$$I_3 = \frac{24}{4} = 6A$$

KCL:

$$I = I_3 + I_2 + 6$$

$$I = 6 + 0 + 6$$

$$I = 12A$$

$$P_{24V} = 24(I) = 24(12)$$

$$P_{24V} = 288W$$

2.85 Given  $I_0 = 8\text{mA}$  in the circuit in Fig. P2.85, find  $I_A$ .


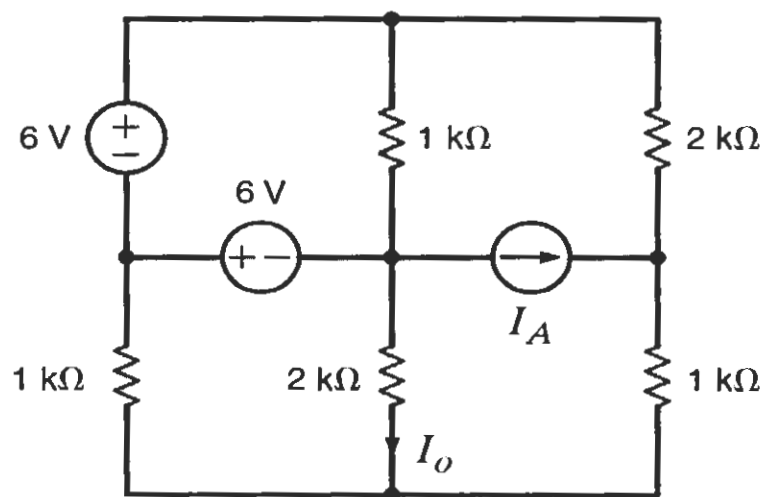


Figure P2.85

Solution: 2.85

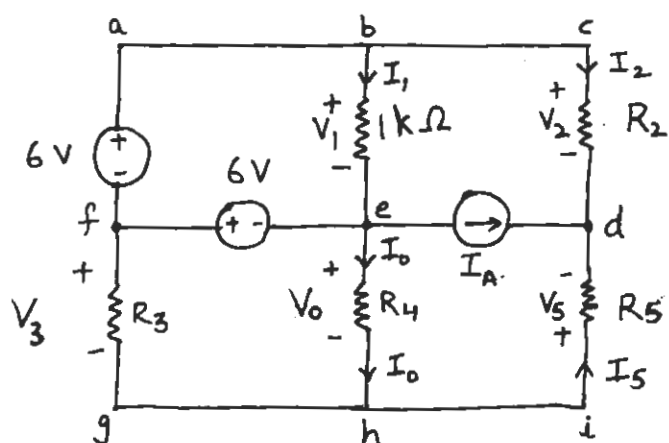

$$R_1 = 1\text{ k}\Omega, R_2 = 2\text{ k}\Omega, R_3 = 1\text{ k}\Omega, R_4 = 2\text{ k}\Omega, R_5 = 1\text{ k}\Omega$$

$$V_0 = R_4 I_0 = 16\text{ V}$$

$$V_3 = 6 + V_0 = 22\text{ V}$$

$$I_3 = V_3 / R_3 = 22\text{ mA}$$

$$I_5 = I_3 + I_0 = 30\text{ mA}$$

$$V_1 = 6 + 6 = 12 \text{ V}$$

$$I_1 = \frac{V_1}{R_1} = 12 \text{ mA}$$

KVL for the loop abcdihgfa

$$V_2 = 6 + I_3 R_3 + I_5 R_5$$

$$V_2 = 58 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = 29 \text{ mA}$$

$$I_A = -I_2 - I_5$$

$$\Rightarrow \boxed{I_A = -59 \text{ mA}}$$

2.86 Given  $I_o = 2 \text{ mA}$  in the network in Fig. P2.86, find  $V_A$ .


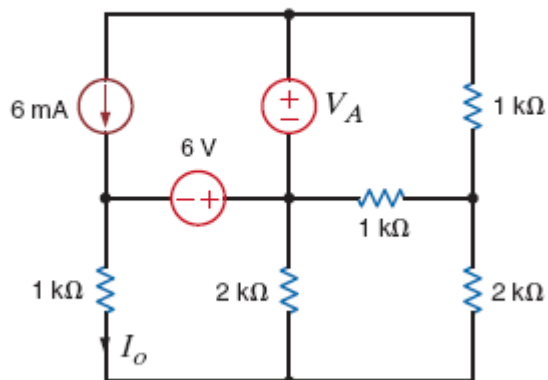


Figure P2.86

**SOLUTION:**

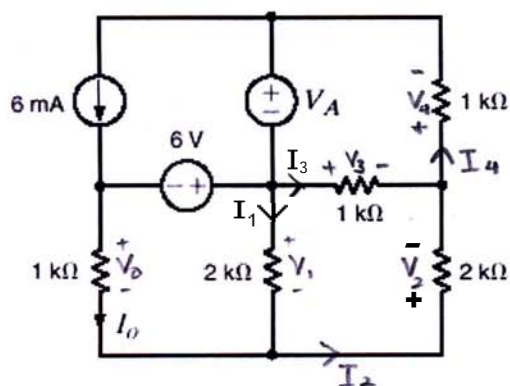

$$V_o = I_o (1k) = 2m(1k) = 2V$$

KVL:

$$V_1 = V_o + 6$$

$$I_1 = \frac{V_1}{2k}$$

$$V_1 = 2 + 6 = 8V$$

$$I_1 = \frac{8}{2k} = 4mA$$

KCL:

$$I_o + I_1 = I_2$$

$$I_2 = 2m + 4m = 6mA$$



$$V_2 = I_2(2k) = 6m(2k) = 12V$$

KVL:

$$V_1 + V_2 = V_3$$

$$V_3 = 8 + 12 = 20V$$

$$I_3 = \frac{V_3}{1k} = \frac{20}{1k} = 20mA$$

KCL:

$$I_2 + I_3 = I_4$$

$$I_4 = 6m + 20m = 26mA$$

$$V_4 = I_4(1k) = 26m(1k) = 26V$$

KVL:

$$V_A + V_4 + V_3 = 0$$

$$V_A = -26 - 20$$

$$V_A = -46V$$

2.87 Given  $V_o$  in the network in Fig. P2.87, find  $I_A$ .


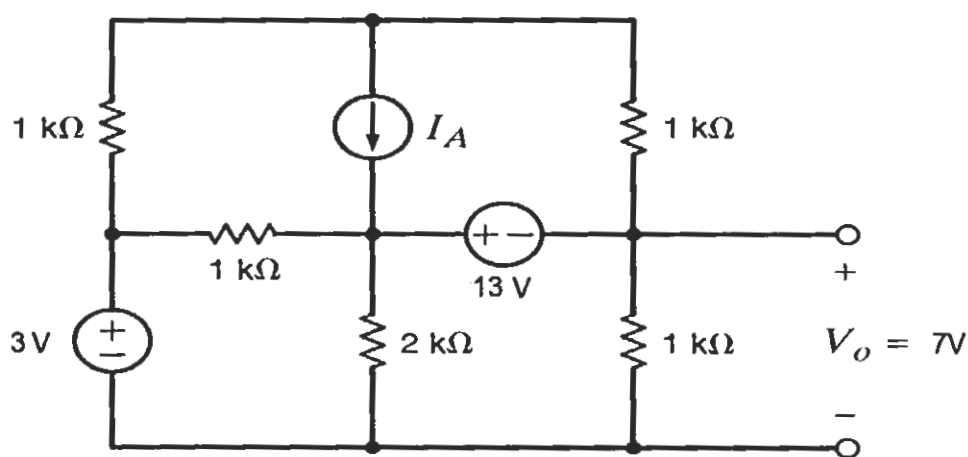


Figure P2.87

Solution: 2.87

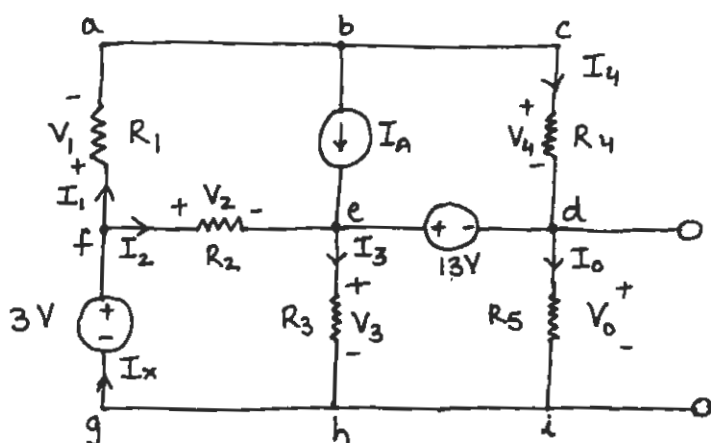

$$R_1 = 1 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega, R_5 = 1 \text{ k}\Omega$$

$$V_o = 7 \text{ V}$$

$$I_o = V_o / R_5 = 7 \text{ mA}$$

$$V_3 = 13 + V_o = 20 \text{ V}$$

$$I_3 = V_3 / R_3 = 10 \text{ mA}$$

$$I_x = I_3 + I_o = 17 \text{ mA}$$

$$V_2 = 3 - V_3 = -17 \text{ V}$$

$$I_2 = V_2 / R_2 = -17 \text{ mA}$$

$$I_1 = I_x - I_2 = 34 \text{ mA}$$

$$V_1 = R_1 I_1 = 34 \text{ V}$$

KVL for the loop a b c d i h g f a  
 $\Rightarrow V_4 + V_0 + V_1 = 3$

$$V_4 = 3 - V_0 - V_1$$

$$= -38 \text{ V}$$

$$I_4 = V_4 / R_4 = -38 \text{ mA}$$

$$I_A + I_4 = I_1$$

So,  $I_A = I_1 - I_4$   
 $= 72 \text{ mA}$

$$\boxed{I_A = 72 \text{ mA}}$$

- 2.88 If the power supplied by the 2-A current source is 40 W, find  $V_S$  and the power absorbed by the 5-V source in the network in Fig. P2.88.


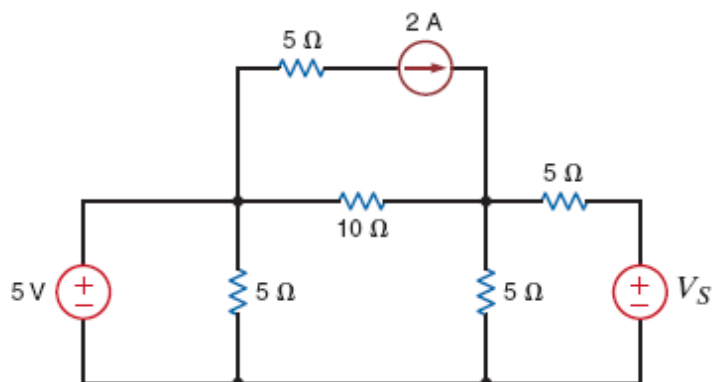


Figure P2.88

**SOLUTION:**

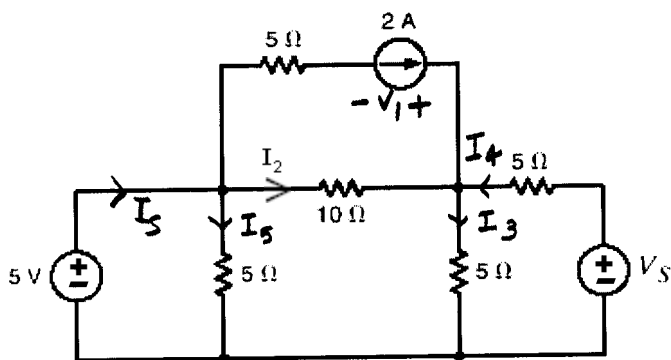

$$P_{2A} = V_1(2)$$

$$V_1 = \frac{P_{2A}}{2} = \frac{40}{2}$$

$$V_1 = 20V$$

$$\text{KVL: } 10I_2 + V_1 = 5(2)$$

$$I_2 = -1A$$

$$\text{KVL: } 5 + V_1 = 5(2) + I_3(5)$$

$$5I_3 = 5 + 20 - 10$$

$$I_3 = 3A$$

$$\text{KCL: } 2 + I_2 + I_4 = I_3$$

$$2 - 1 + I_4 = 3$$

$$I_4 = 2 \text{ A}$$

$$\text{KVL: } V_s = 5I_4 + 5I_3$$

$$V_s = 5(2) + 5(3)$$

$$V_s = 25 \text{ V}$$

$$\text{KCL: } I_s = I_2 + I_5 + 2$$

$$I_5 = \frac{5}{5} = 1 \text{ A}$$

$$I_s = -1 + 1 + 2$$

$$I_s = 2 \text{ A}$$

$$P_{5V} = I_s(5) = 2(5)$$

$$P_{5V} = 10 \text{ W}$$

2.89 The 40-V source in the circuit in Fig. P2.89 is absorbing 80 W of power. Find  $V_x$ .


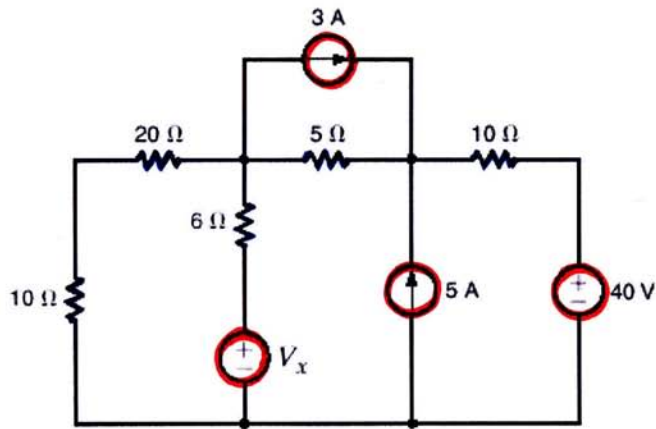


Figure P2.89

**SOLUTION:**

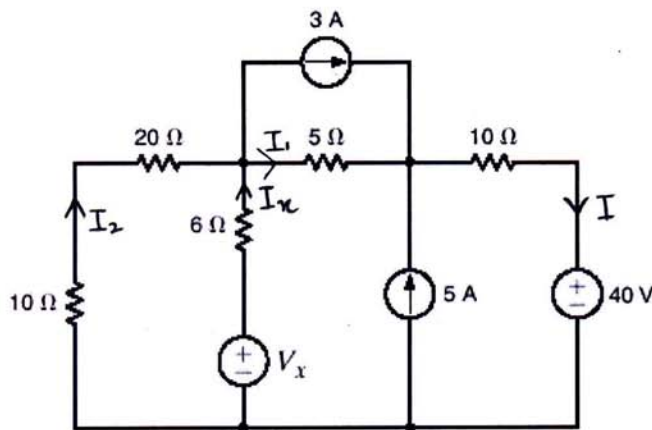

$$P_{40} = 40(I)$$

$$I = \frac{80}{40} = 2 \text{ A}$$

KCL:

$$I_1 + 3 + 5 = I$$

$$I_1 = 2 - 3 - 5$$

$$I_1 = -6 \text{ A}$$

KVL:

$$10I_2 + 20I_2 + 5I_1 + 10I + 40 = 0$$

$$30I_2 = -40 - 5I_1 - 10I$$

$$30I_2 = -40 - 5(-6) - 10(2)$$

$$I_2 = -1A$$

KCL:  $I_2 + I_x = I_1 + 3$

$$I_x = -6 + 3 - (-1)$$

$$I_x = -2A$$


KVL:

$$V_x = 6I_x + 5I_1 + 10I + 40$$

$$V_x = 6(-2) + 5(-6) + 10(2) + 40$$


$$V_x = 18V$$

**2.90** Find the value of  $V_x$  in the circuit in Fig. P2.90 such that the power supplied by the 6-A source is 54 W.

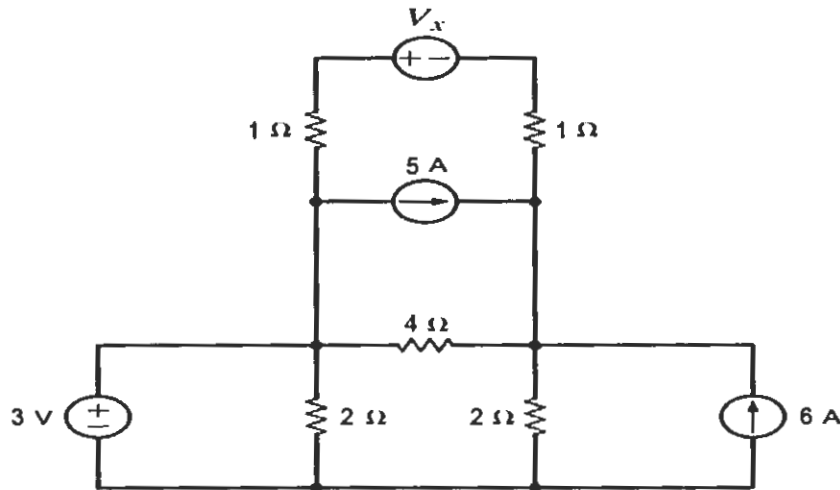

**Figure P2.90**

**Solution:** 2.90

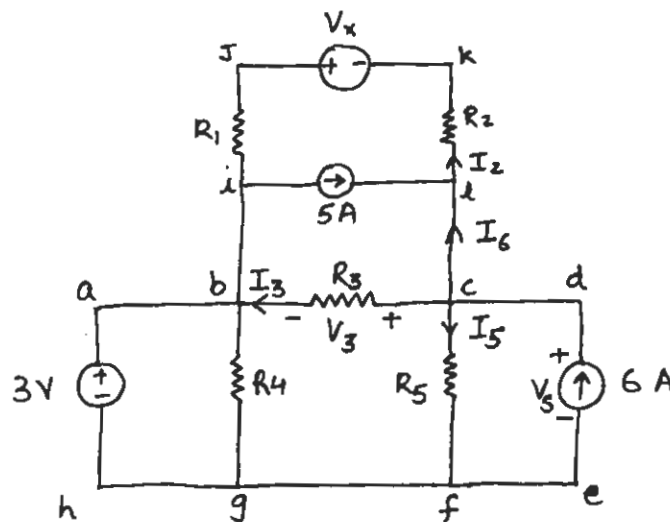

$$R_1 = 1\ \Omega, R_2 = 1\ \Omega, R_3 = 4\ \Omega, R_4 = 2\ \Omega, R_5 = 2\ \Omega$$

$$P_{6A} = 54 = 6V_5 \Rightarrow V_5 = 9\text{ V}$$

$$I_5 = \frac{V_5}{R_5} = 4.5\text{ A}$$



KVL for loop abcdefgha

$$V_3 = V_5 - 3 = 6 \text{ V}$$

$$I_3 = V_3 / R_3 = 1.5 \text{ A}$$

KCL at C:

$$I_6 + I_3 + I_5 = 6$$

$$I_6 = 6 - I_3 - I_5 = 0$$

KCL at d:

$$I_2 = I_6 + 5 = 5 \text{ mA}$$

KVL for loop bijkdcba

$$V_3 + V_x = I_2 R_2 + I_2 R_1$$

$$V_x = I_2 R_2 + I_2 R_1 - V_3$$

$$\boxed{V_x = 4 \text{ V}}$$

2.91 Given that  $V_1 = 4\text{ V}$ , find  $V_A$  and  $R_B$  in the circuit in Fig. P2.91.


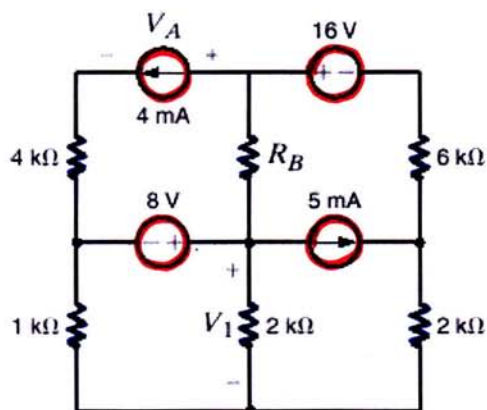


Figure P2.91

**SOLUTION:**

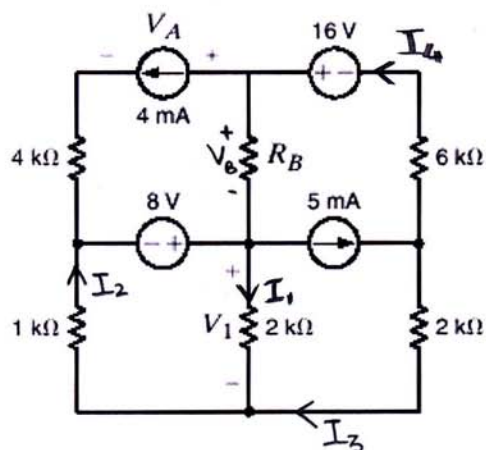

$$V_1 = I_1(2\text{k})$$

$$I_1 = \frac{4}{2\text{k}} = 2\text{ mA}$$

KVL:

$$V_1 + 1\text{k}I_2 = 8$$

$$I_2 = \frac{8 - 4}{1\text{k}} = 4\text{ mA}$$

KCL:

$$I_1 + I_3 = I_2$$

$$I_3 = 4\text{m} - 2\text{m}$$

$$I_3 = 2\text{mA}$$

KCL:

$$I_3 + I_4 = 5\text{mA}$$

$$I_4 = 3\text{mA}$$

KCL:

$$I_4 = I_B + 4\text{m}$$

$$I_B = -1\text{mA}$$

KVL:

$$2\text{K}I_3 + 16 = 6\text{K}I_4 + V_B + V_1$$

$$V_B = 2\text{K}(2\text{m}) + 16 - 6\text{K}(3\text{m}) - 4$$

$$V_B = -2\text{V}$$

$$V_B = I_B R_B$$

$$R_B = \frac{-2}{-1\text{m}} = 2\text{K}\Omega$$

KVL:

$$8 + V_B = V_A + 4k(4m)$$

$$V_A = 8 - 2 - 4k(4m)$$

$$V_A = -10V$$

2.92 Find the power absorbed by the network in Fig. P2.92.


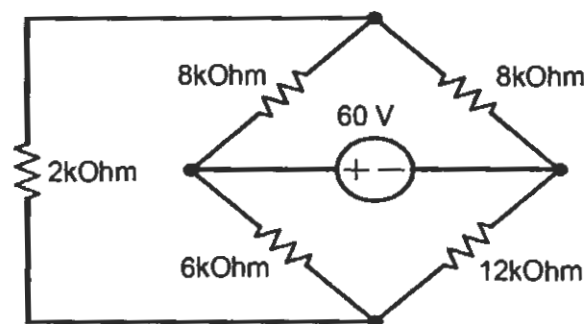


Figure P2.92

Solution: 2.92

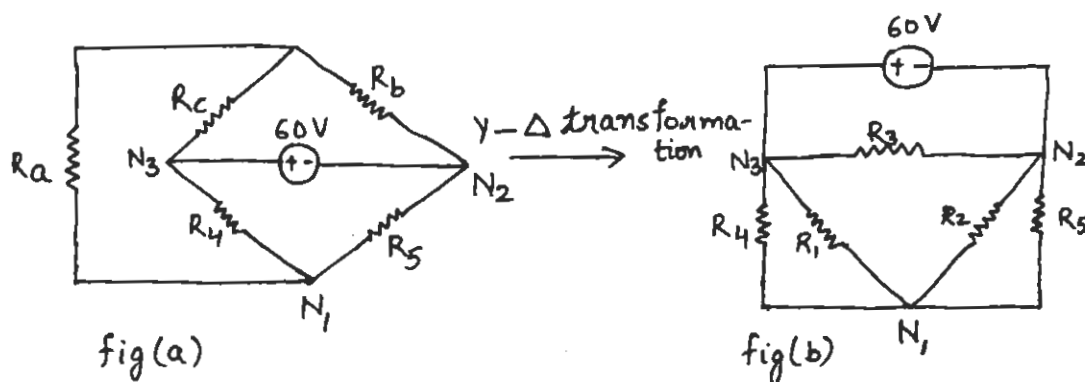

$R_a, R_b, R_c$  connected in Wye configuration


$$R_a = 2 \text{ k}\Omega, R_b = 8 \text{ k}\Omega, R_c = 8 \text{ k}\Omega, R_4 = 6 \text{ k}\Omega, R_5 = 12 \text{ k}\Omega$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b} = 12 \text{ k}\Omega$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c} = 12 \text{ k}\Omega$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a} = 48 \text{ k}\Omega$$

fig (b)  $\rightarrow$  fig (c)

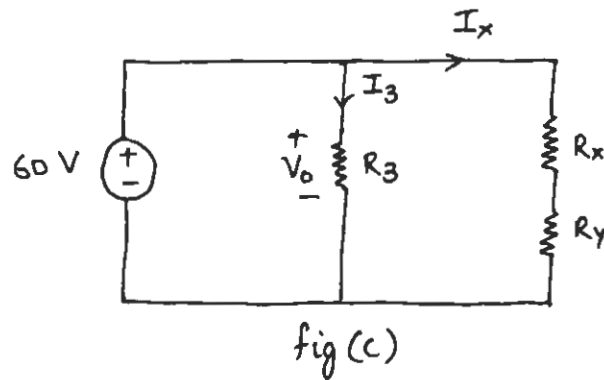

$$R_x = R_1 \parallel R_4 = 4 \text{ k}\Omega$$

$$R_y = R_2 \parallel R_5 = 6 \text{ k}\Omega$$

$$P = \frac{V_o^2}{R_3} + \frac{V_o^2}{R_x + R_y}$$

$$P = 435 \text{ mW}$$

- 2.93 Find the value of  $g$  in the network in Fig. P2.93 such that the power supplied by the 3-A source is 20 W.


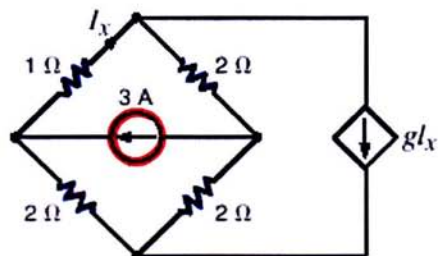


Figure P2.93

**SOLUTION:**

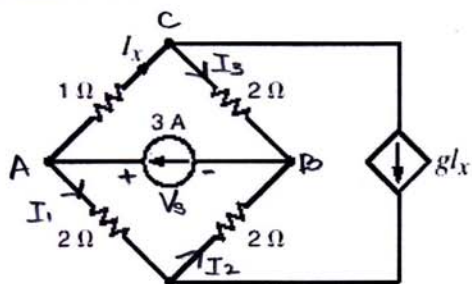

$$P = V_s I_s$$

$$20 = V_s (3)$$

$$V_s = \frac{20}{3} \text{ V}$$

KVL:

$$V_s = I_x + 2I_3 \quad \text{--- ①}$$

KCL at A:

$$3 = I_1 + I_x$$

Putting eq<sup>n</sup> ① for  $I_x$

$$I_x = 3 - I_1$$

$$V_s = \underbrace{3 - I_1}_{I_2} + 2I_3$$

$$\frac{20}{3} - 3 = -I_1 + 2I_3$$

$$\boxed{11 = -3I_1 + 6I_3}$$

KVL:

$$V_s = 2I_1 + 2I_2$$

KCL at B:

$$3 = I_2 + I_3$$

$$I_2 = 3 - I_3$$

$$\frac{20}{3} = 2I_1 + 2(3 - I_3)$$

$$\boxed{2 = 6I_1 - 6I_3}$$

$$-3I_1 + 6I_3 = 11$$

$$6I_1 - 6I_3 = 2$$

$$I_1 = 4.33 \text{ A}$$

$$I_3 = 4 \text{ A}$$



$$I_x = 3 - I_1$$

$$I_x = 3 - 4.33$$

$$I_x = -1.33 \text{ A}$$

KCL at C:

$$I_x = I_3 + gI_x$$

$$-1.33 = 4 + g(-1.33)$$

$$g = 4$$

2.94 Find  $I_o$  in the circuit in Fig. P2.94.



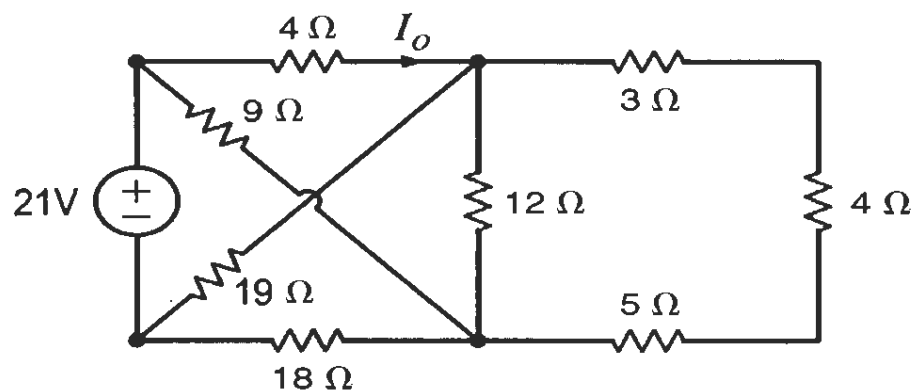


Figure P2.94

Solution: 2.94

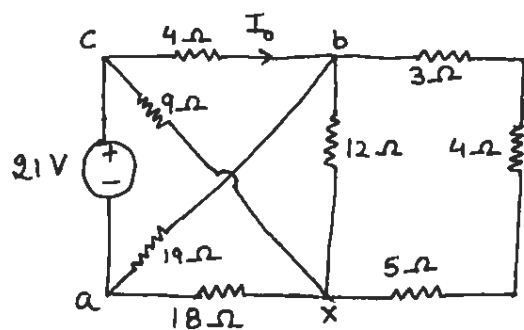


fig(a)

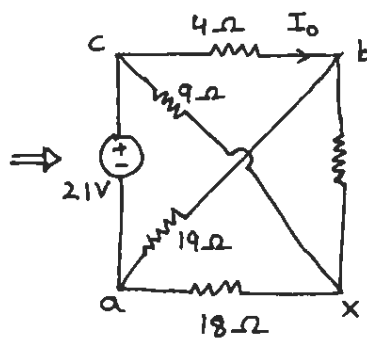

fig(b)


$$R_x = 12 \parallel (3 + 4 + 5) = 6 \Omega$$

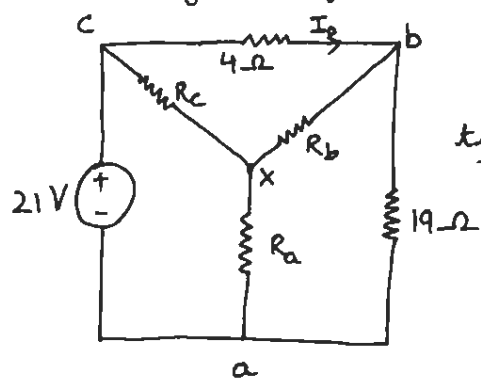In fig(b)  $18\Omega$ ,  $9\Omega$ ,  $R_x$  are in wye connection. Therefore fig(b) is redrawn as fig(c).



fig(c)

wye-delta transformation

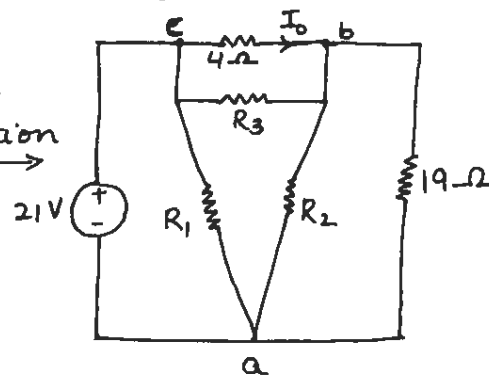

fig(d)

In fig. (c)  $R_a = 18\ \Omega$ ,  $R_b = R_x = 6\ \Omega$ ,  $R_c = 9\ \Omega$


From Wye - delta transformation, we have

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b} = 54\ \Omega$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c} = 36\ \Omega$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a} = 18\ \Omega$$

fig(d) is transformed into fig(e)

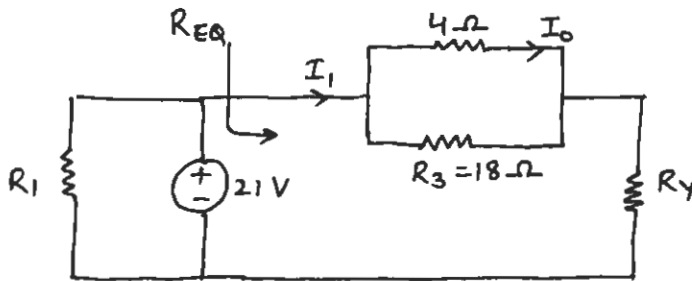

fig(e)

$$R_Y = R_2 \parallel 19$$

$$R_Y = 12.436\ \Omega$$

$$R_{EQ} = 4 \parallel R_3 + R_Y$$

$$= 4 \parallel 18 + 12.436$$

$$R_{EQ} = 15.709\ \Omega$$

$$I_1 = \frac{21}{R_{EQ}} = 1.337\ \text{A}$$

$$I_0 = I_1 \left[ \frac{18}{18+4} \right] = 1.09\ \text{A}$$

$$\boxed{I_0 = 1.09\ \text{A}}$$

2.95 Determine the value of  $V_o$  in the network in Fig. P2.95.


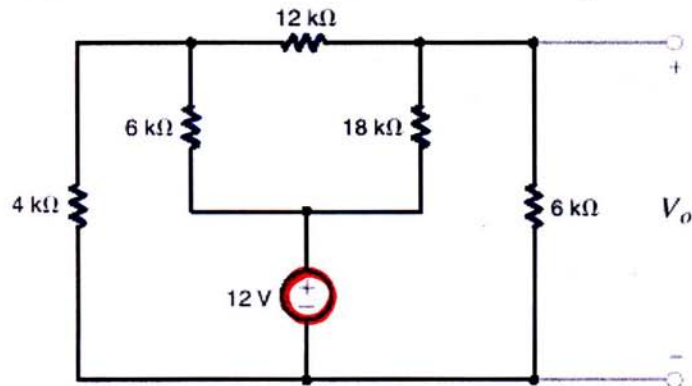


Figure P2.95

**SOLUTION:**

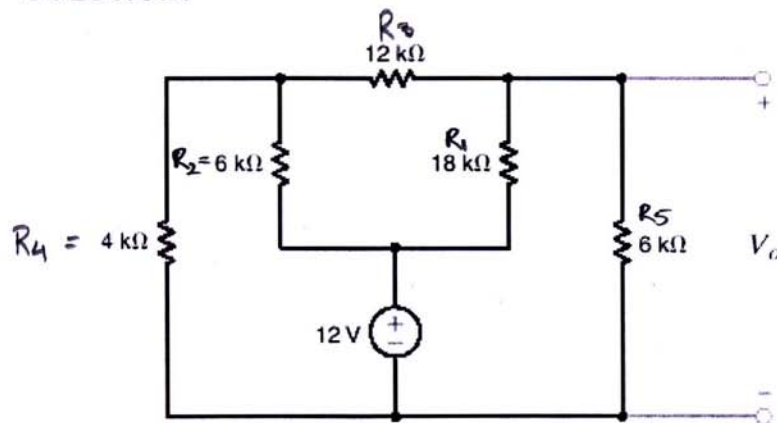


Using a delta to wye transformation:

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3} = \frac{18k(6k)}{18k + 6k + 12k} = 3k\Omega$$



$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3} = \frac{6k(12k)}{18k + 6k + 12k} = 2k\Omega$$
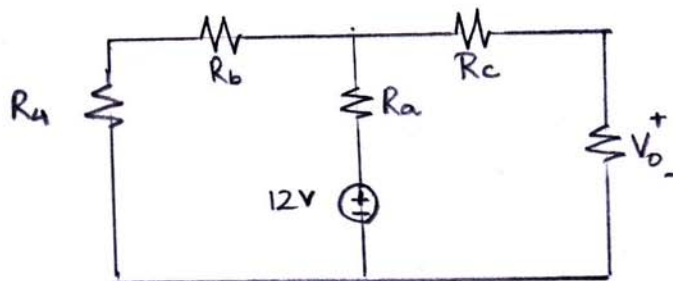
$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3} = \frac{18k(12k)}{18k + 6k + 12k} = 6k\Omega$$



$$R' = R_4 + R_b = 4k + 2k$$

$$R' = 6k \Omega$$

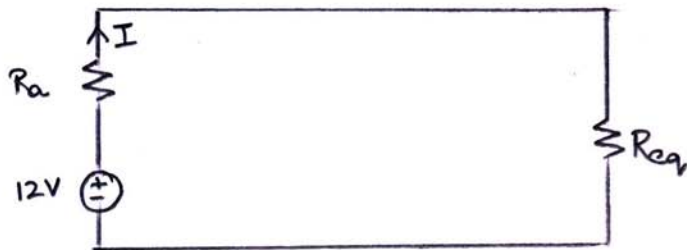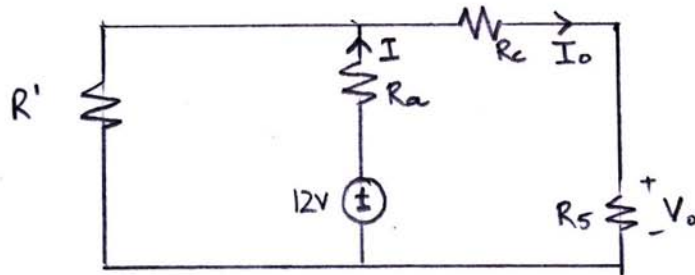

$$R_{eq} = R' \parallel (R_c + R_s) = 6k \parallel (6k + 6k)$$

$$R_{eq} = 6k \parallel 12k = \frac{6k(12k)}{6k + 12k} = 4k \Omega$$

$$I = \frac{12}{R_a + R_{eq}} = \frac{12}{3k + 4k}$$

$$I = 1.714 \text{ mA}$$

Using current division:

$$I_o = \left( \frac{R'}{R' + R_c + R_s} \right) (I)$$

$$I_o = \left( \frac{6k}{6k+6k+6k} \right) (1.714m)$$

$$I_o = 0.571mA$$

$$V_o = I_o R_5 = (0.571m)(6k)$$

$$V_o = 3.43V$$

- 2.96 Find the power supplied by the 6-V source in the network in Fig. P2.96.


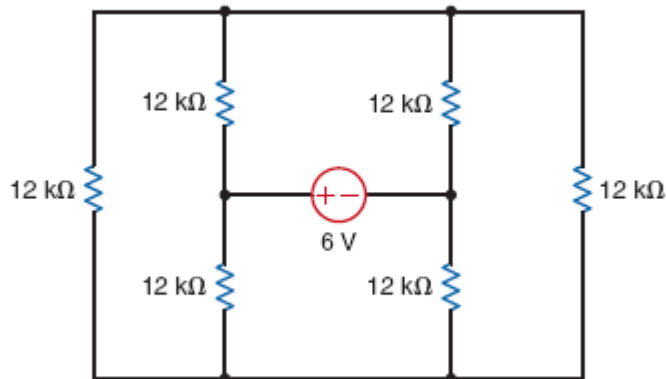
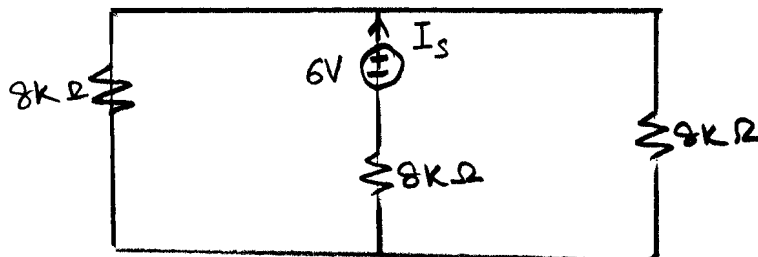


Figure P2.96

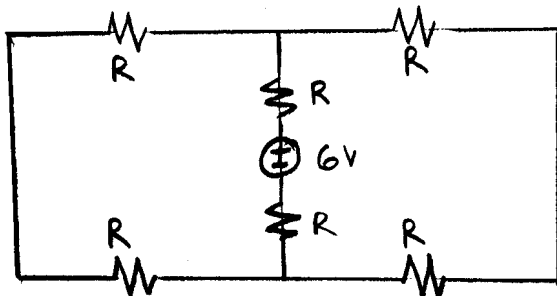
**SOLUTION:**

The three  $12\text{ k}\Omega$  resistors on the left and the three on the right are connected in delta

$$R = \frac{12\text{ k} (12\text{ k})}{12\text{ k} + 12\text{ k} + 12\text{ k}} = 4\text{ k}\Omega$$


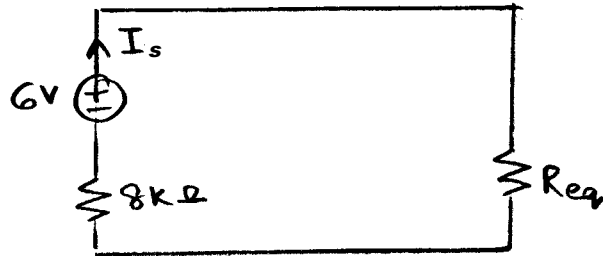
$$R_{eq} = (8k \parallel 8k) = 4k\Omega$$



$$I_s = \frac{6}{8k + R_{eq}} = \frac{6}{8k + 4k}$$

$$I_s = 0.5 \text{ mA}$$

$$P = V_s I_s = 6(0.5 \text{ m})$$

$$P = 3 \text{ mW}$$



2.97 Find  $V_o$  in the circuit in Fig. P2.97.

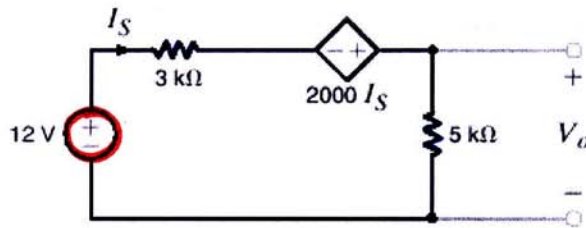


Figure P2.97

**SOLUTION:**

KVL:

$$12 + 2000 I_s = 3kI_s + 5kI_s$$

$$6kI_s = 12$$

$$I_s = 2\text{mA}$$

$$V_o = I_s(5k)$$

$$V_o = 2\text{m}(5k)$$

$$V_o = 10\text{V}$$

2.98 Find  $V_o$  in the network in Fig. P2.98.


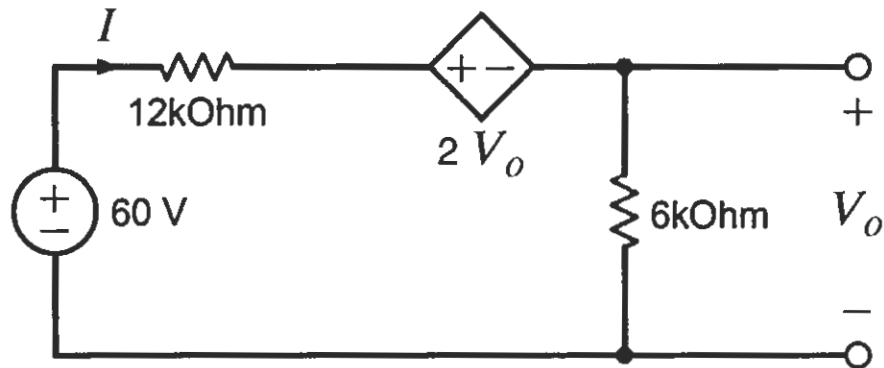


Figure P2.98

Solution: 2.98

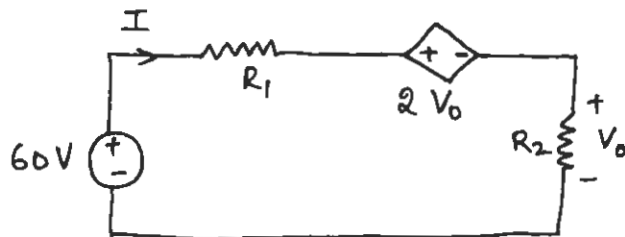

$$R_1 = 12\text{ k}\Omega, R_2 = 6\text{ k}\Omega$$

$$60 = R_1 I + 2V_o + R_2 I$$

$$V_o = R_2 I = 6 I$$

$$60 = 12 I + 12 I + 6 I$$

$$I = 2\text{ A}$$

$$V_o = 12\text{ V}$$

2.99 Find  $I_1$  in the network in Fig. P2.99.


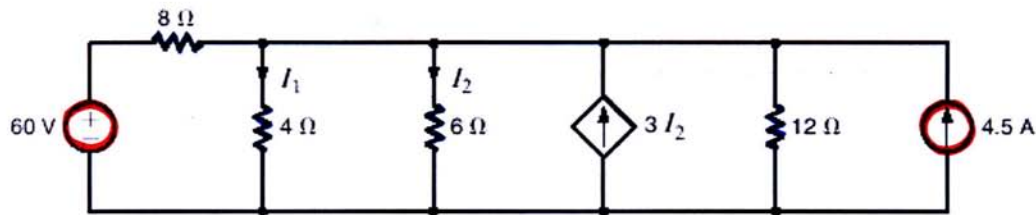


Figure P2.99

**SOLUTION:**

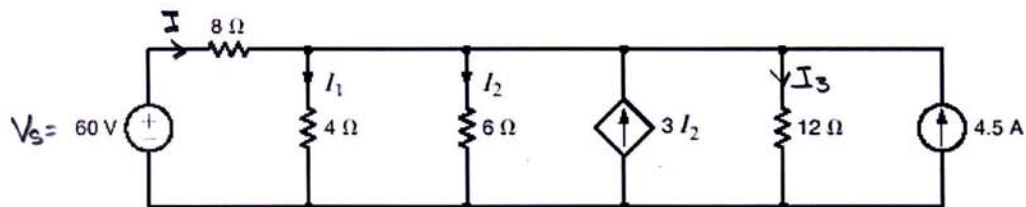

KCL:

$$I + 3I_2 + 4.5 = I_1 + I_2 + I_3$$

$$I = \frac{V_s - V_1}{8}$$

$$\frac{V_s - V_1}{8} + 3\left(\frac{V_1}{6}\right) + 4.5 = \frac{V_1}{4} + \frac{V_1}{6} + \frac{V_1}{12}$$

$$3(60) - 3V_1 + 12V + 108 = 6V_1 + 4V_1 + 2V_1$$

$$3V_1 = 288$$

$$V_1 = 96V$$

$$I_1 = \frac{V_1}{4} = \frac{96}{4} = 24A$$

2.100 Find  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit in Fig. P2.100.


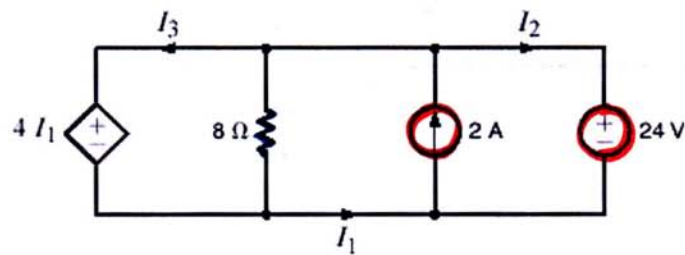


Figure P2.100

**SOLUTION:**

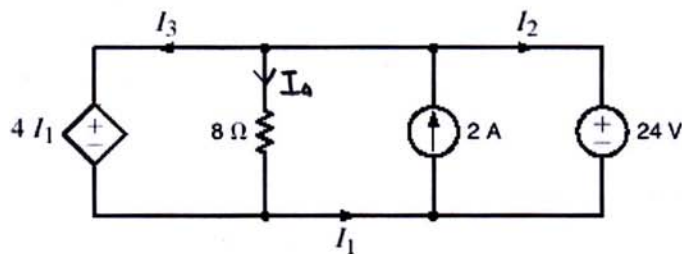

$$I_4 = \frac{24}{8} = 3 \text{ A}$$

$$4I_1 = 24$$

$$I_1 = 6 \text{ A}$$

KCL:

$$I_1 + I_2 = 2$$

$$I_2 = 2 - 6$$

$$I_2 = -4 \text{ A}$$

KCL:

$$I_1 = I_3 + I_4$$

$$\underline{I}_3 = 6 - 3$$

$$\underline{I}_3 = 3\text{ A}$$

2.101 A single-stage transistor amplifier is modeled as shown in Fig. P2.101. Find the current in the load  $R_L$ .


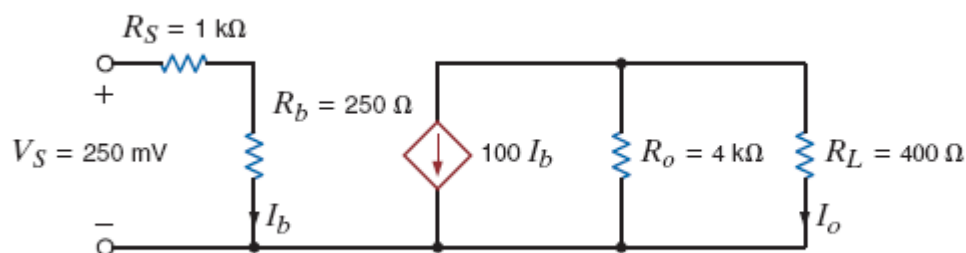


Figure P2.101

**SOLUTION:**

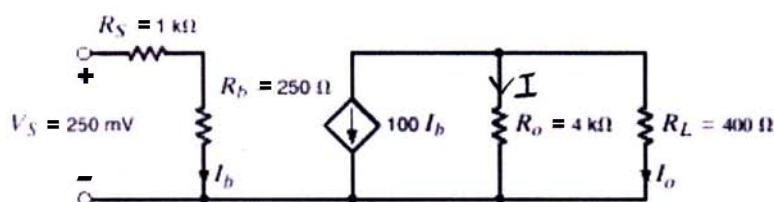

KVL:

$$V_S = I_b R_S + I_b R_b$$

$$I_b = \frac{250\text{m}}{1\text{k} + 250}$$

$$I_b = 0.2\text{mA}$$

KCL:

$$100 I_b + I + I_o = 0$$

$$I_o = -100(0.2\text{m}) - I$$

$$I = \left( \frac{400}{400 + 4\text{k}} \right) (-100 I_b) = \left( \frac{400}{400 + 4\text{k}} \right) (-100)(0.2\text{m})$$

$$I = -1.82\text{mA}$$

$$I_o = -0.02 - (-1.82 \text{ m})$$

$$I_o = -18.18 \text{ mA}$$

2.102 Find  $I_o$  in the network in Fig. P2.102.


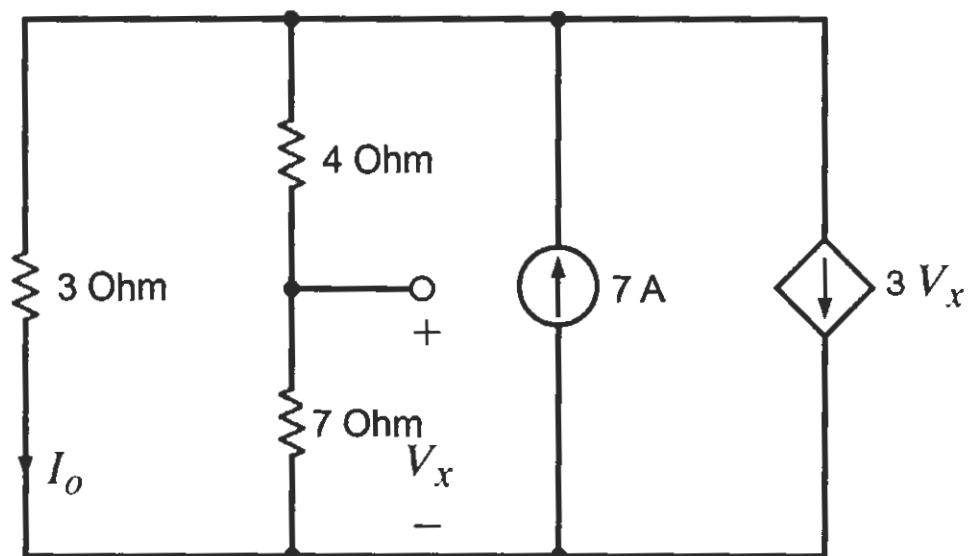


Figure P2.102

Solution: 2.102

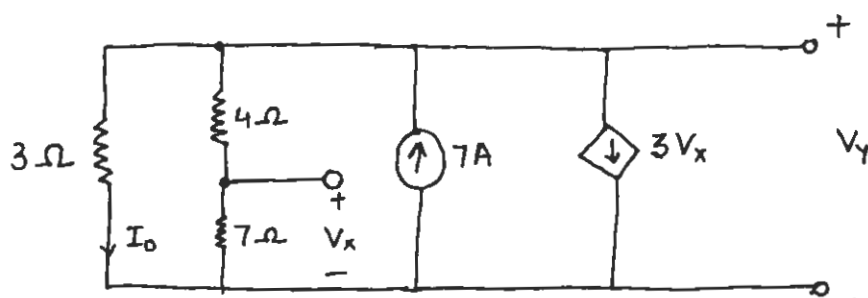

$$7 = 3V_x + \frac{V_y}{11} + \frac{V_y}{3} \dots (1)$$

$$V_x = V_y \left[ \frac{7}{7+4} \right] = \frac{7}{11} V_y$$


$$V_x = \frac{7}{11} V_y \dots \dots \dots (2)$$

Substituting (2) into (1)  $\Rightarrow V_y = 3 \text{ V}$

$$I_o = \frac{V_y}{3} \Rightarrow \boxed{I_o = 1 \text{ A}}$$




**2.103** A typical transistor amplifier is shown in Fig. P2.103. Find the amplifier gain  $G$  (i.e., the ratio of the output voltage to the input voltage).

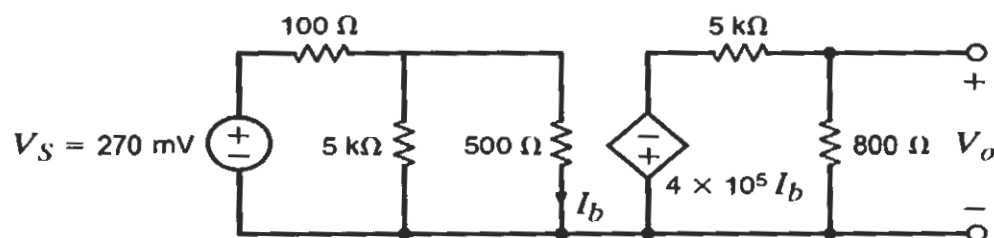

**Figure P2.103**

**Solution:** 2.103

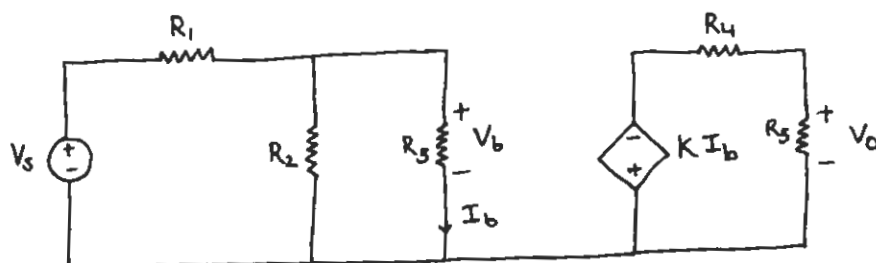

$$V_S = 0.27 \text{ V}, R_1 = 100 \Omega, R_2 = 5 \text{ k}\Omega, R_3 = 500 \Omega,$$

$$K = 4 \times 10^5, R_4 = 5 \text{ k}\Omega, R_5 = 800 \Omega$$

$$V_b = V_S \left[ \frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)} \right] = 0.221 \text{ V}$$

$$I_b = \frac{V_b}{R_3} = 442 \mu\text{A}$$

$$V_o = -K I_b \left[ \frac{R_5}{R_4 + R_5} \right] \Rightarrow V_o = -24.386 \text{ V}$$

$$G = \frac{V_o}{V_S} = -90.319$$

$$\boxed{G = -90.3}$$

2.104 Find the power absorbed by the 12-k $\Omega$  resistor in the network in Fig. P2.104.


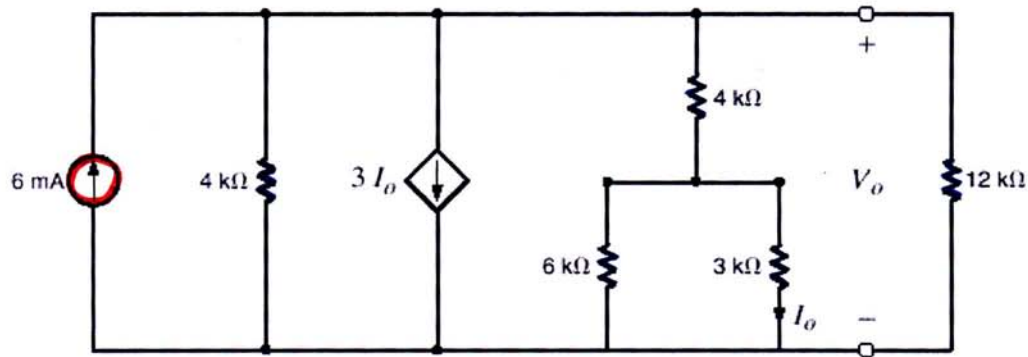


Figure P2.104

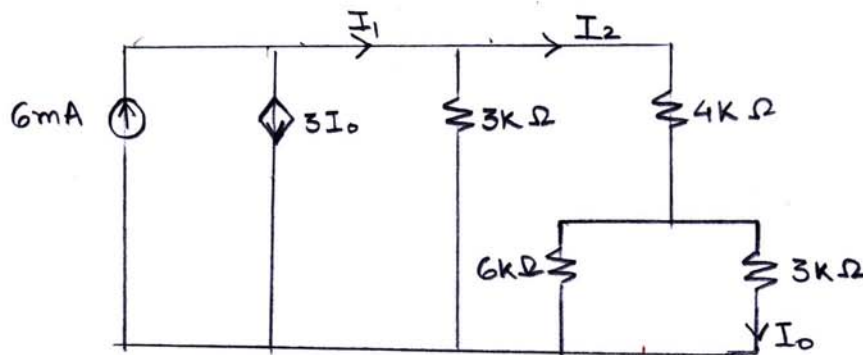**SOLUTION:**

$$R = (4\text{ k}\Omega \parallel 12\text{ k}\Omega) = 3\text{ k}\Omega$$



KCL:

$$3I_o + I_1 = 6\text{ m}$$

$$I_1 = 6\text{ m} - 3I_o$$

$$I_2 = \left( \frac{3\text{ k}}{4\text{ k} + (6\text{ k} \parallel 3\text{ k}) + 3\text{ k}} \right) (6\text{ m} - 3I_o)$$

$$I_2 = 2\text{ m} - I_o$$

$$I_o = 0.8\text{ m A}$$

KCL:

$$6\text{ m} = \frac{V_o}{4\text{ k}} + 3I_o + \frac{V_o}{6\text{ k}} + \frac{V_o}{12\text{ k}}$$

$$6\text{ m} = \frac{V_o}{4\text{ k}} + 3(0.8\text{ m}) + \frac{V_o}{6\text{ k}} + \frac{V_o}{12\text{ k}}$$

$$V_o = 7.2\text{ V}$$

$$P_{12\text{ k}\Omega} = \frac{V_o^2}{12\text{ k}} = \frac{(7.2)^2}{12\text{ k}} = 4.32\text{ mW}$$

2.105 Find the power absorbed by the 12-k $\Omega$  resistor in the network in Fig. P2.105.


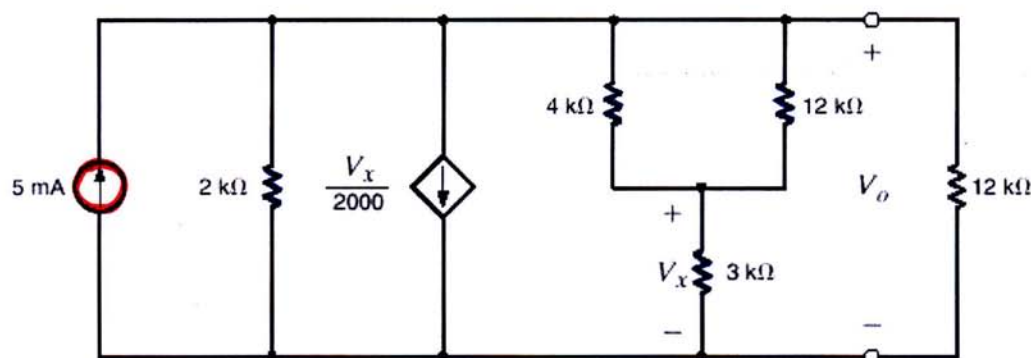


Figure P2.105

**SOLUTION:**

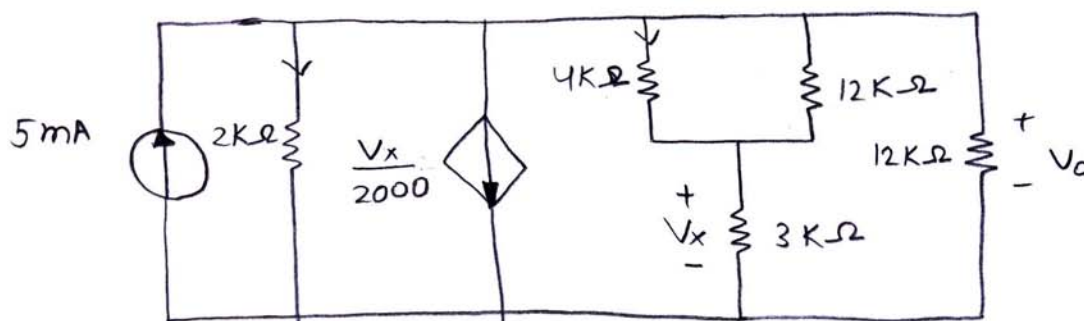

$$V_x = \left( \frac{3K}{(4K/12K) + 3K} \right) V_o$$

$$V_x = \frac{V_o}{2}$$

$$\text{KCL: } 5m = \frac{V_o}{2K} + \frac{V_x}{2000} + \frac{V_o}{(4K/12K) + 3K} + \frac{V_o}{12K}$$

$$5m = \frac{V_o}{2K} + \frac{V_x}{2K} + \frac{V_o}{6K} + \frac{V_o}{12K}$$

$$60 = 6V_o + 6V_x + 2V_o + V_o$$

$$60 = 9V_o + 6\left(\frac{V_o}{2}\right)$$

$$V_o = 5V$$

$$P_{12k\Omega} = \frac{V_o^2}{12k} = \frac{(5)^2}{12k}$$

$$P_{12k\Omega} = 2.08 \text{ mW}$$

2.106 Find the value of  $k$  in the network in Fig. P2.106, such that the power supplied by the 6-A source is 108 W.


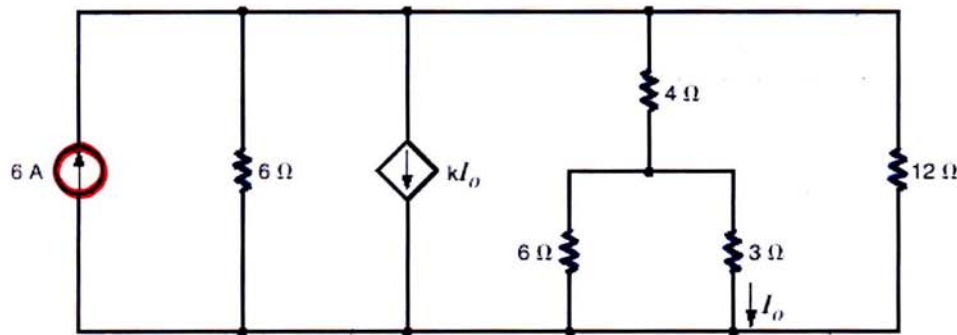


Figure P2.106

**SOLUTION:**

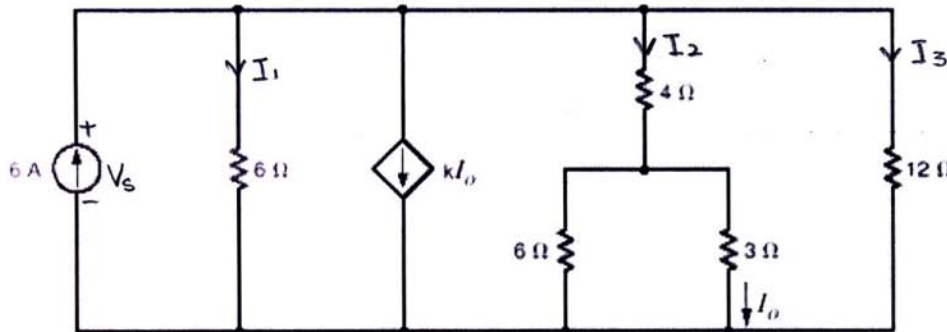

$$P_{6A} = V_s I_3$$

$$V_s = \frac{108}{6} = 18V$$

KCL:

$$6 = \frac{V_s}{6} + kI_o + \frac{V_s}{4 + (6||3)} + \frac{V_s}{12}$$

$$6 = \frac{18}{6} + kI_o + 36 + 18$$

$$12kI_o = -18$$

$$kI_o = -1.5V$$

$$I_2 = \frac{V_6}{4 + (6 \parallel 3)} = \frac{18}{4 + 2} = 3 \text{ A}$$

$$I_o = \left( \frac{6}{3 + 6} \right) I_2 = \left( \frac{6}{3 + 6} \right) (3)$$

$$I_o = 2 \text{ A}$$

$$K = \frac{-1.5}{2}$$

$$K = -0.75$$

**2FE-10** Find the current  $I_x$  in Fig. 2PFE-10.

- a.  $1/2$  A
- b.  $5/3$  A
- c.  $3/2$  A
- d.  $8/3$  A


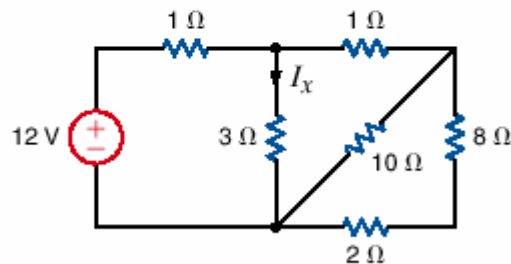


Fig. 2PFE-10

**SOLUTION:**

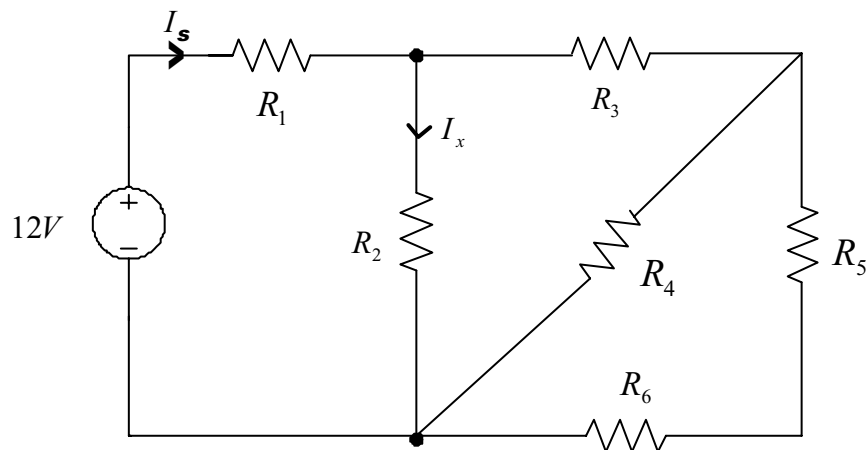

The correct answer is *d*.

$$R_{eq} = \{ [(R_5 + R_6) \parallel R_4] + R_3 \} \parallel R_2 + R_1$$

$$R_{eq} = \{ [(8 + 2) \parallel 10] + 1 \} \parallel 3 + 1$$

$$R_{eq} = (6 \parallel 3) + 1 = 3\Omega$$

$$I_s = \frac{12}{R_{eq}} = \frac{12}{3} = 4A$$

$$R' = [(R_5 + R_6) \parallel R_4] + R_3 = 6\Omega$$

$$I_x = \left( \frac{6}{3 + 6} \right) (4) = \frac{24}{9} = \frac{8}{3}A$$



3.1 Find both  $I_o$  and  $V_o$  in the network in Fig. P3.1 using nodal analysis.


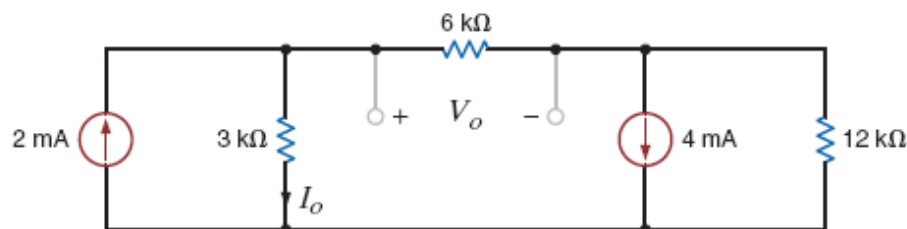


Figure P3.1

**SOLUTION:**

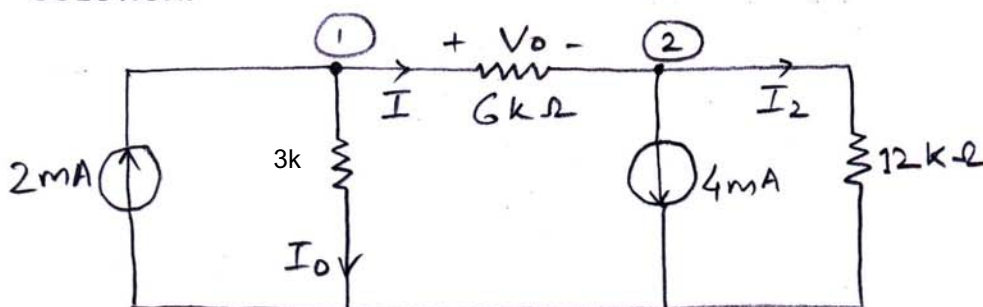

$$\begin{aligned} \text{KCL at } \textcircled{1}: \quad 2\text{ m} &= I_o + I \\ \frac{V_1}{3\text{ k}} + \frac{V_1 - V_2}{6\text{ k}} &= 2\text{ m} \\ 2V_1 + V_1 - V_2 &= 12 \\ \boxed{3V_1 - V_2 = 12} \end{aligned}$$

$$\begin{aligned} \text{KCL at } \textcircled{2}: \quad I &= 4\text{ m} + I_2 \\ \frac{V_1 - V_2}{6\text{ k}} &= 4\text{ m} + \frac{V_2}{12\text{ k}} \\ 2V_1 - 2V_2 &= 48 + V_2 \\ \boxed{2V_1 - 3V_2 = 48} \end{aligned}$$

$$\begin{aligned} 3V_1 - V_2 &= 12 \\ 2V_1 - 3V_2 &= 48 \end{aligned}$$

$$\begin{aligned} V_1 &= -1.71\text{ V} \\ V_2 &= -17.14\text{ V} \end{aligned}$$

$$V_o = V_1 - V_2$$

$$V_o = -1.71 - (-17.14)$$


$$V_o = 15.43 \text{ V}$$

$$I_o = \frac{V_1}{3 \text{ k}}$$

$$= \frac{-1.71}{3 \text{ k}} = -0.57$$


$$I_o = -0.57 \text{ mA}$$

**3.2** Use nodal analysis to find  $V_1$  in the circuit in Fig. P3.2.

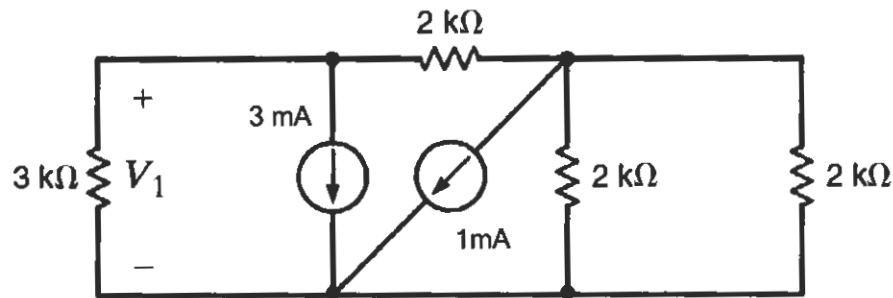

**Figure P3.2**

**SOLUTION: 3.2**

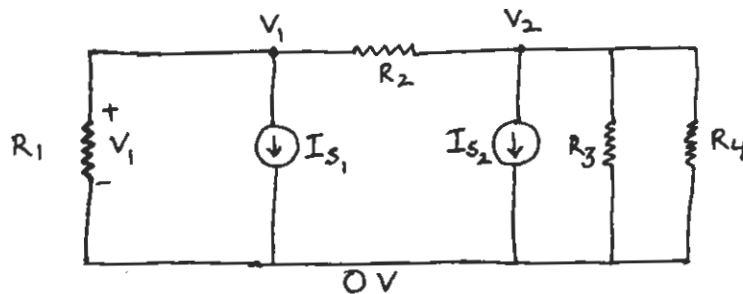

$$R_1 = 3 \text{ k}\Omega, R_2 = R_3 = R_4 = 2 \text{ k}\Omega, I_{s1} = 3 \text{ mA}, I_{s2} = 1 \text{ mA}$$

$$\text{KCL @ } V_1: \frac{V_1}{R_1} + I_{s1} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{3 \times 10^3} + 3 \times 10^{-3} + \frac{V_1 - V_2}{2 \times 10^3} = 0$$

$$5V_1 - 3V_2 = -18 \quad \text{--- (1)}$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_2} + I_{s2} + \frac{V_2}{R_3} + \frac{V_2}{R_4} = 0$$

$$\frac{V_2 - V_1}{2 \times 10^3} + 1 \times 10^{-3} + \frac{V_2}{2 \times 10^3} + \frac{V_2}{2 \times 10^3} = 0$$

$$3V_2 - V_1 = -2 \quad \text{--- (2)}$$

Substituting equation (2) in (1), we get

$$V_2 = -\frac{28}{12}$$

$$V_1 = \frac{3V_2 - 18}{5} \Rightarrow \boxed{V_1 = -5 \text{ V}}$$

- 3.3 Find  $V_1$  and  $V_2$  in the circuit in Fig. P3.3 using nodal analysis. Then solve the problem using MATLAB and compare your answers.


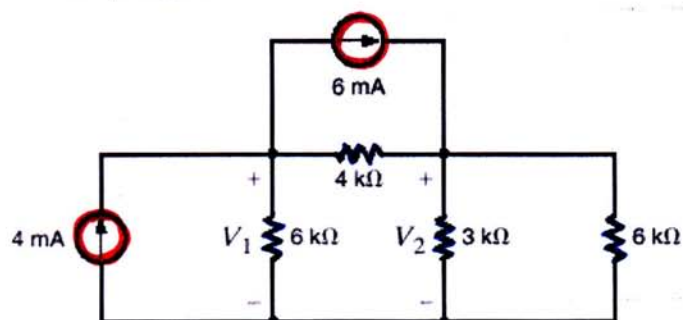


Figure P3.3

**SOLUTION:**

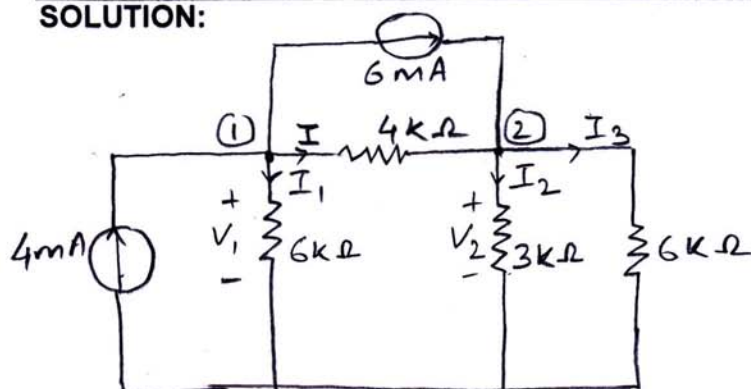

$$\text{KCL at } ①: 4\text{m} = 6\text{m} + I + I_1$$

$$\frac{V_1 - V_2}{4\text{k}} + \frac{V_1}{6\text{k}} = -2\text{m}$$

$$3V_1 - 3V_2 + 2V_1 = -24$$

$$\boxed{5V_1 - 3V_2 = -24}$$

$$\text{KCL at } ②: 6\text{m} + I = I_2 + I_3$$

$$\frac{V_2}{3\text{k}} + \frac{V_2}{6\text{k}} = 6\text{m} + \frac{V_1 - V_2}{4\text{k}}$$

$$4V_2 + 2V_2 = 72 + 3V_1 - 3V_2$$

$$\boxed{-3V_1 + 9V_2 = 72}$$

$$\begin{aligned}5V_1 - 3V_2 &= -24 \\ -3V_1 + 9V_2 &= 72\end{aligned}$$

$$\begin{aligned}V_1 &= 0 \text{ V} \\ V_2 &= 8 \text{ V}\end{aligned}$$

% MATLAB Code and solution for Problem 3.4


```
G = [5, -3; -3, 9];  
Imatrix = [-24; 72];  
V = inv(G)*Imatrix
```

>>

V =


```
0.00  
8.00
```

**3.4** Use nodal analysis to find both  $V_1$  and  $V_o$  in the circuit in Fig. P3.4.

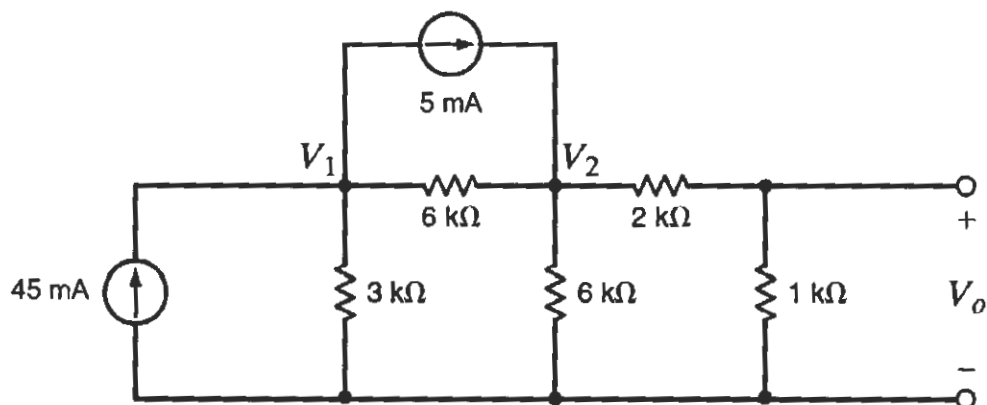

**Figure P3.4**

**SOLUTION:** 3.4

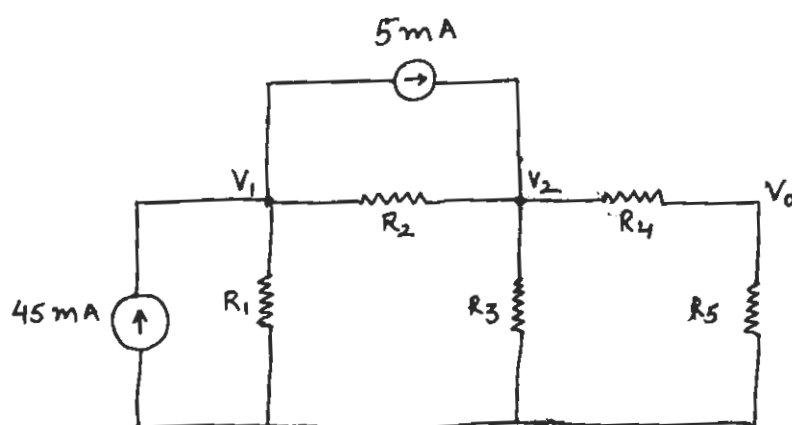

$$R_1 = 3\text{ k}\Omega, R_2 = 6\text{ k}\Omega, R_3 = 6\text{ k}\Omega, R_4 = 2\text{ k}\Omega, R_5 = 1\text{ k}\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_1} + I_{s_2} - I_{s_1} = 0$$

$$\frac{V_1 - V_2}{6 \times 10^3} + \frac{V_1}{3 \times 10^3} + 5 \times 10^{-3} - 45 \times 10^{-3} = 0$$

$$3V_1 - V_2 = 240 \quad \text{--- ①}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + \frac{V_2 - V_o}{R_4} + \frac{V_2}{R_3} - I_{s_2} = 0$$

$$\frac{V_2 - V_1}{6 \times 10^3} + \frac{V_2 - V_0}{2 \times 10^3} + \frac{V_2}{6 \times 10^3} - 5 \times 10^{-3} = 0$$

$$5V_2 - V_1 - 3V_0 = 30 \quad \text{--- (2)}$$

$$\text{KCL at } V_0: \frac{V_2 - V_0}{R_4} - \frac{V_0}{R_5} = 0$$

$$\frac{V_2 - V_0}{2 \times 10^3} - \frac{V_0}{10^3} = 0$$

$$V_2 = 3V_0 \quad \text{--- (3)}$$

Substituting equation (3) in (2), we get

$$5(3V_0) - V_1 - 3V_0 = 30$$

$$12V_0 - 30 = V_1 \quad \text{--- (4)}$$

Substituting equations (3) and (4) in (1), we get

$$3(12V_0 - 30) - 3V_0 = 240$$

$$\boxed{V_0 = 10 \text{ V}}$$

Substituting the value of  $V_0$  in equation (4), we get

$$12(10) - 30 = V_1$$

$$\Rightarrow \boxed{V_1 = 90 \text{ V}}$$

3.5 Find  $V_o$  in the network in Fig. P3.5.


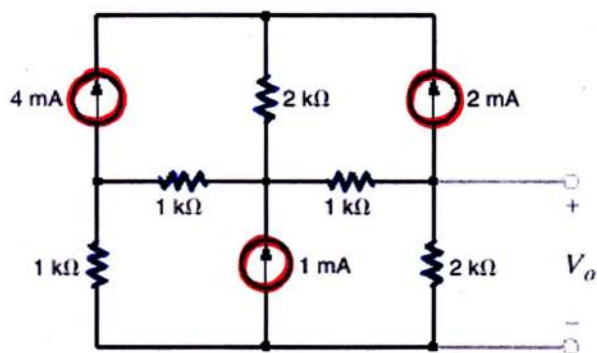


Figure P3.5

**SOLUTION:**

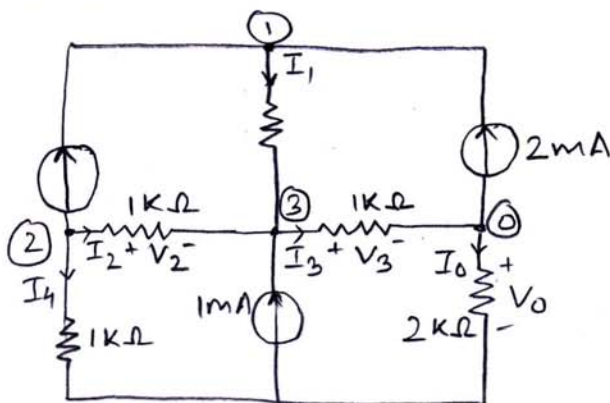

$$\text{KCL at } (2) : 4\text{m} + I_2 + I_4 = 0$$

$$\frac{V_2 - V_3}{1\text{K}} + \frac{V_2}{1\text{K}} = -4\text{m}$$

$$V_2 - V_3 + V_2 = -4$$

$$\boxed{2V_2 - V_3 = -4}$$

$$\text{KCL at } (3) : I_1 + 1\text{m} + I_2 = I_3$$

$$\frac{V_1 - V_3}{2\text{K}} + 1\text{m} + \frac{V_2 - V_3}{1\text{K}} = \frac{V_3 - V_o}{1\text{K}}$$

$$V_1 - V_3 + 2 + 2V_2 - 2V_3 = 2V_3 - 2V_o$$

$$-2V_o + 5V_3 - 2V_2 - V_1 = 2$$

$$\boxed{-2V_o - V_1 - 2V_2 + 5V_3 = 2}$$



$$\text{KCL at } \textcircled{0} : I_3 = 2\text{ m} + I_0$$

$$\frac{V_3 - V_0}{1\text{ k}} = 2\text{ m} + \frac{V_0}{2\text{ k}}$$

$$2V_3 - 2V_0 = 4 + V_0$$

$$\boxed{-3V_0 + 2V_3 = 4}$$

$$\text{KCL at } \textcircled{1} : 4\text{ m} + 2\text{ m} = I_1$$

$$\frac{V_1 - V_3}{2\text{ k}} = 6\text{ m}$$

$$\boxed{V_1 - V_3 = 12}$$

$$0V_0 + 0V_1 + 2V_2 - V_3 = -4$$

$$-2V_0 - V_1 - 2V_2 + 5V_3 = 2$$

$$-3V_0 + 0V_1 + 0V_2 + 2V_3 = 4$$

$$0V_0 + V_1 + 0V_2 - V_3 = 12$$

$$V_0 = 1.6\text{ V}$$

$$V_1 = 16.4\text{ V}$$

$$V_2 = 0.2\text{ V}$$

$$V_3 = 4.4\text{ V}$$

3.6 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.6.


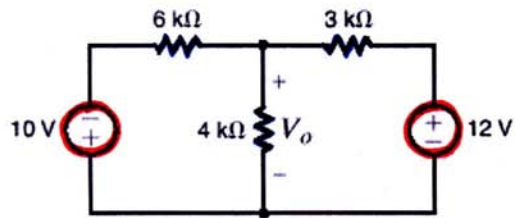


Figure P3.6

**SOLUTION:**

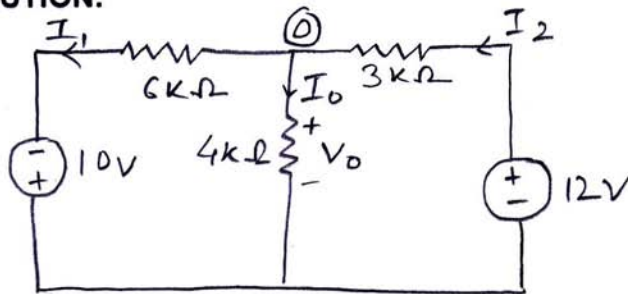

KCL at ①:  $I_2 = I_o + I_1$


$$\frac{12 - V_o}{3k} = \frac{V_o}{4k} + \frac{V_o - (-10)}{6k}$$

$$48 - 4V_o = 3V_o + 2V_o + 20$$

$$9V_o = 28$$


$$V_o = 3.11 \text{ V}$$

**3.7** Find  $V_o$  in the network in Fig. P3.7 using nodal analysis.

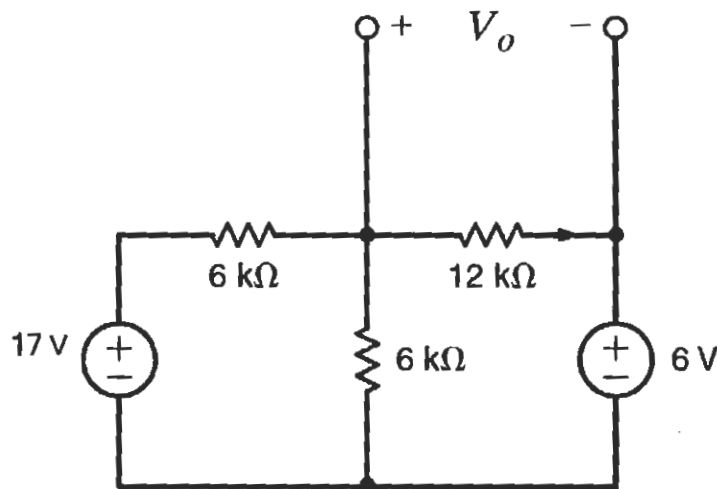

**Figure P3.7**

**SOLUTION:** 3.7

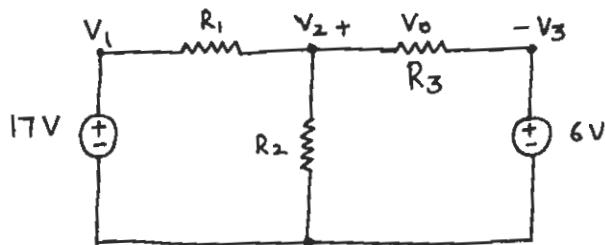

$$R_1 = R_2 = 6 \text{ k}\Omega, \quad R_3 = 12 \text{ k}\Omega$$

$$\text{@ } V_1: \quad V_1 = 17 \text{ V}$$

$$\text{KCL @ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0 \quad \text{--- (1)}$$

$$\text{@ } V_3: \quad V_3 = 6 \text{ V}$$

Substituting values of  $V_1$  and  $V_3$  in equation (1), we get

$$\frac{V_2}{R_1} - \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2}{R_3} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_1}{R_1} - \frac{V_3}{R_3} = 0$$

$$V_2 \left[ \frac{1}{6} + \frac{1}{6} + \frac{1}{12} \right] - \frac{17}{6} - \frac{6}{12} = 0$$

$$V_2 = 8 \text{ V}$$

$$V_0 = V_2 - V_3$$

$$V_0 = 2 \text{ V}$$

3.8 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.8.


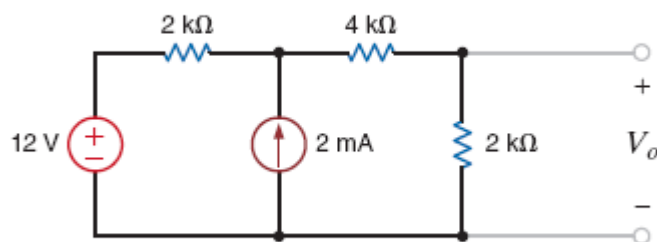


Figure P3.8

**SOLUTION:**

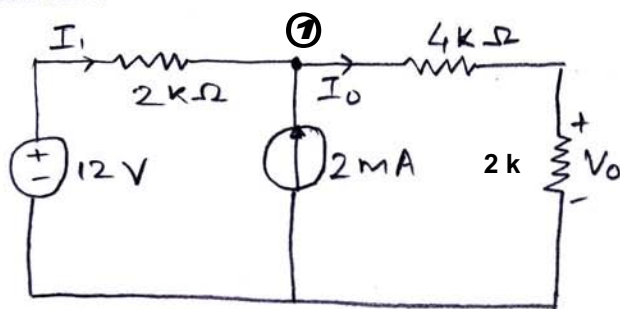

$$\text{KCL at } ① : I_1 + 2\text{ m} = I_o$$

$$\frac{12 - V_1}{2\text{ k}} + 2\text{ m} = \frac{V_1}{4\text{ k} + 2\text{ k}}$$

$$36 - 3V_1 + 12 = V_1$$

$$4V_1 = 48$$

$$V_1 = 12\text{ V}$$

$$I_o = \frac{V_1}{4\text{ k} + 2\text{ k}}$$

$$= \frac{12}{6\text{ k}}$$

$$I_o = 2\text{ mA}$$

$$V_o = I_o (2\text{ k})$$

$$= 2\text{ m} (2\text{ k})$$

$$V_o = 4\text{ V}$$

3.9 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.9.


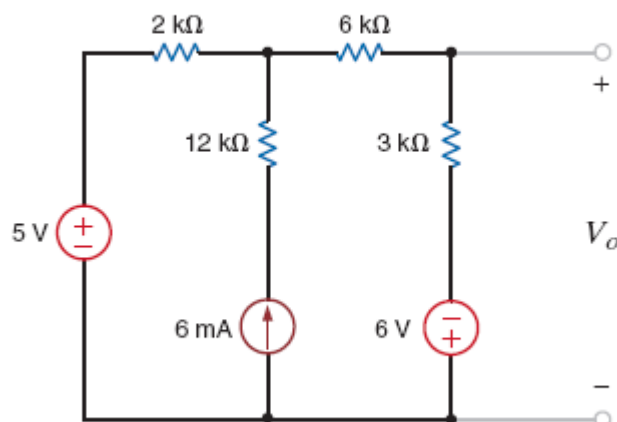


Figure P3.9

**SOLUTION:**

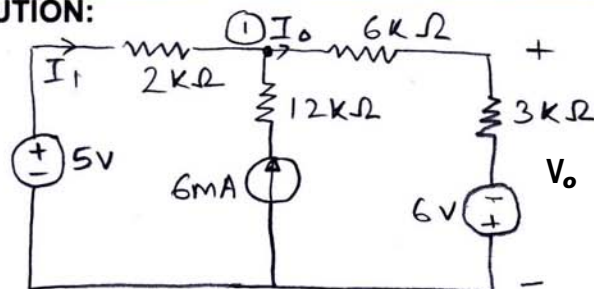

$$\text{KCL at } \textcircled{1}: I_1 + 6\text{m} = I_o$$

$$\frac{5 - V_1}{2\text{k}} + 6\text{m} = \frac{V_1 - (-6)}{6\text{k} + 3\text{k}}$$

$$45 - 9V_1 + 108 = 2V_1 + 12$$

$$11V_1 = 141$$

$$V_1 = 12.82\text{ V}$$

$$I_o = \frac{V_1 - (-6)}{6\text{k} + 3\text{k}}$$

$$= \frac{12.82 + 6}{9\text{k}}$$

$$I_o = 2.09\text{ mA}$$

$$6 + V_o = 3\text{k} I_o$$

$$V_o = 3\text{k}(2.09\text{m}) - 6$$

$$V_o = 0.27\text{ V}$$

3.10 Use nodal analysis to find  $V_o$  in the network in Fig. P3.10.


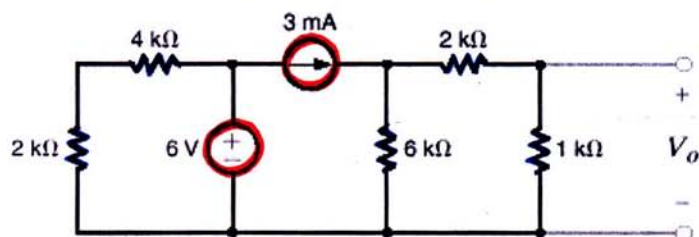


Figure P3.10

**SOLUTION:**

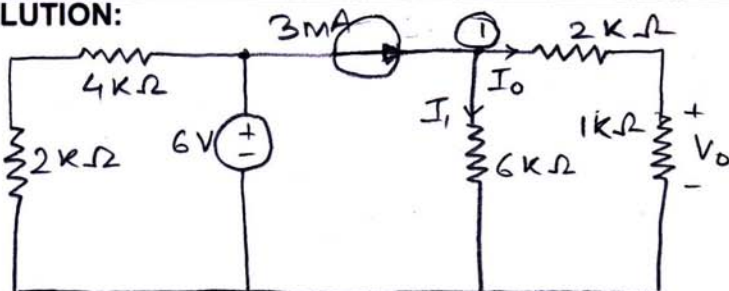

$$\text{KCL at } \textcircled{1}: 3\text{ m} = I_1 + I_o$$

$$\frac{V_1}{6\text{ K}} + \frac{V_1}{2\text{ K} + 1\text{ K}} = 3\text{ m}$$

$$V_1 + 2V_1 = 18$$

$$3V_1 = 18$$

$$V_1 = 6\text{ V}$$

$$I_o = \frac{V_1}{2\text{ K} + 1\text{ K}} = \frac{6}{3\text{ K}}$$

$$I_o = 2\text{ mA}$$

$$V_o = I_o (1\text{ K})$$

$$= 2\text{ m} (1\text{ K})$$

$$V_o = 2\text{ V}$$

3.11 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.11.


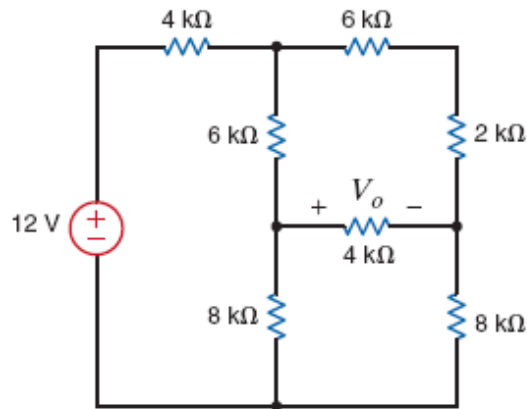


Figure P3.11

**SOLUTION:**

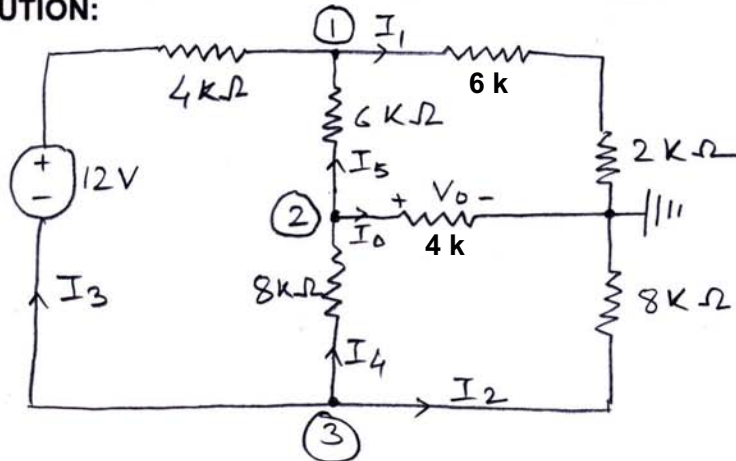

KCL at ①:  $I_3 + I_5 = I_1$

$$\frac{12 - V_1}{4k} + \frac{V_2 - V_1}{6k} = \frac{V_1}{6k + 2k}$$

$$72 - 6V_1 + 4V_2 - 4V_1 = 3V_1$$

$$\boxed{13V_1 - 4V_2 = 72}$$

KCL at ②:  $I_4 = I_0 + I_5$

$$\frac{V_3 - V_2}{8k} = \frac{V_2}{4k} + \frac{V_2 - V_1}{6k}$$

$$3V_3 - 3V_2 = 6V_2 + 4V_2 - 4V_1$$

$$\boxed{4V_1 - 13V_2 + 3V_3 = 0}$$



$$\text{KCL at } \textcircled{3}: I_2 + I_3 + I_4 = 0$$

$$\frac{-12 + V_1}{4\text{K}} + \frac{V_3}{8\text{K}} + \frac{V_3 - V_2}{8\text{K}} = 0$$

$$-24 + 2V_1 + V_3 + V_3 - V_2 = 0$$

$$\boxed{2V_1 - V_2 + 2V_3 = 24}$$

$$13V_1 - 4V_2 + 0V_3 = 72$$

$$4V_1 - 13V_2 + 3V_3 = 0$$

$$2V_1 - V_2 + 2V_3 = 24$$

$$V_1 = 6.68 \text{ V}$$

$$V_2 = 3.71 \text{ V}$$

$$V_3 = 7.18 \text{ V}$$

$$V_0 = V_2 = 3.71 \text{ V}$$

3.12 Find  $I_o$  in the network in Fig. P3.12 using nodal analysis.


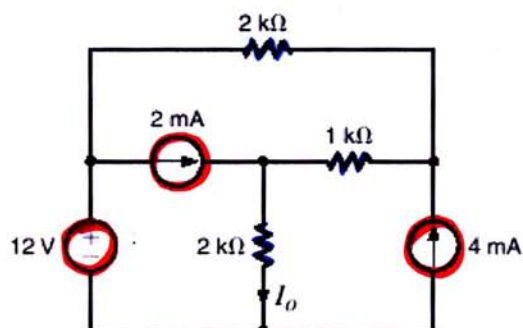


Figure P3.12

**SOLUTION:**

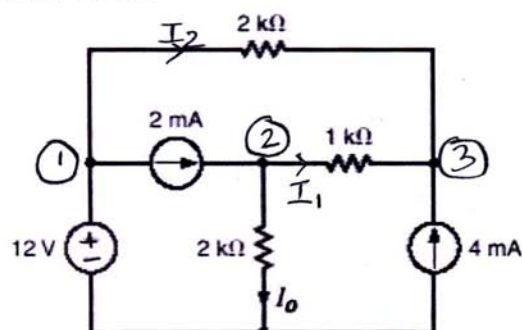

$$\text{KCL at } (2): \quad 2\text{m} = \frac{V_2}{2\text{k}} + \frac{V_2 - V_3}{1\text{k}}$$

$$4 = V_2 + 2V_2 - 2V_3$$

$$\boxed{3V_2 - 2V_3 = 4}$$

$$\text{KCL at } (3): \quad I_1 + I_2 + 4\text{m} = 0$$

$$\frac{V_2 - V_3}{1\text{k}} + \frac{V_1 - V_3}{2\text{k}} + 4\text{m} = 0$$

$$2V_2 - 2V_3 + V_1 - V_3 + 8 = 0$$

$$V_1 = 12\text{V}$$

$$\boxed{2V_2 - 3V_3 = -20}$$

$$3V_2 - 2V_3 = 4$$

$$2V_2 - 3V_3 = -20$$

$$V_2 = 10.4 \text{ V}$$

$$V_3 = 13.6 \text{ V}$$

$$I_0 = \frac{V_2}{2 \text{ K}}$$

$$= \frac{10.4}{2 \text{ K}}$$

$$I_0 = 5.2 \text{ mA}$$

- 3.13 Use nodal analysis to solve for the node voltages in the circuit in Fig. P3.13. Also calculate the power supplied by the 1-A current source.


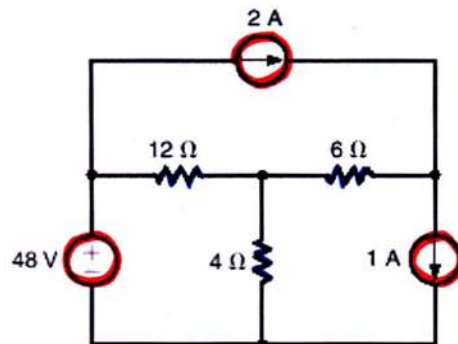


Figure P3.13

**SOLUTION:**

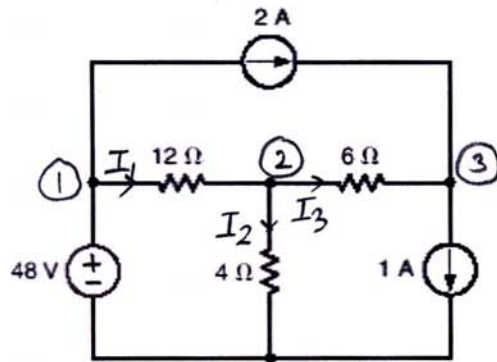

$$\text{KCL at } \textcircled{2}: I_1 = I_2 + I_3$$

$$\frac{V_1 - V_2}{12} = \frac{V_2}{4} + \frac{V_2 - V_3}{6}$$

$$V_1 - V_2 = 3V_2 + 2V_2 - 2V_3$$

$$V_1 = 48 \text{ V}$$

$$\boxed{6V_2 - 2V_3 = 48}$$

$$\text{KCL at } \textcircled{3}: 2 + I_3 - 1 = 0$$

$$\frac{V_2 - V_3}{6} = -1$$

$$\boxed{V_2 - V_3 = -6}$$

$$6V_2 - 2V_3 = 48$$

$$V_2 - V_3 = -6$$

$$V_2 = 15 \text{ V}$$

$$V_3 = 21 \text{ V}$$

$$\begin{aligned} P_{1A} &= V_3 (1) \\ &= 21 (1) \end{aligned}$$

$$P_{1A} = 21 \text{ W}$$

3.14 Find  $V_o$  in the network in Fig. P3.14 using nodal equations.


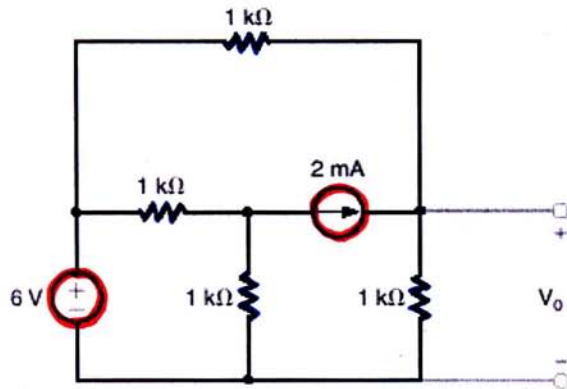


Figure P3.14

**SOLUTION:**

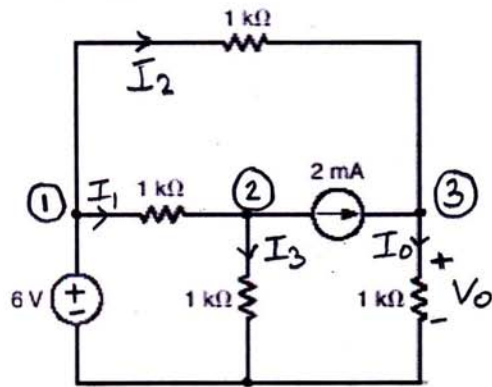

$$\text{KCL at } \textcircled{2} : I_1 = I_3 + 2\text{m}$$

$$\frac{V_1 - V_2}{1\text{K}} = \frac{V_2}{1\text{K}} + 2\text{m}$$

$$V_1 - V_2 = V_2 + 2$$

$$\boxed{V_1 - 2V_2 = 2}$$

$$V_1 = 6\text{V}$$

$$-2V_2 = -4$$

$$V_2 = 2\text{V}$$

$$\text{KCL at } \textcircled{3} : I_2 + 2\text{m} = I_o$$

$$\frac{V_1 - V_3}{1\text{K}} + 2\text{m} = \frac{V_3}{1\text{K}}$$

$$V_1 - V_3 + 2 = V_3$$

$$2V_3 = 8$$

$$V_3 = 4 \text{ V}$$

$$V_0 = V_3$$

$$V_0 = 4 \text{ V}$$

3.15 Find  $I_o$  in the network in Fig. P3.15 using nodal analysis.


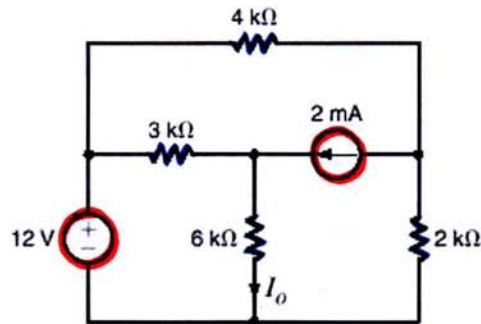


Figure P3.15

**SOLUTION:**

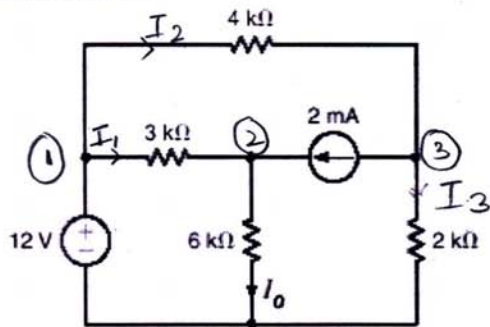

$$\text{KCL at } (2) : I_1 + 2\text{m} = I_o$$

$$\frac{V_1 - V_2}{3\text{k}} + 2\text{m} = \frac{V_2}{6\text{k}}$$

$$2V_1 - 2V_2 + 12 = V_2$$

$$\boxed{2V_1 - 3V_2 = -12}$$

$$\text{KCL at } (3) : I_2 = 2\text{m} + I_3$$

$$\frac{V_1 - V_3}{4\text{k}} = 2\text{m} + \frac{V_3}{2\text{k}}$$

$$V_1 - V_3 = 8 + 2V_3$$

$$\boxed{V_1 - 3V_3 = 8}$$

$$V_1 = 12\text{ V}$$

$$2(12) - 3V_2 = -12$$

$$-3V_2 = -36$$

$$V_2 = 12\text{ V}$$



$$\begin{aligned} I_o &= \frac{V_2}{6K} \\ &= \frac{12}{6K} \\ I_o &= 2mA \end{aligned}$$

3.16 Use nodal analysis to find  $I_o$  in the circuit in Fig. P3.16.


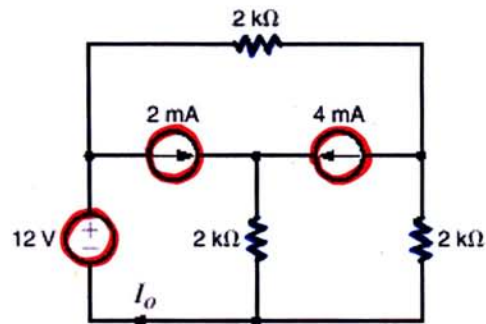


Figure P3.16

**SOLUTION:**

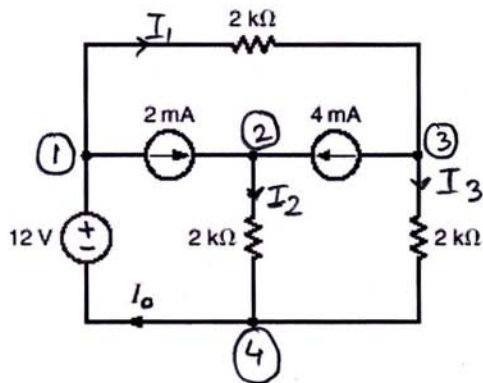

$$\text{KCL at } (2) : 2\text{m} + 4\text{m} = I_2$$

$$\frac{V_2}{2\text{k}} = 6\text{m}$$

$$V_2 = 12\text{V}$$

$$\text{KCL at } (3) : I_1 = 4\text{m} + I_3$$

$$\frac{V_1 - V_3}{2\text{k}} = 4\text{m} + \frac{V_3}{2\text{k}}$$

$$V_1 - V_3 = 8 + V_3$$

$$2V_3 = V_1 - 8$$

$$V_1 = 12\text{V}$$

$$2V_3 = 12 - 8$$

$$V_3 = 2\text{V}$$

$$I_2 = \frac{V_2}{2\text{k}}$$

$$I_2 = \frac{12}{2k} = 6mA$$

$$I_3 = \frac{V_3}{2k} = \frac{2}{2k} = 1mA$$

KCL at ④:  $I_2 + I_3 = I_0$   
 $I_0 = 6mA + 1mA$   
 $I_0 = 7mA$

3.17 Find  $V_o$  in the circuit in Fig. P3.17 using nodal analysis.


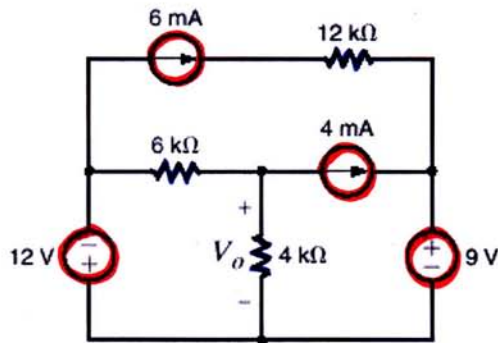


Figure P3.17

**SOLUTION:**

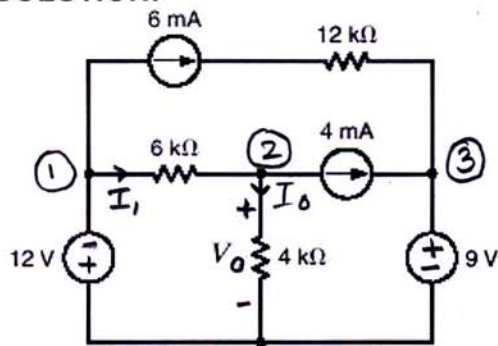

$$\text{KCL at } (2) : I_1 = I_o + 4\text{m}$$

$$\frac{V_1 - V_2}{6\text{K}} = \frac{V_2}{4\text{K}} + 4\text{m}$$

$$2V_1 - 2V_2 = 3V_2 + 48$$

$$\boxed{2V_1 - 5V_2 = 48}$$

$$V_1 = -12\text{ V}$$

$$2(-12) - 5V_2 = 48$$

$$V_2 = -14.4\text{ V}$$

$$V_o = V_2 = -14.4\text{ V}$$

$$V_o = -14.4\text{ V}$$

**3.18** Use nodal analysis to find  $V_o$  in the network in Fig. P3.18.


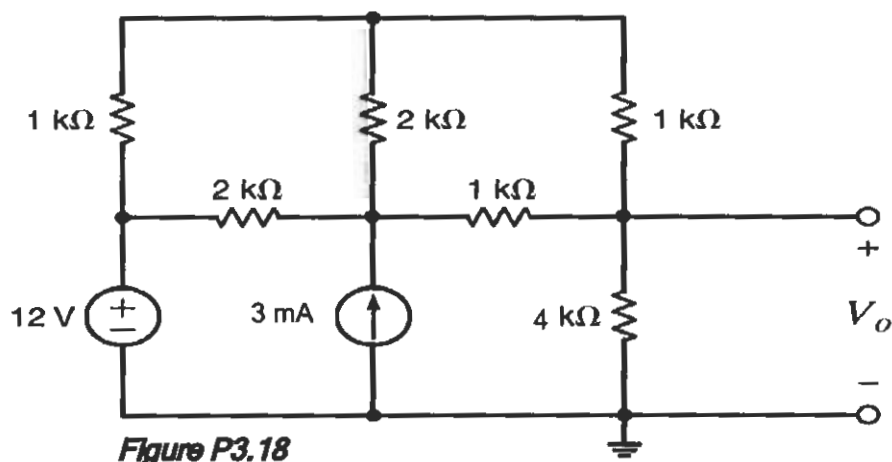


Figure P3.18

SOLUTION: 3-18

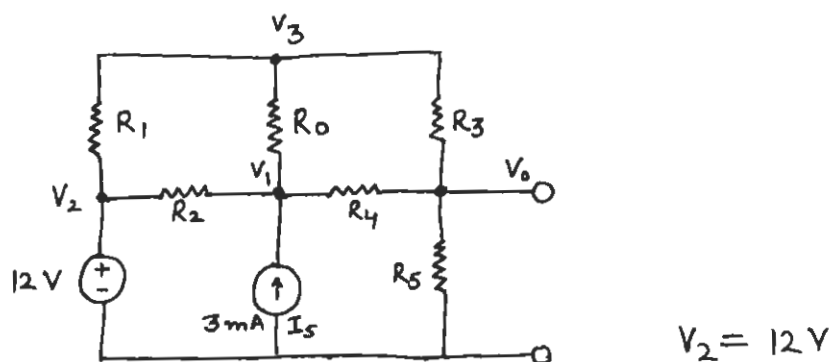

$$R_5 = 4k\Omega, R_1 = 1k\Omega, R_2 = 2k\Omega, R_3 = 1k\Omega, R_4 = 1k\Omega, R_o = 2k\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1 - V_o}{R_4} + \frac{V_1 - V_3}{R_o} + \frac{V_1 - V_2}{R_2} = I_s$$

$$\frac{V_1 - V_o}{1 \times 10^3} + \frac{V_1 - V_3}{2 \times 10^3} + \frac{V_1 - 12}{2 \times 10^3} = 3 \times 10^{-3}$$

$$2V_1 - 2V_o + V_1 - V_3 + V_1 - 12 = 6$$

$$4V_1 - V_3 - 2V_o = 18 \quad \text{--- (1)}$$

$$\text{KCL @ } V_3: \frac{V_3 - V_2}{R_1} + \frac{V_3 - V_1}{R_6} + \frac{V_3 - V_0}{R_3} = 0$$

$$\frac{V_3 - 12}{1 \times 10^3} + \frac{V_3 - V_1}{2 \times 10^3} + \frac{V_3 - V_0}{1 \times 10^3} = 0$$

$$-V_1 + 5V_3 - 2V_0 = 24 \quad \text{--- (2)}$$

$$\text{KCL @ } V_0: \frac{V_0 - V_3}{R_3} + \frac{V_0 - V_1}{R_4} + \frac{V_0}{R_5} = 0$$

$$\frac{V_0 - V_3}{1 \times 10^3} + \frac{V_0 - V_1}{1 \times 10^3} + \frac{V_0}{4 \times 10^3} = 0$$

$$-4V_1 - 4V_3 + 9V_0 = 0 \quad \text{--- (3)}$$

From equation (1)

$$V_1 = \frac{18 + V_3 + 2V_0}{4} \quad \text{--- (4)}$$

Substituting equation (4) in (2), we get

$$19V_3 - 10V_0 = 114 \quad \text{--- (5)}$$

Substituting equation (4) in (3), we get

$$-4V_1 - 4V_3 + 9V_0 = 0$$

$$-4 \left[ \frac{18 + V_3 + 2V_0}{4} \right] - 4V_3 + 9V_0 = 0$$

$$-5V_3 + 7V_0 = 18 \quad \text{--- (6)}$$

From equations (5) and (6), we get

$$83V_0 = 912$$

$$V_0 = \frac{912}{83} = 10.99$$

$$\boxed{V_0 = 11.0V}$$

3.19 Find  $I_o$  in the circuit in Fig. P3.19 using nodal analysis.


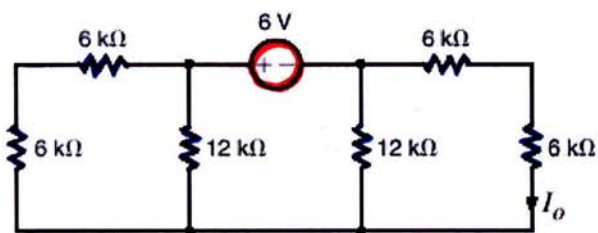


Figure P3.19

**SOLUTION:**

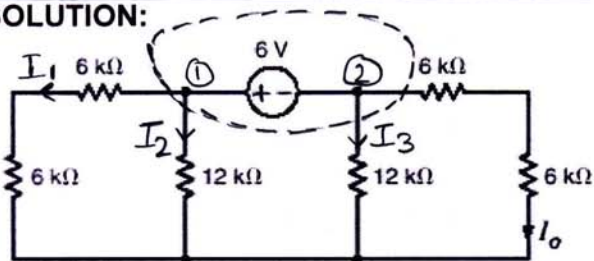

$$\text{KCL at supernode: } I_1 + I_2 + I_3 + I_o = 0$$

$$\frac{V_1}{6k + 6k} + \frac{V_1}{12k} + \frac{V_2}{12k} + \frac{V_2}{6k + 6k} = 0$$

$$V_1 + V_1 + V_2 + V_2 = 0$$

$$\boxed{2V_1 + 2V_2 = 0}$$

$$\boxed{V_1 - V_2 = 6}$$

$$2V_1 + 2V_2 = 0$$

$$V_1 - V_2 = 6$$

$$V_1 = 3 \text{ V}$$

$$V_2 = -3 \text{ V}$$

$$I_o = \frac{V_2}{12k}$$

$$= \frac{-3}{12k}$$

$$I_o = -0.25 \text{ mA}$$

3.20 Use nodal analysis to find  $I_o$  in the circuit in Fig. P3.20.


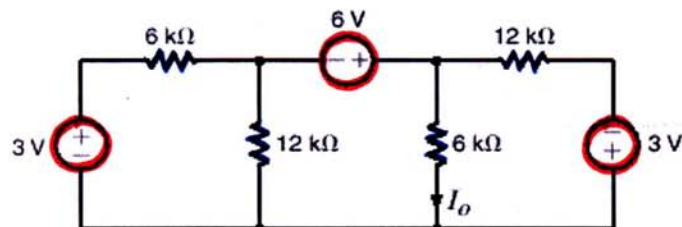


Figure P3.20

**SOLUTION:**

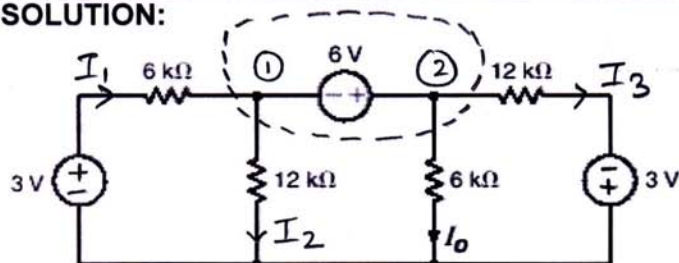

KCL at supernode :  $I = I_2 + I_o + I_3$

$$\frac{3 - V_1}{6K} = \frac{V_1}{12K} + \frac{V_2}{6K} + \frac{V_2 - (-3)}{12K}$$

$$6 - 2V_1 = V_1 + 2V_2 + V_2 + 3$$

$$\boxed{3V_1 + 3V_2 = 3}$$

$$V_2 - V_1 = 6$$

$$\boxed{-V_1 + V_2 = 6}$$

$$3V_1 + 3V_2 = 3$$

$$-V_1 + V_2 = 6$$

$$V_1 = -2.5 \text{ V}$$

$$V_2 = 3.5 \text{ V}$$

$$I_o = \frac{V_2}{6K}$$

$$= \frac{3.5}{6K}$$

$$I_o = 0.583 \text{ mA}$$



3.21 Using nodal analysis, find  $V_o$  in the network in Fig. P3.21.


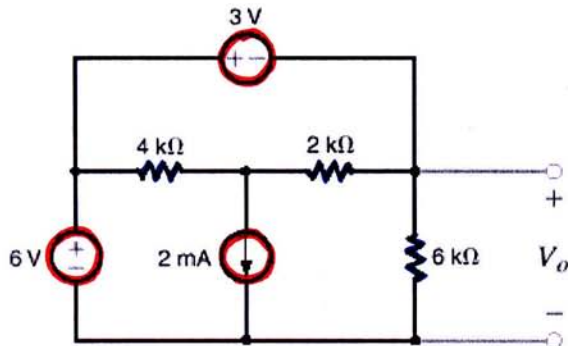


Figure P3.21

**SOLUTION:**

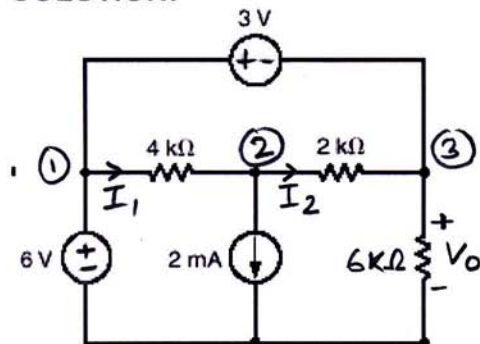

$$\text{KCL at } (2) : I_1 = 2\text{m} + I_2$$

$$\frac{V_1 - V_2}{4\text{K}} = 2\text{m} + \frac{V_2 - V_3}{2\text{K}}$$

$$V_1 - V_2 = 8 + 2V_2 - 2V_3$$

$$\boxed{3V_2 - 2V_3 = -2}$$

$$V_1 - V_3 = 3$$

$$-V_3 = 3 - 6$$

$$V_3 = 3\text{V}$$

$$V_o = V_3 = 3\text{V}$$

$$V_o = 3\text{V}$$

3.22 Find  $V_o$  in the network in Fig. P3.22 using nodal analysis.


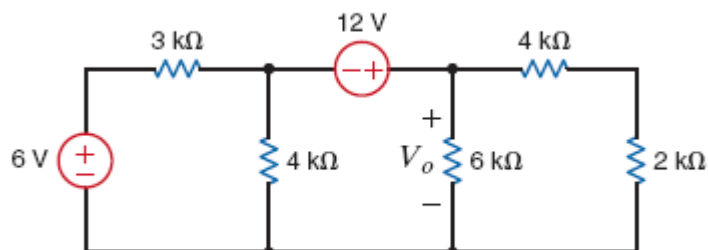


Figure P3.22

**SOLUTION:**

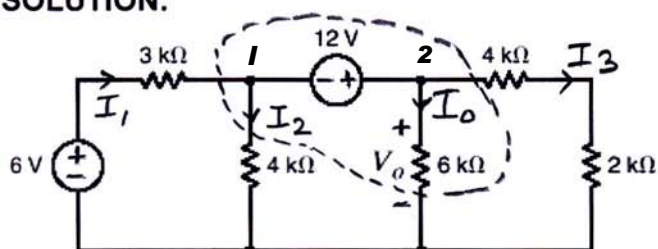

KCL at supernode :  $I_1 = I_2 + I_o + I_3$

$$\frac{6 - V_1}{3k} = \frac{V_1}{4k} + \frac{V_2}{6k} + \frac{V_2}{4k + 2k}$$

$$24 - 4V_1 = 3V_1 + 2V_2 + 2V_2$$

$$\boxed{7V_1 + 4V_2 = 24}$$

$$V_2 - V_1 = 12$$

$$\boxed{-V_1 + V_2 = 12}$$

$$\begin{aligned} 7V_1 + 4V_2 &= 24 \\ -V_1 + V_2 &= 12 \end{aligned}$$

$$V_1 = -2.18 \text{ V}$$

$$V_2 = 9.82 \text{ V}$$

$$V_o = V_2 = 9.82 \text{ V}$$

$$V_o = 9.82 \text{ V}$$

3.23 Find  $V_o$  in the circuit in Fig. P3.23 using nodal analysis.


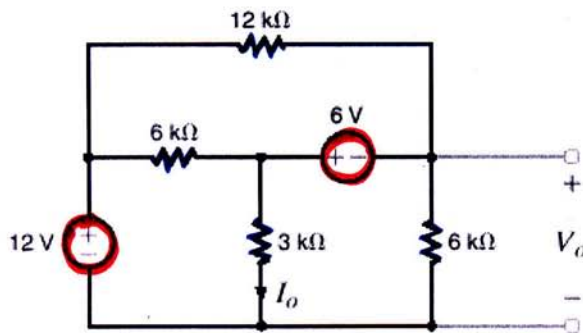


Figure P3.23

**SOLUTION:**

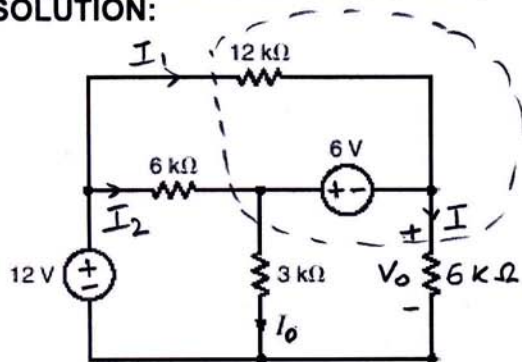

KCL at supernode:  $I_1 + I_2 = I_o + I$

$$\frac{V_1 - V_3}{12k} + \frac{V_1 - V_2}{6k} = \frac{V_2}{3k} + \frac{V_3}{6k}$$

$$V_1 - V_3 + 2V_1 - 2V_2 = 4V_2 + 2V_3$$

$$V_1 = 12V$$

$$6V_2 + 3V_3 = 36$$

$$V_2 - V_3 = 6$$

$$6V_2 + 3V_3 = 36$$

$$V_2 - V_3 = 6$$

$$V_2 = 6V$$

$$V_3 = 0V$$

$$V_o = V_3 = 0V$$

$$V_o = 0V$$

3.24 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.24.


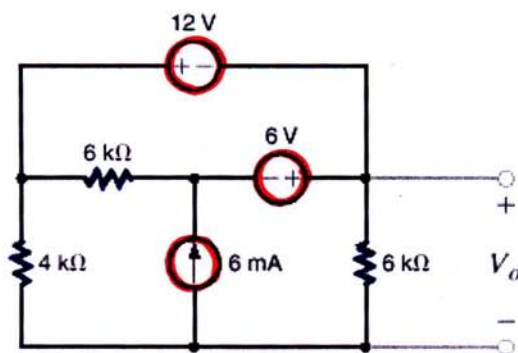


Figure P3.24

**SOLUTION:**

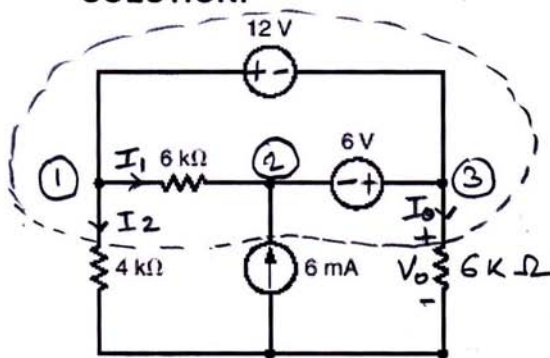

KCL at supernode :  $6\text{m} = I_2 + I_o$

$$\frac{V_1}{4\text{k}} + \frac{V_3}{6\text{k}} = 6\text{m}$$

$$3V_1 + 2V_3 = 72$$

$$V_1 - V_3 = 12$$

$$\begin{aligned} 3V_1 + 2V_3 &= 72 \\ V_1 - V_3 &= 12 \end{aligned}$$

$$V_1 = 19.2 \text{ V}$$

$$V_3 = 7.2 \text{ V}$$

$$V_o = V_3 = 7.2 \text{ V}$$

$$V_o = 7.2 \text{ V}$$

3.25 Find  $V_o$  in the circuit in Fig. P3.25.


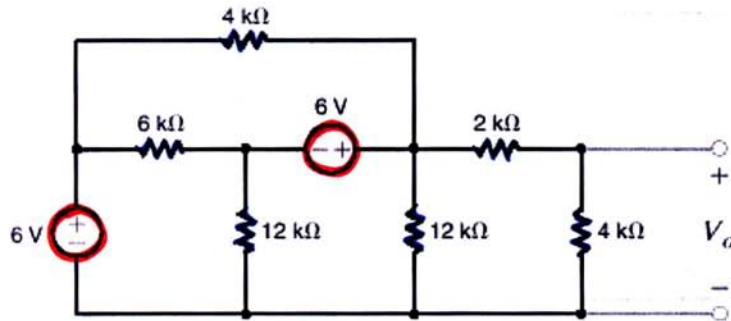


Figure P3.25

**SOLUTION:**

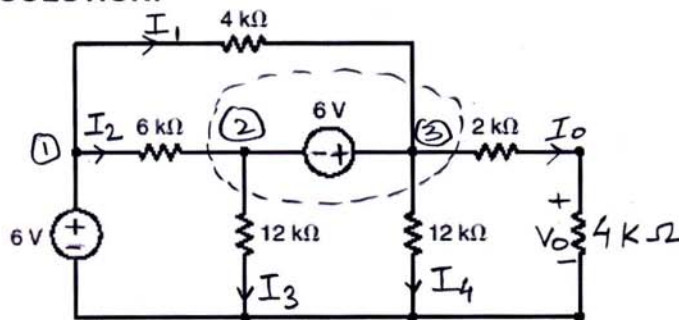

KCL at supernode:  $I_1 + I_2 = I_3 + I_4 + I_o$

$$\frac{V_1 - V_3}{4K} + \frac{V_1 - V_2}{6K} = \frac{V_2}{12K} + \frac{V_3}{12K} + \frac{V_3}{2K + 4K}$$

$$3V_1 - 3V_3 + 2V_1 - 2V_2 = V_2 + V_3 + 2V_3$$

$$V_1 = 6V$$

$$3V_2 + 6V_3 = 30$$

$$V_3 - V_2 = 6$$

$$-V_2 + V_3 = 6$$

$$\begin{aligned} 3V_2 + 6V_3 &= 30 \\ -V_2 + V_3 &= 6 \end{aligned}$$

$$V_2 = -0.667V$$

$$V_3 = 5.33V$$

$$I_o = \frac{V_3}{2K + 4K} = \frac{5.33}{6K} = 0.888mA$$

$$V_o = I_o(4K) = 0.888(4) = 3.55V$$

3.26 Find  $V_o$  in the circuit in Fig. P3.26 using nodal analysis.


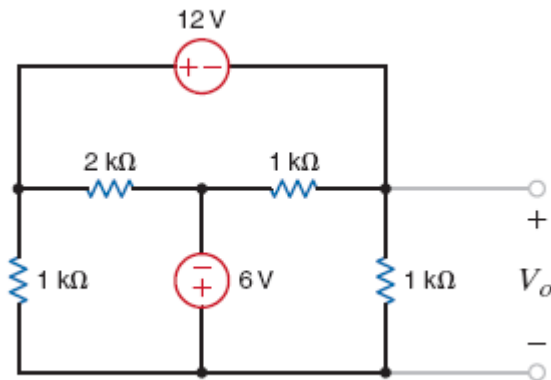


Figure P3.26

**SOLUTION:**

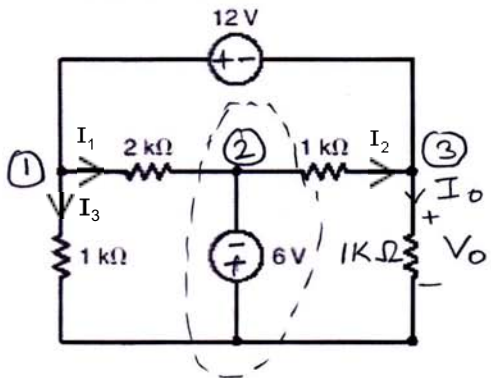

KCL at supernode:  $I_1 + I_3 + I_o = I_2$

$$\frac{V_1 - V_2}{2k} + \frac{V_1}{1k} + \frac{V_3}{1k} = \frac{V_2 - V_3}{1k}$$

$$V_1 - V_2 + 2V_1 + 2V_3 = 2V_2 - 2V_3$$

$$V_2 = -6V$$

$$3V_1 + 4V_3 = -18$$

$$V_1 - V_3 = 12$$

$$V_1 = 4.29V$$

$$V_3 = -7.71V$$

$$V_o = V_3 = -7.71V$$

$$V_o = -7.71V$$



3.27 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.27.


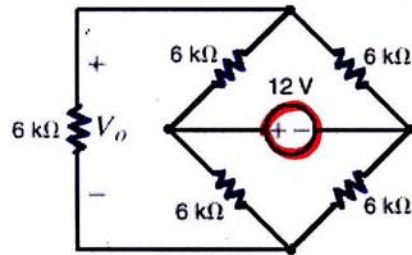


Figure P3.27

**SOLUTION:**

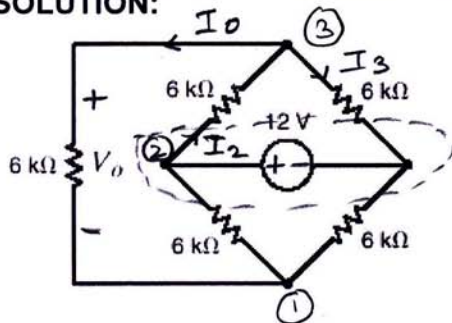

KCL at supernode:  $I_1 + I_4 + I_3 = I_2$

$$\frac{V_1}{6K} + \frac{V_1 - V_2}{6K} + \frac{V_3}{6K} = \frac{V_2 - V_3}{6K}$$

$$V_1 + V_1 - V_2 + V_3 = V_2 - V_3$$

$$\boxed{2V_1 - 2V_2 + 2V_3 = 0}$$

KCL at ①:  $I_0 = I_1 + I_4$

$$\frac{V_3 - V_1}{6K} = \frac{V_1}{6K} + \frac{V_1 - V_2}{6K}$$

$$V_3 - V_1 = V_1 + V_1 - V_2$$

$$\boxed{3V_1 - V_2 - V_3 = 0}$$

$$\boxed{V_2 = 12V}$$

$$\boxed{2V_1 + 2V_3 = 24}$$

$$\boxed{3V_1 - V_3 = 12}$$

$$2V_1 + 2V_3 = 24$$

$$3V_1 - V_3 = 12$$

$$\begin{aligned}2V_1 + 2V_3 &= 24 \\3V_1 - V_3 &= 12\end{aligned}$$

$$V_1 = 6 \text{ V}$$


$$V_3 = 6 \text{ V}$$

$$\begin{aligned}V_o &= V_3 - V_1 = 6 - 6 \\V_o &= 0 \text{ V}\end{aligned}$$

It should be noted that this circuit is a balanced Wheatstone bridge. Therefore, the output voltage is zero.




**3.28** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.28.

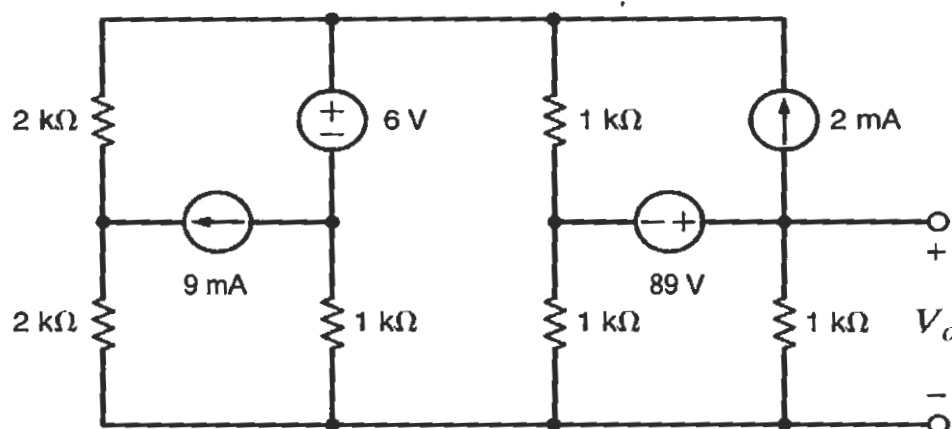

**Figure P3.28**

**SOLUTION:** 3.28

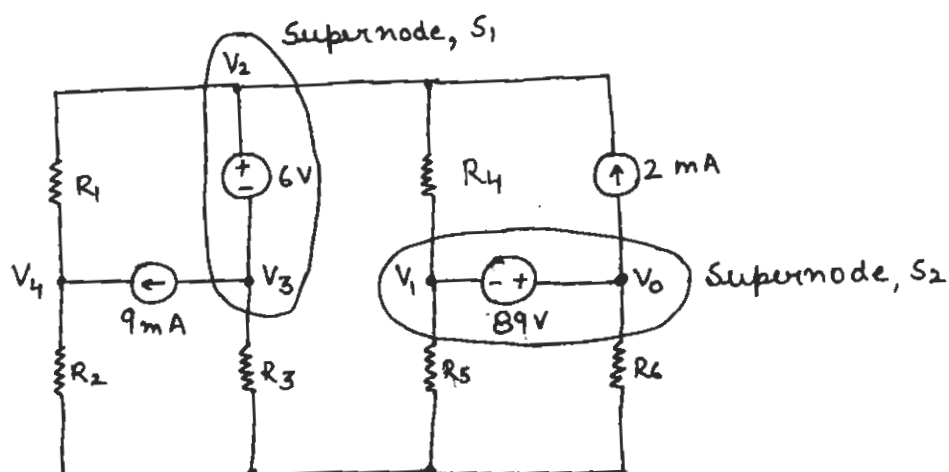

$$R_1 = R_2 = 2 \text{ k}\Omega, \quad R_3 = R_4 = R_5 = R_6 = 1 \text{ k}\Omega$$

$$V_2 - V_3 = 6 \text{ V} \quad \text{---} \quad (1)$$

$$V_o - V_1 = 89 \text{ V} \quad \text{---} \quad (2)$$

$$\text{KCL @ } S_1: \frac{V_2 - V_4}{R_1} + \frac{V_2 - V_1}{R_4} - 2 \times 10^{-3} + 9 \times 10^{-3} + \frac{V_3}{R_3} = 0$$

$$-2V_1 + 3V_2 + 2V_3 - V_4 = -14 \quad \text{---} \quad (3)$$

$$\text{KCL @ } S_2: 2 \times 10^{-3} + \frac{V_o}{R_6} + \frac{V_1 - V_2}{R_4} + \frac{V_1}{R_5} = 0$$

$$V_o + 2V_1 - V_2 = -2 \quad \text{---} \quad (4)$$

$$\text{KCL at } V_4: \frac{V_4 - V_2}{R_1} - 9 \times 10^{-3} + \frac{V_4}{R_2} = 0$$

$$V_4 = 9 + \frac{V_2}{2} \quad \text{---} \quad (5)$$

Substituting equations (1), (2) and (5) in (3), we get

$$-2(V_0 - 89) + 3V_2 + 2(V_2 - 6) - \left(9 + \frac{V_2}{2}\right) = -14$$

$$-4V_0 + 9V_2 = -342 \quad \text{---} \quad (6)$$

Substituting equation (1) in (4), we get

$$V_2 = 3V_0 - 176$$


Substituting the value of  $V_2$  in equation (6), we get

$$-4V_0 + 9(3V_0 - 176) = -342$$

$$V_0 = 53.7 \text{ V}$$


$$\boxed{V_0 = 54.0 \text{ V}}$$

**3.29** Find  $V_o$  in the network in Fig. P3.29.

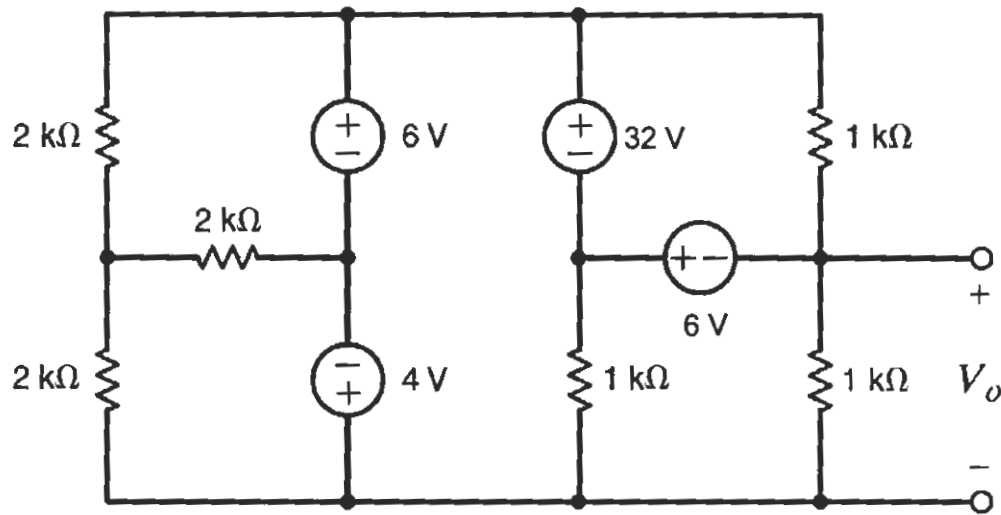


**Figure P3.29**

**SOLUTION:** 3.29

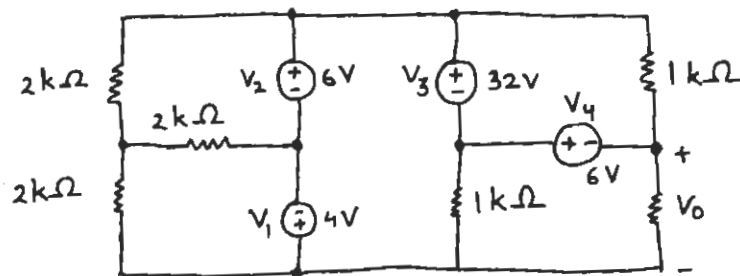


$$\begin{aligned}
 \text{KVL : } V_1 - V_2 + V_3 + V_4 + V_o &= 0 \\
 4 - 6 + 32 + 6 + V_o &= 0 \\
 36 + V_o &= 0 \\
 \boxed{V_o = -36.0 \text{ V}}
 \end{aligned}$$

**3.30** Find  $I_o$  in the circuit in Fig. P3.30 using nodal analysis.

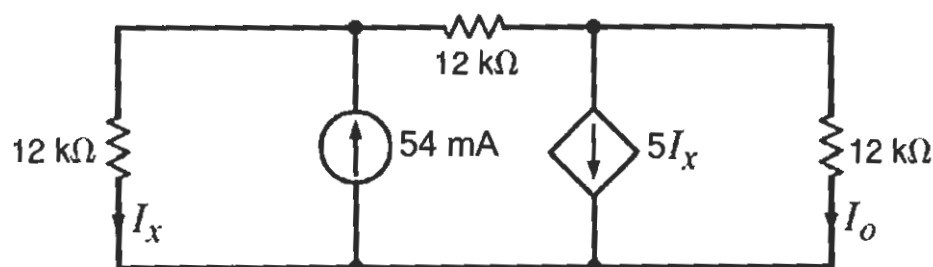

**Figure P3.30**

**SOLUTION:** 3.30

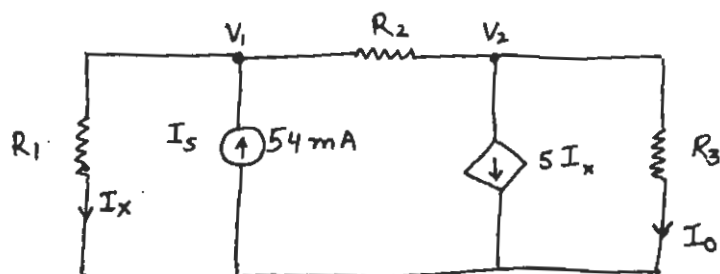

$$R_1 = R_2 = R_3 = 12 \text{ k}\Omega$$

$$\text{KCL @ } V_1 : \frac{V_1}{R_1} - I_s + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{12 \times 10^3} - 54 \times 10^{-3} + \frac{V_1 - V_2}{12 \times 10^3} = 0$$

$$2V_1 - V_2 = 648 \quad \text{--- (1)}$$

$$I_x = \frac{V_1}{R_1}$$

$$I_o = \frac{V_2}{R_3} \quad \text{--- (2)}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_2} + 5I_x + \frac{V_2}{R_3} = 0$$

$$\frac{V_2 - V_1}{12 \times 10^3} + 5 \cdot \frac{V_1}{12 \times 10^3} + \frac{V_2}{12 \times 10^3} = 0$$

$$2V_1 + V_2 = 0 \quad \text{---} \quad \textcircled{3}$$

From equations ① and ③, we get

$$V_2 = -324 \text{ V}$$

Substituting the value of  $V_2$  in equation ②, we get

$$I_0 = \frac{V_2}{R_3}$$

$$\boxed{I_0 = -27.0 \text{ mA}}$$

3.31 Find  $V_o$  in the circuit in Fig. P3.31 using nodal analysis.


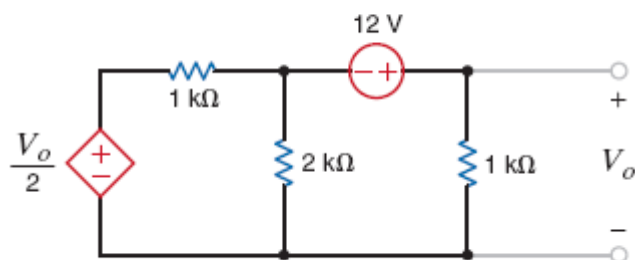


Figure P3.31

**SOLUTION:**

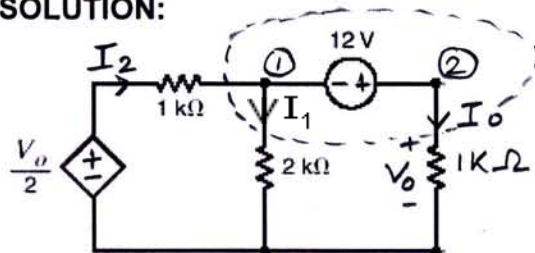

KCL at supernode:  $I_2 = I_1 + I_o$

$$\frac{\frac{V_o}{2} - V_1}{1K} = \frac{V_1}{2K} + \frac{V_2}{1K}$$

$$V_o = V_2$$

$$\frac{\frac{V_2}{2} - V_1}{1K} = \frac{V_1}{2K} + \frac{V_2}{1K}$$

$$V_2 - 2V_1 = V_1 + 2V_2$$

$$\boxed{3V_1 + V_2 = 0}$$

$$V_2 - V_1 = 12$$

$$\boxed{-V_1 + V_2 = 12}$$

$$3V_1 + V_2 = 0$$

$$-V_1 + V_2 = 12$$


$$V_1 = -3V$$

$$V_2 = 9 \text{ V}$$

$$V_0 = V_2 = 9 \text{ V}$$


$$V_0 = 9 \text{ V}$$

**3.32** Find  $V_o$  in the circuit in Fig. P3.32.

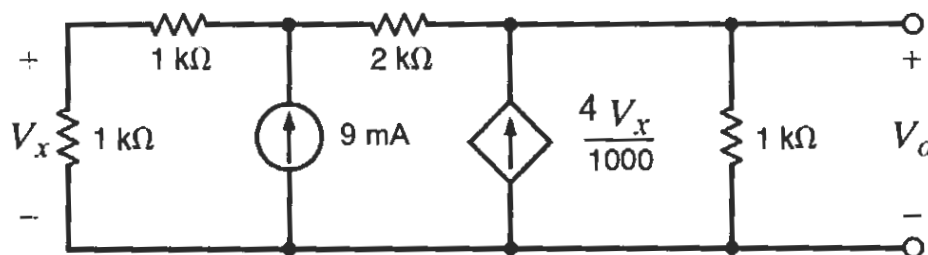

**Figure P3.32**

**SOLUTION:** 3.32

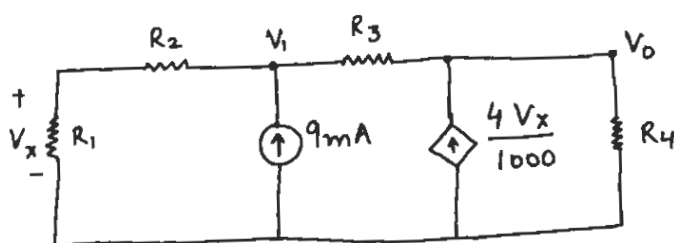

$$R_1 = R_2 = 1 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega$$

$$\text{KCL @ } V_1: \frac{V_1}{R_1 + R_2} - 9 \times 10^{-3} + \frac{V_1 - V_o}{R_3} = 0$$

$$\frac{V_1}{2 \times 10^3} + \frac{V_1 - V_o}{2 \times 10^3} = 9 \times 10^{-3}$$

$$2V_1 - V_o = 18 \quad \text{--- (1)}$$

$$\text{Voltage Division: } V_x = V_1 \frac{R_1}{R_1 + R_2}$$

$$V_x = \frac{V_1}{2} \quad \text{--- (2)}$$

$$\text{KCL @ } V_o: \frac{-4V_x}{1000} + \frac{V_o - V_1}{R_3} + \frac{V_o}{R_4} = 0$$

$$\frac{V_o - V_1}{2 \times 10^3} + \frac{V_o}{1 \times 10^3} = \frac{4V_x}{1000} \quad \text{--- (3)}$$

Substituting equation (2) in (3), we get

$$5V_1 - 3V_o = 0 \quad \text{--- (4)}$$

From equation (1) and (3), we get

$$\boxed{V_o = 90.0 \text{ V}}$$



3.33 Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.33.


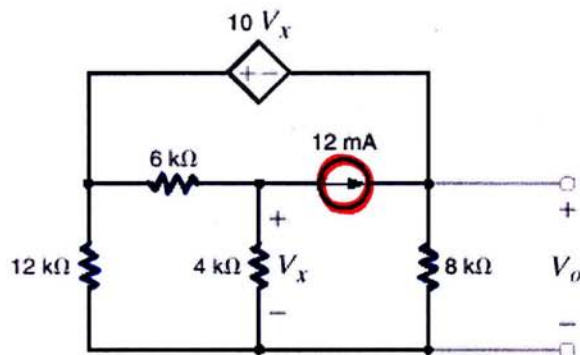


Figure P3.33

**SOLUTION:**

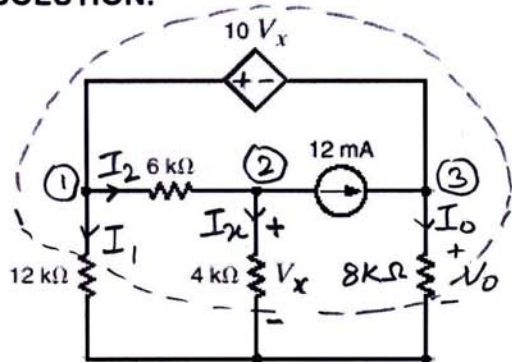

KCL at supernode:  $I_1 + I_x + I_o = 0$

$$\frac{V_1}{12K} + \frac{V_2}{4K} + \frac{V_3}{8K} = 0$$

$$2V_1 + 6V_2 + 3V_3 = 0$$

KCL at ②:  $I_2 = I_x + 12m$

$$\frac{V_1 - V_2}{6K} = \frac{V_2}{4K} + 12m$$

$$2V_1 - 2V_2 = 3V_2 + 144$$

$$2V_1 - 5V_2 = 144$$

$$V_1 - V_3 = 10V_x$$

$$V_x = V_2$$

$$V_1 - V_3 = 10V_2$$

$$V_1 - 10V_2 - V_3 = 0$$

$$2V_1 + 6V_2 + 3V_3 = 0$$

$$2V_1 - 5V_2 + 0V_3 = 144$$

$$V_1 - 10V_2 - V_3 = 0$$

$$V_1 = 150.26 \text{ V}$$


$$V_2 = 31.3 \text{ V}$$

$$V_3 = -162.78 \text{ V}$$

$$V_0 = V_3 = -162.78 \text{ V}$$


$$V_0 = -162.78 \text{ V}$$

**3.34** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.34.

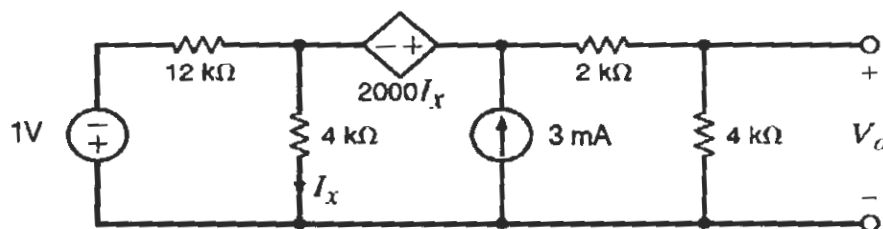

**Figure P3.34**

SOLUTION: 3.34

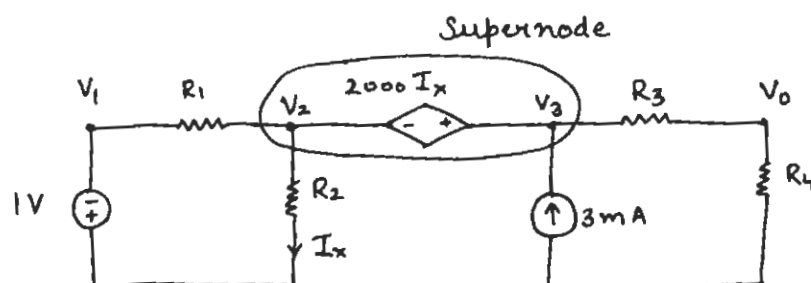

$$R_1 = 12 \text{ k}\Omega, R_2 = R_4 = 4 \text{ k}\Omega, R_3 = 2 \text{ k}\Omega$$

$$V_1 = -1 \text{ V} \quad \text{--- (1)}$$

$$V_3 - V_2 = 2000 I_x \quad \text{--- (2)}$$

$$I_x = \frac{V_2}{R_2} = \frac{V_2}{4 \times 10^3} \quad \text{--- (3)}$$

Substituting equation (3) in (2), we get

$$V_3 - \frac{3}{2} V_2 = 0$$

$$V_2 = \frac{2}{3} V_3 \quad \text{--- (4)}$$

KCL @ Supernode:

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3 - V_0}{R_3} - 3 \times 10^{-3} = 0$$

$$\frac{V_2 - V_1}{12 \times 10^3} + \frac{V_2}{4 \times 10^3} + \frac{V_3 - V_0}{2 \times 10^3} - 3 \times 10^{-3} = 0$$

$$6 V_3 + 4 V_2 - V_1 - 6 V_0 = 36 \quad \text{--- (5)}$$

KCL @  $V_0$  :  $\frac{V_0}{R_4} + \frac{V_0 - V_3}{R_3} = 0$

$$\frac{V_0}{4 \times 10^3} + \frac{V_0 - V_3}{2 \times 10^3} = 0$$

$$3 V_0 - 2 V_3 = 0$$

$$V_3 = \frac{3}{2} V_0 \quad \text{---} \quad (6)$$

Substituting equations (1) and (4) in (5), we get

$$26 V_3 - 18 V_0 = 105 \quad \text{---} \quad (7)$$

Substituting equation (6) in (7), we get

$$21 V_0 = 105$$

$$\boxed{V_0 = 5.00 \text{ V}}$$

3.35 Determine  $V_o$  in the network in Fig. P3.35 using nodal analysis.


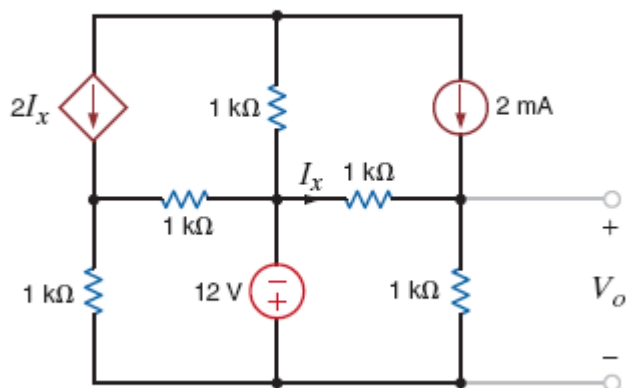


Figure P3.35

**SOLUTION:**

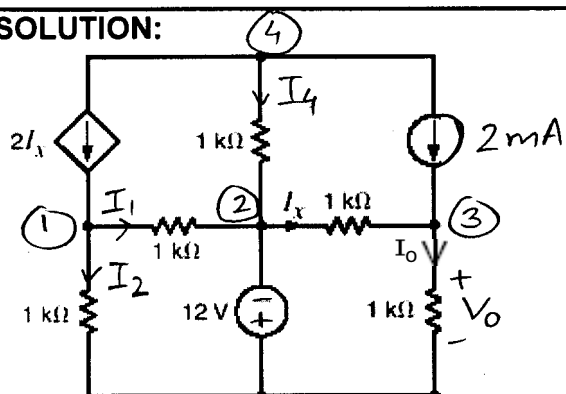

$$\text{KCL at } (4) : 2I_x + I_4 + 2\text{mA} = 0$$

$$I_x = \frac{V_2 - V_3}{1\text{K}}$$

$$2 \left[ \frac{V_2 - V_3}{1\text{K}} \right] + \frac{V_4}{1\text{K}} + 2\text{mA} = 0$$

$$2V_2 - 2V_3 + V_4 + 2 = 0$$

$$\boxed{2V_2 - 2V_3 + V_4 = -2}$$

$$\text{KCL at } \textcircled{3}: I_x + 2\text{m} = I_o$$

$$\frac{V_2 - V_3}{1\text{k}} + 2\text{m} = \frac{V_3}{1\text{k}}$$

$$V_2 - V_3 + 2 = V_3$$

$$\boxed{V_2 - 2V_3 = -2}$$

$$\text{KCL at } \textcircled{1}: 2I_x = I_1 + I_2$$

$$2 \left[ \frac{V_2 - V_3}{1\text{k}} \right] = \frac{V_1 - V_2}{1\text{k}} + \frac{V_1}{1\text{k}}$$

$$2V_2 - 2V_3 = V_1 - V_2 + V_1$$

$$\boxed{2V_1 - 3V_2 + 2V_3 = 0}$$

$$V_2 = -12\text{ V}$$

$$-12 - 2V_3 = -2$$

$$-2V_3 = 10$$

$$V_3 = -5\text{ V}$$

$$V_o = V_3 = -5\text{ V}$$

$$V_o = -5\text{ V}$$

3.36 Determine  $V_o$  in the network in Fig. P3.36.


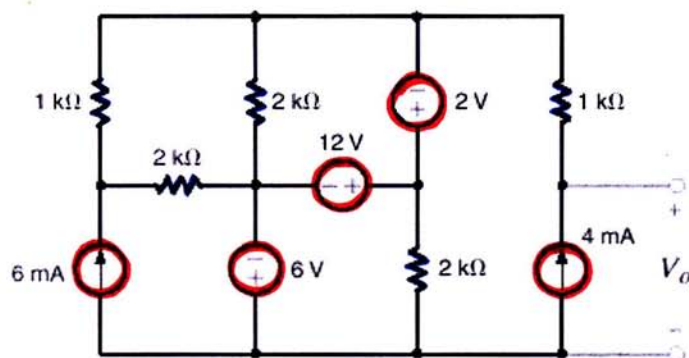


Figure P3.36

**SOLUTION:**

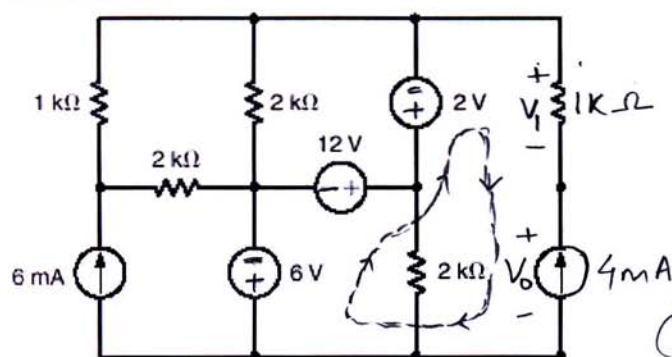

(Loop indicated by arrows)

$$V_1 = 1k(-4m) = -4V$$

$$\text{KVL in loop: } 12 = 6 + 2 + V_1 + V_o$$

$$V_o = 12 - 8 + 4$$

$$V_o = 8 V$$

3.37 Find  $I_o$  in the circuit in Fig. P3.37.


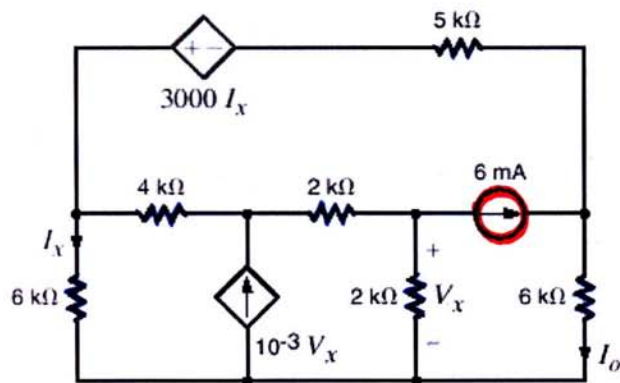


Figure P3.37

**SOLUTION:**

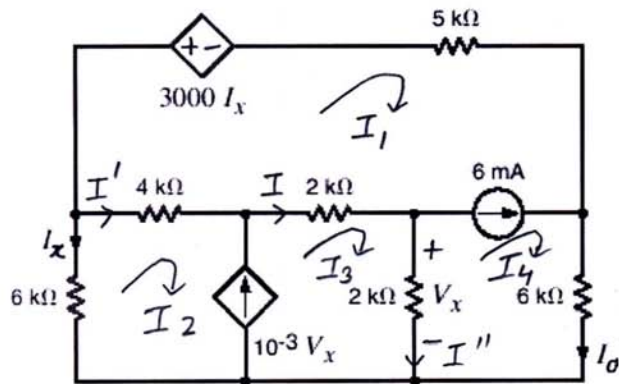

$$I_2 = -I_x \quad ; \quad I_4 = I_o$$

$$\text{KCL: } I_2 = I' + I_1 \\ I' = I_2 - I_1$$

$$\text{KCL: } I'' + I_4 = I_3 \\ I'' = I_3 - I_4$$

$$\text{KCL: } I = I'' + 6\text{ m} \\ I = I_3 - I_4 + 6\text{ m}$$

$$\text{KCL: } I_3 = 10^{-3} V_x + I_2 \\ -I_2 + I_3 = 10^{-3} V_x$$

$$V_x = 2\text{ k} I''$$

$$V_x = 2\text{ k} (I_3 - I_4)$$



$$-I_2 + I_3 = 10^{-3} (2K) (I_3 - I_4)$$

$$\boxed{I_2 + I_3 - 2I_4 = 0}$$

$$\text{KCL: } I_1 + 6\text{m} = I_4$$

$$\boxed{I_1 - I_4 = -6\text{m}}$$

$$\text{KVL: } 3000I_2 + 5KI_1 + 6KI_4 + 6KI_2 = 0$$

$$3000(-I_2) + 5KI_1 + 6KI_4 + 6KI_2 = 0$$

$$\boxed{5KI_1 + 3KI_2 + 6KI_4 = 0}$$

$$\text{KVL: } 4KI' + 2KI + 2KI'' + 6KI_2 = 0$$

$$0 = 4K(I_2 - I_1) + 2K(I_3 - I_4 + 6\text{m}) + 2K(I_3 - I_4) + 6KI_2$$

$$\boxed{-4KI_1 + 10KI_2 + 4KI_3 - 4KI_4 = -12}$$

$$I_2 + I_3 - 2I_4 = 0$$

$$I_1 - I_4 = -6\text{m}$$

$$5KI_1 + 3KI_2 + 6KI_4 = 0$$

$$-4KI_1 + 10KI_2 + 4KI_3 - 4KI_4 = -12$$

$$I_1 = -1.64 \text{ mA}$$

$$I_2 = -6 \text{ mA}$$

$$I_3 = 14.7 \text{ mA}$$

$$I_4 = 4.36 \text{ mA}$$

$$I_0 = I_4$$

$$I_0 = 4.36 \text{ mA}$$

3.38 Use nodal analysis to solve for  $I_A$  in the network in Fig. P3.38.


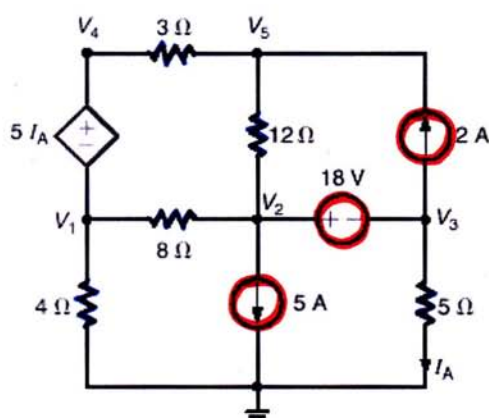


Figure P3.38

**SOLUTION:**

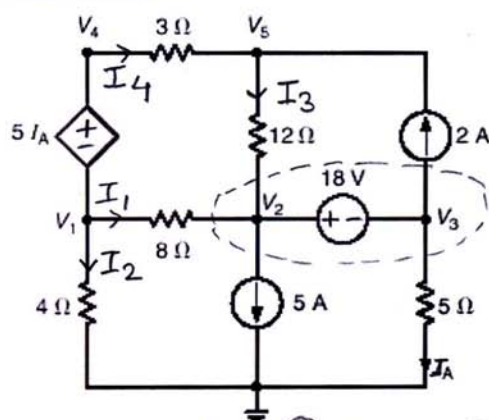

$$\text{KCL at } \textcircled{5}: \quad I_4 + 2 = I_3$$

$$\frac{V_4 - V_5}{3} + 2 = \frac{V_5 - V_2}{12}$$

$$4V_4 - 4V_5 + 24 = V_5 - V_2$$

$$\boxed{V_2 + 4V_4 - 5V_5 = -24}$$

$$\text{KCL at supernode: } I_3 + I_1 = 5 + I_A + 2$$

$$\frac{V_5 - V_2}{12} + \frac{V_1 - V_2}{8} = 5 + \frac{V_3}{5} + 2$$

$$5V_5 - 5V_2 + 7.5V_1 - 7.5V_2 = 300 + 12V_3 + 120$$

$$\boxed{7.5V_1 - 12.5V_2 - 12V_3 + 5V_5 = 420}$$

$$V_4 - V_1 = 5I_A$$

$$I_A = \frac{V_3}{5}$$

$$V_4 - V_1 = 5(V_3/5)$$

$$V_4 - V_1 = V_3$$

$$-V_1 - V_3 + V_4 = 0$$

$$V_2 - V_3 = 18$$

KCL at reference:  $I_2 + 5 + I_A = 0$

$$\frac{V_1}{4} + 5 + \frac{V_3}{5} = 0$$

$$5V_1 + 100 + 4V_3 = 0$$

$$5V_1 + 4V_3 = -100$$

$$0V_1 + V_2 + 0V_3 + 4V_4 - 5V_5 = -24$$

$$7.5V_1 - 12.5V_2 - 12V_3 + 0V_4 + 5V_5 = 420$$

$$-V_1 + 0V_2 - V_3 + V_4 + 0V_5 = 0$$

$$0V_1 + V_2 - V_3 + 0V_4 + 0V_5 = 18$$

$$5V_1 + 0V_2 + 4V_3 + 0V_4 + 0V_5 = -100$$

$$V_1 = 3.22 \text{ V}$$

$$V_2 = -11.02 \text{ V}$$

$$V_3 = -29.02 \text{ V}$$

$$V_4 = -25.81 \text{ V}$$

$$V_5 = -18.05 \text{ V}$$

$$I_A = \frac{V_3}{5} = \frac{-29.02}{5}$$

$$I_A = -5.8 \text{ A}$$

3.39 Use nodal analysis to find  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  in the circuit in Fig. P3.39.


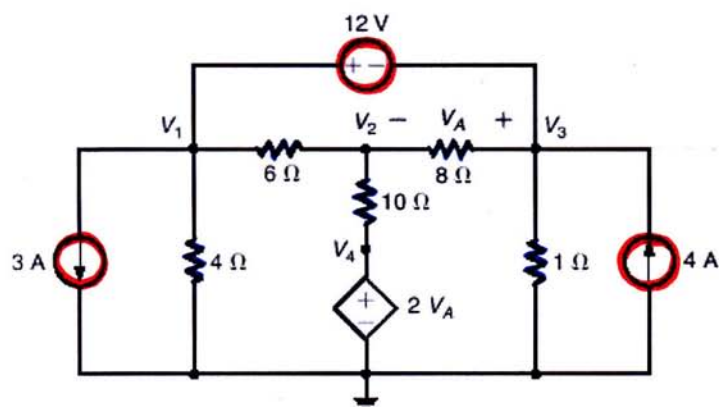


Figure P3.39

**SOLUTION:**

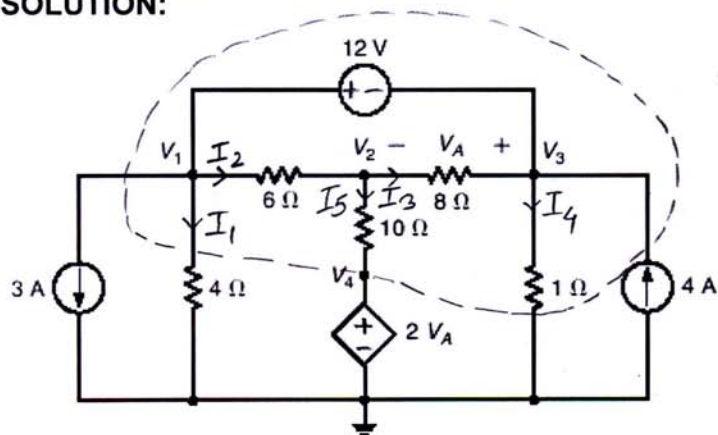

KCL at (2):  $I_2 = I_5 + I_3$

$$\frac{V_1 - V_2}{6} = \frac{V_2 - V_4}{10} + \frac{V_2 - V_3}{8}$$

$$5V_1 - 5V_2 = 3V_2 - 3V_4 + 3.75V_2 - 3.75V_3$$

$$5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 = 0$$

KCL at supernode:  $3 + I_1 + I_5 + I_4 = 4$

$$\frac{V_1}{4} + \frac{V_2 - V_4}{10} + \frac{V_3}{1} = 1$$

$$5V_1 + 2V_2 - 2V_4 + 20V_3 = 20$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 - V_3 = 12$$

$$V_4 = 2V_A$$

$$V_A = V_3 - V_2$$

$$V_4 = 2(V_3 - V_2)$$

$$-2V_2 + 2V_3 - V_4 = 0$$

$$5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 = 0$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 + 0V_2 - V_3 + 0V_4 = 12$$

$$0V_1 - 2V_2 + 2V_3 - V_4 = 0$$

$$V_1 = 9.68 \text{ V}$$

$$V_2 = 1.45 \text{ V}$$

$$V_3 = -2.32 \text{ V}$$

$$V_4 = -7.54 \text{ V}$$



3.40 Use nodal analysis to find  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  in the network in Fig. P3.40


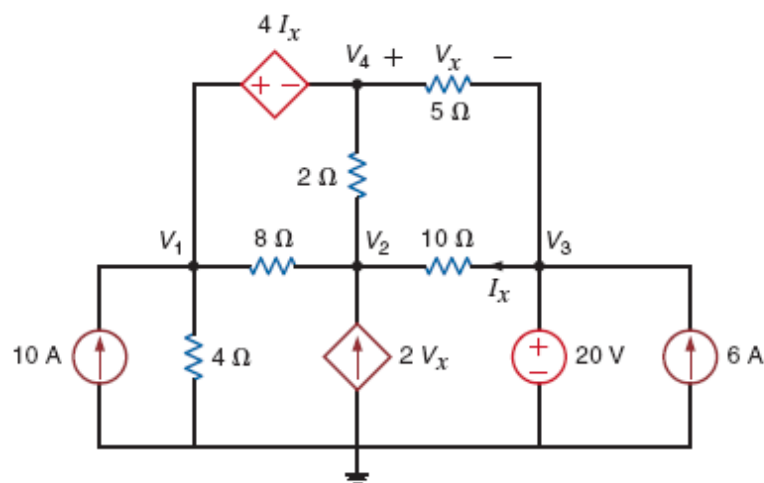


Figure P3.40

**SOLUTION:**

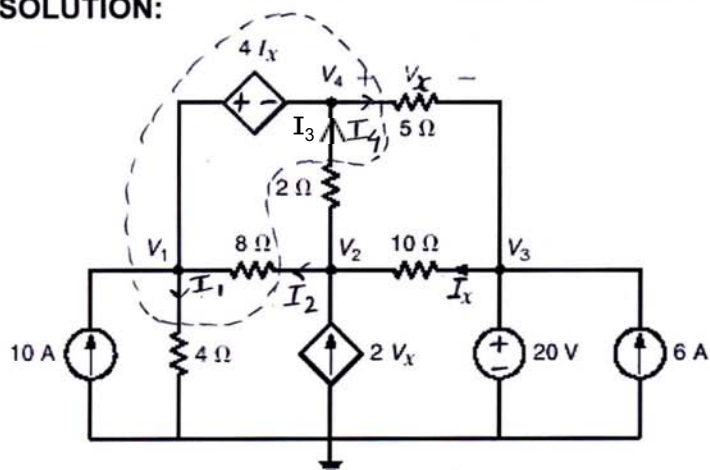

$$\text{KCL at } \textcircled{2}: 2V_x + I_x = I_2 + I_3$$

$$V_x = V_4 - V_3$$

$$2(V_4 - V_3) + \frac{V_3 - V_2}{10} = \frac{V_2 - V_1}{8} + \frac{V_2 - V_4}{2}$$

$$80V_4 - 80V_3 + 4V_3 - 4V_2 = 5V_2 - 5V_1 + 20V_2 - 20V_4$$

$$\boxed{5V_1 - 29V_2 - 76V_3 + 100V_4 = 0}$$

$$V_3 = 20\text{ V}$$

$$\boxed{5V_1 - 29V_2 + 100V_4 = 1520}$$

$$\text{KCL at supernode: } 10 + I_2 + I_3 = I_1 + I_4$$

$$10 + \frac{V_2 - V_1}{8} + \frac{V_2 - V_4}{2} = \frac{V_1}{4} + \frac{V_4 - V_3}{5}$$

$$400 + 5V_2 - 5V_1 + 20V_2 - 20V_4 = 10V_1 + 8V_4 - 8V_3$$

$$\boxed{-15V_1 + 25V_2 + 8V_3 - 28V_4 = -400}$$

$$\boxed{-15V_1 + 25V_2 - 28V_4 = -560}$$

$$V_1 - V_4 = 4I_x$$

$$I_x = \frac{V_3 - V_2}{10}$$

$$V_1 - V_4 = 4 \left( \frac{V_3 - V_2}{10} \right)$$

$$10V_1 - 10V_4 = 4V_3 - 4V_2$$

$$\boxed{10V_1 + 4V_2 - 4V_3 - 10V_4 = 0}$$

$$\boxed{10V_1 + 4V_2 - 10V_4 = 80}$$

$$5V_1 - 24V_2 + 100V_4 = 1520$$

$$-15V_1 + 25V_2 - 28V_4 = -560$$

$$10V_1 + 4V_2 - 10V_4 = 80$$


$$V_1 = 21.14 \text{ V}$$

$$V_2 = 9.07 \text{ V}$$

$$V_4 = 16.77 \text{ V}$$


$$V_3 = 20 \text{ V}$$

**3.41** Find  $I_o$  in the network in Fig. P3.41 using nodal analysis.

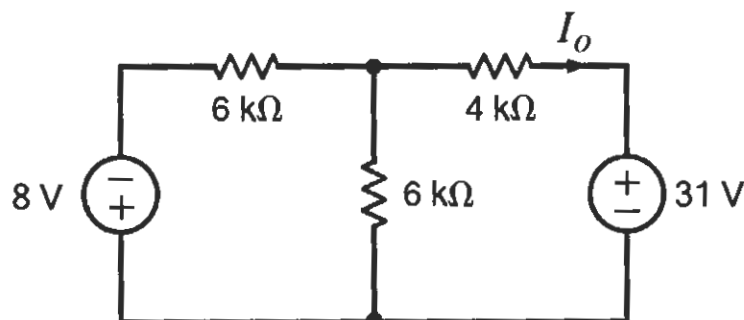

**Figure P3.41**

**SOLUTION:** 3.41

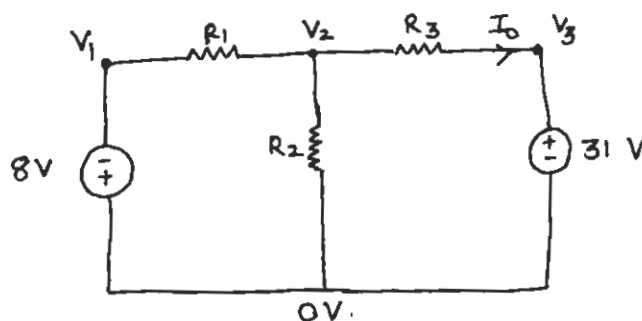

$$R_1 = R_2 = 6 \text{ k}\Omega, \quad R_3 = 4 \text{ k}\Omega, \quad I_o = \frac{V_2 - V_3}{R_3} \quad \text{--- (1)}$$

$$\text{@ } V_1 : \quad V_1 = -8 \text{ V} \quad \text{--- (2)}$$

$$\text{KCL @ } V_2 : \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$\frac{V_2 - V_1}{6 \times 10^3} + \frac{V_2}{6 \times 10^3} + \frac{V_2 - V_3}{4 \times 10^3} = 0$$

$$7V_2 - 3V_3 - 2V_1 = 0 \quad \text{--- (3)}$$

$$\text{@ } V_3 : \quad V_3 = 31 \text{ V} \quad \text{--- (4)}$$

Substituting equations (4) and (2) in (3), we get

$$7V_2 - 3V_3 - 2V_1 = 0$$

$$7V_2 - 3(31) - 2(-8) = 0$$

$$V_2 = 11 \text{ V} \quad \text{--- (5)}$$



Substituting equations ④ and ⑤ in ①, we get

$$I_0 = \frac{V_2 - V_3}{R_3}$$

$$I_0 = -5.00 \text{ mA}$$

**3.42** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.42.


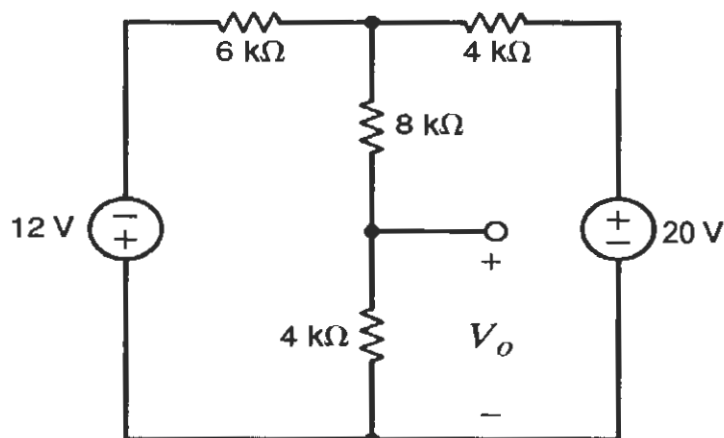


Figure P3.42

SOLUTION: 3.42

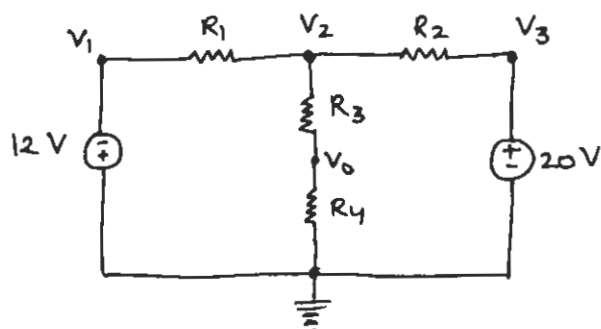

$$R_1 = 6 \text{ k}\Omega, \quad R_2 = R_4 = 4 \text{ k}\Omega, \quad R_3 = 8 \text{ k}\Omega$$

$$V_1 = -12 \text{ V}; \quad V_3 = 20 \text{ V}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_o}{R_3} + \frac{V_2 - V_3}{R_2} = 0$$

$$\frac{V_2 + 12}{6 \times 10^3} + \frac{V_2 - V_o}{8 \times 10^3} + \frac{V_2 - 20}{4 \times 10^3} = 0$$

$$\Rightarrow 13V_2 - 3V_o = 72 \quad \text{--- (1)}$$

$$\text{KCL @ } V_o : \frac{V_o}{R_4} + \frac{V_o - V_2}{R_3} = 0$$

$$\frac{V_o}{4 \times 10^3} + \frac{V_o - V_2}{8 \times 10^3} = 0$$

$$\Rightarrow 3V_o - V_2 = 0 \quad \text{--- (2)}$$

From equations ① and ②, we get

$$12 V_2 = 72$$


$$V_2 = 6 \text{ V}$$

Substituting the value of  $V_2$  in Equation ②, we get

$$3V_0 - V_2 = 0$$


$$V_0 = 2.00 \text{ V}$$

**3.43** Find  $I_o$  in the circuit in Fig. P3.43.

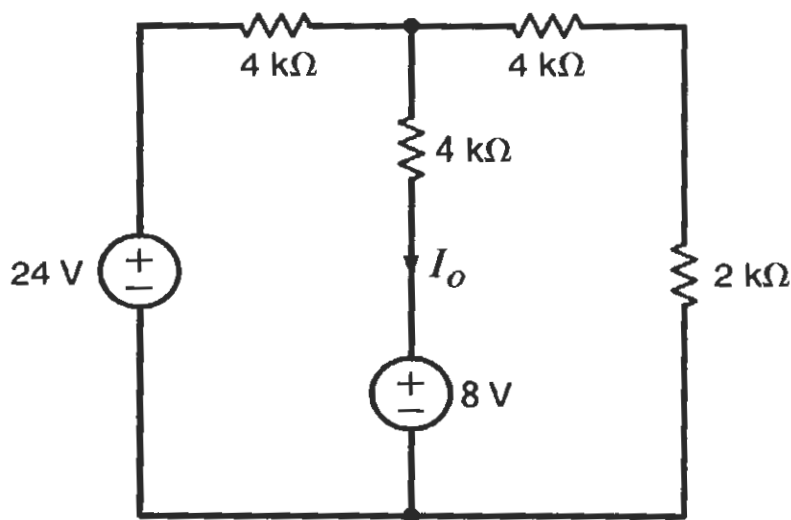

**Figure P3.43**

**SOLUTION:** 3.43

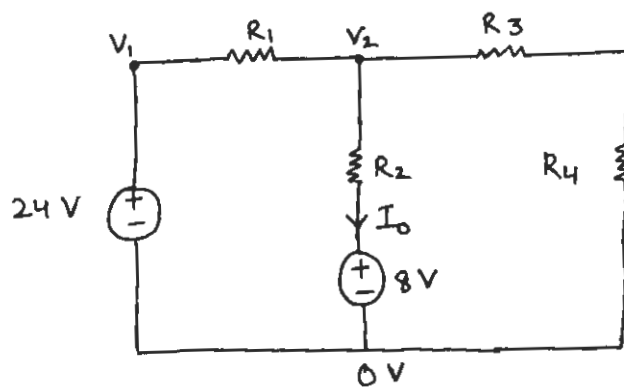

$$R_1 = R_2 = R_3 = 4 \text{ k}\Omega, R_4 = 2 \text{ k}\Omega$$

$$\text{@ } V_1: V_1 = 24 \text{ V} \quad \text{--- ①}$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2 - 8}{R_2} + \frac{V_2}{R_3 + R_4} = 0$$

$$\frac{V_2 - V_1}{4 \times 10^3} + \frac{V_2 - 8}{4 \times 10^3} + \frac{V_2}{6 \times 10^3} = 0$$

$$\Rightarrow 8V_2 - 3V_1 = 24 \quad \text{--- ②}$$

Substituting equation ① in ②, we get


$$8V_2 - 3V_1 = 24$$

$$\Rightarrow V_2 = 12 \text{ V}$$

$$I_0 = \frac{V_2 - 8}{R_2}$$


$$I_0 = 1.00 \text{ mA}$$

**3.44** Find  $V_o$  in the network in Fig. P3.44 using mesh equations.

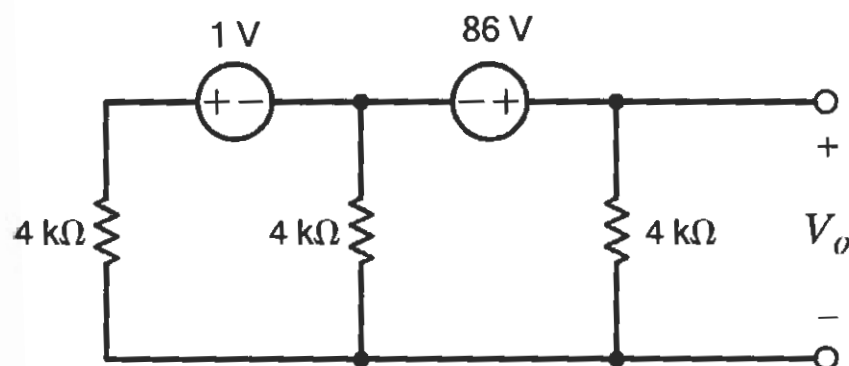

**Figure P3.44**

**SOLUTION:** 3.44

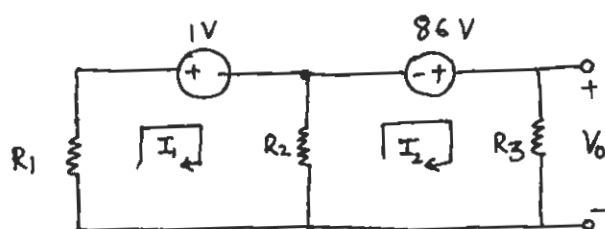

$$R_1 = R_2 = R_3 = 4 \text{ k}\Omega$$

$$\text{KVL @ } I_1 : I_1 R_1 + 1 + (I_1 - I_2) R_2 = 0$$

$$I_1 (4 \times 10^3) + (I_1 - I_2) (4 \times 10^3) = -1$$

$$8 I_1 - 4 I_2 = -1 \times 10^{-3} \quad \text{①}$$

$$\text{KVL @ } I_2 : (I_2 - I_1) R_2 - 86 + I_2 R_3 = 0$$

$$(I_2 - I_1) (4 \times 10^3) + I_2 (4 \times 10^3) = 86$$

$$-8 I_1 + 16 I_2 = 172 \times 10^{-3} \quad \text{②}$$

From equations ① and ②, we get

$$12 I_2 = 171 \times 10^{-3}$$

$$I_2 = \frac{171}{12} \times 10^{-3} \text{ A}$$

$$\begin{aligned}V_0 &= I_2 R_3 \\&= \frac{171}{12} \times 10^{-3} \times 4 \times 10^3 \\V_0 &= 57.0V\end{aligned}$$

3.45 Find  $V_o$  in the network in Fig. P3.45 using mesh equations.


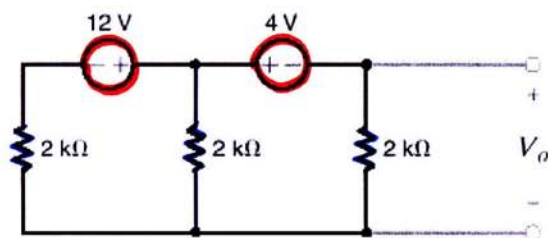


Figure P3.45

**SOLUTION:**

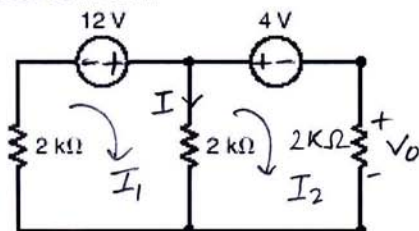

$$I_1 = I + I_2$$

$$I = I_1 - I_2$$

KVL left loop:  $12 = 2KI_1 + 2KI$

$$2KI_1 + 2K(I_1 - I_2) = 12$$

$$\boxed{4KI_1 - 2KI_2 = 12}$$

KVL right loop:  $4 + 2KI_2 + 2K(-I) = 0$

$$2KI_2 - 2K(I_1 - I_2) = -4$$

$$\boxed{-2KI_1 + 4KI_2 = -4}$$

$$4KI_1 - 2KI_2 = 12$$

$$-2KI_1 + 4KI_2 = -4$$

$$I_1 = 3.333 \text{ mA} \quad ; \quad I_2 = 0.667 \text{ mA}$$

$$V_o = I_2(2K) = 0.667 \text{ m}(2K)$$

$$V_o = 1.33 \text{ V}$$



3.46 Find  $I_o$  in the circuit in Fig. P3.46.


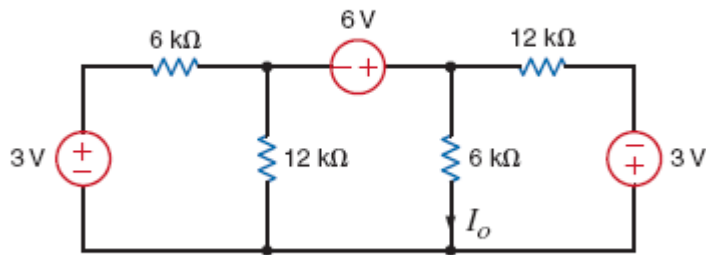


Figure P3.46

**SOLUTION:**

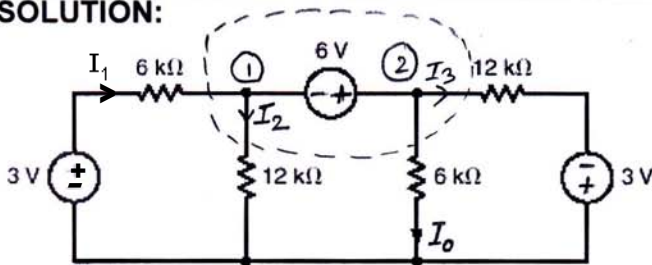

KCL at supernode:  $I_1 = I_2 + I_o + I_3$

$$\frac{3 - V_1}{6K} = \frac{V_1}{12K} + \frac{V_2}{6K} + \frac{V_2 - (-3)}{12K}$$

$$6 - 2V_1 = V_1 + 2V_2 + V_2 + 3$$

$$\boxed{3V_1 + 3V_2 = 3}$$

$$V_2 - V_1 = 6$$

$$\boxed{-V_1 + V_2 = 6}$$

$$3V_1 + 3V_2 = 3$$

$$-V_1 + V_2 = 6$$


$$V_1 = -2.5 \text{ V}$$

$$V_2 = 3.5 \text{ V}$$

$$I_o = \frac{V_2}{6K} = \frac{3.5}{6K}$$


$$I_o = 0.5833 \text{ mA}$$

**3.47** Find  $V_o$  in the circuit in Fig. P3.47 using nodal analysis.

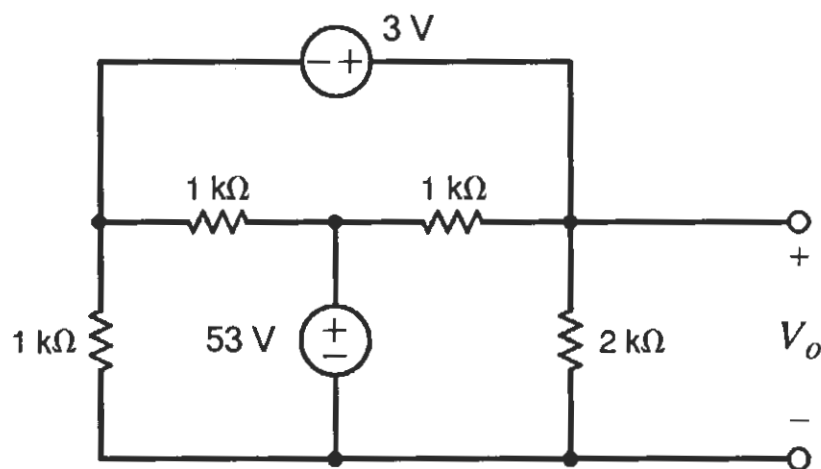

**Figure P3.47**

**SOLUTION: 3.47**

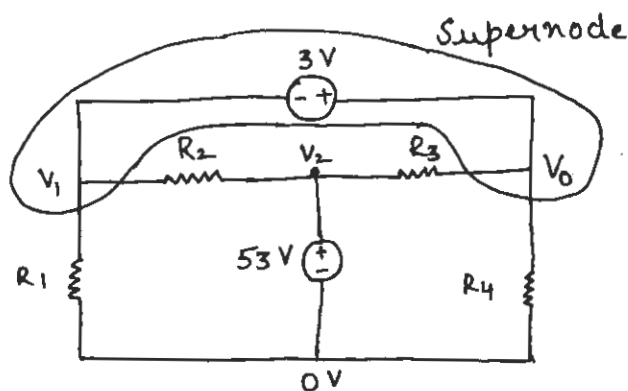

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, R_4 = 2 \text{ k}\Omega$$

$$V_o - V_1 = 3 \text{ V} \quad \text{--- ①}$$

$$V_2 = 53 \text{ V}$$

KVL @ supernode,

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_o}{R_4} + \frac{V_o - V_2}{R_3} = 0$$

$$4V_1 + 3V_o = 212 \quad \text{--- ②}$$

Substituting equation ① in ②, we get

$$4(V_o - 3) + 3V_o = 212$$

$$\boxed{V_o = 32.0 \text{ V}}$$

3.48 Solve Problem 3.23 using loop analysis.


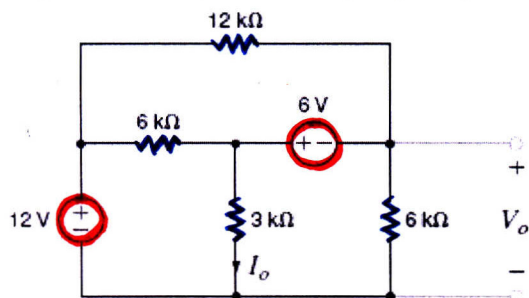


Figure P3.23

**SOLUTION:**

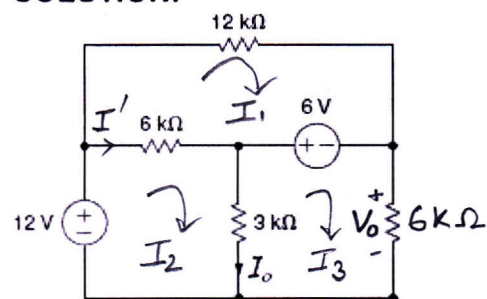

$$\text{KCL: } I_2 = I' + I_1$$

$$I' = I_2 - I_1$$

$$\text{KVL: } 12KI_1 + 6KI_3 = 12$$

$$\text{KCL: } I_o + I_3 = I_2$$

$$I_o = I_2 - I_3$$

$$\text{KVL: } 6 + 6KI_3 + 3K(-I_o) = 0$$

$$6 + 6KI_3 - 3K(I_2 - I_3) = 0$$

$$-3KI_2 + 9KI_3 = -6$$

$$\text{KVL: } 12 = 6KI + 6 + 6KI_3$$

$$6K(I_2 - I_1) + 6KI_3 = 6$$

$$-6KI_1 + 6KI_2 + 6KI_3 = 6$$

$$12KI_1 + 0I_2 + 6KI_3 = 12$$

$$0I_1 - 3KI_2 + 9KI_3 = -6$$

$$-6KI_1 + 6KI_2 + 6KI_3 = 6$$

$$I_1 = 1 \text{ mA}$$

$$I_2 = 2 \text{ mA}$$

$$I_3 = 0 \text{ A}$$

$$V_o = 6 \text{ k}\Omega I_3$$

$$V_o = 6 \text{ k}\Omega (0)$$

$$V_o = 0 \text{ V}$$

3.49 Solve Problem 3.27 using loop analysis.


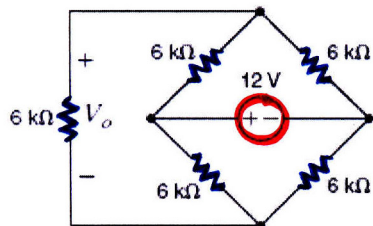


Figure P3.27

**SOLUTION:**

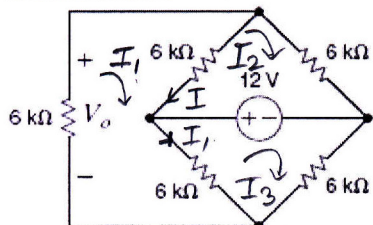

$$\begin{aligned} \text{KCL : } I_1 &= I + I_2 \\ I &= I_1 - I_2 \end{aligned}$$

$$\begin{aligned} \text{KCL : } I' + I_3 &= I_1 \\ I' &= I_1 - I_3 \end{aligned}$$

$$\text{KVL : } \boxed{6KI_1 + 6KI_2 + 6KI_3 = 0}$$

$$\begin{aligned} \text{KVL : } 12 &= 6K(-I) + 6KI_2 \\ &= -6K(I_1 - I_2) + 6KI_2 = 12 \end{aligned}$$


$$\boxed{-6KI_1 + 12KI_2 = 12}$$

$$\begin{aligned} 6KI_1 + 6KI_2 + 6KI_3 &= 0 \\ 18KI_1 - 6KI_2 - 6KI_3 &= 0 \\ -6KI_1 + 12KI_2 + 0I_3 &= 12 \end{aligned}$$

$$\begin{aligned} I_1 &= 0 \text{ A} \\ I_2 &= 1 \text{ mA} \\ I_3 &= -1 \text{ mA} \end{aligned}$$


$$\begin{aligned} V_o &= -I_1(6K) \\ V_o &= 0 \text{ V} \end{aligned}$$

**3.50** Use loop analysis to find  $V_o$  in the network in Fig. P3.50.

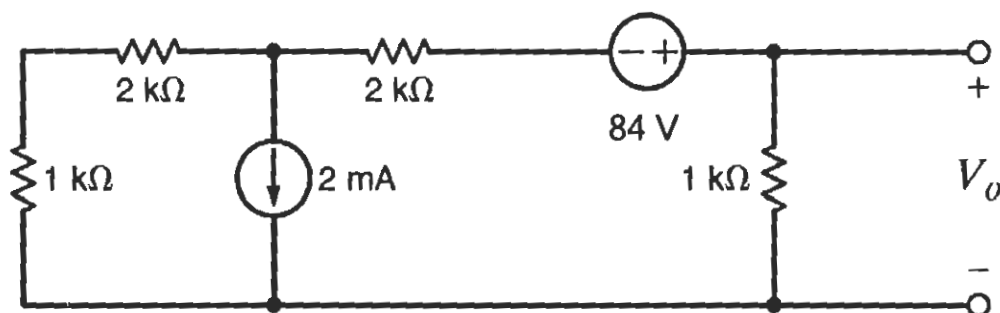

**Figure P3.50**

**SOLUTION:** 3.50

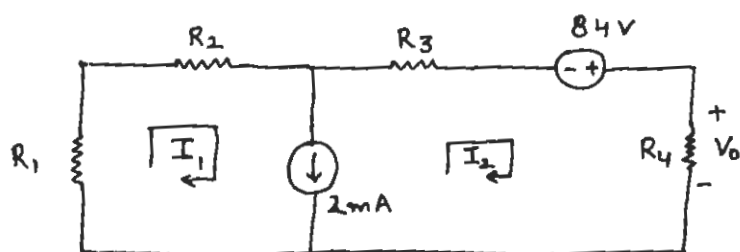

$$R_1 = R_4 = 1 \text{ k}\Omega, \quad R_2 = R_3 = 2 \text{ k}\Omega$$

$$V_o = I_2 R_4$$

$$I_1 - I_2 = 2 \times 10^{-3} \text{ A} \quad \text{--- (1)}$$

$$I_1 R_1 + I_1 R_2 + I_2 R_3 - 84 + I_2 R_4 = 0$$

$$I_1 (R_1 + R_2) + I_2 (R_3 + R_4) = 84$$

$$(3 \times 10^3) I_1 + (3 \times 10^3) I_2 = 84$$

$$I_1 + I_2 = 28 \times 10^{-3} \text{ --- (2)}$$

From equations (1) and (2), we get

$$2I_1 = 30 \times 10^{-3}$$


$$I_1 = 15 \text{ mA and } I_2 = 13 \text{ mA}$$

$$V_o = I_2 R_4$$

$$= 13 \times 10^{-3} \times 1 \times 10^3$$


$$\boxed{V_o = 13.0 \text{ V}}$$

**3.51** Use mesh analysis to find  $V_o$  in the network in Fig. P3.51.

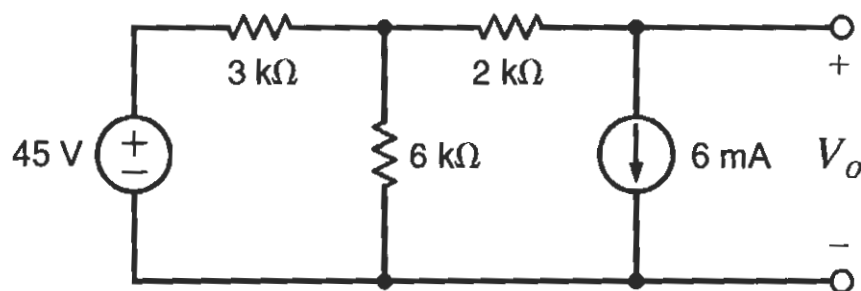

**Figure P3.51**

**SOLUTION:** 3.51

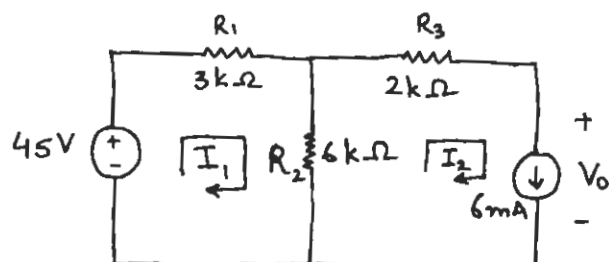

$$I_2 = 6 \text{ mA}$$

$$\text{KVL @ } I_1: -45 + I_1 R_1 + (I_1 - I_2) R_2 = 0$$

$$I_1 (R_1 + R_2) - I_2 R_2 = 45$$

$$9 \times 10^3 (I_1) - 6 \times 10^3 (I_2) = 45$$

$$I_1 = 9 \times 10^{-3}$$

$$= 9 \text{ mA}$$

$$\text{KVL @ } I_2: -45 + I_1 R_1 + I_2 R_3 + V_o = 0$$

$$-45 + [9 \times 10^{-3} \times 3 \times 10^3] + [(6 \times 10^{-3}) \times (2 \times 10^3)] + V_o = 0$$

$$\boxed{V_o = 6.00 \text{ V}}$$

3.52 Find  $I_o$  in the circuit in Fig. P3.52 using mesh analysis.


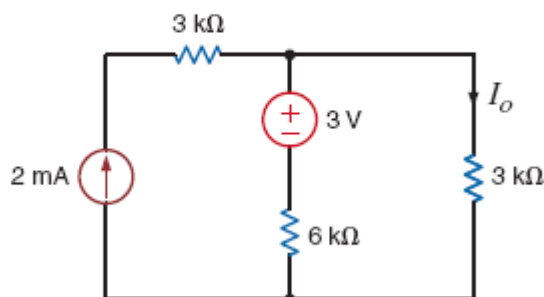


Figure P3.52

**SOLUTION:**

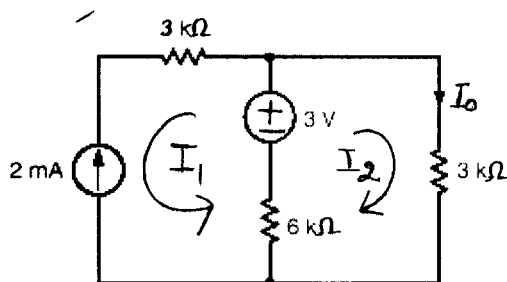

Let the loop currents be  $I_1$  &  $I_2$  mA

From loop 1:

$$I_1 = -2 \text{ mA} \quad \text{--- (1)}$$

Applying KVL in second loop:

$$3 = 3I_2 + 6(I_1 + I_2)$$

$$\Rightarrow 3 = 9I_2 + 6I_1 \quad \text{--- (2)}$$

From equation (1) & (2)

$$3 = 9(I_2) + 6I_1 = 9I_2 + 6(-2)$$



$$\Rightarrow I_2 = \frac{15}{9}$$

$$\Rightarrow I_2 = \frac{5}{3} = 1.667 \text{ mA}$$

$$I_o = I_2 = 1.67 \text{ mA}$$

3.53 Find  $V_o$  in the circuit in Fig. P3.53 using mesh analysis.


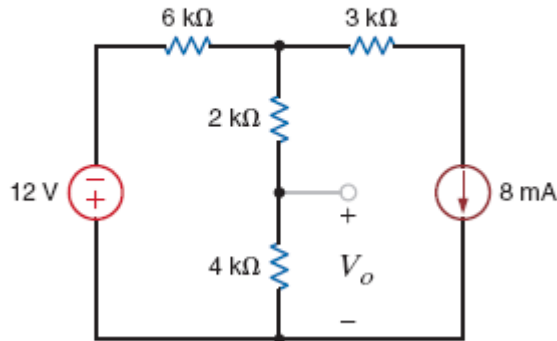


Figure P3.53

**SOLUTION:**

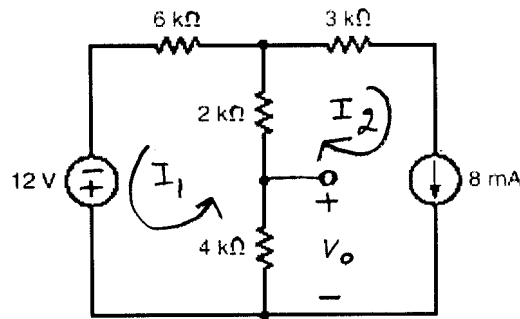

Let  $I_1$  &  $I_2$  be two loop currents in mA.

From loop 2 :

$$I_2 = 8 \text{ mA} \quad - (1)$$

KVL in the loop 1 :

$$12 = 4(I_1 + I_2) + 2(I_1 + I_2) + 6I_1$$

$$\Rightarrow 12 = 12I_1 + 6I_2 \quad - (2)$$

Substituting the value of  $I_2$  from ① in ②

$$\Rightarrow 12 = 12I_1 + 6(8)$$

$$\Rightarrow I_1 = -3 \text{ mA} \quad - \text{ ③}$$

$$V_o = -4 \times (I_1 + I_2)$$

$$\Rightarrow V_o = -4(-3 + 8)$$

$$\Rightarrow V_o = -4(5)$$

$$V_o = -20 \text{ Volts}$$

3.54 Use mesh analysis to find  $V_o$  in the circuit in Fig. P3.54.


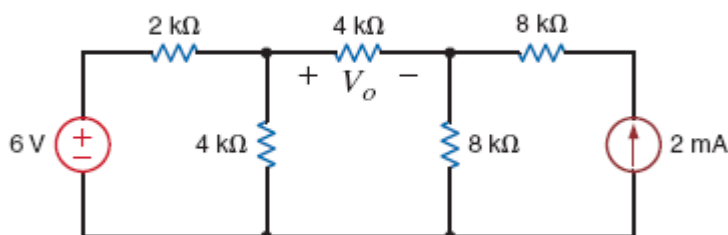


Figure P3.54

**SOLUTION:**

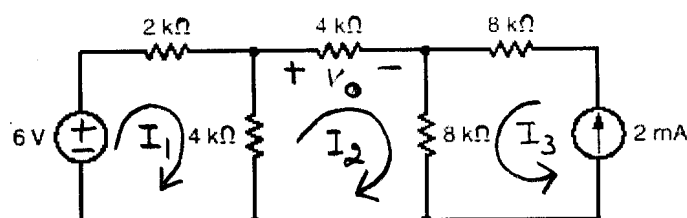

Let the loop currents be  $I_1$ ,  $I_2$  and  $I_3$  mA as shown in the diagram.

KVL in the first loop gives :

$$6 = 2I_1 + 4(I_1 - I_2)$$

$$\Rightarrow 6 = 6I_1 - 4I_2 \quad \text{--- (1)}$$

KVL in the second loop gives :

$$0 = 4(I_2 - I_1) + 4I_2 + 8(I_2 + I_3)$$

$$\Rightarrow 0 = 16I_2 - 4I_1 + 8I_3 \quad \text{--- (2)}$$

From the third loop:

$$I_3 = 2 \text{ mA} \quad \text{--- (3)}$$

From equation (2) & (3)

$$0 = 16I_2 - 4I_1 + 8(2)$$

$$\Rightarrow 16 = 4I_1 - 16I_2 \quad \text{--- (4)}$$

$$\Rightarrow 4 = I_1 - 4I_2$$

$$6 = 6I_1 - 4I_2 \quad \text{--- (1)}$$

Solving these two equations

$$2 = 5I_1 \quad \therefore I_1 = \frac{2}{5} = 0.4 \text{ mA}$$

$$I_2 = -0.9 \text{ mA}$$

$$V_o = I_2 \times 4 \text{ K} = 4 \times (-0.9) = -3.6 \text{ Volts.}$$

3.55 Use mesh analysis to find  $I_o$  in the network in Fig. P3.55.


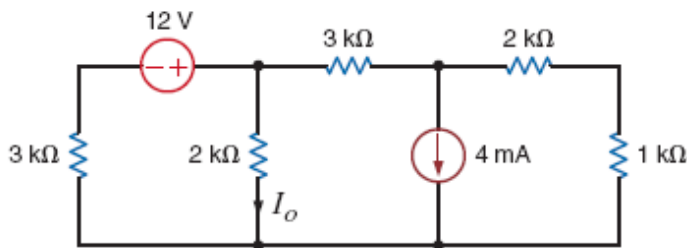


Figure P3.55

**SOLUTION:**

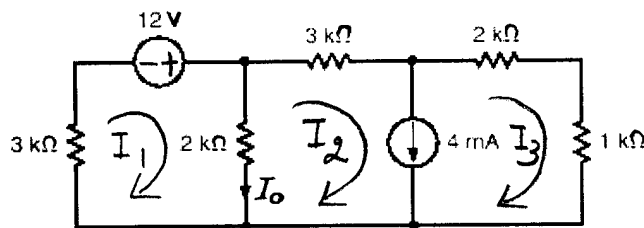

Let  $I_1$ ,  $I_2$  and  $I_3$  be the loop currents (in mA) as shown in the diagram.

KVL in the first loop:

$$12 = 2(I_1 - I_2) + 3I_1$$

$$\Rightarrow 12 = 5I_1 - 2I_2 \quad \text{--- (1)}$$

From the second loop:

$$I_2 - I_3 = 4 \quad \text{--- (2)}$$

KVL in the loop outer to loop 2 & 3

$$0 = 3I_2 + 2I_3 + I_3 + 2(I_2 - I_1)$$

$$\Rightarrow 0 = 5I_2 + 3I_3 - 2I_1 \quad \text{--- (3)}$$

upon solving these three equations, we get

$$I_1 = \frac{10}{3} \text{ mA}, \quad I_2 = \frac{7}{3} \text{ mA}, \quad I_3 = -\frac{5}{3} \text{ mA}$$

$$I_o = I_1 - I_2$$

$$\Rightarrow I_o = \frac{10}{3} - \frac{7}{3} = \frac{3}{3} = 1 \text{ mA}$$

$$I_o = 1 \text{ mA}$$

3.56 Find  $I_o$  in the network in Fig. P3.56 using loop analysis.


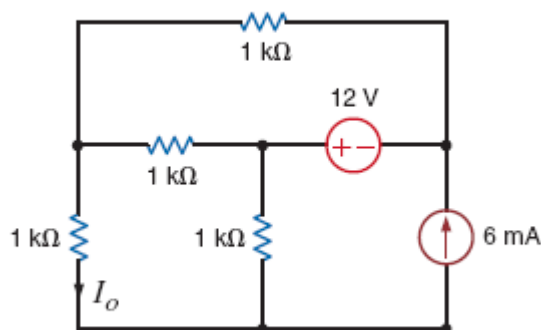


Figure P3.56

**SOLUTION:**

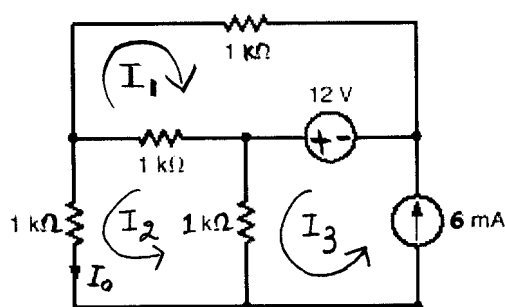

Let  $I_1$ ,  $I_2$  and  $I_3$  be the loop currents (in mA).

KVL in the first loop:

$$12 = 1(I_1 + I_2) + 1 \times I_1$$

$$\Rightarrow 12 = 2I_1 + I_2 \quad \text{--- (1)}$$

From the third loop:

$$I_3 = 6 \text{ mA} \quad \text{--- (2)}$$

KVL in the second loop:

$$1(I_1 + I_2) + 1(I_2) + 1(I_2 - I_3) = 0$$



$$\Rightarrow I_1 + 3I_2 - I_3 = 0 \quad \text{--- (3)}$$

From equation (2) & (3), we get:

$$I_1 + 3I_2 = I_3 = 6 \quad \text{--- (4)}$$

From equation (1) & (4):

$$12 = 2I_1 + I_2 \quad \text{--- (1)}$$

$$6 = I_1 + 3I_2$$

$$\Rightarrow 12 = 2I_1 + 6I_2 \quad \text{--- (5)}$$

$$5I_2 = 0 \quad \{ \text{eq. (5)} - \text{eq. (1)} \}$$

$$\text{or } \boxed{I_2 = 0 \text{ mA}}$$

3.57 Use loop analysis to find  $I_o$  and  $I_1$  in the network in Fig. P3.57.


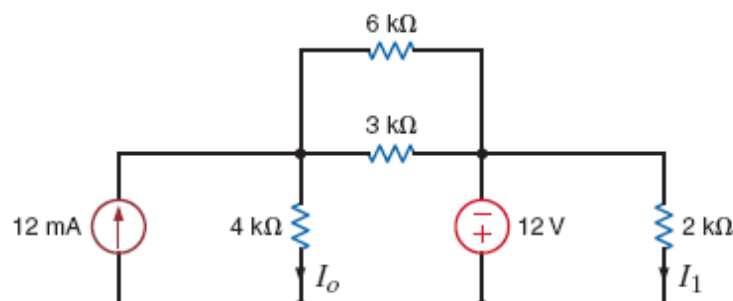


Figure P3.57

**SOLUTION:**

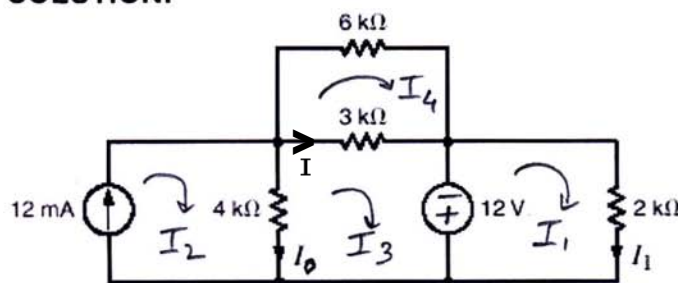

$$I_2 = 12 \text{ mA}$$

$$\begin{aligned} \text{KCL : } I_o + I_3 &= I_2 \\ I_o &= I_2 - I_3 \end{aligned}$$

$$\begin{aligned} \text{KCL : } I_2 &= I + I_o + I_4 \\ I &= I_2 - I_o + I_3 - I_4 \\ I &= I_3 - I_4 \end{aligned}$$

$$\begin{aligned} \text{KVL : } 12 &= -2KI_1 \\ I_1 &= -6 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{KVL : } 12 &= 4K(-I_o) + 6KI_4 \\ &= -4K(-I_o) + 6KI_4 \\ &= -4K(I_2 - I_3) + 6KI_4 = 12 \\ &= -4KI_2 + 4KI_3 + 6KI_4 = 12 \end{aligned}$$

$$\boxed{4KI_3 + 6KI_4 = 60}$$

$$\begin{aligned} \text{KVL: } 12 &= 4\text{K}(-I_0) + 3\text{K}I_1 \\ -4\text{K}(I_2 - I_3) + 3\text{K}(I_3 - I_4) &= 12 \end{aligned}$$

$$7I_3 - 4I_2 - 3I_4 = 12$$

$$\text{KVL: } 6\text{K}I_4 + 3\text{K}(I_4 - I_3) = 0$$

$$I_4 = I_3/3$$

$$I_3 = 10\text{mA}$$

$$I_4 = 3.33\text{mA}$$

$$I_0 = I_2 - I_3 = 12\text{mA} - 10\text{mA} = 2\text{mA}$$

$$I_0 = 2\text{mA}$$

- 3.58 Find  $I_o$  in the network in Fig. P3.58 using loop analysis. Then solve the problem using MATLAB and compare your answers.


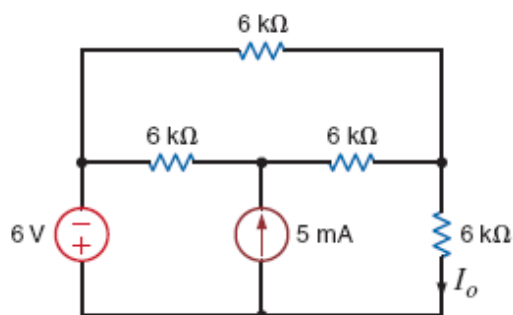


Figure P3.58

**SOLUTION:**

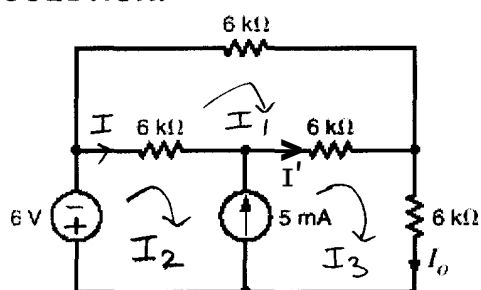

$$I_3 = I_o$$

$$\text{KCL: } I_2 = I + I_1$$

$$I = I_2 - I_1$$

$$\text{KCL: } I_1 + I' = I_3$$

$$I' = I_3 - I_1$$

$$\text{KVL: } \text{KVL in the top loop:}$$

$$18I_1 - 6I_2 - 6I_3 = 0$$

$$3I_1 - I_2 - I_3 = 0$$

$$\text{KVL: } 6 + 6KI + 6KI' + 6KI_o = 0$$

$$6K(I_2 - I_1) + 6K(I_3 - I_1) + 6KI_3 = -6$$

$$-12KI_1 + 6KI_2 + 12KI_3 = -6 \Rightarrow 2I_1 - I_2 - 2I_3 = 1$$

$$\text{KCL: } I_3 = 5\text{m} + I_2$$

$$-I_2 + I_3 = 5\text{m}$$

upon solving these equations we get,  $i_3 = 2/5 = 0.4 \text{ mA}$

% MATLAB Code and Solution for Problem 3.65

$$R = \begin{bmatrix} 3 & -1 & -1 \\ 2 & -1 & -2 \\ 0 & -2 & 1 \end{bmatrix};$$

$$V = \begin{bmatrix} 0 \\ 1 \\ 5 \end{bmatrix}$$

$$I_{\text{matrix}} = \text{inv}(R) * V$$

>>


$I_{\text{matrix}} =$

- 0.0016

- 0.0044


0.0006

**3.59** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.59.

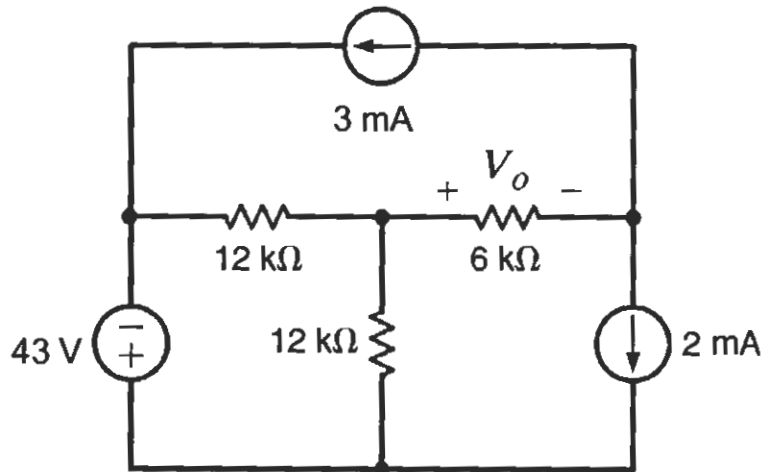

**Figure P3.59**

**SOLUTION:** 3.59

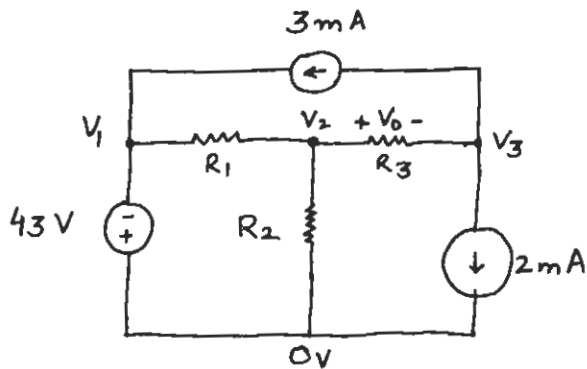

$$R_1 = R_2 = 12 \text{ k}\Omega, R_3 = 6 \text{ k}\Omega$$

$$V_1 = -43 \text{ V}$$

$$V_2 - V_3 = V_o$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_3} + \frac{V_2}{R_2} = 0 \quad \text{---} \quad \textcircled{1}$$

$$\text{KCL @ } V_3: \frac{V_3 - V_2}{R_3} + 2 \times 10^{-3} + 3 \times 10^{-3} = 0$$

$$V_2 - V_3 = 30 \quad \text{---} \quad \textcircled{2}$$

From equations  $\textcircled{1}$  and  $\textcircled{2}$ , we get

$$\boxed{V_o = 30.0 \text{ V}}$$

3.60 Determine  $V_o$  in the circuit in Fig. P3.60 using loop analysis.


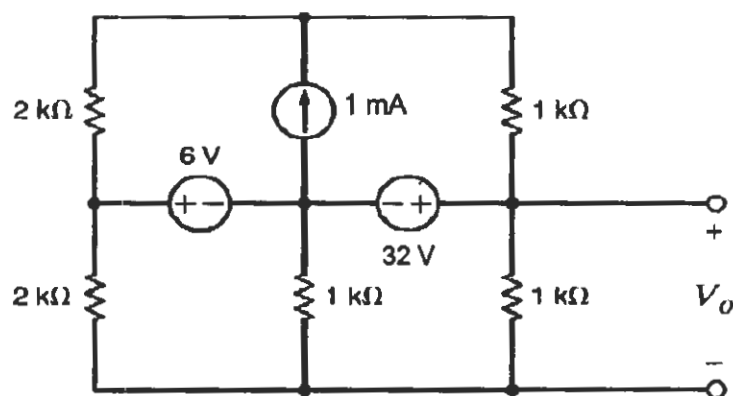


Figure P3.60

Solution: 3.60

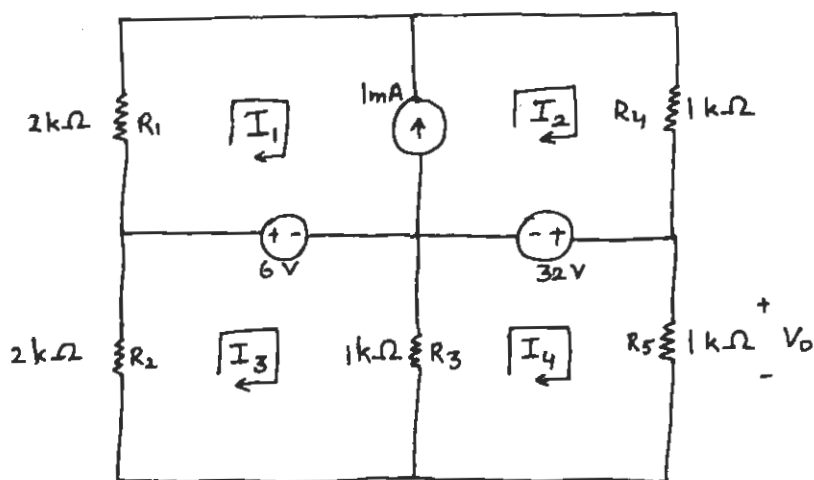

$$V_o = I_4 R_5 \quad I_2 - I_1 = 1 \text{ mA}$$

$$\text{KVL @ } I_3 : I_3 R_2 + 6 + (I_3 - I_4) R_3 = 0$$

$$I_3 (R_2 + R_3) - I_4 R_3 = -6$$

$$I_3 (3 \times 10^3) - I_4 (10^3) = -6$$

$$3I_3 - I_4 = -6 \times 10^{-3} \quad \text{--- (1)}$$

$$\text{KVL @ } I_4 : (I_4 - I_3) R_3 - 32 + I_4 R_5 = 0$$

$$2I_4 - I_3 = 32 \times 10^{-3} \quad \text{--- (2)}$$

$$5I_4 = 90 \times 10^{-3}$$

$$I_4 = 18 \text{ mA}$$


$$V_o = I_4 R_5$$

$$V_o = 18 \times 10^{-3} \times 10^3$$

$$V_o = 18.0 \text{ V}$$




**3.61** Find  $I_o$  in the circuit in Fig. P3.61.

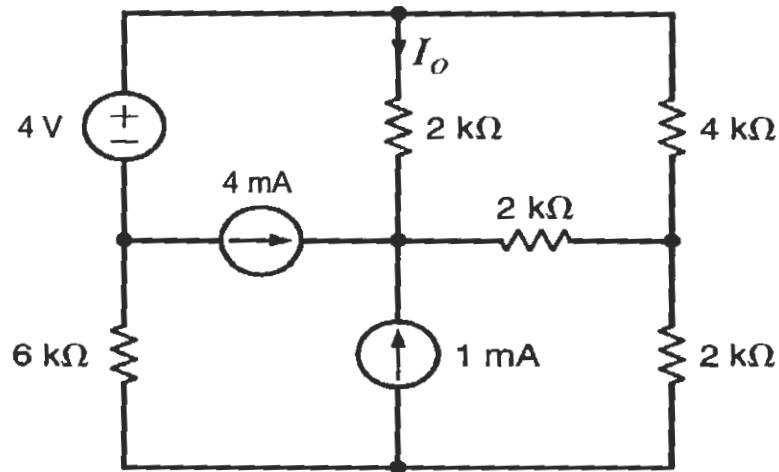

**Figure P3.61**

**SOLUTION:** 3-61

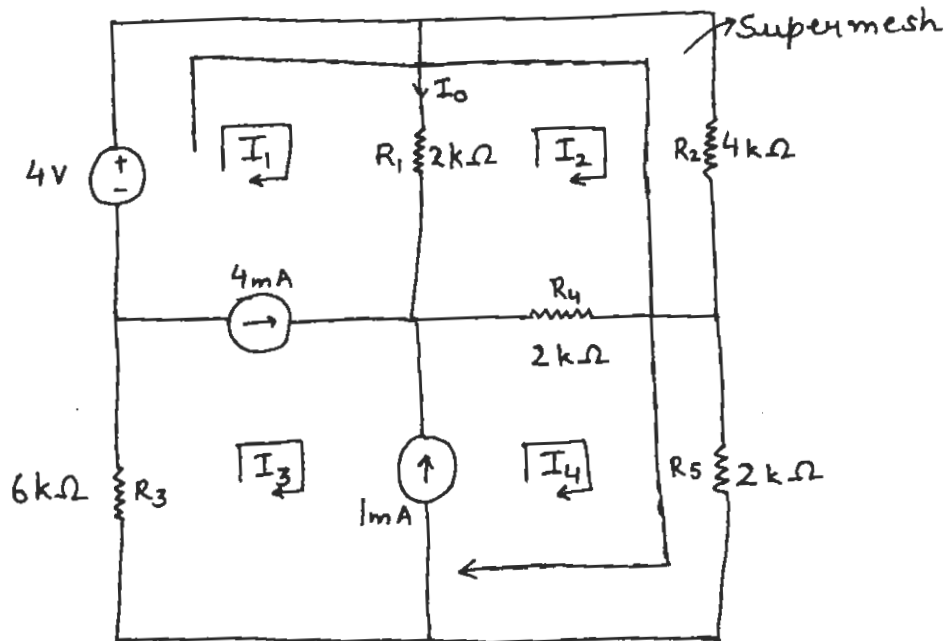

$$I_3 - I_1 = 4 \times 10^{-3} \text{ A} = 4 \text{ mA}$$

$$\Rightarrow I_3 = 4 \text{ mA} + I_1 \quad \text{---} \quad (1)$$

$$I_4 - I_3 = 1 \times 10^{-3} \text{ A} = 1 \text{ mA}$$

$$\Rightarrow I_4 = 1 \text{ mA} + I_3 = 5 \text{ mA} + I_1 \quad \text{---} \quad (2)$$

$$I_1 - I_2 = I_0$$

$$\Rightarrow I_2 = I_1 - I_0 \quad \text{---} \quad (3)$$

$$\text{KVL for } I_2: (I_2 - I_1)R_1 + I_2 R_2 + (I_2 - I_4)R_4 = 0$$

$$I_2 (R_1 + R_2 + R_4) - I_1 R_1 - I_4 R_4 = 0$$

$$I_2 (8 \times 10^3) - 2 \times 10^3 I_1 - (2 \times 10^3) I_4 = 0$$

$$\Rightarrow 4I_2 - I_1 - I_4 = 0 \quad \text{---} \quad (4)$$

$$\text{KVL for supermesh: } -4 + I_2 R_2 + I_4 R_5 + I_3 R_3 = 0$$

$$I_2 (4 \times 10^3) + I_4 (2 \times 10^3) + I_3 (6 \times 10^3) = 4$$

$$\Rightarrow 2I_2 + I_4 + 3I_3 = 2 \times 10^{-3} \quad \text{---} \quad (5)$$

Substituting equations (2) and (3) in (4), we get

$$4(I_1 - I_0) - I_1 - [(5 \times 10^{-3}) + I_1] = 0$$

$$2I_1 - 4I_0 = 5 \times 10^{-3} \quad \text{---} \quad (6)$$

Substituting equations (1), (2) and (3) in (5), we get


$$2(I_1 - I_0) + 5 \times 10^{-3} + I_1 + 3(4 \times 10^{-3} + I_1) = 2 \times 10^{-3}$$

$$6I_1 - 2I_0 = -15 \times 10^{-3} \quad \text{---} \quad (7)$$

From equations (6) and (7), we get


$$\boxed{I_0 = -3.00 \text{ mA}}$$

**3.62** Use loop analysis to find  $I_o$  in the network in Fig. P3.62.

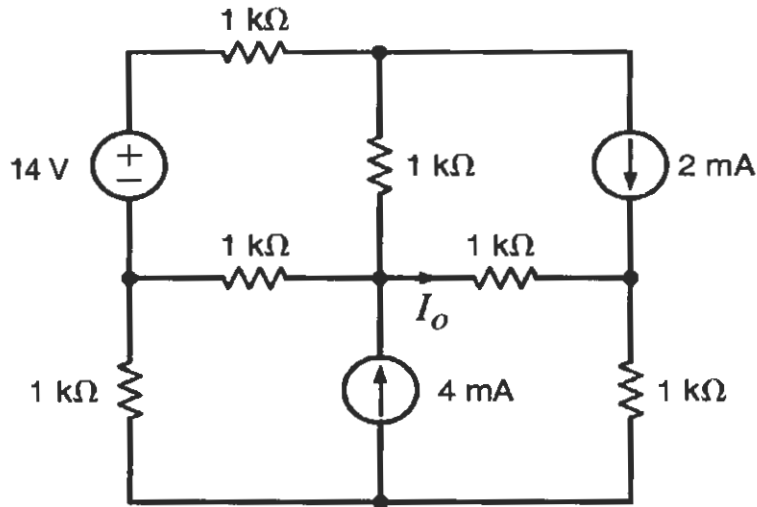

**Figure P3.62**

**SOLUTION:** 3-62

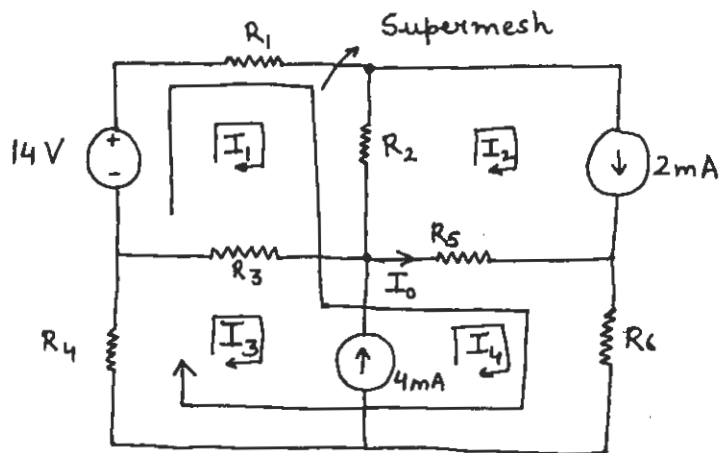

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 1\text{ k}\Omega$$

$$I_2 = 2\text{ mA}$$

$$I_4 - I_2 = I_o \Rightarrow I_4 = I_o + 2\text{ mA} \quad \text{---} \quad \textcircled{1}$$

$$I_4 - I_3 = 4\text{ mA}$$

$$I_3 = I_4 - 4 \times 10^{-3}$$

$$= I_0 + 2 \times 10^{-3} - 4 \times 10^{-3}$$

$$I_3 = I_0 - 2 \times 10^{-3} \quad \text{---} \quad (2)$$

$$\text{KVL @ } I_1: -14 + I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_3 = 0$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = 14$$

Substituting  $I_2 = 2 \text{ mA}$ ,  $I_3 = I_0 - 2 \text{ mA}$  in above equation, we get

$$3 I_1 - I_0 = 14 \times 10^{-3} \quad \text{---} \quad (3)$$

$$\text{KVL @ Supermesh: } -14 + I_1 R_1 + (I_1 - I_2) R_2 + (I_4 - I_2) R_5 + I_4 R_6 + I_3 R_4 = 0$$

$$I_1 (R_1 + R_2) - I_2 (R_2 + R_5) + I_3 R_4 + I_4 (R_5 + R_6) = 14$$

$$2 I_1 - 2 I_2 + I_3 + 2 I_4 = 14 \times 10^{-3}$$


$$2 I_1 - 2 (2 \times 10^{-3}) + I_0 - 2 \times 10^{-3} + 2 (I_0 + 2 \times 10^{-3}) = 14 \times 10^{-3}$$

$$2 I_1 + 3 I_0 = 16 \times 10^{-3} \quad \text{---} \quad (4)$$

From equations (3) and (4), we get


$$\boxed{I_0 = 1.82 \text{ mA}}$$

3.63 Use loop analysis to find  $I_o$  in the network in Fig. P3.63.

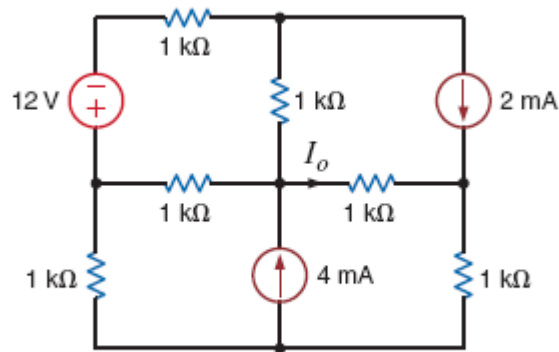

**Figure P3.63**

**SOLUTION:**

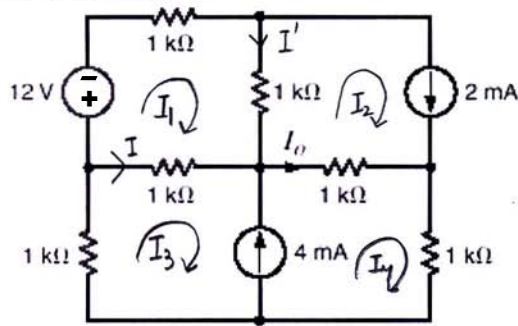

$$I_2 = 2\text{mA}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

KCL:  $I' + I_2 = I_1$   
 $I' = I_1 - I_2$

$$\begin{aligned} \text{KCL: } I_0 + 2m &= I_y \\ I_0 &= I_y - 2m \end{aligned}$$

$$\begin{aligned} \text{KVL: } 0 &= 12 + 1kI_1 + 1kI'_1 + 1k(-I_1) \\ 1kI_1 + 1k(I_1 - I_2) - 1k(I_3 - I_1) &= -12 \\ 3kI_1 - 1kI_2 - 1kI_3 &= -12 \end{aligned}$$

$$3kI_1 - 1kI_3 = -10$$

$$\begin{aligned} \text{KVL: } 1kI_3 + 1kI + 1kI_0 + 1kI_4 &= 0 \\ 1kI_3 + 1k(I_3 - I_1) + 1k(I_4 - 2m) + 1kI_4 &= 0 \end{aligned}$$

$$-1kI_1 + 2kI_3 + 2kI_4 = 2$$

$$\text{KCL: } I_4 = 4m + I_3$$

$$-I_3 + I_4 = 4m$$

$$\text{KVL: } 0 = 12 + 1kI_1 + 1kI' + 1kI_0 + 1kI_4 + 1kI_3$$

$$1kI_1 + 1k(I_1 - I_2) + 1k(I_4 - 2m) + 1kI_4 + 1kI_3 = -12$$

$$2kI_1 - 1kI_2 + 1kI_3 + 2kI_4 = -10$$

$$2kI_1 + 1kI_3 + 2kI_4 = -8$$

$$3kI_1 - 1kI_3 = -10$$

$$-1kI_1 + 2kI_3 + 2kI_4 = 2$$

$$-I_3 + I_4 = 4m$$

$$I_1 = -4.18mA$$

$$I_3 = -2.55mA$$


$$I_4 = 1.45mA$$

$$I_0 = I_4 - 2m$$

$$I_0 = 1.45m - 2m$$


$$I_0 = -0.55mA$$

**3.64** Use loop analysis to find  $V_o$  in the network in the Fig. P3.64.

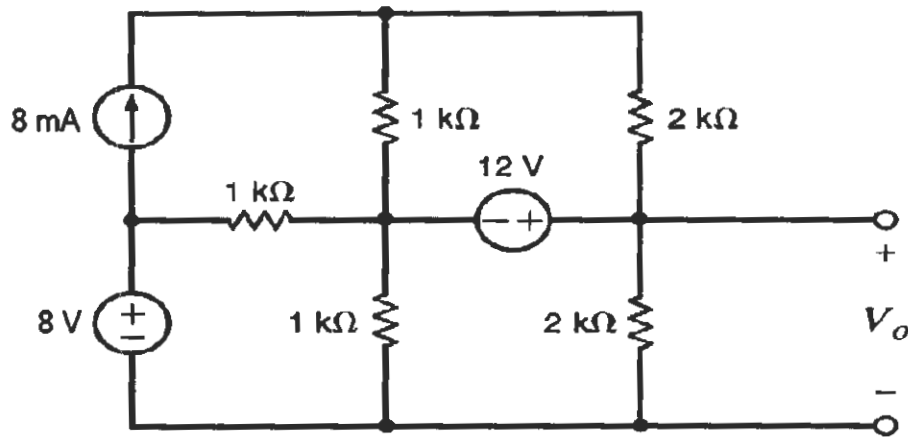

**Figure P3.64**

**Solution:** 3-64

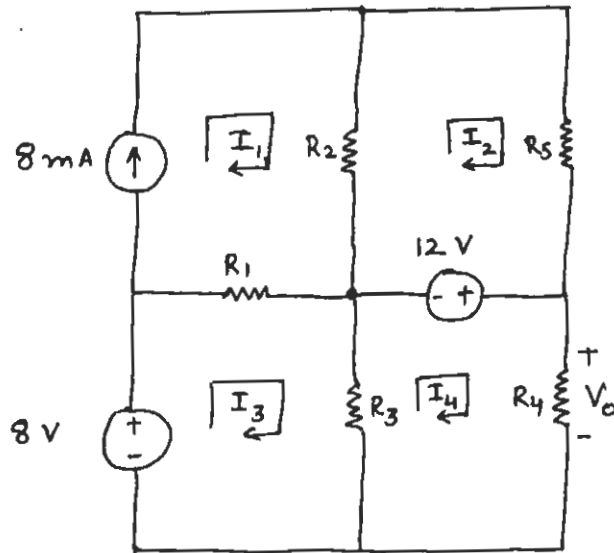

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, \quad R_5 = R_4 = 2 \text{ k}\Omega$$

$$V_0 = I_4 R_4 \quad \text{---} \quad (1)$$

$$I_1 = 8 \text{ mA}$$

$$\text{KVL @ } I_2: (I_2 - I_1)R_2 + I_2R_5 + 12 = 0$$

$$I_2 = -2 \text{ mA}$$

$$\text{KVL @ } I_3: -8 + (I_3 - I_1)R_1 + (I_3 - I_4)R_3 = 0$$

$$I_3(R_1 + R_3) - I_1R_1 - I_4R_3 = 8$$

$$I_3(2 \times 10^3) - (8 \times 10^{-3})(10^3) - I_4(10^3) = 8$$

$$2I_3 - I_4 = 16 \times 10^{-3} \quad \text{--- (2)}$$

$$\text{KVL @ } I_4: (I_4 - I_3)R_3 - 12 + I_4R_4 = 0$$

$$I_4(R_3 + R_4) - I_3R_3 = 12$$

$$(3 \times 10^3)I_4 - (10^3)I_3 = 12$$

$$3I_4 - I_3 = 12 \times 10^{-3} \quad \text{--- (3)}$$

From equations (2) and (3), we get

$$I_4 = 8 \text{ mA}$$

Substituting the value of  $I_4$  in equation (1), we get

$$V_0 = (8 \times 10^{-3})(2 \times 10^3)$$

$$\boxed{V_0 = 16.0 \text{ V}}$$



3.65 Using loop analysis, find  $V_o$  in the network in Fig. P3.65.


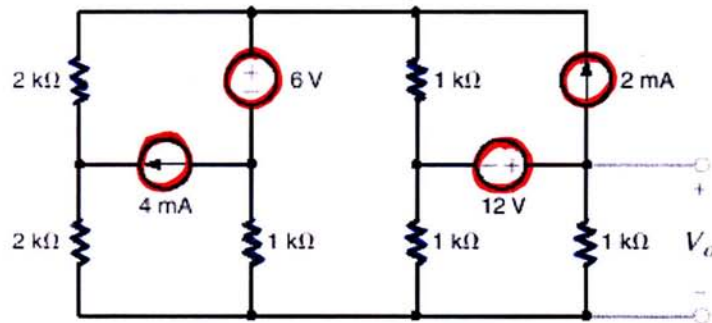


Figure P3.65

**SOLUTION:**

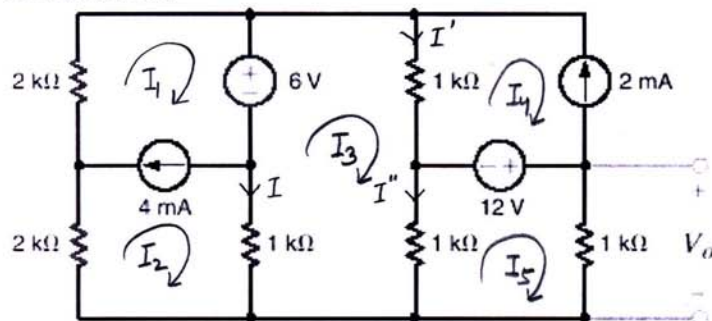

$$\begin{aligned} \text{KCL: } I_3 + I &= I_2 \\ I &= I_2 - I_3 \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_3 &= I' + I_4 \\ I' &= I_3 - I_4 \end{aligned}$$

$$\begin{aligned} \text{KCL: } I'' + I_5 &= I_3 \\ I'' &= I_3 - I_5 \end{aligned}$$

$$\begin{aligned} \text{KVL: } 12 &= 1k I_5 + 1k (-I'') \\ -1k (I_3 - I_5) + 1k I_5 &= 12 \end{aligned}$$

$$\boxed{-1k I_3 + 2k I_5 = 12}$$

$$\begin{aligned} \text{KVL: } 6 &= 1k I' + 1k I'' + 1k (-I) \\ 1k (I_3 - I_4) + 1k (I_3 - I_5) - 1k (I_2 - I_3) &= 6 \end{aligned}$$

$$-1kI_2 + 3kI_3 - 1kI_4 - 1kI_5 = 6$$

$$\text{KVL: } 2kI_1 + 1kI' + 1kI_5 + 2kI_2 = 12$$

$$2kI_1 + 1k(I_3 - I_4) + 1kI_5 + 2kI_2 = 12$$

$$2kI_1 + 2kI_2 + 1kI_3 - 1kI_4 + 1kI_5 = 12$$

$$\text{KCL: } I_2 + 4m = I_1$$

$$-I_1 + I_2 = -4m$$

$$I_4 = -2mA$$

$$-1kI_2 + 3kI_3 - 1k(-2m) - 1kI_5 = 6$$

$$-1kI_2 + 3kI_3 - 1kI_5 = 4$$

$$2kI_1 + 2kI_2 + 1kI_3 - 1k(-2m) + 1kI_5 = 12$$

$$2kI_1 + 2kI_2 + 1kI_3 + 1kI_5 = 10$$

$$0I_1 + 0I_2 - 1kI_3 - 1k(-2m) + 1kI_5 = 12$$

$$-I_1 + I_2 + 0I_3 + 0I_5 = -4m$$

$$0I_1 - 1kI_2 + 3kI_3 - 1kI_5 = 4$$

$$2kI_1 + 2kI_2 + 1kI_3 + 1kI_5 = 10$$

$$I_1 = 1.83mA$$

$$I_2 = -2.17mA$$

$$I_3 = 3.13mA$$

$$I_5 = 7.57mA$$

$$V_o = 1k(I_5) = 1k(7.57m)$$

$$V_o = 7.57V$$

3.66 Using loop analysis, find  $I_o$  in the circuit in Fig. P3.66.


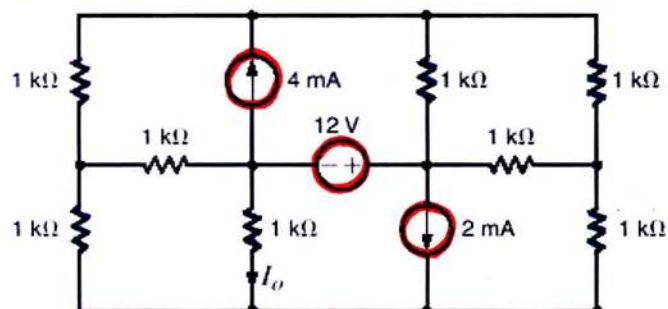


Figure P3.66

**SOLUTION:**

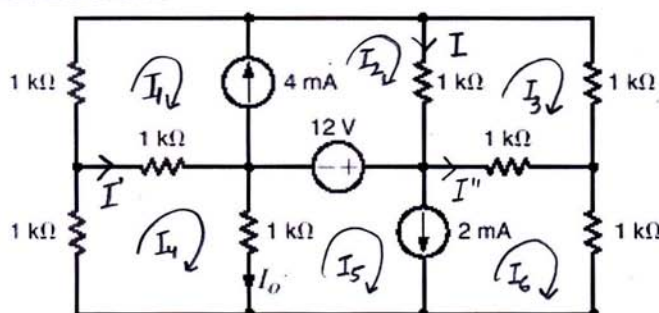

$$\begin{aligned} \text{KCL: } I_2 &= I + I_3 \\ I &= I_2 - I_3 \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_3 + I'' &= I_6 \\ I'' &= I_6 - I_3 \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_4 &= I_1 + I' \\ I' &= I_4 - I_1 \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_o + I_5 &= I_4 \\ I_o &= I_4 - I_5 \end{aligned}$$

$$\begin{aligned} \text{KVL: } 12 &= 1kI'' + 1kI_6 + 1k(-I_o) \\ 1k(I_6 - I_3) + 1kI_6 - 1k(I_4 - I_5) &= 12 \end{aligned}$$

$$\boxed{-1kI_3 - 1kI_4 + 1kI_5 + 2kI_6 = 12}$$

$$\begin{aligned} \text{KVL: } 1k I_1' + 1k I_0 + 1k I_4 &= 0 \\ 1k (I_4 - I_1) + 1k (I_4 - I_5) + 1k I_4 &= 0 \\ \boxed{-1k I_1 + 3k I_4 - 1k I_5 = 0} \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_6 + 2m &= I_5 \\ \boxed{-I_5 + I_6 = -2m} \end{aligned}$$

$$\begin{aligned} \text{KCL: } I_1 + 4m &= I_2 \\ \boxed{I_1 - I_2 = -4m} \end{aligned}$$

$$\begin{aligned} \text{KVL: } 1k I_1 + 1k I_3 + 1k (-I'') + 12 + 1k (-I') &= 0 \\ 1k I_1 + 1k I_3 - 1k (I_6 - I_3) - 1k (I_4 - I_1) &= -12 \\ \boxed{2k I_1 + 2k I_3 - 1k I_4 - 1k I_6 = -12} \end{aligned}$$

$$\begin{aligned} \text{KVL: } 1k I_3 + 1k (-I'') + 1k (-I) &= 0 \\ 1k I_3 - 1k (I_6 - I_3) - 1k (I_2 - I_3) &= 0 \\ \boxed{-1k I_2 + 3k I_3 - 1k I_6 = 0} \end{aligned}$$

$$\begin{aligned} 0I_1 + 0I_2 - 1k I_4 + 1k I_5 + 2k I_6 &= 12 \\ -1k I_1 + 0I_2 + 0I_3 + 3k I_4 - 1k I_5 + 0I_6 &= 0 \\ 0I_1 + 0I_2 + 0I_3 + 0I_4 - I_5 + I_6 &= -2m \\ I_1 - I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 &= -4m \\ 2k I_1 + 0I_2 + 2k I_3 - 1k I_4 + 0I_5 - 1k I_6 &= -12 \\ 0I_1 - 1k I_2 + 3k I_3 + 0I_4 + 0I_5 - 1k I_6 &= 0 \end{aligned}$$

$$I_1 = -4.93 \text{ mA}$$

$$I_2 = -0.933 \text{ mA}$$

$$I_3 = 0.933 \text{ mA}$$

$$I_4 = 0.267 \text{ mA}$$


$$I_5 = 5.73 \text{ mA}$$

$$I_6 = 3.73 \text{ mA}$$

$$I_0 = I_4 - I_5 = 0.267 \text{ mA} - 5.73 \text{ mA}$$


$$I_0 = -5.46 \text{ mA}$$

**3.67** Use MATLAB to find the mesh currents in the network in Fig. P3.6.

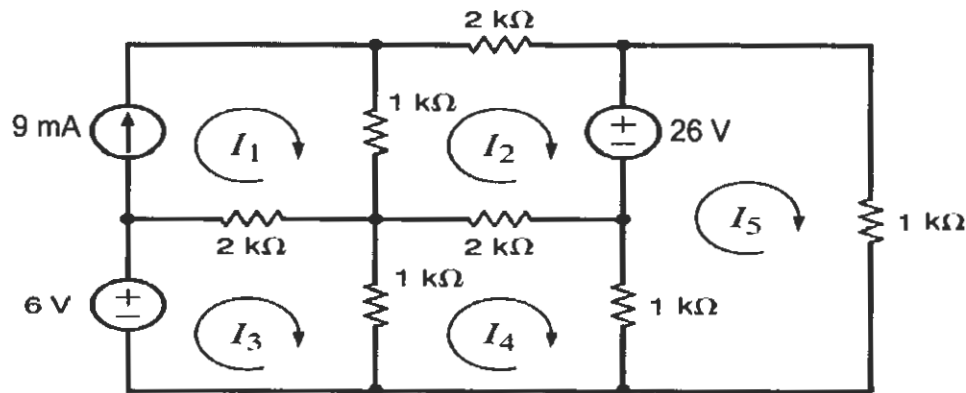

**Figure P3.67**

SOLUTION: 3.67

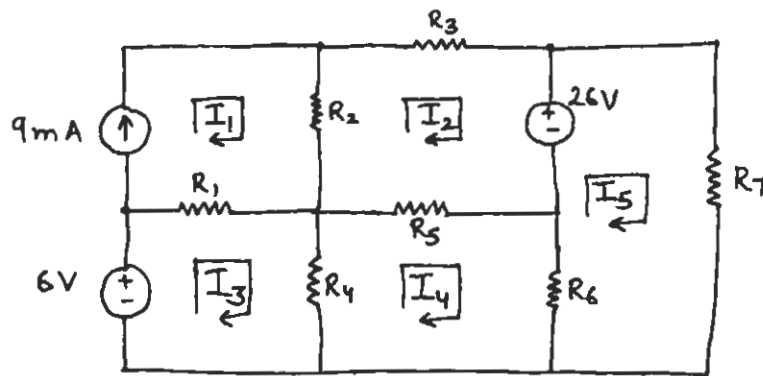

$$R_1 = R_3 = R_5 = 2 \text{ k}\Omega, \quad R_2 = R_4 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_1 = 9 \times 10^{-3} \text{ A}$$

$$\begin{aligned} \text{KVL @ } I_2: & (I_2 - I_1)R_2 + I_2 R_3 + 26 + (I_2 - I_4)R_5 = 0 \\ & -I_1(R_2) + I_2(R_2 + R_3 + R_5) - I_4 R_5 = -26 \\ & -I_1(10^3) + I_2(5 \times 10^3) - I_4(2 \times 10^3) = -26 \\ & -I_1 + 5I_2 - 2I_4 = -26 \times 10^{-3} \end{aligned}$$

$$\begin{aligned} \text{KVL @ } I_3: & -6 + (I_3 - I_1)R_1 + (I_3 - I_4)R_4 = 0 \\ & -I_1 R_1 + I_3(R_1 + R_4) - I_4(R_4) = 6 \\ & -I_1(2 \times 10^3) + I_3(3 \times 10^3) - I_4(10^3) = 6 \\ & -2I_1 + 3I_3 - I_4 = 6 \times 10^{-3} \end{aligned}$$



$$\begin{aligned}
 \text{KVL @ } I_4: & (I_4 - I_3)R_4 + (I_4 - I_2)R_5 + (I_4 - I_5)R_6 = 0 \\
 & -I_2R_5 - I_3R_4 + I_4(R_4 + R_5 + R_6) - I_5R_6 = 0 \\
 & -I_2(2 \times 10^3) - I_3(10^3) + I_4(4 \times 10^3) - I_5(10^3) = 0 \\
 & -2I_2 - I_3 + 4I_4 - I_5 = 0
 \end{aligned}$$

$$\begin{aligned}
 \text{KVL @ } I_5: & -26 + I_5R_7 + (I_5 - I_4)R_6 = 0 \\
 & -I_4R_6 + I_5(R_6 + R_7) = 26 \\
 & -I_4(10^3) + I_5(2 \times 10^3) = 26 \\
 & -I_4 + 2I_5 = 26 \times 10^{-3}
 \end{aligned}$$

In matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ -1 & 5 & 0 & -2 & 0 \\ -2 & 0 & 3 & -1 & 0 \\ 0 & -2 & -1 & 4 & -1 \\ 0 & 0 & 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} 0.009 \\ -0.026 \\ 0.006 \\ 0 \\ 0.026 \end{bmatrix}$$

3.68 Use loop analysis to find  $V_o$  in the network in Fig. P3.68.


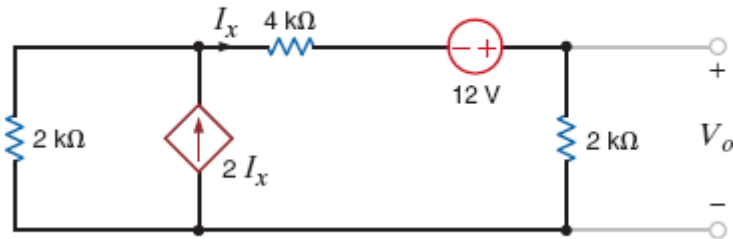


Figure P3.68

**SOLUTION:**

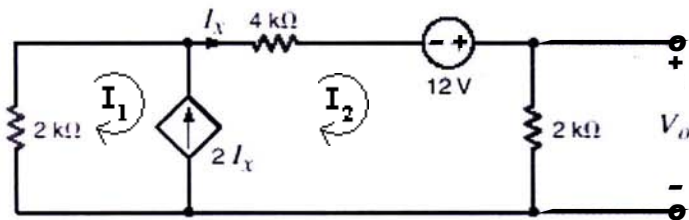

$$\begin{aligned} \text{KCL: } I_1 + 2I_x &= I_x \\ I_1 &= -I_x \text{ and } I_2 = I_x \end{aligned}$$

$$\begin{aligned} \text{KVL: } 12 &= 2kI_1 + 4kI_2 + 2kI_2 \\ 2kI_1 + 6kI_2 &= 12 \\ 2k(-I_x) + 6k(I_x) &= 12 \\ 4kI_x &= 12 \\ I_x &= 3\text{mA} \end{aligned}$$

$$\begin{aligned} V_o &= 2kI_x = 2k(3\text{mA}) \\ V_o &= 6\text{V} \end{aligned}$$



3.69 Find  $V_o$  in the circuit in Fig. P3.69 using nodal analysis.


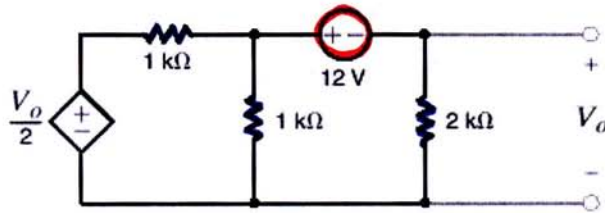


Figure P3.69

**SOLUTION:**

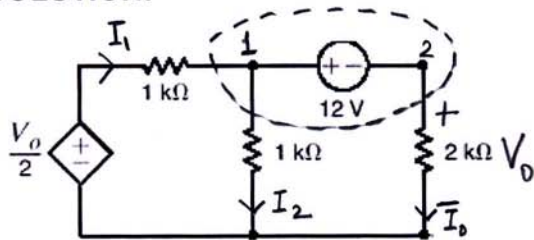

KCL at supernode:

$$I_1 = I_2 + I_o$$

$$\frac{\frac{V_o}{2} - V_1}{1k} = \frac{V_1}{1k} + \frac{V_2}{2k}$$

$$V_o - 2V_1 = 2V_1 + V_2$$

$$V_2 = V_o$$


$$V_1 = 0V$$

$$V_1 - V_2 = 12$$

$$V_2 = -12V$$


$$V_o = -12V$$

**3.70** Use nodal analysis to find  $V_o$  in Fig. P3.70.

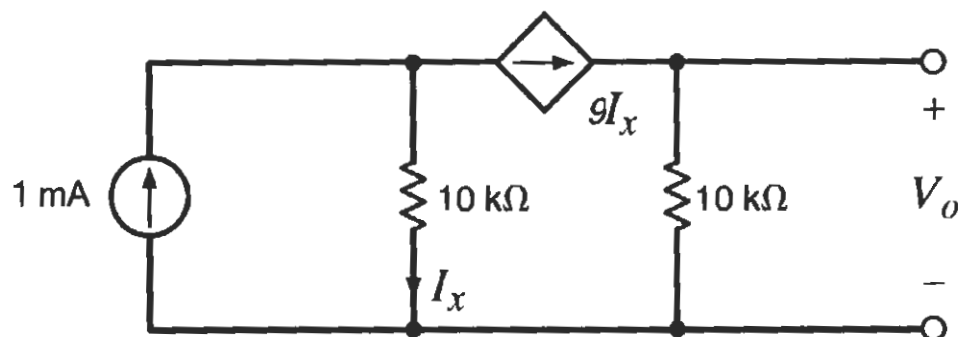

**Figure P3.70**

**SOLUTION:** 3.70

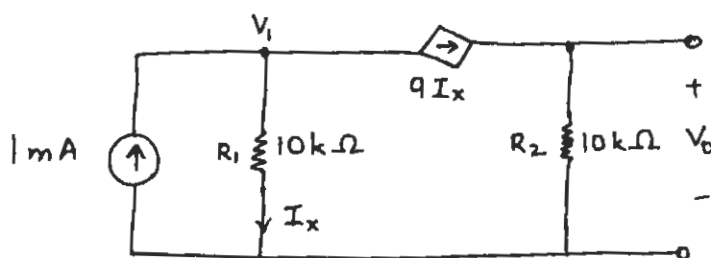

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$I_x = \frac{V_1}{R_1} \Rightarrow I_x = \frac{V_1}{10 \times 10^3} = \frac{V_1}{10} \times 10^{-3}$$

$$\text{KCL @ } V_1: -1 \times 10^{-3} + \frac{V_1}{R_1} + 9 I_x = 0$$

$$V_1 = 1 \text{ V}$$

$$\text{KCL @ } V_o: -9 I_x + \frac{V_o}{R_2} = 0$$

$$V_o = 9 V_1$$

$$\boxed{V_o = 9 \text{ V}}$$

3.71 Use nodal analysis to find  $V_o$  in the network in Fig. P3.71.


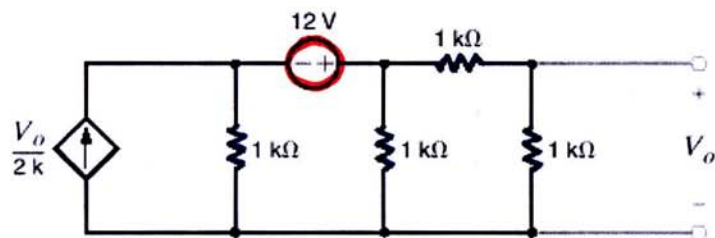


Figure P3.71

**SOLUTION:**

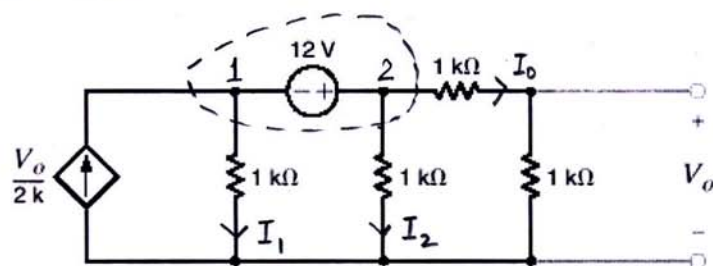

KCL at supernode:

$$\frac{V_o}{2k} = I_1 + I_2 + I_o$$

$$\frac{V_1}{1k} + \frac{V_2}{1k} + \frac{V_2}{1k+1k} = \frac{V_o}{2k}$$

$$2V_1 + 2V_2 + V_2 = V_o$$

$$2V_1 + 3V_2 = V_o$$

$$-V_1 + V_2 = 12$$

$$V_o = I_o(1k)$$

$$I_o = \frac{V_2}{1k+1k} = \frac{V_2}{2k}$$

$$V_o = \frac{V_2}{2}$$

$$2V_1 + 3V_2 = \frac{V_2}{2}$$

$$4V_1 + 6V_2 = V_2$$

$$\boxed{4V_1 + 5V_2 = 0}$$

$$-V_1 + V_2 = 12$$

$$4V_1 + 5V_2 = 0$$


$$V_1 = -6.67V$$

$$V_2 = 5.33V$$

$$V_o = \frac{V_2}{2} = \frac{5.33}{2}$$


$$V_o = 2.67V$$

**3.72** Find the power supplied by the 4-A current source in the network in Fig. P3.72 using nodal analysis.

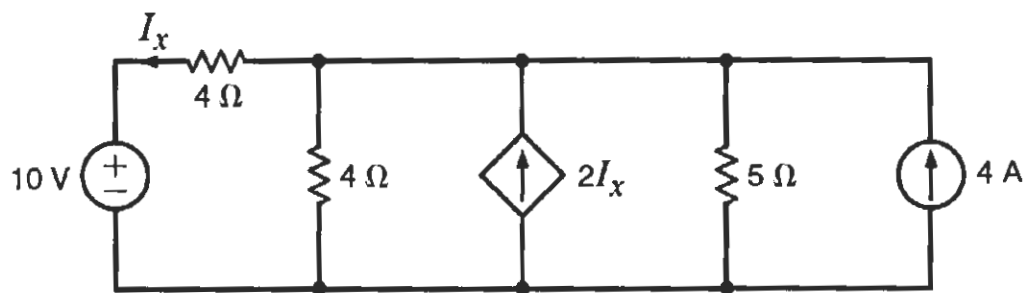

**Figure P3.72**

**SOLUTION:** 3-12

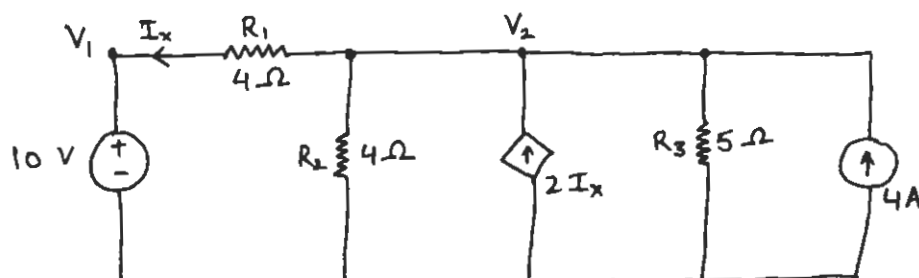

$$R_1 = R_2 = 4\Omega, \quad R_3 = 5\Omega$$

$$V_1 = 10\text{ V}; \quad I_x = \frac{V_2 - V_1}{R_1} = \frac{V_2 - V_1}{4} = \frac{V_2 - 10}{4} \text{ A}$$

$$\text{KCL @ } V_2: \quad \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} - 2I_x + \frac{V_2}{R_3} - 4 = 0$$

$$\frac{V_2 - 10}{4} + \frac{V_2}{4} - 2\left(\frac{V_2 - 10}{4}\right) + \frac{V_2}{5} - 4 = 0$$


$$V_2 = 7.5\text{ V}$$

Power supplied by 4-A source,

$$P_{4A} = 4 \times 7.5$$


$$P_{4A} = 30.0\text{ W}$$

**3.73** Find  $I_o$  in the network in Fig. P3.73.

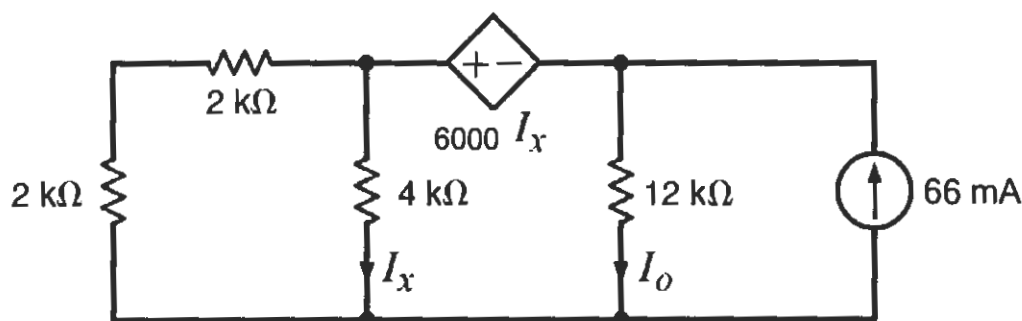

**Figure P3.73**

**SOLUTION: 3.73**

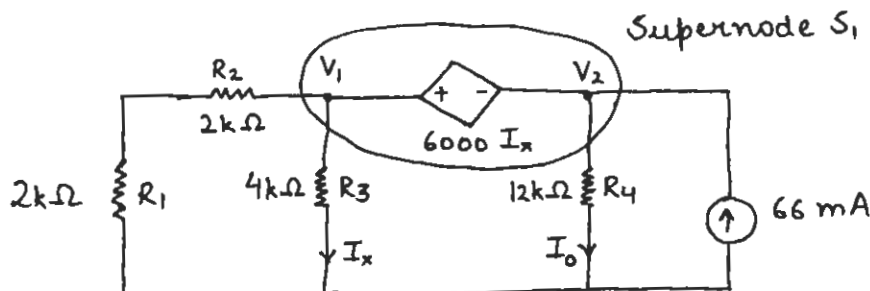

$$R_1 = R_2 = 2 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, R_4 = 12 \text{ k}\Omega$$

$$V_1 - V_2 = 6000 I_x$$

$$\text{Using } I_x = \frac{V_1}{R_3},$$

$$V_1 - V_2 = \frac{3}{2} V_1 \Rightarrow V_1 = -2 V_2 \quad \text{--- (1)}$$

$$\text{KCL @ } S_1 : \frac{V_1}{R_1 + R_2} + \frac{V_1}{R_3} + \frac{V_2}{R_4} - 66 \times 10^{-3} = 0$$

$$6 V_1 + V_2 = 792 \quad \text{--- (2)}$$

From equations (1) and (2) we get,


$$-11 V_2 = 792$$

$$V_2 = -72.0 \text{ V}$$

$$\begin{aligned} I_O &= \frac{V_2}{R_4} \\ &= \frac{-72}{12 \times 10^3} \end{aligned}$$


$$I_O = -6 \text{ mA}$$

**3.74** Find  $V_o$  in the circuit in Fig. P3.74 using nodal analysis.

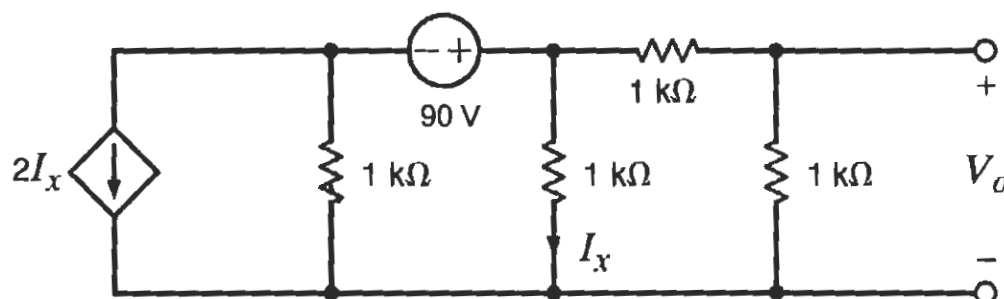

**Figure P3.74**

SOLUTION: 3.74

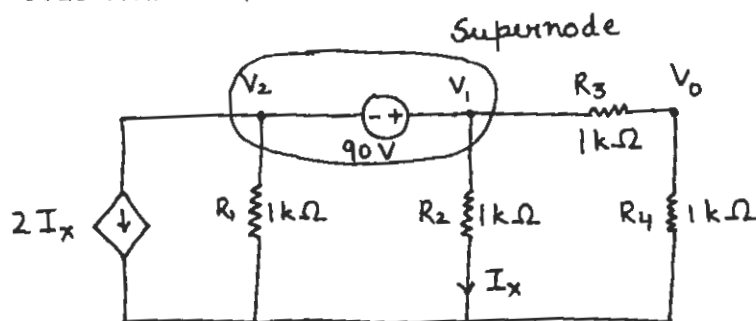

$$R_1 = R_2 = R_3 = R_4 = 1 \text{ k}\Omega$$

$$V_1 - V_2 = 90 \text{ V} \quad \text{---} \quad (1)$$

$$I_x = \frac{V_1}{R_2} = \frac{V_1}{10^3}$$

$$\text{KCL @ Supernode: } 2I_x + \frac{V_2}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3} = 0$$

$$4V_1 + V_2 - V_o = 0 \quad \text{---} \quad (2)$$

$$\text{KCL @ } V_o: \frac{V_o}{R_4} + \frac{V_o - V_1}{R_3} = 0$$

$$V_o = \frac{V_1}{2} \quad \text{---} \quad (3)$$

Substituting equation (3) in (2), we get

$$4V_1 + V_2 - \frac{V_1}{2} = 0$$



$$7V_1 + 2V_2 = 0$$

— (4)

From equations (1) and (4), we get

$$V_1 = 20 \text{ V}$$

$$V_0 = \frac{V_1}{2}$$

$$\boxed{V_0 = 10 \text{ V}}$$

3.75 Find  $V_o$  in the network in Fig. P3.75 using nodal analysis.


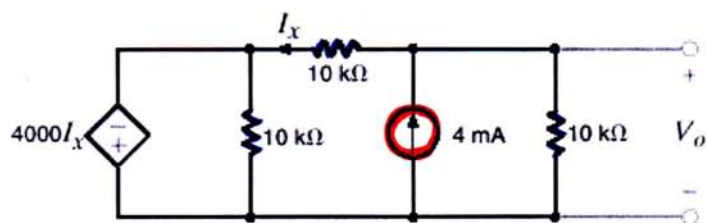


Figure P3.75

**SOLUTION:**

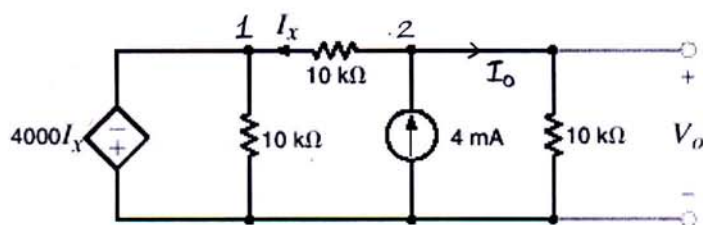

$$V_1 = -4000I_x$$

$$I_x = \frac{V_2 - V_1}{10k}$$

$$\text{KCL at 2: } 4m = I_x + I_o$$

$$\frac{V_2 - V_1}{10k} + \frac{V_2}{10k} = 4m$$

$$V_2 - V_1 + V_2 = 40$$

$$\boxed{-V_1 + 2V_2 = 40}$$

$$V_1 = -4000 \left( \frac{V_2 - V_1}{10k} \right)$$

$$V_1 = -2/5 V_2 + 2/5 V_1$$

$$5V_1 = -2V_2 + 2V_1$$

$$\boxed{-3V_1 - 2V_2 = 0}$$

$$-V_1 + 2V_2 = 40$$

$$-3V_1 - 2V_2 = 0$$


$$V_1 = -10V$$

$$V_2 = 15V$$

$$V_0 = V_2 = 15V$$


$$V_0 = 15V$$

**3.76** Use both nodal analysis and mesh analysis to find  $V_o$  in the circuit in Fig. P3.76.

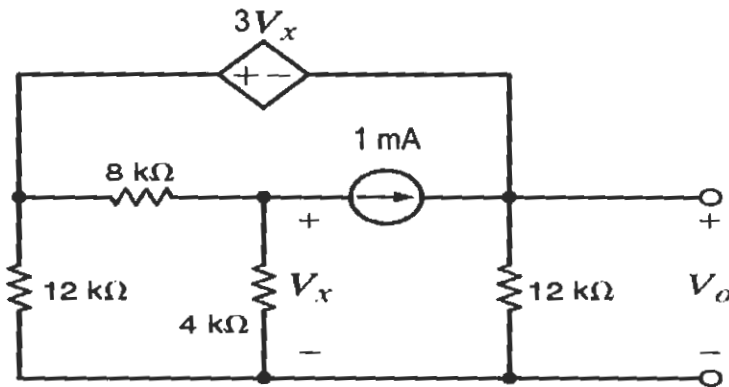

**Figure P3.76**

SOLUTION: 3.76 (a)

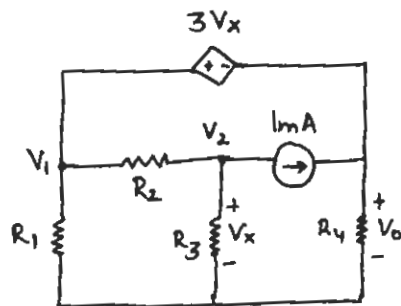

$$R_1 = R_4 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega, V_x = V_2$$

$$V_1 - V_o = 3V_x$$

$$\Rightarrow V_1 - V_o = 3V_2 \quad \text{---} \quad (1)$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + 1 \times 10^{-3} = 0$$

$$3V_2 - V_1 = -8$$


$$V_2 = \frac{-8 + V_1}{3} \quad \text{---} \quad (2)$$

Substituting equation (2) in (1), we get

$$V_1 - V_o = \frac{3(V_1 - 8)}{3}$$

$$V_o = 8.00 \text{ V}$$

3.76(b)

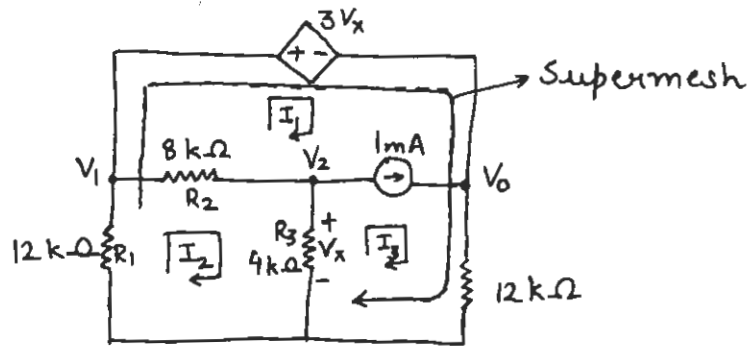

$$R_1 = R_4 = 12 \text{ k}\Omega, R_2 = 8 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega$$

$$I_3 - I_1 = 10^{-3} \text{ A} \quad \text{---} \quad (1)$$

$$V_x = (I_2 - I_3) R_3$$

$$V_0 = I_3 R_4$$

$$\text{KVL @ Supermesh: } 3V_x + I_3 R_4 + I_2 R_1 = 0$$

$$3I_2 R_3 - 3I_3 R_3 + I_3 R_4 + I_2 R_1 = 0$$

$$I_2 = 0 \text{ A} \quad \text{---} \quad (2)$$

$$\text{KVL @ } I_2 : I_2 R_1 + (I_2 - I_1) R_2 + (I_2 - I_3) R_3 = 0$$

$$2I_1 + I_3 = 0$$

$$I_1 = -\frac{I_3}{2} \quad \text{---} \quad (3)$$

Substituting equation (3) in (2), we get

$$I_3 = \frac{2}{3} \times 10^{-3} \text{ A}$$

$$V_0 = I_3 R_4$$

$$\boxed{V_0 = 8.00 \text{ V}}$$

3.77 Find  $V_x$  in the circuit in Fig. P3.77.


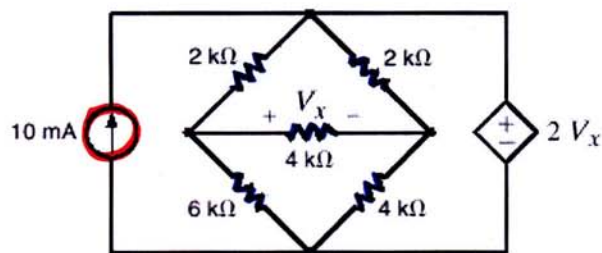


Figure P3.77

**SOLUTION:**

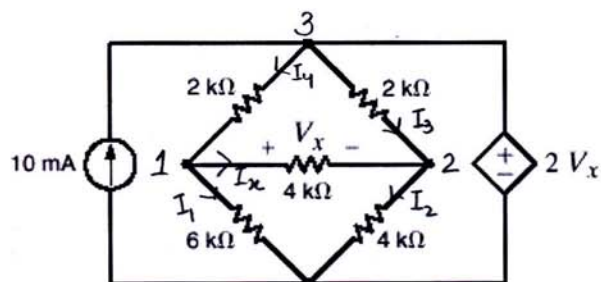

$$\text{KCL at 1: } I_4 = I_x + I_1$$

$$\frac{V_3 - V_1}{2k} = \frac{V_1 - V_2}{4k} + \frac{V_1}{6k}$$

$$6V_3 - 6V_1 = 3V_1 - 3V_2 + 2V_1$$

$$11V_1 - 3V_2 - 6V_3 = 0$$

$$\text{KCL at 2: } I_x + I_3 = I_2$$

$$\frac{V_1 - V_2}{4k} + \frac{V_3 - V_2}{2k} = \frac{V_2}{4k}$$

$$V_1 - V_2 + 2V_3 - 2V_2 = V_2$$

$$V_1 - 4V_2 + 2V_3 = 0$$

$$V_3 = 2V_x$$

$$V_x = V_1 - V_2$$

$$V_3 = 2(V_1 - V_2)$$

$$2V_1 - 2V_2 - V_3 = 0$$

$$11V_1 - 3V_2 - 6V_3 = 0$$

$$V_1 - 4V_2 + 2V_3 = 0$$

$$2V_1 - 2V_2 - V_3 = 0$$

$$V_1 = 0V$$

$$V_2 = 0V$$

$$V_3 = 0V$$

$$V_x = V_1 - V_2$$

$$V_x = 0V$$

**3.78** Using mesh analysis, find  $V_o$  in the circuit in Fig. P3.78.


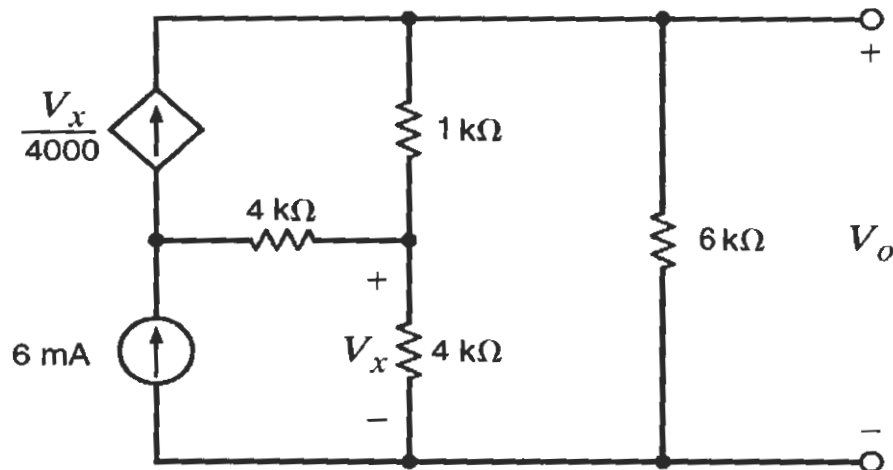


Figure P3.78

SOLUTION: 3.78

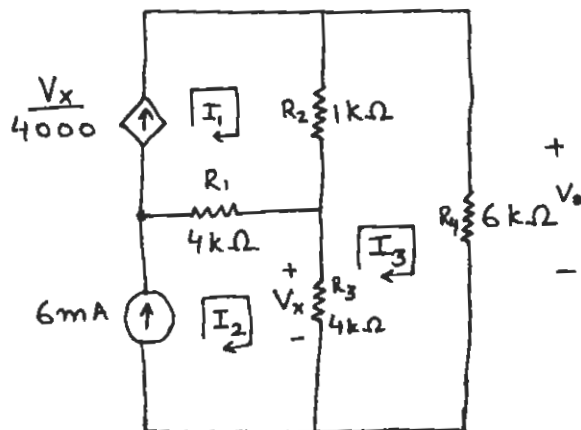

$$R_1 = R_3 = 4 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_4 = 6 \text{ k}\Omega$$

$$I_2 = 6 \times 10^{-3} \text{ A} \quad \text{---} \quad \textcircled{1}$$

$$V_x = (I_2 - I_3) R_3 \quad \text{---} \quad \textcircled{2}$$

$$I_1 = \frac{V_x}{4000} \quad \text{---} \quad \textcircled{3}$$

$$V_o = I_3 R_4$$



$$\text{KVL @ } I_3: (I_3 - I_1)R_2 + I_3R_4 + (I_3 - I_2)R_3 = 0$$

$$11 I_3 - I_1 = 24 \times 10^{-3} \quad \text{--- (4)}$$

Substituting equations (1) and (2) in (3), we get

$$I_1 = 6 \times 10^{-3} - I_3 \quad \text{--- (5)}$$

Substituting equation (5) in (4), we get

$$I_3 = \frac{30}{12} \times 10^{-3} \text{ A}$$

$$V_o = I_3 R_4$$

$$= \frac{30}{12} \times 10^{-3} \times 6 \times 10^3$$

$$\boxed{V_o = 15.0 \text{ V}}$$

3.79 Find  $I_o$  in the circuit in Fig. P3.79.


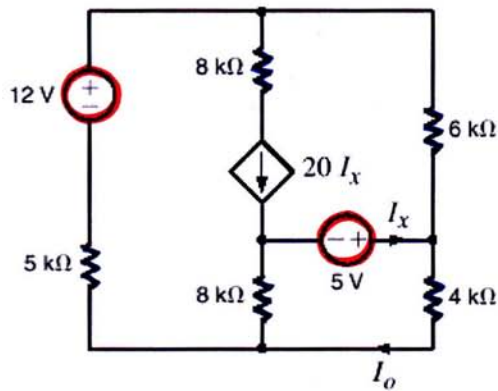


Figure P3.79

**SOLUTION:**

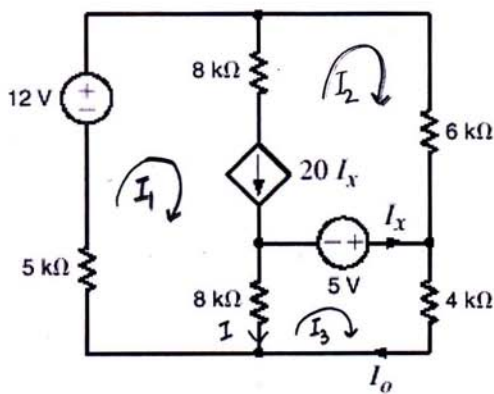

$$\text{KVL: } 12 = 5kI_1 + 6kI_2 + 4kI_3$$

$$\boxed{5kI_1 + 6kI_2 + 4kI_3 = 12}$$

$$\text{KCL: } I + I_3 = I_1$$

$$I = I_1 - I_3$$

$$\text{KVL: } 5 = 4kI_3 + 8k(-I)$$

$$4kI_3 - 8k(I_1 - I_3) = 5$$

$$\boxed{-8kI_1 + 12kI_3 = 5}$$

$$\text{KCL: } I_1 = 20I_x + I_2$$

$$I_1 - I_2 - 20(I_3 - I_2) = 0$$

$$I_1 + 19I_2 - 20I_3 = 0$$

$$5kI_1 + 6kI_2 + 4kI_3 = 12$$

$$-8kI_1 + 0I_2 + 12kI_3 = 5$$

$$I_1 + 19I_2 - 20I_3 = 0$$

$$I_1 = 0.66mA$$

$$I_2 = 0.871mA$$

$$I_3 = 0.861mA$$

$$I_0 = I_3$$

$$I_0 = 0.861mA$$

3.80 Write mesh equations for the circuit in Fig. P3.80 using the assigned currents.


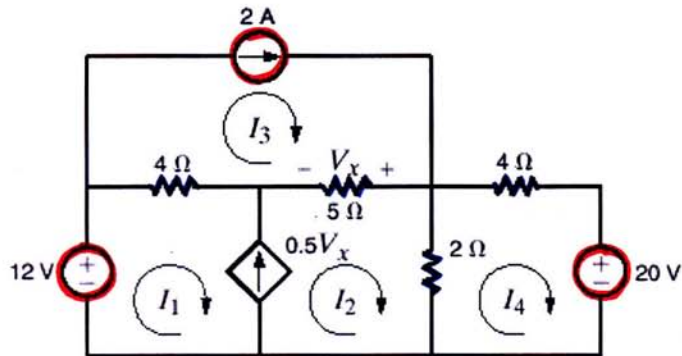


Figure P3.80

**SOLUTION:**

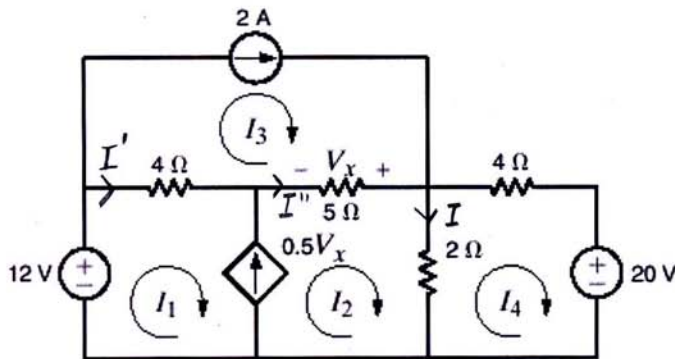

$$\text{KCL: } I_1 = I' + I_3$$

$$I' = I_1 - I_3$$

$$\text{KCL: } I + I_4 = I_2$$

$$I = I_2 - I_4$$

$$\text{KCL: } I'' + I_3 = I + I_4$$

$$I'' = -I_3 + I_4 + I_2 - I_4$$

$$I'' = I_2 - I_3$$

$$\text{KCL: } I_2 = 0.5V_x + I_1$$

$$-I_1 + I_2 - 0.5V_x = 0$$

$$V_x = -I''(5) = -5(I_2 - I_3)$$

$$V_x = -5I_2 + 5I_3$$

$$-I_1 + I_2 - 0.5(-5I_2 + 5I_3) = 0$$

$$\boxed{-I_1 + 3.5I_2 - 2.5I_3 = 0}$$

$$I_3 = 2A$$

$$\text{KVL: } 4I_y + 20 + 2(-I) = 0$$

$$4I_y - 2(I_2 - I_y) = -20$$

$$\boxed{-2I_2 + 16I_y = -20}$$

$$\text{KVL: } 12 = 4I' + 5I'' + 4I_y + 20$$

$$4(I_1 - I_3) + 5(I_2 - I_3) + 4I_y = -8$$

$$4I_1 + 5I_2 - 9I_3 + 4I_y = -8$$

$$\boxed{4I_1 + 5I_2 + 4I_y = 10}$$

$$-I_1 + 3.5I_2 - 2.5I_3 = 0$$

$$-2I_2 + 6I_y = -20$$

$$4I_1 + 5I_2 + 4I_y = 10$$

$$I_3 = 2A$$

$$-I_1 + 3.5I_2 = 5$$

$$-2I_2 + 6I_y = -20$$


$$4I_1 + 5I_2 + 4I_y = 10$$

$$I_1 = 2.46A$$

$$I_2 = 2.13A$$


$$I_y = -2.62A$$

**3.81** Find  $V_o$  in the network in Fig. P3.81.

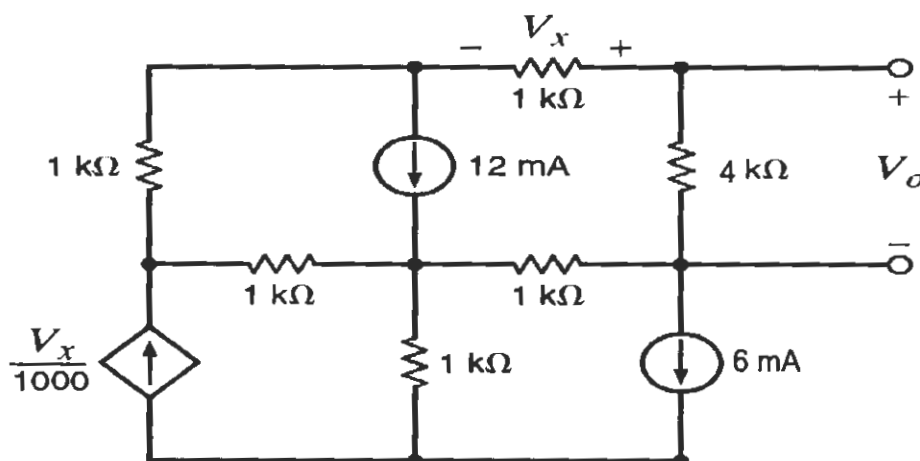

**Figure P3.81**

**SOLUTION:** 3-81

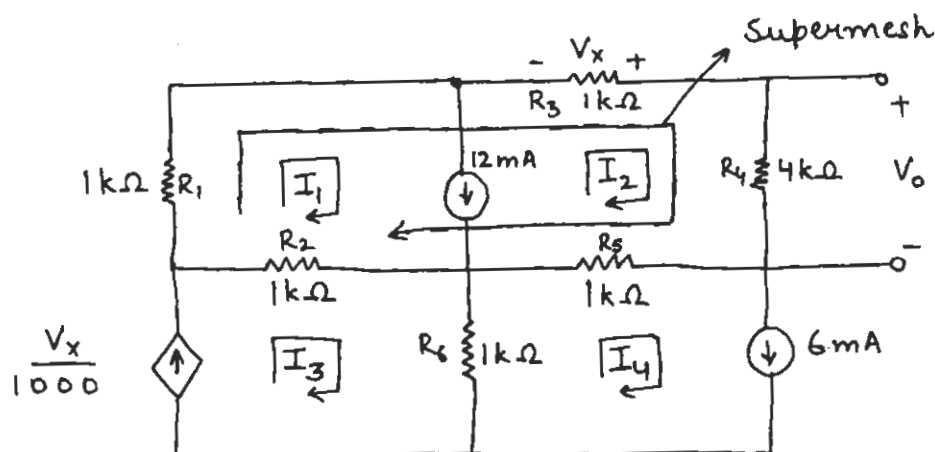

$$R_1 = R_2 = R_3 = R_5 = R_6 = 1 \text{ k}\Omega, R_4 = 4 \text{ k}\Omega$$

$$I_1 - I_2 = 12 \text{ mA} \quad \text{---} \quad (1)$$

$$I_4 = 6 \text{ mA}$$

$$V_x = -I_2 R_3$$

$$I_3 = \frac{V_x}{1000}$$

$$V_o = I_2 R_4$$

$$\text{KVL @ supermesh: } I_1 R_1 + I_2 R_3 + I_2 R_4 + (I_2 - I_4) R_5 + (I_1 - I_3) R_2 = 0$$

$$I_1 (R_1 + R_2) + I_2 (R_3 + R_4 + R_5) - I_3 R_2 - I_4 R_5 = 0$$

$$2 \times 10^3 I_1 + 6 \times 10^3 I_2 - 10^3 I_3 - 10^3 I_4 = 0$$

$$2 I_1 + 6 I_2 - I_3 - I_4 = 0$$

Substituting  $I_3 = \frac{V_x}{1000}$  and  $V_x = -I_2 R_3$

$$2 I_1 + 7 I_2 = 6 \times 10^{-3} \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$I_2 = -2 \text{ mA}$$

$$V_o = I_2 R_4$$

$$V_o = -2 \times 10^{-3} \times 4 \times 10^3$$

$$\boxed{V_o = -8.00 \text{ V}}$$

3.82 Using nodal analysis, find  $V_o$  in the circuit in Fig. P3.82.


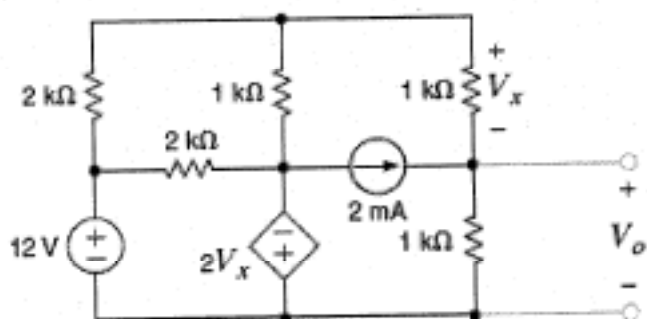


Figure P3.82

Solution: 3.82

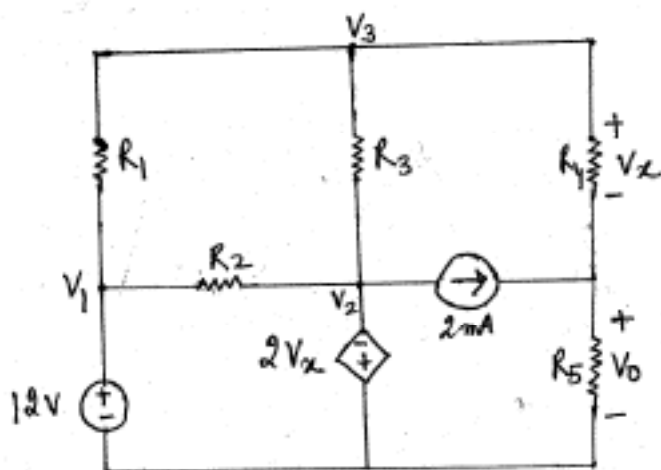

$$R_1 = R_2 = 2 \text{ k}\Omega$$

$$R_3 = R_4 = R_5 = 1 \text{ k}\Omega$$

$$V_x = V_3 - V_o$$

$$V_1 = 12 \text{ V}$$

$$V_2 = -2V_x$$

$$\text{at } V_3 : \frac{V_3 - V_1}{R_1} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_o}{R_4} = 0$$

$$\text{at } V_o : \frac{V_3 - V_o}{R_4} + 2 \times 10^{-3} = \frac{V_o}{R_5}$$

$$\text{Solve for } V_o : \boxed{V_o = 2.5 \text{ V}}$$



3.83 Solve for the assigned mesh currents in the network in Fig. P3.83.


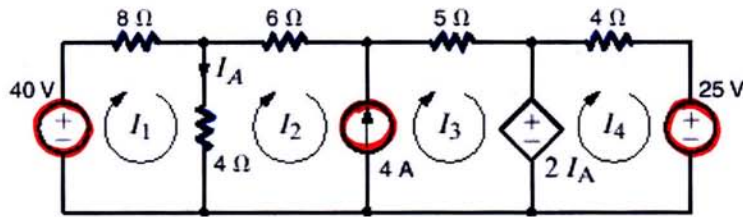


Figure P3.83

**SOLUTION:**

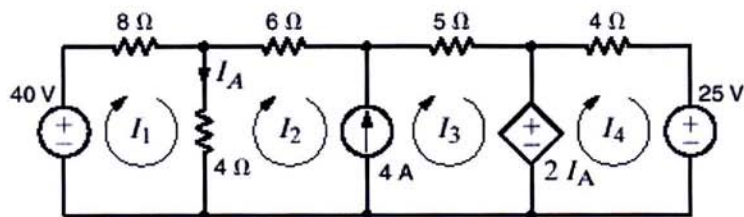

$$\text{KCL: } I_1 = I_A + I_2$$

$$I_A = I_1 - I_2$$

$$\text{KVL: } 8I_1 + 4I_A = 40$$

$$8I_1 + 4(I_1 - I_2) = 40$$

$$\boxed{12I_1 - 4I_2 = 40}$$

$$\text{KVL: } 2I_A = 4I_4 + 25$$

$$2(I_1 - I_2) = 4I_4 + 25$$

$$\boxed{2I_1 - 2I_2 - 4I_4 = 25}$$

$$\text{KVL: } 8I_1 + 6I_2 + 5I_3 + 4I_4 + 25 = 40$$

$$\boxed{8I_1 + 6I_2 + 5I_3 + 4I_4 = 15}$$

$$\text{KCL: } I_2 + 4 = I_3$$

$$\boxed{-I_2 + I_3 = 4}$$

$$12I_1 - 4I_2 + 0I_3 + 0I_4 = 40$$

$$2I_1 - 2I_2 + 0I_3 - 4I_4 = 25$$

$$8I_1 + 6I_2 + 5I_3 + 4I_4 = 15$$

$$0I_1 - I_2 + I_3 + 0I_4 = 4$$

$$I_1 = 2.97A$$

$$I_2 = -1.08A$$

$$I_3 = 2.92A$$

$$I_4 = -4.22A$$

- 3.84 Using the assigned mesh currents shown in Fig. P3.84 solve for the power supplied by the dependent voltage source.


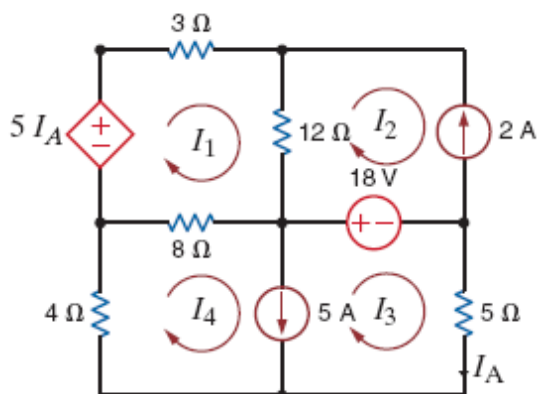


Figure P3.84

**SOLUTION:**

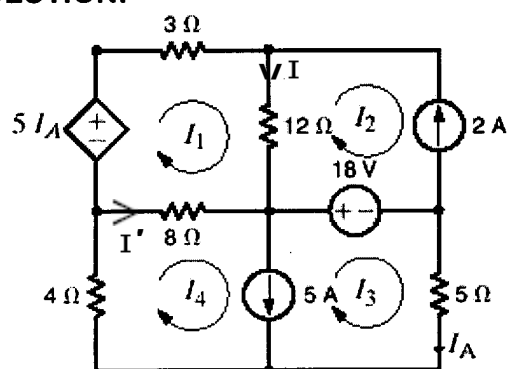

$$\text{KCL: } I_1 = I + I_2$$

$$I = I_1 - I_2$$

$$\text{KCL: } I_4 = I' + I_1$$

$$I' = I_4 - I_1$$

$$\text{KVL: } 3I_1 + 12I + 8(-I') = 5I_A$$

$$I_A = I_3$$

$$3I_1 + 12(I_1 - I_2) - 8(I_4 - I_1) = 5I_3$$

$$\boxed{23I_1 - 12I_2 - 5I_3 - 8I_4 = 0}$$

$$\text{KVL: } 8I' + 5I_3 + 4I_4 + 18 = 0$$

$$8(I_4 - I_1) + 5I_3 + 4I_4 = -18$$

$$\boxed{-8I_1 + 5I_3 + 12I_4 = -18}$$

$$\text{KCL: } I_3 + 5 = I_4$$

$$I_2 = -2A$$

$$I_3 - I_4 = -5$$

$$23I_1 - 5I_3 - 8I_4 = -24$$

$$23I_1 - 5I_3 - 8I_4 = -24$$

$$-8I_1 + 5I_3 + 12I_4 = -18$$

$$0I_1 + I_3 - I_4 = -5$$

$$I_1 = -2.59A$$

$$I_3 = -5.8A$$

$$I_4 = -0.8A$$

$$\text{and } I_2 = -2A$$

$$\therefore P_{5IA} = (5 \times -5.8)(-2.59) = 75W$$

3.85 Determine  $V_0$  in the network in the Fig. P3.85 using loop analysis.


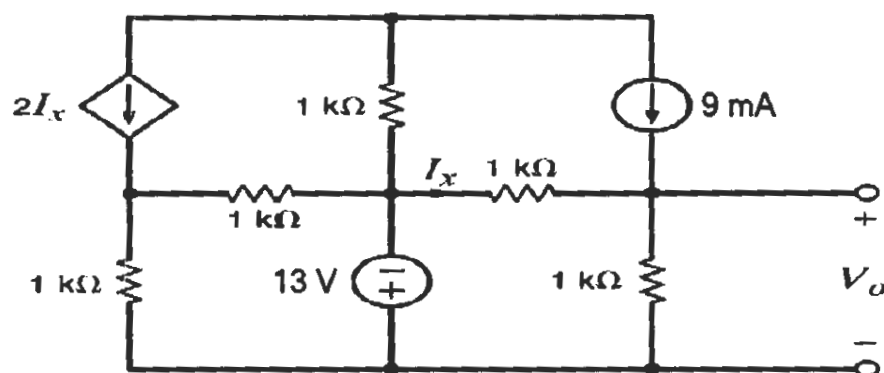


Figure P3.85

Solution: 3.85

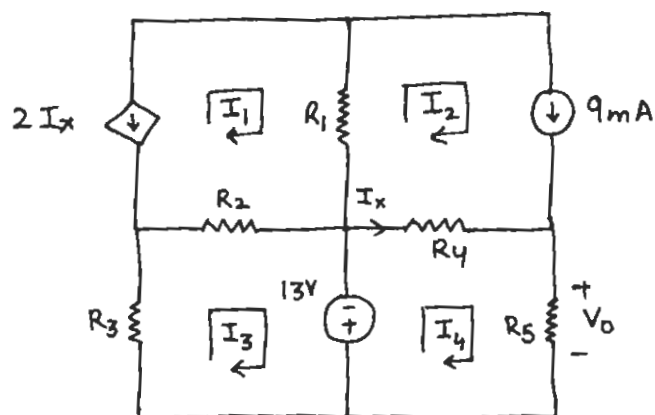

$$R_1 = R_2 = R_3 = R_4 = R_5 = 1 \text{ k}\Omega$$

$$I_2 = 9 \text{ mA}$$

$$I_x = (I_4 - I_2)$$

$$I_1 = -2I_x$$

$$= -2(I_4 - I_2)$$

$$V_0 = I_4 R_5$$

$$\text{KVL @ } I_4: 13 + (I_4 - I_2)R_4 + I_4 R_5 = 0$$

$$13 + 10^3 I_4 - 10^3 I_2 + 10^3 I_4 = 0$$

$$I_4 = -2 \times 10^{-3} \text{ A}$$

$$V_0 = I_4 R_5 = -2 \times 10^{-3} \times 1 \times 10^3$$

$$\boxed{V_0 = -2.00 \text{ V}}$$

3.86 Using loop analysis, find  $V_o$  in the network in Fig. P3.86.


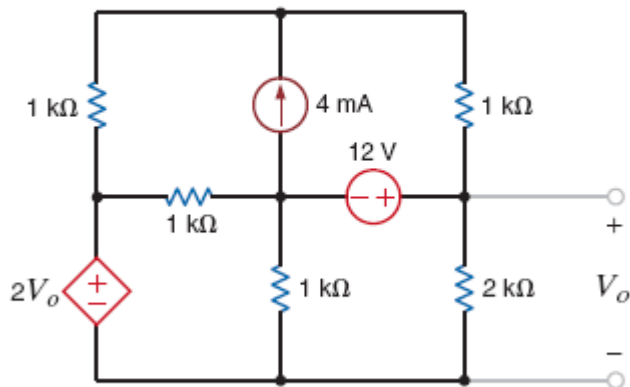


Figure P3.86

**SOLUTION:**

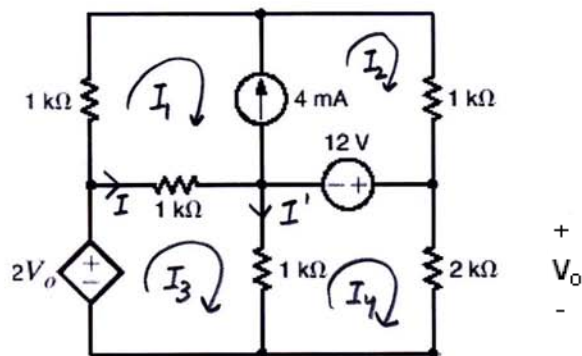

$$\text{KCL: } I_1 + 4\text{ m} = I_2$$

$$\boxed{I_1 - I_2 = -4\text{ m}}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

$$\text{KCL: } I' + I_4 = I_3$$

$$I' = I_3 - I_4$$

$$\text{KVL: } 2\text{ k} I_4 + 1\text{ k} (-I') = 12$$

$$-1\text{ k} (I_3 - I_4) + 2\text{ k} I_4 = 12$$

$$\boxed{-1\text{ k} I_3 + 3\text{ k} I_4 = 12}$$

$$\text{KVL: } 1k I + 1k I' = 2V_0$$

$$V_0 = 2k I_4$$

$$1k(I_3 - I_1) + 1k(I_3 - I_4) = 2(2k I_4)$$

$$\boxed{-1k I_1 + 2k I_3 - 5k I_4 = 0}$$

$$\text{KVL: } 2V_0 = 1k I_1 + 1k I_2 + 2k I_4$$

$$V_0 = 2k I_4$$

$$\boxed{1k I_1 + 1k I_2 - 2k I_4 = 0}$$

$$I_1 - I_2 + 0I_3 + 0I_4 = -4m$$

$$0I_1 + 0I_2 - 1k I_3 + 3k I_4 = 12$$

$$-1k I_1 + 0I_2 + 2k I_3 - 5k I_4 = 0$$

$$1k I_1 + 1k I_2 + 0I_3 - 2k I_4 = 0$$

In the matrix form the equations can be represented/restructured as:

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 2 & 0 & -2 \\ 0 & 0 & 4 & -12 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -4 \\ 4 \\ -4 \\ 44 \end{bmatrix}$$

$$V_0 = \infty$$

Since there are only 3 independent equations for 4 unknowns (1 to 4), it can be not be solved for a unique solution.

This is because current equations are contradictory.  
 $\therefore V_0 = \text{not defined (open circuit)}$ .

3.87 Using loop analysis, find  $V_o$  in the circuit in Fig. P3.87.


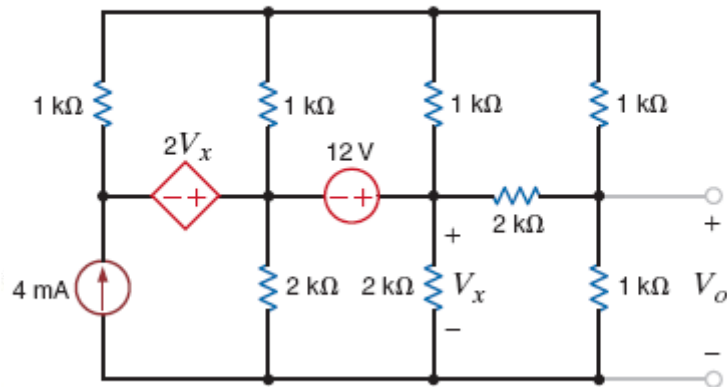


Figure P3.87

**SOLUTION:**

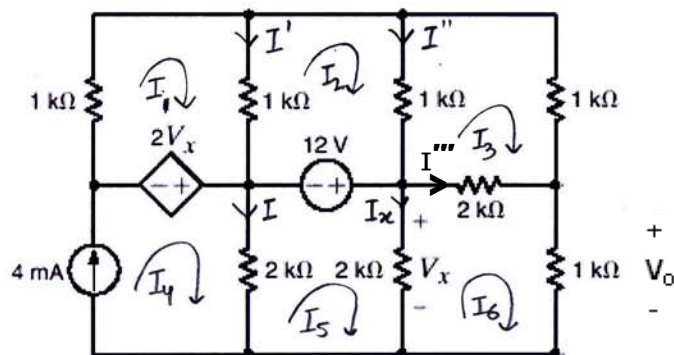

$$\text{KCL: } I_1 = I' + I_2$$

$$I' = I_1 - I_2$$

$$\text{KCL: } I_2 = I'' + I_3$$

$$I'' = I_2 - I_3$$

$$\text{KCL: } I + I_5 = I_4$$

$$I = I_4 - I_5$$

$$\text{KCL: } I_x + I_6 = I_5$$

$$I_x = I_5 - I_6$$

$$\text{KCL: } I_3 + I''' = I_6$$

$$I''' = I_6 - I_3$$

$$\text{KVL: } 2V_x + 1kI_1 + 1kI' = 0$$



$$V_x = I_x(2k) = (I_5 - I_6)2k$$

$$2(2k)(I_5 - I_6) + 1kI_1 + 1k(I_1 - I_2) = 0$$

$$4kI_5 - 4kI_6 + 2kI_1 - 1kI_2 = 0$$

$$\boxed{2kI_1 - 1kI_2 + 4kI_5 - 4kI_6 = 0}$$

$$\text{KVL: } 12 + 1k(-I') + 1kI'' = 0$$

$$-1k(I_1 - I_2) + 1k(I_2 - I_3) = -12$$

$$-1kI_1 + 2kI_2 - 1kI_3 = -12$$

$$\text{KVL: } 1k(-I'') + 1kI_3 + 2k(-I''') = 0$$

$$-1k(I_2 - I_3) + 1kI_3 - 2k(I_6 - I_3) = 0$$

$$\boxed{-1kI_2 + 4kI_3 - 2kI_6 = 0}$$

$$\text{KVL: } 12 = 2k(-I) + 2kI_x$$

$$-2k(I_4 - I_5) + 2k(I_5 - I_6) = 12$$

$$I_4 = 4\text{mA}$$

$$\boxed{4kI_5 - 2kI_6 = 20}$$

$$\text{KVL: } 2kI''' + 1kI_6 + 2k(-I_x) = 0$$

$$2k(I_6 - I_3) + 1kI_6 - 2k(I_5 - I_6) = 0$$

$$\boxed{-2kI_3 - 2kI_5 + 5kI_6 = 0}$$

$$2kI_1 - 1kI_2 + 0I_3 + 4kI_5 - 4kI_6 = 0$$

$$-1kI_1 + 2kI_2 - 1kI_3 + 0I_5 + 0I_6 = -12$$

$$0I_1 - 1kI_2 + 4kI_3 + 0I_5 - 2kI_6 = 0$$

$$0I_1 + 0I_2 + 0I_3 + 4kI_5 - 2kI_6 = 20$$

$$0I_1 + 0I_2 - 2kI_3 - 2kI_5 + 5kI_6 = 0$$

$$I_1 = -18\text{mA}$$

$$I_2 = -17\text{mA}$$

$$I_3 = -4\text{mA}$$

$$I_5 = 5.25\text{mA}$$

$$I_6 = 0.5\text{mA}$$

$$V_o = 1\text{k}(I_6) = 1\text{k}(0.5\text{mA})$$

$$V_o = 0.5\text{V}$$

3.88 Use loop analysis to determine  $I_o$  in the circuit in the Fig. P3.88.


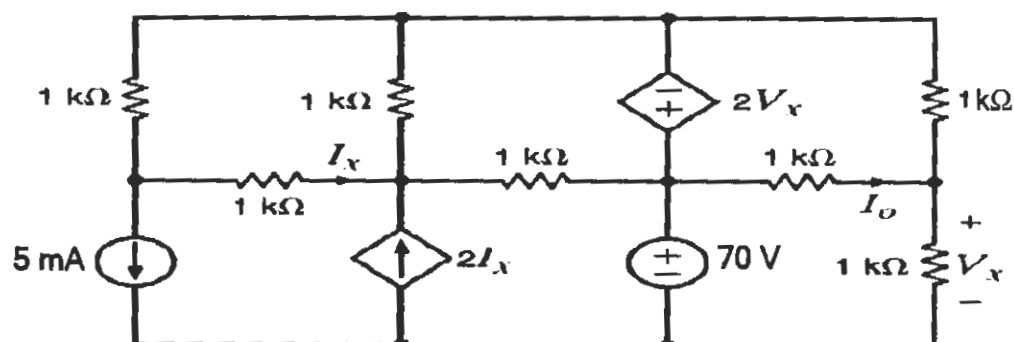


Figure P3.88

Solution: 3.88

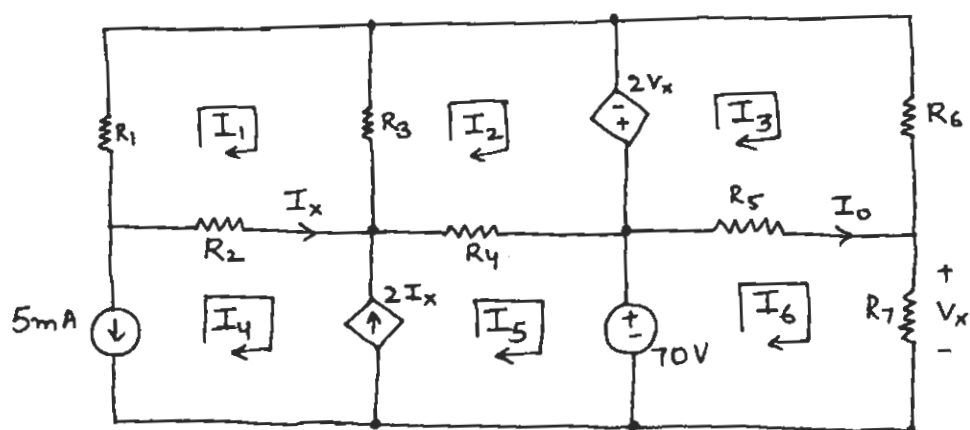

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_4 = 5 \text{ mA}$$

$$2I_x = I_5 - I_4$$

$$I_x = I_4 - I_1$$

$$I_o = I_6 - I_3$$

$$V_x = I_6 R_7$$

$$\text{KVL @ } I_1: I_1 R_1 + (I_1 - I_2) R_3 + (I_1 - I_4) R_2 = 0$$

$$3I_1 - I_2 = 5 \times 10^{-3}$$

$$\text{KVL @ } I_2: (I_2 - I_1)R_3 - 2V_x + (I_2 - I_5)R_4 = 0$$

$$-I_1 + 2I_2 - I_5 - 2I_6 = 0$$

$$\text{KVL @ } I_3: 2V_x + I_3R_6 + (I_3 - I_6)R_5 = 0$$

$$2I_3 + I_6 = 0 \quad \text{---} \quad (1)$$

$$\text{KVL @ } I_6: -70 + (I_6 - I_3)R_5 + I_6R_7 = 0$$

$$-I_3 + 2I_6 = 70 \times 10^{-3} \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$I_6 = 28 \text{ mA}$$

Substituting the value of  $I_6$  in (1), we get

$$2I_3 = -28 \times 10^{-3}$$

$$I_3 = -14 \text{ mA}$$

$$I_0 = I_6 - I_3$$

$$\boxed{I_0 = 42.0 \text{ mA}}$$

3.89 Using loop analysis, find  $I_o$  in the circuit in Fig. P3.89.


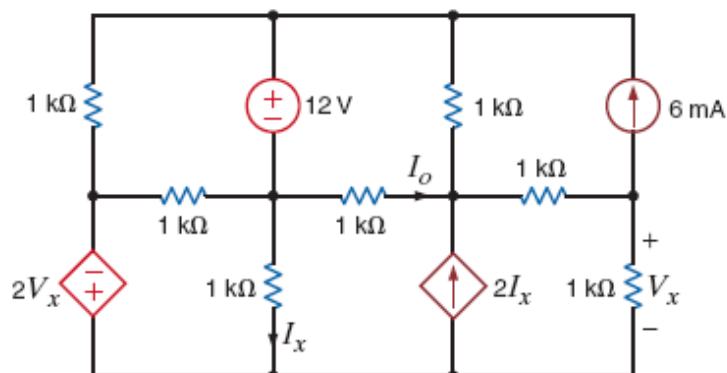


Figure P3.89

**SOLUTION:**

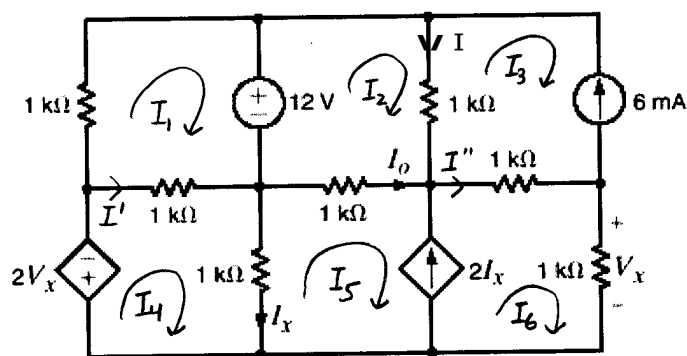

$$\text{KCL: } I_2 = I + I_3$$

$$I = I_2 - I_3$$

$$\text{KCL: } I_4 = I' + I_1$$

$$I' = I_4 - I_1$$

$$\text{KCL: } I_3 + I'' = I_6$$

$$I'' = I_6 - I_3$$

$$\text{KCL: } I_5 + I_x = I_4$$

$$I_x = I_4 - I_5$$

$$\text{KCL: } I_o + I + 2I_x = I''$$

$$I_o = I'' - I - 2I_x = I_6 - I_3 - I_2 + I_3 - 2I_x$$

$$I_o = I_6 - I_2 - 2(I_4 - I_5)$$

$$I_o = -I_2 - 2I_4 + 2I_5 + I_6$$

$$\text{KVL: } 1kI_1 + 12 + 1k(-I_1') = 0$$

$$1kI_1 - 1k(I_4 - I_1) = -12$$

$$\boxed{2kI_1 - 1kI_4 = -12}$$

$$\text{KVL: } 1kI + 1k(-I_0) = 12$$

$$1k(I_2 - I_3) - 1k(-I_2 - 2I_4 + 2I_5 + I_6) = 12$$

$$\boxed{2kI_2 - 1kI_3 + 2kI_4 - 2kI_5 - 1kI_6 = 12}$$

$$\text{KVL: } 2V_x + 1kI' + 1kI_x = 0$$

$$V_x = 1kI_6$$

$$2(1kI_6) + 1k(I_4 - I_1) + 1k(I_4 - I_5) = 0$$

$$\boxed{-1kI_1 + 2kI_4 - 1kI_5 + 2kI_6 = 0}$$

$$\text{KCL: } I_6 = 2I_x + I_5$$

$$I_5 - I_6 + 2(I_4 - I_5) = 0$$

$$\boxed{2I_4 - I_5 - I_6 = 0}$$

$$\text{KVL: } 2V_x + 1kI' + 1kI_0 + 1kI'' + 1kI_6 = 0$$

$$2(1kI_6) + 1k(I_4 - I_1) + 1k(-I_2 - 2I_4 + 2I_5 + I_6) + 1k(I_6 - I_3) + 1kI_6$$

$$\boxed{-1kI_1 - 1kI_2 - 1kI_3 - 1kI_4 + 2kI_5 + 5kI_6 = 0}$$

$$I_3 = -6\text{mA}$$

$$\boxed{2kI_2 + 2kI_4 - 2kI_5 - 1kI_6 = 6}$$

$$\boxed{-1kI_1 - 1kI_2 - 1kI_4 + 2kI_5 + 5kI_6 = -6}$$

$$\begin{aligned}
 2kI_1 + 0I_2 - 1kI_4 + 0I_5 + 0I_6 &= -12 \\
 0I_1 + 2kI_2 + 2kI_4 - 2kI_5 - 1kI_6 &= 6 \\
 -1kI_1 + 0I_2 + 2kI_4 - 1kI_5 + 2kI_6 &= 0 \\
 0I_1 + 0I_2 + 2I_4 - I_5 - I_6 &= 0 \\
 -1kI_1 - 1kI_2 - 1kI_4 + 2kI_5 + 5kI_6 &= -6
 \end{aligned}$$

$$I_1 = -6.48 \text{ mA}$$

$$I_2 = 3.12 \text{ mA}$$

$$I_4 = -0.96 \text{ mA}$$

$$I_5 = 0.24 \text{ mA}$$

$$I_6 = -2.16 \text{ mA}$$

$$I_0 = -I_2 - 2I_4 + 2I_5 + I_6$$

$$I_0 = -3.12 \text{ m} - 2(-0.96 \text{ m}) + 2(0.24 \text{ m}) - 2.16 \text{ m}$$

$$I_0 = -2.88 \text{ mA}$$

- 3.90 Use mesh analysis to determine the power delivered by the independent 3-V source in the network in Fig. P3.90.


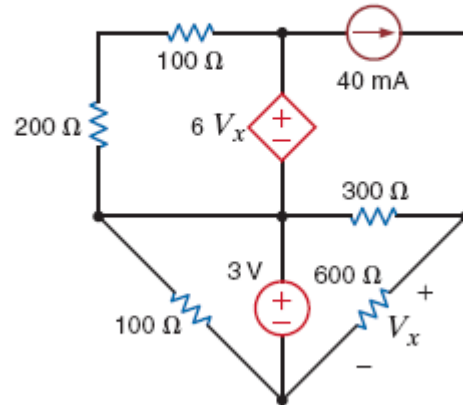


Figure P3.90

**SOLUTION:**

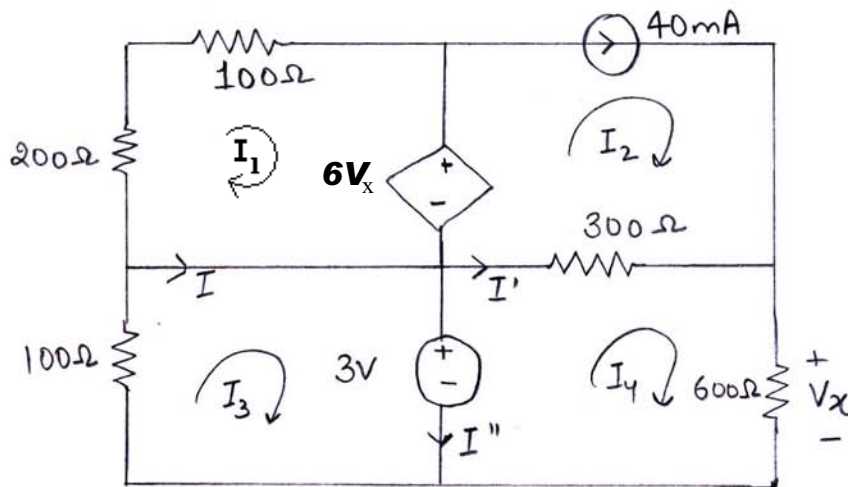

$$I_2 = 40 \text{ mA}$$

$$\text{KCL: } I_3 = I + I_1$$

$$I = I_3 - I_1$$

$$\text{KCL: } 40 \text{ mA} + I' = I_4$$

$$I' = I_4 - 40 \text{ mA}$$

$$\text{KVL: } 200 I_1 + 100 I_1 + 6V_x = 0$$

$$V_x = 600 I_4$$

$$300 I_1 + 3600 I_4 = 0$$

$$\text{KVL: } 100 I_3 + 3 = 0$$



$$\begin{aligned}I_3 &= -30 \text{ mA} \\ \text{KVL: } 3 &= 300I' + 600I_4 \\ 600I_4 + 300(I_4 - 40\text{m}) &= 3 \\ 900I_4 &= 15 \\ I_4 &= 16.67 \text{ mA}\end{aligned}$$

$$\begin{aligned}\text{KCL: } I_4 + I'' &= I_3 \\ I'' &= I_3 - I_4\end{aligned}$$

$$\begin{aligned}P_{3V} &= I''(3) = 3(I_3 - I_4) \\ P_{3V} &= 3(-30\text{m} - 16.67\text{m}) \\ P_{3V} &= -140.01 \text{ mW} \\ P_{3V} &= 140.01 \text{ mW}\end{aligned}$$

**3.91** Use mesh analysis to find the power delivered by the current-controlled voltage source in the circuit in Fig. P3.91.


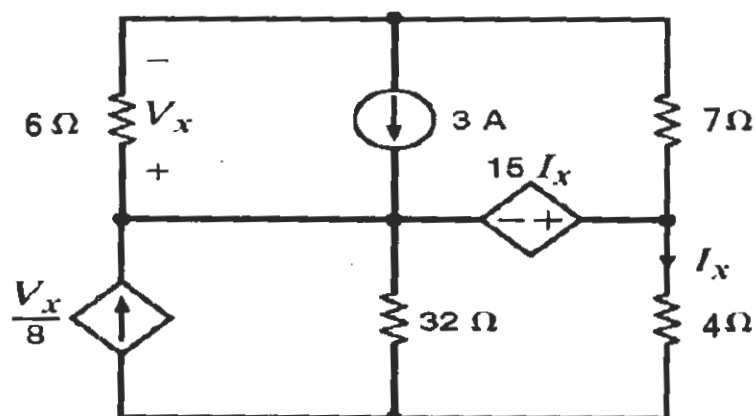


Figure P3.91

Solution: 3-41

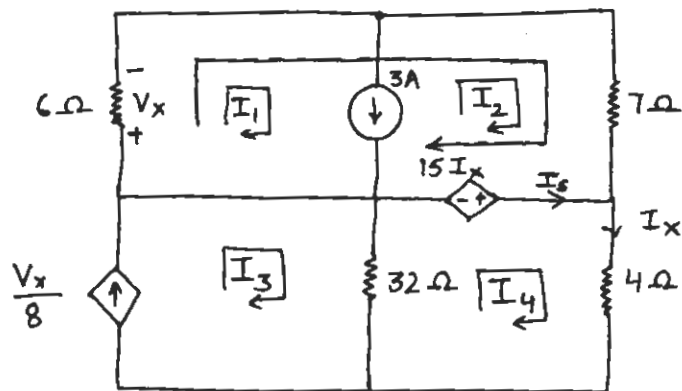

$$I_1 - I_2 = 3$$

$$V_x = 6 I_1$$

$$I_s = I_4 - I_2$$

$$I_x = I_4$$

$$I_3 = \frac{V_x}{8} = \frac{3}{4} I_1$$

$$\text{KVL @ } I_4 : 32(I_4 - I_3) - 15 I_x + 4 I_4 = 0$$

$$21 I_4 - 32 I_3 = 0$$

$$I_4 = 1.52 I_3$$

$$\text{KVL @ Supermesh: } 6I_1 + 7I_2 + 15I_x = 0$$

$$23.18I_1 + 7I_2 = 0 \quad \text{---} \quad (2)$$

From equations (1) and (2), we get

$$I_1 = 0.696 \text{ A}$$

$$I_3 = \frac{3}{4} I_1 = 0.522 \text{ A}$$

$$I_4 = 1.52 I_3 = 0.793 \text{ A}$$

$$I_s = I_4 - I_2 = 3.09 \text{ A}$$

$$P_{ccvs} = (15I_x) I_s$$

$$\boxed{P_{ccvs} = 37.0 \text{ W}}$$

3.92 Use nodal analysis to determine  $I_o$  in the circuit in Fig. P3.92.


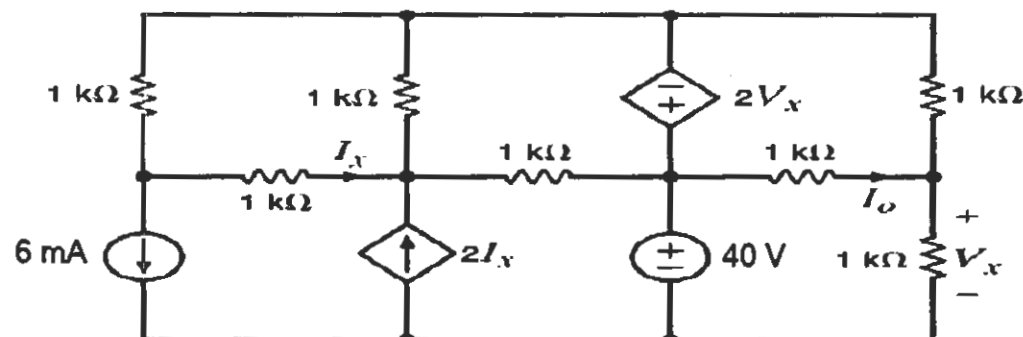


Figure P3.92

Solution: 3.92

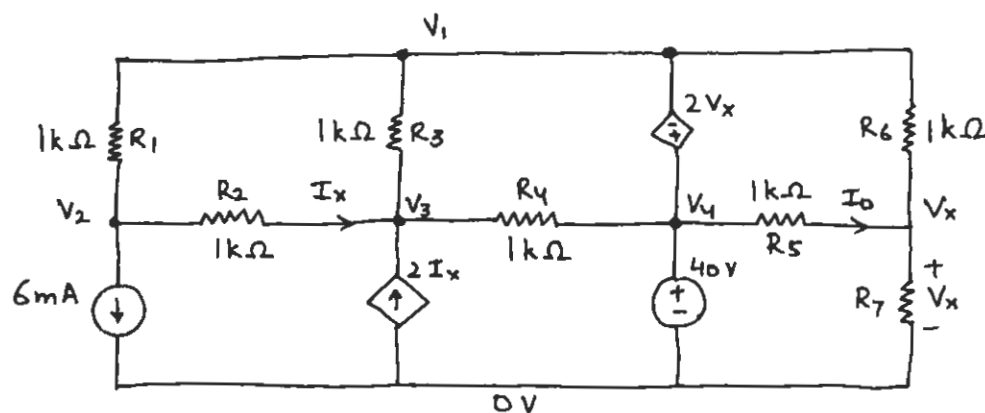

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$V_4 = 40 \text{ V}$$

$$V_4 - V_1 = 2V_x \quad \text{--- (1)}$$

$$\frac{V_2 - V_3}{R_2} = I_x$$

$$I_o = \frac{V_5 - V_x}{R_5}$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_3}{R_2} + 6 \times 10^{-3} = 0$$

$$-V_1 + 2V_2 - V_3 = -6$$

$$\begin{aligned} \text{KCL @ } V_3 : \frac{V_3 - V_2}{R_2} - 2 I_x + \frac{V_3 - V_1}{R_3} + \frac{V_3 - V_4}{R_4} &= 0 \\ -V_1 - 3V_2 + 5V_3 &= 40 \quad (\text{Using } V_4 = 40 \text{ V}) \end{aligned}$$

$$\text{KCL @ } V_x : \frac{V_x - V_4}{R_5} + \frac{V_x - V_1}{R_6} + \frac{V_x}{R_7} = 0$$

$$3V_x - V_4 - V_1 = 0 \quad \text{--- (2)}$$

Substituting equation (1) in (2), we get

$$3\left(\frac{V_4 - V_1}{2}\right) - V_4 - V_1 = 0$$

$$-\frac{5}{2}V_1 + \frac{1}{2}V_4 = 0$$

$$-5V_1 + 40 = 0$$

$$V_1 = 8 \text{ V}$$

$$(\text{Using } V_4 = 40 \text{ V})$$

$$V_x = \frac{V_4 - V_1}{2} = \frac{40 - 8}{2}$$


$$V_x = 16 \text{ V}$$

$$I_0 = \frac{V_4 - V_x}{R_5}$$

$$= \frac{40 - 16}{1 \times 10^3}$$


$$\boxed{I_0 = 24.0 \text{ mA}}$$

**3.93** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.93.

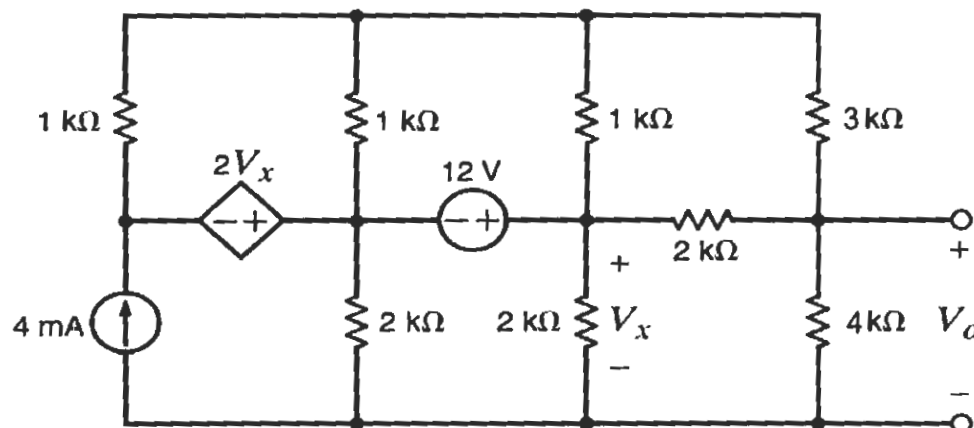

**Figure P3.93**

**SOLUTION:** 3.93

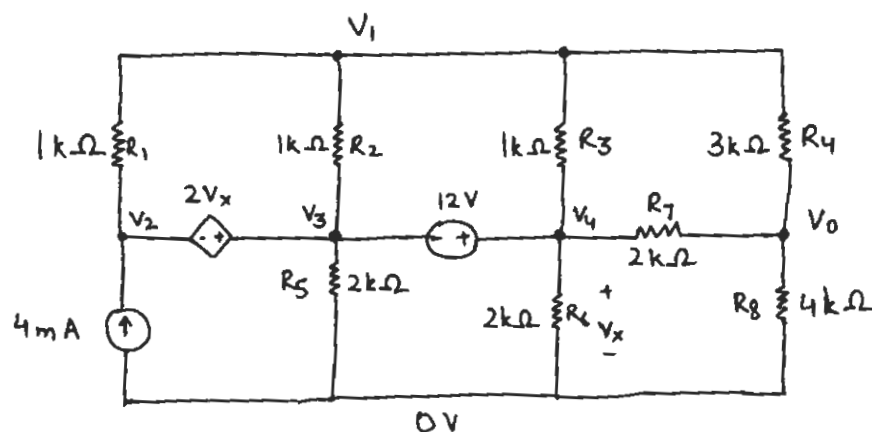

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega, R_4 = 3 \text{ k}\Omega, R_5 = R_6 = R_7 = 2 \text{ k}\Omega, R_8 = 4 \text{ k}\Omega$$

$$V_3 - V_2 = 2V_x \quad \text{---} \quad \textcircled{1}$$

$$V_4 - V_3 = 12 \text{ V} \quad \text{---} \quad \textcircled{2}$$

$$V_x = V_4 \quad \text{---} \quad \textcircled{3}$$

$$\begin{aligned} \text{KCL @ } V_1: \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_2} + \frac{V_1 - V_4}{R_3} + \frac{V_1 - V_0}{R_4} &= 0 \\ -3V_4 - 3V_3 - 3V_2 + 10V_1 - V_0 &= 0 \quad \text{---} \quad \textcircled{4} \end{aligned}$$

$$\begin{aligned} \text{KCL @ reference: } \frac{V_3}{R_5} + \frac{V_4}{R_6} + \frac{V_0}{R_8} &= 4 \times 10^{-3} \\ 4V_3 + V_0 &= -8 \quad \text{---} \quad \textcircled{5} \end{aligned}$$

$$\text{KCL at } V_0: \frac{V_0 - V_1}{3 \times 10^3} + \frac{V_0 - V_4}{2 \times 10^3} + \frac{V_0}{4 \times 10^3} = 0$$

$$V_1 = \frac{13V_0 - 6V_4}{4} \quad \text{---} \quad (6)$$

Substituting equations (1), (2), (3) and (6) in (4), we get

$$-3V_4 - 3V_3 - 3V_2 + 10 \cdot \frac{13V_0 - 6V_4}{4} - V_0 = 0$$

$$-18(12 + V_3) - 3V_3 - 3(V_3 - 2(12 + V_3)) + \frac{63}{2}V_0 = 0$$

$$-4V_3 + 7V_0 = 32 \quad \text{---} \quad (7)$$

From equations (5) and (7) we get

$$\boxed{V_0 = 3.00 \text{ V}}$$

**3.94** Find  $I_o$  in the network in Fig. P3.94 using nodal analysis.


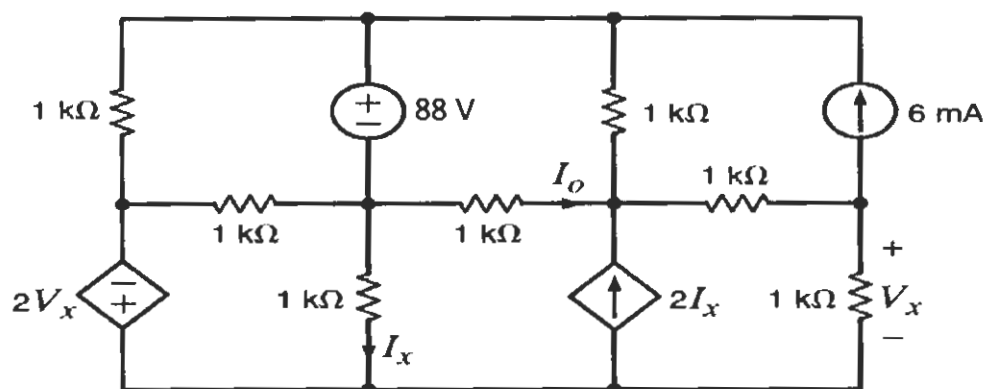


Figure P3.94

SOLUTION: 3.94

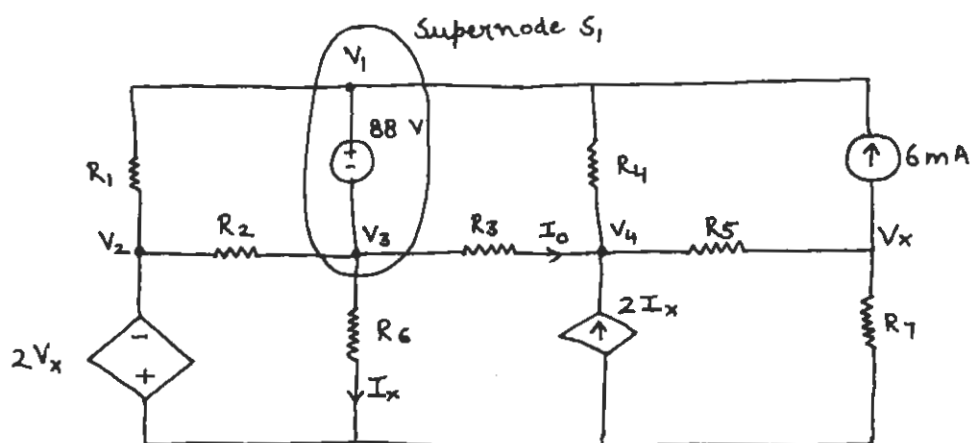

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = 1 \text{ k}\Omega$$

$$I_x = \frac{V_3}{R_6} \quad \text{--- (1)}$$

$$V_1 - V_3 = 88 \text{ V} \quad \text{--- (2)}$$

$$V_2 = -2V_x \Rightarrow V_x = -\frac{V_2}{2}$$

$$\text{KCL @ } S_1: \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_4}{R_4} - 6 \times 10^{-3} + \frac{V_3 - V_2}{R_2} + \frac{V_3}{R_6} + \frac{V_3 - V_4}{R_3} = 0$$

$$2V_1 - 2V_2 + 3V_3 - 2V_4 = 6 \quad \text{--- (3)}$$

$$\text{KCL @ } V_4: \frac{V_4 - V_3}{R_3} - 2I_x + \frac{V_4 - V_x}{R_5} + \frac{V_4 - V_1}{R_4} = 0$$



$$-2V_1 + V_2 - 6V_3 + 6V_4 = 0 \quad \text{---} \quad (4)$$

$$\text{KCL @ } V_x : \frac{V_x - V_4}{R_5} + \frac{V_x}{R_7} + 6 \times 10^{-3} = 0$$

$$V_2 + V_4 = 6 \quad \text{---} \quad (5)$$

Substituting equations (2) and (5) in (3), we get

$$2V_1 - 2V_2 + 3V_3 - 2V_4 = 6$$

$$V_3 = -31.6 \text{ V}$$

Substituting equations (2) and (5) in (4), we get

$$-2V_1 + V_2 - 6V_3 + 6V_4 = 0$$

$$V_4 = -16.56$$

$$\begin{aligned} I_0 &= \frac{V_3 - V_4}{R_3} \\ &= \frac{-31.6 + 16.56}{10^3} \end{aligned}$$

$$\boxed{I_0 = -15.04 \text{ mA}}$$

- 4.1 An op-amp based amplifier has supply voltages of  $\pm 5$  V and a gain of 10. Sketch the input waveform from the output waveform in Fig. P4.1. What are (a) the minimum and (b) the maximum values of the input voltage?

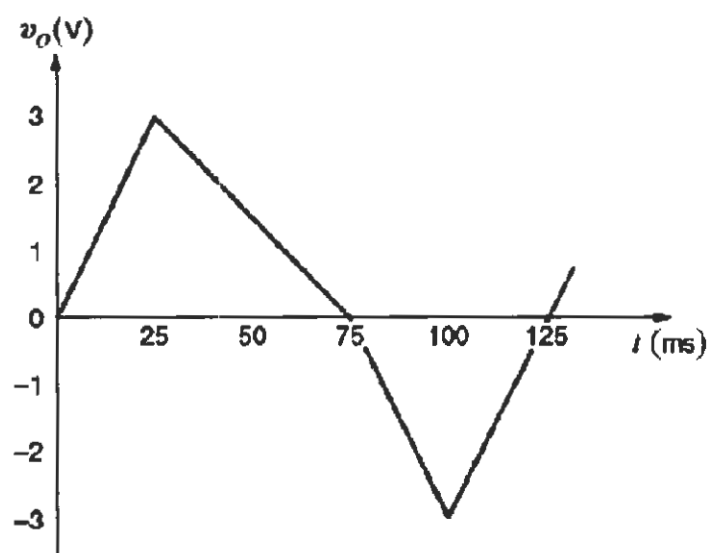


Figure P4.1


Solution: 4.1

$$G = \frac{V_o}{V_s} \quad \therefore V_s = \frac{V_o}{G}$$

$$\text{At } t = 25 \text{ ms}, V_o = 3 \text{ V}, V_s = 0.3 \text{ V}$$

$$\text{At } t = 100 \text{ ms}, V_o = -3 \text{ V}, V_s = -0.3 \text{ V}$$

The input waveform is drawn

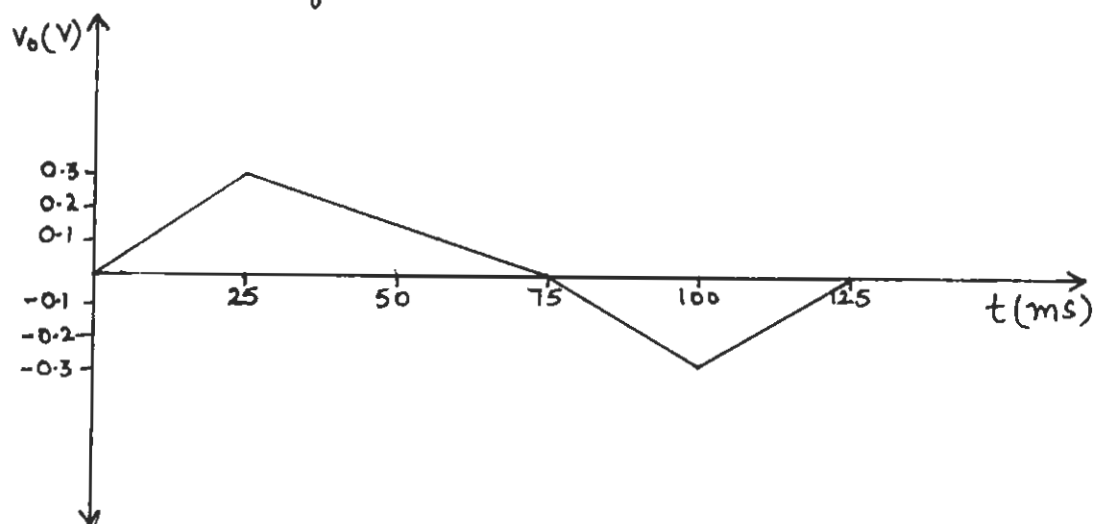

- (a) The minimum value of the input voltage is  $-0.3\text{ V}$ .
- (b) The maximum value of the input voltage is  $+0.3\text{ V}$ .

4.2 For an ideal op-amp, the voltage gain and input resistance are infinite while the output resistance is zero. What are the consequences for

- (a) the op-amp's input voltage?
- (b) the op-amp's input currents?
- (c) the op-amp's output current?

---

**SOLUTION:**


(a) With infinite gain, an input voltage of zero will produce a finite output voltage,  
 $V_{in} = 0V$  and, if  $V_{in}$  is a finite value  
the  $V_{out} = \pm\infty$ .

(b) No input current flows;

$$R_{in} = \infty$$

$$i_{in} = 0A$$

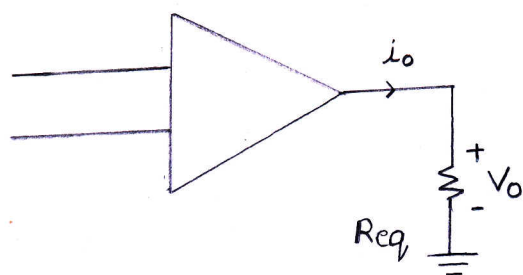(c) With  $R_{out} = 0\Omega$ , the output current is limited only by external circuit variables,



$$i = \frac{V_o}{R_{eq}}$$

4.3 Revisit your answers in Problem 4.2 under the following nonideal scenarios.

(a)  $R_{in} = \infty$ ,  $R_{out} = 0$ ,  $A_o \neq \infty$ .

(b)  $R_{in} = \infty$ ,  $R_{out} > 0$ ,  $A_o = \infty$ .

(c)  $R_{in} \neq \infty$ ,  $R_{out} = 0$ ,  $A_o = \infty$ .

**SOLUTION:**

(a)  $R_{in} = \infty$ ,  $R_{out} = 0$ ,  $A_o \neq \infty$

If  $R_{in} = \infty$ , then  $i_{in} = 0A$

If  $R_{out} = 0$ , then  $i_{out} = \frac{V_{out}}{R_L}$  ( $R_L = \text{external resistor}$ )

If  $A_o \neq \infty$ ,  $V_{in} \neq 0$

(b)  $R_{in} = \infty$ ,  $R_{out} > 0$ ,  $A_o = \infty$

If  $R_{in} = \infty$ ,  $i_{in} = 0A$

If  $A_o = \infty$ ,  $V_{in} = 0V$

If  $R_{out} > 0$ ,  $i_{out}$  will be limited by both  $R_{out}$  and  $R_L$

$$\Rightarrow i_{out} = \frac{V_{out}}{(R_L + R_{out})}$$

(c)  $R_{in} \neq \infty$ ,  $R_{out} = 0$ ,  $A_o = \infty$

If  $A_o = \infty$ ,  $V_{in} = 0V$

If  $R_{in} \neq \infty$ ,  $i_{in} = \frac{V_{in}}{R_{in}}$

$i_{in} = 0A$  due to the fact that  $V_{in} = 0V$   
If  $R_{out} = 0$ , then  $i_{out}$  is limited only by  $R_L$ .

$$\Rightarrow i_{out} = \frac{V_{out}}{R_L}$$

4.4 Revisit the exact analysis of the inverting configuration in Section 4.3.

- Find an expression for the gain if  $R_{in} = \infty$ ,  $R_{out} = 0$ ,  $A_o \neq \infty$ .
- Plot the ratio of the gain in (a) to the ideal gain versus  $A_o$  for  $1 \leq A_o \leq 1000$  for an ideal gain of  $-10$ .
- From your plot, does the actual gain approach the ideal value as  $A_o$  increases or decreases?
- From your plot, what is the minimum value of  $A_o$  if the actual gain is within 5% of the ideal case?

### SOLUTION:

(a) From section 4.3:

$$\frac{V_o}{V_s} = \frac{\frac{-R_2}{R_1}}{1 - \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in}} \right) \left( \frac{1}{R_2} + \frac{1}{R_o} \right) \frac{1}{\frac{1}{R_2} \left( \frac{1}{R_2} - \frac{A_o}{R_o} \right)}}$$

When  $R_{in} = \infty$ ,  $R_{out} = 0$ , and  $A_o \neq \infty$

$$\frac{1}{R_{in}} \ll \frac{1}{R_1} \quad \text{and} \quad \frac{1}{R_{in}} \ll \frac{1}{R_2}$$

$$\frac{1}{R_o} \gg \frac{1}{R_2}$$

$$\frac{V_o}{V_s} = \frac{\frac{-R_2}{R_1}}{1 + \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \frac{1}{R_o}}$$

$$\frac{V_o}{V_s} = \frac{\frac{-R_2}{R_1}}{1 + \frac{\frac{1}{R_2} \left( \frac{A_o}{R_o} \right)}{\frac{R_2 + R_1}{R_2 R_1}}}$$

$$\frac{V_o}{V_s} = \frac{\frac{-R_2}{R_1}}{1 + \left( \frac{R_1 + R_2}{R_1} \right) \frac{1}{A_o}}$$

$$\frac{V_o}{V_s} = \frac{\frac{-R_2}{R_1}}{1 + \frac{1}{A_o} \left( 1 + \frac{R_2}{R_1} \right)}$$

$$(b) \quad A_{ideal} = \frac{-R_2}{R_1}$$


$$A_{ideal} = -10$$

$$A_{actual} = \frac{V_o}{V_s}$$

$$A_{actual} = \frac{-10}{1 + \frac{1}{A_o} (1+10)}$$

$$A_{actual} = \frac{-10}{1 + \frac{11}{A_o}}$$

$$1 \leq A_o \leq 1000$$

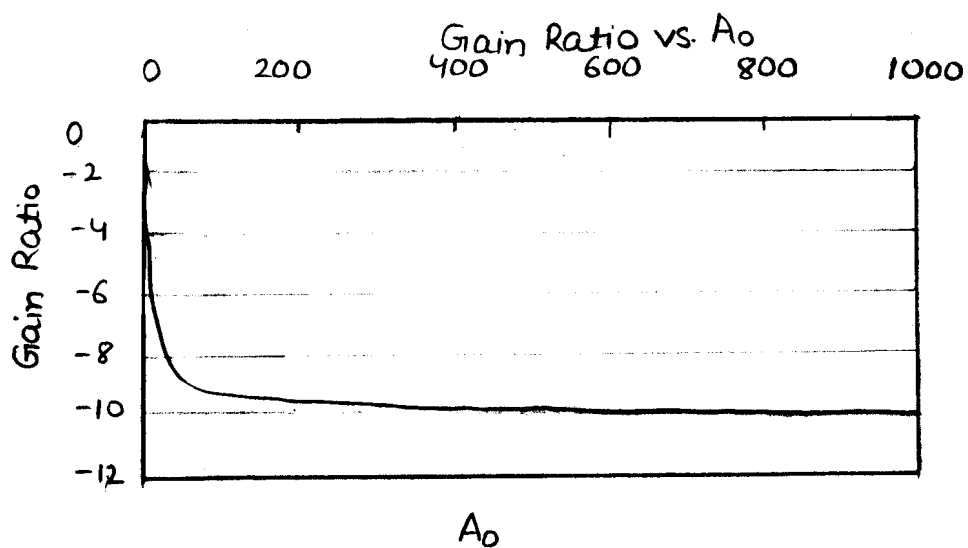

(c) When  $A_0$  increases,  $A_{\text{actual}}$  approaches  $A_{\text{ideal}}$

$$(d) \frac{A_{\text{actual}}}{A_{\text{ideal}}} = \frac{\frac{-10}{1 + \frac{11}{A_0}}}{-10}$$

$$\frac{\frac{-10}{1 + \frac{11}{A_0}}}{-10} \leq 0.95$$

$$A_0 \geq 209$$



- 4.5 Find an expression for the voltage gain of the inverting op-amp. If  $R_{in} \neq \infty$ ,  $R_{out} = 0$ ,  $A_0 \neq \infty$ . Find the gain if  $R_1 = 15\Omega$ ,  $R_2 = 10\Omega$ ,  $R_i = 24\Omega$ ,  $A_0 = 15$ .

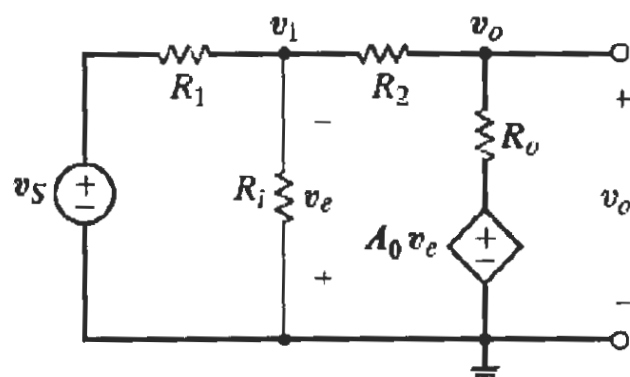


Figure P4.5

Solution: 4.5

Since  $R_{in} \neq \infty$  and  $A_0 \neq \infty$ , this is a non-ideal inverting op-amp.

$$\text{Therefore, } \frac{V_o}{V_s} = A_{\text{actual}} = \frac{-R_2/R_1}{1 - \frac{\left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2}\right) \left(\frac{1}{R_2} + \frac{1}{R_o}\right)}{\frac{1}{R_2} \left(\frac{1}{R_2} - \frac{A_0}{R_o}\right)}}$$

$$\text{For } R_o = 0, \frac{1}{R_o} \gg \frac{1}{R_2} \text{ and } \frac{A_0}{R_o} \gg \frac{1}{R_2}$$

$$\text{So, } A_{\text{actual}} = \frac{-R_2/R_1}{1 + \frac{\left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2}\right)}{A_0/R_2}}$$

$$A_{\text{actual}} = \frac{-R_2/R_1}{1 + \frac{1}{A_0} \left( \frac{R_2}{R_1} + \frac{R_2}{R_i} + 1 \right)} \quad \text{--- (1)}$$

$$R_1 = 15\Omega, R_2 = 10\Omega, R_i = 24\Omega, A_0 = 15$$

From (1), we get

$$A_{\text{actual}} = -0.585$$

- 4.6 An op-amp based amplifier has  $\pm 24$  V supplies and a gain of -80. Over what input range is the amplifier linear?  
Find (a) the minimum and (b) the maximum values.

---

Solution: 4.6

For linear operation

$$\frac{V_o}{V_{in}} = -80$$

Due to output limits,  $V_{o(max)} = 24$  V,  $V_{o(min)} = -24$  V

Therefore, input range of the amplifier over which the amplifier is linear is

$$-\frac{24}{80} \leq V_{in} \leq \frac{24}{80}$$

$$-0.300 \text{ V} \leq V_{in} \leq 0.300 \text{ V}$$

$$V_{in(min)} = -0.300 \text{ V}$$

$$V_{in(max)} = 0.300 \text{ V}$$

- 4.7 Determine the gain of the amplifier in Fig. P4.7. What is the value of  $I_o$ ?


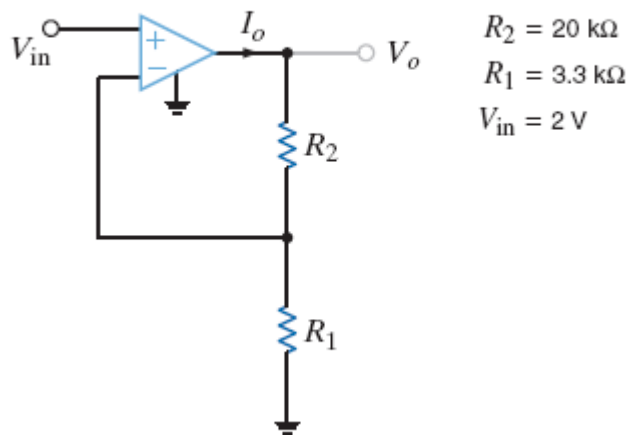


Figure P4.7

**SOLUTION:**

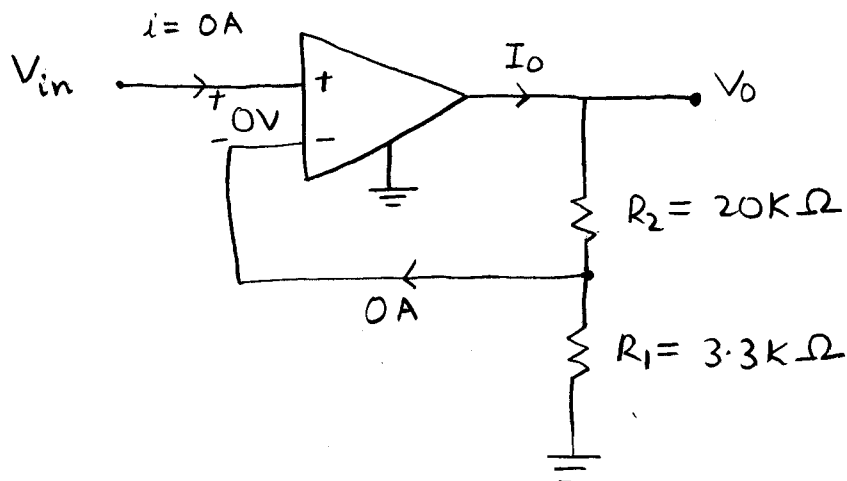

Non-inverting configuration:

$$\frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o}{V_{in}} = 1 + \frac{20 \times 10^3}{3.3 \times 10^3}$$

$$\frac{V_o}{V_{in}} = 7.06$$

$$\text{for } V_{in} = 2 \text{ V}$$

$$V_o = 7.06 (2)$$

$$V_o = 14.12 \text{ V}$$

$$I_o = \frac{V_o}{R_1 + R_2}$$

$$I_o = \frac{14.12}{3.3 \times 10^3 + 20 \times 10^3}$$

$$I_o = 606 \mu\text{A}$$

4.8 For the amplifier in Fig.P4.8, find (a) the gain (b)  $I_0$ .

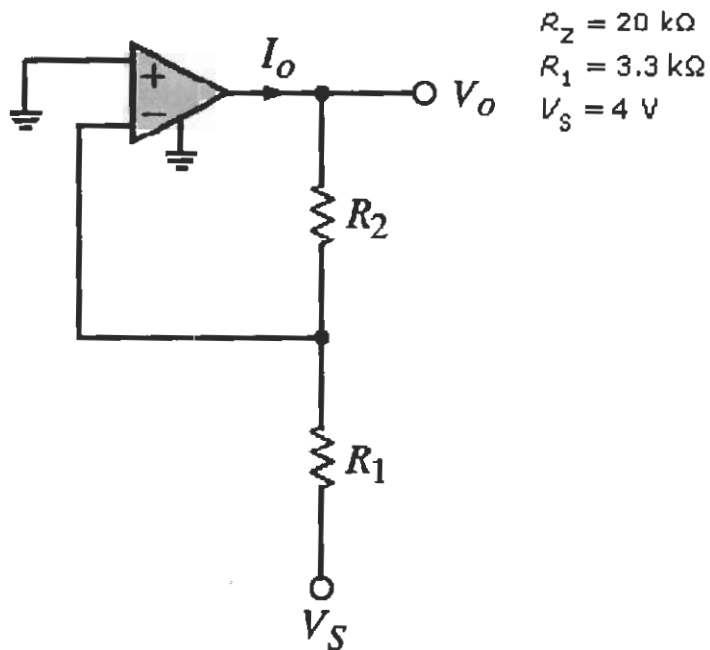


Figure P4.8

Solution: 4.8

(a) Basic inverting configuration,

$$G = \frac{V_o}{V_s} = -\frac{R_2}{R_1}$$

$$G = \frac{-20}{3.3} = -6.06$$

$$\boxed{G = -6.06}$$

(b)  $I_0 = \frac{V_o}{R_2}$

$$V_o = -6.06 V_s$$

$$V_o = -24.24 \text{ V}$$

$$I = \frac{-24.24}{20}$$

$$\boxed{I = -1.212 \text{ mA}}$$

- 4.9 Using the ideal op-amp assumptions, determine the values of  $V_o$  and  $I_1$  in Fig. P4.9.


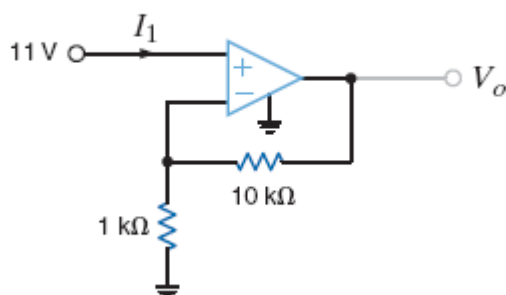


Figure P4.9

**SOLUTION:**

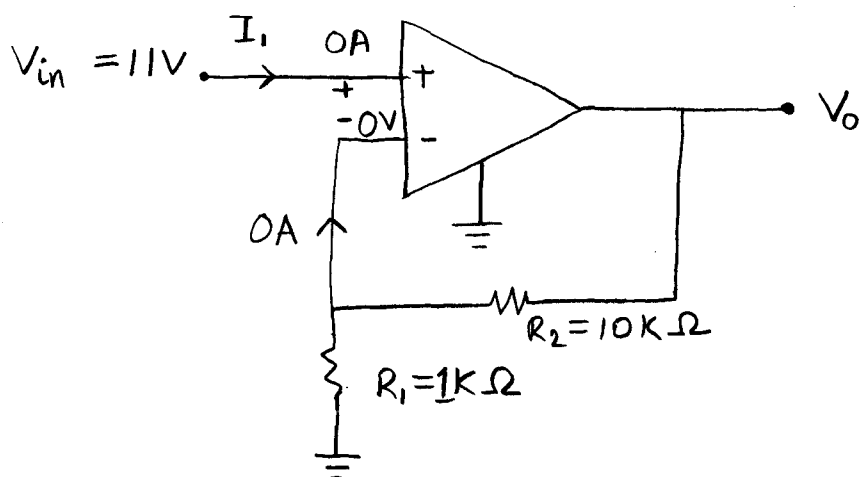

Non-inverting configuration:

$$\frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1} = 1 + \frac{10 \times 10^3}{1 \times 10^3}$$

$$\frac{V_o}{V_{in}} = 11$$

$$V_o = 11 V_{in} = 11(11)$$

$$V_o = 121 \text{ V}$$

$$\text{If } R_{in} = \infty, \text{ then } I_{in} = 0$$

$$I_1 = 0 \text{ A}$$

4.10 Using the ideal op-amp assumptions, determine (a)  $I_1$ , (b)  $I_2$  and (c)  $I_3$  in Fig. P4.10.

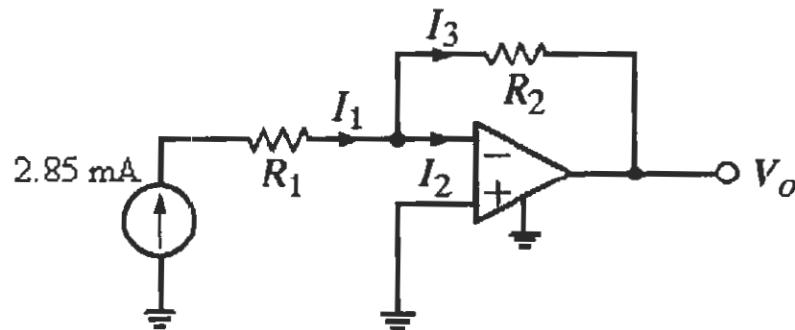


Figure P4.10

Solution: 4.10

For ideal op-amp assumption,

$$I_1 = 2.85 \text{ mA}$$

$$I_2 = 0$$

Applying KCL at the inverting terminal

$$I_3 = I_1 - I_2$$

$$I_3 = 2.85 \text{ mA}$$

- 4.11 In a useful application, the amplifier drives a load. The circuit in Fig. P4.11 models this scenario.
- Sketch the gain  $V_o/V_s$  for  $10\ \Omega \leq R_L \leq \infty$ .
  - Sketch  $I_o$  for  $10\ \Omega \leq R_L \leq \infty$  if  $V_s = 0.1\text{ V}$ .
  - Repeat (b) if  $V_s = 1.0\text{ V}$ .
  - What is the minimum value of  $R_L$  if  $|I_o|$  must be less than  $100\text{ mA}$  for  $|V_s| < 0.5\text{ V}$ ?
  - What is the current  $I_s$  if  $R_L$  is  $100\ \Omega$ ? Repeat for  $R_L = 10\text{ k}\Omega$ .

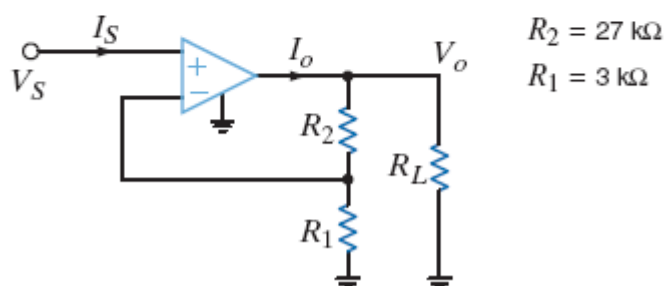
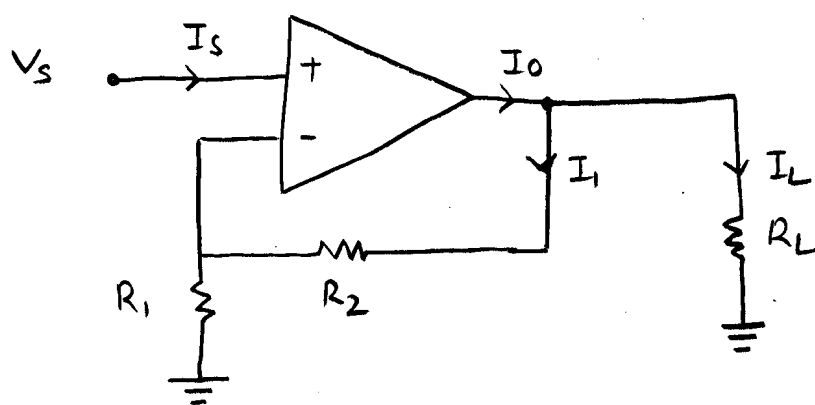


Figure P4.11


**SOLUTION:**

$$R_1 = 3\text{ k}\Omega, R_2 = 27\text{ k}\Omega$$

$$\frac{V_o}{V_s} = 1 + \frac{R_2}{R_1} = 1 + \frac{27 \times 10^3}{3 \times 10^3}$$

$$\frac{V_o}{V_s} = 10$$



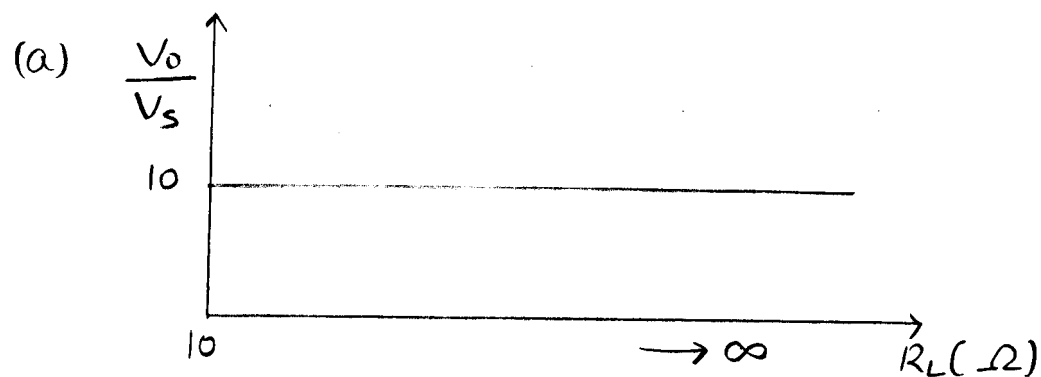


(b)  $V_s = 0.1\text{V}$  ,  $V_o = 10(0.1) = 1\text{V}$

$$I_o = I_L + I_1$$


$$I_o = \frac{V_o}{30 \times 10^3} + \frac{V_o}{R_L}$$
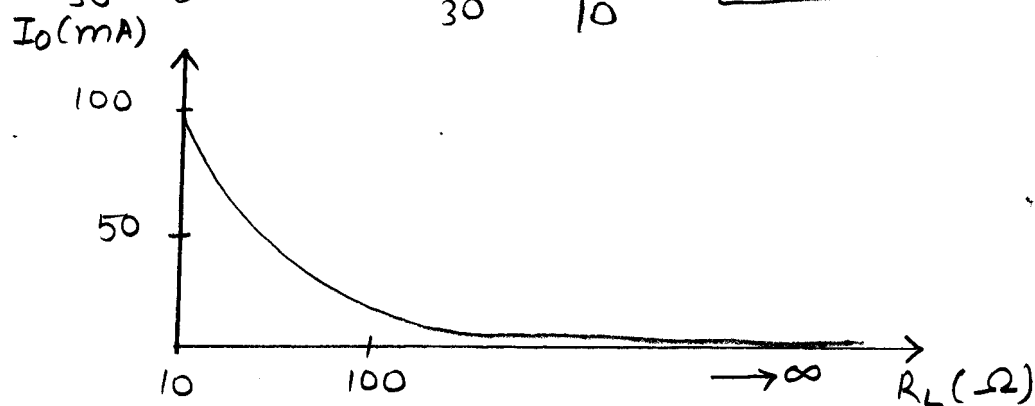
$$\frac{10^{-3}}{30} + \frac{1}{\infty} \leq I_o \leq \frac{10^{-3}}{30} + \frac{1}{10} \Rightarrow 33.3 \mu\text{A} \leq I_o \leq 10003 \mu\text{A}$$



$$(c) \quad V_s = 1V, \quad V_o = 10V$$
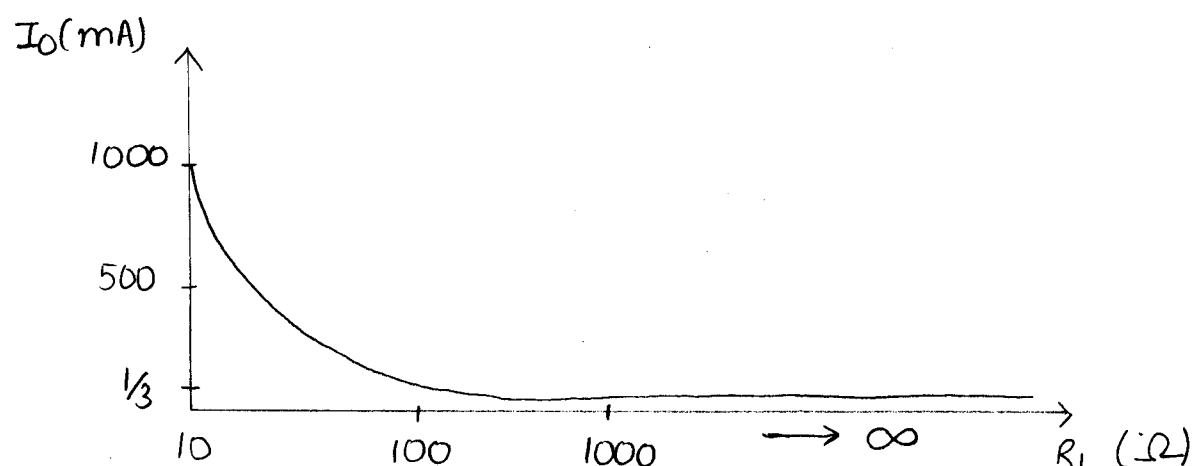
$$I_o = \frac{10}{30 \times 10^3} + \frac{10}{R_L}$$



$$(d) \quad V_s = 0.5V, \quad V_o = 5V$$

$$I_o = \frac{5}{30 \times 10^3} + \frac{5}{R_L}$$

$$\frac{5}{30 \times 10^3} + \frac{5}{R_L} < 100 \times 10^{-3}$$

$$R_L > 50.1 \Omega$$

(e)  $I_s$  flows into the non-inverting input of the op-amp.

$I_s = 0$ , the value of  $R_L$  doesn't matter.

4.12 Repeat Problem 4.11 for the circuit in Fig. P4.12.



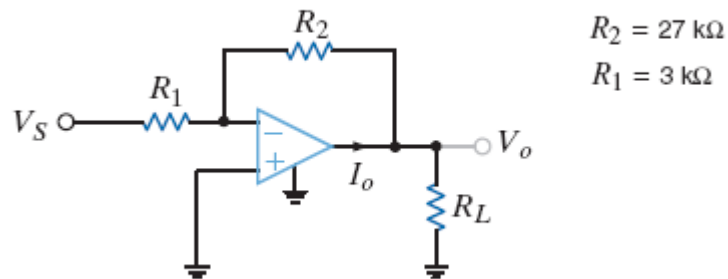


Figure P4.12

**SOLUTION:**

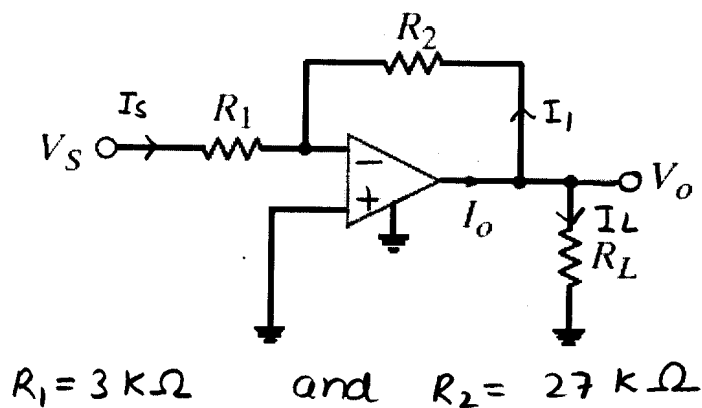

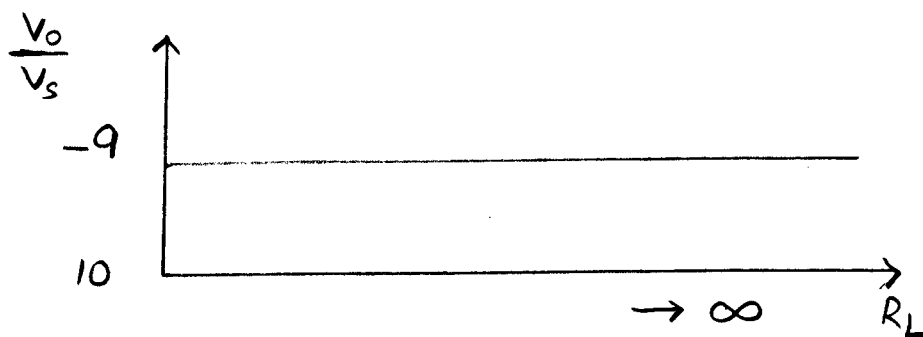
$$\begin{aligned}
 (a) \quad V_o &= -\frac{R_2}{R_1} V_S \\
 V_o &= -\frac{27\text{K}}{3\text{K}} V_S \\
 V_o &= -9V_S \\
 I_o &= I_1 + I_L \\
 I_o &= \frac{V_o}{R_2} + \frac{V_o}{R_L}
 \end{aligned}$$



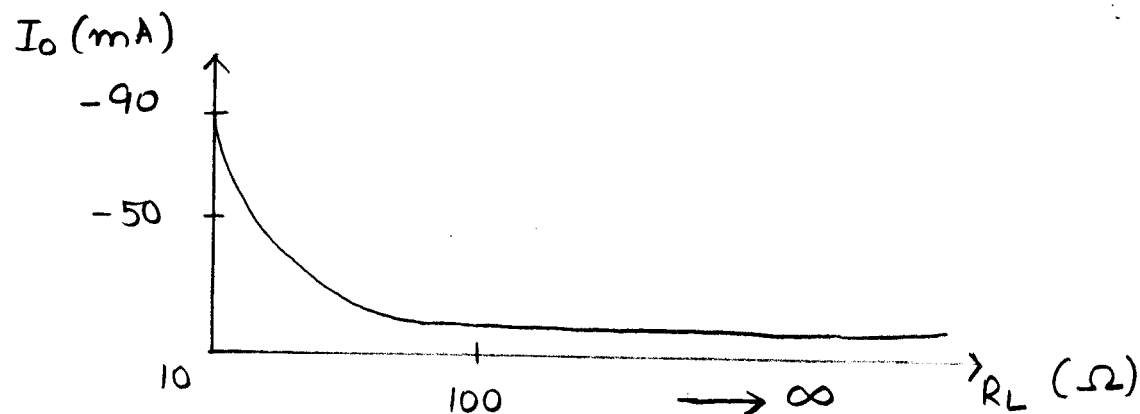
(b)  $V_s = 0.1 \text{ V}$  , and  $V_o = -0.9 \text{ V}$   

$$I_o = \frac{-0.9}{27 \times 10^3} - \frac{0.9}{R_L}$$



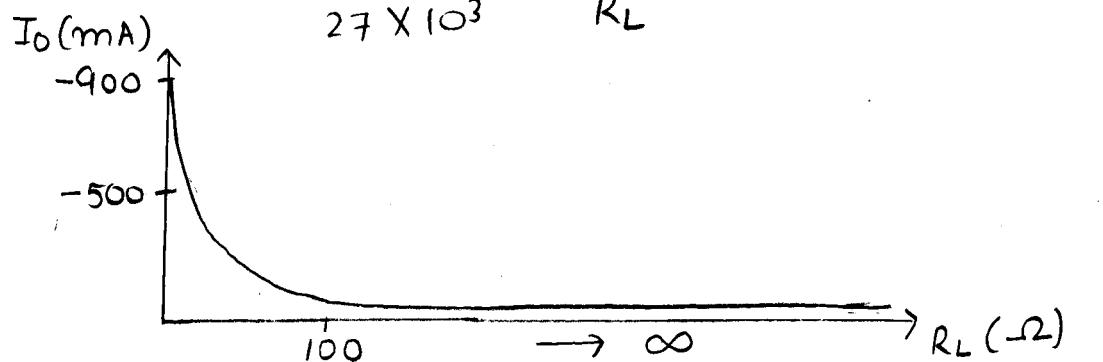(c)  $V_s = 1 \text{ V}$  , and  $V_o = -9 \text{ V}$   

$$I_o = \frac{-9}{27 \times 10^3} - \frac{9}{R_L}$$



$$(d) \quad I_0 = \frac{-9V_s}{27 \times 10^3} - \frac{9V_s}{R_L}$$

$$\text{at } V_s = 0.5 \text{ V}$$

$$|I_0| = \frac{-9(0.5)}{27 \times 10^3} - \frac{9(0.5)}{R_L}$$

$$|I_0| = \frac{4.5}{27 \times 10^3} + \frac{4.5}{R_L} < 100 \text{ mA}$$

$$R_L > 45.1 \, \Omega$$

$$(e) \quad I_s = \frac{V_s}{R_1}$$

$$I_s = \frac{V_s}{3000}, \quad I_s \text{ is independent of } R_L$$

$$\text{at } V_s = 0.5 \text{ V}$$

$$I_s = \frac{0.5}{3000}$$

$$I_s = 167 \, \mu\text{A}$$

- 4.13 The op-amp in the amplifier in Fig. P4.13 operates with  $\pm 15$  V supplies and can output no more than 200 mA. What is the maximum gain allowable for the amplifier if the maximum value of  $V_s$  is 1 V?

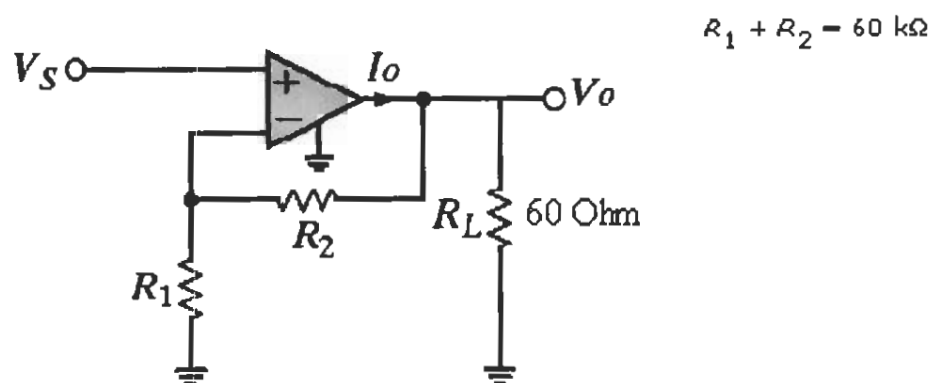


Figure P4.13

Solution: 4.13

Basic non-inverting configuration

$$A_v = \frac{V_o}{V_s} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1} = \frac{60 \times 10^3}{R_1} = \frac{6 \times 10^4}{R_1}$$

$$|V_o| = |V_s| \left( \frac{6 \times 10^4}{R_1} \right) \leq 15 \quad [\text{For linear operation}]$$

$$V_{s_{\max}} = 1 \text{ V}$$

$$\text{For } V_{s_{\max}} = 1 \text{ V, } V_o = \frac{6 \times 10^4}{R_1}$$

$$\begin{aligned} \text{Also, } I_o &= \frac{V_o}{R_1 + R_2} + \frac{V_o}{R_L} \\ &= \frac{6 \times 10^4}{R_1 \times 60 \times 10^3} + \frac{6 \times 10^4}{R_1 \times 60} \\ &= \frac{1001}{R_1} \end{aligned}$$

$$\therefore \frac{1001}{R_1} \leq 200 \text{ mA}$$

$$R_1 \geq \frac{1001}{200 \times 10^{-3}}$$

$$\therefore R_1 \geq 5005 \Omega \text{ and } R_2 \leq 54995 \Omega$$

$$A_{v_{\max}} = 1 + \frac{R_{2_{\max}}}{R_{1_{\min}}} = 1 + 10.988$$

$$\boxed{A_{v_{\max}} = 12}$$

4.14 For the amplifier in Fig. P4.14, the maximum value of  $V_S$  is 2 V and the op-amp can deliver no more than 100 mA.

- If  $\pm 10$  V supplies are used, what is the maximum allowable value of  $R_2$ ?
- Repeat for  $\pm 3$  V supplies.
- Discuss the impact of the supplies on the maximum allowable gain.


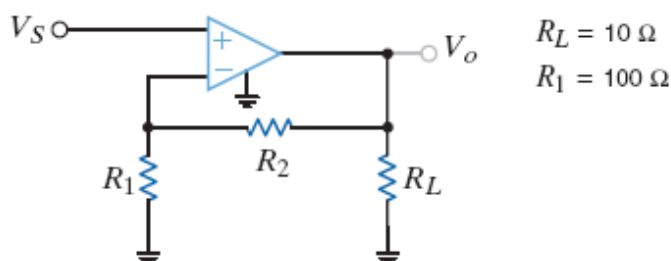


Figure P4.14

**SOLUTION:**

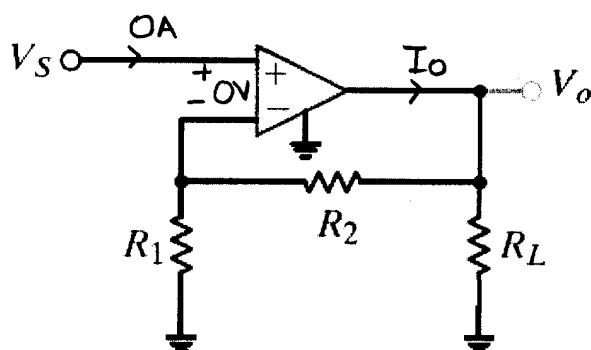

$$R_1 = 100 \text{ k}\Omega$$

$$R_L = 10 \text{ k}\Omega$$

(a) Non-inverting op-amp:

$$V_O = \left(1 + \frac{R_2}{R_1}\right) V_S$$

$$I_O = \frac{V_O}{R_L \parallel (R_1 + R_2)}$$

$$\text{for } V_S = 2 \text{ V}$$

$$V_O = \left(1 + \frac{R_2}{R_1}\right) (2)$$

$$\left(1 + \frac{R_2}{R_1}\right) 2 \leq 10$$

$$R_2 \leq 400 \text{ k}\Omega$$

$$I_o = \frac{10}{10 \times 10^3 \parallel (100 \times 10^3 + 400 \times 10^3)}$$

$$I_o = 1.02 \text{ mA} \leq 100 \text{ mA}$$

$R_2 = 400 \text{ k}\Omega$  satisfies both current and voltage limit.

(b)  $V_o = \left(1 + \frac{R_2}{R_1}\right) (2)$

$$\left(1 + \frac{R_2}{R_1}\right) (2) \leq 3$$

$$R_2 \leq 50 \text{ k}\Omega$$

$$I_o = \frac{3}{10 \times 10^3 \parallel (100 \times 10^3 + 50 \times 10^3)}$$

$$I_o = 320 \mu\text{A}$$

- (c) For any value of  $V_s$ ,  $A_{v\max}$  is a linear function of the supply voltage. This relationship exists until the  $I_o$  limit is an issue. The limit on  $I_o$  is  $100 \text{ mA}$ .



4.15 For the circuit in Fig. P4.15, find  $V_o$ , if  $V_1 = 3\text{ V}$  and  $V_2 = 9\text{ V}$ .


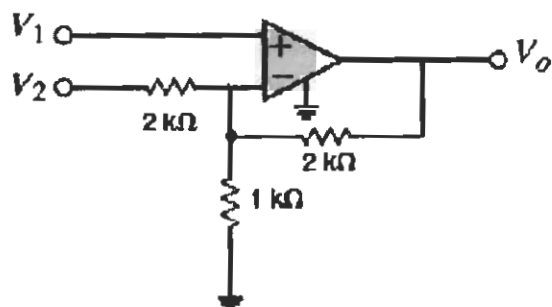


Figure P4.15

Solution: 4.15

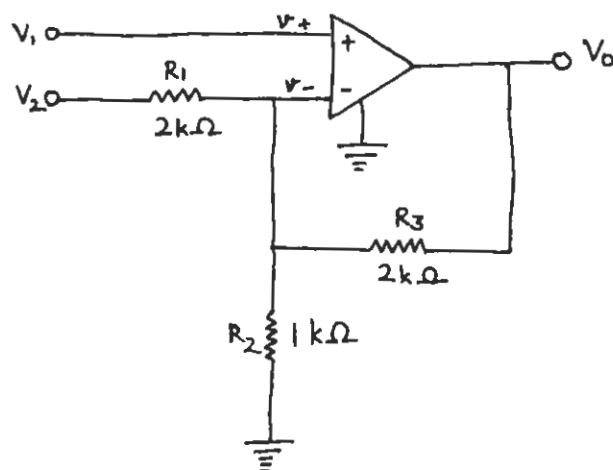

$$v_+ = v_- = V_1$$

$$\text{KCL at } v_- \text{ input: } \frac{V_2 - V_1}{R_1} = \frac{V_1}{R_2} + \frac{V_1 - V_o}{R_3}$$

$$\Rightarrow V_o = V_1 \left( 1 + \frac{R_3}{R_2} + \frac{R_3}{R_1} \right) - V_2 \left( \frac{R_3}{R_1} \right)$$

$$R_1 = 2\text{ k}\Omega, R_2 = 1\text{ k}\Omega, R_3 = 2\text{ k}\Omega, V_1 = 3\text{ V}, V_2 = 9\text{ V}$$

$$\therefore V_o = 4V_1 - V_2$$

$$\boxed{V_o = 3\text{ V}}$$

4.16 Find  $V_o$  in the circuit in Fig. P4.16 assuming the op-amp is ideal.


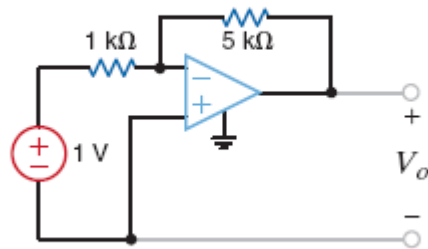


Figure P4.16

**SOLUTION:**

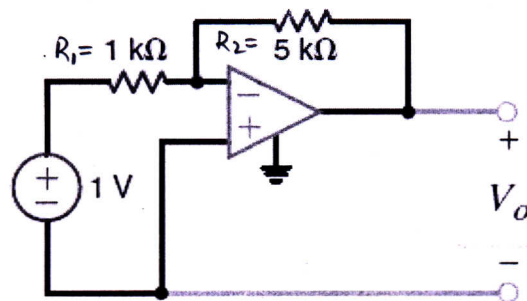

Inverting op-amp configuration:

$$V_o = \left( \frac{-R_2}{R_1} \right) V_s$$

$$V_o = \left( \frac{-5000}{1000} \right) (1)$$

$$V_o = -5V$$

- 4.17 The network in Fig. P4.17 is a current-to-voltage converter or transconductance amplifier. Find  $v_o/i_s$  for this network.


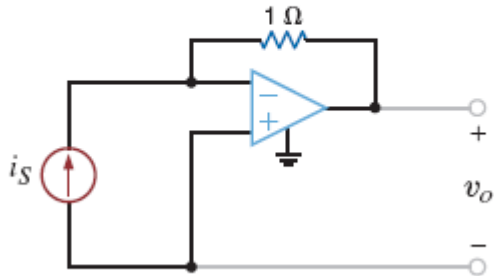


Figure P4.17

**SOLUTION:**

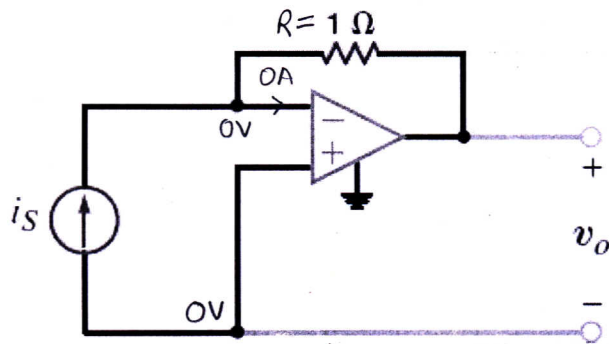

$$\text{KCL at } V^- : \quad i_s = 0 + \frac{0 - V_o}{R}$$

$$i_s = -\frac{V_o}{R}$$

$$\frac{V_o}{i_s} = -R$$

$$\frac{V_o}{i_s} = -1$$

4.18 Calculate the transfer function  $i_o/v_1$  for the network shown in Fig. P4.18.


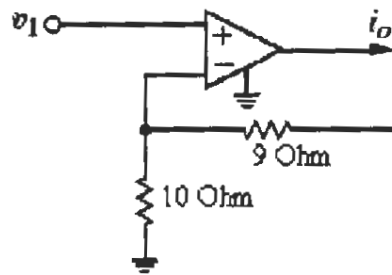


Figure P4.18

Solution: 4.18

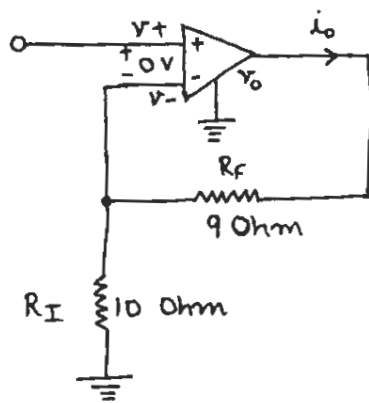

$$v_+ = v_- = v_1$$

KCL at  $v_-$  input

$$\frac{v_1}{R_I} = \frac{v_o - v_1}{R_F}$$

$$\frac{v_o}{v_1} \left( 1 + \frac{R_F}{R_I} \right) = \frac{R_I + R_F}{R_I}$$

$$v_1 = \frac{v_o}{R_I + R_F} \times R_I$$

$$\frac{v_o}{R_I + R_F} = \frac{v_1}{R_I}$$

$$i_o = \frac{v_o}{R_I + R_F} = \frac{v_1}{R_I}$$

$\therefore$  Transfer function  $\frac{i_o}{v_1} = \frac{1}{R_I}$

$$\boxed{\frac{i_o}{v_1} = 0.100 \text{ S}}$$

4.19 Determine the relationship between  $v_1$  and  $i_o$  in the circuit shown in Fig. P4.19. Find  $i_o/v_1$ .


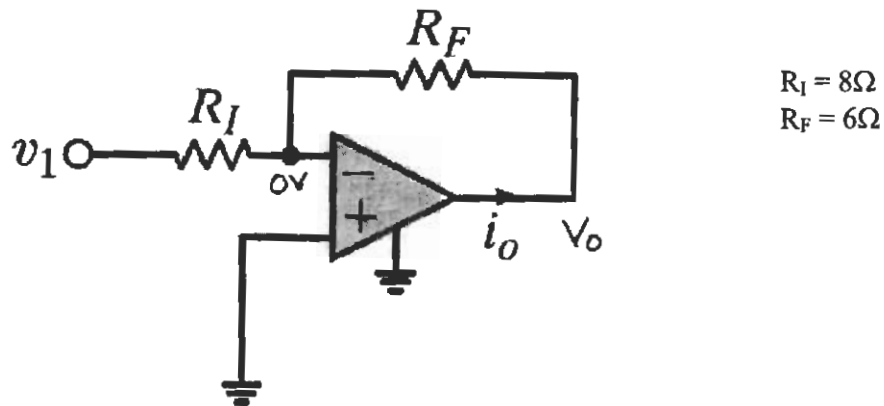


Figure P4.19

Solution: 4.19

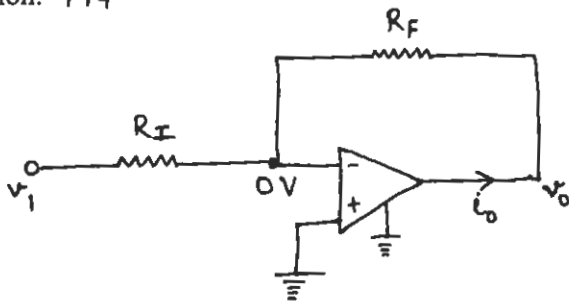

Basic inverting configuration:

$$\frac{v_o}{v_1} = -\frac{R_F}{R_I}$$

$$i_o = \frac{v_o}{R_F} = -\frac{v_1}{R_I}$$

$$\frac{i_o}{v_1} = -\frac{1}{R_I}$$

$$R_I = 8\Omega, \quad \frac{i_o}{v_1} = -\frac{1}{8}$$

$$\boxed{\frac{i_o}{v_1} = -0.125 \text{ S}}$$

4.20 Find  $V_o$  in the network in Fig. P4.20.


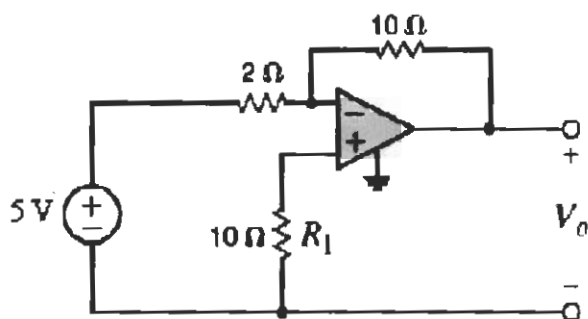


Figure P4.20

Solution: 4.20

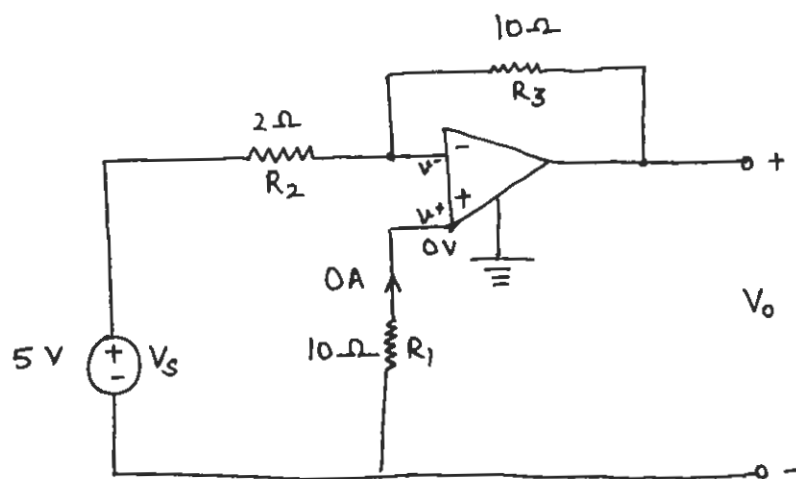

$I_{in} = 0$ ,  $v_+ = 0$  for ideal op-amp.

$\therefore$  Voltage across  $R_1$  is 0.

Result is a basic inverting configuration.

$$\frac{V_o}{V_s} = -\frac{R_3}{R_2}$$

$$\Rightarrow V_o = -5 \left( \frac{10}{2} \right)$$

$$= -25 \text{ V}$$

$$\boxed{V_o = -25 \text{ V}}$$

4.21 Determine the value of  $v_o$  in the network in Fig. P4.21.


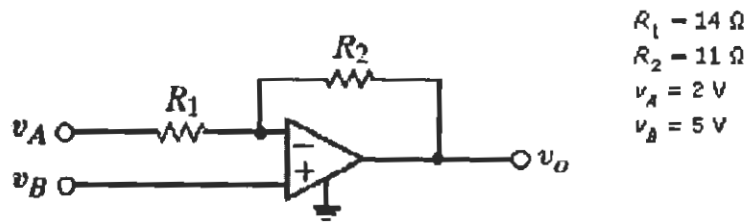


Figure P4.21

Solution: 4.21

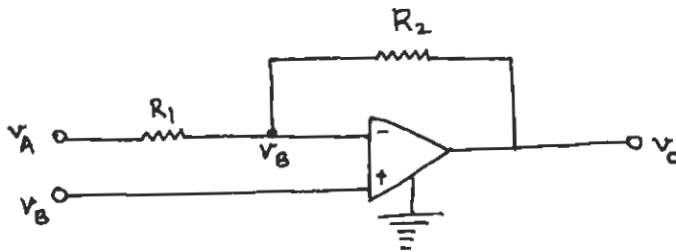

KCL at  $v_-$  node

$$\frac{v_A - v_-}{R_1} + \frac{v_o - v_-}{R_2} = 0$$

$$\frac{2 - 5}{14} + \frac{v_o - 5}{11} = 0$$

$$v_o = 7.36 \, \text{V}$$

4.22 Show that the output of the circuit in Fig. P4.22 is

$$V_o = \left[ 1 + \frac{R_2}{R_1} \right] V_1 - kV_2$$

Find  $k$ , if  $R_1 = 5 \, \Omega$ ,  $R_2 = 46 \, \Omega$ ,  $R_3 = 6 \, \Omega$ ,  $R_4 = 12 \, \Omega$ .


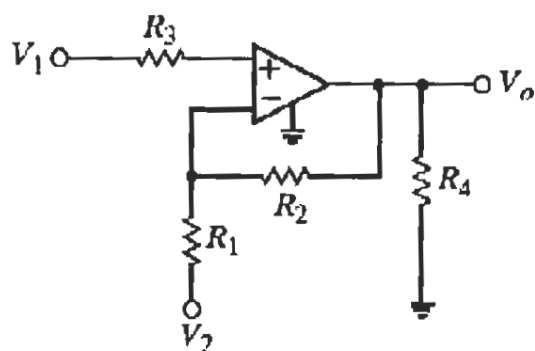


Figure P4.22

Solution: 4.22

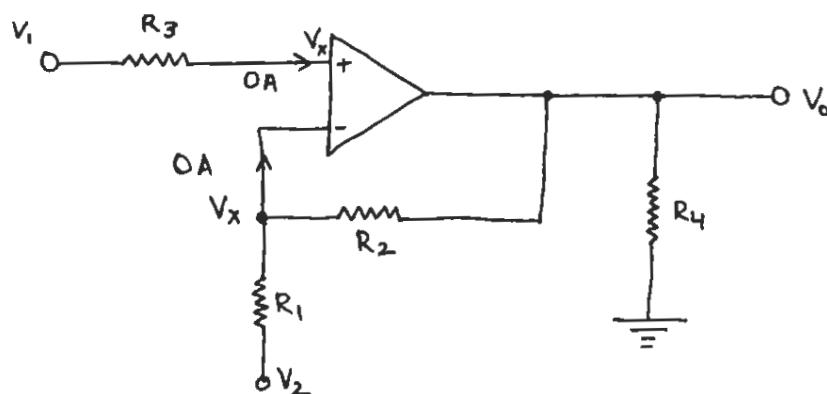

$$\text{KCL at } v_+ \text{ input: } \frac{V_1 - V_x}{R_3} = 0 \Rightarrow V_1 = V_x$$

$$\text{KCL at } v_- \text{ input: } \frac{V_2 - V_x}{R_1} + \frac{V_o - V_x}{R_2} = 0$$

$$V_o = V_x \left( 1 + \frac{R_2}{R_1} \right) - V_2 \left( \frac{R_2}{R_1} \right)$$

$$\therefore V_o = \left[ 1 + \frac{R_2}{R_1} \right] V_1 - kV_2, \text{ where } k = \frac{R_2}{R_1}$$

$$k = \frac{R_2}{R_1} = 9.2$$

$$\boxed{k = 9.2}$$



4.23 Find  $V_o$  in the network in Fig. P4.23.


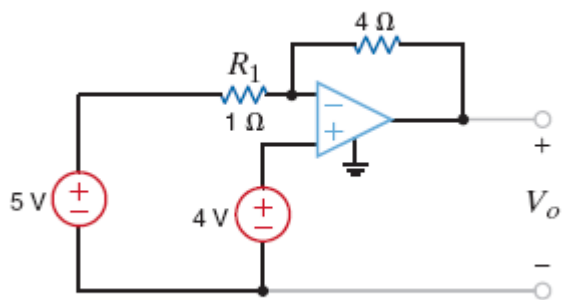


Figure P4.23

**SOLUTION:**

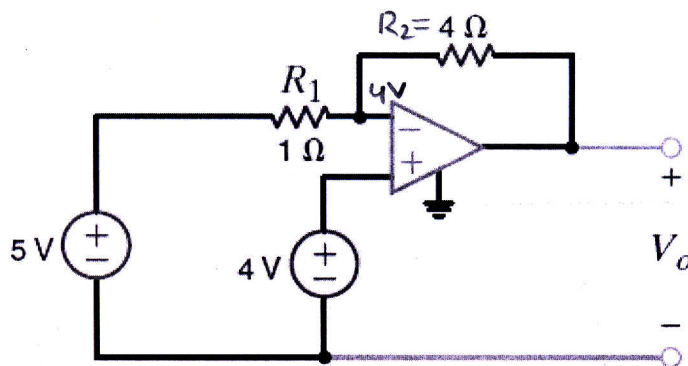

$$\text{KCL at } V_- : \frac{5-4}{R_1} = \frac{4-V_o}{R_2}$$

$$V_o = 4 - \frac{R_2}{R_1}(1)$$

$$V_o = 4 - \frac{4}{1}(1)$$

$$V_o = 0V$$

4.24 Find the voltage gain of the op-amp circuit shown in Fig. P4.24.


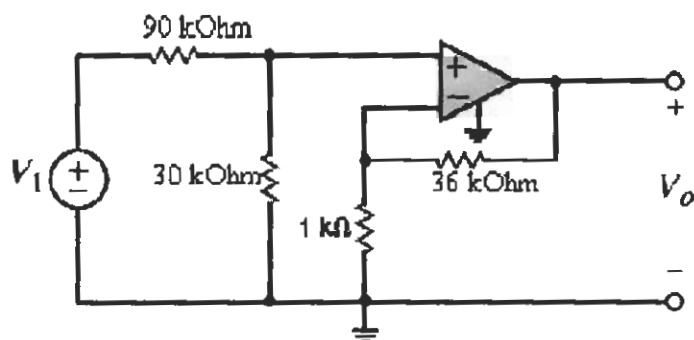


Figure P4.24

Solution: 4.24

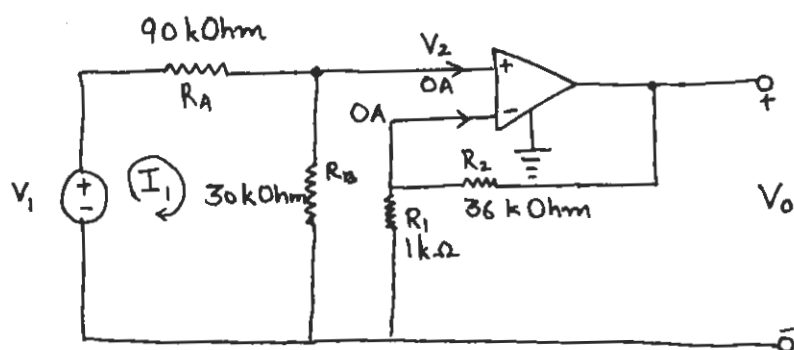

Two step solution : 1) Find  $V_2/V_1$   
2) Find  $V_0/V_2$

1) Loop analysis :  $V_1 = I_1 R_A + I_1 R_B$

$$V_2 = I_1 R_B \Rightarrow I_1 = V_2/R_B$$

$$\frac{V_2}{V_1} = \frac{R_B}{R_A + R_B} = 0.25 \quad \frac{V_2}{V_1} = 0.25$$

2) op-amp is in basic non-inverting configuration

$$\frac{V_0}{V_2} = 1 + \frac{R_2}{R_1} = 37$$

Overall gain is  $A = \frac{V_0}{V_1} = \left(\frac{V_2}{V_1}\right) \left(\frac{V_0}{V_2}\right)$

$$\boxed{A = 9.25}$$

4.25 For the circuit in Fig. P4.25 find the value of  $R_1$  that produces a voltage gain of 10.


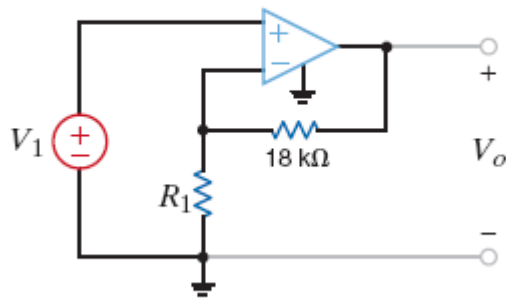


Figure P4.25

**SOLUTION:**

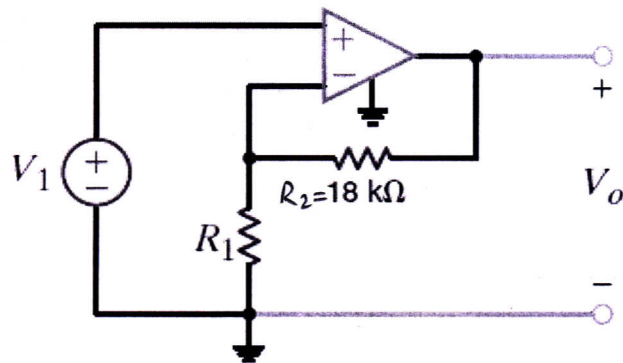

Non-inverting op-amp:

$$\frac{V_o}{V_1} = 1 + \frac{R_2}{R_1}$$

$$10 = 1 + \frac{18 \times 10^3}{R_1}$$

$$R_1 = 2 \text{ k}\Omega$$

4.26 Determine the relationship between  $v_o$  and  $v_{in}$  in the circuit in Fig. P4.26.


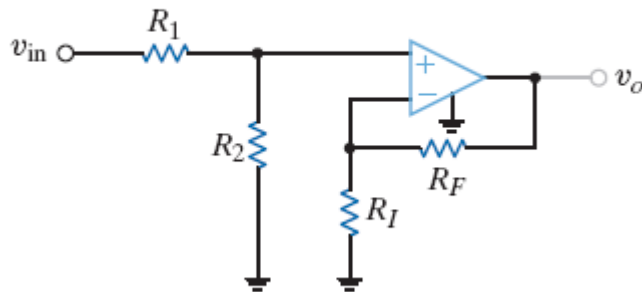


Figure P4.26

**SOLUTION:**

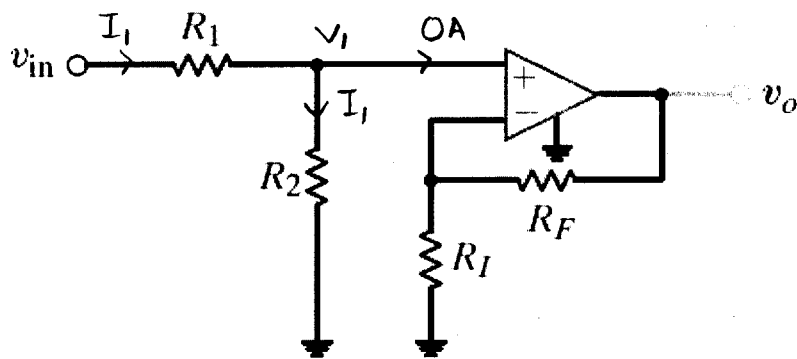

$$\begin{aligned} \text{KVL: } v_{in} &= I_1 R_1 + I_1 R_2 \\ v_1 &= I_1 R_2 \\ I_1 &= \frac{v_1}{R_2} \end{aligned}$$

$$v_{in} = \left( \frac{v_1}{R_2} \right) (R_1) + \left( \frac{v_1}{R_2} \right) R_2$$

$$v_{in} = v_1 + \frac{R_1}{R_2} v_1$$

$$\frac{v_1}{v_{in}} = \frac{R_2}{R_1 + R_2}$$

Non-inverting op-amp :

$$\frac{V_o}{V_i} = 1 + \frac{R_F}{R_I}$$

Overall gain:

$$\frac{V_o}{V_{in}} = \left( \frac{V_o}{V_i} \right) \left( \frac{V_i}{V_{in}} \right)$$

$$\frac{V_o}{V_{in}} = \left( 1 + \frac{R_F}{R_I} \right) \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{V_o}{V_{in}} = \left( \frac{R_I + R_F}{R_I} \right) \left( \frac{R_2}{R_1 + R_2} \right)$$

4.27 In the network in the Fig. P4.27 determine the value of  $V_o$ .


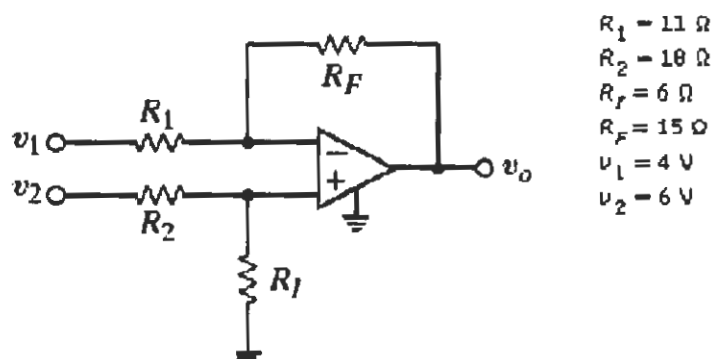


Figure P4.27

Solution: 4.27

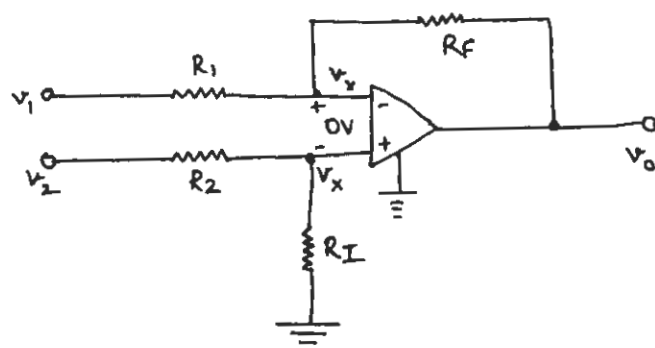

$$\text{KCL at } v_+ \text{ input: } \frac{v_2 - v_x}{R_2} = \frac{v_x}{R_I} \Rightarrow v_x = \frac{R_I}{R_I + R_2} v_2 \quad \text{--- (1)}$$

$$\text{KCL at } v_- \text{ input: } \frac{v_1 - v_x}{R_1} = \frac{v_x - v_o}{R_F}$$

$$\Rightarrow v_o = v_x \left( 1 + \frac{R_F}{R_I} \right) - \frac{R_F}{R_I} v_1 \quad \text{--- (2)}$$

Substituting the value of  $v_x$  from equation (1) in (2), we get

$$v_o = v_2 \left( \frac{R_I}{R_I + R_2} \right) \left( \frac{R_I + R_F}{R_I} \right) - \frac{R_F}{R_I} v_1$$

$$\boxed{V_o = -1.91 \, \text{V}}$$

4.28 Find  $V_o$  in the circuit in Fig. P4.28.


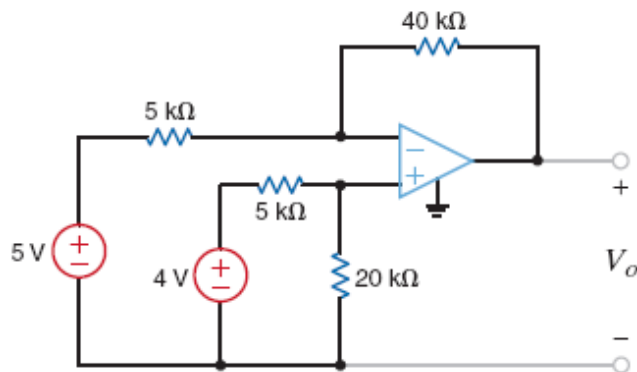


Figure P4.28

**SOLUTION:**

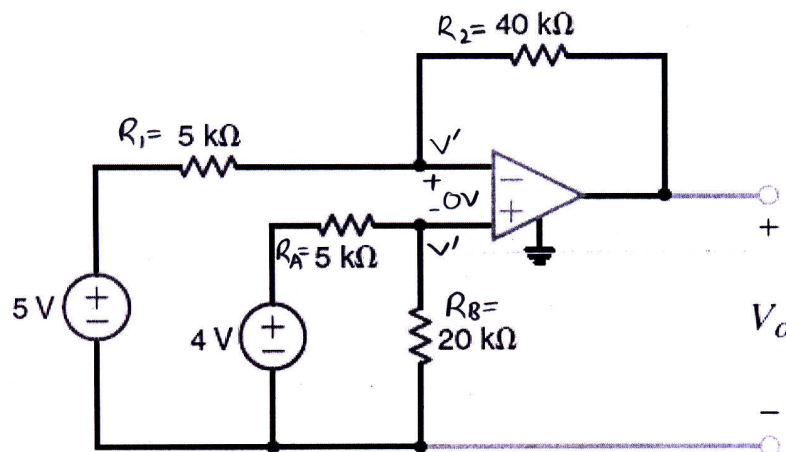

$$\text{KCL at } V_- : \frac{5 - V'}{R_1} = \frac{V' - V_o}{R_2}$$

$$\frac{V'}{R_2} + \frac{V'}{R_1} = \frac{5}{R_1} + \frac{V_o}{R_2}$$

$$V' \left( \frac{R_1 + R_2}{R_1 R_2} \right) = \frac{5 R_2 + R_1 V_o}{R_1 R_2}$$

$$V' = 5 \left( \frac{R_2}{R_1 + R_2} \right) + V_o \left( \frac{R_1}{R_1 + R_2} \right)$$

$$\text{KCL at } V_t : \frac{4 - V'}{R_A} = \frac{V'}{R_B}$$

$$V' = \frac{4R_B}{R_A + R_B}$$

$$5 \left( \frac{R_2}{R_1 + R_2} \right) + V_0 \left( \frac{R_1}{R_1 + R_2} \right) = \frac{4R_B}{R_A + R_B}$$

$$V_0 = \left( \frac{4R_B}{R_A + R_B} - \frac{5R_2}{R_1 + R_2} \right) \left( \frac{R_1 + R_2}{R_1} \right)$$

$$V_0 = -11.2 \text{ V}$$



4.29 Find  $V_o$  in the circuit in Fig. P4.29.


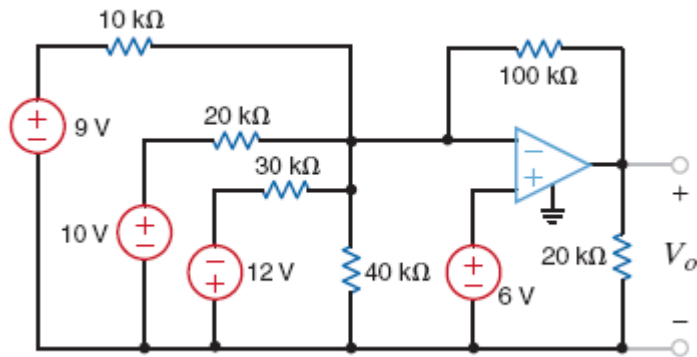


Figure P4.29

**SOLUTION:**

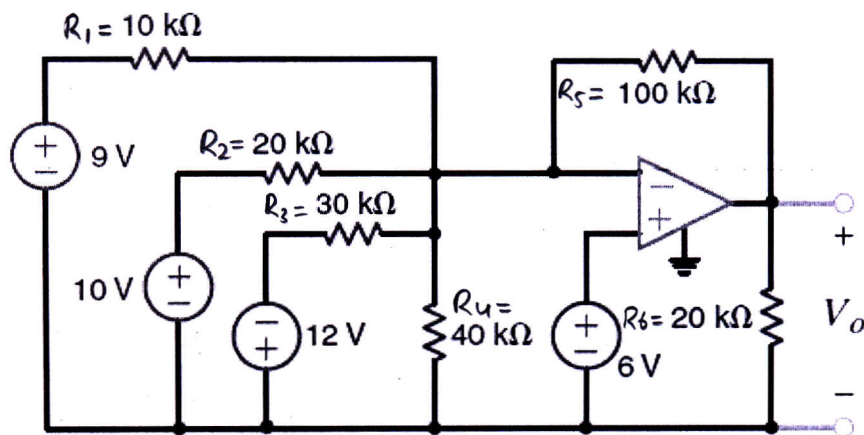


$$\text{KCL at } V_- : \frac{9-6}{R_1} + \frac{10-6}{R_2} + \frac{-12-6}{R_3} = \frac{6}{R_4} + \frac{6-V_o}{R_5}$$

$$\frac{3}{R_1} + \frac{4}{R_2} - \frac{18}{R_3} - \frac{6}{R_4} - \frac{6}{R_5} = -\frac{V_o}{R_5}$$


$$V_o = 31\text{V}$$

**4.30** Determine the value of the output voltage,  $v_o$ , of the inverting summer circuit in the Fig. P4.30.

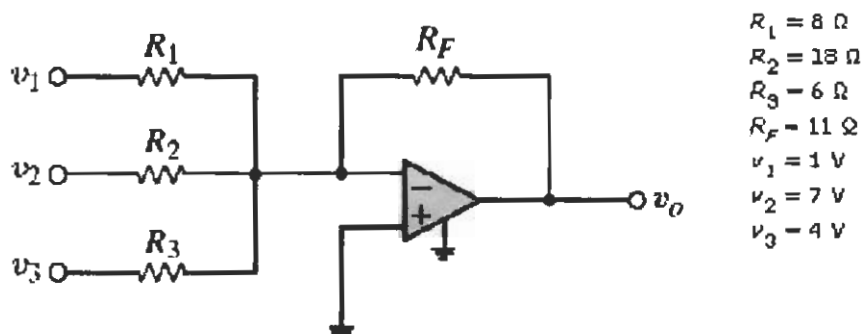

**Figure P4.30**

Solution: 4.30

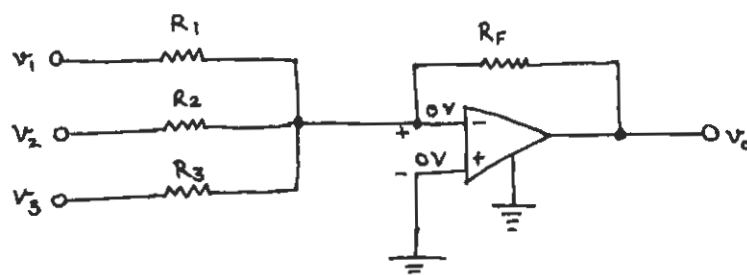

$$\text{KCL at } v_- \text{ input: } \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3} = \frac{0 - v_o}{R_F}$$

$$v_o = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3$$

$$\Rightarrow \boxed{v_o = -13.0 \, \text{V}}$$

4.31 Determine the value of the output voltage,  $V_o$ , of the noninverting averaging circuit shown in the Fig. P4.31.


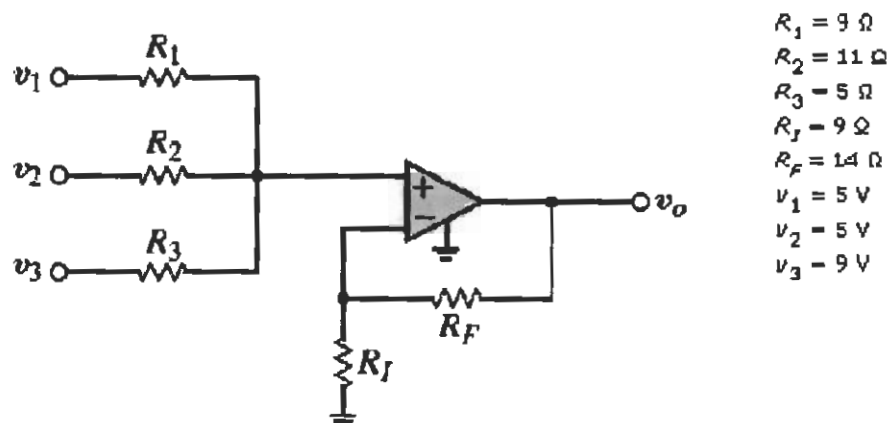


Figure P4.31

Solution: 4.31

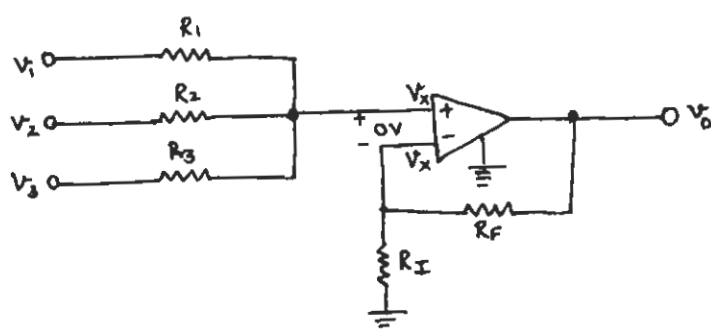

$$\text{KCL at } v_{+} \text{ input} = \frac{v_1 - v_x}{R_1} + \frac{v_2 - v_x}{R_2} + \frac{v_3 - v_x}{R_3} = 0 \quad \text{--- (1)}$$

$$\text{KCL at } v_{-} \text{ input} = \frac{v_o - v_x}{R_F} = \frac{v_x}{R_I} \Rightarrow v_x = v_o \left( \frac{R_I}{R_I + R_F} \right) \quad \text{--- (2)}$$

Substituting equation (2) in (1), we get

$$v_o = \left( \frac{R_I + R_F}{R_I} \right) \left[ \frac{R_2 R_3 v_1 + R_1 R_3 v_2 + R_1 R_2 v_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right]$$

$$\Rightarrow v_o = 17.863 \text{ V}$$

$$\boxed{v_o = 17.9 \text{ V}}$$

- 4.32 Find the input/output relationship for the current amplifier shown in Fig. P4.32.


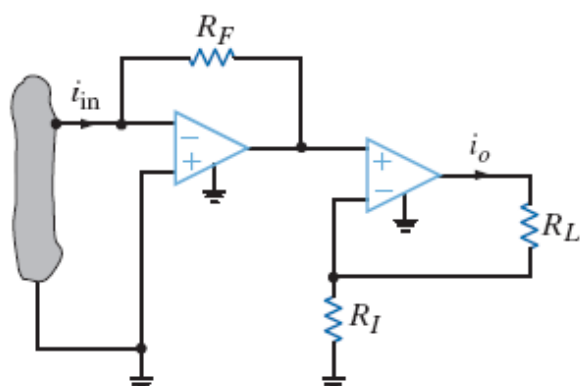


Figure P4.32

**SOLUTION:**

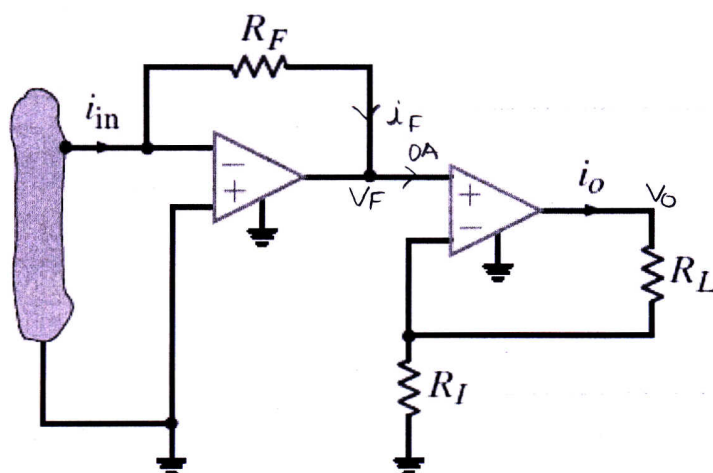

KCL at  $V_-$  of the op-amp on the left side :

$$i_{in} = \frac{0 - V_F}{R_F}$$

$$V_F = -i_{in} R_F$$

op-amp on the right is a non-inverting op-amp :

$$V_O = \left( 1 + \frac{R_L}{R_I} \right) V_F$$

$$i_o = \frac{V_o - V_F}{R_L}$$

$$i_o = \frac{V_F \left( \frac{R_I + R_L}{R_I} \right) - V_F}{R_L}$$

$$i_o = \frac{V_F \left( \frac{R_I + R_L - R_I}{R_I} \right)}{R_L}$$

$$i_o = \frac{V_F}{R_I}$$

$$\frac{i_o}{i_{in}} = \left( \frac{V_F}{i_{in}} \right) \left( \frac{i_o}{V_F} \right)$$

$$\frac{i_o}{i_{in}} = \left( \frac{-i_{in} R_F}{i_{in}} \right) \left( \frac{\frac{V_F}{R_I}}{V_F} \right)$$

$$\frac{i_o}{i_{in}} = \frac{-R_F}{R_I}$$

4.33 Find  $V_o$  in the circuit in Fig. P4.33.


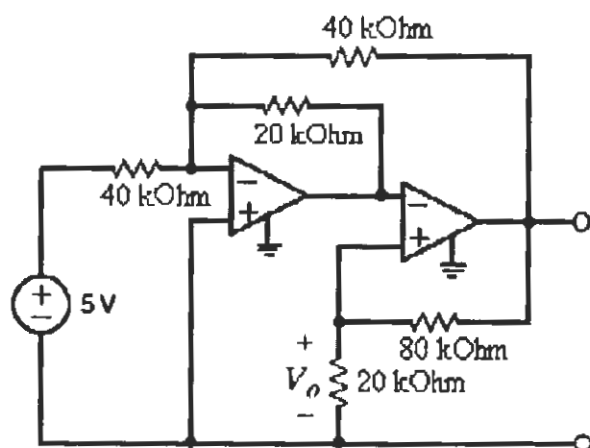


Figure P4.33

Solution: 4-33

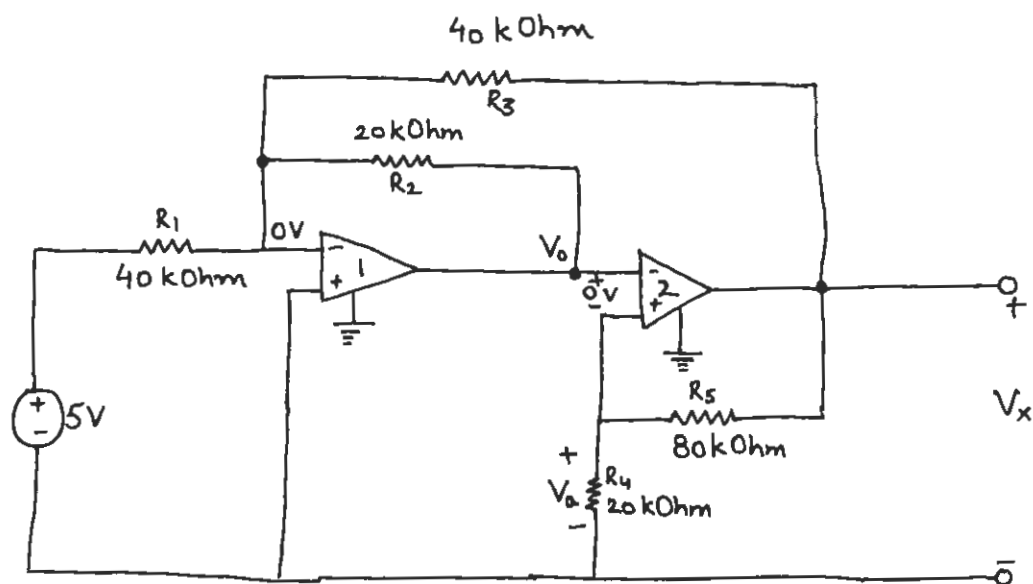

$$\text{KCL at } v_- \text{ input of 1st op-amp: } \frac{5}{R_1} + \frac{V_o}{R_2} + \frac{V_x}{R_3} = 0$$

$$\Rightarrow V_x = -\frac{R_3}{R_1}(5) - \frac{R_3}{R_2}V_o \quad \text{--- (1)}$$

$$\text{KCL at } v_+ \text{ input of 2nd op-amp: } \frac{V_o}{R_4} + \frac{V_o - V_x}{R_5} = 0$$

$$\Rightarrow V_x = V_o \left(1 + \frac{R_5}{R_4}\right) \quad \text{--- (2)}$$

From ②  $V_x = 5V_o$

Substituting  $V_x = 5V_o$  in equation ①, we get

$$V_o = -0.714 \text{ V}$$

4.34 Find  $v_o$  in the circuit in Fig. P4.34.


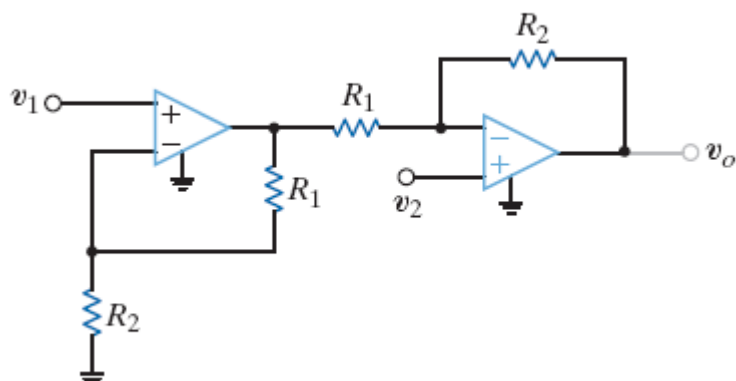


Figure P4.34

**SOLUTION:**

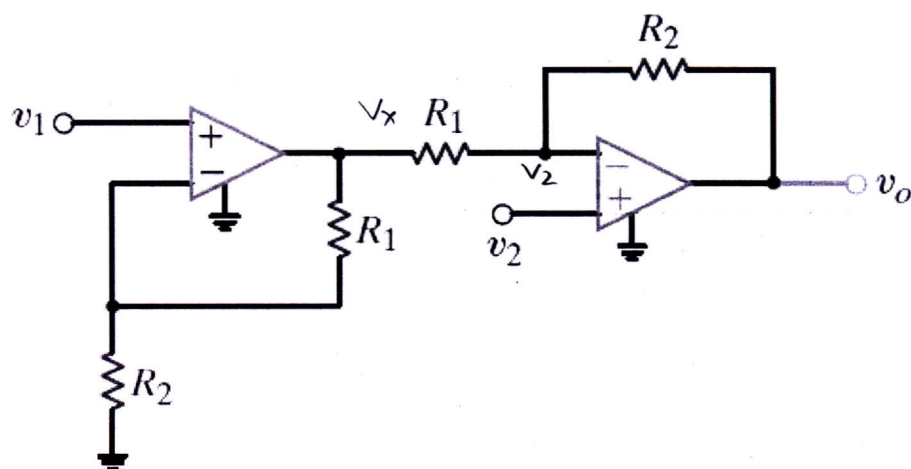

The first op-amp is a non-inverting configuration.

$$\frac{v_x}{v_1} = 1 + \frac{R_1}{R_2}$$

$$v_x = v_1 \left( \frac{R_2 + R_1}{R_2} \right)$$

KCL at  $v_-$  of the 2<sup>nd</sup> op-amp:



$$\frac{V_x - V_2}{R_1} + \frac{V_0 - V_2}{R_2} = 0$$

$$V_0 = V_2 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_x$$

$$V_0 = V_2 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \left( V_1 \left[ \frac{R_2 + R_1}{R_2} \right] \right)$$

$$V_0 = \left( 1 + \frac{R_2}{R_1} \right) (V_2 - V_1)$$

4.35 Determine the value of  $V_o$  in the differential amplifier circuit shown in the Fig. P4.35.


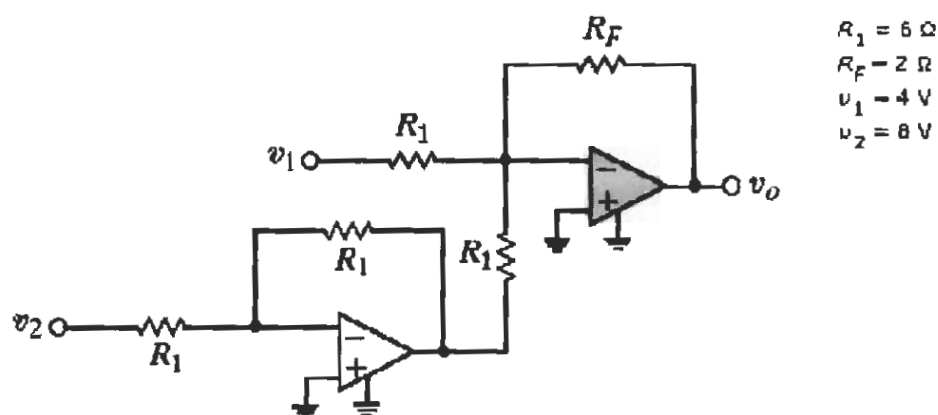


Figure P4.35

Solution: 4.35

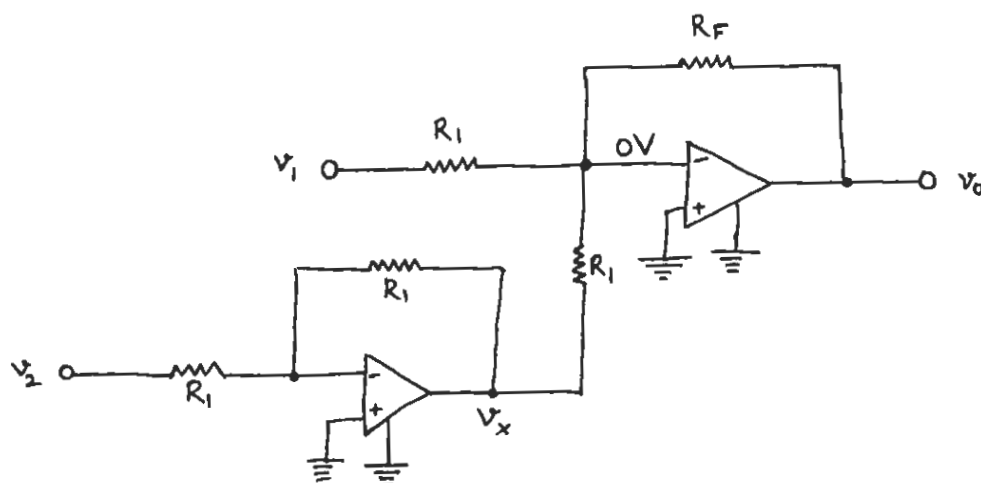

1st op-amp is in inverting configuration:

$$v_x = -\frac{R_1}{R_1} v_2 \Rightarrow v_x = -v_2 \quad \text{--- (1)}$$

KCL at  $v_-$  input of 2nd op-amp:  $\frac{v_1}{R_1} + \frac{v_x}{R_1} + \frac{v_o}{R_F} = 0$

--- (2)

Substituting equation (1) in (2) we get

$$v_o = \frac{R_F}{R_1} (v_2 - v_1)$$

$$v_o = 1.33 \text{ V}$$

4.36 Find  $v_o$  in the circuit in Fig. P4.36.


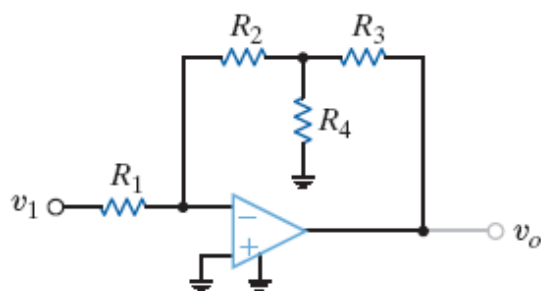


Figure P4.36

**SOLUTION:**

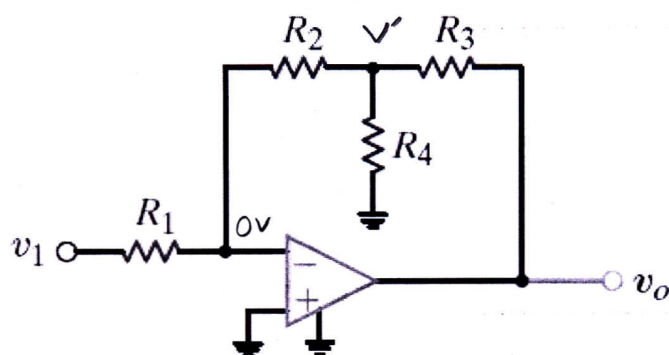

$$\text{KCL at } v_- : \frac{v_1}{R_1} + \frac{v'}{R_2} = 0$$

$$v' = -\frac{R_2}{R_1} v_1$$

$$\text{KCL at } v' : \frac{v'}{R_2} + \frac{v'}{R_4} + \frac{v' - v_o}{R_3} = 0$$

$$v_o = \left( \frac{R_3}{R_2} + \frac{R_3}{R_4} + 1 \right) v'$$

$$v_o = \left( \frac{R_3}{R_2} + \frac{R_3}{R_4} + 1 \right) \left( -\frac{R_2}{R_1} \right) v_1$$

4.37 Find the output voltage,  $V_o$ , in the circuit in Fig. P4.37.

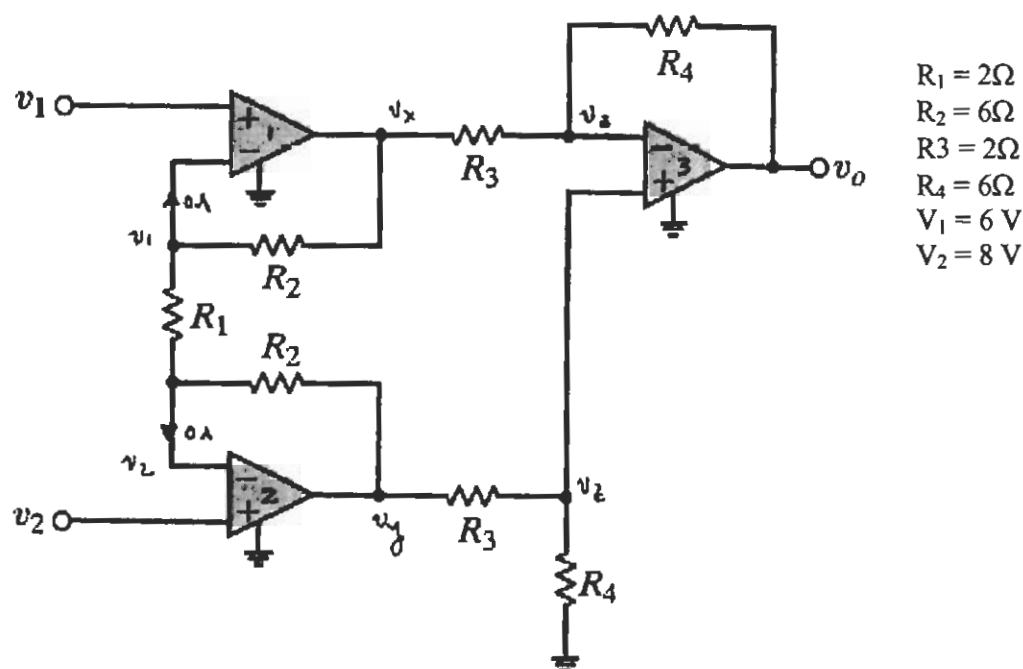


Figure P4.37

Solution: 4.37

$$\begin{aligned} \text{KCL at } v_- \text{ of op-amp 1: } \frac{v_x - v_1}{R_2} &= \frac{v_1 - v_2}{R_1} \\ \Rightarrow v_x &= v_1 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} v_2 \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{KCL at } v_- \text{ of op-amp 2: } \frac{v_y - v_2}{R_2} &= \frac{v_2 - v_1}{R_1} \\ \Rightarrow v_y &= v_2 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} v_1 \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} \text{KCL at } v_+ \text{ of op-amp 3: } \frac{v_y - v_z}{R_3} &= \frac{v_z}{R_4} \\ \Rightarrow v_z &= v_y \left( \frac{R_4}{R_3 + R_4} \right) \quad \text{--- (3)} \end{aligned}$$

$$\begin{aligned} \text{KCL at } v_- \text{ of op-amp 3: } \frac{v_x - v_z}{R_3} + \frac{v_o - v_z}{R_4} &= 0 \\ \Rightarrow v_o &= v_z \left( 1 + \frac{R_4}{R_3} \right) - \frac{R_4}{R_3} v_x \quad \text{--- (4)} \end{aligned}$$

From ①, we get,  $v_x = 0$

From ②, we get,  $v_y = 14 \text{ V}$

Substituting the value of  $v_y$  in equation ③, we get

$$v_z = \frac{21}{2} \text{ V}$$

Substituting the values of  $v_z$  and  $v_x$  in equation ④, we get

$$v_o = 42 \text{ V}$$

- 4.38 The electronic ammeter in Example 4.9 has been modified and is shown in Fig. P4.38. The selector switch allows the user to change the range of the meter. Using values for  $R_1$  and  $R_2$  from Example 4.9, find the values of  $R_A$  and  $R_B$  that will yield a 10-V output when the current being measured is 100 mA and 10 mA, respectively.


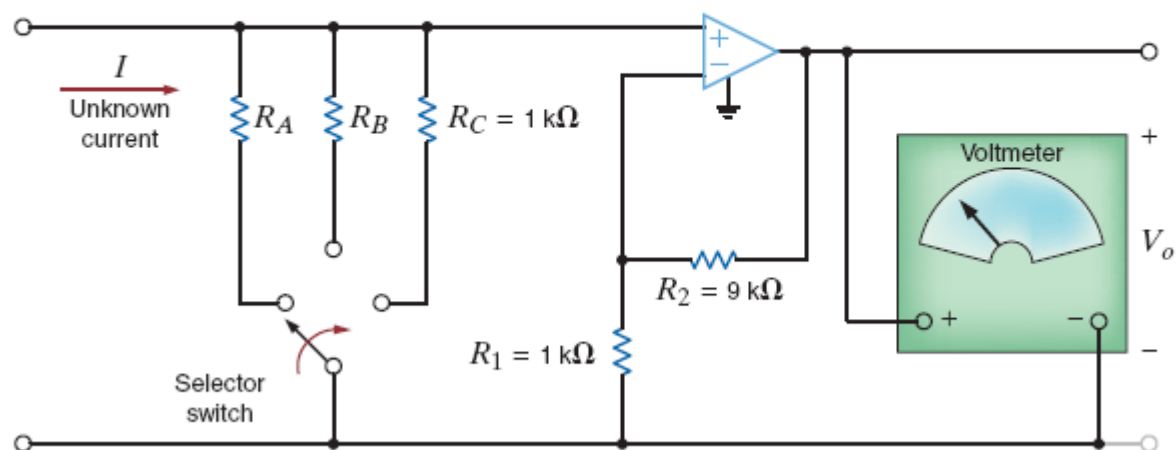


Figure P4.38

SOLUTION:

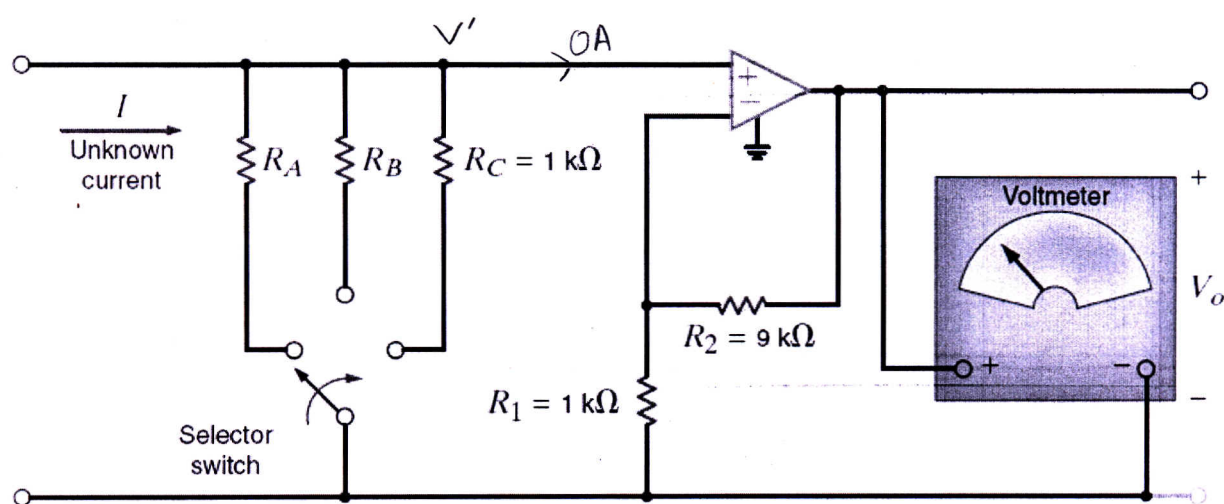

Non-inverting op-amp:

$$V_o = \left( 1 + \frac{R_2}{R_1} \right) V' = 10V'$$

$$V' = IR_A = 0.1R_A$$

$$V_o = 10V'$$

$$V_0 = 10(0.1 R_A) = 10$$

$$R_A = 10 \Omega$$

$$V' = I R_B = 0.01 R_B$$

$$V_0 = 10V' = 10(0.01 R_B) = \frac{R_B}{10}$$

$$\frac{R_B}{10} = 10$$

$$R_B = 100 \Omega$$


- 4.39 Given a box of 10-k $\Omega$  resistors and an op-amp, design a circuit that will have an output voltage of

$$V_o = -2V_1 - 4V_2$$

**SOLUTION:**

$$V_o = -2V_1 - 4V_2$$


A summer will produce the output given:

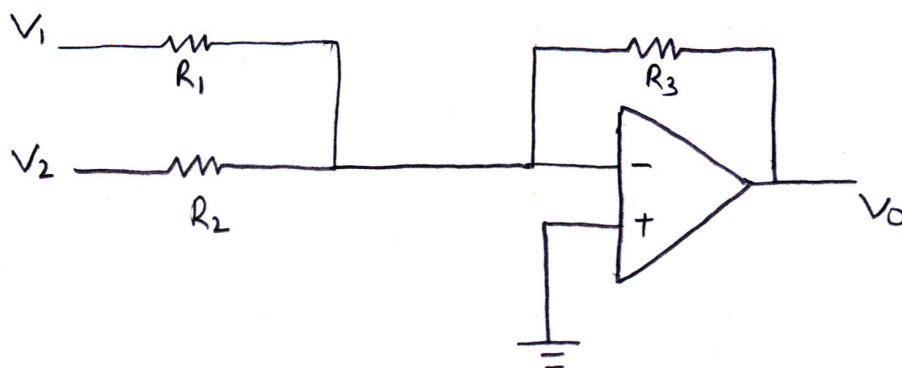

$$V_o = -\frac{R_3}{R_1} V_1 - \frac{R_3}{R_2} V_2$$


$$V_o = -2V_1 - 4V_2$$

The following circuit will work:

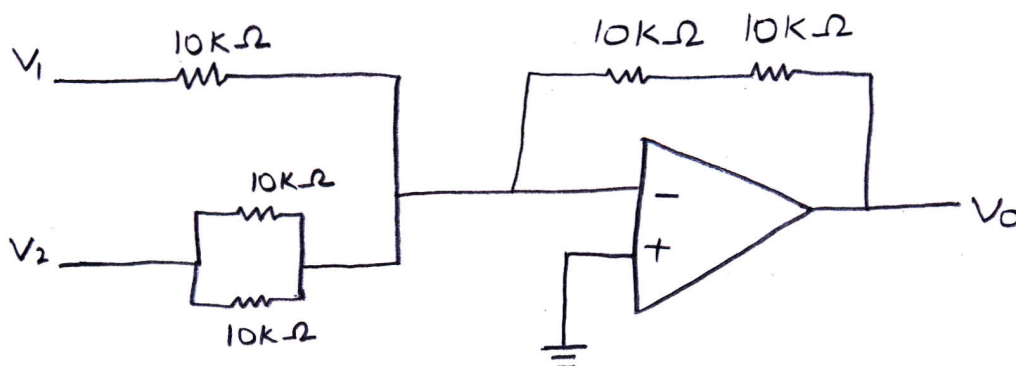




**4.40** Design an op-amp circuit that has a gain of  $-110$  using resistors no smaller than  $1\text{ k}\Omega$ . The circuit is given

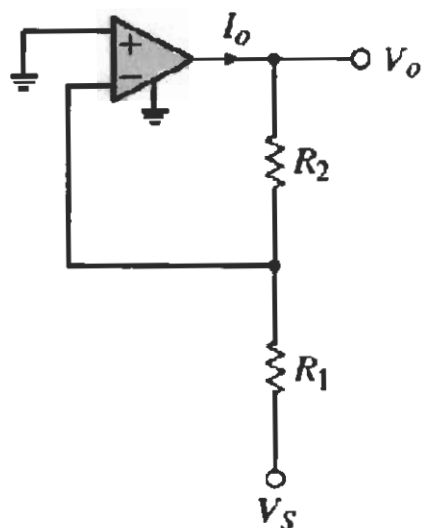

**Figure P4.40**

If  $R_1 = 3\text{ k}\Omega$ , Find  $R_2$ .

Solution: 4.40

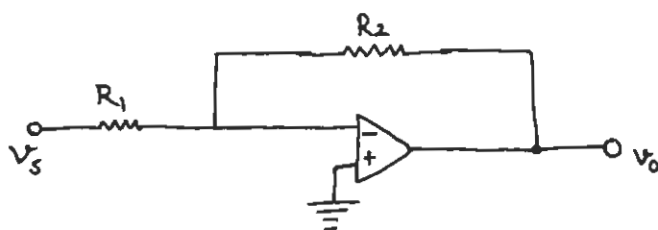

Since the gain is negative, use inverting configuration:

$$\frac{V_O}{V_S} = -\frac{R_2}{R_1} = -110$$

$$\frac{R_2}{R_1} = 110$$

Choose  $R_1 = 5\text{ k}\Omega$ , then  $R_2 = 550\text{ k}\Omega$

If  $R_1 = 3\text{ k}\Omega$ ,


$$R_2 = 330\text{ k}\Omega$$

- 4.41 Design a two-stage op-amp network that has a gain of  $-50,000$  while drawing no current into its input terminal. Use no resistors smaller than  $1\text{ k}\Omega$ .

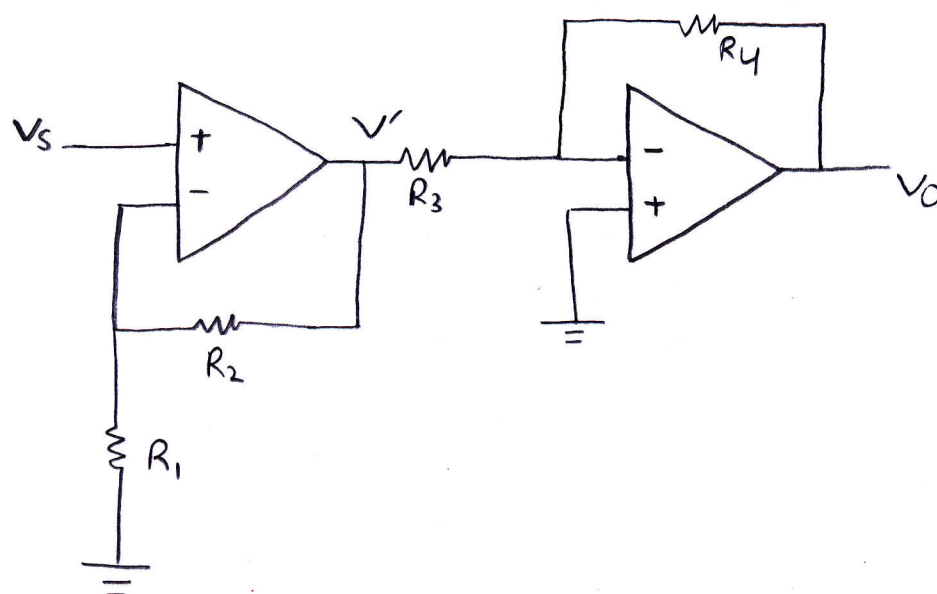**SOLUTION:**

For no input current, a non-inverting op-amp can be used

For a negative value, an inverting op-amp can be used.



$$\frac{V'}{V_s} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o}{V'} = -\frac{R_4}{R_3}$$

$$\frac{V_o}{V_s} = -\frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\text{Select } \frac{V_x}{V_s} = 250$$

$$\text{and } \frac{V_o}{V_x} = -200$$

$$R_1 = R_3 = 2 \text{ k}\Omega$$


$$250 = 1 + \frac{R_2}{2000}$$

$$R_2 = 498 \text{ k}\Omega$$

$$-200 = \frac{-R_4}{2000}$$

$$R_4 = 400 \text{ k}\Omega$$


**4.42** Design an op-amp circuit that has the following input/output relationship:  
 $V_o = -18V_1 + 0.5V_2$ . The circuit is given

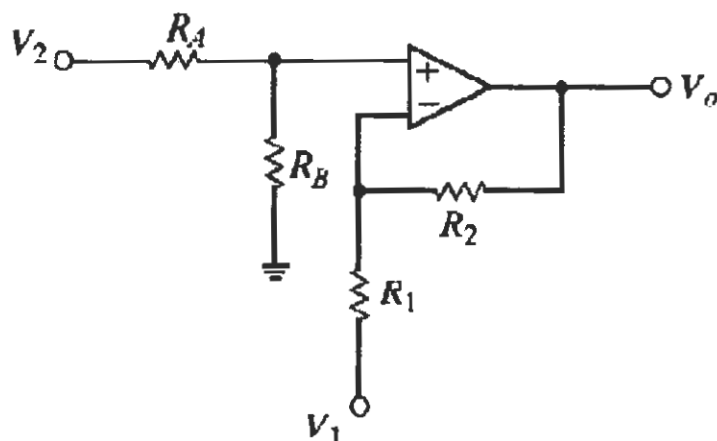

**Figure P4.42**

If  $R_B = 1\text{ k}\Omega$  and  $R_1 = 1\text{ k}\Omega$ , Find (a)  $R_A$  and (b)  $R_2$ .

Solution: 4.42

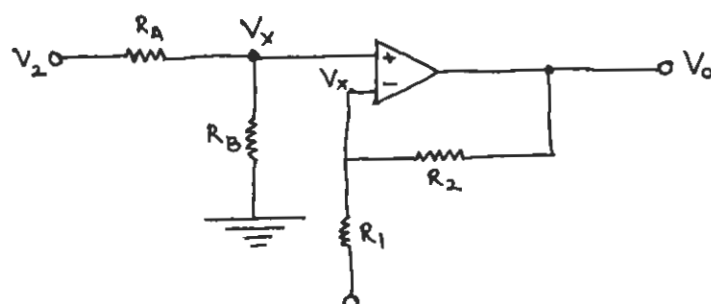

$$\begin{aligned} \text{KCL at } v_+ : \quad \frac{V_2 - V_x}{R_A} &= \frac{V_x}{R_B} \\ \Rightarrow \quad \frac{V_x}{V_2} &= \frac{R_B}{R_A + R_B} \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{KCL at } v_- : \quad \frac{V_o - V_x}{R_2} &= \frac{V_x - V_1}{R_1} \\ \Rightarrow \quad V_o &= V_x \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_1 \quad \text{--- (2)} \end{aligned}$$

Substituting equation (1) in (2), we get

$$V_o = -\frac{R_2}{R_1} V_1 + \frac{R_B}{R_A + R_B} \left( 1 + \frac{R_2}{R_1} \right) V_2 \quad \text{--- (3)}$$

$$= -18 V_1 + 0.5 V_2$$

$$\therefore \frac{R_2}{R_1} = 18 \quad \text{choose } R_1 = 2 \text{ k}\Omega, R_2 = 36 \text{ k}\Omega$$

Substituting  $\frac{R_2}{R_1} = 18$  in equation (3), we get

$$V_o = -18 V_1 + \frac{R_B}{R_A + R_B} (1 + 18) V_2$$

$$= -18 V_1 + \frac{19 R_B}{R_A + R_B} V_2$$

$$= -18 V_1 + 0.5 V_2$$

$$\text{Therefore } \frac{19 R_B}{R_A + R_B} = 0.5$$

$$\Rightarrow \frac{R_A}{R_B} = 37 \quad \text{choose } R_B = 5 \text{ k}\Omega, R_A = 185 \text{ k}\Omega$$

Therefore, for the given input/output relationship, we can choose  $R_1 = 2 \text{ k}\Omega, R_2 = 36 \text{ k}\Omega, R_A = 185 \text{ k}\Omega, R_B = 5 \text{ k}\Omega$

If  $R_B = 1 \text{ k}\Omega, R_1 = 1 \text{ k}\Omega$

$$R_A = 37 \text{ k}\Omega$$


$$R_2 = 18 \text{ k}\Omega$$

- 4.43 A voltage waveform with a maximum value of 200 mV must be amplified to a maximum of 10 V and inverted. However, the circuit that produces the waveform can provide no more than 100  $\mu$ A. Design the required amplifier.

**SOLUTION:**

A non-inverting op-amp followed by an inverting op-amp will work.

$$\text{gain} = \frac{-10}{0.2} = -50$$

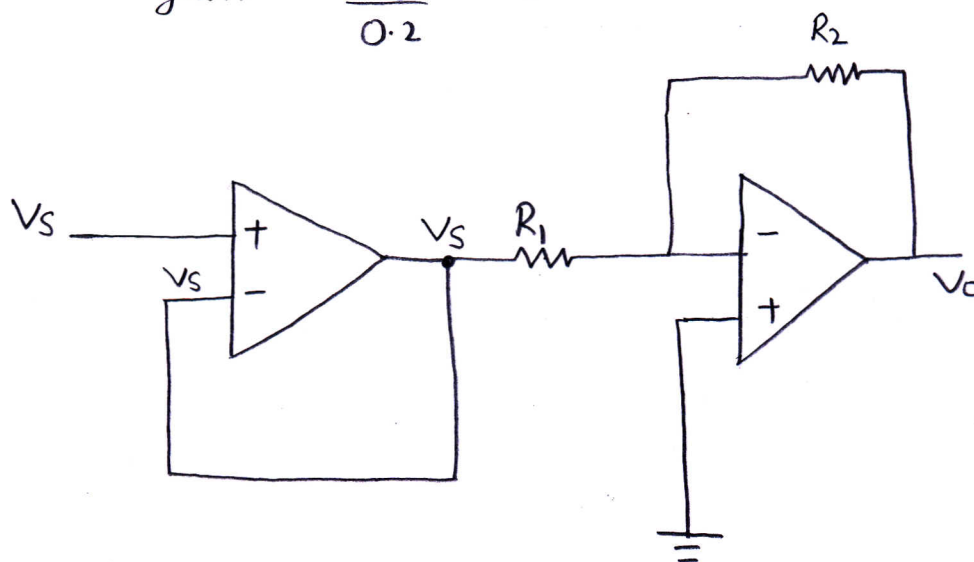

$$\frac{V_o}{V_s} = \frac{-R_2}{R_1}$$

Select  $R_1 = 1 \text{ k}\Omega$

$$R_2 = -50(-1000)$$

$$R_2 = 50 \text{ k}\Omega$$

4.44 An amplifier with a gain of  $\pi \pm 1\%$  is needed. Design the amplifier. The amplifier is drawn


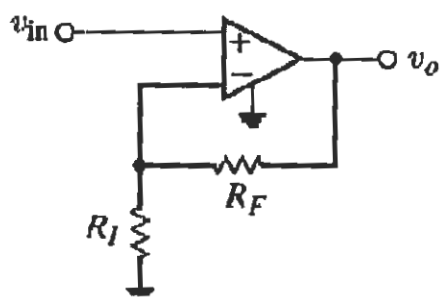


Figure P4.44

If  $R_I = 8 \text{ k}\Omega$ , Find  $R_F$ .

Solution: 4.44

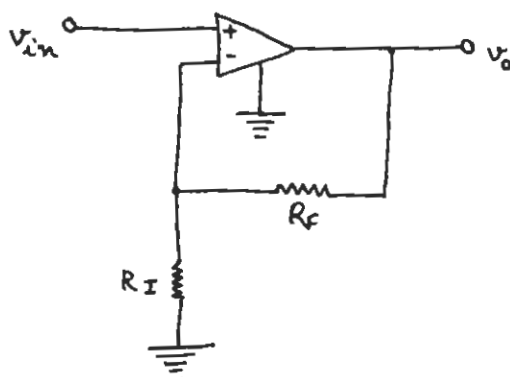

For positive gain, use non-inverting configuration

$$\frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_I} = A$$

$$\text{For } A = \pi \pm 1\%, \quad 2.111 \leq \frac{R_F}{R_I} \leq 2.174$$

We choose  $R_I = 20 \text{ k}\Omega$ ,  $R_F = 43 \text{ k}\Omega$

$A = 3.15$  and this is within the limit  $3.111 < A < 3.174$

$$\text{If } R_I = 8 \text{ k}\Omega, \quad 1 + \frac{R_F}{R_I} = 3.15$$


$$\boxed{R_F = 17.2 \text{ k}\Omega}$$

4.45 Design an op-amp-based circuit to produce the function

$$V_o = 5V_1 - 4V_2$$

**SOLUTION:**

$$V_o = 5V_1 - 4V_2$$

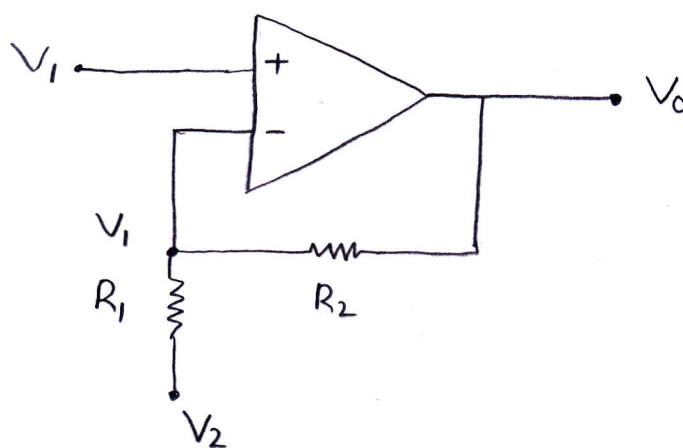

$$\text{KCL at } V_- : \frac{V_o - V_1}{R_2} = \frac{V_1 - V_2}{R_1}$$

$$V_o = \frac{R_2}{R_1} V_1 + V_1 - \frac{R_2}{R_1} V_2$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_1 - \frac{R_2}{R_1} V_2$$

$$\text{Select } R_1 = 5\text{K}\Omega$$

$$R_2 = 20\text{K}\Omega$$



4.46 Design an op-amp-based circuit to produce the function

$$V_o = 5V_1 - 7V_2.$$

The circuit is given


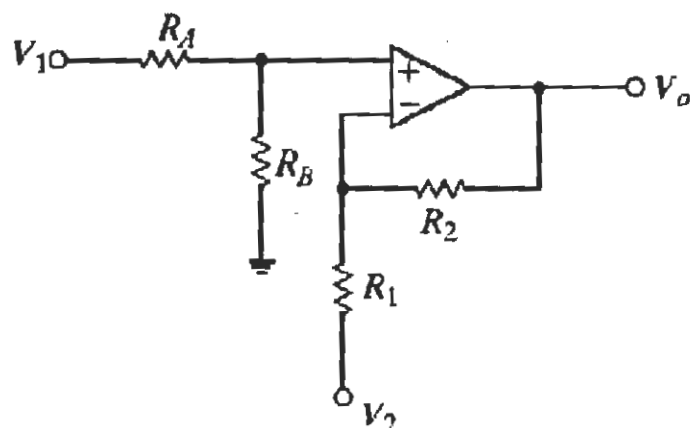


Figure P4.46

If  $R_B = 40 \text{ k}\Omega$  and  $R_1 = 8 \text{ k}\Omega$ , Find (a)  $R_A$  and (b)  $R_2$ .

Solution: 4.46

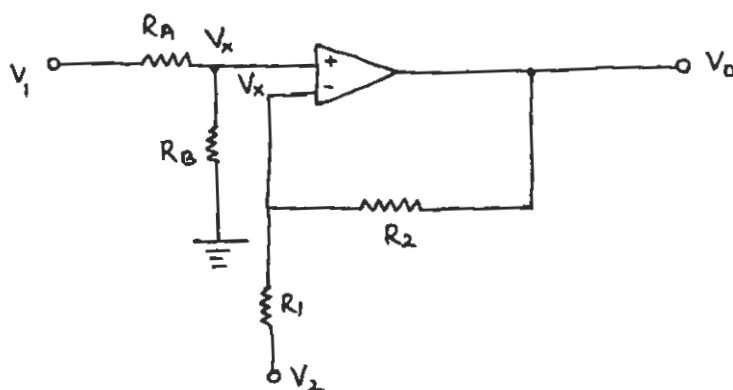

Use both + and - inputs to get + and - gains

KCL at  $v_+$  input:  $\frac{V_1 - V_x}{R_A} = \frac{V_x}{R_B}$

$$\Rightarrow \frac{V_x}{V_1} = \frac{R_B}{R_A + R_B} \quad \text{--- (1)}$$

KCL at  $v_-$  input:  $\frac{V_o - V_x}{R_2} = \frac{V_x - V_2}{R_1}$

$$\Rightarrow V_o = V_x \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_2 \quad \text{--- (2)}$$

Substituting  $V_x$  from equation (1) in (2), we get

$$V_o = V_1 \left( \frac{R_B}{R_A + R_B} \right) \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_2$$

$$\frac{R_2}{R_1} = 7 \quad \text{Choose } R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 7 \text{ k}\Omega$$

$$\left( \frac{R_B}{R_A + R_B} \right) 8 = 5 \quad \text{Choose } R_B = 5 \text{ k}\Omega \Rightarrow R_A = 3 \text{ k}\Omega$$

If  $R_B = 40 \text{ k}\Omega$  and  $R_1 = 8 \text{ k}\Omega$ ,

$$\boxed{R_A = 24 \text{ k}\Omega}, \quad \boxed{R_2 = 56 \text{ k}\Omega}$$

4.47 Show that the circuit in Fig. P4.47 can produce the output

$$V_o = K_1 V_1 - K_2 V_2$$

only for  $0 \leq K_1 \leq K_2 + 1$ .


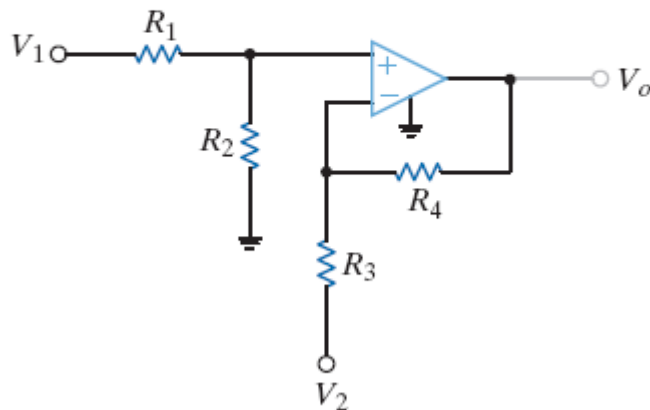


Figure P4.47

**SOLUTION:**

$$V_o = K_1 V_1 - K_2 V_2$$

$$0 \leq K_1 \leq K_2 + 1$$

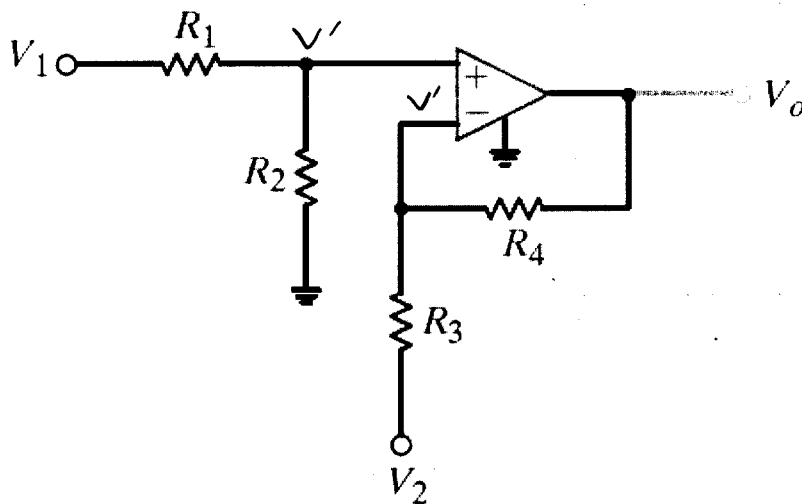

$$\text{KCL at } V' : \frac{V_1 - V'}{R_1} = \frac{V'}{R_2}$$

$$V' \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_1}{R_1}$$

$$V' = \left( \frac{R_2}{R_1 + R_2} \right) V_1$$

$$\text{KCL at } V_- : \frac{V_0 - V'}{R_4} = \frac{V' - V_2}{R_3}$$

$$V_0 = \left( \frac{1}{R_3} + \frac{1}{R_4} \right) R_4 V' - \frac{R_4}{R_3} V_2$$

$$V_0 = \left( 1 + \frac{R_4}{R_3} \right) V' - \frac{R_4}{R_3} V_2$$

$$V_0 = \left( 1 + \frac{R_4}{R_3} \right) \left( \frac{R_2}{R_1 + R_2} \right) V_1 - \frac{R_4}{R_3} V_2$$

$$V_0 = K_1 V_1 - K_2 V_2$$

$$K_2 = \frac{R_4}{R_3}$$

$$\text{If } R_2 = 0 \, \Omega, \quad K_1 = 0$$

$$\text{If } R_2 \neq 0 \, \Omega \text{ and } R_1 = 0 \, \Omega$$

$$K_1 = 1 + \frac{R_4}{R_3}$$

$$K_1 = 1 + K_2$$

$$0 \leq k_1 \leq k_2 + 1$$

- 4.48 A  $170^{\circ}\text{C}$  maximum temperature digester is used in a paper mill to process wood chips that will eventually become paper. As shown in Fig. P4.48a, three electronic thermometers are placed along its length. Each thermometer outputs  $0\text{ V}$  at  $0^{\circ}\text{C}$ , and the voltage changes  $25\text{ mV}/^{\circ}\text{C}$ . We will use the average of the three thermometer voltages to find an aggregate digester temperature. Furthermore,  $1\text{ volt}$  should appear at  $V_o$  for every  $10^{\circ}\text{C}$  of average temperature. Design such an averaging circuit using the op-amp configuration shown in Fig. P4.48b if the final output voltage must be positive.

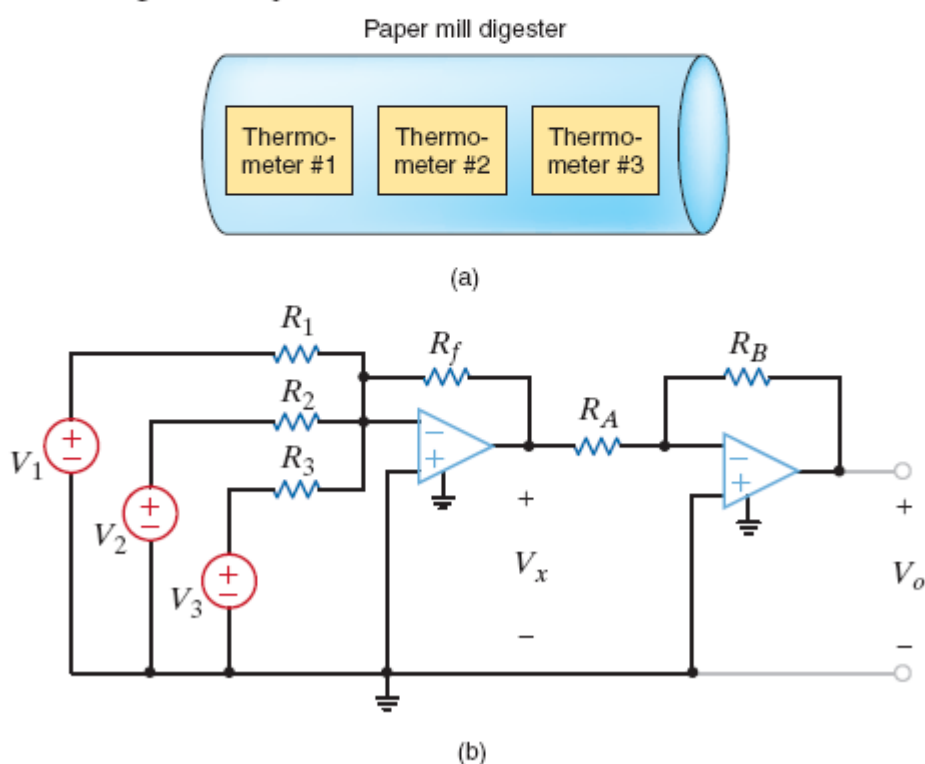
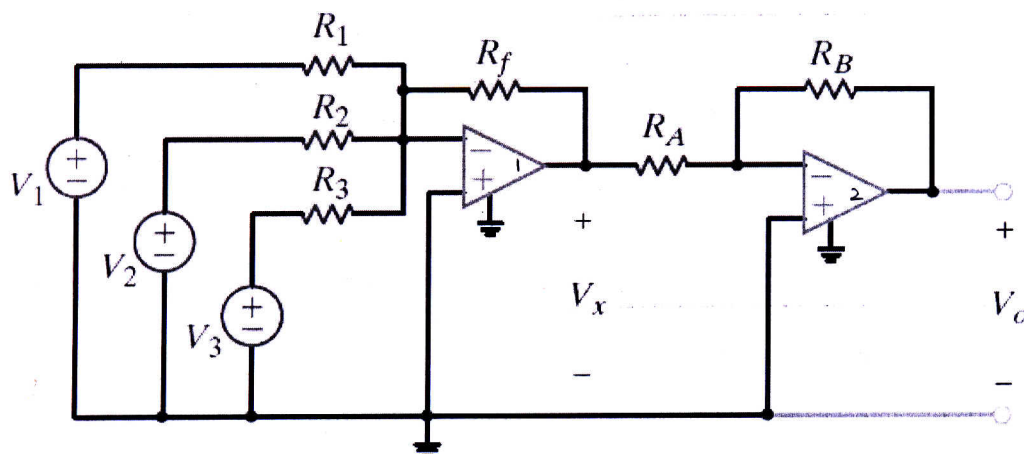


Figure P4.48

**SOLUTION:**

op-amp #1 is a summer.

op-amp #2 is an inverting op-amp.

$$V_x = - \left[ \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

$$V_o = \frac{-R_B}{R_A} V_x$$

$$V_o = \frac{R_B}{R_A} \left[ \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

$$\text{Select } \frac{R_F}{R_1} = \frac{R_F}{R_2} = \frac{R_F}{R_3} = \frac{1}{3}$$

$$V_o = \frac{R_B}{R_A} \left( \frac{V_1 + V_2 + V_3}{3} \right)$$

$$\text{If } \Delta T_1 = 10^\circ\text{C}, \Delta V = 0.25\text{V} \\ \text{and } \Delta V_o = 1\text{V}$$

$$\frac{\Delta V_o}{\Delta V_1} = \frac{R_B}{R_A} \left( \frac{1}{3} \right)$$

$$\frac{\Delta V_o}{\Delta V_1} = \frac{1}{0.25}$$

$$\frac{\Delta V_o}{\Delta V_i} = 4$$

$$\text{Select } R_A = R_F = 1 \text{ k}\Omega$$

$$R_1 = R_2 = R_3 = 3 \text{ k}\Omega$$

$V_o$  should be 4 times average of 3 temperatures.

$$\therefore \left( \frac{V_1 + V_2 + V_3}{3} \right) \times 4 = V_o$$

$$\therefore \frac{R_B}{R_A} = 12 \Rightarrow \boxed{R_B = 12 \text{ k}\Omega}$$



- 4.49 A  $0.1\text{-}\Omega$  shunt resistor is used to measure current in a fuel-cell circuit. The voltage drop across the shunt resistor is to be used to measure the current in the circuit. The maximum current is 20 A. Design the circuit shown in Fig. P4.49 so that a voltmeter attached to the output will read 0 volts when the current is 0 A and 20 V when the current is 20 A. Be careful not to load the shunt resistor, since loading will cause an inaccurate reading.


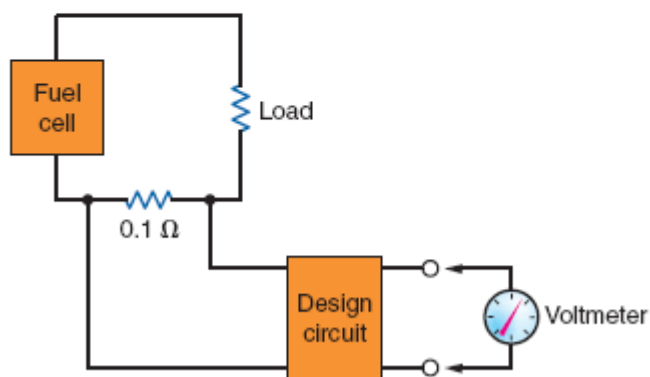


Figure P4.49

**SOLUTION:**

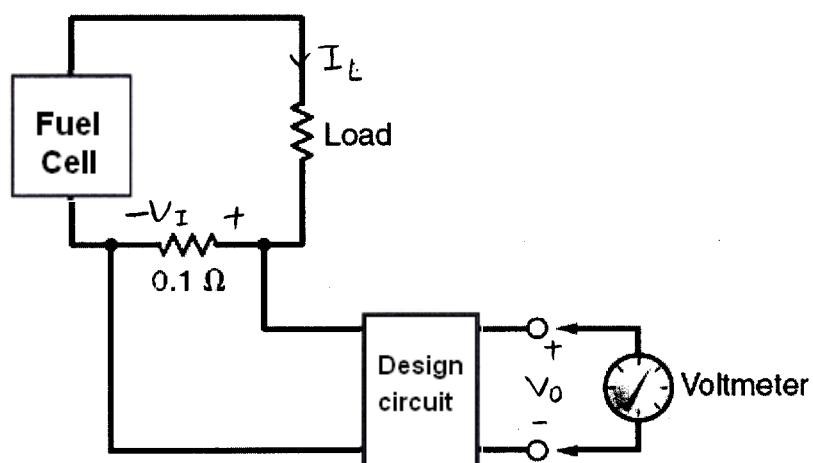


$$\text{When } I_L = 20\text{ A, } V_I = 0.1 I_L$$

$$V_I = 0.1(20)$$

$$V_I = 2\text{ V}$$

$$\text{and } V_0 = 20\text{ V.}$$

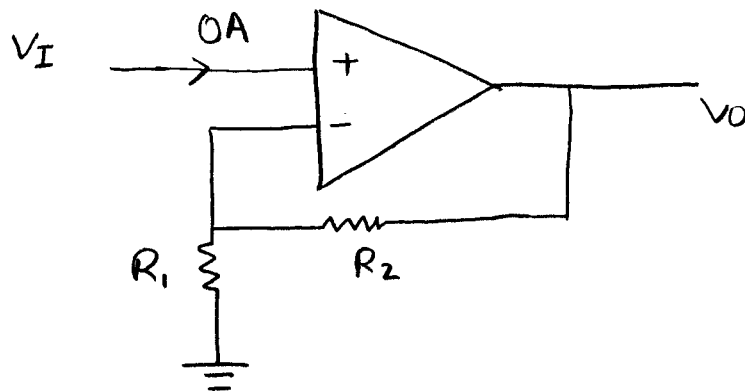a gain of 10 is needed with a buffered input. The op-amp should be a non-inverting configuration.



$$\frac{V_O}{V_I} = 1 + \frac{R_2}{R_1}$$


$$\frac{V_O}{V_I} = 10$$

$$\text{Select } R_1 = 1\text{K}\Omega$$

$$10 = 1 + \frac{R_2}{1 \times 10^3}$$

$$R_2 = 9\text{K}\Omega$$


**4.50** Wood pulp is used to make paper in a paper mill. The amount of lignin present in pulp is called the kappa number. A very sophisticated instrument is used to measure kappa, and the output of this instrument ranges from 1 to 5 volts, where 1 volt represents a kappa number of 12 and 5 volts represents a kappa number of 20. The pulp mill operator has asked to have a kappa meter installed on his console. Design a circuit that will employ as input the 1-to 5-volt signal and output the kappa number. An electronics engineer in the plant has suggested the circuit shown in Fig. P4.50.

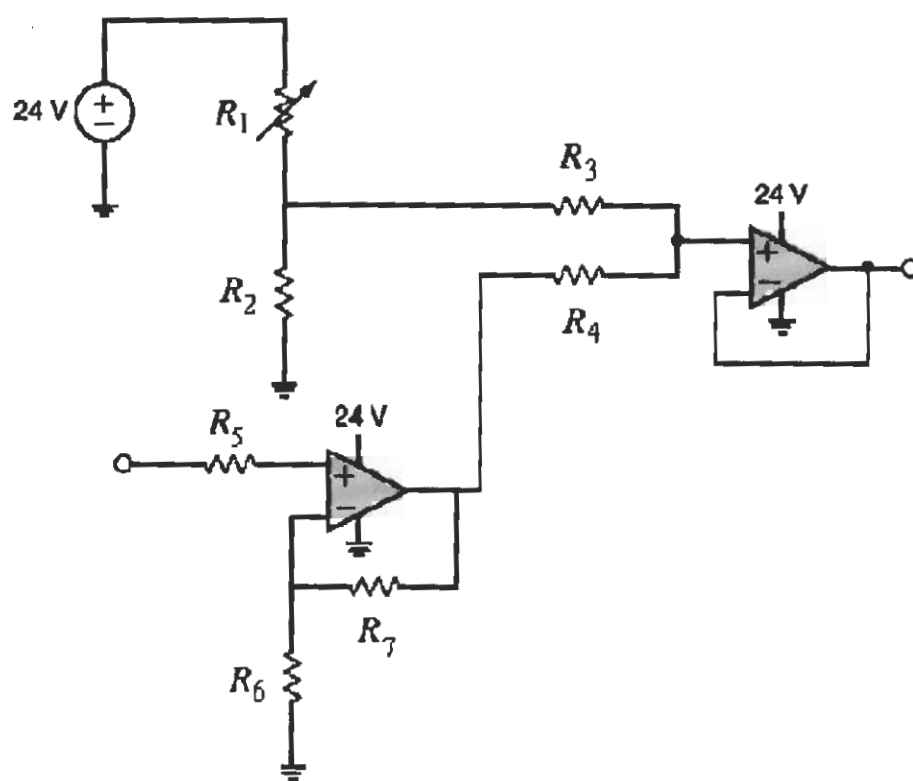

**Figure P4.50**

If  $R_1 = 1\text{ k}\Omega$ ,  $R_2 = R_3 = R_4 = R_5 = 7.5\text{ k}\Omega$ ,  $R_6 = 19\text{ k}\Omega$ , Find  $R_7$ .

**Solution:** 4.50

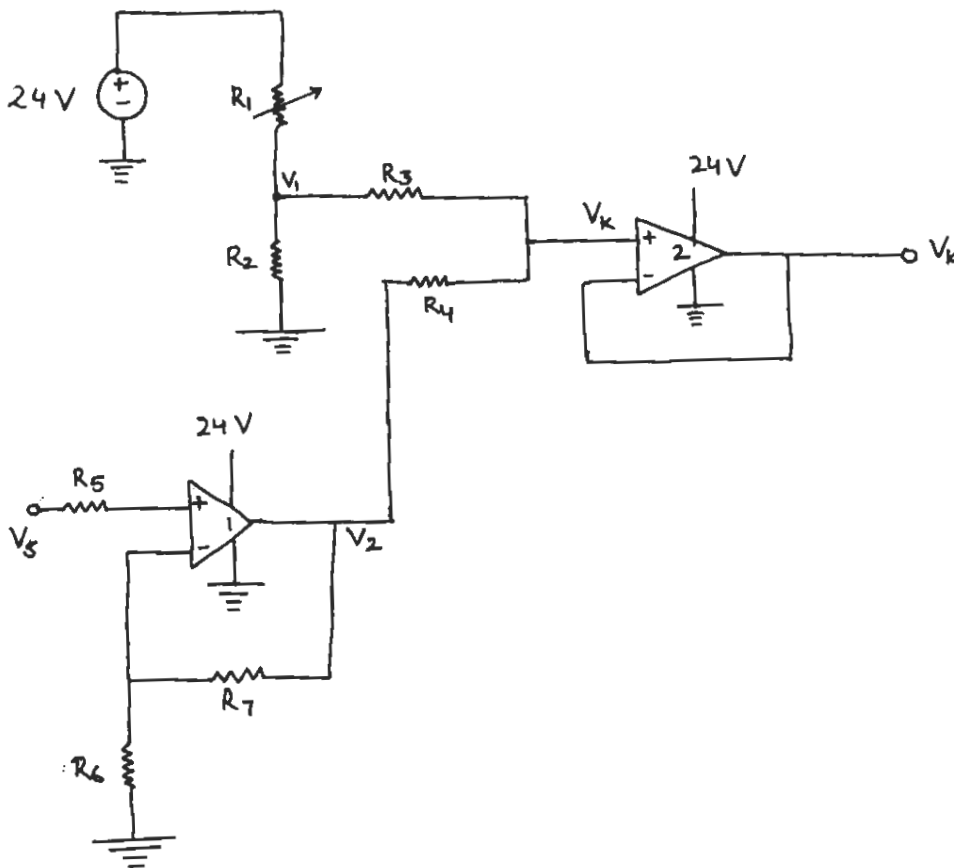

$$\text{KCL at } V_1 : \frac{24 - V_1}{R_1} = \frac{V_1}{R_2} + \frac{V_1 - V_k}{R_3} \quad \text{--- ①}$$

$$\text{KCL at } V_k : \frac{V_1 - V_k}{R_3} = \frac{V_k - V_2}{R_4} \quad \text{--- ②}$$

op-amp 1 is at non-inverting configuration :

$$V_2 = V_s \left( 1 + \frac{R_7}{R_6} \right) = g V_s$$

$$\text{Let } R_2 = R_3 = R_4 = R_5 = R$$

$$\text{@ } V_k : V_1 = 2V_k - V_2 \quad \text{--- ④}$$

$$\text{@ } V_1 : 24R = V_1(2R_1 + R) - V_k R_1 \quad \text{--- ⑤}$$

$$\text{yields } V_k = \frac{24R}{3R_1 + 2R} + g \frac{(2R_1 + R)}{3R_1 + 2R} V_s \quad \text{--- ⑥}$$

$$\text{Also, } V_k = b + mV_s$$

$$\text{At } V_s = 1V, V_k = 12V \text{ and at } V_s = 5V, V_k = 20V$$

$$\text{Therefore } m = \frac{\Delta V_k}{\Delta V_s} = \frac{8}{4} = 2 \text{ and } b = 10$$

$$V_k = 10 + 2V_s = \frac{24R}{3R_1 + 2R} + g \frac{(2R_1 + R)}{3R_1 + 2R} V_s \quad \text{--- (7)}$$

We have,  $R_1 = 1 \text{ k}\Omega$ ,  $R = 7.5 \text{ k}\Omega$

Substituting the values of  $R$ , and  $R$  in equation (7), we get

$$V_k = 10 + 2V_s = 10 + \frac{9.5}{18} g V_s$$

$$\therefore 2V_s = \frac{9.5}{18} g V_s$$

$$\Rightarrow g = \frac{36}{9.5} = 3.79$$

From equation (3), we get  $1 + \frac{R_7}{R_6} = 3.79$

$$R_6 = 19 \text{ k}\Omega$$

$$\therefore \boxed{R_7 = 53.01 \text{ k}\Omega}$$

- 4.51 An operator in a chemical plant would like to have a set of indicator lights that indicate when a certain chemical flow is between certain specific values. The operator wants a RED light to indicate a flow of at least 10 GPM (gallons per minute), RED and YELLOW lights to indicate a flow of 60 GPM, and RED, YELLOW, and GREEN lights to indicate a flow rate of 80 GPM. The 4–20 mA flow meter instrument outputs 4 mA when the flow is zero and 20 mA when the flow rate is 100 GPM.

An experienced engineer has suggested the circuit shown in Fig. P4.51. The 4–20 mA flow meter and 250  $\Omega$  resistor provide a 1–5 V signal, which serves as one input for the three comparators. The light bulbs will turn on when the negative input to a comparator is higher than the positive input. Using this network, design a circuit that will satisfy the operator's requirements.

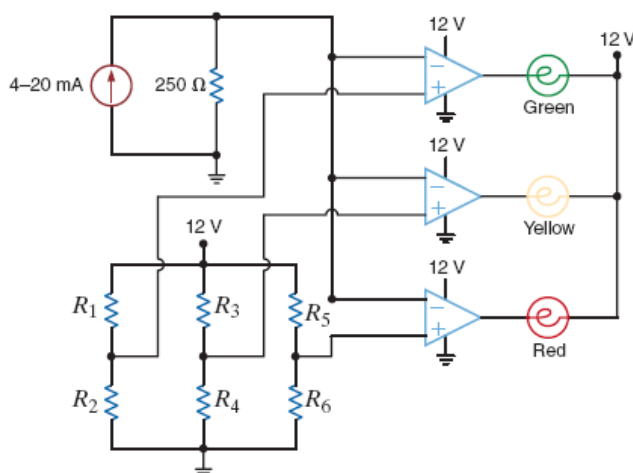
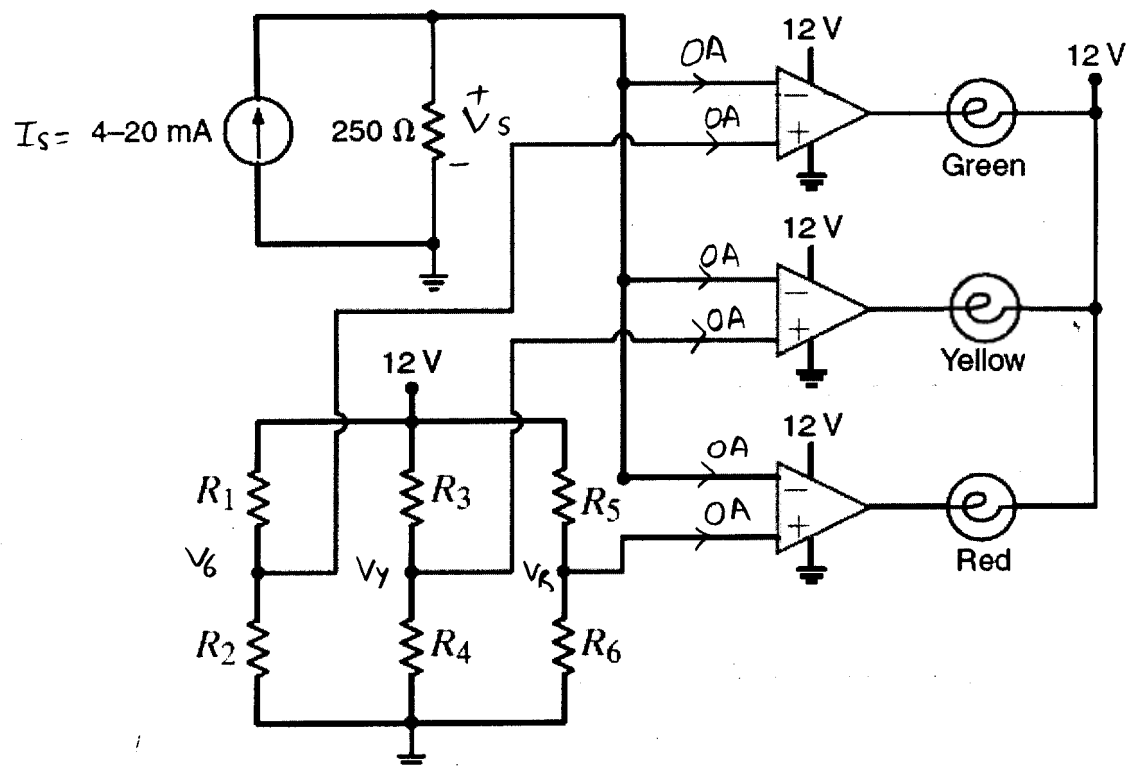


Figure P4.51

**SOLUTION:**

want  $V_6 = V_5$  when flow = 806 Pm

$$I_s = m(\text{flow}) + b$$

$$\text{flow} = 0, \quad I_s = 4 \text{ mA}$$

$$\text{flow} = 100, \quad I_s = 20 \text{ mA}$$

$$4 \times 10^{-3} = m(0) + b$$

$$b = 4 \times 10^{-3}$$

$$20 \times 10^{-3} = m(100) + 4 \times 10^{-3}$$

$$m = 0.16 \times 10^{-3}$$

$$I_s = 0.16 \times 10^{-3} \text{ flow} + 4 \times 10^{-3}$$

$$\text{at flow} = 806 \text{ Pm}, \quad I_s = 16.8 \text{ mA}$$

$$V_s = 250 I_s$$

$$V_s = 250 (16.8 \times 10^{-3})$$

$$V_s = 4.2 \text{ V}$$

$$V_o = \left( \frac{R_2}{R_1 + R_2} \right) (12)$$

$$\text{Select } R_2 = 1\text{K}\Omega$$

$$R_1 = 1.86\text{K}\Omega$$

$$\text{at flow} = 606\text{PM}$$

$$I_s = 0.16 \times 10^{-3}(60) + 4 \times 10^{-3}$$

$$I_s = 13.6\text{mA}$$

$$V_s = 250(13.6 \times 10^{-3})$$

$$V_s = 3.4\text{V}$$

$$\text{Want } V_y = 3.4\text{V}$$

$$V_y = \frac{12R_4}{R_4 + R_3}$$

$$3.4 = \frac{12R_4}{R_4 + R_3}$$

$$\text{Select } R_4 = 1\text{K}\Omega, R_3 = 2.53\text{K}\Omega$$

$$\text{at flow} = 106\text{PM}$$



$$I_s = 0.16 \times 10^{-3}(10) + 4 \times 10^{-3}$$

$$I_s = 5.6 \text{ mA}$$

$$V_s = 250(5.6 \times 10^{-3})$$

$$V_s = 1.4 \text{ V}$$

$$V_R = 1.4 \text{ V}$$

$$1.4 = \frac{12R_6}{R_6 + R_5}$$

$$\text{Select } R_6 = 1 \text{ k}\Omega, R_5 = 7.57 \text{ k}\Omega$$

$$\text{Select } R_2 = R_4 = R_6 = 1 \text{ k}\Omega$$

$$R_1 = 1.86 \text{ k}\Omega$$

$$R_3 = 2.53 \text{ k}\Omega$$

$$R_5 = 7.57 \text{ k}\Omega$$

- 4.52** An industrial plant has a requirement for a circuit that uses as input the temperature of a vessel and outputs a voltage proportional to the vessel's temperature. The vessel's temperature ranges from  $0^{\circ}\text{C}$  to  $500^{\circ}\text{C}$ , and the corresponding output of the circuit should range from 0 to 10V. A RTD (resistive thermal device), which is a linear device whose resistance changes with temperature according to the plot in Fig. P4.52a, is available. The problem then is to use this RTD to design a circuit that employs this device as an input and produces a 0-to 12-V signal at the output, where 0 V corresponds to  $0^{\circ}\text{C}$  and 12 V corresponds to  $500^{\circ}\text{C}$ . An engineer familiar with this problem suggests the use of the circuit shown in Fig. P4.52b in which the RTD bridge circuit provides the input to a standard instrumentation amplifier. Determine the component values in this network needed to satisfy the design requirements. If  $R_1 = R_2 = R_3 = 100\Omega$ ,  $R_4 = R_5 = 4\text{K}\Omega$  Find  $R_G$ .

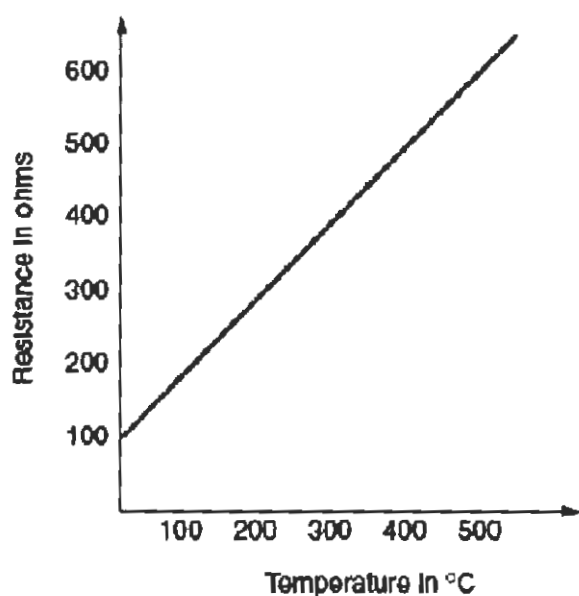


Figure P4.52a


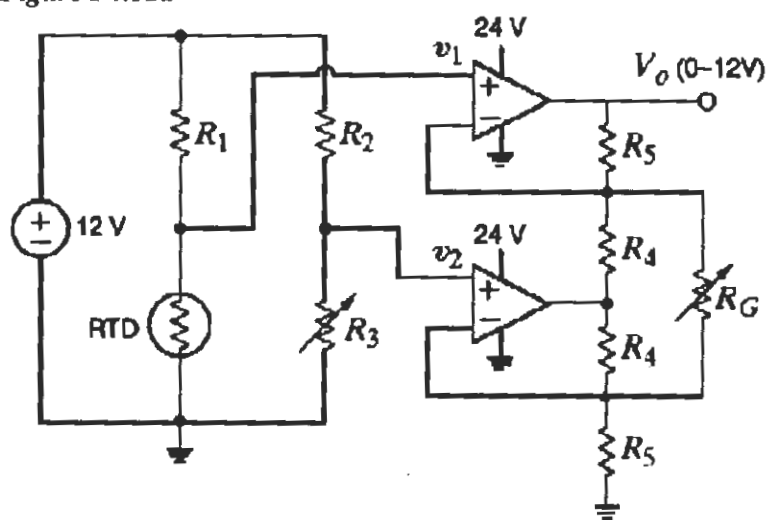


Figure P4.52b

Solution: 4.52

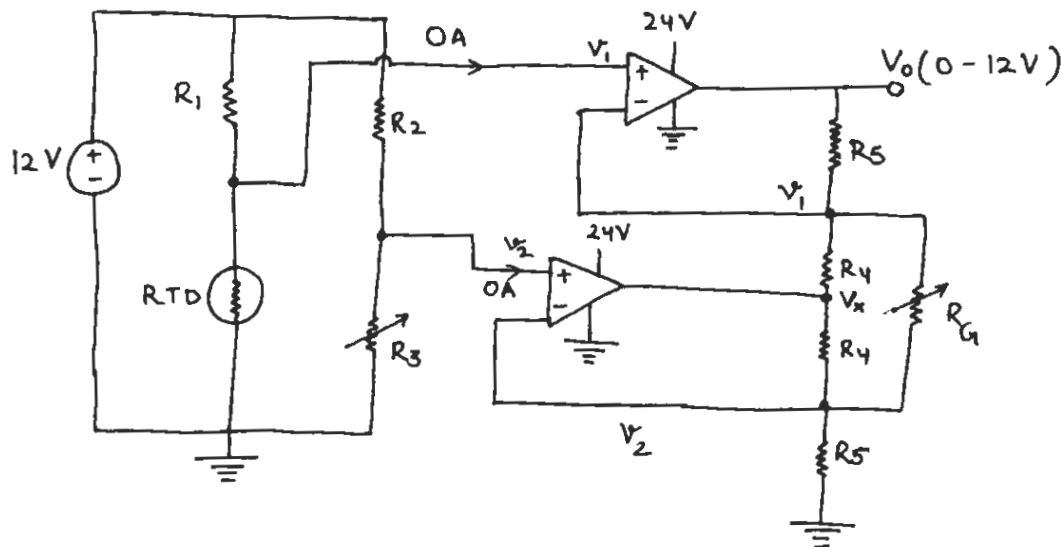

$$\text{KCL at } R_{RTD} : \frac{12 - V_1}{R_1} = \frac{V_1}{R_{RTD}}$$

$$\Rightarrow 12 R_{RTD} = V_1 (R_1 + R_{RTD})$$

$$V_1 = \frac{12 R_{RTD}}{(R_1 + R_{RTD})} \quad \text{--- (1)}$$

$$\text{KCL at } V_2 : V_2 = \frac{12 R_3}{R_2 + R_3} \quad \text{--- (2)}$$

$$R_{RTD}(T) : R_{RTD} = K_1 + K_2 T$$

$$\text{At } T = 0^\circ\text{C}, R_{RTD} = K_1 = 100 \Omega$$

$$\text{At } T = 500^\circ\text{C}, R_{RTD} = 600 \Omega = 100 + K_2(500)$$

$$K_2 = 1 \Omega / ^\circ\text{C}$$

$$\Rightarrow R_{RTD} = 100 + T \quad \text{--- (3)}$$

$$\text{We have } R_1 = R_2 = R_3 = 100 \Omega$$

$$\text{Now } \frac{12 - V_1}{100} = \frac{V_1}{100 + T}$$

$$\Rightarrow 12 - V_1 = \frac{V_1}{1 + T/100} \quad \text{--- (4)}$$

Substituting  $R_2 = R_3 = 100 \Omega$  in equation (2), we get

$$V_2 = \frac{12 \times 100}{100 + 100} = 6 \text{ V}$$

KCL at  $v_1$  at  $R_4 - R_5$  node:

$$\frac{v_o - v_1}{R_5} = \frac{v_1 - v_2}{R_G} + \frac{v_1 - v_x}{R_4} \quad \text{---} \quad (5)$$

KCL at  $v_2$  at  $R_5 - R_4$  node:

$$\frac{v_x - v_2}{R_4} + \frac{v_1 - v_2}{R_G} = \frac{v_2}{R_5} \quad \text{---} \quad (6)$$

We have  $R_4 = R_5 = 4 \text{ k}\Omega$

From equation (5), we get

$$\frac{v_o - v_1}{R_4} = \frac{v_1 - v_2}{R_G} + \frac{v_1 - v_x}{R_4} \quad \text{---} \quad (7)$$

From equation (6), we get

$$\frac{v_x - v_2}{R_4} + \frac{v_1 - v_2}{R_G} = \frac{v_2}{R_4} \quad \text{---} \quad (8)$$

From equations (7) and (8), we get

$$v_o = 24 \left( \frac{100 + T}{200 + T} - \frac{1}{2} \right) \left( 1 + \frac{R_4}{R_G} \right)$$

At  $T = 0$ ,  $v_o = 0 \text{ V}$


At  $T = 500^\circ \text{C}$

$$v_o = 24 \left( \frac{600}{700} - \frac{1}{2} \right) \left( 1 + \frac{4 \times 10^4}{R_G} \right) = 12$$

$$\boxed{R_G = 10 \text{ k}\Omega}$$

**4FE-1** Given the summing amplifier shown in Fig. 4PFE-1, select the values of  $R_2$  that will produce an output voltage of  $-3$  V.

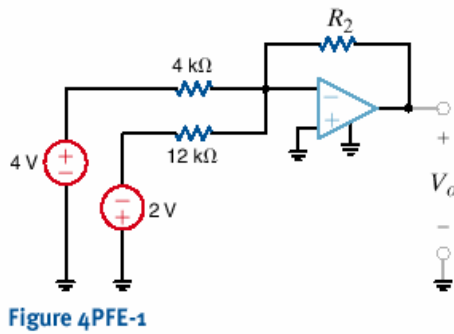- a.  $4.42 \text{ k}\Omega$       b.  $6.33 \text{ k}\Omega$   
c.  $3.6 \text{ k}\Omega$       d.  $5.14 \text{ k}\Omega$



### SOLUTION:

The correct answer is *c*.

$$V_o = \left( \frac{-R_2}{4k} \right) (4) - \left( \frac{R_2}{12k} \right) (-2)$$

$$V_o = -3V$$

$$-3 = -1m(R_2) + \frac{1}{6}m(R_2)$$

$$-\frac{5}{6}m(R_2) = -3$$

$$R_2 = 3.6k\Omega$$

**4FE-2** Determine the output voltage  $V_o$  of the summing op-amp circuit shown in Fig. 4PFE-2.

- a. 6 V                      b. 18 V  
c. 9 V                      d. 10 V


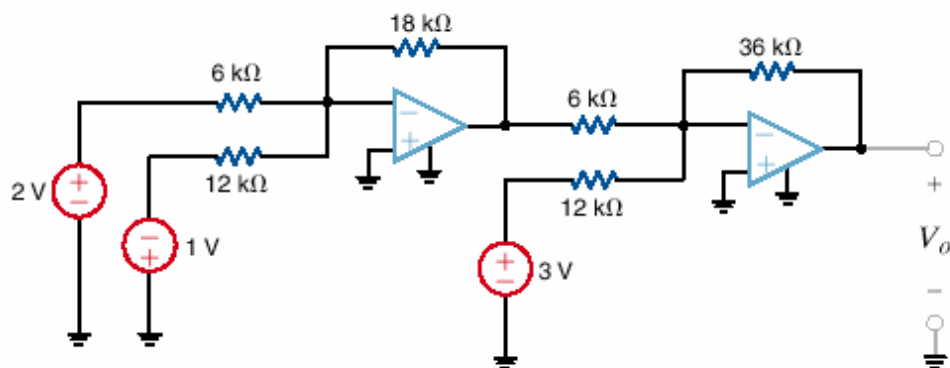


Figure 4PFE-2

**SOLUTION:**

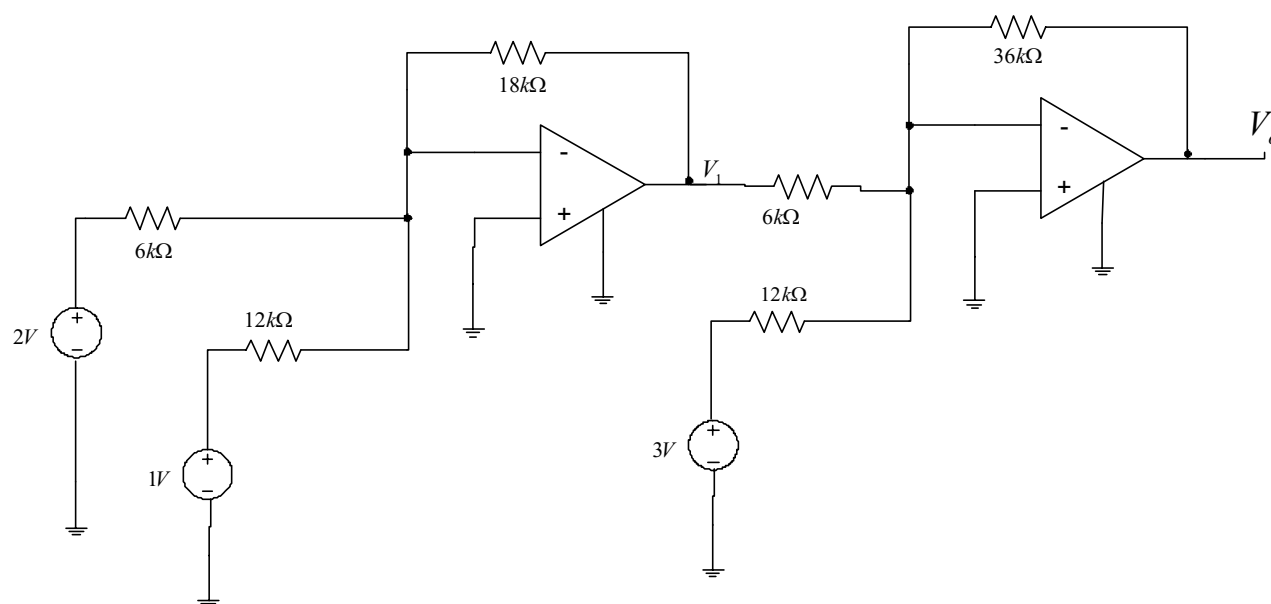

The correct answer is *b*.

$$V_1 = -2\left(\frac{18k}{6k}\right)(4) + 1\left(\frac{18k}{12k}\right) = -4.5V$$

$$V_o = -V_1\left(\frac{36k}{6k}\right) - 3\left(\frac{36k}{12k}\right)$$

$$V_o = 4.5\left(\frac{36k}{6k}\right) - 3\left(\frac{36k}{12k}\right)$$

$$V_o = 18V$$

**4FE-3** What is the output voltage  $V_o$  in Fig. 4PFE-3?

- a.  $-5\text{ V}$                       b.  $6\text{ V}$   
c.  $4\text{ V}$                          d.  $-7\text{ V}$


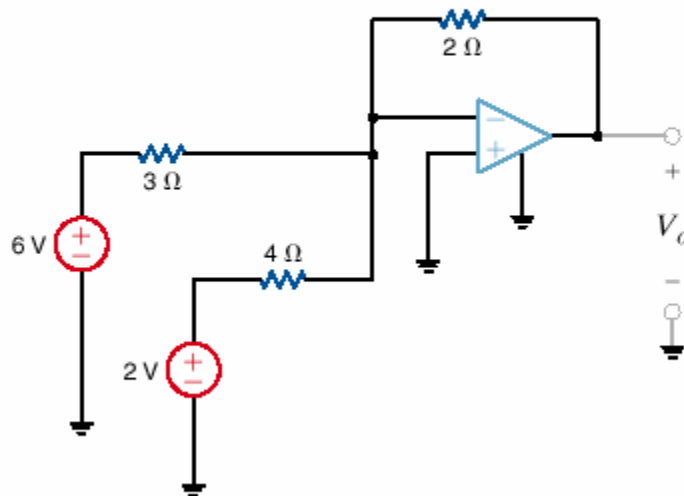


Figure 4PFE-3

**SOLUTION:**

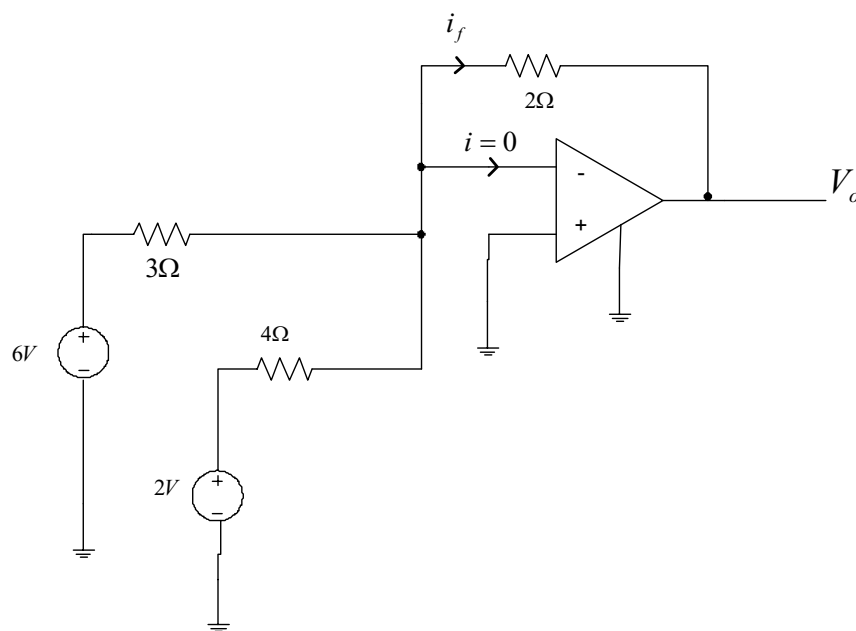

The correct answer is *a*.

$$i_f = \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{6}{3} + \frac{2}{4} = 2.5\text{ A}$$

$$V_o = -i_f R_f = -(2.5)(2)$$

$$V_o = -5\text{ V}$$

**4FE-4** What value of  $R_f$  in the op-amp circuit of Fig. 4PFE-4 is required to produce a voltage gain of 50?

- a. 135 k $\Omega$
- b. 210 k $\Omega$
- c. 180 k $\Omega$
- d. 245 k $\Omega$

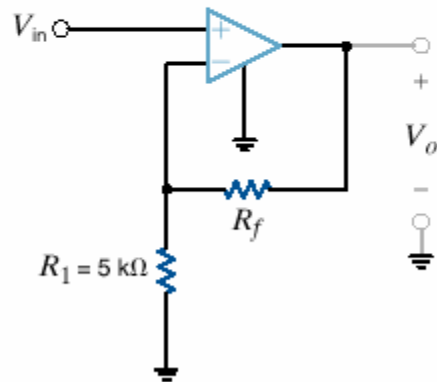


Figure 4PFE-4

### SOLUTION:

The correct answer is *d*.

The op-amp is a noninverting op-amp.

$$A = 1 + \frac{R_f}{R_1}$$

$$R_f = (A - 1)R_1$$

$$R_f = (50 - 1)5k = 245k\Omega$$



**4FE-5** What is the voltage  $V_o$  in the circuit in Fig. 4PFE-5?

- a. 3 V
- b. 6 V
- c. 8 V
- d. 5 V


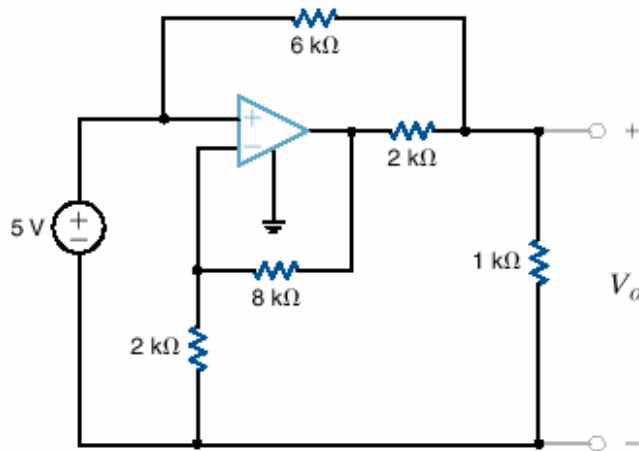


Figure 4PFE-5

**SOLUTION:**

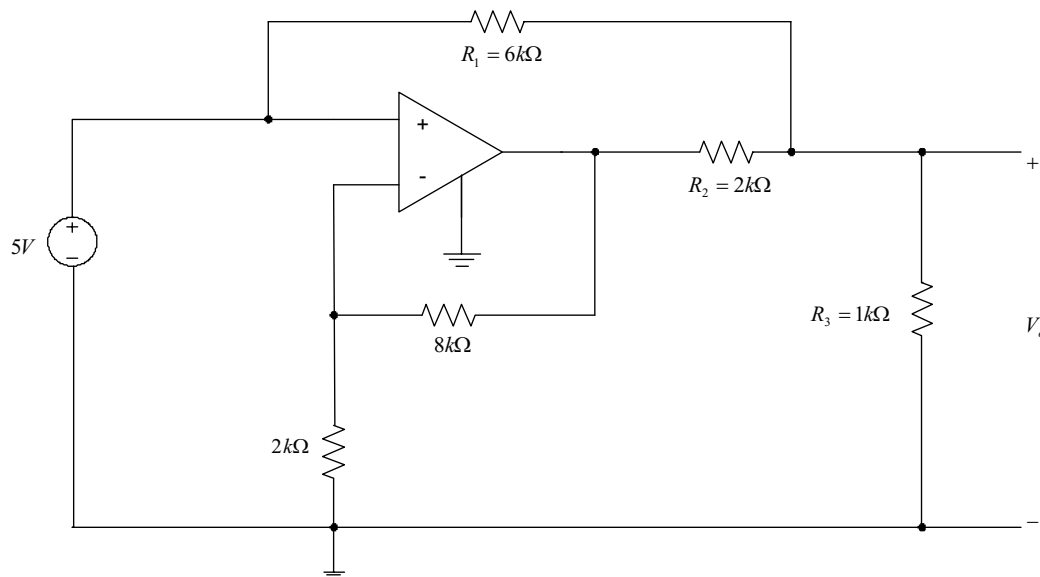

The correct answer is *c*.

The  $8k\Omega$  and  $2k\Omega$  resistors make up a noninverting op-amp.

$$V_1 = \left(1 + \frac{8k}{2k}\right)5 = 25V$$

Use nodal analysis at node A:

$$\frac{V_o}{R_3} + \frac{V_o - V_i}{R_1} + \frac{V_o - 25}{2k} = 0$$

$$\frac{V_o}{1k} + \frac{V_o - 5}{6k} + \frac{V_o - 25}{2k} = 0$$

$$6V_o + V_o - 5 + 3V_o - 75 = 0$$

$$10V_o = 80$$

$$V_o = 8V$$

5.1 Find  $I_o$  in the network in Fig. P5.1 using linearity and the assumption that  $I_o = 1$  mA.


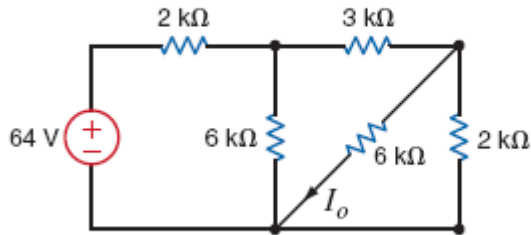


Figure P5.1

**SOLUTION:**

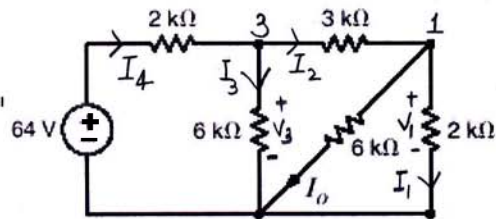

Assume  $I_o = 1$  mA

$$V_1 = I_o (6k) = 1m(6k) = 6V$$

$$I_1 = \frac{6}{2k} = 3mA$$

$$\text{KCL at 1: } I_2 = I_o + I_1$$

$$I_2 = 1m + 3m = 4mA$$

KVL around right outer loop:

$$V_3 = I_2(3k) + V_1 = 4m(3k) + 6 = 18V$$

$$\text{KCL at 3: } I_4 = I_3 + I_2$$

$$I_4 = \frac{V_3}{6k} + 4m = \frac{18}{6k} + 4m = 7mA$$

KVL around left loop:


$$V_s = I_4(2k) + V_3 = 2k(7m) + 18 = 32V$$

The actual value is  $V_s = 64V$

$$\frac{32}{1m} = \frac{64}{x}$$


$$x = \frac{64}{32}(1m) = I_o = 2mA$$

5.2 Find  $I_o$  in the network in Fig. P5.2 using linearity and the assumption that  $I_o = 1$  mA.

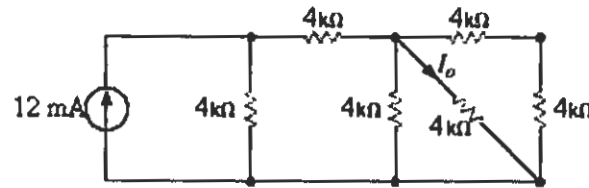

**Figure P5.2**

**Solution:** 5.2

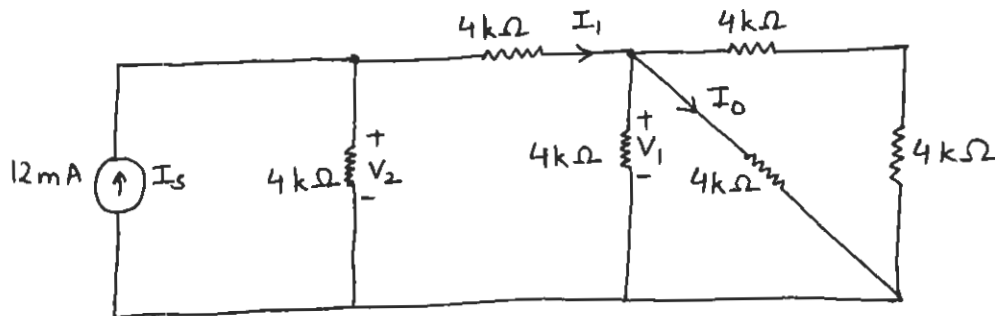

$$\text{If } I_o = 1 \text{ mA}, V_1 = I_o(4000) = 4 \text{ V}$$

$$I_1 = \frac{V_1}{4000} + I_o + \frac{V_1}{8000} = 2.50 \text{ mA}$$

$$V_2 = 4000 I_1 + V_1 = 14.0 \text{ V}$$

$$I_s = \frac{V_2}{4000} + I_1 = 6.00 \text{ mA}$$

But  $I_s$  actually equals 12 mA

$$\text{So, } I_o = 10^{-3} \times \frac{12 \times 10^{-3}}{6 \times 10^{-3}}$$

$$\boxed{I_o = 2.00 \text{ mA}}$$

5.3 Find  $I_o$  in the network in Fig. P5.3 using linearity and the assumption that  $I_o = 1$  mA.


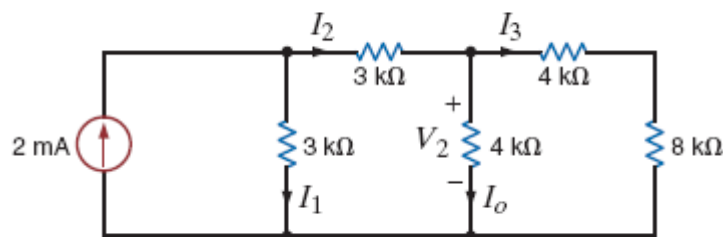


Figure P5.3

**SOLUTION:**

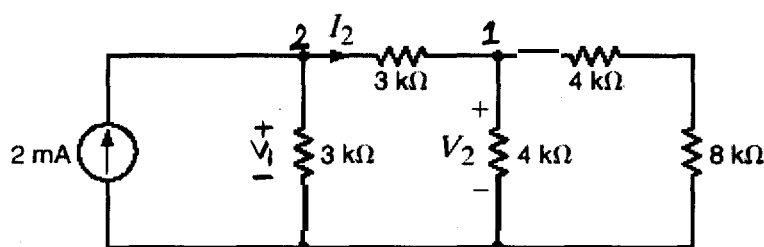

Assume  $I_o = 1$  mA.

$$V_2 = 4k(I_o) = 4k(1m) = 4V$$

$$\text{KCL at 1: } I_2 = I_3 + I_o$$

$$I_2 = \frac{V_2}{12k} + 1m = \frac{4}{12k} + 1m = 1.33mA$$

KVL around middle loop:

$$V_1 = I_2(3k) + V_2 = 1.33m(3k) + 4 = 8V$$


$$\text{KCL at 2: } I_s = I_1 + I_2$$

$$I_s = \frac{V_1}{3k} + 1.33m = \frac{8}{3k} + 1.33m = 4mA$$

Actually,  $I_s = 2mA$ .


$$I_o = 1m \left( \frac{2m}{4m} \right) = 0.5mA$$

5.4 Find  $V_o$  in the network in Fig. P5.4 using linearity and the assumption that  $V_o = 1$  V.

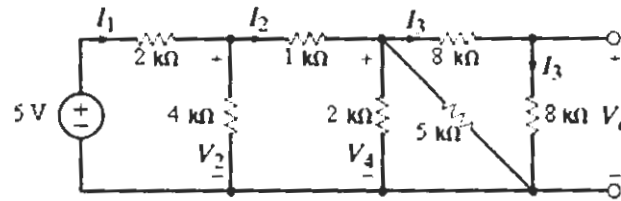

**Figure P5.4**

**Solution:** 5.4

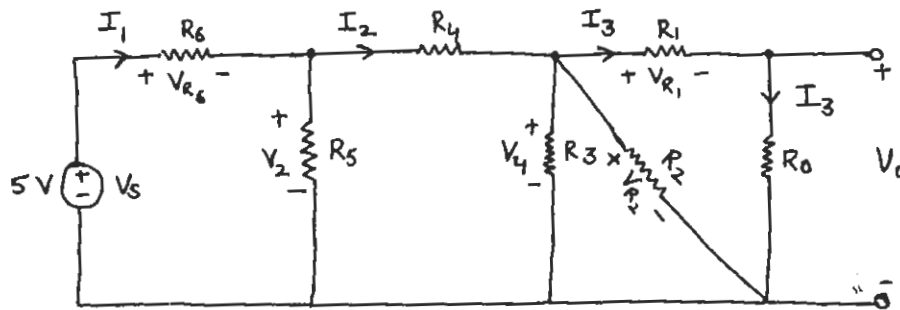

$$R_0 = R_1 = 8 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = R_6 = 2 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega, R_5 = 4 \text{ k}\Omega$$

$$\text{If } V_o = 1 \text{ V}, I_3 = \frac{V_o}{R_0} = \frac{1}{8} \text{ mA}$$

$$V_{R_1} = I_3 R_1 = 1 \text{ V}$$

$$V_{R_2} = V_{R_1} + V_o = 2 \text{ V}, I_{R_2} = 0.40 \text{ mA}$$

$$V_4 = V_{R_2} = 2 \text{ V},$$

$$I_2 = \frac{V_4}{R_3} + \frac{V_{R_2}}{R_2} + I_3 = 1.53 \text{ mA}$$

$$V_2 = I_2 R_4 + V_4 = 3.53 \text{ V}$$

$$I_1 = \frac{V_2}{R_5} + I_2 = 2.41 \text{ mA}$$

$$V_s = I_1 R_6 + V_2 = 8.35 \text{ V}$$

But  $V_s$  actually equals 5V

$$\text{So, } V_o = (1) \frac{5}{8.35} = 0.598 \text{ V}$$

$$\boxed{V_o = 0.60 \text{ V}}$$

5.5 Find  $I_o$  in the network in Fig. P5.5 using superposition.



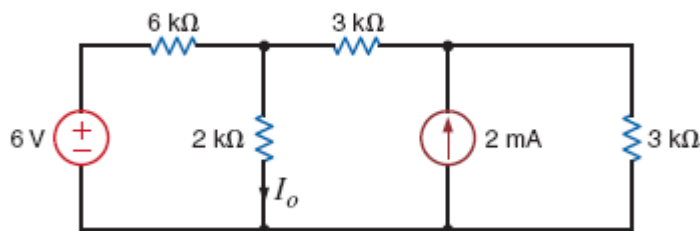


Figure P5.5

**SOLUTION:**

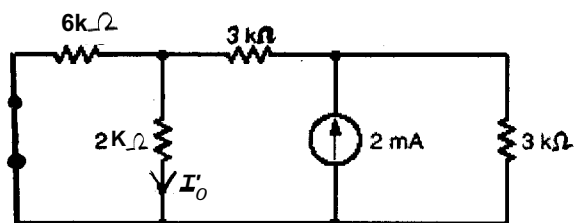


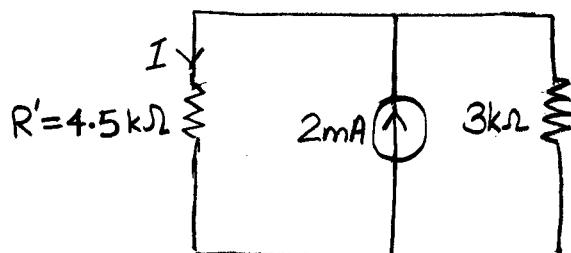
$$R' = (6k \parallel 2k) + 3k = 4.5k \Omega$$



$$I = \frac{3k}{3k + 4.5k} (2m) = 0.8mA$$
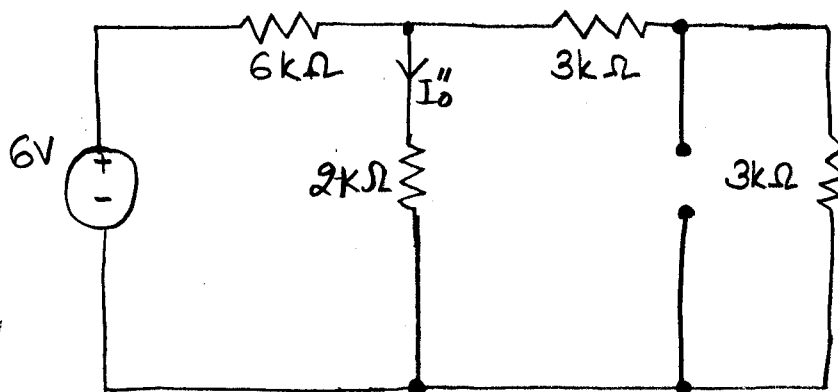
$$I_o' = \frac{6k}{6k + 2k} (0.8m) = 0.6mA$$



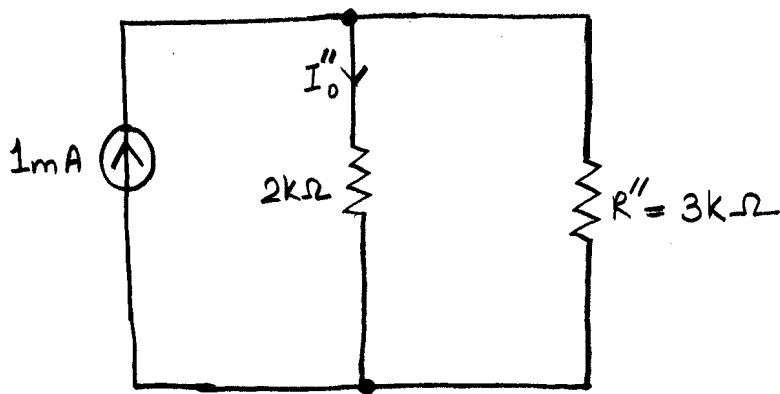

$$R'' = (6k \parallel (3k + 3k)) = 3k\Omega$$

$$I''_0 = \left( \frac{3k}{2k + 3k} \right) (1m) = 0.6mA$$

$$I_0 = 0.6m + 0.6m = 1.2mA$$



5.6 In the network in Fig. P5.6 find  $I_o$  using superposition.



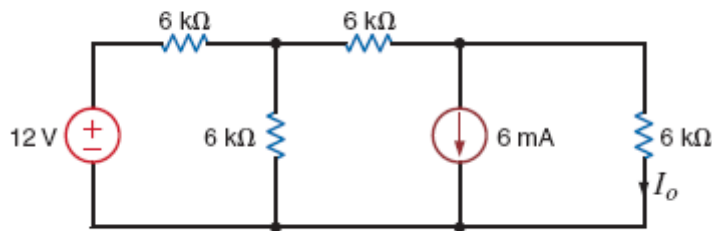


Figure P5.6



**SOLUTION:**

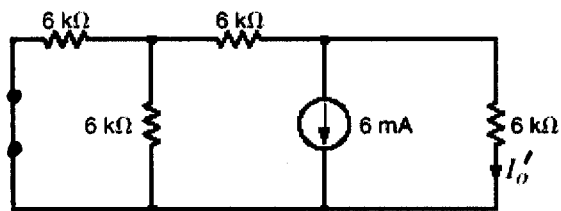
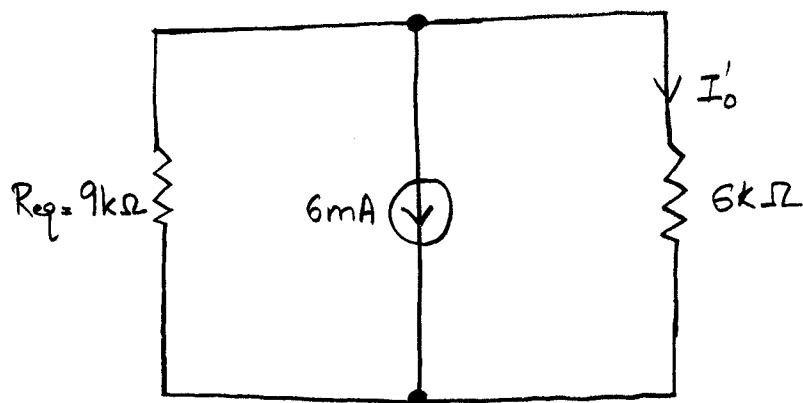
$$R_{eq} = (6k \parallel 6k) + 6k = 9k \Omega$$


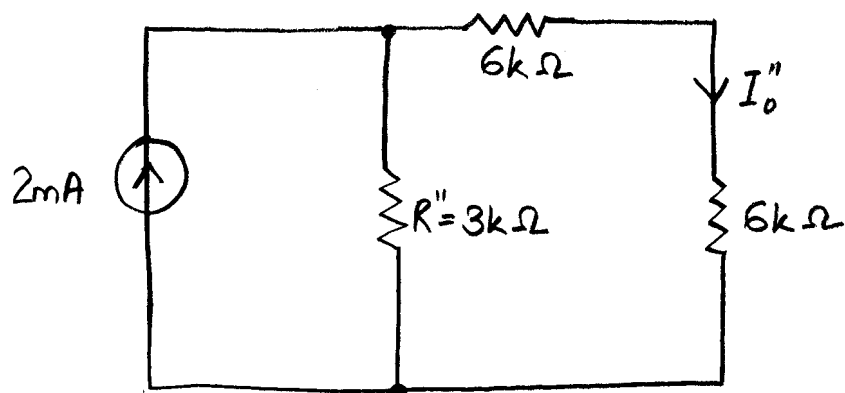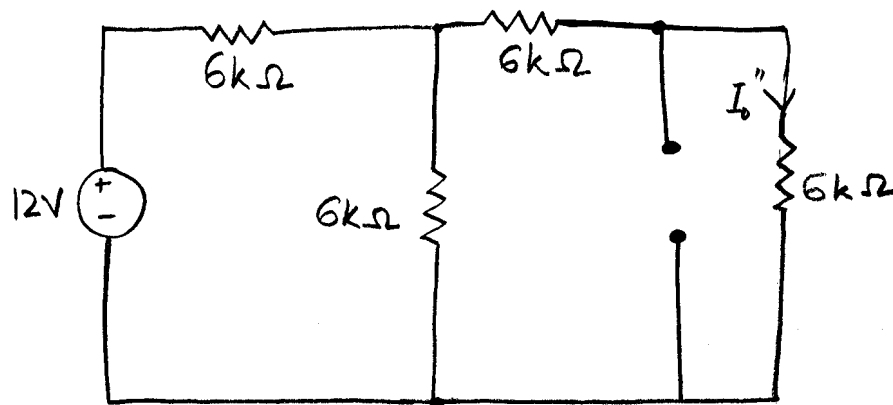
$$I'_o = \left( \frac{9k}{9k + 6k} \right) (-6m) = -3.6mA$$



$$R'' = (6k \parallel 6k) = 3k\Omega$$

$$I_o'' = \left( \frac{3k}{3k + 6k + 6k} \right) (2m) = 0.4mA$$

$$I_o = -3.6m + 0.4m = -3.2mA$$

5.7 Find  $I_o$  in the circuit in Fig. P5.7 using superposition.



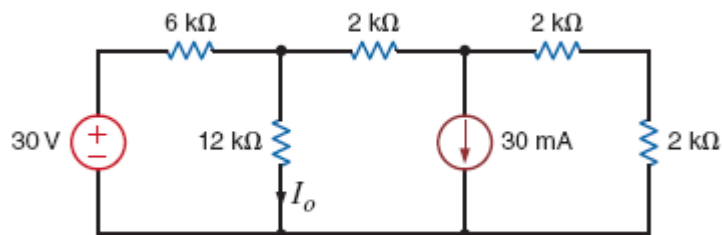
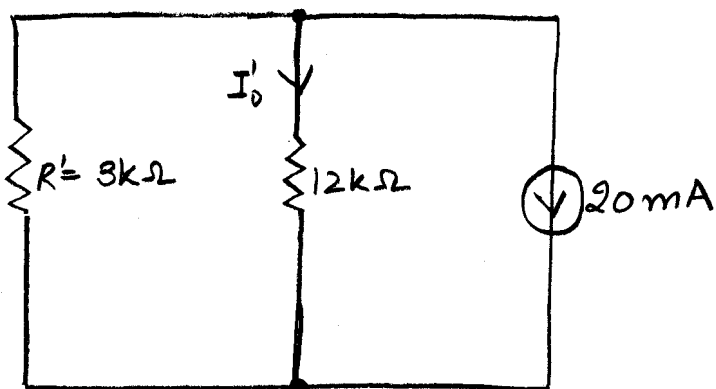
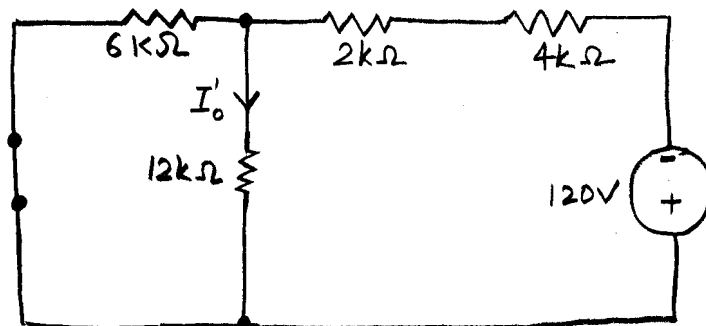


Figure P5.7

**SOLUTION:**

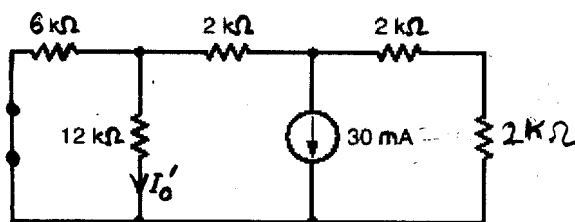
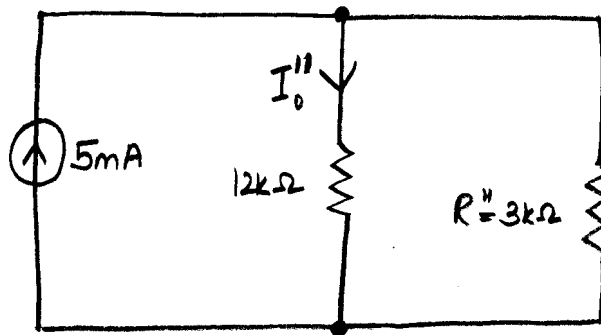
$$I_o' = \left( \frac{3k}{3k + 12k} \right) (-20m) = -4mA$$




$$R'' = (6k \parallel (2k + 2k + 2k)) = 3k\Omega$$

$$I''_0 = \left( \frac{3k}{3k + 12k} \right) (5m) = 1mA$$


$$I_0 = -4m + 1m = -3mA$$

5.8 Find  $V_o$  in the network in Fig. P5.8 using superposition.

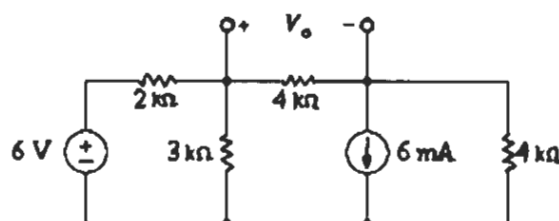


**Figure P5.8**

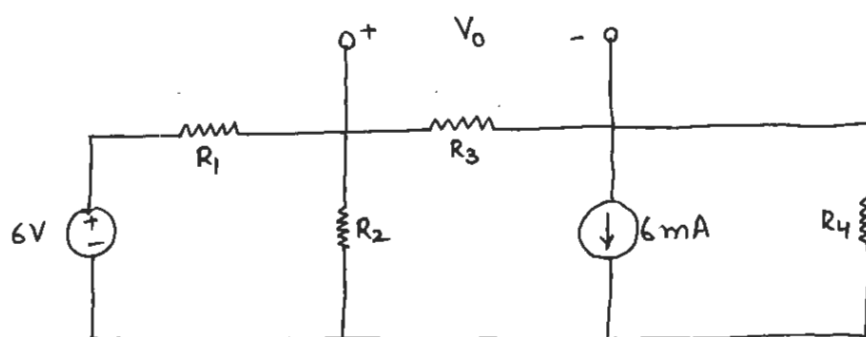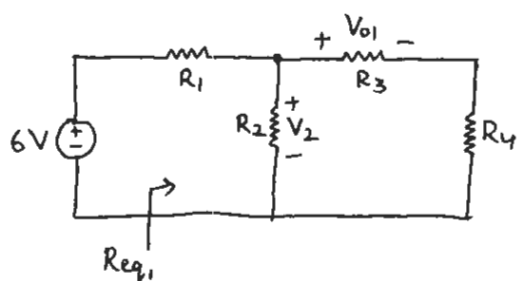**Solution:** 5.8



$$R_1 = 2\text{ k}\Omega, R_2 = 3\text{ k}\Omega, \\ R_3 = 4\text{ k}\Omega, R_4 = 4\text{ k}\Omega$$




$$R_{eq1} = R_2 \parallel (R_3 + R_4) = 2.18\text{ k}\Omega$$

$$V_2 = 6 \left[ \frac{R_{eq1}}{R_{eq1} + R_1} \right] = 3.13\text{ V}$$


$$V_{o1} = V_2 \left[ \frac{R_3}{R_3 + R_4} \right] = 1.565\text{ V}$$

$$V_o = V_{o1} + V_{o2}$$

$$\boxed{V_o = 12.0\text{ V}}$$

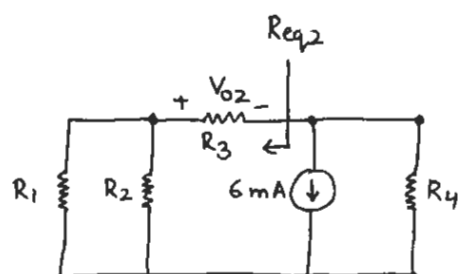
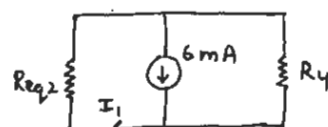
$$R_{eq2} = (R_1 \parallel R_2) + R_3 = 5.20\text{ k}\Omega$$



$$I_1 = 6 \times 10^{-3} \left[ \frac{R_4}{R_4 + R_{eq2}} \right]$$

$$I_1 = 2.61\text{ mA}$$

$$V_{o2} = I_1 R_3 = 10.44\text{ V}$$

5.9 Find  $V_o$  in the network in Fig. P5.9 using superposition.



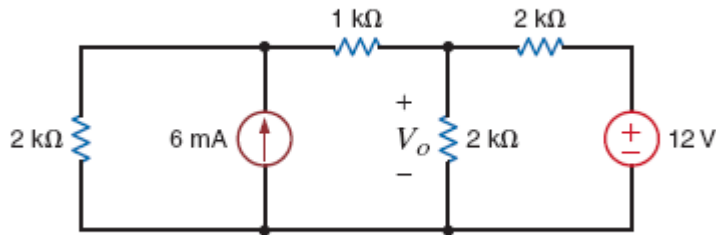


Figure P5.9

**SOLUTION:**

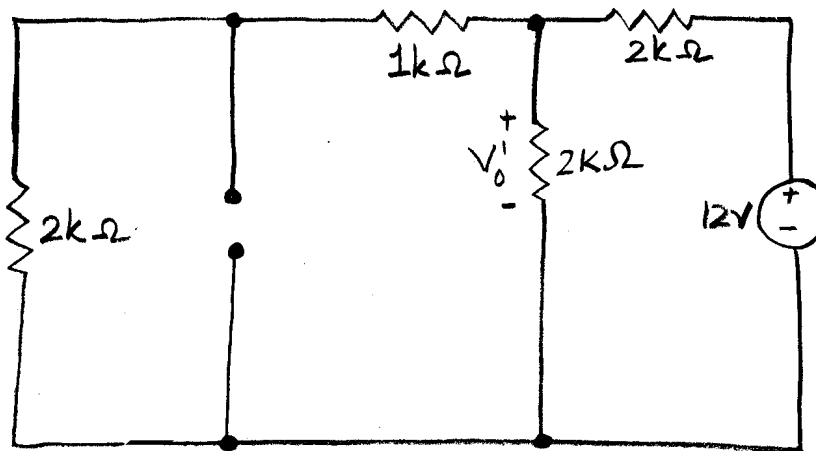


$$R' = 3k \parallel 2k = 1.2k\Omega$$

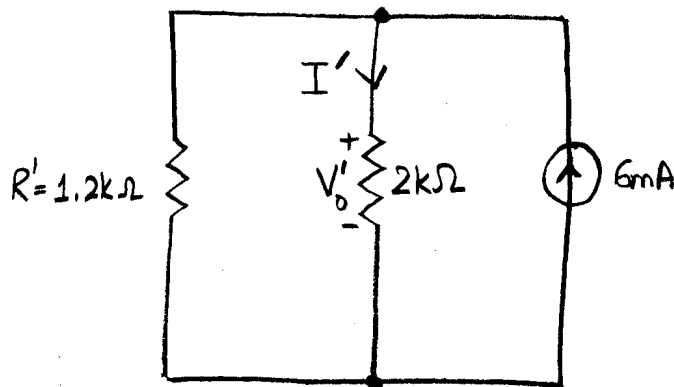


$$I' = \left( \frac{1.2k}{1.2k + 2k} \right) (6m) = 2.25mA$$

$$V'_o = 2k(2.25m) = 4.5V$$

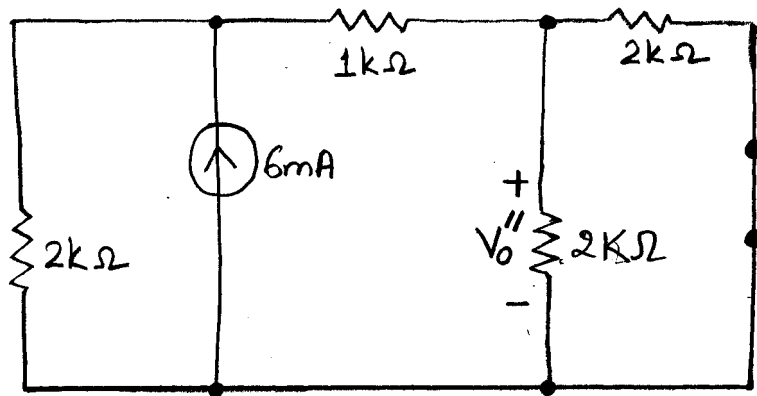

$$R'' = 3k \parallel 2k = 1.2k\Omega$$

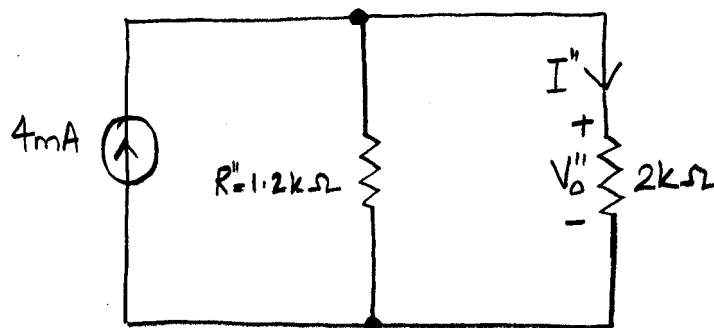

$$I'' = \left( \frac{1.2k}{1.2k + 2k} \right) (4m) = 1.5mA$$

$$V_o'' = 2k(1.5m) = 3V$$

$$V_o = 4.5 + 3 = 7.5V$$

5.10 Find  $V_o$  in the network in Fig. P5.10 using superposition.



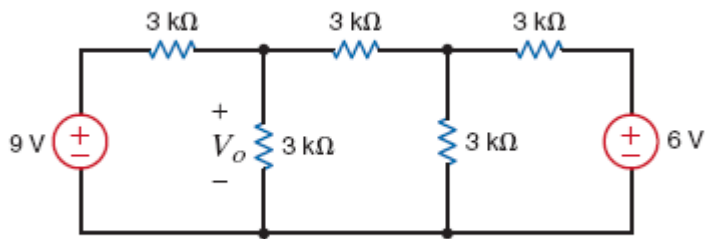
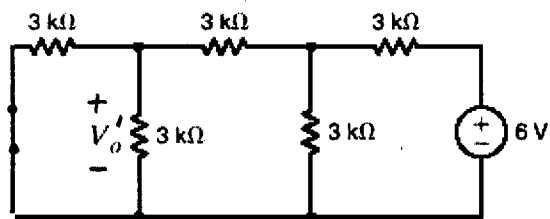


Figure P5.10

**SOLUTION:**

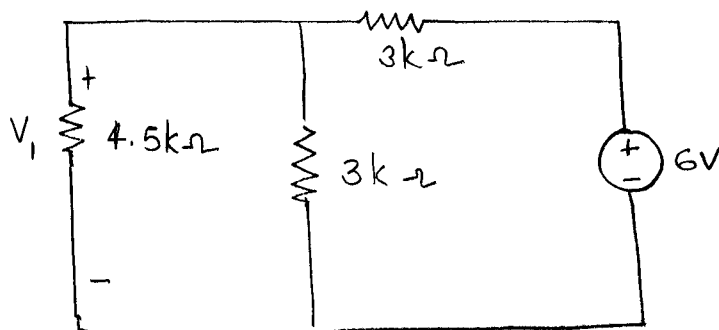


$$R' = 3k \parallel 3k = 1.5k\Omega$$

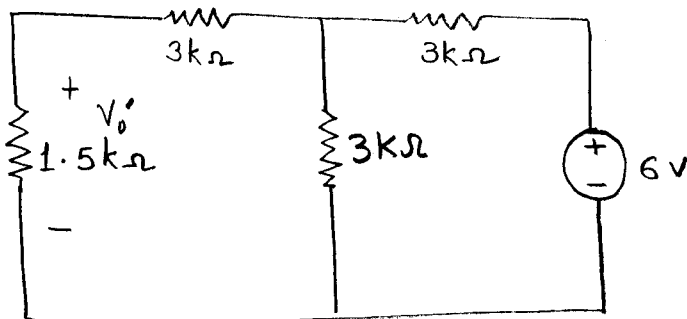

$$V_1 \times \frac{1.5}{4.5} = V_o'$$






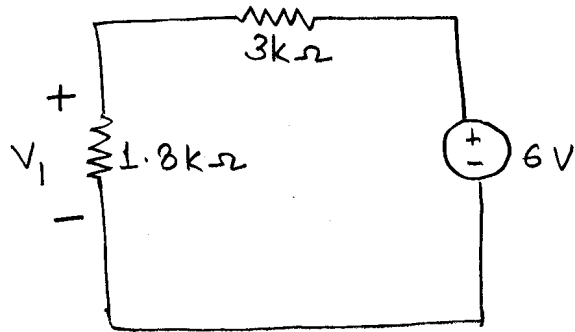


$$V_1 = 6 \times \frac{1.8}{4.8}$$

$$\therefore V_0' = 6 \times \frac{1.8}{4.8} \times \frac{1.5}{4.5} = 0.75V$$

Shorting 6V source

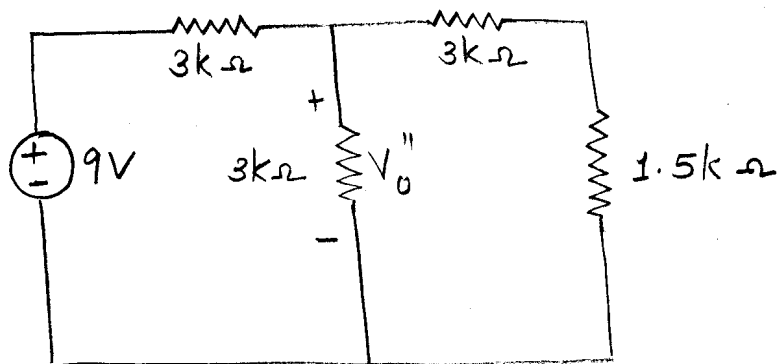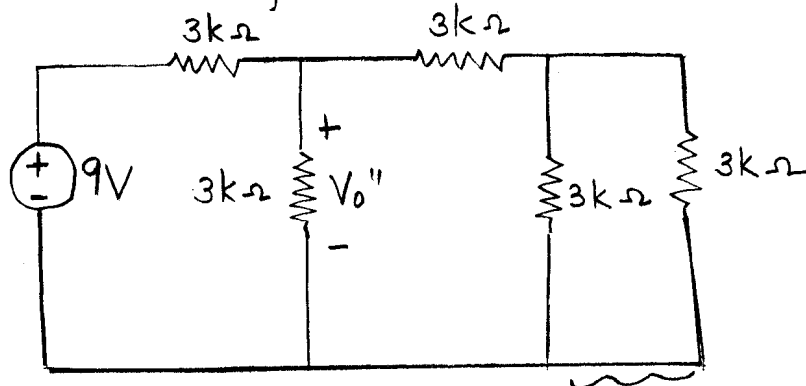

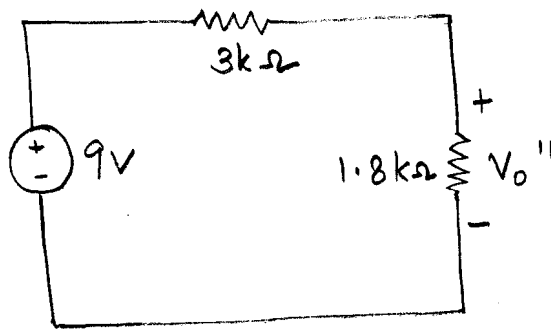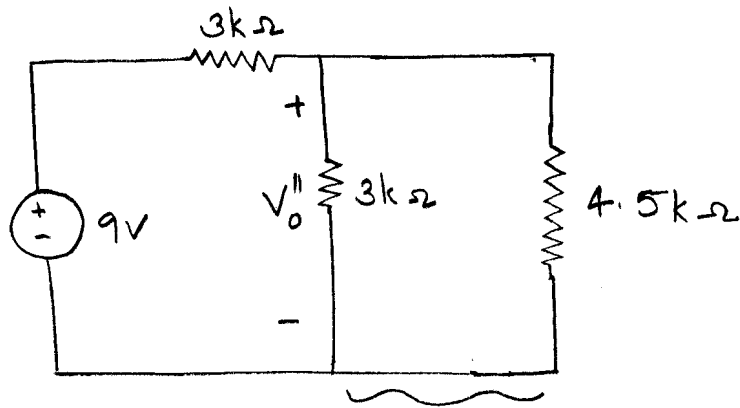

$$\therefore V_o'' = 9 \times \frac{1.8}{4.8} = 3.375 \text{ V} \\ \approx 3.38 \text{ V}$$

Using superposition

$$\boxed{\therefore V_o'' + V_o' = 3\text{V}}$$

5.11 Find  $I_o$  in the network in Fig. P5.11 using superposition.



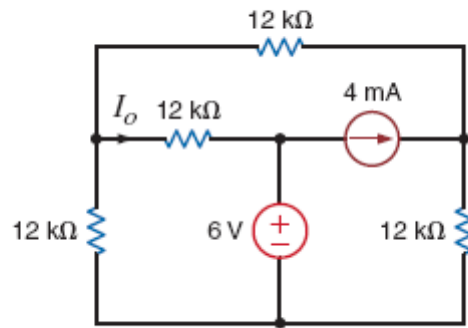
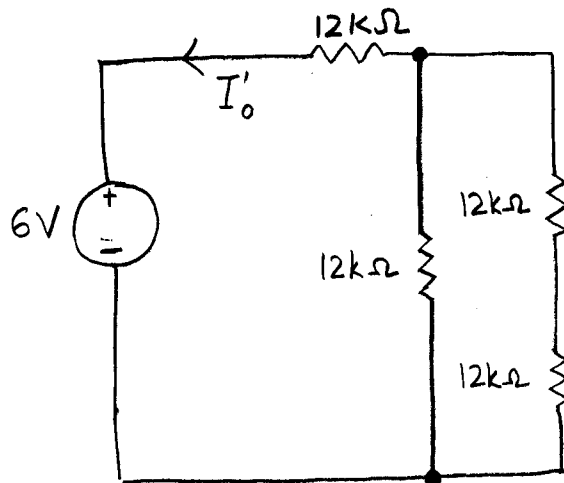


Figure P5.11




**SOLUTION:**

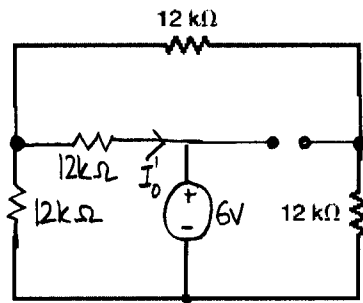


$$R_{eq} = ((12k + 12k) || 12k) + 12k = 20k\Omega$$

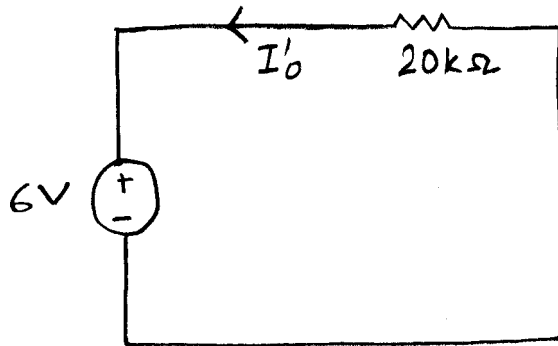
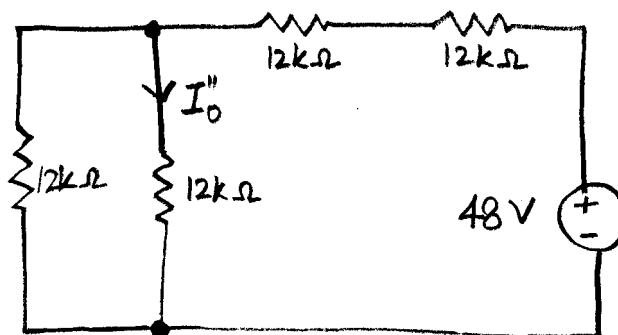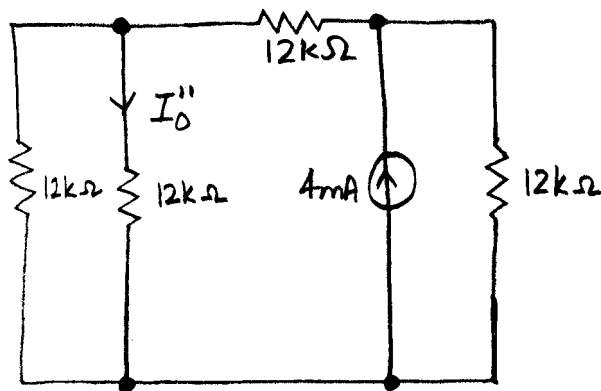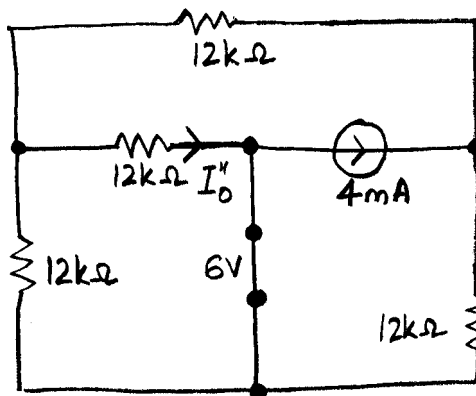
$$I'_0 = \frac{-6}{20k} = -0.3 \text{ mA}$$



$$R'' = 12k \parallel 24k = 8k\Omega$$

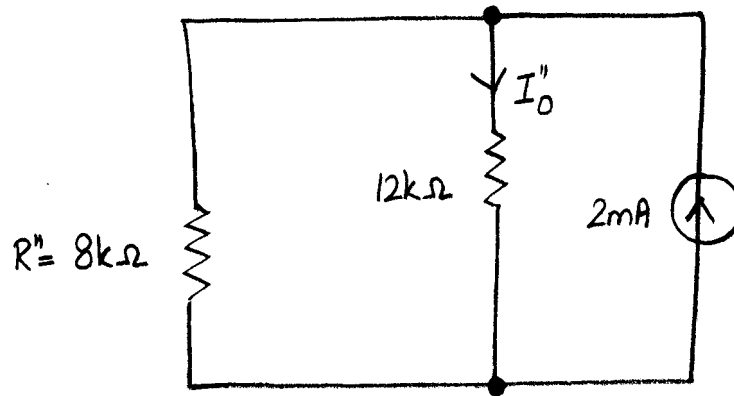

$$I_0' = \left( \frac{8k}{8k + 12k} \right) 2m = 0.8mA$$

$$I_0 = -0.3m + 0.8m = 0.5mA$$

5.12 Find  $I_o$  in the network in Fig. P5.12 using superposition.



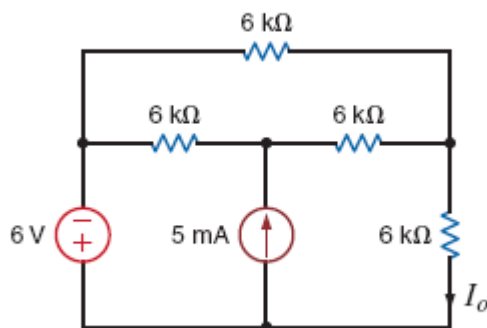
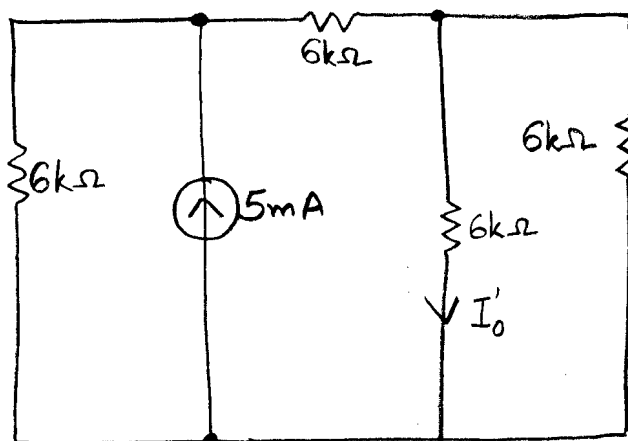


Figure P5.12


**SOLUTION:**

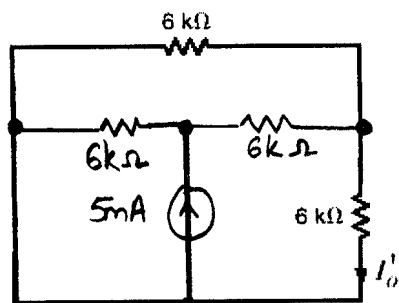




$$R' = 6k + 6k = 12k\Omega$$

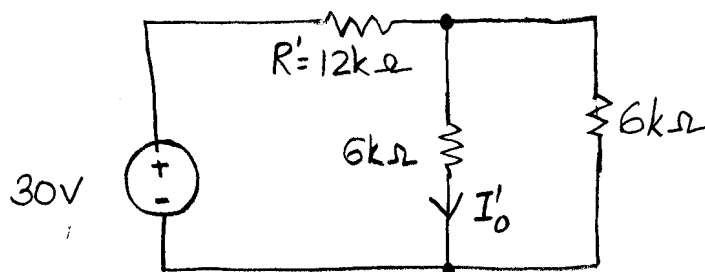

$$R'' = 6k \parallel 12k = 4k\Omega$$

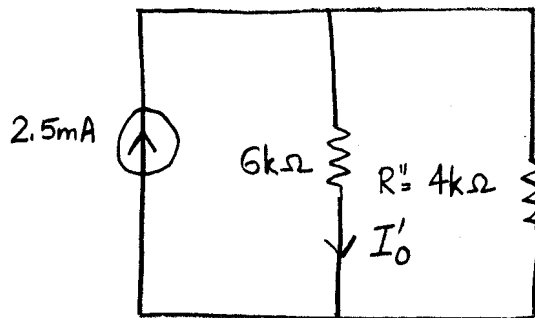
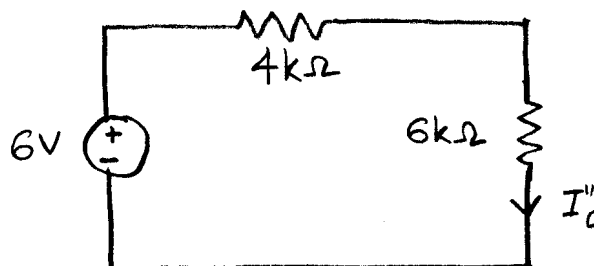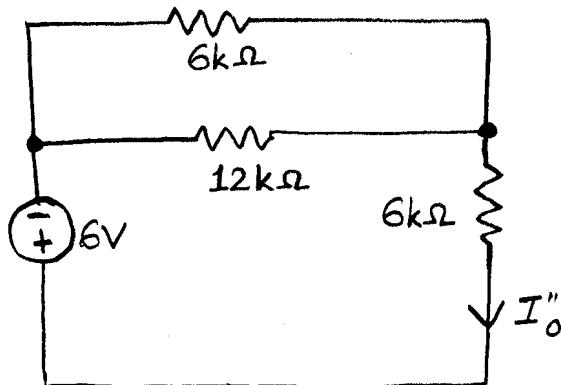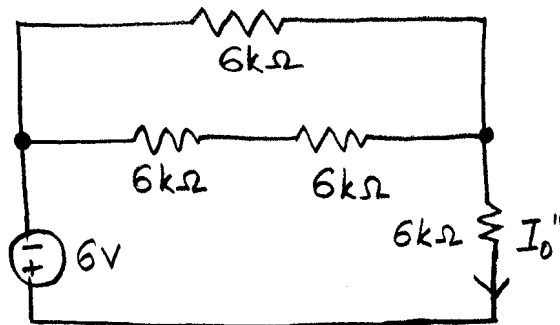
$$I'_0 = \left( \frac{4k}{4k + 6k} \right) (2.5\text{mA}) = 1\text{mA}$$



$$I_o' = \left( \frac{-6}{4k + 6k} \right) = -0.6mA$$

$$I_o = 1mA - 0.6mA = 0.4mA$$



5.13 Find  $I_A$  in the network in Fig. P5.13 using superposition.



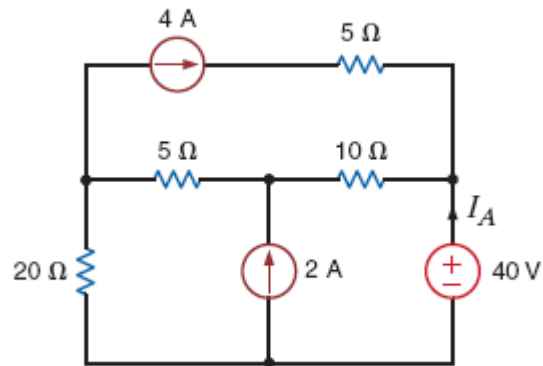


Figure P5.13


**SOLUTION:**

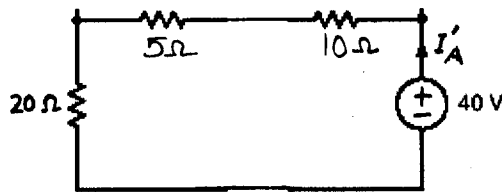
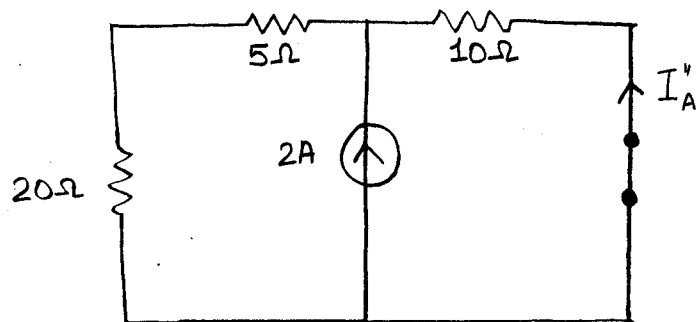
$$I'_A = \left( \frac{40}{20+5+10} \right) = \frac{8}{7} \text{ A}$$


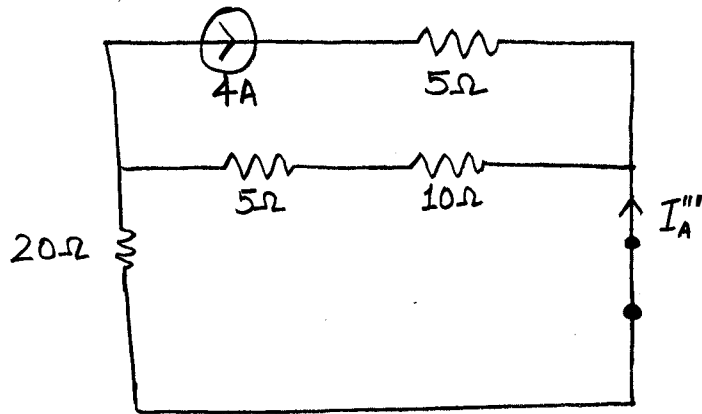
$$I''_A = \left( \frac{5+20}{20+5+10} \right) (-2) = -\frac{10}{7} \text{ A}$$



$$I_A'' = \left( \frac{5+10}{5+10+20} \right) (-4) = -\frac{12}{7} \text{ A}$$

$$I_A = \frac{8}{7} - \frac{10}{7} - \frac{12}{7} = -2 \text{ A}$$

5.14 Find  $I_A$  in the network in Fig. P5.14 using superposition.



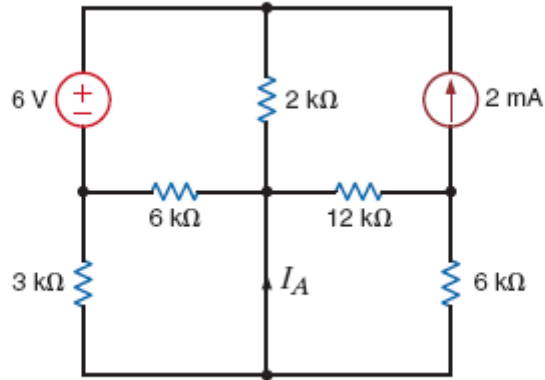
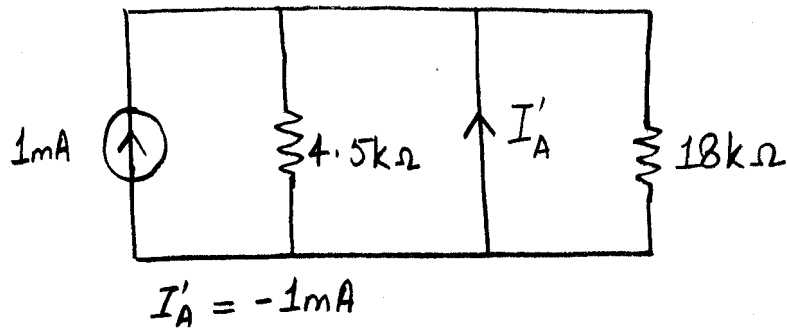
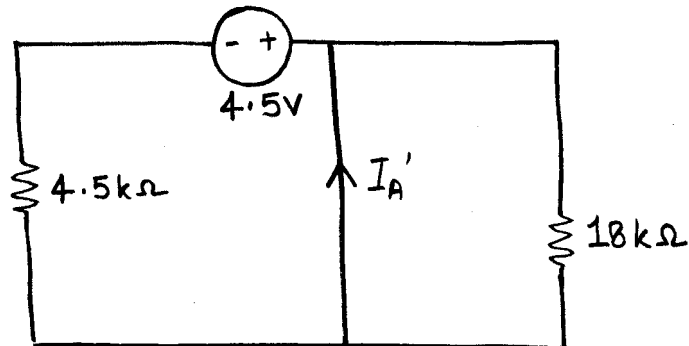


Figure P5.14

**SOLUTION:**

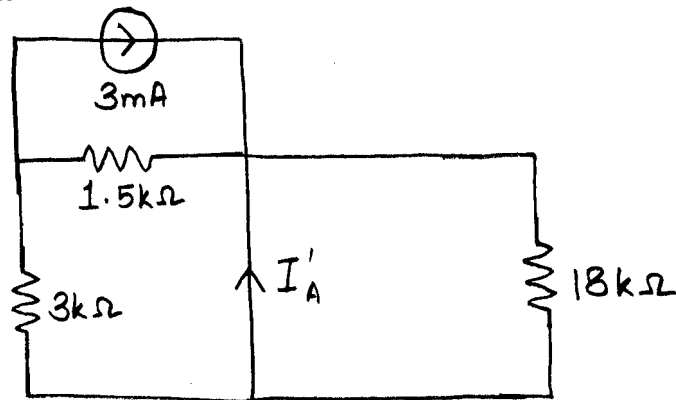

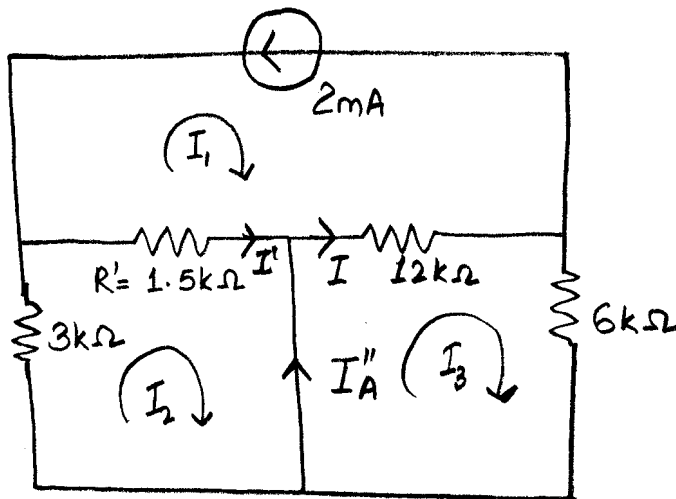

$$I_1 = -2\text{mA}$$

$$I_2 + I_A'' = I_3$$

$$I_A'' = I_3 - I_2$$

$$I_2 = I_1 + I'$$

$$I' = I_2 - I_1$$

$$I_1 + I = I_3$$

$$I = I_3 - I_1$$

KVL outer loop:

$$3I_2 + 1.5I' + 12kI + 6kI_3 = 0$$

$$4.5I_2 + 18kI_3 = -27$$

KVL right loop:

$$12kI + 6kI_3 = 0$$

$$18kI_3 = -24$$

$$I_3 = -1.33\text{mA}$$

$$4.5 I_2 + 18k(-1.33m) = -27$$

$$I_2 = -0.667mA$$


$$I_A'' = -1.33m + 0.667m$$

$$= -0.667mA$$

$$I_A = -1m - 0.667m$$


$$= -1.667mA$$

5.15 Find  $V_o$  in the circuit in Fig. P5.15 using superposition.

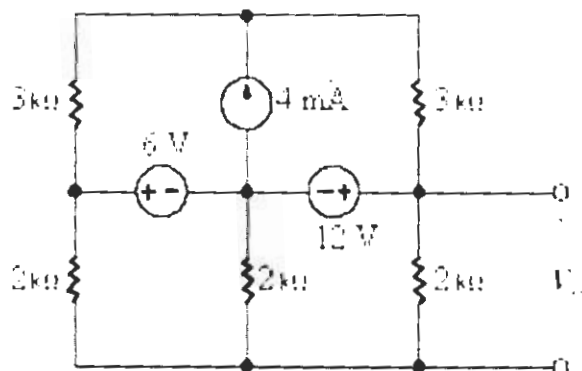


**Figure P5.15**

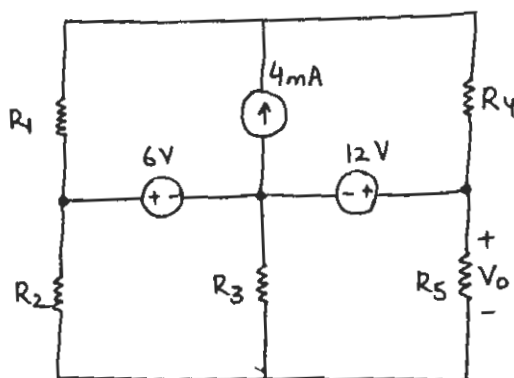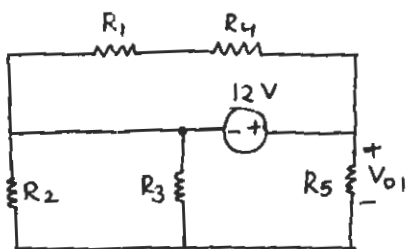**Solution:** 5.15




$$R_1 = R_4 = 3\text{ k}\Omega, R_2 = R_3 = R_5 = 2\text{ k}\Omega$$




$$R_A = R_2 \parallel R_3 = 1\text{ k}\Omega$$
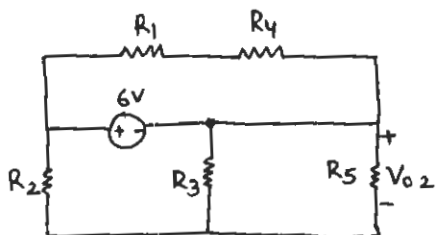
$$V_{o1} = 12 \cdot \frac{R_5}{R_A + R_5} = 8\text{ V}$$



$$R_B = R_3 \parallel R_5 = 1\text{ k}\Omega$$
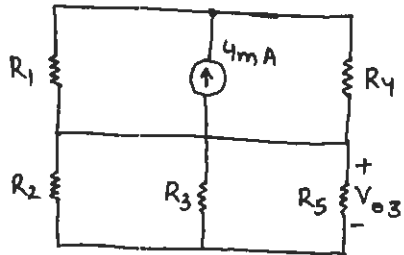
$$V_{o2} = -6 \cdot \frac{R_B}{R_B + R_2} = -2\text{ V}$$



$$V_{03} = 0 \text{ V}$$

$$V_0 = V_{01} + V_{02} + V_{03}$$

$$V_0 = 6 \text{ V}$$

5.16 Use superposition to find  $I_o$  in the network in Fig. P5.16.


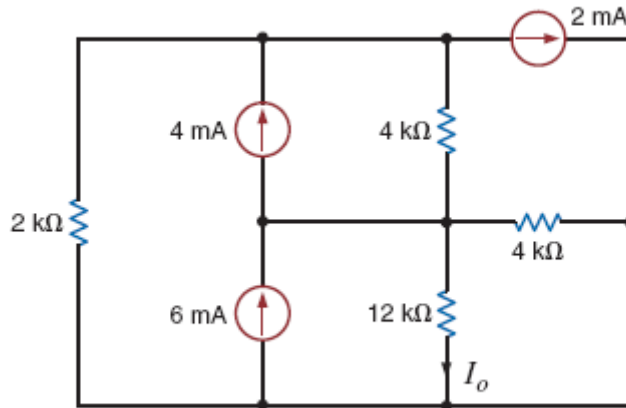



Figure P5.16

**SOLUTION:**


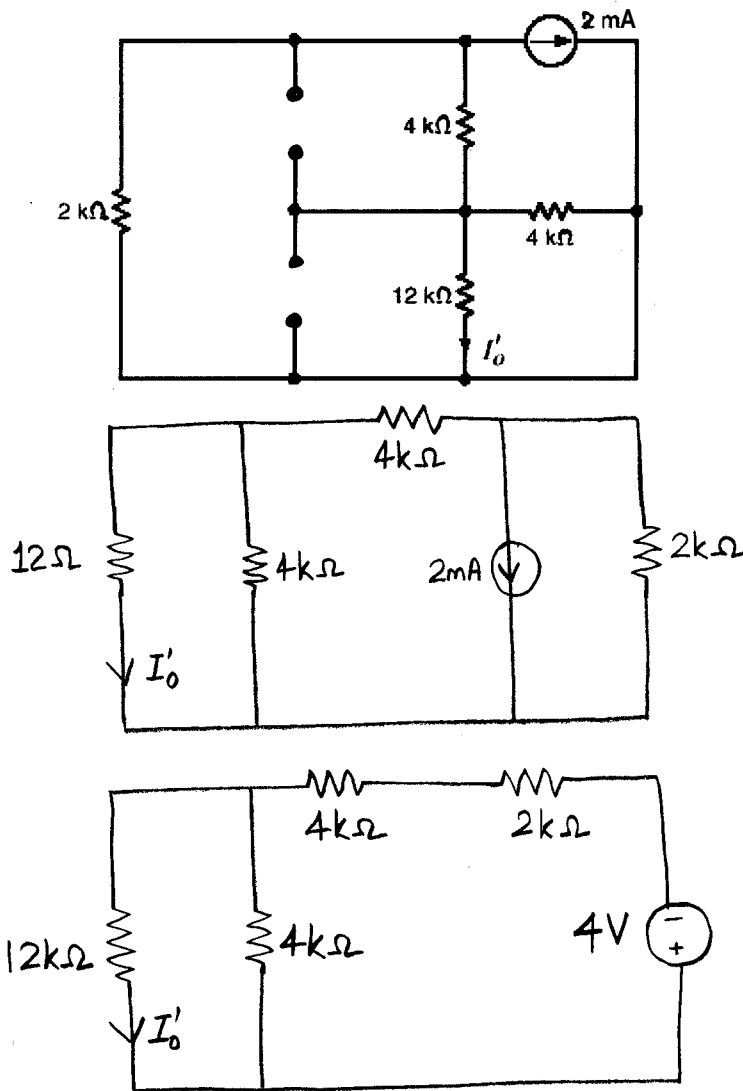





$$R' = 6k \parallel 4k = 2.4k\Omega$$

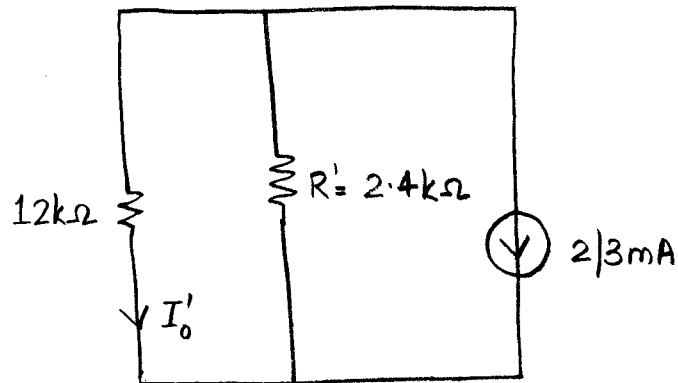

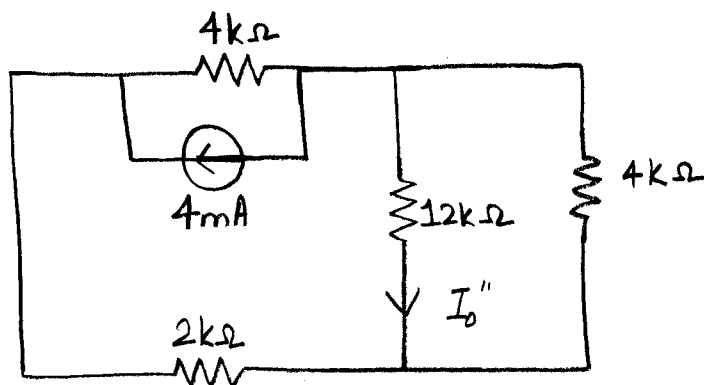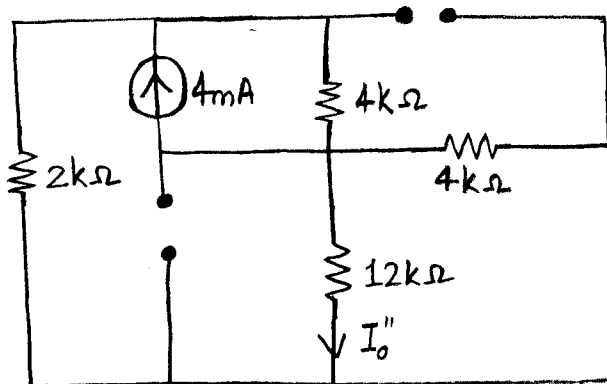
$$I'_0 = \left( \frac{-2.4k}{2.4k + 12k} \right) \left( \frac{2}{3} \text{ mA} \right) = -0.111 \text{ mA}$$



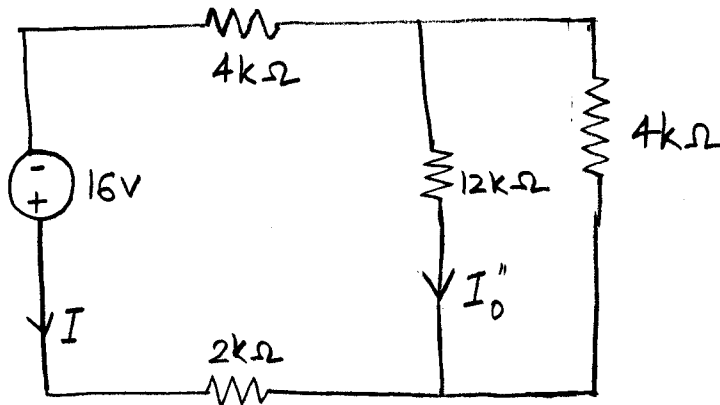

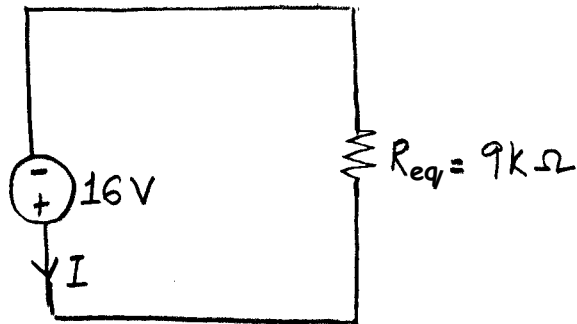
$$R_{eq} = 12k \parallel 4k + 6k = 9k\Omega$$




$$I = \frac{16}{9k} = 1.78mA$$
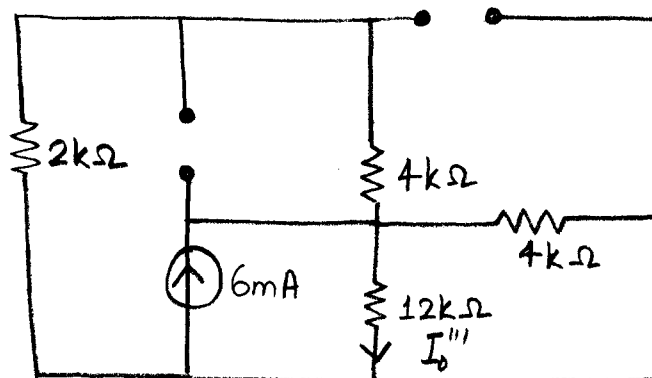
$$I_0'' = \left( \frac{4k}{12k + 4k} \right) (-1.78mA) = -0.445mA$$



$$R = 6k \parallel 4k = 2.4k\Omega$$

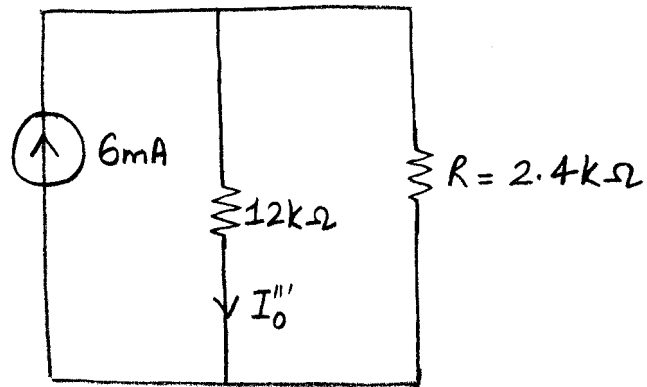

$$I_0'' = \left( \frac{2.4k}{2.4k + 12k} \right) (6m) = 1mA$$

$$I_0 = -0.111m - 0.445m + 1m = 0.444mA$$

5.17 Find  $I_o$  in the circuit in Fig. P5.17 using superposition.



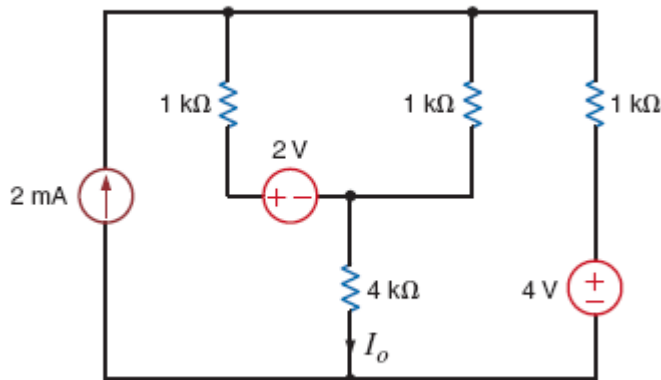
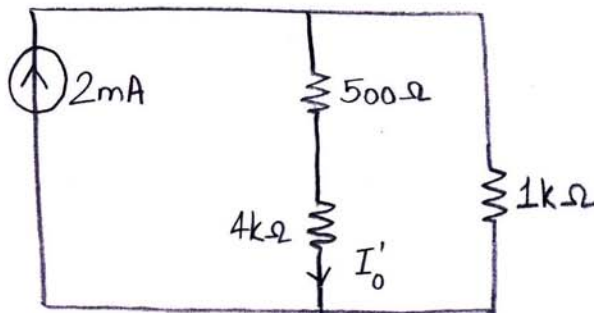
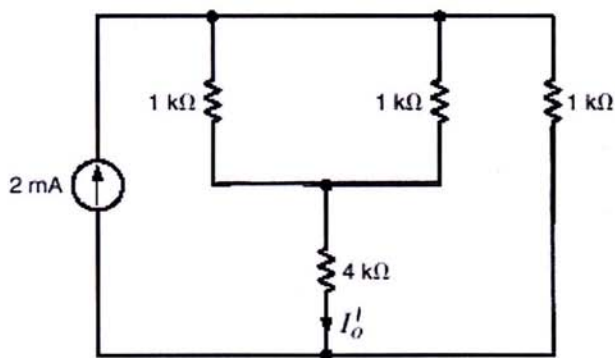
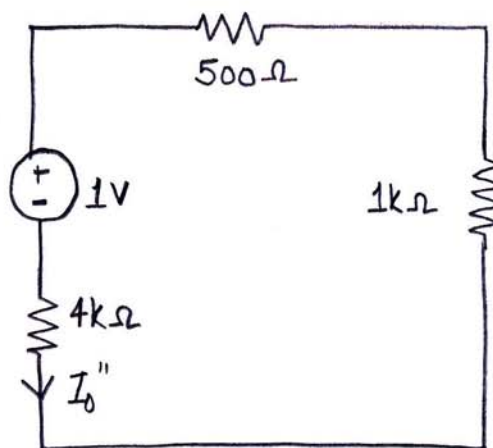


Figure P5.17



**SOLUTION:**

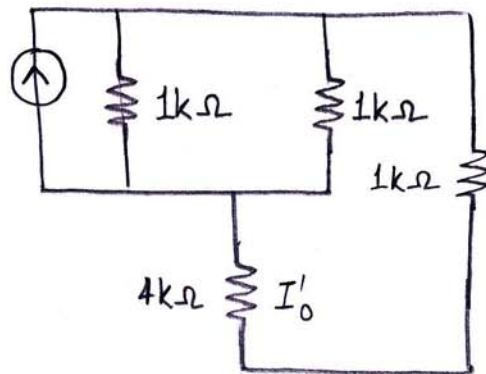
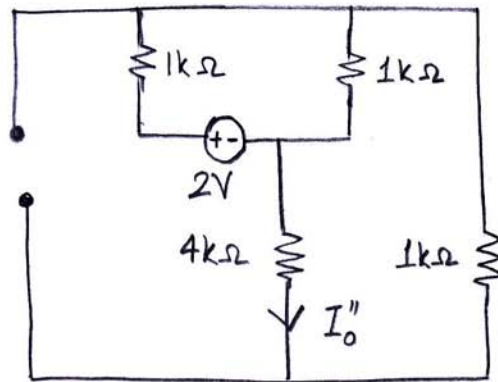
$$I'_o = \left( \frac{1k}{1k + 500 + 4k} \right) (2m) = 0.364mA$$



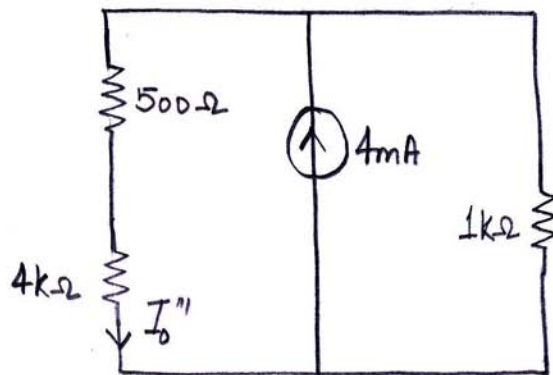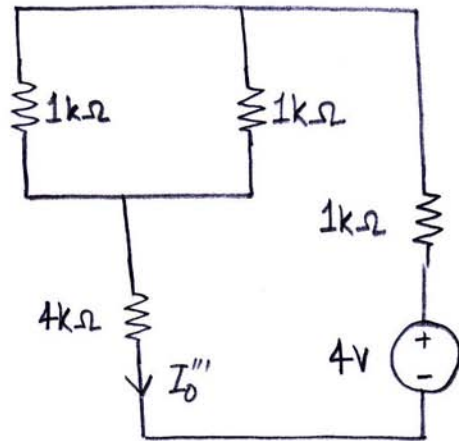
$$I_o'' = \frac{-1}{4k + 500 + 1k} = -0.182 \text{ mA}$$



$$I_0''' = \left( \frac{1k}{1k + 500 + 4k} \right) (4m) = 0.727mA$$


$$I_0 = 0.364m - 0.182m + 0.727m \\ = 0.909mA$$

5.18 Use superposition to find  $I_o$  in the circuit in Fig. P5.18.

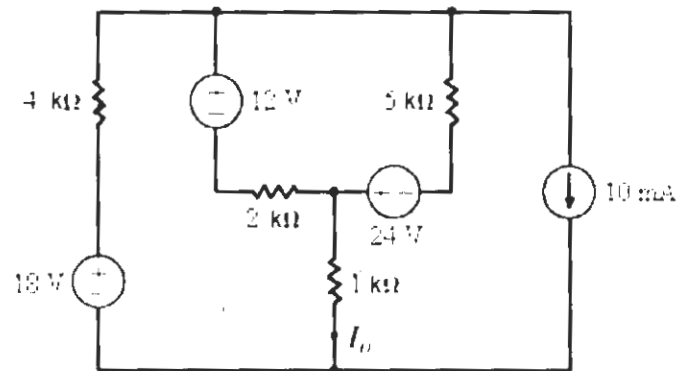


**Figure P5.18**

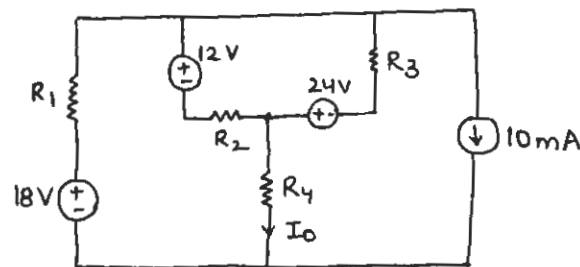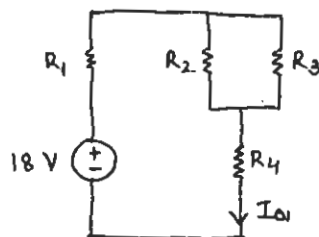**Solution:** 5.18




$$R_1 = 4 \text{ k}\Omega, R_2 = 2 \text{ k}\Omega, R_3 = 5 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega$$



$$R_A = R_2 \parallel R_3 = 1.43 \text{ k}\Omega$$

$$I_{o1} = \frac{18}{R_1 + R_A + R_4}$$

$$I_{o1} = 2.80 \text{ mA}$$

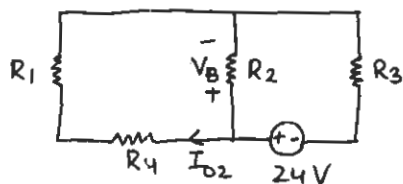


$$R_B = (R_1 + R_4) \parallel R_2 = 1.43 \text{ k}\Omega$$

$$V_B = 24 \cdot \frac{R_B}{R_B + R_3}$$

$$V_B = 5.34 \text{ V}$$
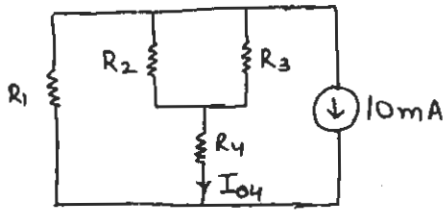
$$I_{o2} = \frac{V_B}{R_1 + R_4}, I_{o2} = 1.07 \text{ mA}$$



$$R_D = R_4 + (R_2 \parallel R_3) = 2.43 \text{ k}\Omega$$

$$I_{04} = -10 \times 10^{-3} \cdot \frac{R_1}{R_1 + R_D}$$

$$= -6.22 \text{ mA}$$

$$I_0 = I_{01} + I_{02} + I_{03} + I_{04}$$

$$I_0 = -3.68 \text{ mA}$$



5.19 Use superposition to find  $I_o$  in the circuit in Fig. P5.19.



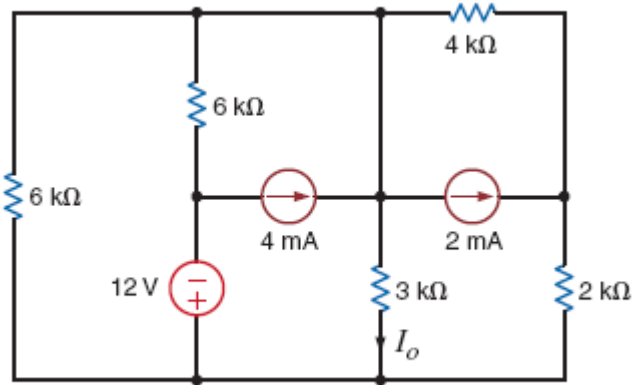
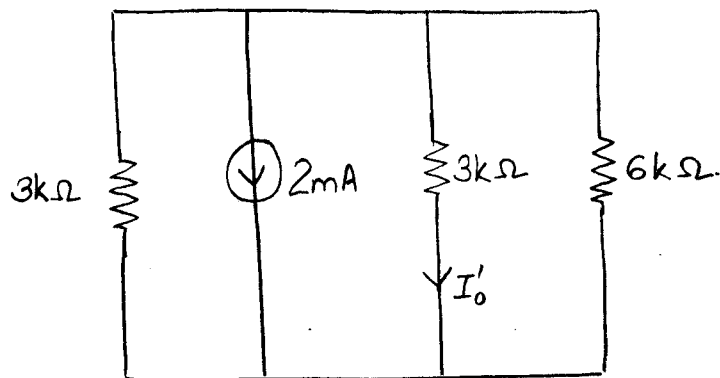


Figure P5.19




**SOLUTION:**

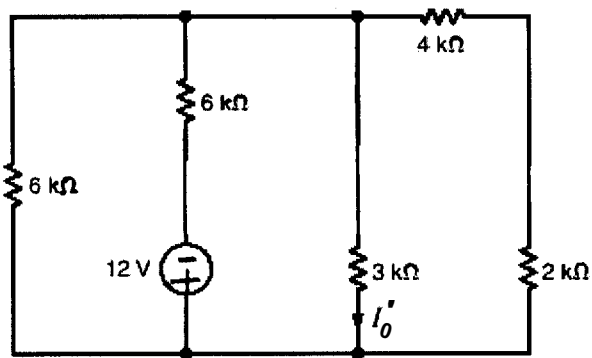


$$R' = 6k \parallel 3k = 2k\Omega$$


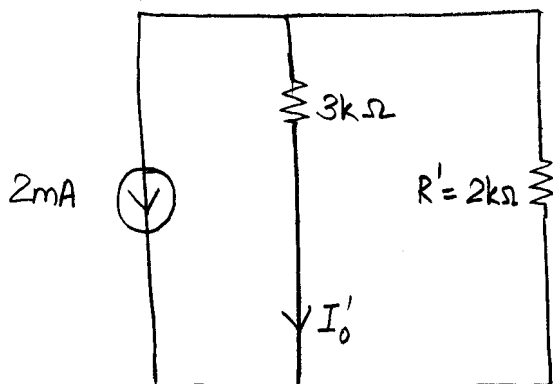

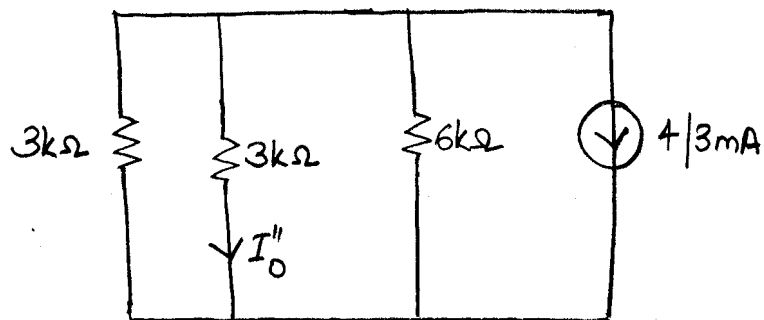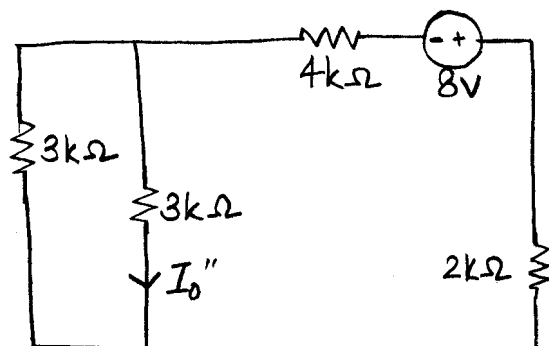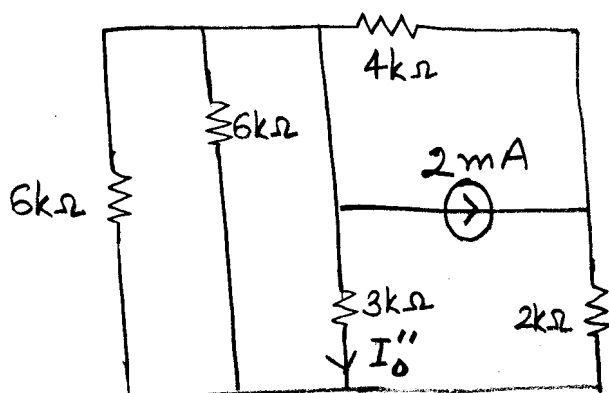
$$I'_0 = \left( \frac{2k}{2k + 3k} \right) (-2m) = -0.8mA$$




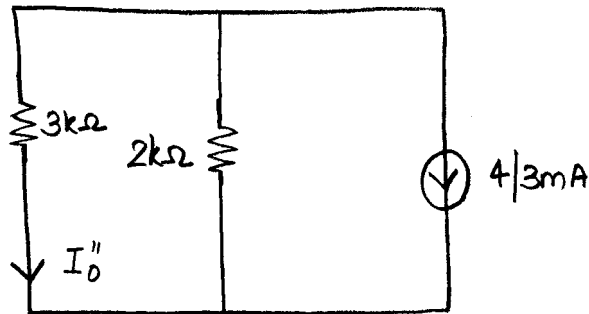
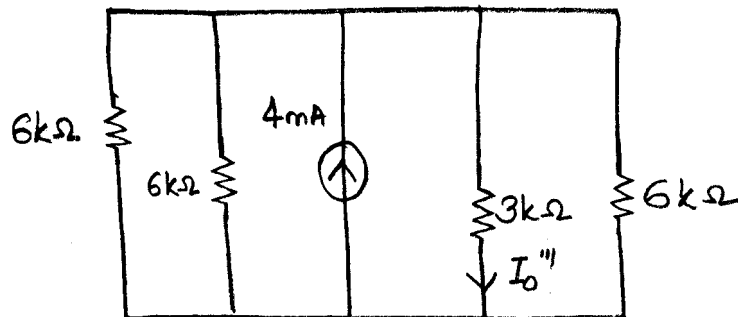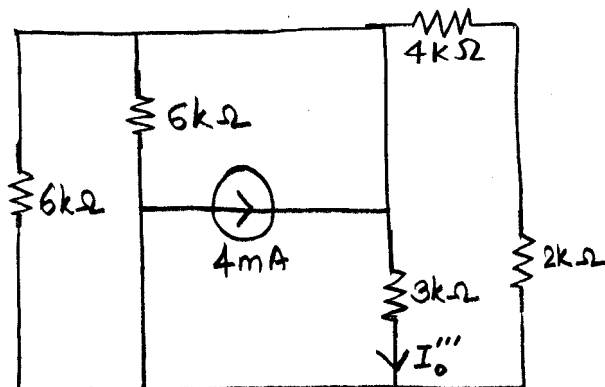
$$I''_0 = \left( \frac{2k}{2k+3k} \right) \left( -\frac{4}{3} m \right) = -\frac{8}{15} mA$$




$$R''' = 6k \parallel 6k \parallel 6k$$

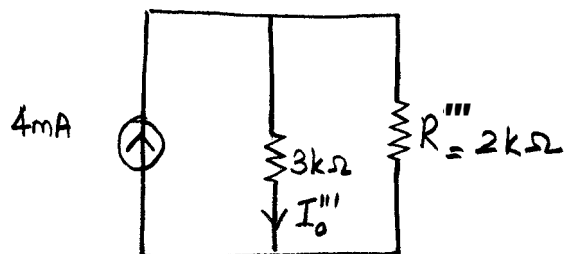

$$I_0'' = \left( \frac{2k}{2k + 3k} \right) (4m) = 1.6mA$$


$$I_0 = -0.8m - \frac{8}{15}m + 1.6m = 0.27mA$$

5.20 Use Thévenin's theorem to find  $V_o$  in the network in Fig. P5.20.

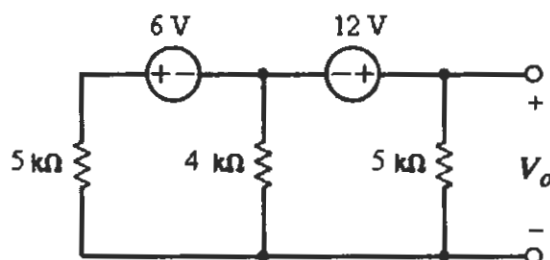


**Figure P5.20**

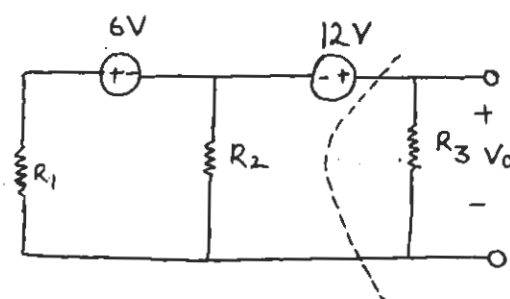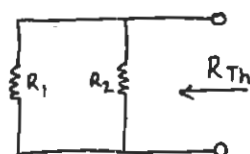
**Solution:** 5.20




$$R_1 = 5 \text{ k}\Omega, R_2 = 4 \text{ k}\Omega, R_3 = 5 \text{ k}\Omega$$


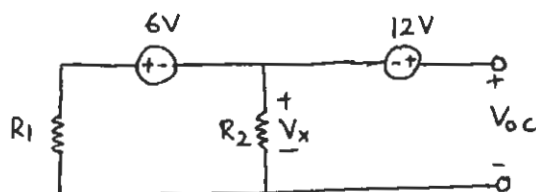
$$R_{Th} = R_1 \parallel R_2 = 5 \parallel 4 = \frac{20}{9} = 2.22 \text{ k}\Omega$$


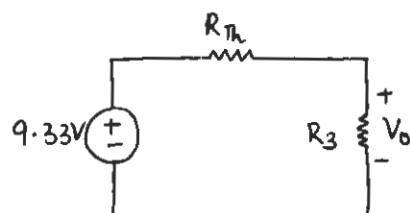
$$\begin{aligned} V_x &= (-6) \cdot \frac{R_2}{R_1 + R_2} \\ &= (-6) \cdot \frac{4}{9} \\ &= -\frac{8}{3} = -2.66 \text{ V} \\ V_{oc} &= 12 + V_x \\ &= 12 - \frac{8}{3} \\ &= 9.33 \text{ V} \end{aligned}$$



$$\begin{aligned} V_o &= 9.33 \times \frac{R_3}{R_3 + R_{Th}} \\ &= 9.33 \times \frac{5}{7.22} \end{aligned}$$

$$\boxed{V_o = 6.46 \text{ V}}$$

5.21 Use Thévenin's theorem to find  $V_o$  in the network in Fig. P5.21



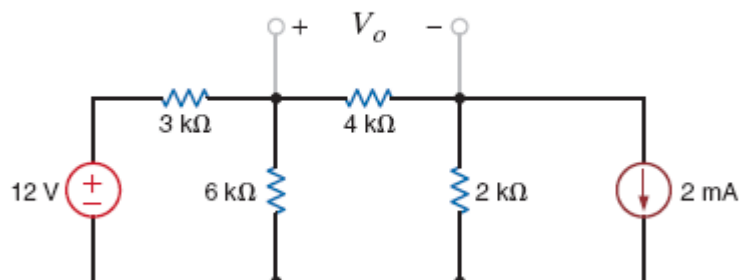


Figure P5.21

**SOLUTION:**

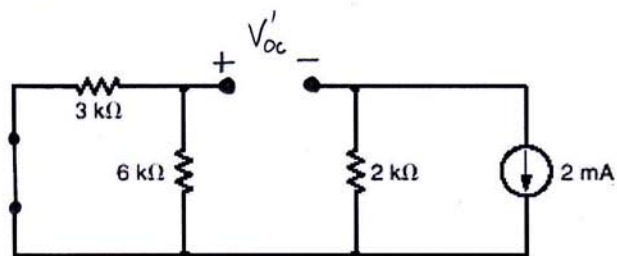


$$V'_{oc} = 2m(2k) = 4V$$

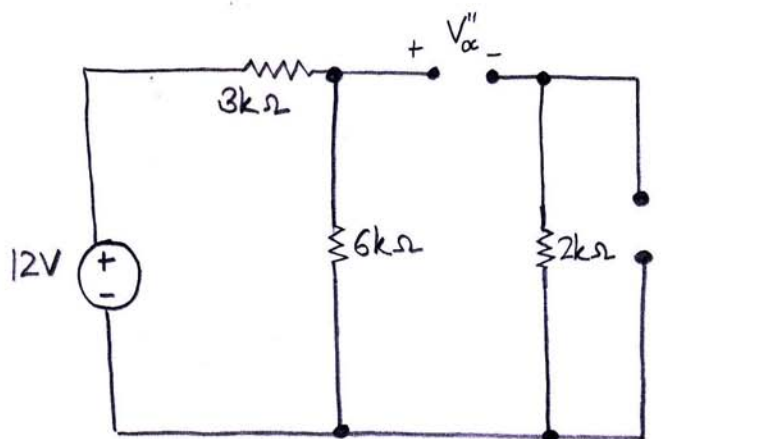


$$V''_{oc} = \left( \frac{6k}{3k + 6k} \right) (12) = 8V$$

$$V_{oc} = 4 + 8 = 12V$$

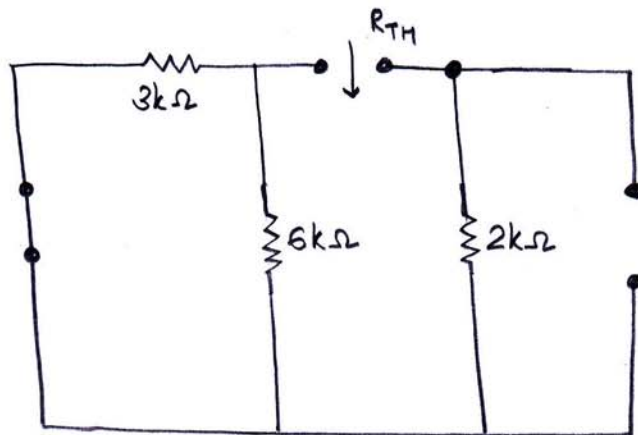
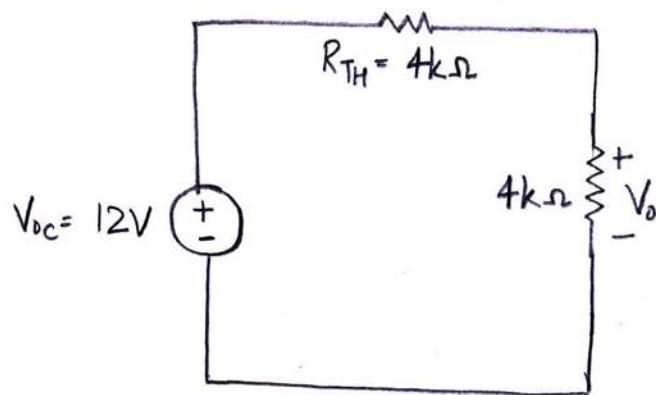
$$R_{TH} = (3k \parallel 6k) + 2k = \frac{3k(6k)}{3k+6k} + 2k = 4k\Omega$$



$$V_o = \left( \frac{4k}{4k+4k} \right) (12) = 6V$$

5.22 Find  $I_o$  in the network in Fig. P5.22 using Thévenin's theorem.



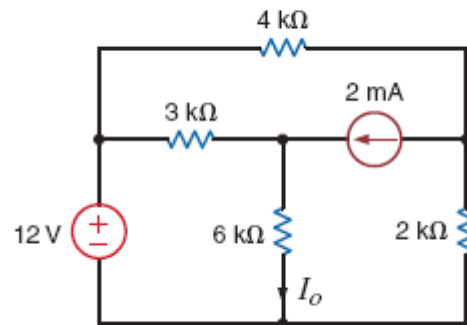
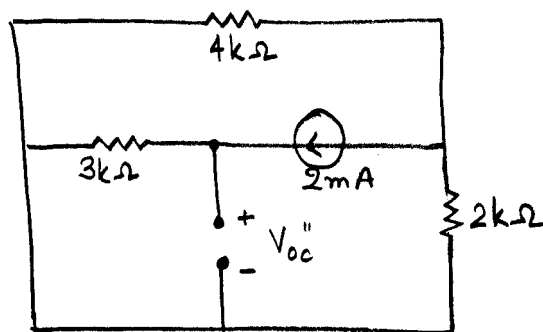


Figure P5.22


**SOLUTION:**

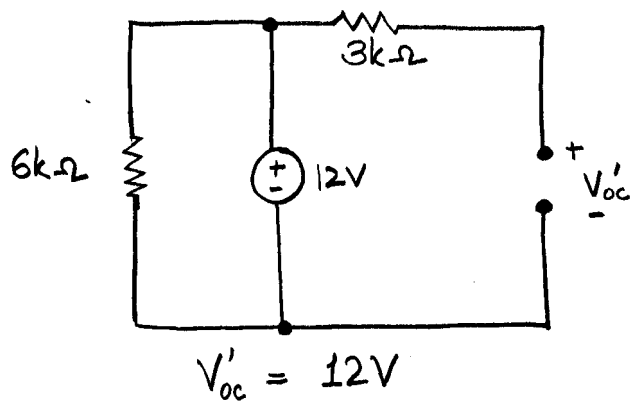

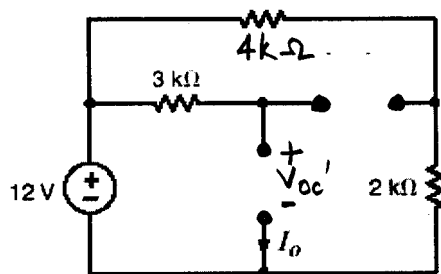


$$V_{oc}'' = 2m(3k) = 6V$$

$$V_{oc} = 12 + 6 = 18V$$

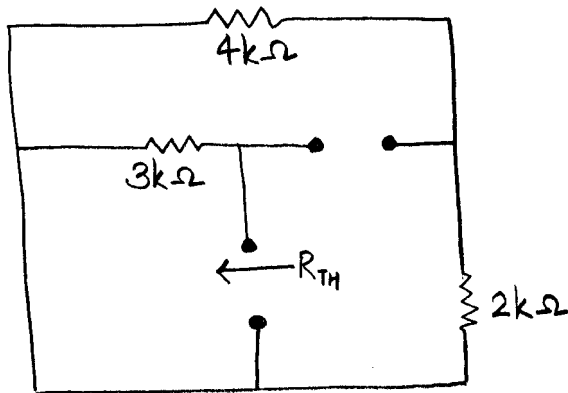

$$R_{TH} = 3k\Omega$$

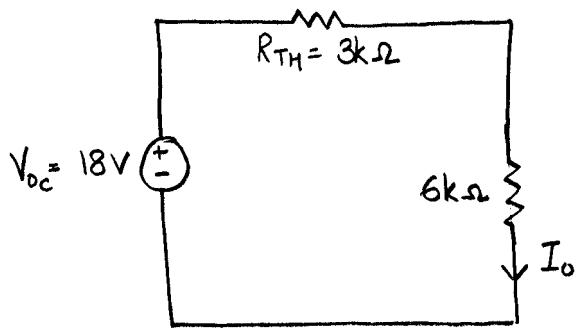

$$I_o = \frac{18}{3k + 6k} = 2mA$$

5.23 Find  $V_o$  in the circuit in Fig. P5.23 using Thévenin's theorem.



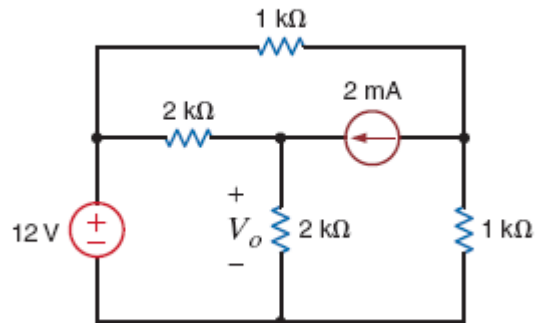


Figure P5.23

**SOLUTION:**

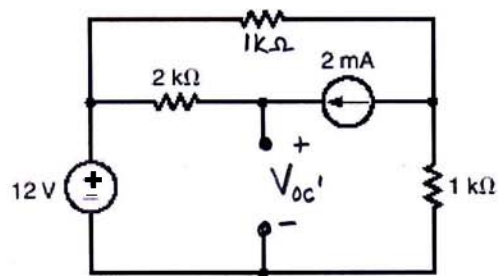


$$V'_{oc} = 2m(2k) = 4V$$

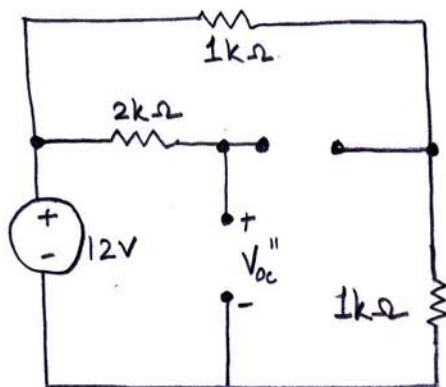


$$V''_{oc} = 12V$$

$$V_{oc} = 4 + 12 = 16V$$

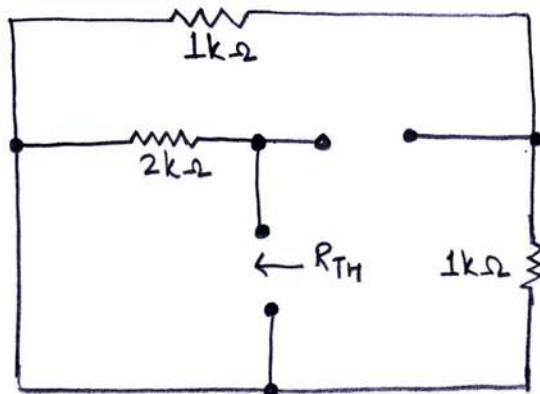

$$R_{TH} = 2k\Omega$$

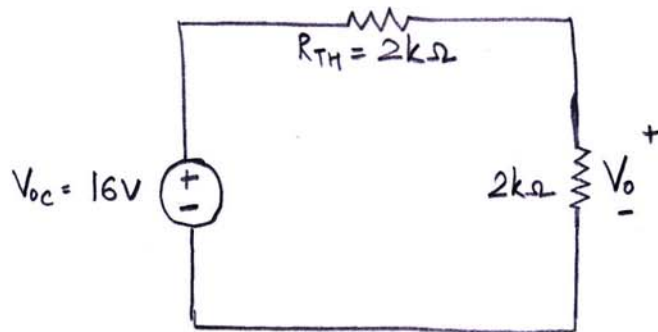

$$V_O = \left( \frac{2k}{2k + 2k} \right) (16) = 8V$$

5.24 Use Thévenin's theorem to find  $I_o$  in the network in Fig. P5.24.



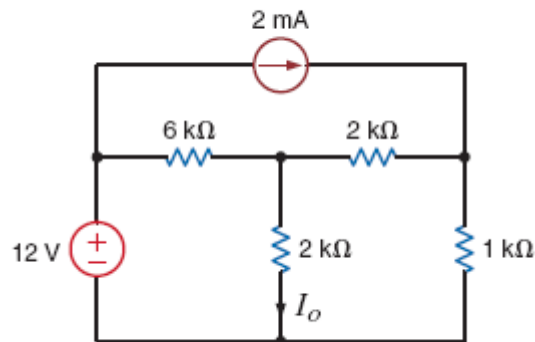


Figure P5.24

**SOLUTION:**

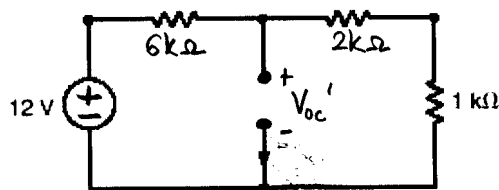

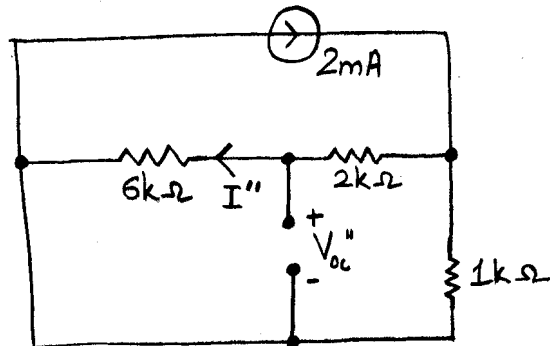
$$V'_{oc} = \left( \frac{3k}{3k + 6k} \right) (12) = 4V$$




$$I'' = \left( \frac{1k}{1k + 6k + 2k} \right) (2m) = 0.222mA$$

$$V''_{oc} = 6k(0.222m) = 1.333V$$

$$V_{oc} = 4 + 1.333 = 5.333V$$

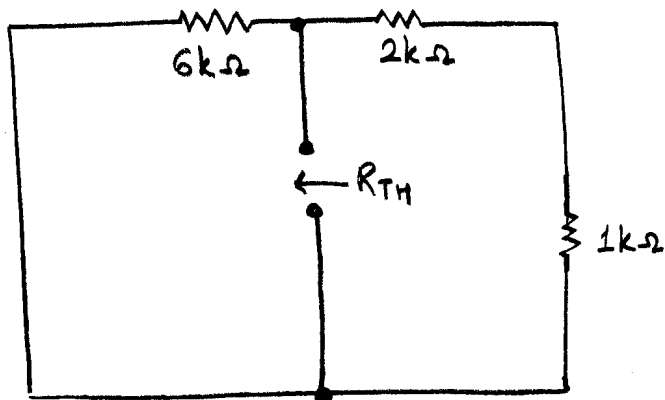

$$R_{TH} = 6k \parallel 3k = 2k\Omega$$

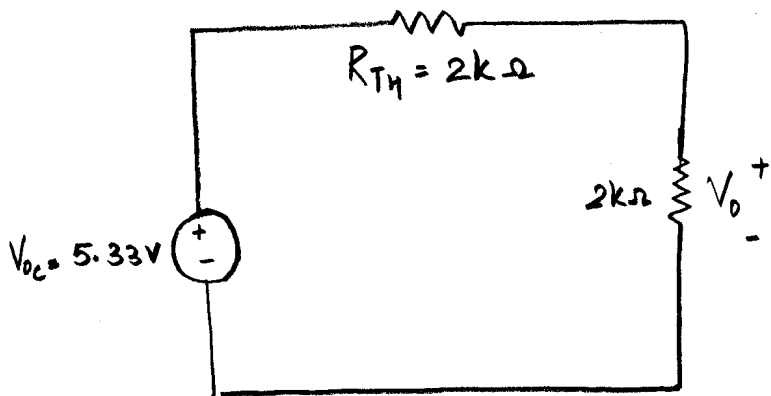

$$I_0 = \frac{5.333}{4k} = 1.333 \text{ mA}$$

5.25 Find  $V_o$  in the network in Fig. P5.25 using Thévenin's theorem.


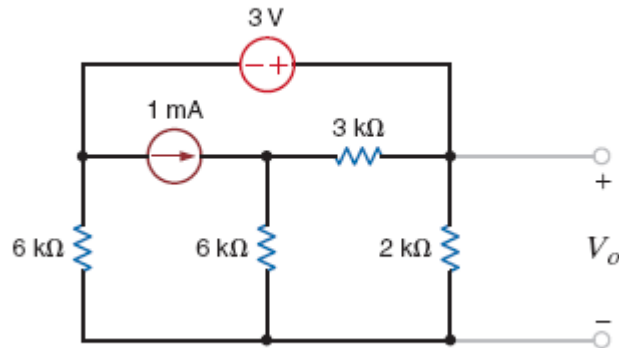
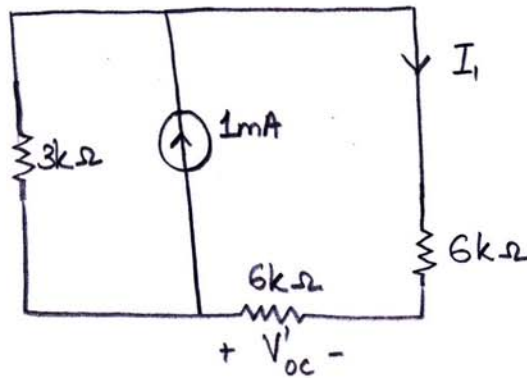



Figure P5.25

**SOLUTION:**

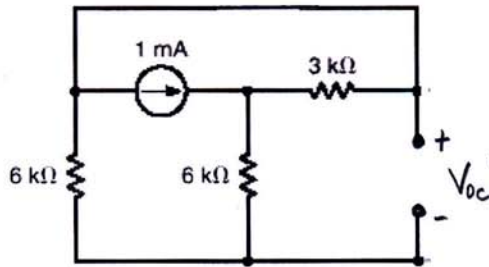


$$I_1 = \left( \frac{3k}{3k + 12k} \right) (1m) = 0.2mA$$

$$V'_{oc} = -0.2m(6k) = -1.2V$$

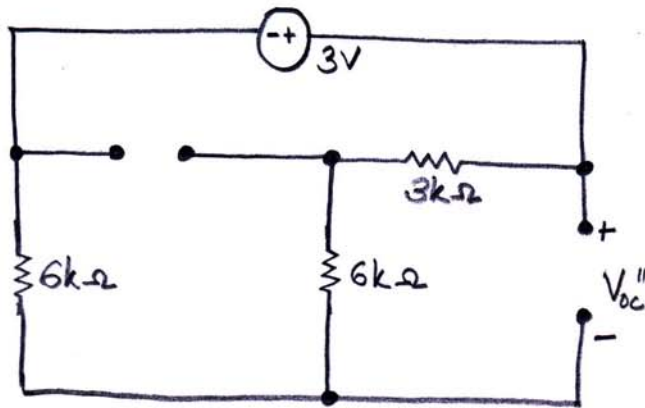


$$V''_{oc} = \left( \frac{9k}{9k + 6k} \right) (3) = 1.8V$$

$$V_{oc} = -1.2 + 1.8 = 0.6V$$

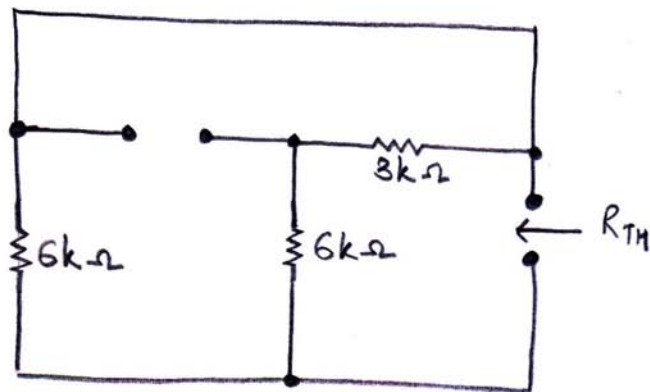

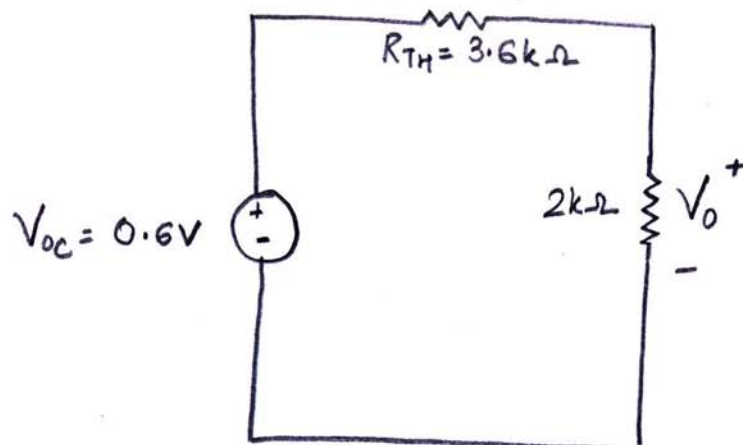
$$R_{TH} = (6k + 3k) \parallel 6k = 3.6k\Omega$$



$$V_o = \left( \frac{2k}{2k + 3.6k} \right) (0.6) = 0.21V$$




5.26 Find  $I_o$  in the circuit in Fig. P5.26 using Thévenin's theorem.

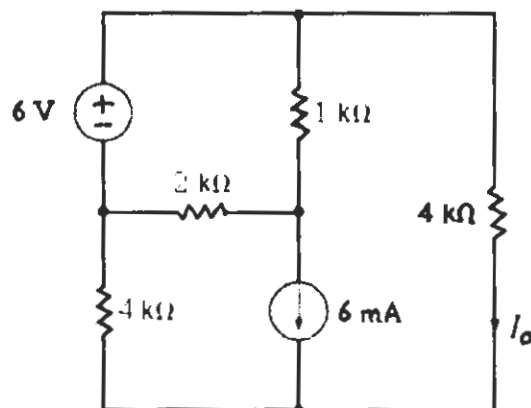


**Figure P5.26**

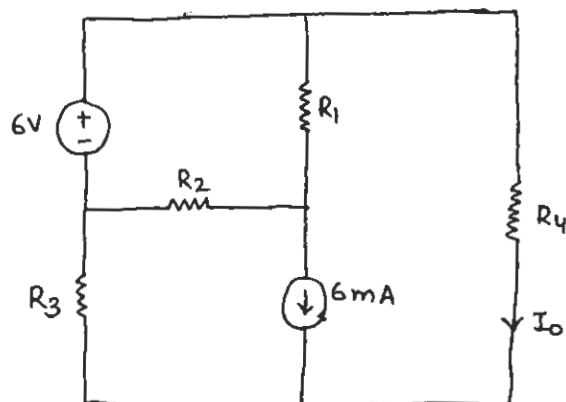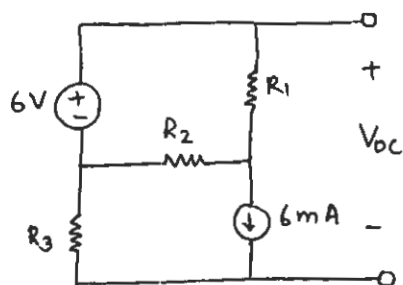**Solution:** 5.26




$$R_1 = 1\text{ k}\Omega, R_2 = 2\text{ k}\Omega, R_3 = R_4 = 4\text{ k}\Omega$$




$$-6 + V_{oc} + 6 \times 10^{-3} R_3 = 0$$

$$\Rightarrow V_{oc} = -18\text{ V}$$

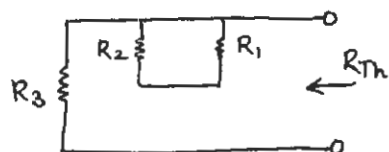

$$R_{Th} = R_3 = 4\text{ k}\Omega$$

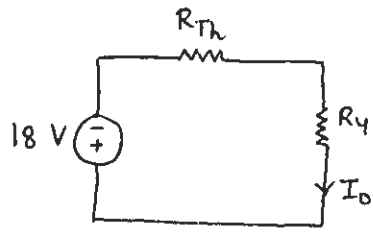

$$I_0 = \frac{-18}{R_4 + R_{Th}}$$

$$I_0 = -2.25 \text{ mA}$$

5.27 Find  $I_o$  in the network in Fig. P5.27 using Thévenin's theorem.



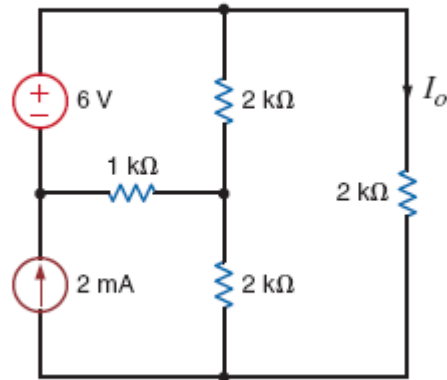



Figure P5.27

**SOLUTION:**

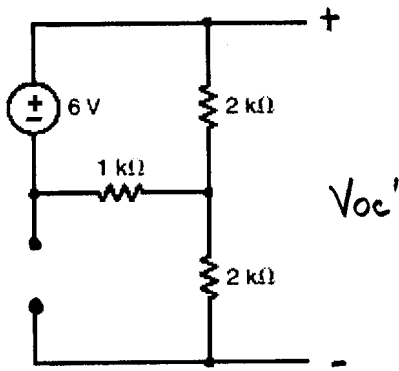

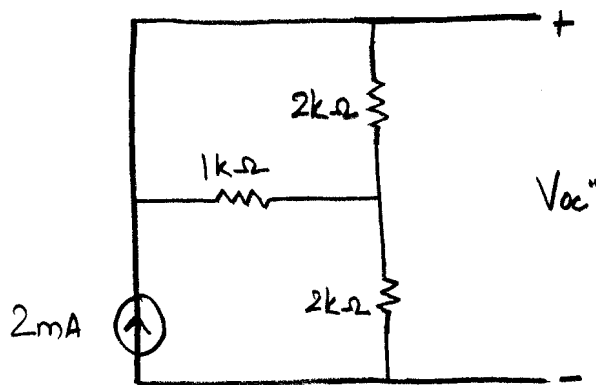
$$V'_{oc} = \left( \frac{2k}{2k + 1k} \right) (6) = 4V$$




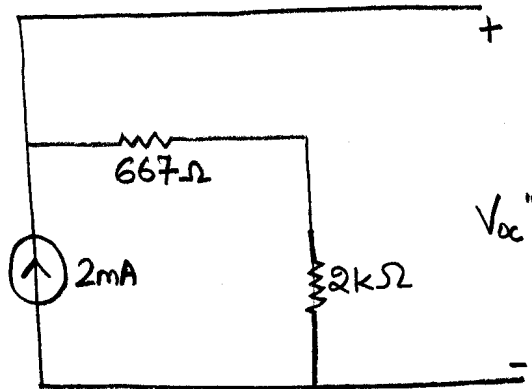
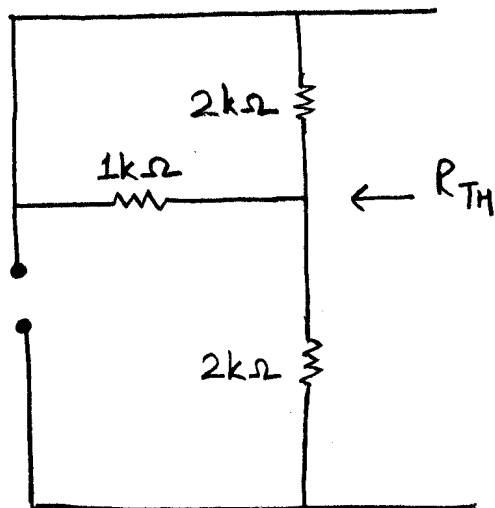
$$V''_{oc} = 2\text{m}(667 + 2\text{k}) = 5.334\text{V}$$
$$V_{oc} = 4 + 5.334 = 9.334\text{V}$$




$$R_{TH} = (1\text{k} || 2\text{k}) + 2\text{k} = 2.67\text{k}\Omega$$

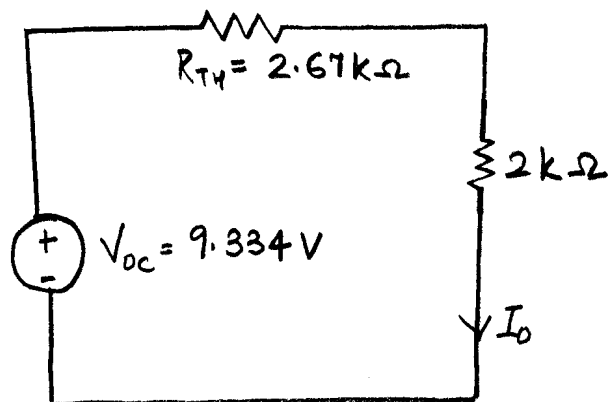


$$I_0 = \frac{9.334}{2.67\text{k} + 2\text{k}} = 2\text{mA}$$

5.28 Find  $I_o$  in the network in Fig. P5.28 using Thévenin's theorem.

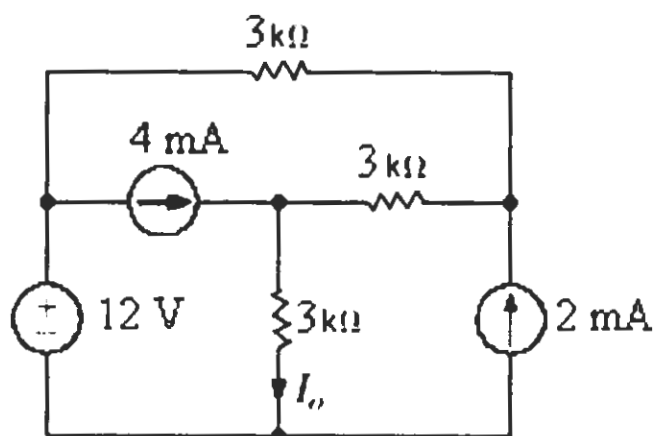


**Figure P5.28**

Solution: 5.28

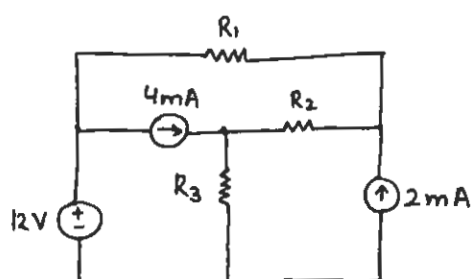


$$R_1 = R_2 = R_3 = 3\text{ k}\Omega$$

By Superposition

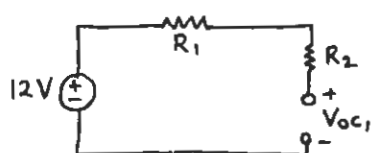

$$V_{oc1} = 12\text{ V}$$

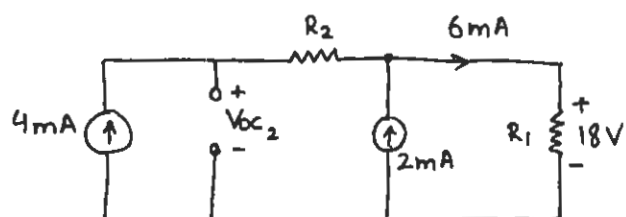


$$V_{oc2} = 4 \times 10^{-3} R_2 + 6 \times 10^{-3} R_1$$


$$V_{oc2} = 30\text{ V}$$

$$V_{oc} = V_{oc1} + V_{oc2}$$

$$V_{oc} = 42.0\text{ V}$$

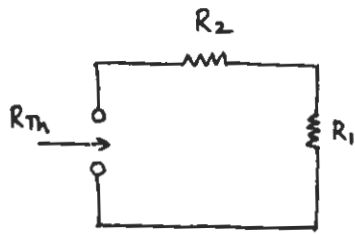

$$R_{Th} = R_1 + R_2 = 6k\Omega$$

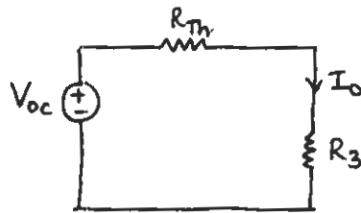

$$I_0 = \frac{V_{oc}}{R_3 + R_{Th}}$$

$$I_0 = 4.67 \text{ mA}$$

5.29 Find  $I_o$  in the network in Fig. P5.29 using Thévenin's theorem.



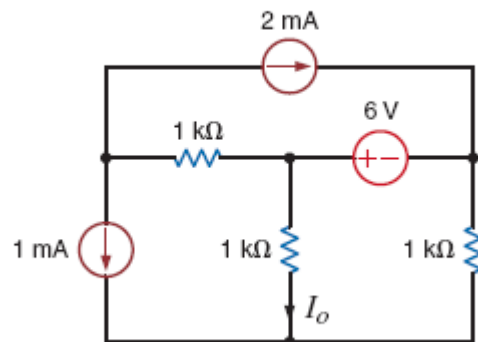


Figure P5.29


**SOLUTION:**

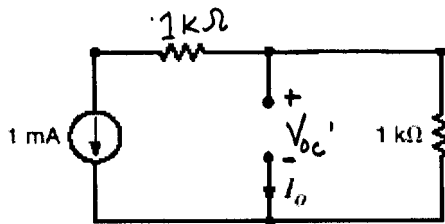


$$V'_{oc} = 1k(-1m) = -1V$$

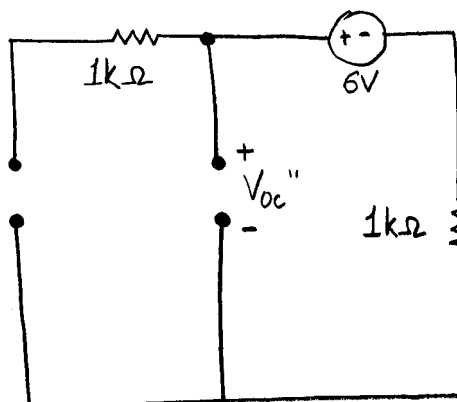


$$V''_{oc} = 6V$$

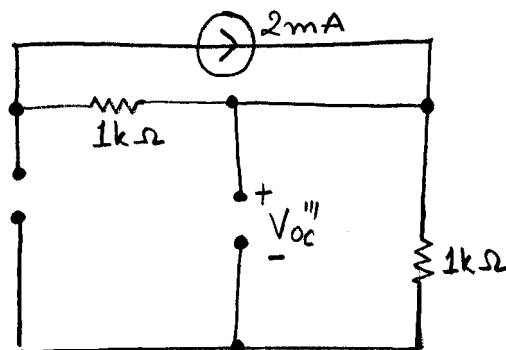
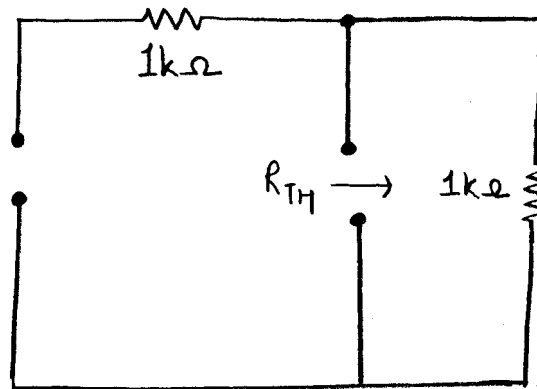
$$V_{oc}'' = 0 \text{ Volt}$$
$$V_{oc} = -1 + 6 + 0 = 5 \text{ V}$$



$$R_{TH} = 1k\Omega$$

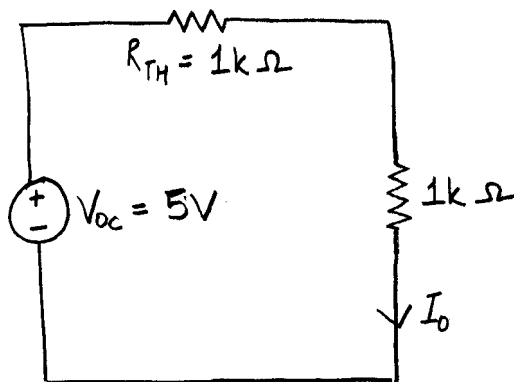

$$I_0 = \frac{5}{2k} = 2.5\text{mA}$$



5.30 Find  $V_o$  in the Fig. P5.30 using Thévenin's theorem.



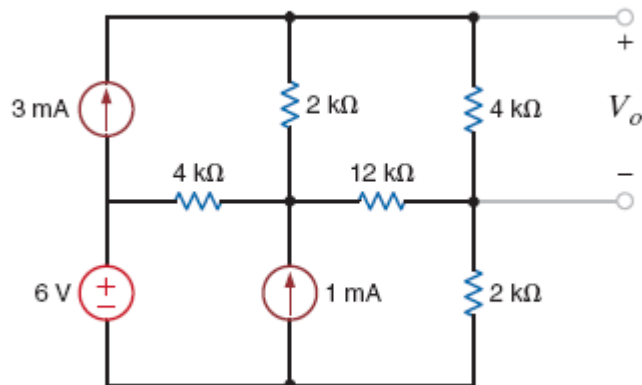



Figure P5.30

**SOLUTION:**

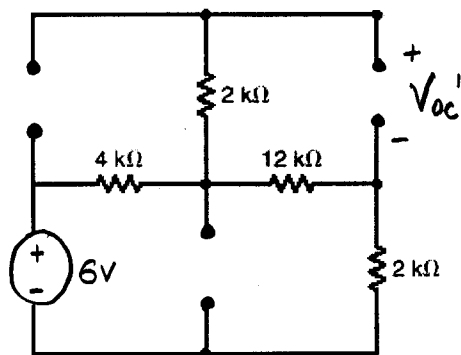

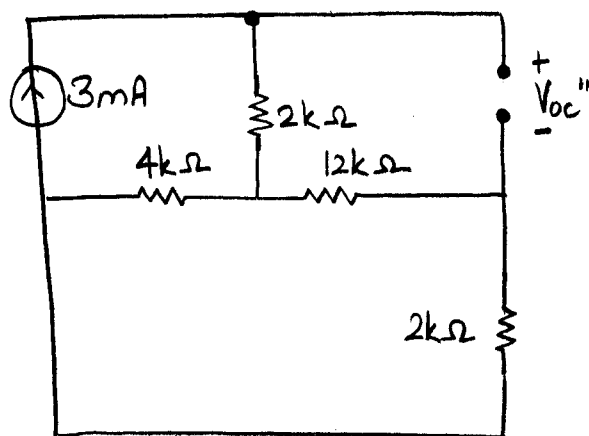
$$V'_{oc} = \left( \frac{12k}{4k + 12k + 2k} \right) (6) = 4V$$



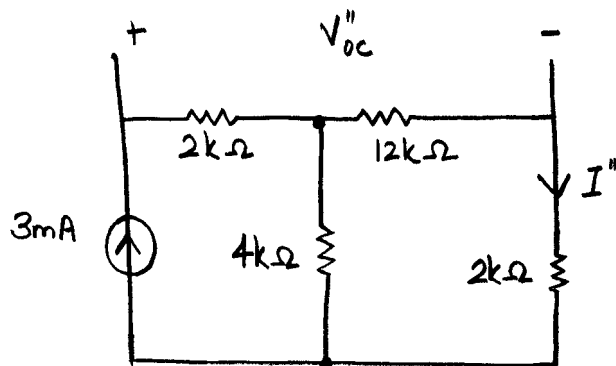

$$I'' = \left( \frac{4k}{4k + 12k + 2k} \right) (3m) = 0.67mA$$


$$V''_{oc} = 2k(3m) + 12k(0.67m) = 14V$$

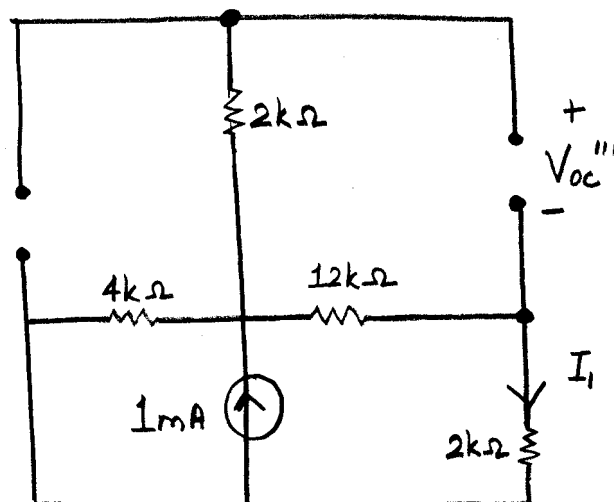


$$I_1 = \left( \frac{4k}{4k + 12k + 2k} \right) (1m) = 0.222mA$$

$$V'''_{oc} = 12k(0.222m) = 2.67V$$

$$V_{oc} = 4 + 14 + 2.67 = 20.67V$$

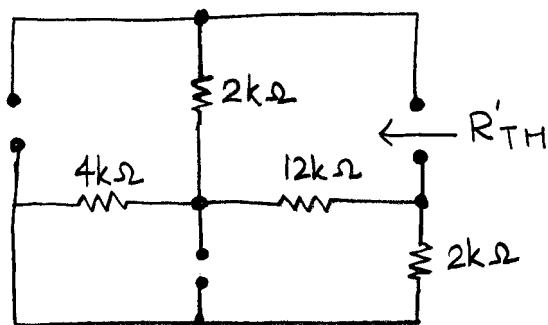

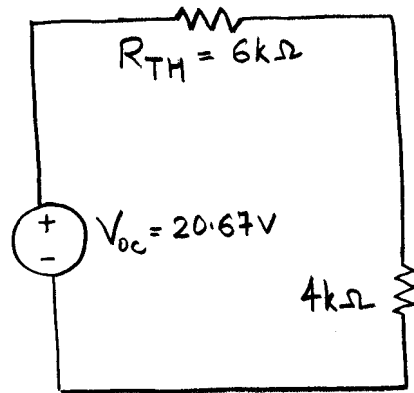

$$R_{TH} = [(2k + 4k) \parallel 12k] + 2k = 6k\Omega$$

$$V_o = \left( \frac{4k}{4k + 6k} \right) (20.67) = 8.27V$$

5.31 Use Thévenin's theorem to find  $V_o$  in the circuit in Fig. P5.31


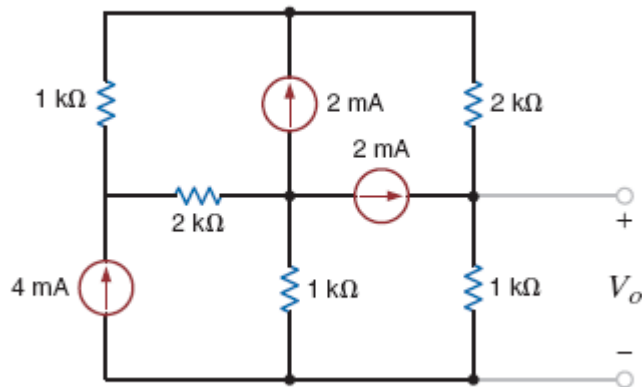



Figure P5.31

**SOLUTION:**

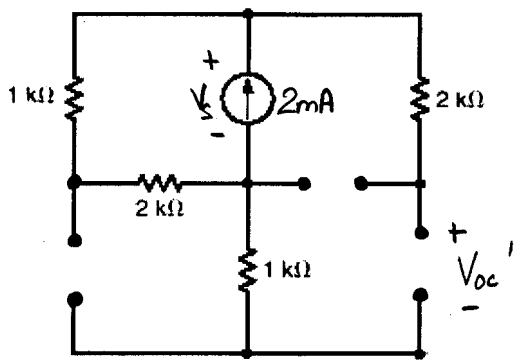


$$V_s = 1k(2m) + 2k(2m) = 2 + 4 = 6V$$

$$V'_{oc} = 6V$$

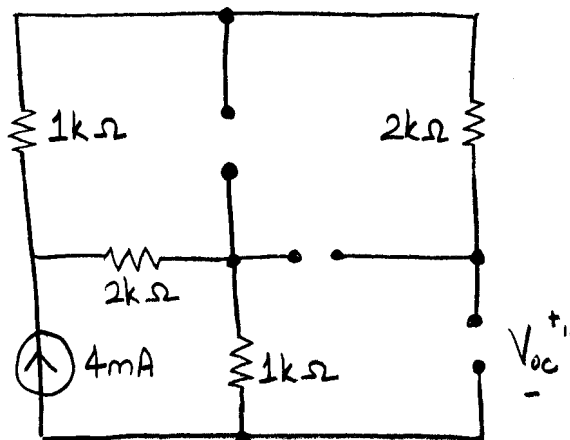

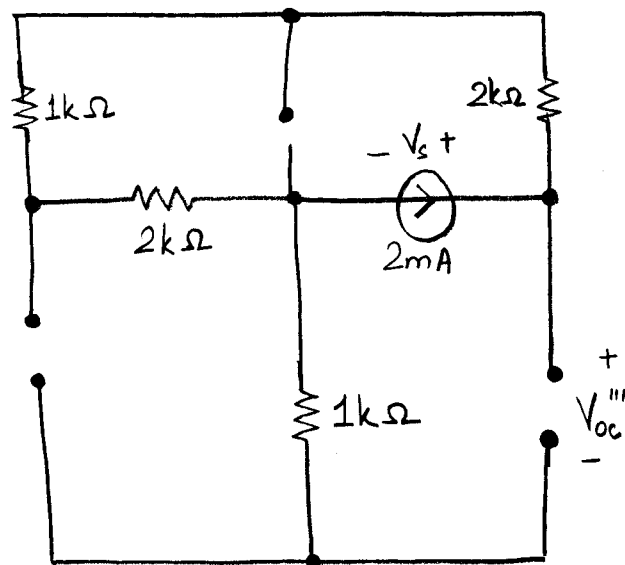
$$V''_{oc} = 2k(4m) + 1k(4m) = 8 + 4 = 12V$$




$$V_s = 2k(2m) + 1k(2m) + 2k(2m) = 10V$$

$$V_{oc}'' = 10V$$

$$V_{oc} = 6 + 12 + 10 = 28V$$

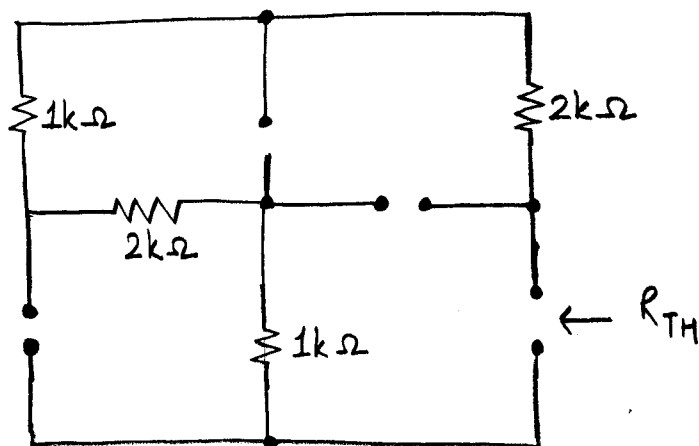

$$R_{TH} = 6k\Omega$$

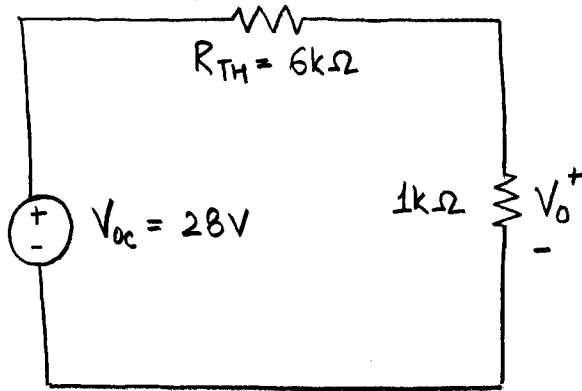

$$V_o = \left( \frac{1k}{1k + 6k} \right) (28) = 4V$$

5.32 Find  $I_o$  in the circuit in Fig. P5.32 using Thévenin's theorem.



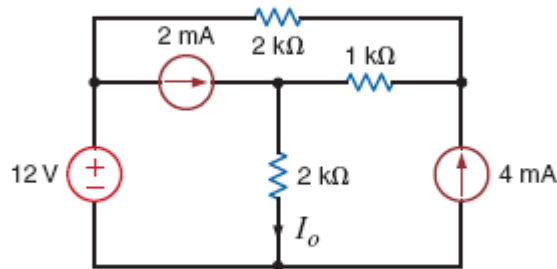


Figure P5.32

**SOLUTION:**

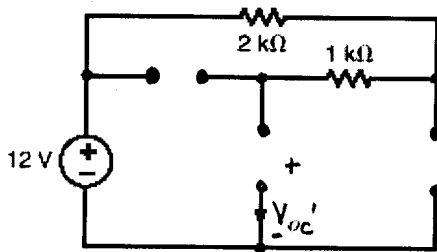


$$V'_{oc} = 12\text{V}$$

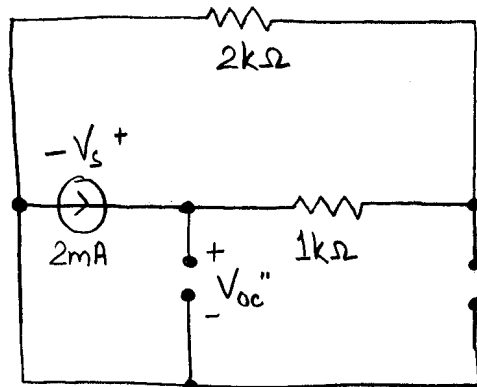


$$V_s = 1k(2m) + 2k(2m) = 2 + 4 = 6\text{V}$$

$$V''_{oc} = 6\text{V}$$

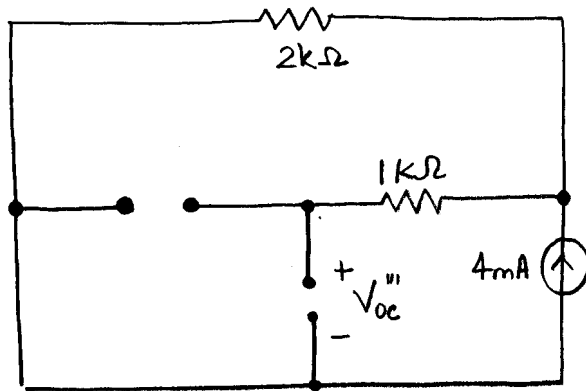


$$V''_{oc} = 2k(4m) = 8V$$

$$V_{oc} = 12 + 6 + 8 = 26V$$

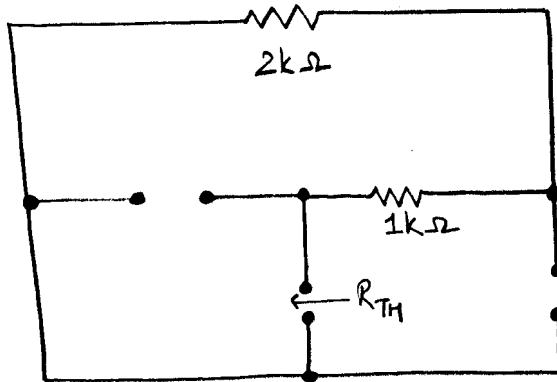


$$R_{TH} = 3k\Omega$$

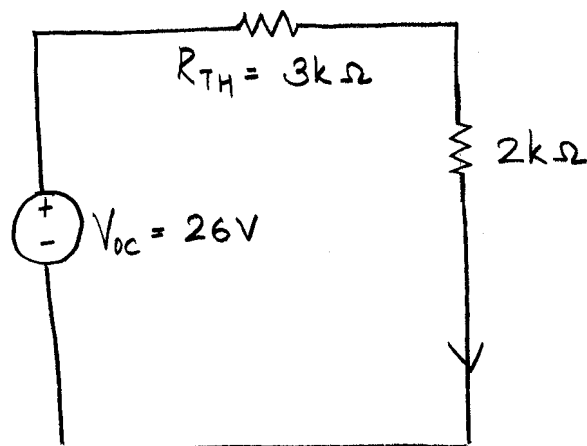

$$I_o = \frac{26}{5k} = 5.2mA$$




5.33 Find  $V_o$  in the network in Fig. P5.33 using Thévenin's theorem.

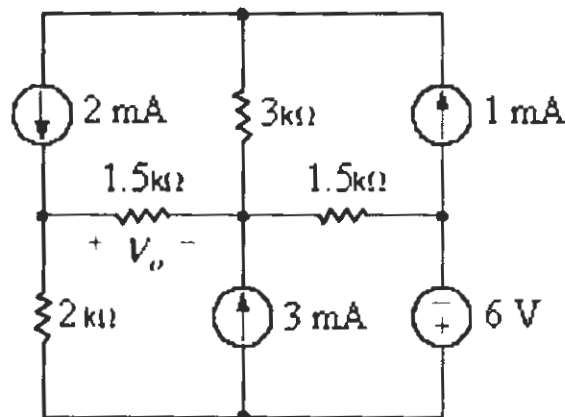


**Figure P5.33**

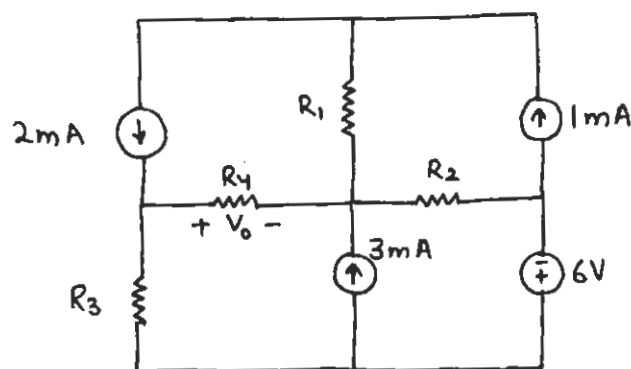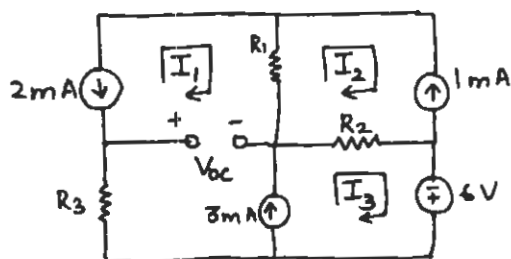Solution: 5.33



$$R_1 = 3 \text{ k}\Omega, \quad R_2 = R_4 = 1.5 \text{ k}\Omega, \quad R_3 = 2 \text{ k}\Omega$$




$$I_1 = -2 \text{ mA}, \quad I_2 = -1 \text{ mA}$$


$$I_3 - I_1 = 3 \text{ mA} \Rightarrow I_3 = 1 \text{ mA}$$

$$I_1 R_3 + V_{oc} + (I_3 - I_2) R_2 - 6 = 0$$

$$V_{oc} = 7 \text{ V}$$

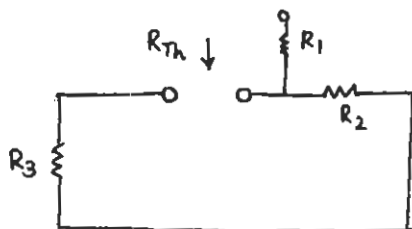
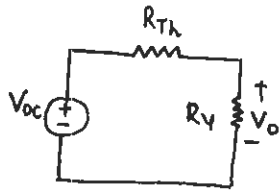
$$R_{Th} = R_3 + R_2 = 3.5 \text{ k}\Omega$$



$$V_o = V_{oc} \cdot \frac{R_L}{R_L + R_{Th}}$$

$$V_o = 2.10 \text{ V}$$

5.34 Using Thévenin's theorem, find  $I_A$  in the circuit in Fig. P5.34.



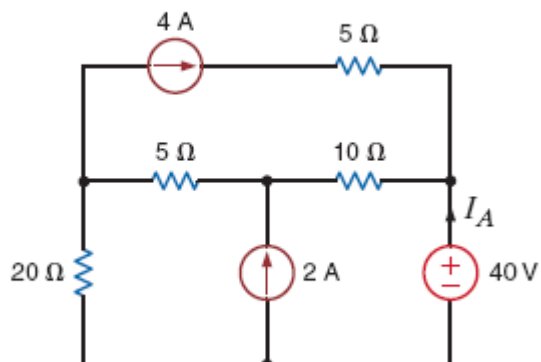


Figure P5.34

**SOLUTION:**

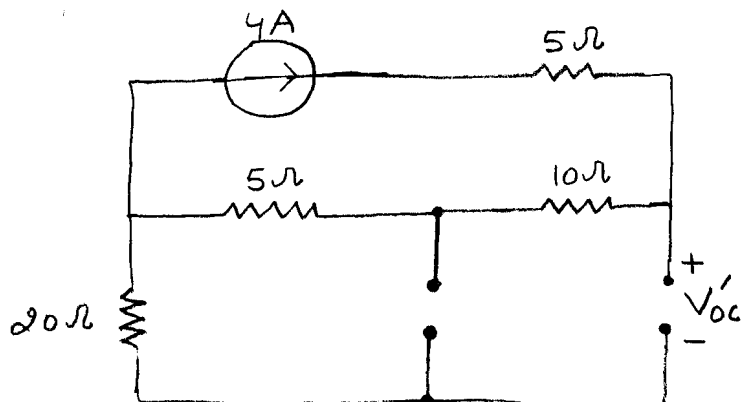


$$V'_{oc} = 5(4) + 10(4) = 60\text{ V}$$

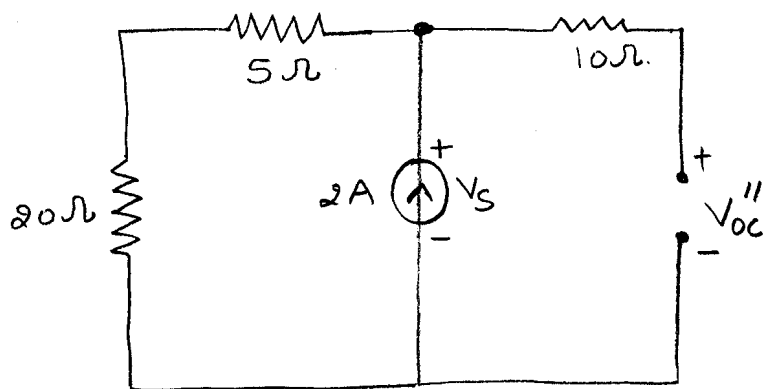


$$V_S = 5(2) + 20(2) = 50\text{ V}$$

$$V''_{oc} = 50\text{ V}$$

$$V_{oc} = 60 + 50 = 110V$$

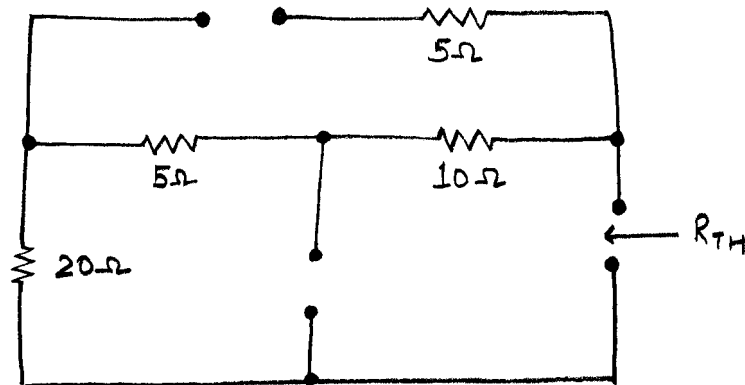

$$R_{TH} = 35\Omega$$

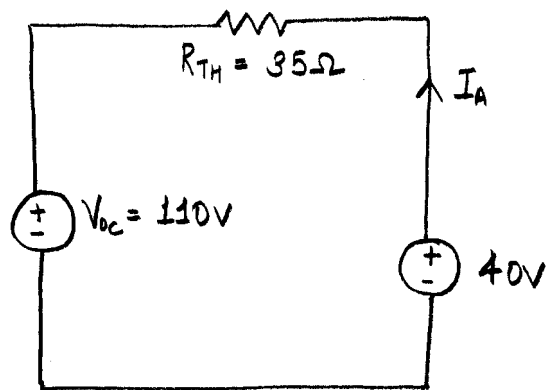

$$\text{KVL: } 40 = 110 + I_A(35)$$

$$I_A = -2A$$

5.35 Find  $V_o$  in the network in Fig. P5.35 using Thévenin's theorem.


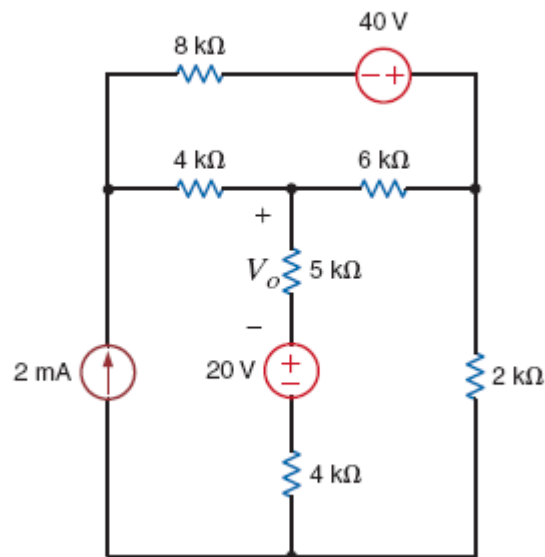



Figure P5.35

**SOLUTION:**

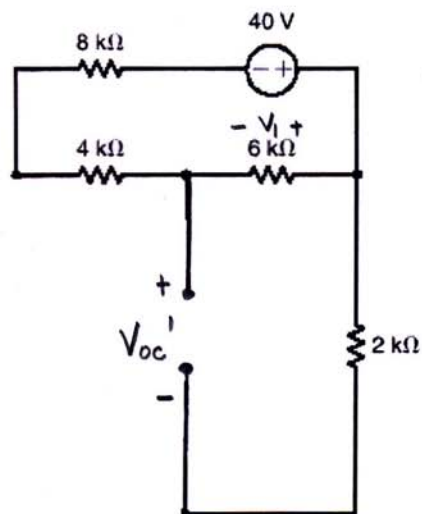

$$V_1 = \left( \frac{6k}{6k + 4k + 8k} \right) (40) = \frac{40}{3} \text{ V}$$


$$V_{oc}' = -\frac{40}{3} \text{ V}$$

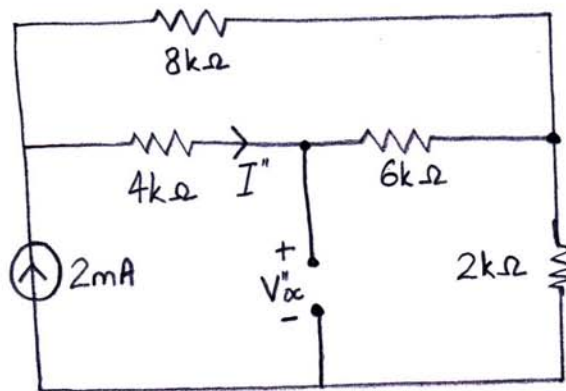


$$I'' = \left( \frac{8k}{8k + 4k + 6k} \right) (2m) = 0.89mA$$

$$V''_{oc} = 6k(0.89m) + 2k(2m) = \frac{28}{3}V$$
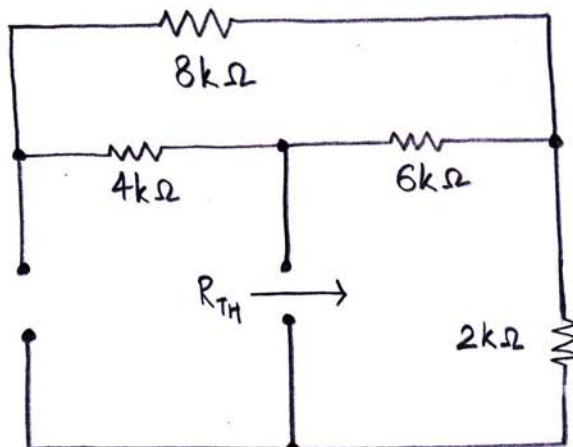
$$V_{oc} = -\frac{40}{3} + \frac{28}{3} = -4V$$


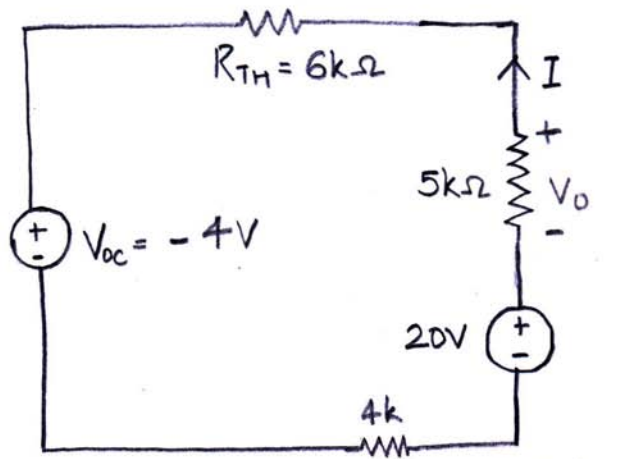
$$R_{TH} = [(4k + 8k) \parallel 6k] + 2k = 6k\Omega$$



$$20 = -4 + (6k + 5k + 4k)I$$

$$I = 1.6mA$$

$$V_o = -5k(1.6m) = -8V$$

5.36 Use Thévenin's theorem to find  $I_o$  in the network in Fig. P5.36.



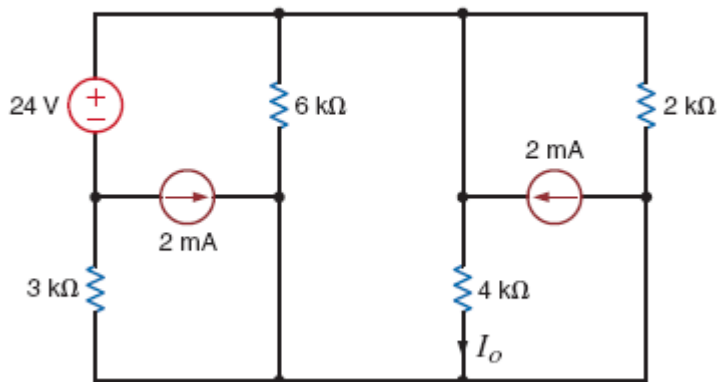


Figure P5.36

**SOLUTION:**

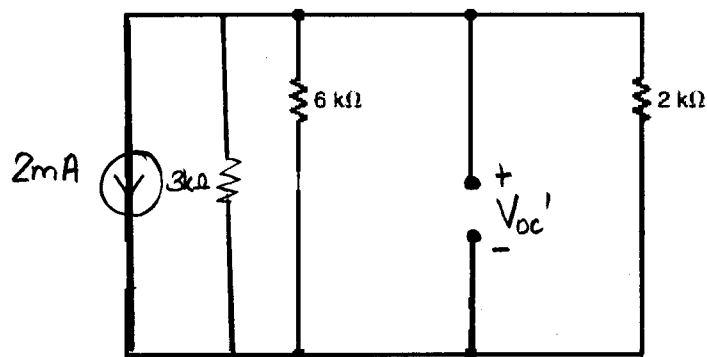



$$R' = 3k \parallel 6k = 2k\Omega$$

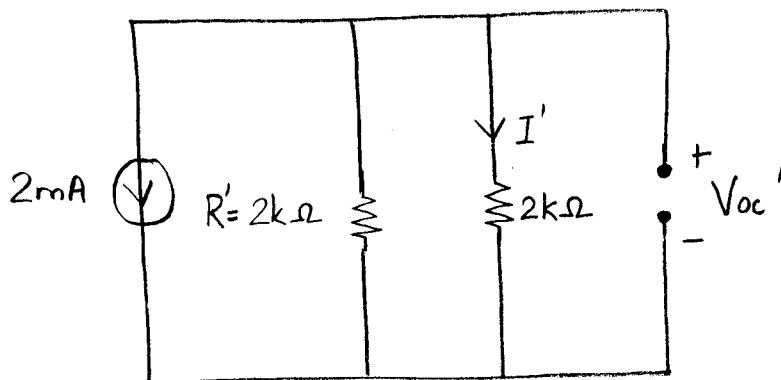

$$I' = \left( \frac{2k}{2k + 2k} \right) (-2m) = -1mA$$


$$V'_{oc} = 2k(-1m) = -2V$$




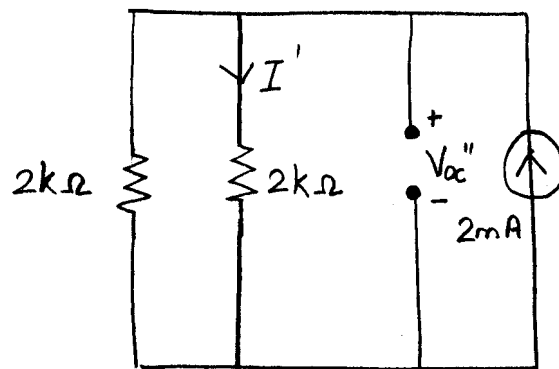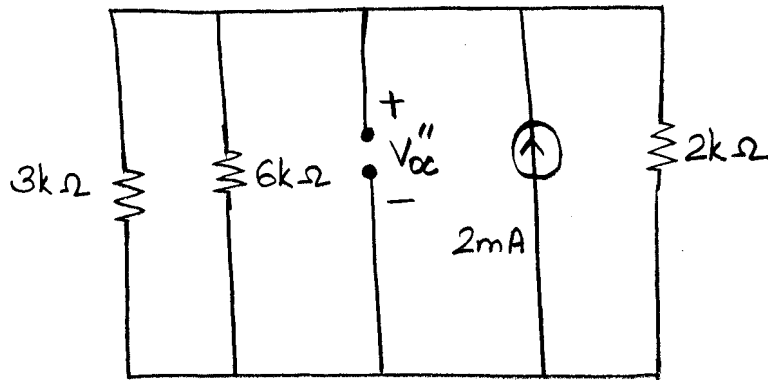

$$I' = \left( \frac{2k}{2k + 2k} \right) (2m) = 1mA$$

$$V''_{oc} = 2k(1m) = 2V$$

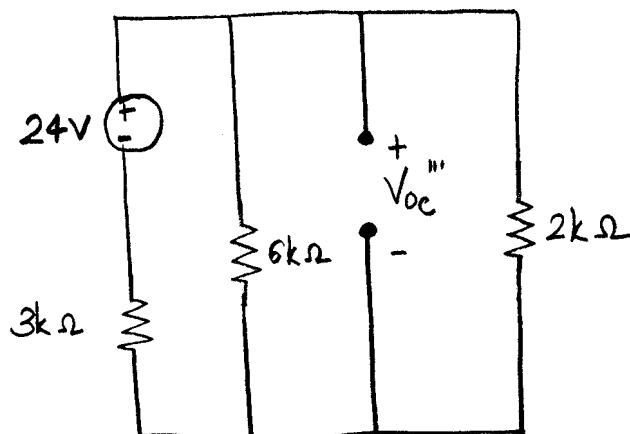


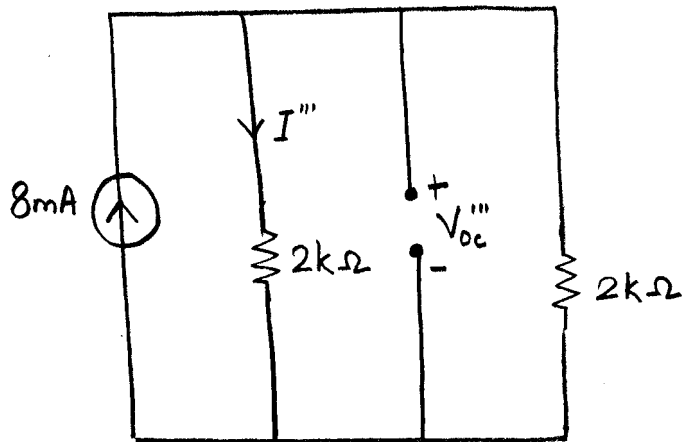


$$I''' = \left( \frac{2k}{2k + 2k} \right) (8m) = 4mA$$

$$V'''_{oc} = 2k(4m) = 8V$$

$$V_{oc} = -2 + 2 + 8 = 8V$$

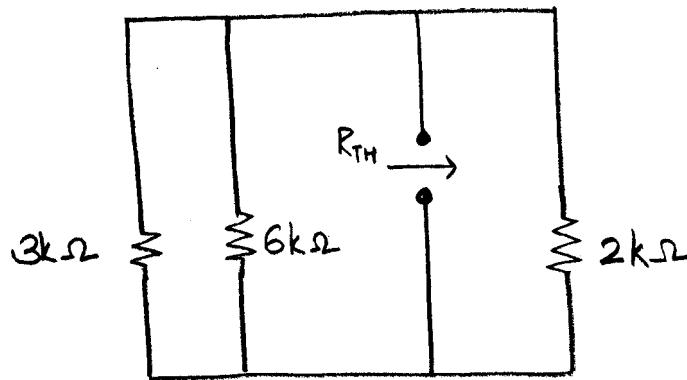


$$R_{TH} = (3k || 6k) || 2k = 1k\Omega$$

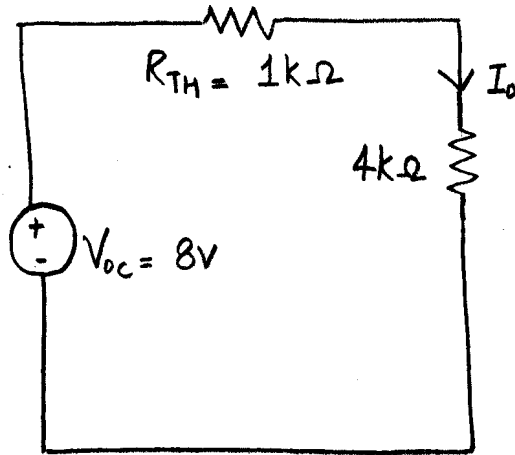


$$I_o = \frac{8}{1k + 4k} = 1.6mA$$

5.37 Find  $I_o$  in the network in the Fig. P5.37 using Thévenin's theorem.

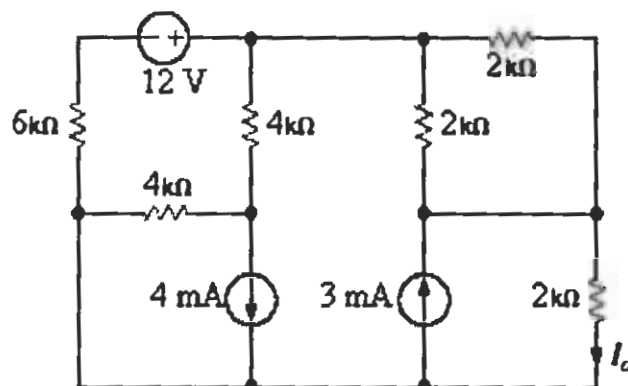


**Figure P5.37**

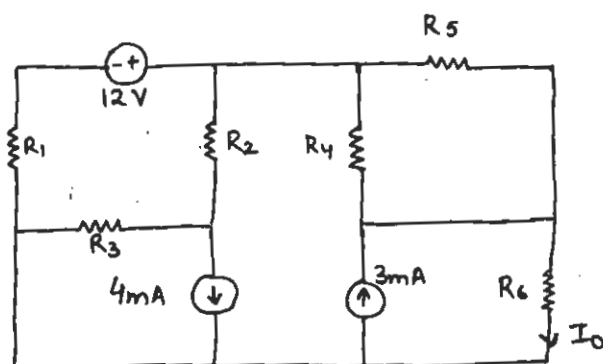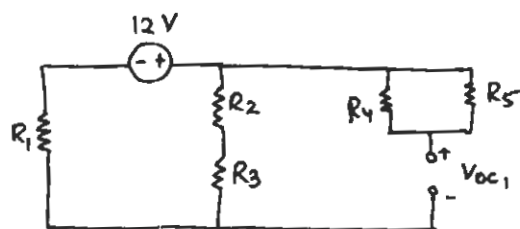
**Solution:** 5.37



$$R_1 = 6\text{ k}\Omega, R_2 = R_3 = 4\text{ k}\Omega, R_4 = R_5 = R_6 = 2\text{ k}\Omega$$


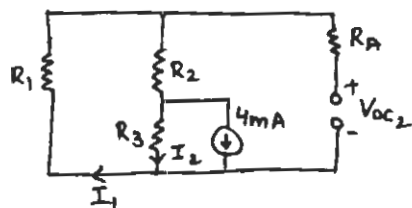
$$V_{oc1} = 12 \frac{R_2 + R_3}{R_1 + R_2 + R_3} = 6.86\text{ V}$$




$$R_A = R_4 \parallel R_5 = 1\text{ k}\Omega$$

$$I_1 = 4 \times 10^{-3} \cdot \frac{R_3}{R_1 + R_2 + R_3} = 1.14\text{ mA}$$

$$I_2 = -4 \times 10^{-3} \cdot \frac{R_1 + R_2}{R_1 + R_2 + R_3} = -2.86\text{ mA}$$

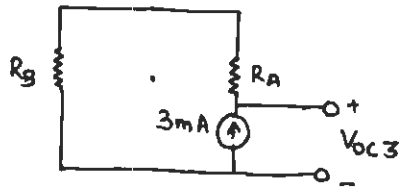
$$V_{oc2} = I_1 R_2 + I_2 R_3 = -6.87\text{ V}$$




$$R_B = R_1 \parallel (R_2 + R_3) = 3.43 \text{ k}\Omega$$

$$V_{OC3} = 3 \times 10^{-3} (R_A + R_B) = 13.3 \text{ V}$$
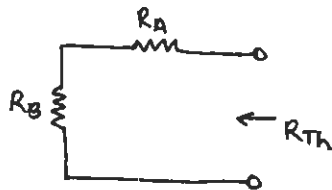
$$V_{OC} = V_{OC1} + V_{OC2} + V_{OC3} = 13.3 \text{ V}$$


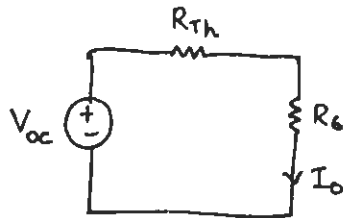
$$R_{TH} = R_A + R_B = 4.43 \text{ k}\Omega$$




$$I_O = \frac{V_{OC}}{R_L + R_{TH}}$$

$$= \frac{13.284}{2 + 4.428}$$

$$= 2.0665 = 2.07 \text{ mA}$$


$$\boxed{I_O = 2.07 \text{ mA}}$$

**5.38** Given the linear circuit in Fig. P5.38, it is known that when a  $2\text{-k}\Omega$  load is connected to the terminals  $A$ - $B$ , the load current is  $16\text{ mA}$ . If a  $14\text{-k}\Omega$  load is connected to the terminals, the load current is  $14\text{ mA}$ . Find the current in a  $28\text{-k}\Omega$  load.

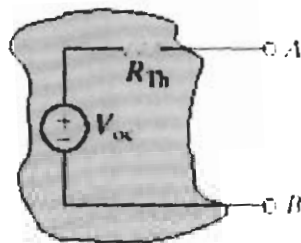

**Figure P5.38**

Solution: 5.38

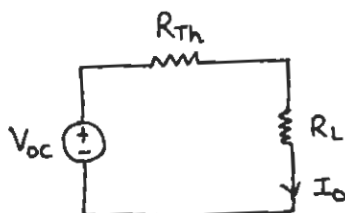

$$I_0 = \frac{V_{oc}}{R_{Th} + R_L} \quad \text{--- (1)}$$

Case 1  $R_L = 2\text{ k}\Omega$ ,  $I_0 = 16\text{ mA}$

From equation (1) :  $16 \times 10^{-3} = \frac{V_{oc}}{R_{Th} + 2 \times 10^3}$

$$V_{oc} = 16 \times 10^{-3} (R_{Th} + 2 \times 10^3) \quad \text{--- (2)}$$

Case 2  $R_L = 14\text{ k}\Omega$ ,  $I_0 = 14\text{ mA}$

From equation (1) :  $14 \times 10^{-3} = \frac{V_{oc}}{R_{Th} + 14 \times 10^3}$

$$V_{oc} = 14 \times 10^{-3} (R_{Th} + 14 \times 10^3) \quad \text{--- (3)}$$

From equations (2) and (3), we get

$$R_{Th} = 82\text{ k}\Omega, \quad V_{oc} = 1344\text{ V}$$

Case 3  $R_L = 28\text{ k}\Omega$

$$I_0 = \frac{V_{oc}}{R_{Th} + R_L}$$

$$\boxed{I_0 = 12.2\text{ mA}}$$

- 5.39 If an  $8\text{-k}\Omega$  load is connected to the terminals of the network in Fig. P5.39,  $V_{AB} = 16\text{ V}$ . If a  $2\text{-k}\Omega$  load is connected to the terminals,  $V_{AB} = 8\text{ V}$ . Find  $V_{AB}$  if a  $20\text{-k}\Omega$  load is connected to the terminals.


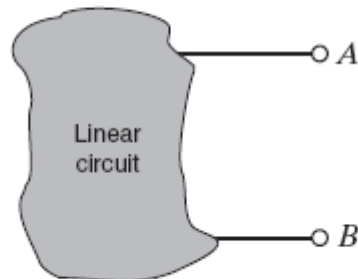


Figure P5.39

**SOLUTION:**

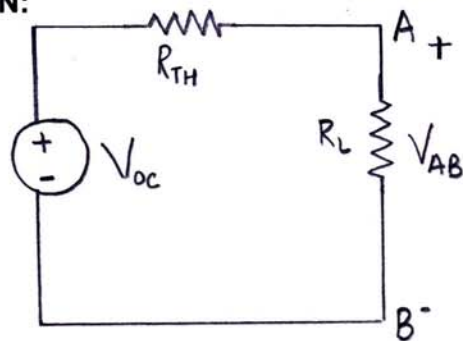

$$V_{AB} = \left( \frac{R_L}{R_L + R_{TH}} \right) (V_{oc})$$

$$16 = \left( \frac{8k}{8k + R_{TH}} \right) (V_{oc})$$

$$V_{oc} = \frac{16(8k + R_{TH})}{8k}$$

$$8 = \left( \frac{2k}{2k + R_{TH}} \right) (V_{oc})$$

$$\frac{16(8k + R_{TH})}{8k} = \frac{8(2k + R_{TH})}{2k}$$

$$R_{TH} = 4k\Omega$$

$$V_{oc} = \frac{16(8k + 4k)}{8k} = 24V$$

$$V_{AB} = \left( \frac{20k}{20k + 4k} \right) (24) = 20V$$



5.40 Find  $I_o$  in the network in Fig. P5.40 using Norton's theorem.



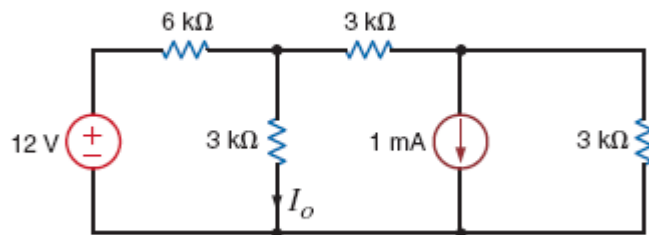
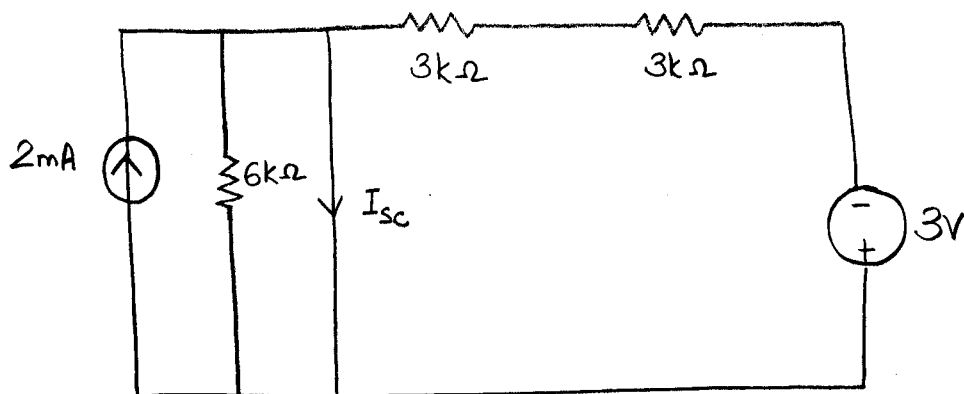


Figure P5.40


**SOLUTION:**

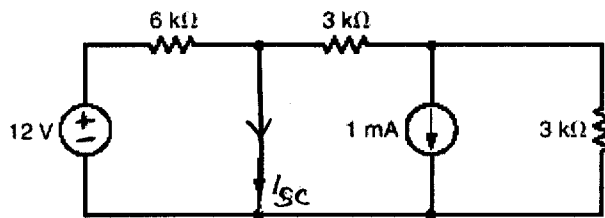


$$R' = 6k \parallel 6k = 3k\Omega$$

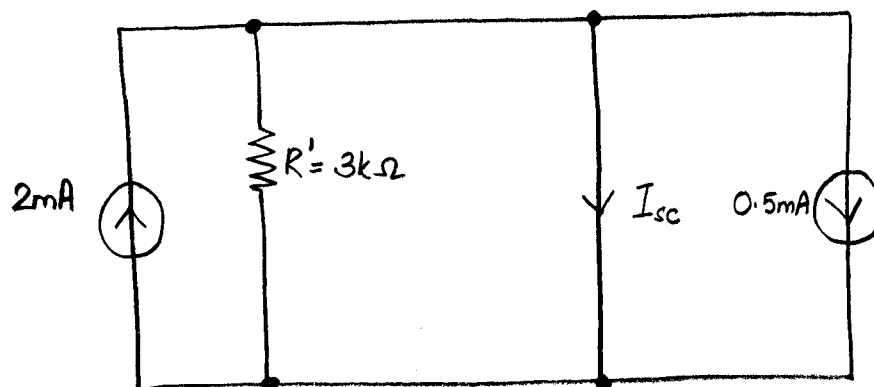

$$I_{sc} = 2m - 0.5m = 1.5mA$$

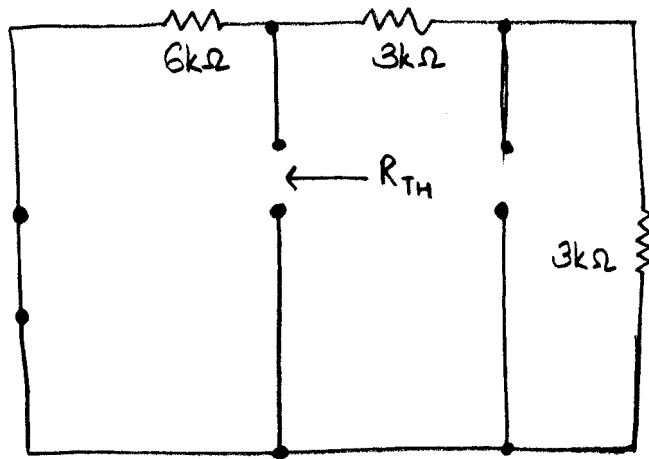
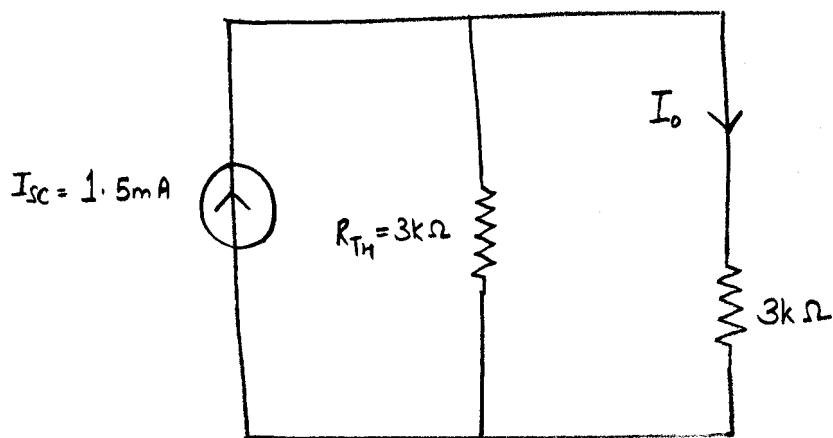
$$R_{TH} = (6k \parallel 6k) = 3k\Omega$$



$$I_o = \left( \frac{3k}{3k + 3k} \right) (1.5m) = 0.75mA$$

5.41 Use Norton's theorem to find  $I_o$  in the circuit in Fig. P5.41.



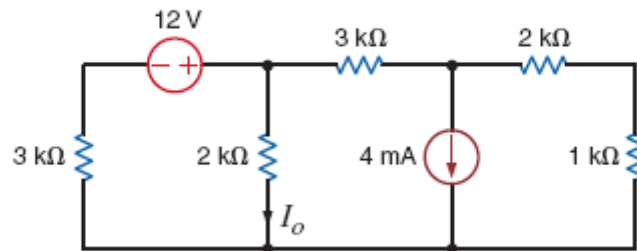


Figure P5.41



**SOLUTION:**

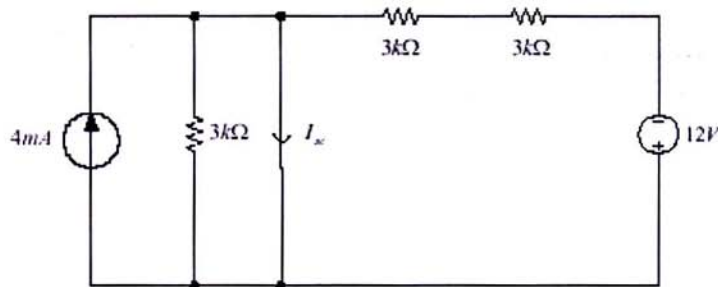


$$R' = 6k \parallel 3k = 2k \Omega$$

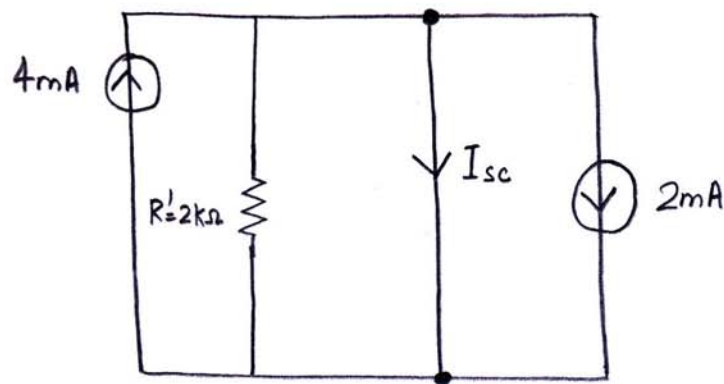

$$I_{sc} = 4m - 2m = 2mA$$

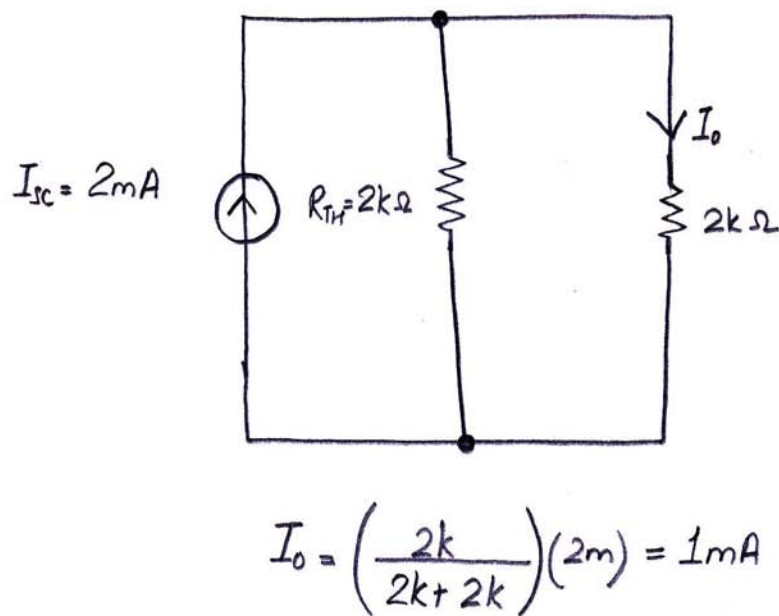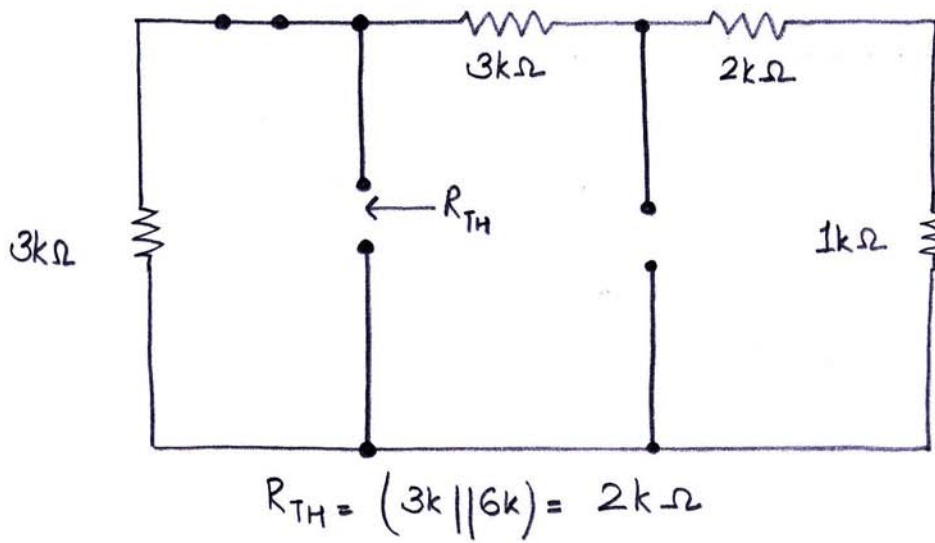


5.42 Use Norton's theorem to find  $I_o$  in the circuit in Fig. P5.42.

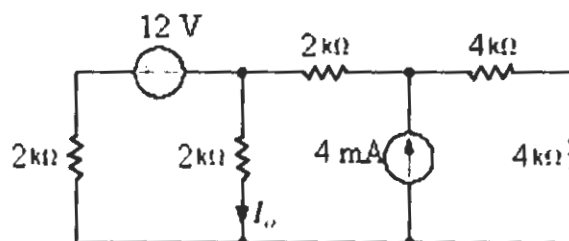


**Figure P5.42**

Solution: 5.42

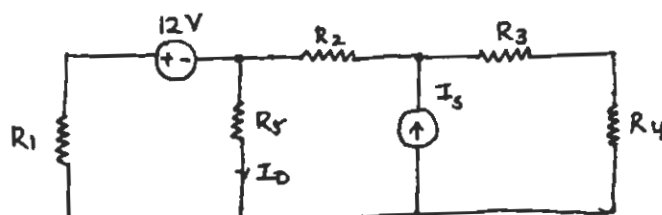

$$R_1 = R_2 = R_5 = 2\text{ k}\Omega; R_3 = R_4 = 4\text{ k}\Omega, I_s = 4\text{ mA}$$

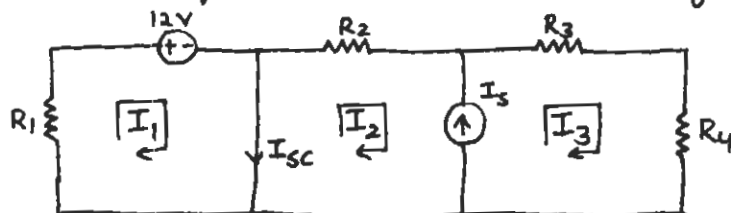[To apply Norton's theorem we first short circuit current]



$$I_1 = \frac{-12}{R_1} = -6\text{ mA}$$

$$R_2 I_2 + (R_3 + R_4) I_3 = 0 \quad \text{---} \quad \textcircled{1}$$

$$I_3 - I_2 = I_s = 4\text{ mA} \quad \text{---} \quad \textcircled{2}$$


From equations  $\textcircled{1}$  and  $\textcircled{2}$

$$I_3 = 0.8\text{ mA}$$

$$I_2 = -3.2\text{ mA}$$

$$I_{sc} = I_1 - I_2 = -2.8\text{ mA}$$
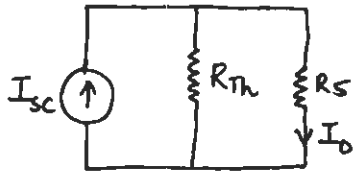
$$R_{Th} = R_1 \parallel (R_2 + R_3 + R_4) = \frac{5}{3}\text{ k}\Omega$$



$$I_o = I_{sc} \frac{R_{Th}}{R_{Th} + R_S}$$

$$I_o = -1.27 \text{ mA}$$

5.43 Find  $I_o$  in the network in Fig. P5.43 using Norton's theorem.


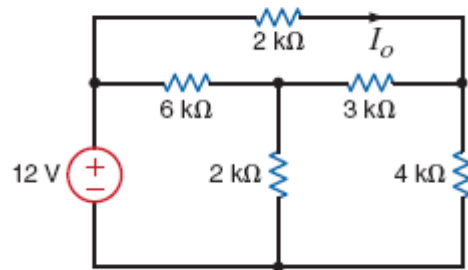


Figure P5.43

**SOLUTION:**

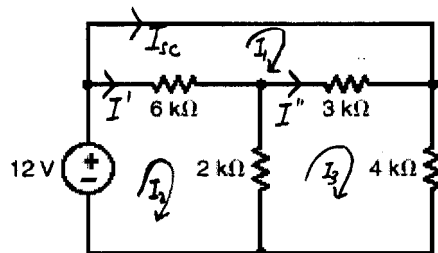

$$\begin{aligned}
 I_1 &= I_{sc} \\
 I_2 &= I' + I_{sc} \\
 I' &= I_2 - I_1 \\
 I'' + I_1 &= I_3 \\
 I'' &= I_3 - I_1 \\
 I &= I_2 - I_3
 \end{aligned}$$

$$\text{KVL left loop: } 12 = 6kI' + 2kI$$

$$12 = 6k(I_2 - I_1) + 2k(I_2 - I_3)$$

$$\text{KVL right loop: } 3kI'' + 4kI_3 - I(2k) = 0$$

$$3k(I_3 - I_1) + 4kI_3 - (I_2 - I_3)(2k) = 0$$

$$-3kI_1 - 2kI_2 + 9kI_3 = 0$$

$$\text{KVL outer loop: } 12 = 4k I_3$$

$$I_3 = 3mA$$

$$-3k I_1 - 2k I_2 = -27$$

$$12 = -6k I_1 + 8k I_2 - 2k(3mA)$$


$$-6k I_1 + 8k I_2 = 18$$

$$-3k I_1 - 2k I_2 = -27$$


$$I_1 = 5mA$$

$$I_2 = 6mA$$

$$I_{sc} = 5mA$$

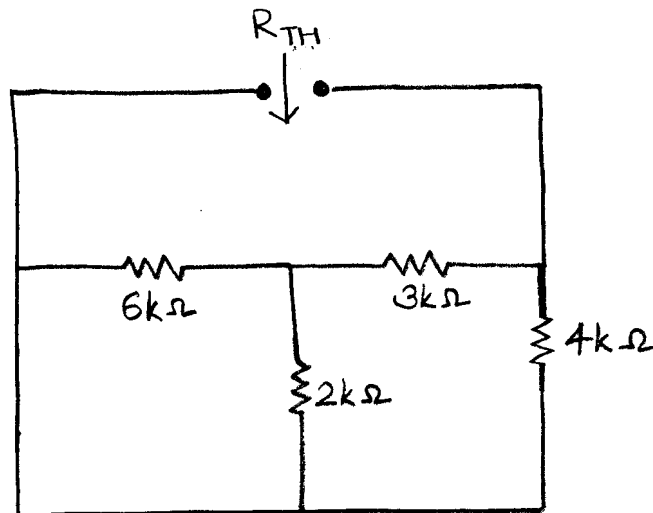


$$R_{TH} = [(6k || 2k) + 3k] || 4k = 2.12k\Omega$$

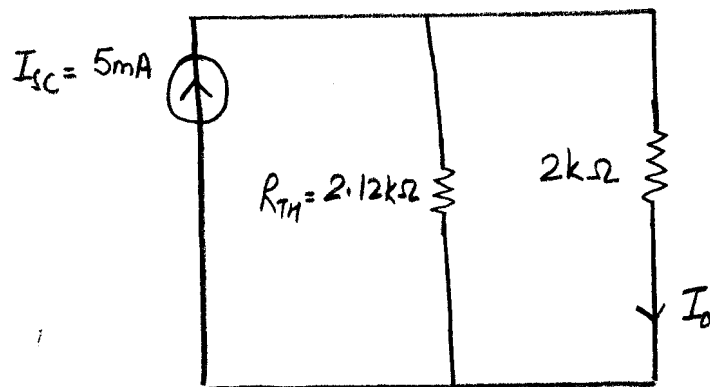




$$I_0 = \left( \frac{2.12k}{2.12k + 2k} \right) (5m) = 2.57mA$$

5.44 Use Norton's theorem to find  $V_o$  in the network in Fig. P5.44.

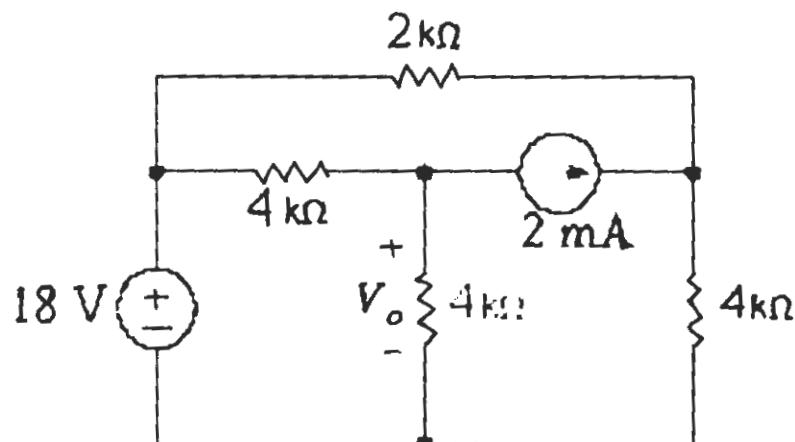


**Figure P5.44**

Solution: 5.44

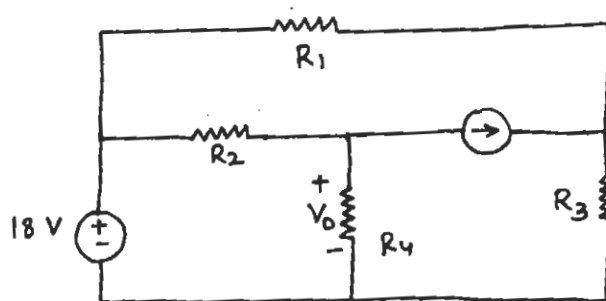


$$R_1 = 2\text{ k}\Omega,$$

$$R_2 = R_3 = R_4 = 4\text{ k}\Omega$$

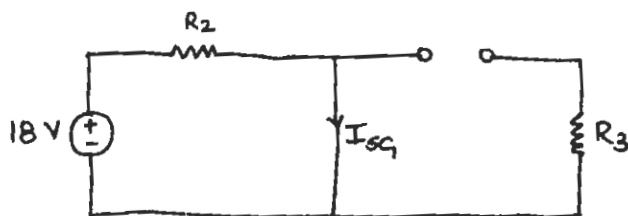

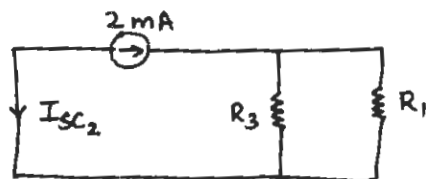
$$I_{sc1} = \frac{18}{R_2} = 4.5\text{ mA}$$




$$I_{sc2} = -2\text{ mA}$$
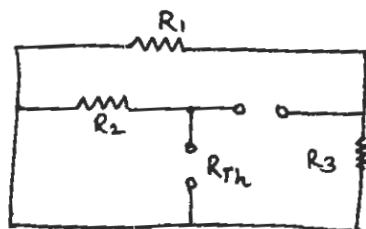
$$I_{sc} = I_{sc1} + I_{sc2} = 2.50\text{ mA}$$



$$R_{th} = R_2 = 4\text{ k}\Omega$$

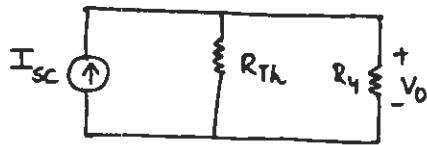

$$V_o = I_{sc} [R_{Th} || R_L]$$

$$V_o = 5.00 \text{ V}$$

5.45 Use Norton's theorem to find  $V_o$  in the network in Fig. P5.45.



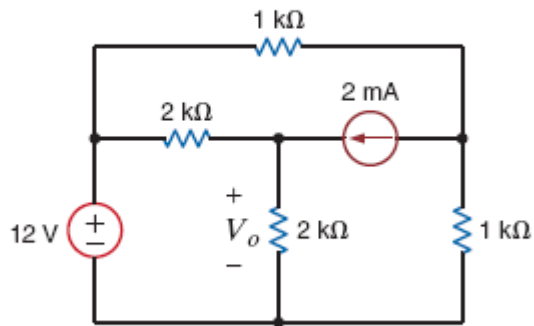
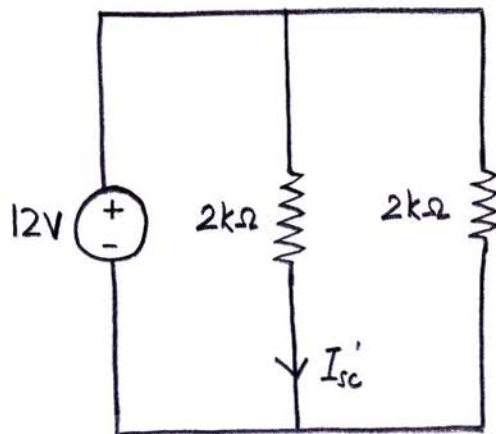
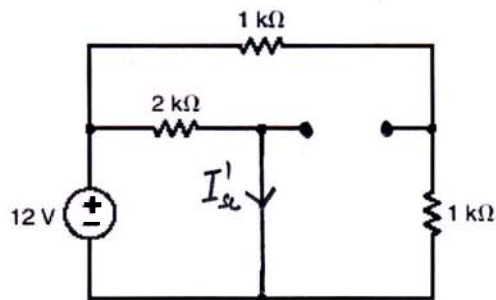


Figure P5.45

**SOLUTION:**

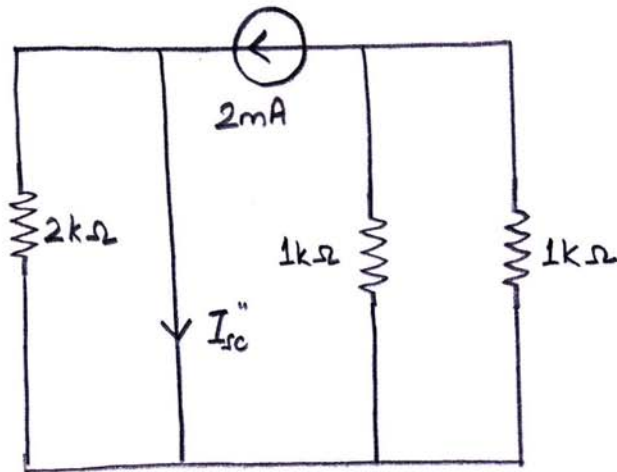


$$I'_{sc} = \frac{12}{2k} = 6\text{mA}$$

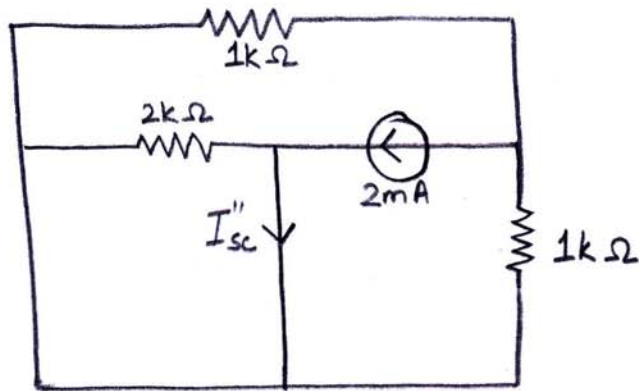


$$I_{sc}'' = 2mA$$

$$I_{sc} = 6mA + 2mA = 8mA$$

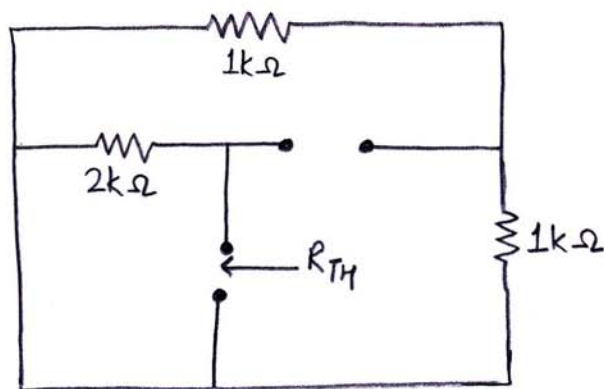

$$R_{TH} = 2k\Omega$$

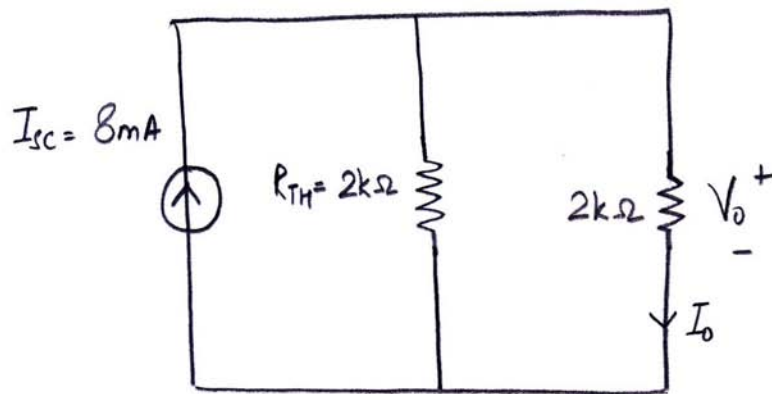

$$I_o = \left( \frac{2\text{k}}{2\text{k} + 2\text{k}} \right) (8\text{mA}) = 4\text{mA}$$

$$V_o = 2\text{k}(4\text{mA}) = 8\text{V}$$

5.46 Find  $V_o$  in the network in Fig. P5.46 using Norton's theorem.



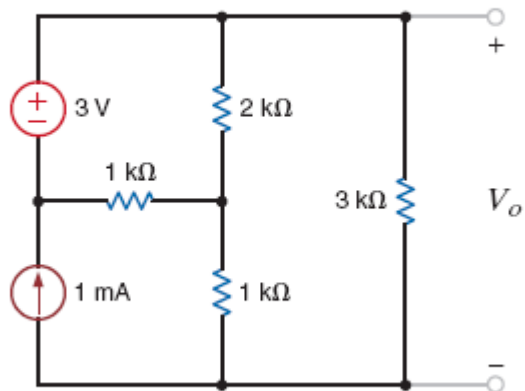



Figure P5.46

**SOLUTION:**

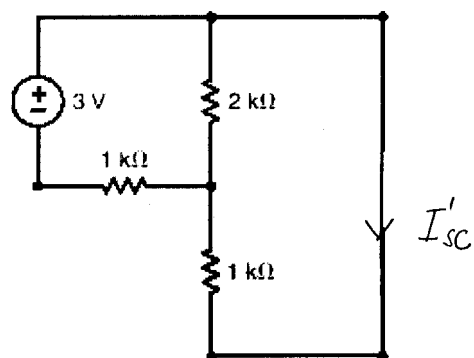


$$R' = 1k \parallel 2k = 667\Omega$$

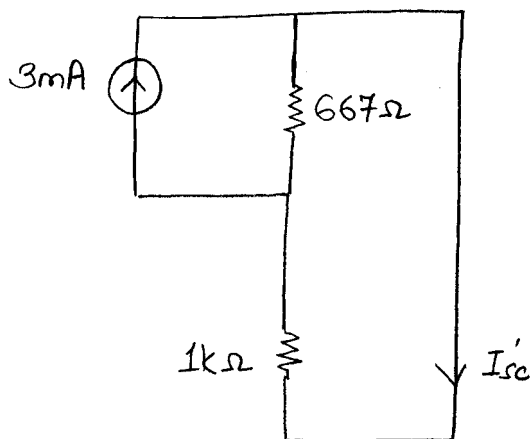

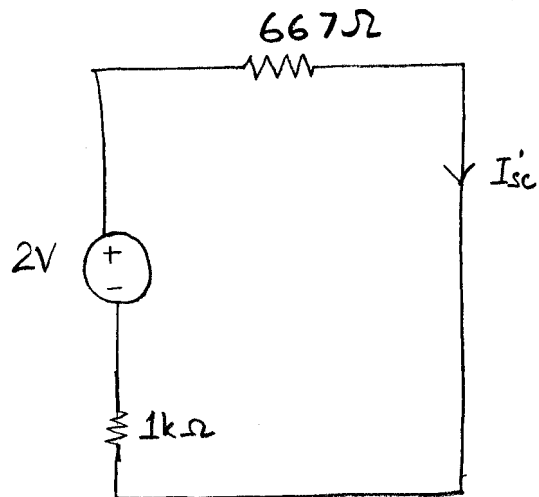

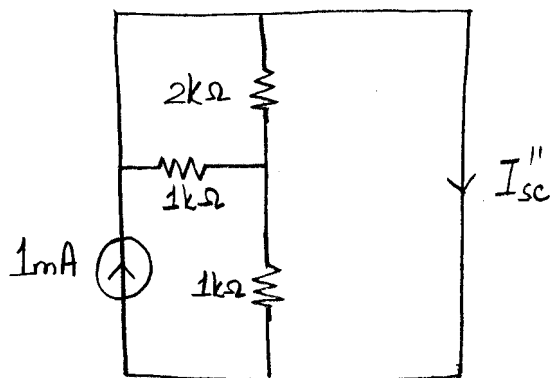
$$I'_{sc} = \frac{2}{1k + 667} = 1.2\text{mA}$$




$$I''_{sc} = 1\text{mA}$$
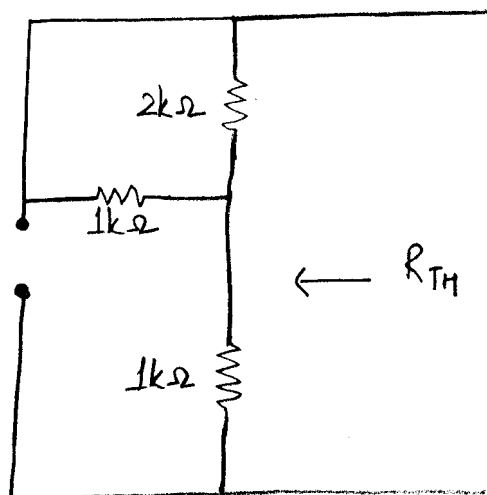
$$I_{sc} = 1.2\text{m} + 1\text{m} = 2.2\text{mA}$$





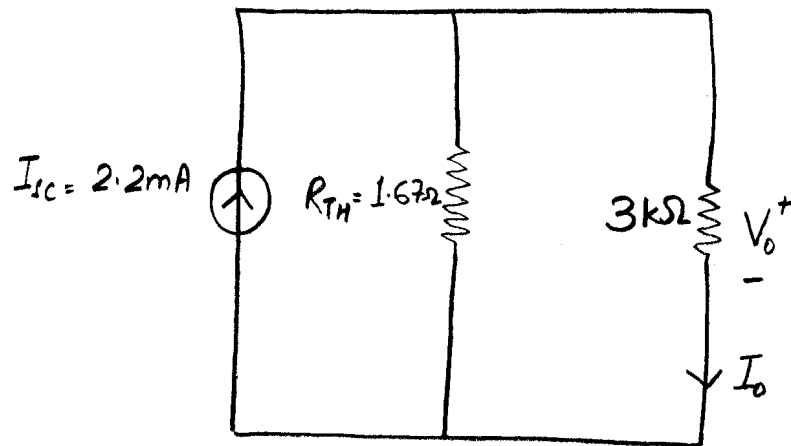
$$R_{TH} = (1k \parallel 2k) + 1k = 1.67 \Omega$$



$$I_o = \left( \frac{1.67 \text{ k}}{1.67 \text{ k} + 3 \text{ k}} \right) (2.2 \text{ m}) = 0.787 \text{ mA}$$


$$V_o = (0.787 \text{ m})(3 \text{ k}) = 2.36 \text{ V}$$

5.47 Find  $I_o$  in the network in Fig. P5.47 using Norton's theorem.

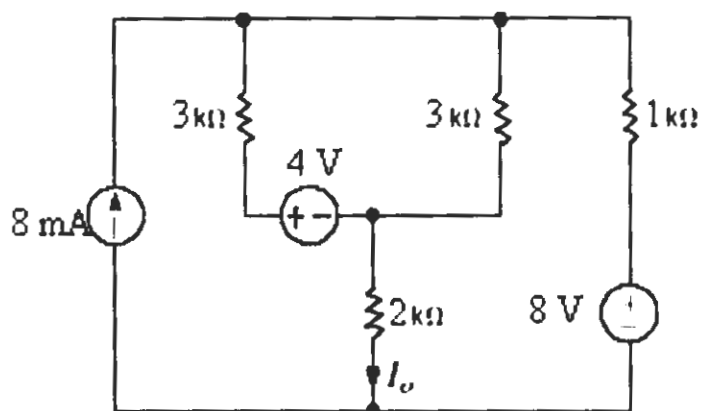


**Figure P5.47**

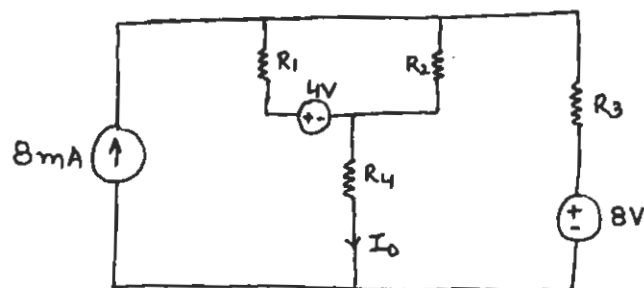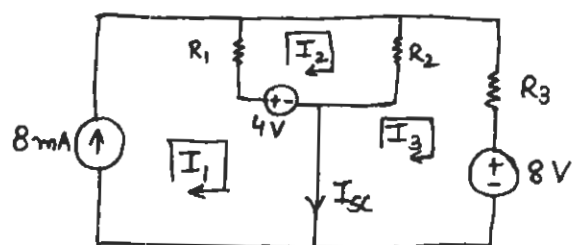Solution: 5.47



$$R_1 = R_2 = 3 \text{ k}\Omega; R_3 = 1 \text{ k}\Omega; R_4 = 2 \text{ k}\Omega$$



$$I_1 = 8 \text{ mA} \quad \text{---} \quad \textcircled{1}$$

$$\text{KVL @ } I_2 : (I_2 - I_1)R_1 + (I_2 - I_3)R_2 - 4 = 0$$

$$6I_2 - 3I_3 = 28 \times 10^{-3} \quad \text{---} \quad \textcircled{2}$$


$$\text{KVL @ } I_3 : (I_3 - I_2)R_2 + I_3R_3 + 8 = 0$$

$$4I_3 - 3I_2 = -8 \times 10^{-3} \quad \text{---} \quad \textcircled{3}$$


From equations ② and ③, we get

$$I_3 = 2.4 \text{ mA}$$

$$I_{sc} = I_1 - I_3 = 5.6 \text{ mA}$$

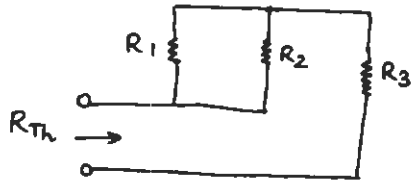
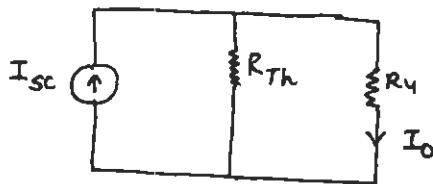
$$R_{th} = (R_1 \parallel R_2) + R_3 = 2.5 \text{ k}\Omega$$



$$I_o = I_{sc} \frac{R_{th}}{R_{th} + R_4}$$

$$I_o = 3.11 \text{ mA}$$

5.48 Find  $V_o$  in the circuit in Fig. P5.48 using Norton's theorem.



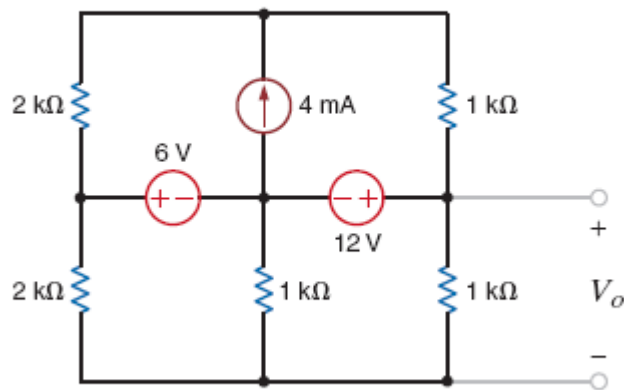
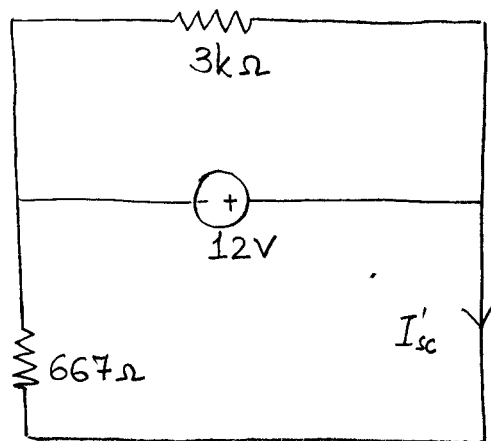
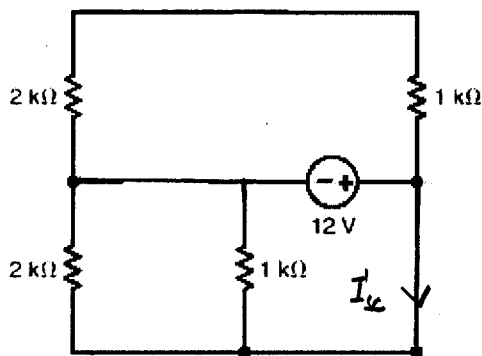


Figure P5.48

**SOLUTION:**

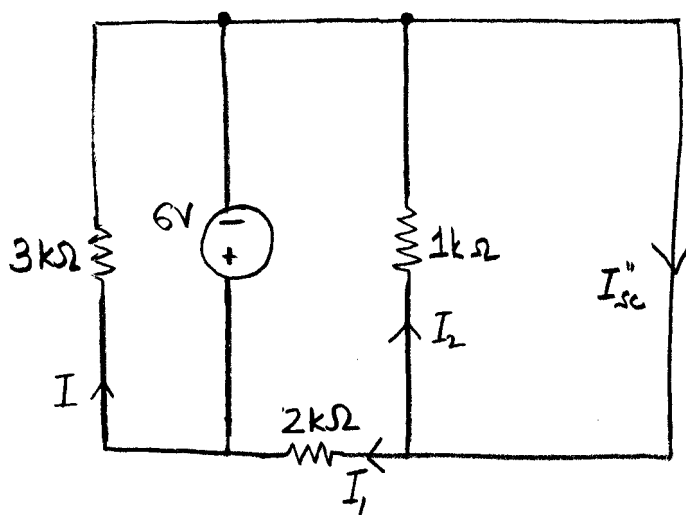



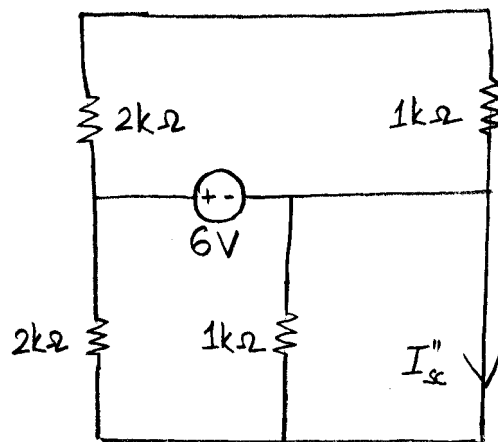
$$I'_{sc} = \frac{12}{667} = 18 \text{ mA}$$



$$I = \frac{6}{3k} = 2\text{mA}$$

$$\text{KVL around the outer loop: } 3kI + 2kI_1 = 0$$


$$I_{sc}'' = I_1 = -3\text{mA}$$

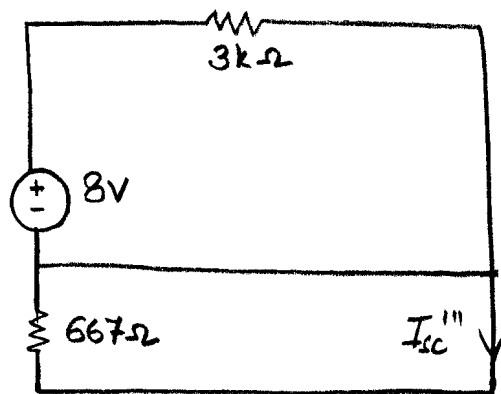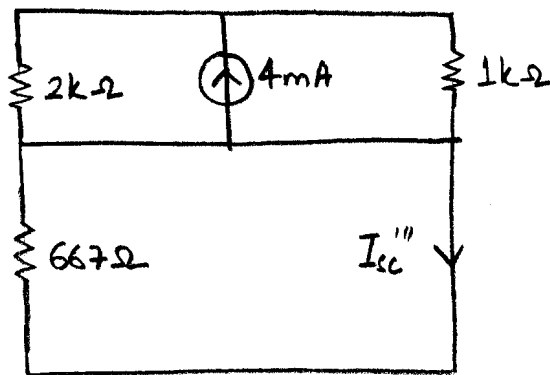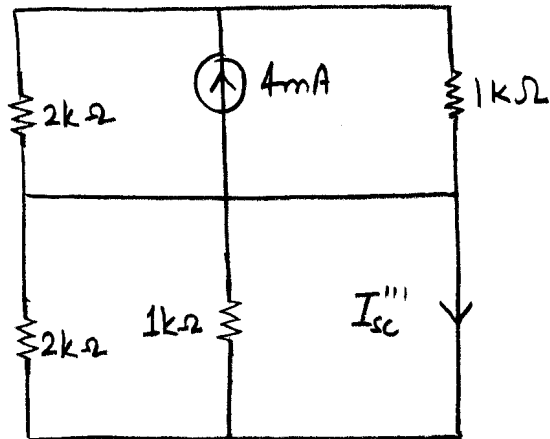


KVL around outer loop yields:

$$I_{sc}''' = 0A$$

$$I_{sc} = 18m - 3m + 0 = 15mA$$

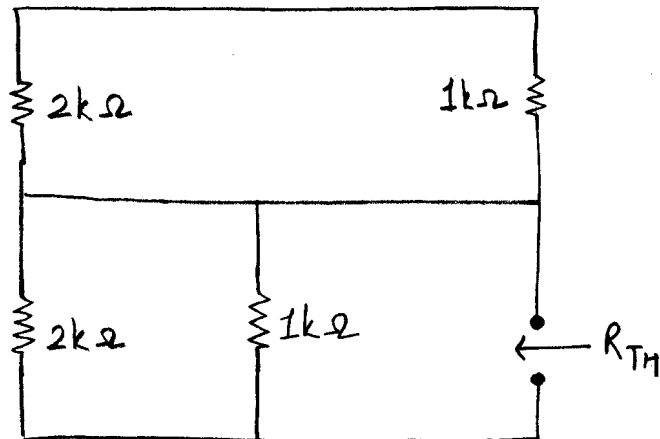

$$R_{TH} = 2k \parallel 1k = 667\Omega$$

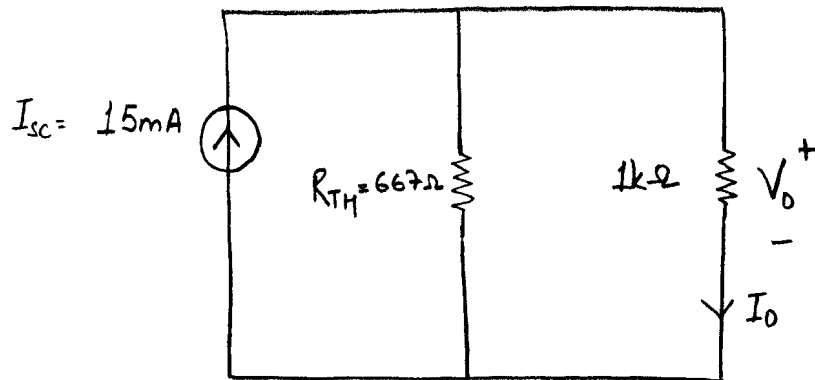

$$I_0 = \left( \frac{667}{667 + 1k} \right) (15m) = 6mA$$

$$V_0 = 6m(1k) = 6V$$

5.49 Use Norton's theorem to find  $I_o$  in the network in Fig. P5.49.



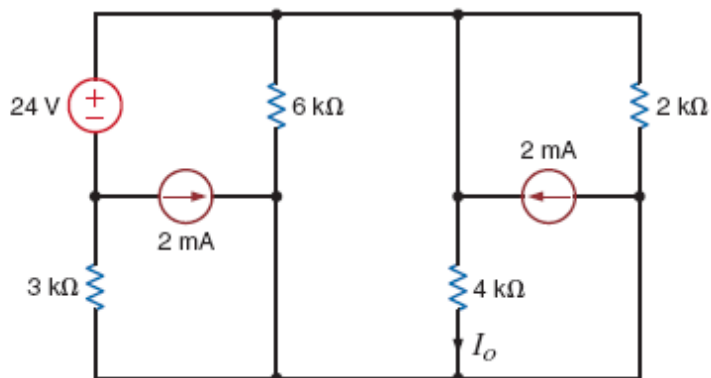




Figure P5.49

**SOLUTION:**

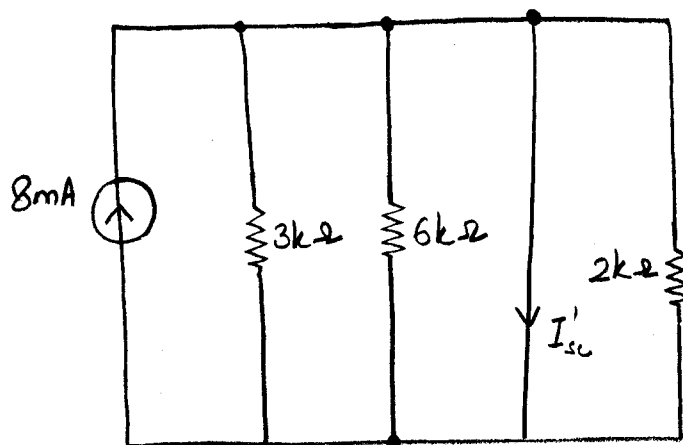




$$I'_{sc} = 8 \text{ mA}$$

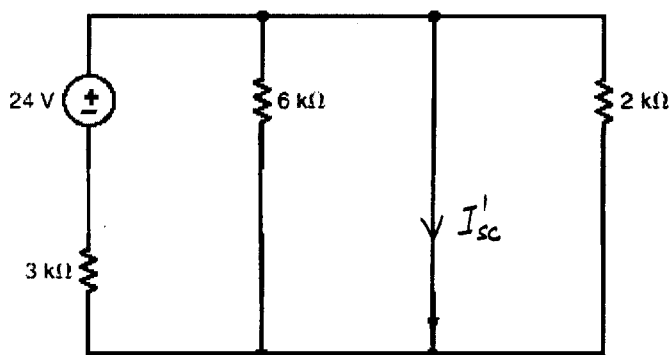

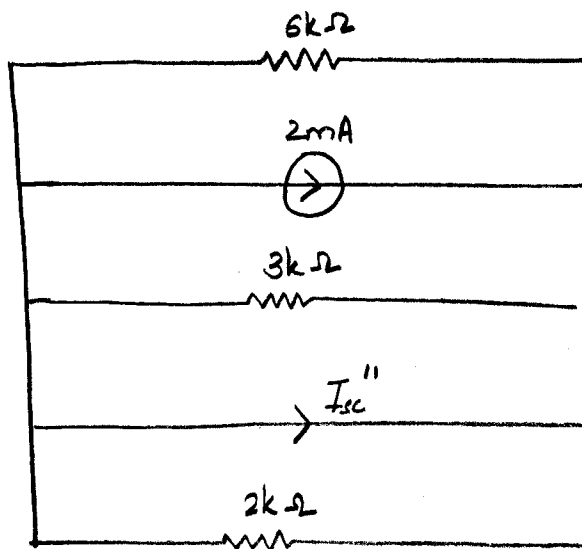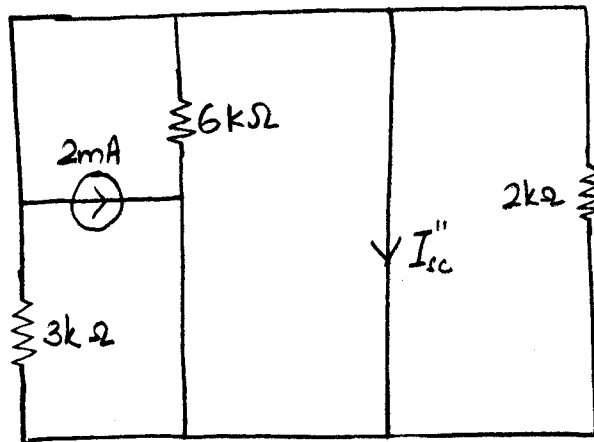


$$I_{sc}'' = -2\text{mA}$$

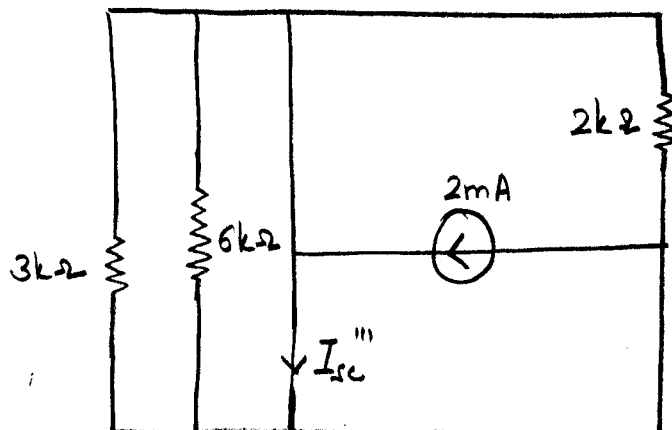

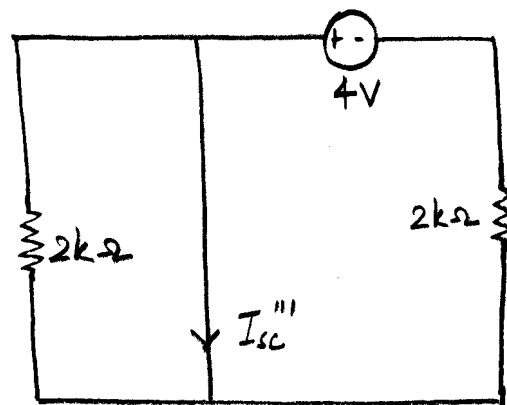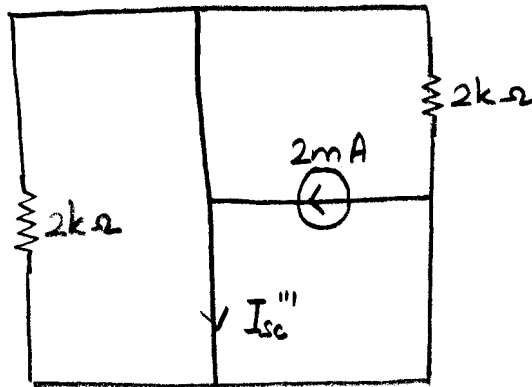


$$I_{sc}''' = \frac{4}{2k} = 2mA$$

$$I_{sc} = 8mA - 2mA + 2mA = 8mA$$

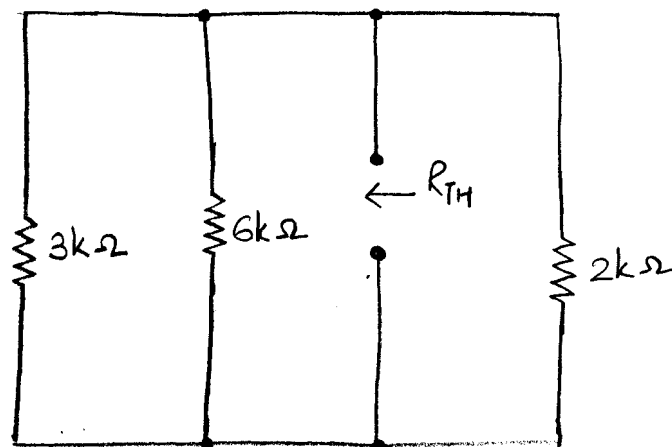

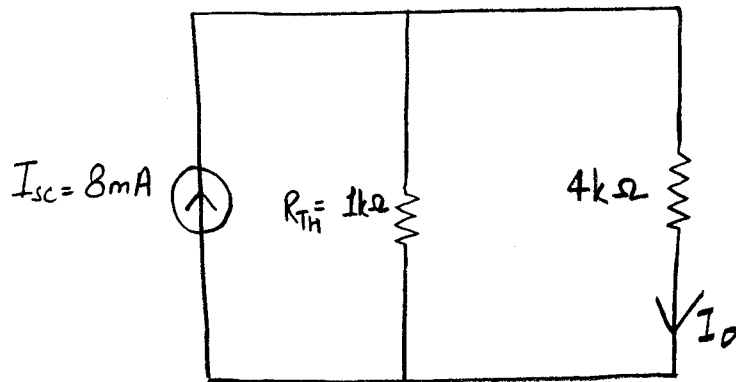
$$R_{TH} = (3k \parallel 6k) \parallel 2k = 1k\Omega$$




$$I_o = \left( \frac{1k}{1k + 4k} \right) (8m) = 1.6mA$$

5.50 Find  $I_o$  in the network in the Fig. P5.50 using Norton's theorem.

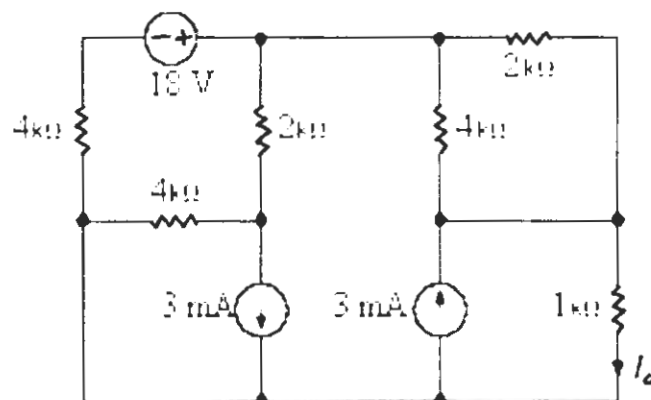


**Figure P5.50**

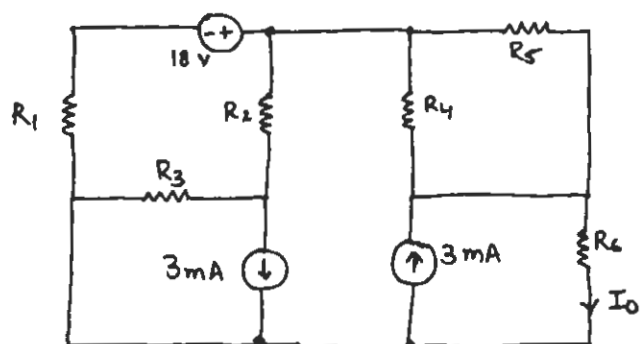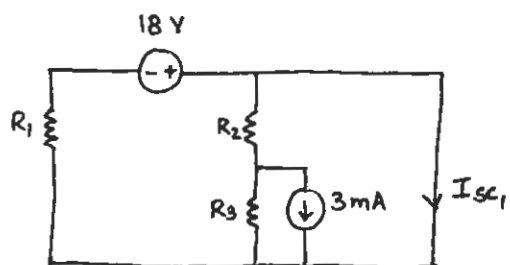Solution: 5.50




$$R_1 = R_3 = R_4 = 4 \text{ k}\Omega ; R_2 = R_5 = 2 \text{ k}\Omega ; R_6 = 1 \text{ k}\Omega$$



Using Superposition

$$I_{sc1} = \frac{18}{R_1} - 3 \times 10^{-3} \cdot \frac{R_3}{R_2 + R_3}$$

$$I_{sc1} = 2.5 \text{ mA}$$

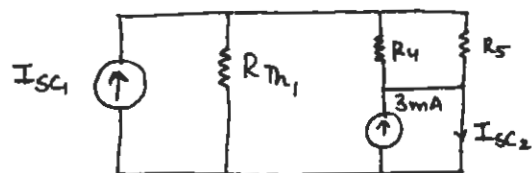

$$R_{Th1} = R_1 \parallel (R_2 + R_3) = 2.4 \text{ k}\Omega$$

$$R_A = R_4 \parallel R_5 = \frac{4}{3} \text{ k}\Omega$$

$$I_{sc2} = 3 \times 10^{-3} + I_{sc1} \cdot \frac{R_{Th1}}{R_{Th1} + R_A}$$

$$\begin{aligned}I_{SC2} &= 4.61 \text{ mA} \\R_{Th2} &= R_{Th1} + R_4 = 3.73 \text{ k}\Omega \\I_0 &= I_{SC2} \frac{R_{Th2}}{R_{Th2} + R_6} \\I_0 &= 3.63 \text{ mA}\end{aligned}$$

5.51 Find  $V_o$  in the network in Fig. P5.51 using Thévenin's theorem.


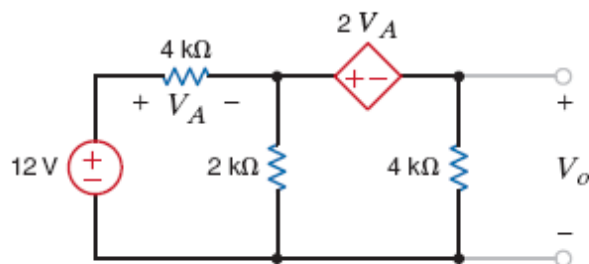


Figure P5.51


**SOLUTION:**

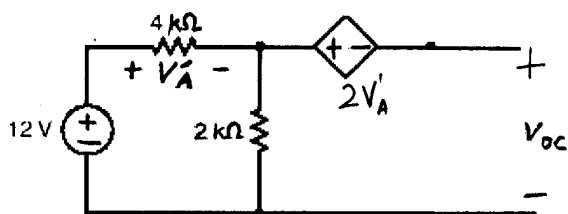

$$V'_A = \left( \frac{4k}{4k+2k} \right) (12) = 8V$$

$$12 = V'_A + 2V'_A + V_{oc}$$

$$V_{oc} = 12 - 3(8) = -12V$$

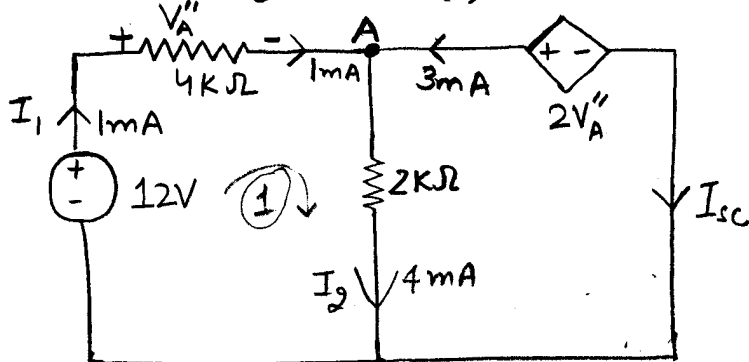

KVL around the outer loop:

$$3V''_A - 12 = 0$$

$$V''_A = 4V$$

$$\frac{V''_A}{4k} = I_1 = 1mA$$

KVL in loop (1):

$$12 = V_A'' + 2k I_2$$


$$I_2 = 4mA$$

KCL at A

$$I_1 - I_{sc} = I_2$$

$$\Rightarrow I_{sc} = I_1 - I_2 = \boxed{-3mA}$$

$$R_{TH} = \frac{-12}{-3m} = 4k\Omega$$

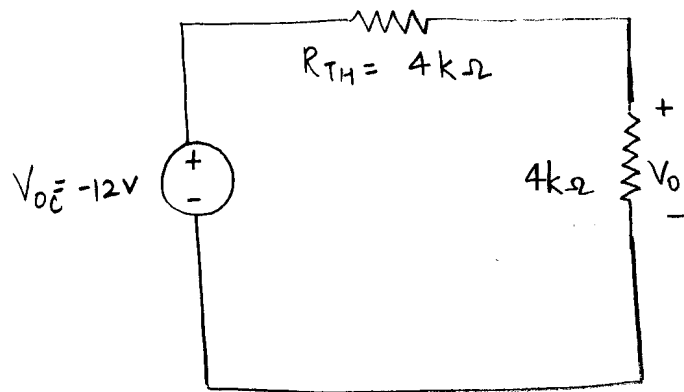

$$V_o = \left( \frac{4k}{4k + 4k} \right) (-12) = -6V$$

5.52 Use Thévenin's theorem to find  $V_o$  in the circuit in Fig. P5.52



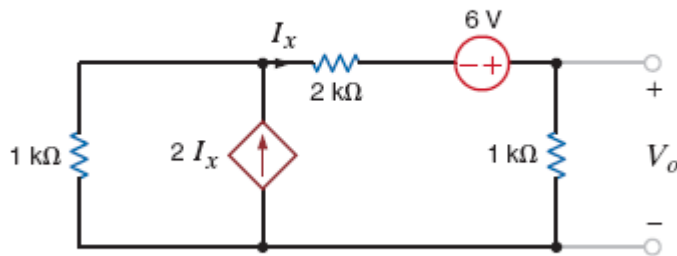


Figure P5.52

**SOLUTION:**

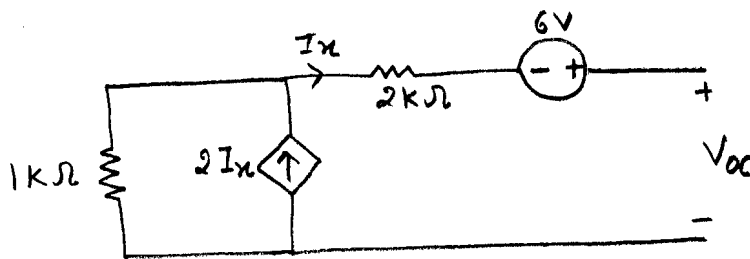

$$V_{oc} = 6V$$

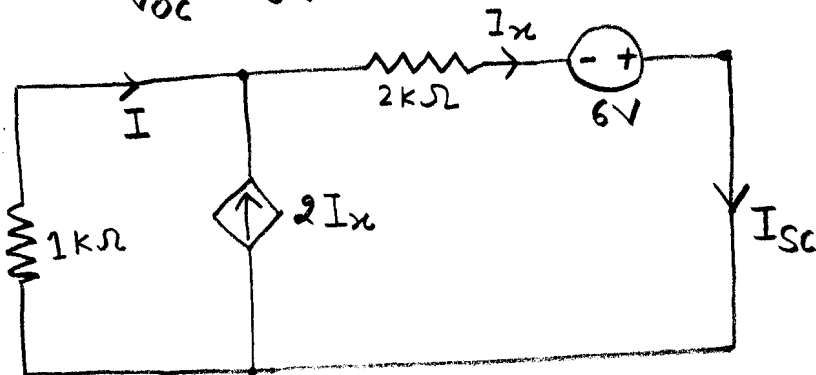

$$2I_x + I = I_x$$

$$I = -I_x$$

$$6 = I(1k) + I_x(2k)$$


$$6 = -I_x(1k) + I_x(2k)$$

$$I_x = 6mA$$

$$I_{sc} = I_x = 6mA$$



$$R_{TH} = \frac{6}{6m} = 1k\Omega$$

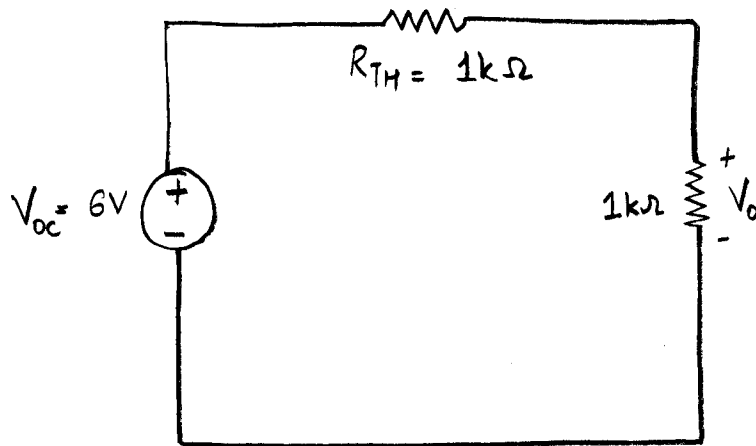

$$V_0 = \left( \frac{1k}{1k + 1k} \right) (6) = 3V$$

5.53 In the network in Fig. P5.53, find  $V_o$  using Thévenin's theorem.


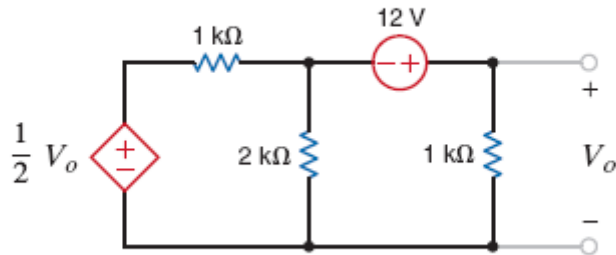


Figure P5.53

**SOLUTION:**

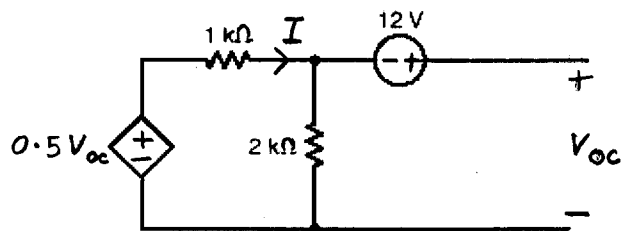


$$3kI = 0.5V_{oc}$$

$$I = 0.167mV_{oc}$$


$$V_{oc} = 2k(0.167mV_{oc}) + 12$$

$$V_{oc} = 18V$$

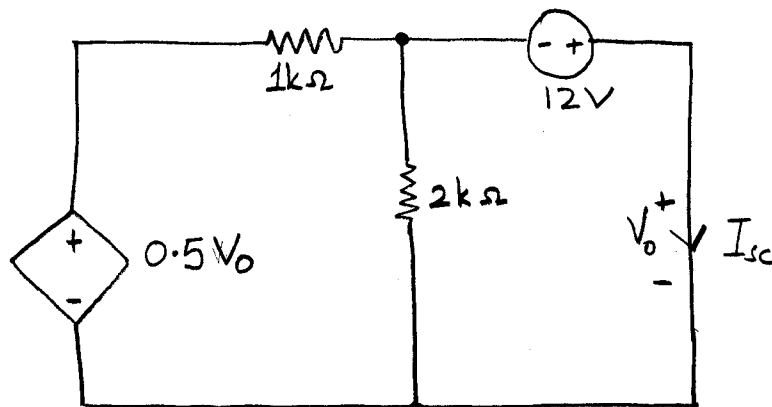

$$I_{sc} = \frac{12}{1k \parallel 2k} = 18mA$$
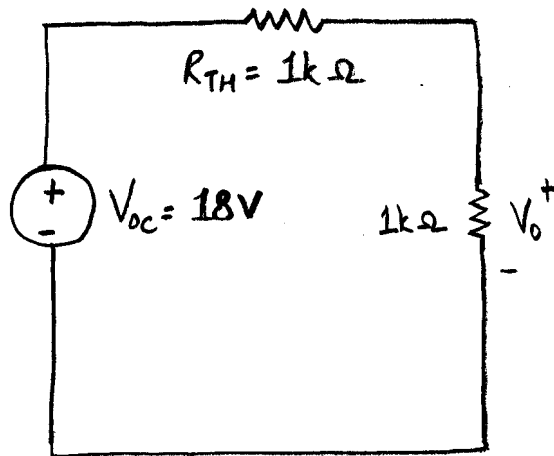
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{18}{18\text{m}} = 1\text{k}\Omega$$



$$V_o = \left( \frac{1\text{k}}{1\text{k} + 1\text{k}} \right) (18) \\ = 9\text{V}$$

5.54 Use Thévenin's theorem to find  $I_o$  in the circuit in Fig. P5.54.


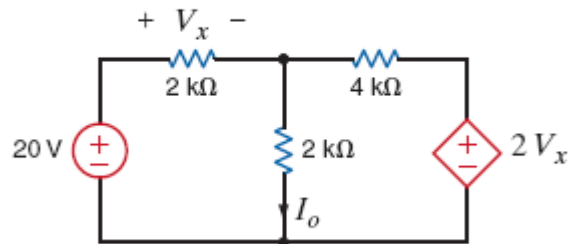


Figure P5.54

**SOLUTION:**

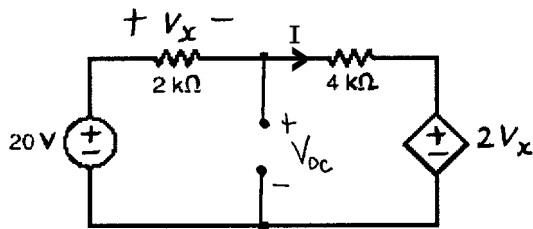

$$20 = V_x + 4kI + 2V_x$$

$$20 = 3V_x + 4kI$$

$$V_x = \frac{20 - 4kI}{3}$$

$$20 = 2kI + 4kI + 2V_x$$



$$20 = 2kI + 4kI + 2 \left[ \frac{20 - 4kI}{3} \right]$$

$$20 = 6kI + \frac{40}{3} - \frac{8k}{3}I$$

$$I = 2mA$$

$$V_x = \frac{20 - 4k(2mA)}{3} = 4V$$

$$V_{oc} = 4k(2mA) + 2(4) = 16V$$

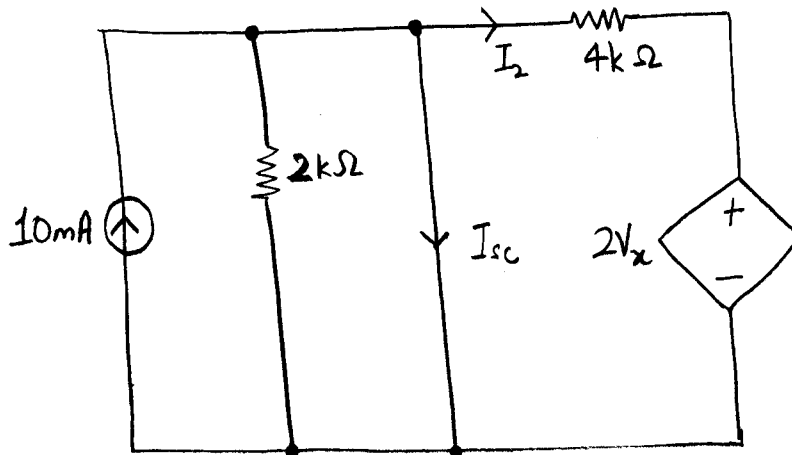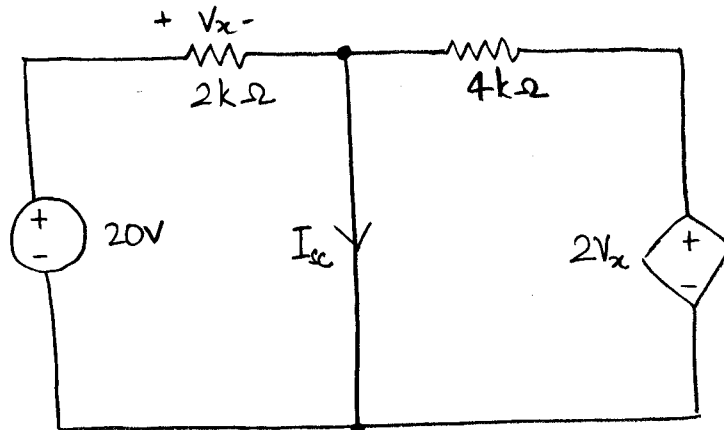

$$V_x = 20V$$


$$4kI_2 + 2V_x = 0$$

$$I_2 = -\frac{2(20)}{4k} = -10mA$$

$$10m = I_{sc} + I_2$$


$$I_{sc} = 20mA$$

$$R_{TH} = \frac{16}{20m} = 800\Omega$$

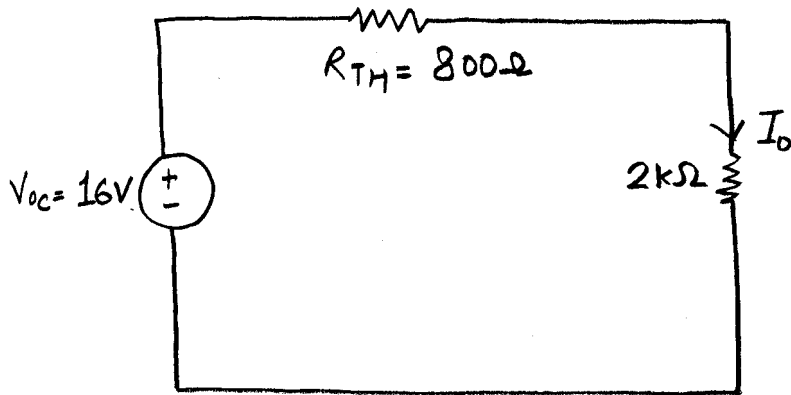


$$I_O = \left( \frac{16V}{2k + 800} \right) = 5.71mA$$

5.55 Use Thévenin's theorem to find  $I_o$  in the circuit in Fig. P5.55.

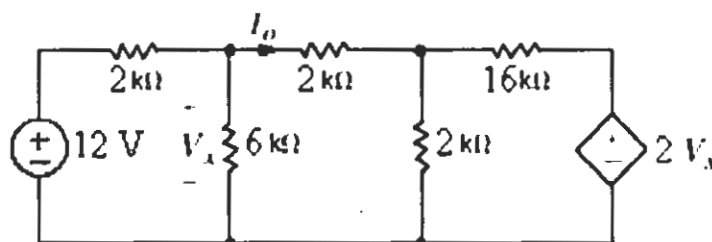


**Figure P5.55**

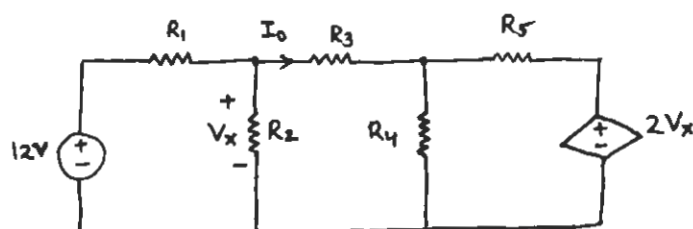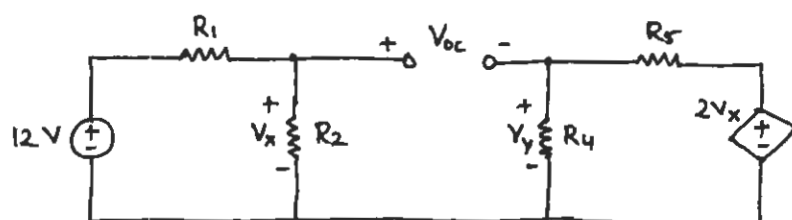Solution: 5.55




$$R_1 = R_3 = R_4 = 2 \text{ k}\Omega ; R_2 = 6 \text{ k}\Omega ; R_5 = 16 \text{ k}\Omega$$



$$V_x = 12 \cdot \frac{R_2}{R_1 + R_2} = 9 \text{ V}$$

$$V_y = 2 V_x \cdot \frac{R_4}{R_4 + R_5} = 2 \text{ V}$$

$$V_{oc} = V_x - V_y = 7 \text{ V}$$

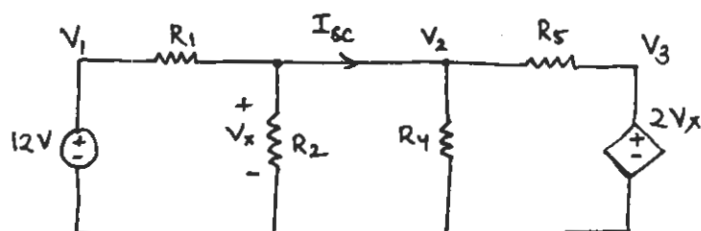


$$V_1 = 12 \text{ V}, V_2 = V_x, V_3 = 2 V_x = 2 V_2$$

$$\text{KCL @ } V_2 : \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_2}{R_4} + \frac{V_2 - V_3}{R_5} = 0$$

$$V_2 = 5.43 \text{ V}$$
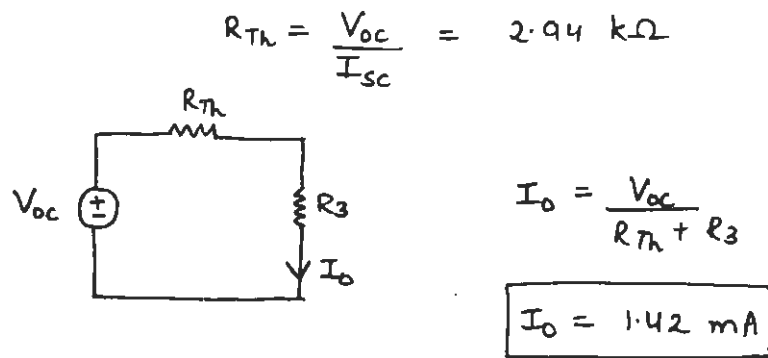
$$I_{sc} = \frac{V_1 - V_2}{R_1} - \frac{V_2}{R_2} = 2.38 \text{ mA}$$





5.56 Use Thévenin's theorem to find  $V_o$  in the circuit in Fig. P5.56.


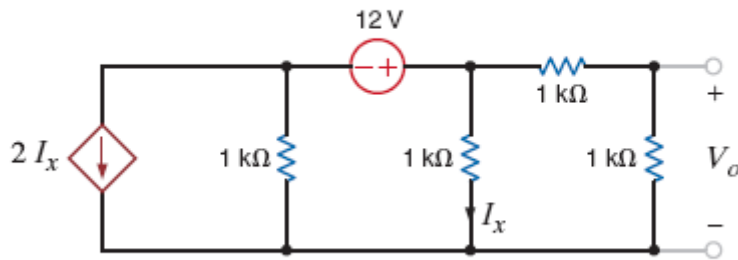


Figure P5.56

**SOLUTION:**

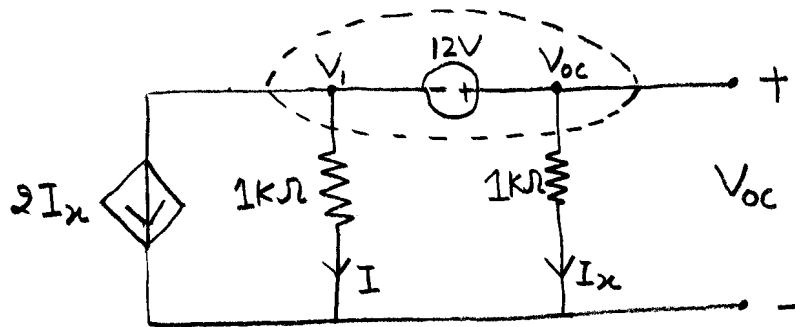

$$2I_x + \frac{V_1}{1k} + \frac{V_{oc}}{1k} = 0$$

$$V_{oc} - V_1 = 12$$

$$V_{oc} = I_x(1k)$$

$$I_x = \frac{V_{oc}}{1k}$$


$$2\left(\frac{V_{oc}}{1k}\right) + \frac{V_1}{1k} + \frac{V_{oc}}{1k} = 0$$

$$3V_{oc} + V_1 = 0$$

$$V_{oc} - V_1 = 12$$

$$V_{oc} = 3V$$

$$V_1 = -9V$$

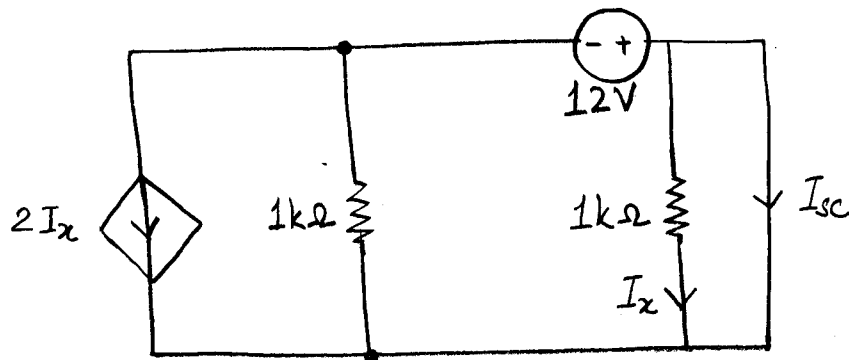


$$I_x = 0$$

$$I_{sc}(1k) = 12$$


$$I_{sc} = 12\text{mA}$$
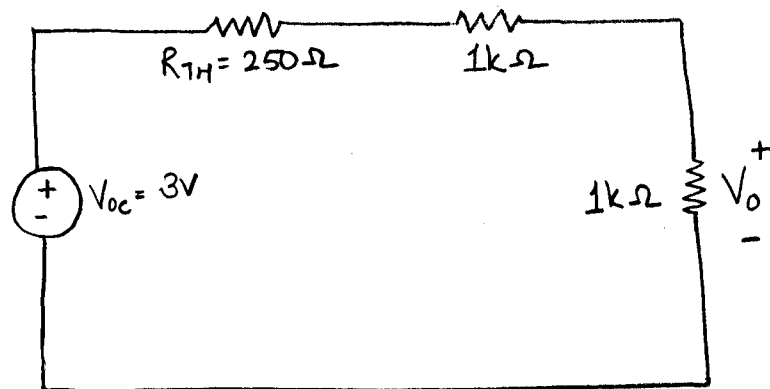
$$R_{TH} = \frac{3}{12\text{m}} = 250\Omega$$




$$V_o = \left( \frac{1k}{1k + 1k + 250} \right) (3) = 1.33\text{V}$$

5.57 Find  $V_o$  in the network in Fig. P5.57 using Thévenin's theorem.

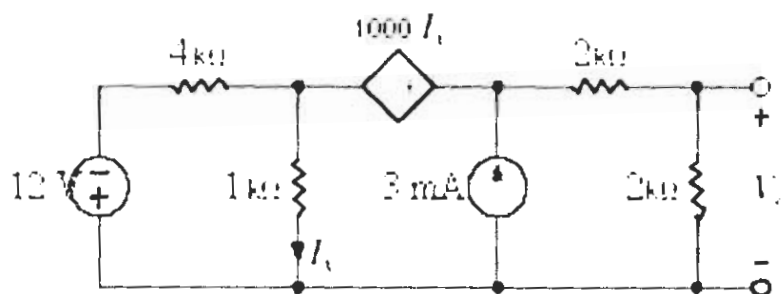


**Figure P5.57**

Solution: 5.57

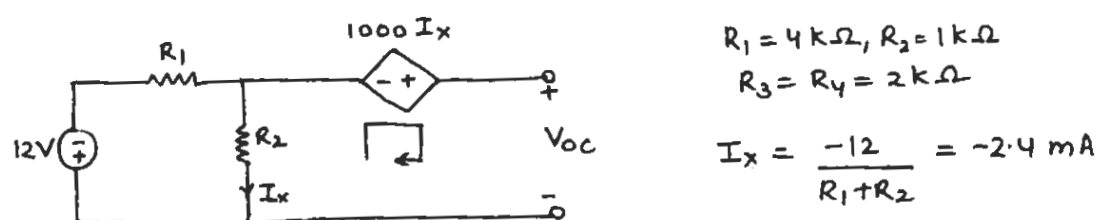

$$\text{KVL: } -I_x R_2 - 1000 I_x + V_{oc} = 0$$

$$V_{oc} = -4.8\text{ V}$$

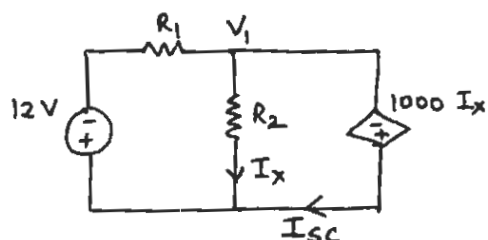


$$I_x = \frac{V_1}{R_2} \quad V_1 = 1000 I_x$$

$$I_x = 0\text{ mA} \Rightarrow V_1 = 0\text{ V}$$

$$I_{sc} = \frac{-12}{R_1} = -3\text{ mA}$$
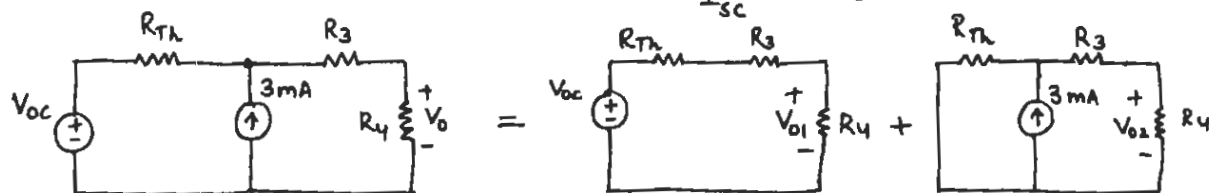
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{-4.8}{-3} = 1.6\text{ k}\Omega$$



$$V_o = V_{o1} + V_{o2}$$

$$= V_{oc} \cdot \frac{R_4}{R_3 + R_4 + R_{Th}} + 3 \times 10^{-3} \cdot \frac{R_{Th}}{R_3 + R_4 + R_{Th}} \times R_4$$

$$= -1.71 + 1.71$$

$$\boxed{V_o = 0\text{ V}}$$

5.58 Use Norton's theorem to find  $V_o$  in the network in Fig. P5.58.


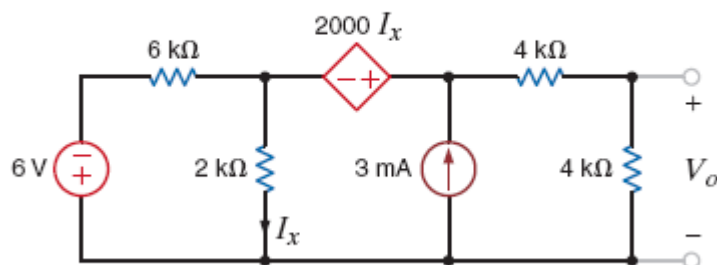


Figure P5.58

**SOLUTION:**

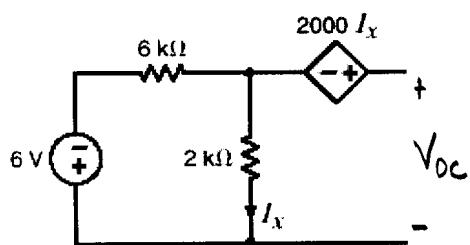


$$-6 = (6k + 2k) I_x$$


$$I_x = \frac{-6}{8k} = -0.75 \text{ mA}$$

$$V_{oc} = 2000 I_x + 2k I_x$$

$$V_{oc} = 2000(-0.75 \text{ m}) + 2k(-0.75 \text{ m})$$



$$V_{oc} = -3 \text{ V}$$

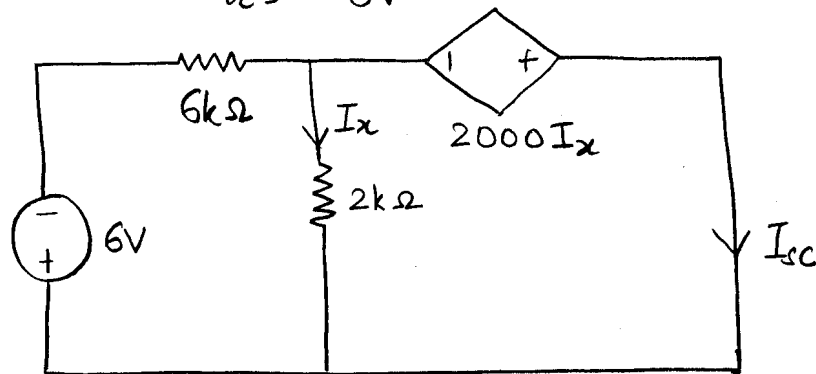

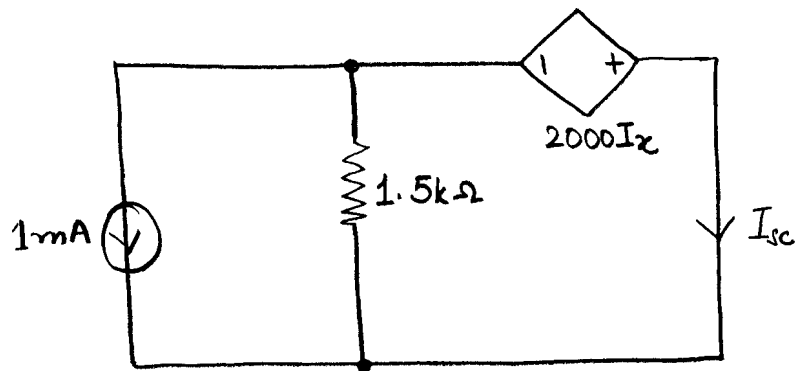

$$I_{sc} = -1\text{mA}$$

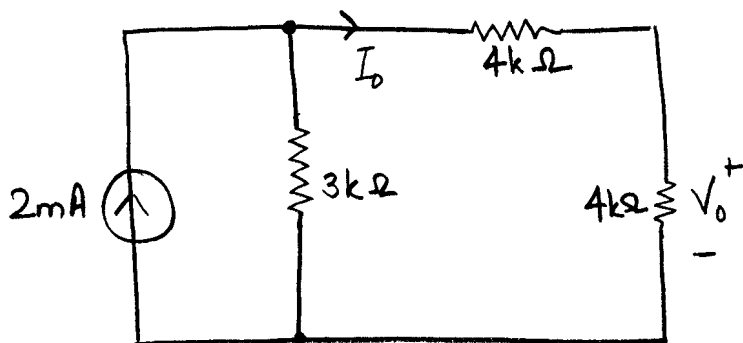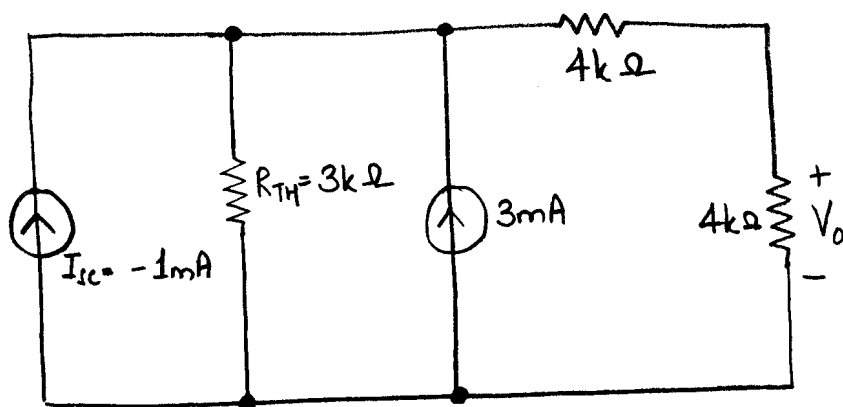
$$R_{TH} = \frac{-3}{-1\text{m}} = 3\text{k}\Omega$$



$$I_o = \left( \frac{3k}{3k + 4k + 4k} \right) (2m)$$
$$= 0.545mA$$


$$V_o = (0.545m)(4k)$$
$$= 2.18V$$

5.59 Find  $V_o$  in the circuit in Fig. P5.59 using Thévenin's theorem.

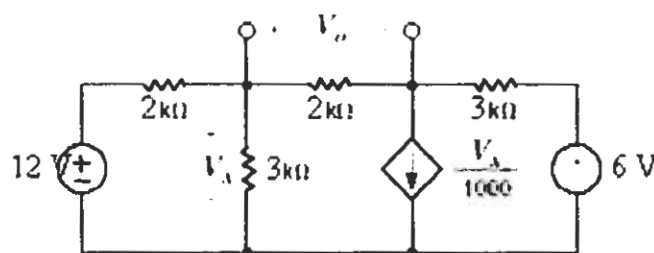


**Figure P5.59**

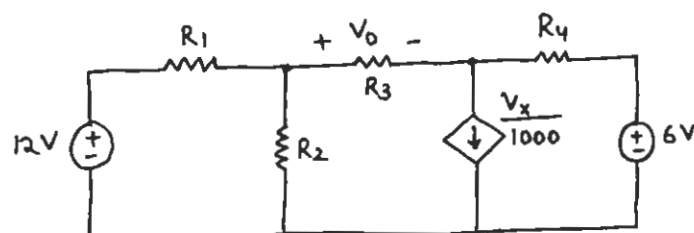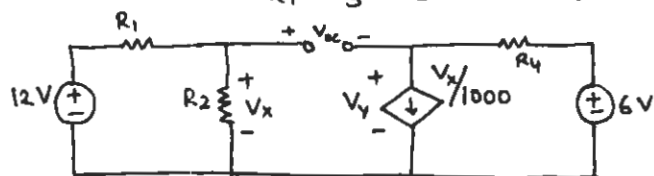Solution: 5.59




$$R_1 = R_3 = 2\text{ k}\Omega \quad R_2 = R_4 = 3\text{ k}\Omega$$



$$V_x = 12 \cdot \frac{R_2}{R_1 + R_2} = 7.2\text{ V}$$

$$V_y = 6 - \frac{V_x}{1000} R_4 = -15.6\text{ V}$$

$$V_{oc} = V_x - V_y = 22.8\text{ V}$$

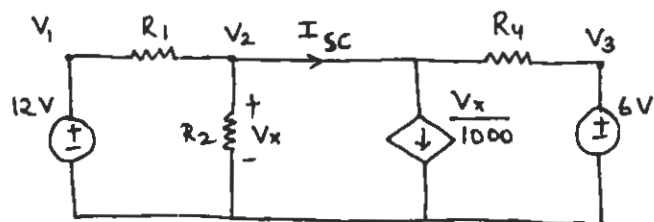


$$V_1 = 12\text{ V}, \quad V_3 = 6\text{ V}, \quad V_2 = V_x$$

$$\text{KCL @ } V_2: \quad \frac{V_2 - V_1}{R_1} - \frac{V_2}{R_2} + \frac{V_x}{1000} + \frac{V_2 - V_3}{R_4} = 0$$

$$V_2 = 3.69\text{ V}$$

$$I_{sc} = \frac{V_1 - V_2}{R_1} - \frac{V_2}{R_2} = 2.93\text{ mA}$$
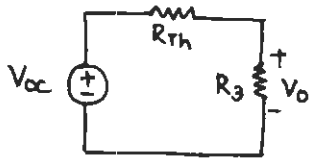
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = 7.78\text{ k}\Omega$$



$$V_o = V_{oc} \cdot \frac{R_3}{R_3 + R_{Th}}$$

$$V_o = 4.66 \text{ V}$$



5.60 Find  $V_o$  in the network in Fig. P5.60 using Norton's theorem.


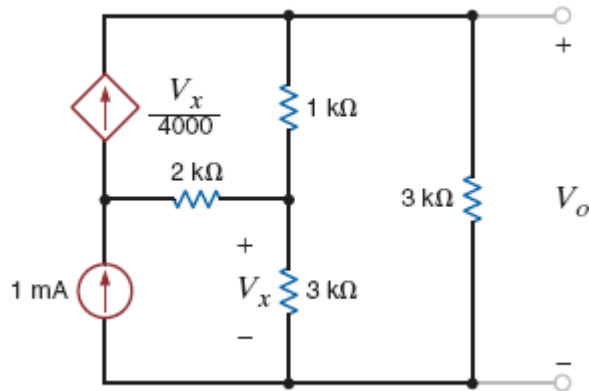


Figure P5.60

**SOLUTION:**

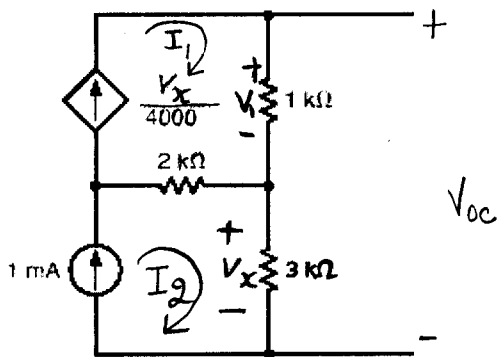


$$V_1 = \frac{V_x}{4000} (1k) = \frac{V_x}{4}$$

$$V_x = 3k(1m) = 3V$$

$$V_1 = \frac{3}{4} V$$
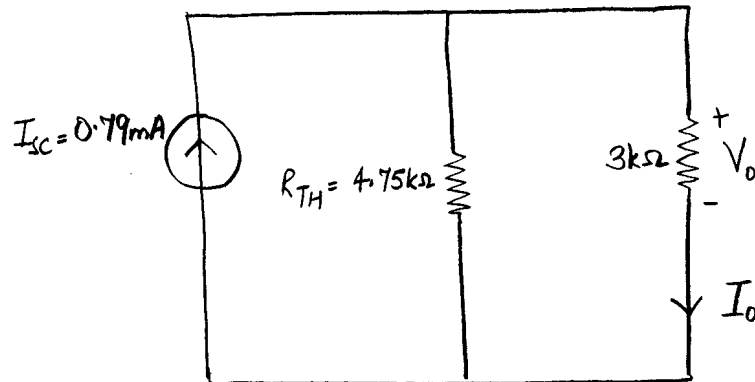
$$V_{oc} = V_x + V_1 = 3 + \frac{3}{4} = \frac{15}{4} V$$






$$I_o = \left( \frac{4.75k}{4.75k + 3k} \right) (0.79m) = 0.484mA$$


$$\begin{aligned} V_o &= (0.484m)(3k) \\ &= 1.45V \end{aligned}$$

5.61 Find  $I_o$  in the network in Fig. P5.61 using Thévenin's theorem.

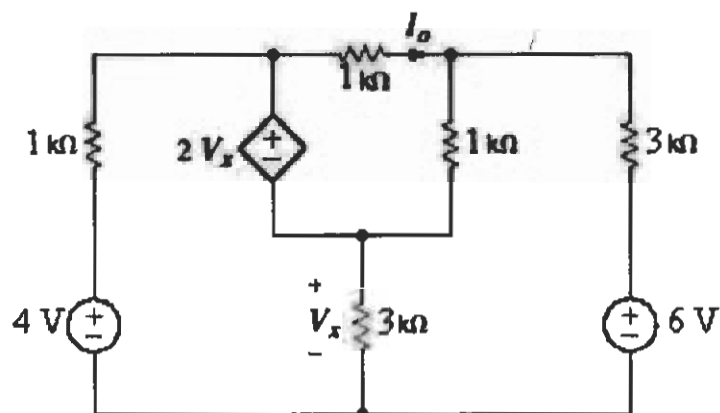

**Figure P5.61**

Solution: 5.61

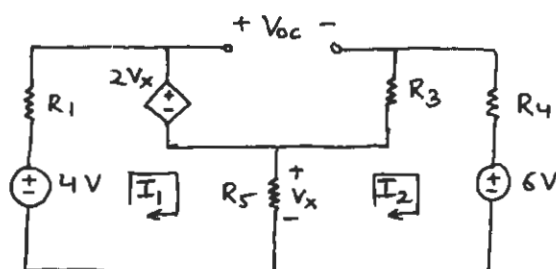

$$R_1 = R_2 = R_3 = 1\text{ k}\Omega, R_4 = R_5 = 3\text{ k}\Omega$$


$$\begin{aligned} \text{KVL @ } I_1: & -4 + I_1 R_1 + 2V_x + (I_1 - I_2) R_5 = 0 \\ & -4 + 10^3 I_1 + 2(I_1 - I_2) 3 \times 10^3 + (I_1 - I_2) 3 \times 10^3 = 0 \\ & I_1 + 9(I_1 - I_2) = 4 \times 10^{-3} \\ & 10I_1 - 9I_2 = 4 \times 10^{-3} \quad \text{--- (1)} \\ \text{KVL @ } I_2: & (I_2 - I_1) R_5 + I_2 R_3 + I_2 R_4 + 6 = 0 \\ & (I_2 - I_1) 3 \times 10^3 + I_2 \times 10^3 + I_2 \times 3 \times 10^3 + 6 = 0 \\ & 7I_2 - 3I_1 = -6 \times 10^{-3} \quad \text{--- (2)} \end{aligned}$$

From equations (1) and (2) we get

$$I_1 = -0.61\text{ mA}, \quad I_2 = -1.12\text{ mA}$$

$$\begin{aligned} V_x &= (I_1 - I_2) R_5 = (-0.61 + 1.12) 3 \\ &= 1.52\text{ V} \end{aligned}$$

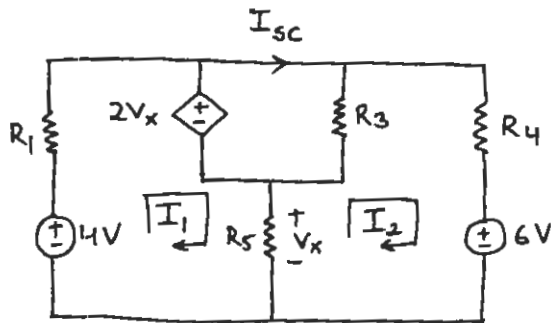
$$V_{oc} = 2V_x + R_3 I_2 = 3.04 - 1.12 = 1.92\text{ V}$$



$$2V_x = (I_{sc} - I_2) R_3$$

$$2(1.52) = (I_{sc} \times 1 \times 10^3) + 1.12$$

$$I_{sc} = 1.92 \text{ mA}$$

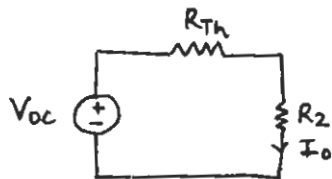


$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{1.92}{1.92} = 1 \text{ k}\Omega$$

$$I_0 = \frac{V_{oc}}{R_2 + R_{Th}} = \frac{1.92}{1+1} = 0.96 \text{ mA}$$


$$\boxed{I_0 = 0.96 \text{ mA}}$$

**5.62** Use Thévenin's theorem to find the power supplied by the 2-V source in the circuit in Fig. P5.62.

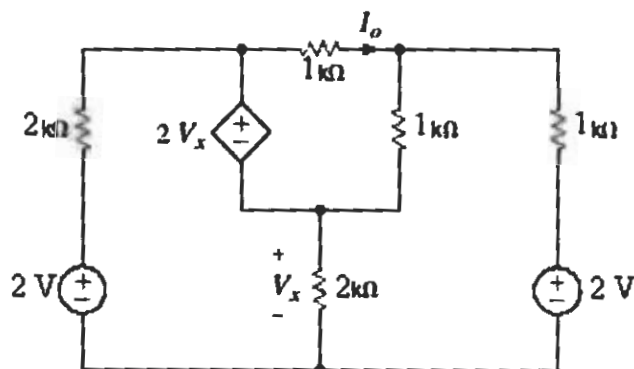


**Figure P5.62**

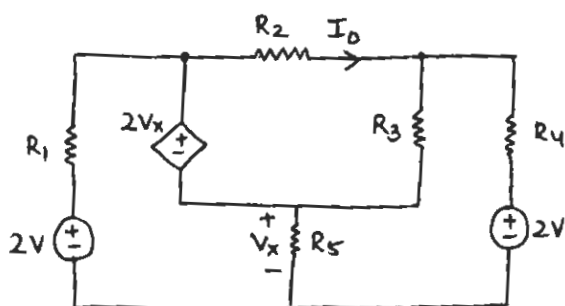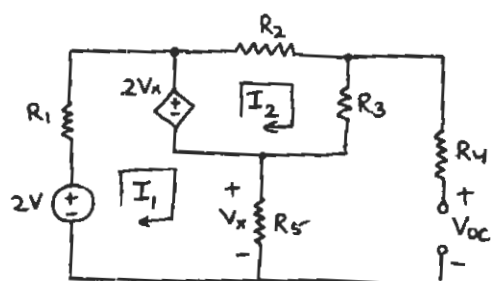Solution: 5.62



$$R_1 = R_5 = 2\text{ k}\Omega, R_2 = R_3 = R_4 = 1\text{ k}\Omega$$



$$V_x = I_1 R_5$$

$$\text{KVL @ } I_1: -2 + I_1 R_1 + 2V_x + I_1 R_5 = 0$$


$$I_1 = 0.25\text{ mA}$$

$$\text{KVL @ } I_2: -2V_x + I_2(R_2 + R_3) = 0$$

$$I_2 = 0.5\text{ mA}$$

$$V_{oc} = I_2 R_3 + I_1 R_5$$

$$V_{oc} = 1\text{ V}$$

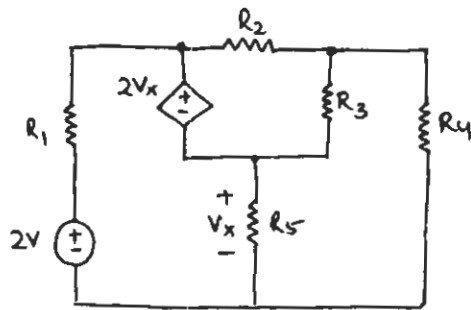


KVL @  $I_{sc}$ :

$$I_{sc}(R_5 + R_3 + R_4) - I_1 R_5 - I_2 R_3 = 0$$

$$I_{sc} = 0.25 \text{ mA}$$
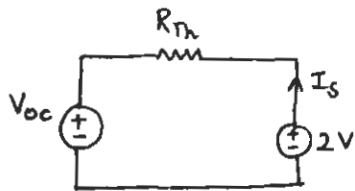
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = 4 \text{ k}\Omega$$




$$I_s = \frac{2 - V_{oc}}{R_{Th}} = 0.25 \text{ mA}$$

$$P_{2V} = 2 I_s$$


$$P_{2V} = 0.50 \text{ mW}$$

5.63 Find  $V_o$  in the circuit in Fig. P5.63 using Thévenin's theorem.

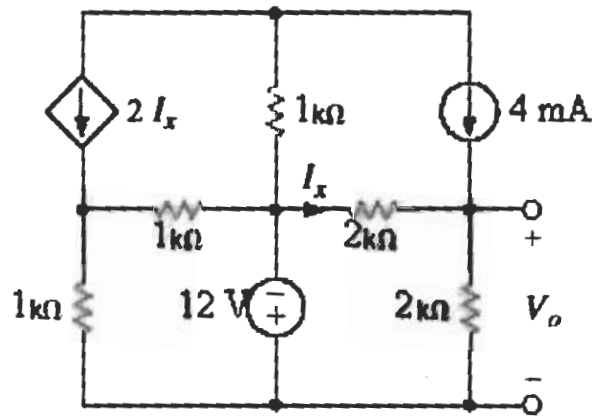


**Figure P5.63**

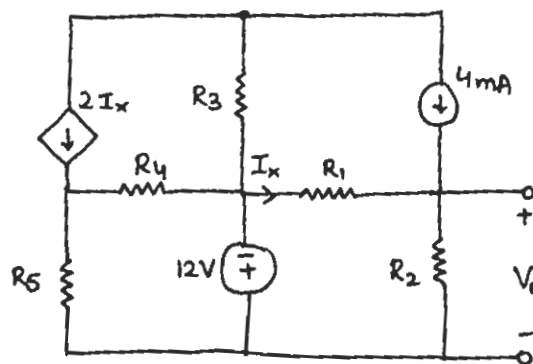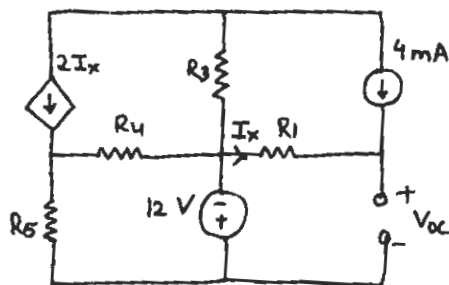Solution: 5.63




$$R_1 = R_2 = 2 \times 10^3 \, \Omega, \quad R_3 = R_4 = R_5 = 1 \, \text{k}\Omega$$



$$12 - (4 \times 10^{-3})R_1 + V_{oc} = 0$$

$$V_{oc} = -4 \, \text{V}$$




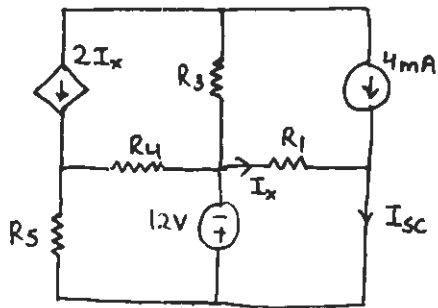

$$I_x = \frac{-12}{R_1} = -6 \text{ mA}$$

$$I_{sc} = 4 \times 10^{-3} + I_x = -2 \text{ mA}$$
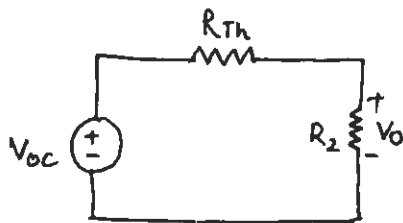
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = 2 \text{ k}\Omega$$



$$V_0 = V_{oc} \frac{R_2}{R_2 + R_{Th}}$$

$$V_0 = -2.00 \text{ V}$$

5.64 Find  $V_o$  in the network in Fig. P5.64 using Thévenin's theorem.


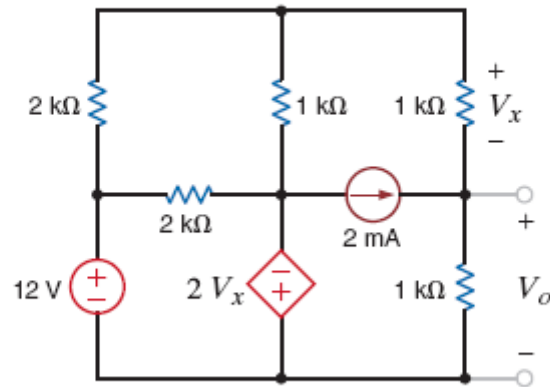


Figure P5.64

**SOLUTION:**

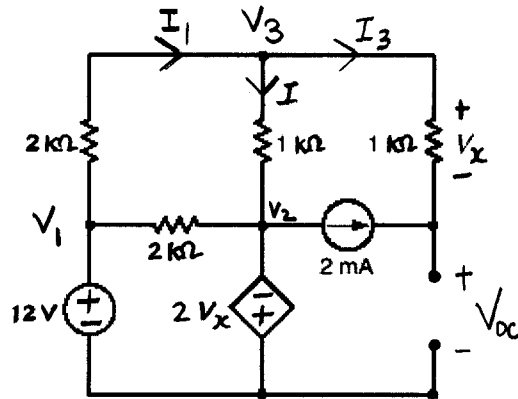

$$V_1 = 12V$$

$$V_2 = -2V_x$$

$$V_x = V_3 - V_{oc}$$

$$I_1 = I_2 + I_3$$

$$\frac{V_1 - V_3}{2k} = \frac{V_3 - V_2}{1k} + \frac{V_3 - V_{oc}}{1k}$$

$$-V_1 - 2V_2 + 5V_3 - 2V_{oc} = 0$$

$$I_3 = -2mA$$

$$\frac{V_3 - V_{oc}}{1k} = -2m$$

$$V_3 - V_{oc} = -2$$


$$V_2 = -2V_3 + 2V_{oc}$$

$$-12 - 2[-2V_3 + 2V_{oc}] + 5V_3 - 2V_{oc} = 0$$

$$9V_3 - 6V_{oc} = 12$$

$$V_3 = 8V$$

$$V_{oc} = 10V$$

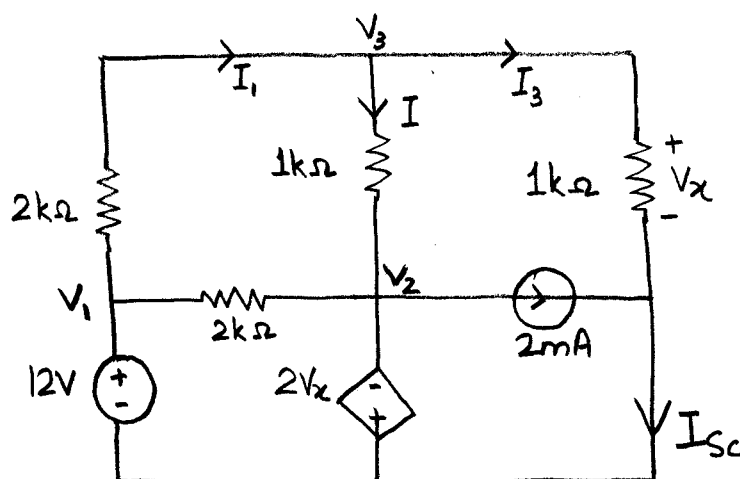

$$V_3 = V_x$$

$$V_1 = 12V$$

$$V_2 = -2V_x$$

$$\frac{V_1 - V_3}{2k} = \frac{V_3 - V_2}{1k} + \frac{V_3}{1k}$$

$$V_1 + 2V_2 - 5V_3 = 0$$

$$-12 + 2[-2V_x] - 5V_x = 0$$


$$V_x = \frac{4}{3} V$$

$$V_3 = V_x = \frac{4}{3} V$$

$$2m + \frac{V_3}{1k} = I_{sc}$$

$$I_{sc} = 3.33mA$$

$$R_{TH} = \frac{10}{3.33m} = 3k\Omega$$

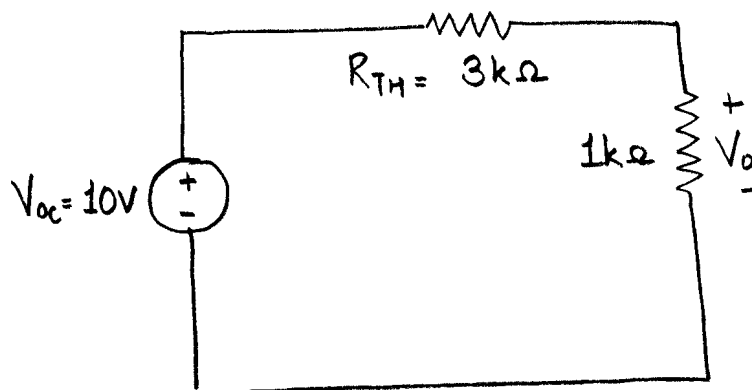

$$V_o = \left( \frac{1k}{1k + 3k} \right) (10) = 2.5V$$

5.65 Find  $V_o$  in the network of Fig. P5.65 using Thévenin's theorem.


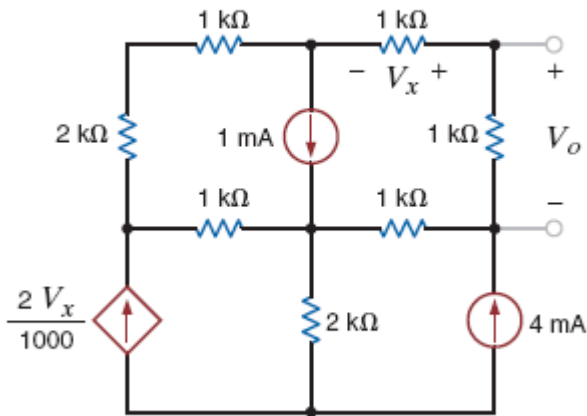


Figure P5.65

**SOLUTION:**

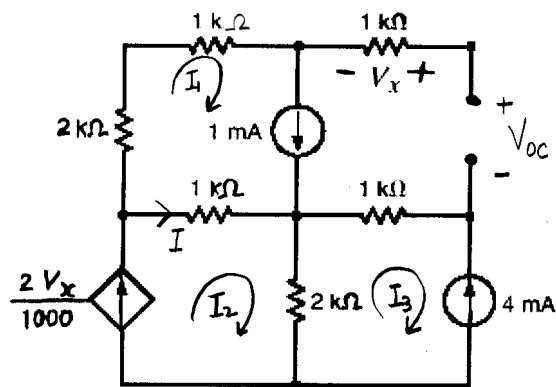

$$I_1 = 1 \text{ mA}$$

$$I_2 = \frac{V_x}{500}$$

$$I_3 = -4 \text{ mA}$$

$$V_x = 0 \text{ V}$$


$$I_2 = 0 \text{ A}$$

$$I_1 + I = 0$$

$$I = -1 \text{ mA}$$

$$V_{oc} + 2kI_1 + 1kI_1 = 1kI_3 + 1kI$$
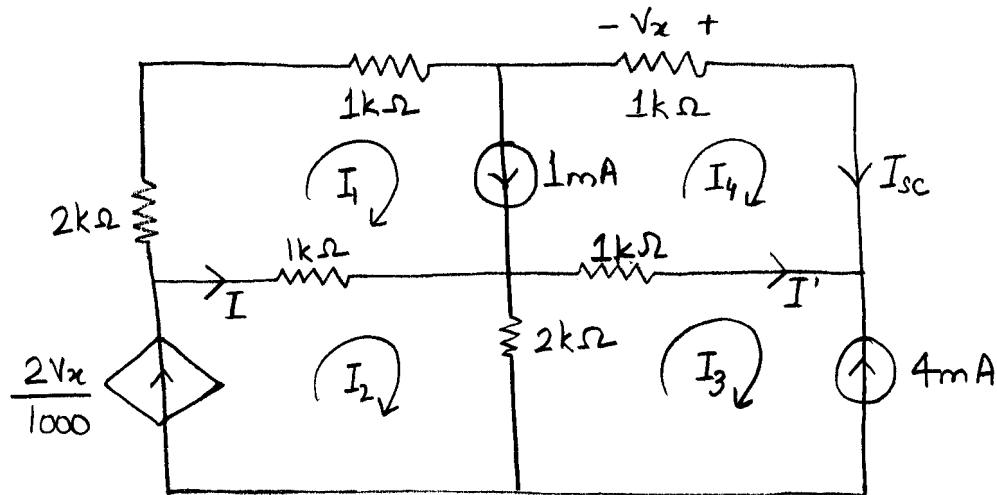
$$V_{oc} = -4 - 1 - 1 - 2 = -8 \text{ V}$$



$$I_2 = \frac{V_x}{500}$$

$$I_3 = -4\text{mA}$$

$$I_4 = I_{sc}$$

$$V_x = -1kI_4$$

$$I + I_1 = \frac{V_x}{500}$$

$$I' + I_4 = I_3$$

$$I' = I_3 - I_4$$

$$I_1 = 1\text{m} + I_4$$

$$3kI_1 + 1kI_4 + 1k(I_4 - I_3) + 1k(I_1 - I_2) = 0$$


$$4kI_1 + 4kI_4 = -4$$

$$I_1 = 0\text{A}$$

$$I_4 = -1\text{mA}$$


$$I_{sc} = -1\text{mA}$$
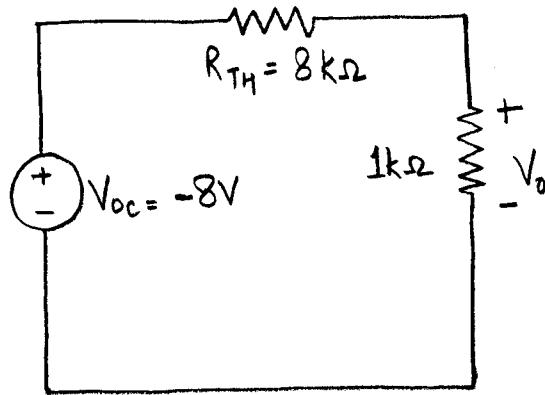
$$R_{TH} = \frac{-8}{-1\text{m}} = 8k\Omega$$





$$V_o = \left( \frac{1k}{1k + 8k} \right) (-8)$$
$$= -0.889V$$

5.66 Use Thévenin's theorem to find  $I_o$  in the network in Fig. P5.66.

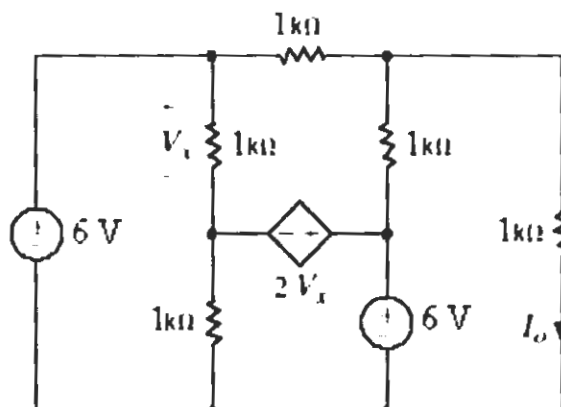

**Figure P5.66**

Solution: 5.66

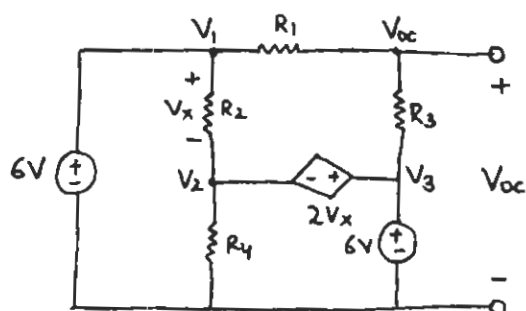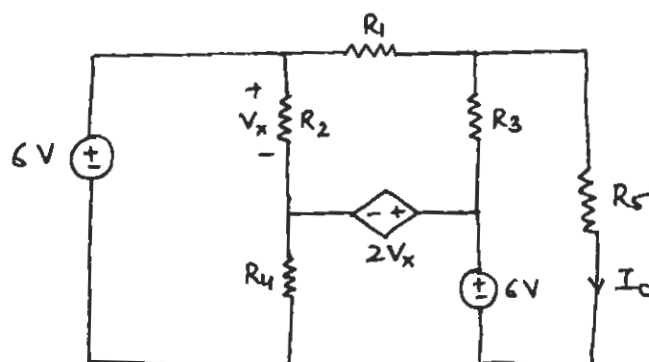


$$R_1 = R_2 = R_3 = R_4 = R_5 = 1\text{ k}\Omega$$

$$V_1 = 6\text{ V}, V_3 = 6\text{ V}, V_x = V_1 - V_2$$

$$V_3 - V_2 = 2V_x$$

$$\text{KCL @ } V_{oc}: \frac{V_{oc} - V_1}{R_1} + \frac{V_{oc} - V_3}{R_3} = 0$$

$$V_{oc} = 6\text{ V}$$

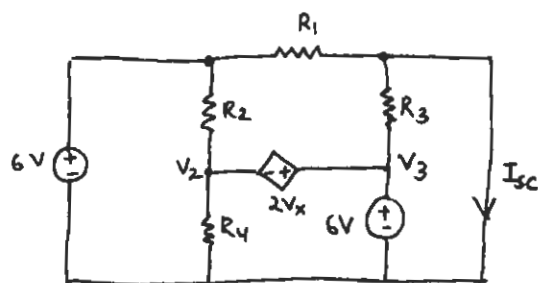


$$V_1 = 6\text{ V}, V_3 = 6\text{ V}, V_x = V_1 - V_2$$

$$V_3 - V_2 = 2V_x$$

$$\frac{V_1}{R_1} + \frac{V_3}{R_3} = I_{sc}$$

$$I_{sc} = 12\text{ mA}$$



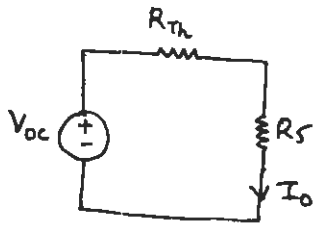

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = 0.5 \text{ k}\Omega$$

$$I_o = \frac{V_{oc}}{R_{Th} + R_L}$$

$$I_o = 4.00 \text{ mA}$$

5.67 Use Thévenin's theorem to find  $V_o$  in the network in Fig. P5.67.


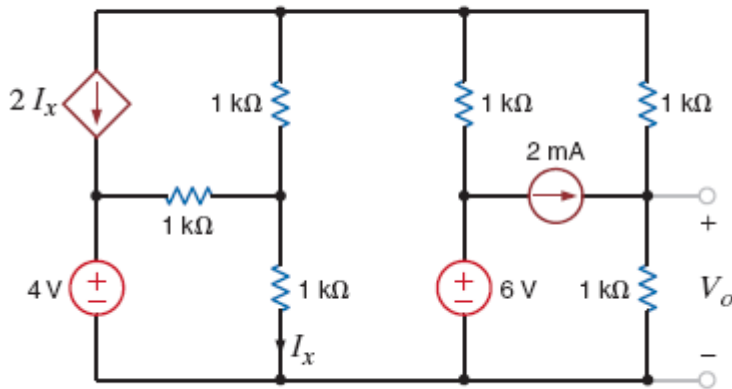


Figure P5.67

**SOLUTION:**

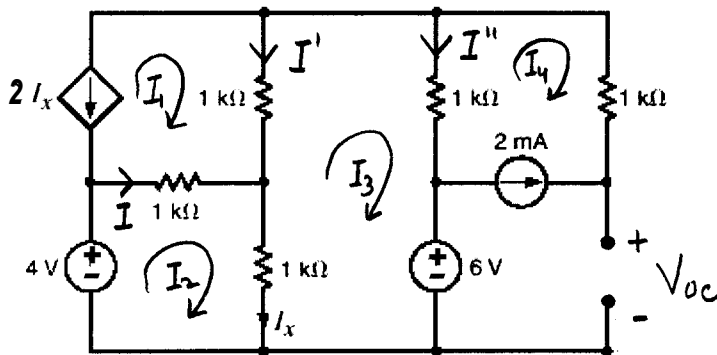

$$\begin{aligned}
 I_1 &= -2I_x \\
 I_x &= I_2 - I_3 \\
 I_4 &= -2\text{mA} \\
 I_2 &= I + I_1 \\
 I &= I_2 - I_1 \\
 4 &= 1kI + 1kI_x \\
 4 &= 1k(I_2 - I_1) + 1k(I_2 - I_3) \\
 I_1 + I_3 &= I_2 \\
 I_1 &= I_2 - I_3 \\
 I_3 &= I_1 + I_4
 \end{aligned}$$




$$-6 = -1kI_1 - 1kI_2 + 3kI_3 - 1kI_4$$

$$6 = -1kI_1 + 1kI_4$$

$$6 = -1kI_3 + 2kI_4$$

$$I_5 = I_{sc} = 3.4mA$$
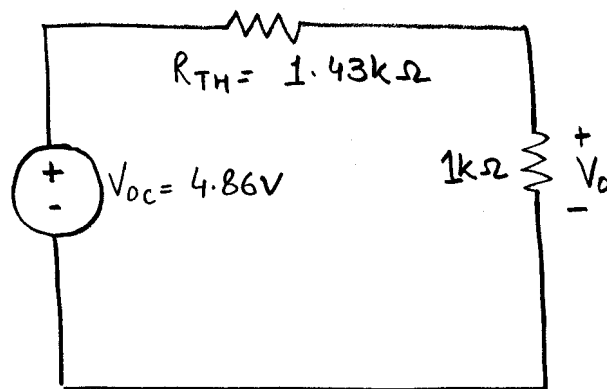
$$R_{TH} = \frac{4.86}{3.4m} = 1.43k\Omega$$



$$V_O = \left( \frac{1k}{1k + 1.43k} \right) (4.86) = 2V$$

- 5.68 Find the Thévenin equivalent of the circuit in Fig. P5.68 at the terminals A-B.


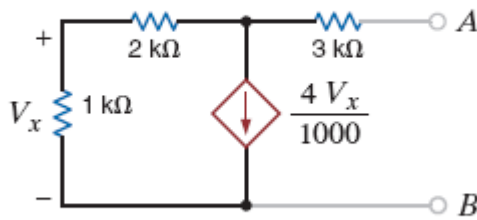


Figure P5.68

**SOLUTION:**

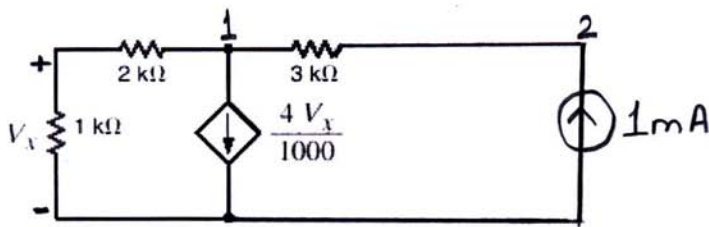

$$1\text{m} = \frac{V_1}{3\text{k}} + \frac{4V_x}{1000}$$

$$3 = V_1 + 12V_x$$

$$V_x = \frac{V_1}{3\text{k}}(1\text{k}) = \frac{V_1}{3}$$

$$3 = V_1 + 12\left(\frac{V_1}{3}\right)$$

$$V_1 = \frac{3}{5}\text{V}$$


$$V_x = \frac{1}{3}\left(\frac{3}{5}\right) = \frac{1}{5}\text{V}$$

$$V_2 - V_1 = 3\text{k}(1\text{m})$$

$$V_2 = \frac{3}{5} + 3\text{k}(1\text{m}) = \frac{18}{5} = 3.6\text{V}$$

$$R_{\text{TH}} = \frac{3.6}{1\text{m}} = 3.6\text{k}\Omega$$

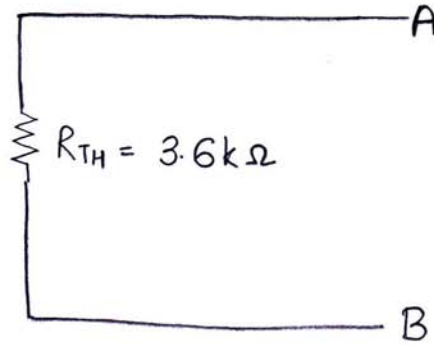Since there are no independent sources,  
 $V_{oc} = 0V$ .



- 5.69 Find the Thévenin equivalent of the network in Fig. P5.69 at the terminals  $A-B$  using a 1-mA current source.


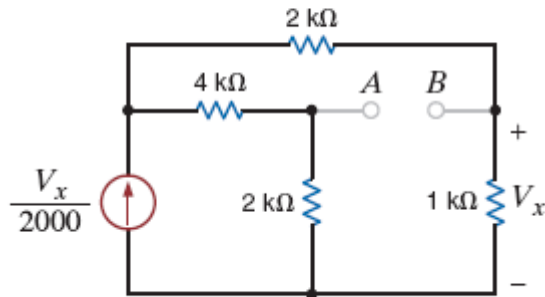


Figure P5.69

**SOLUTION:**

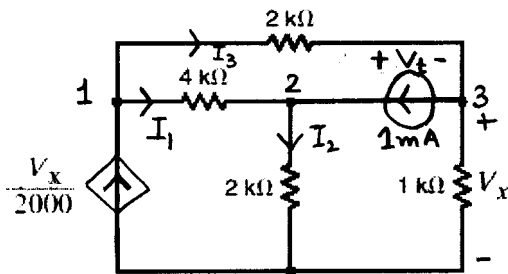

$$\text{KCL at 2: } \frac{V_1 - V_2}{4k} + 1m = \frac{V_2}{2k}$$

$$V_1 - 3V_2 = -4$$

$$\text{KCL at 3: } \frac{V_1 - V_3}{2k} = 1m + \frac{V_3}{1k}$$

$$V_1 - 3V_3 = 2$$

$$\text{KCL at 1: } \frac{V_x}{2000} = \frac{V_1 - V_2}{4k} + \frac{V_1 - V_3}{2k}$$

$$V_x = V_3$$

$$\frac{V_3}{(2000)} = \frac{V_1 - V_2}{4k} + \frac{V_1 - V_3}{2k}$$

$$3V_1 - V_2 - 4V_3 = 0$$

$$V_1 - 3V_2 = -4$$

$$V_2 = \frac{V_1 + 4}{3}$$

$$V_1 - 3\left(\frac{V_1 + 4}{3}\right) - 4V_3 = 0$$

$$V_3 = -1V$$

$$V_1 - 3(-1) = 2$$


$$V_1 = -1V$$

$$V_2 = \frac{-1 + 4}{3} = 1V$$

$$V_t = 1 + 1 = 2V$$


$$R_{TH} = \frac{2}{1m} = 2k\Omega$$

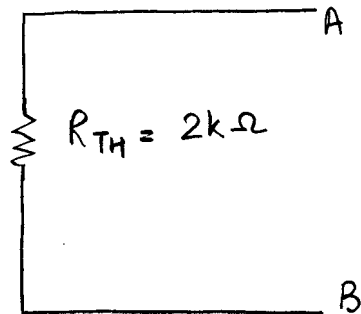Since there are no independent sources,  
 $V_{oc} = 0V$ .






5.70 Find the Thévenin equivalent of the network in Fig. P5.70 at the terminals A-B.

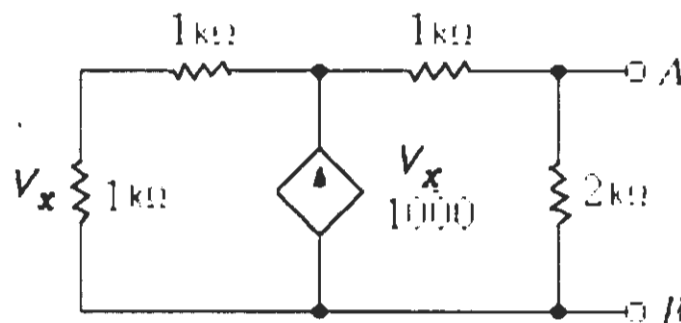


**Figure P5.70**

Solution: 5.70

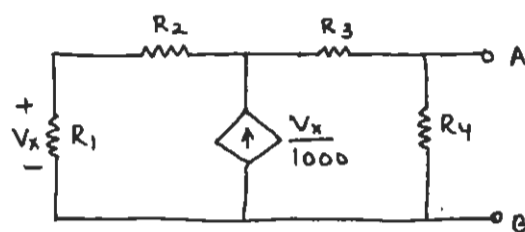


Only dependent source  $\Rightarrow V_{oc} = 0V$
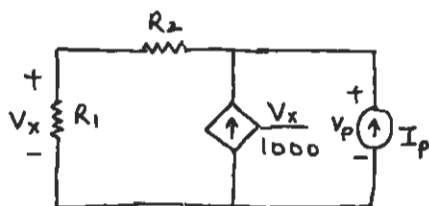
$$R_1 = R_2 = R_3 = 1k\Omega; R_4 = 2k\Omega$$



$$I_p + \frac{V_x}{1000} - \frac{V_x}{R_1} = 0$$

$$\Rightarrow I_p = 0$$

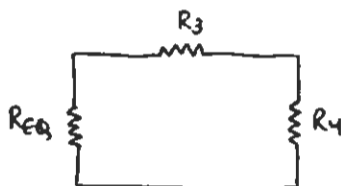

$$R_{eq} = \frac{V_p}{I_p} = \infty$$


$$R_{th} = R_4 \parallel (R_3 + R_{eq})$$

$$= \frac{R_4 (R_3 + R_{eq})}{R_4 + R_3 + R_{eq}}$$

$$\approx R_4$$


$$R_{Th} = 2k\Omega$$

Thevenin Eq

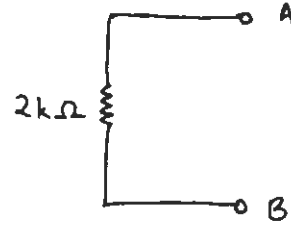


$$(\because V_{oc} = 0V)$$

5.71 Find the Thévenin equivalent of the network in Fig. P5.71 at the terminals  $A$ - $B$ .

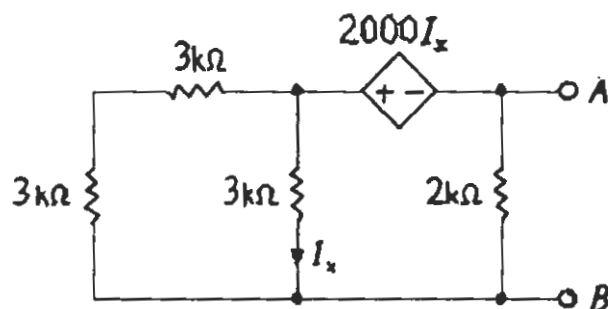


**Figure P5.71**

Solution: 5.71

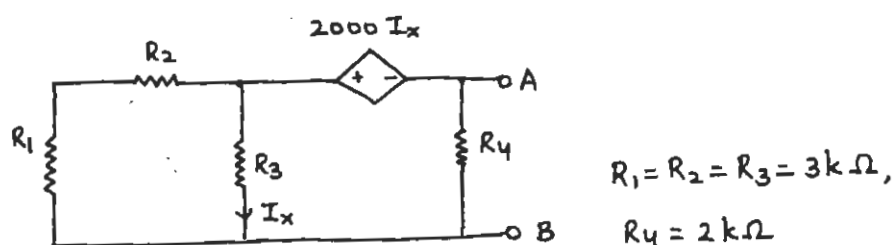

$$V_{oc} = 0\text{ V}$$

$$R_0 = R_1 + R_2 = 6\text{ k}\Omega$$

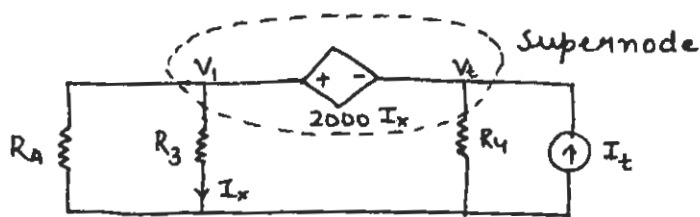

$$V_1 - V_t = 2000 I_x \quad \text{---} \quad \textcircled{1}$$

$$I_x = \frac{V_1}{R_3} \quad \text{---} \quad \textcircled{2}$$

From ① and ②, we get


$$V_1 = 3V_t$$

$$\text{KCL @ supernode: } \frac{V_1}{R_1} + \frac{V_1}{R_3} + \frac{V_t}{R_4} - I_t = 0$$

$$\frac{V_t}{I_t} = 0.50\text{ k}\Omega$$

$$R_{Th} = \frac{V_t}{I_t} \Rightarrow R_{Th} = 0.50\text{ k}\Omega$$

Thevenin Eq

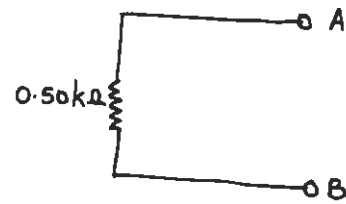

5.72 Find the Thévenin equivalent of the network below at the terminals A-B in Fig. P5.72.


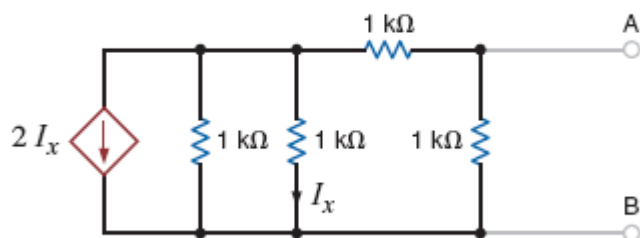


Figure P5.72

**SOLUTION:**

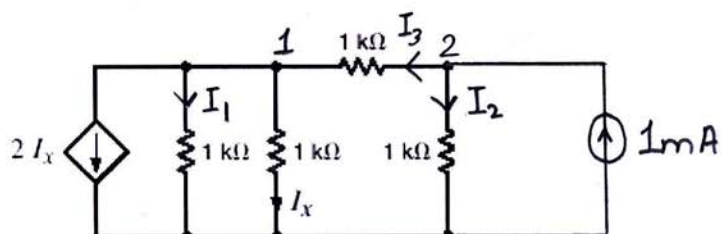

$$\text{KCL at 2: } 1\text{m} = \frac{V_2}{1\text{k}} + \frac{V_2 - V_1}{1\text{k}}$$

$$-V_1 + 2V_2 = 1$$

$$\text{KCL at 1: } \frac{V_2 - V_1}{1\text{k}} = \frac{V_1}{1\text{k}} + \frac{V_1}{1\text{k}} + 2I_x$$

$$I_x = \frac{V_1}{1\text{k}}$$

$$\frac{V_2 - V_1}{1\text{k}} = \frac{V_1}{1\text{k}} + \frac{V_1}{1\text{k}} + 2\left(\frac{V_1}{1\text{k}}\right)$$

$$5V_1 - V_2 = 0$$


$$V_1 = 0.111\text{V}$$

$$V_2 = 0.556\text{V}$$

$$R_{TH} = \frac{0.556}{1\text{m}}$$

$$= 556\Omega$$

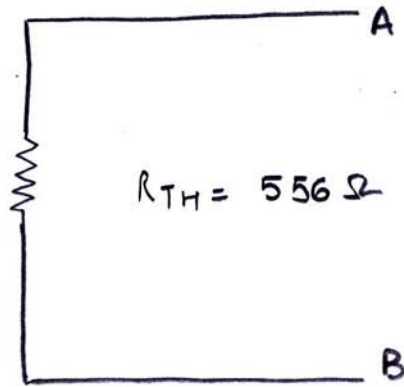Since there are no independent sources,  
 $V_{oc} = 0V.$



- 5.73 Find the Thévenin equivalent circuit of the network in Fig. P5.73 at terminals A-B.


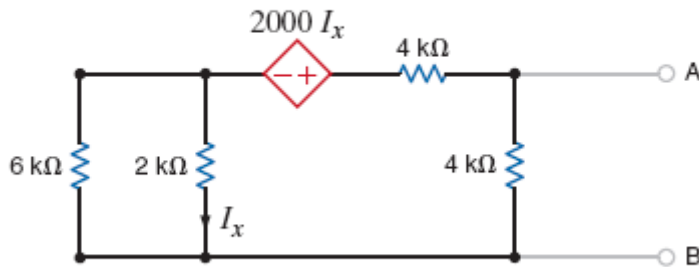


Figure P5.73

**SOLUTION:**

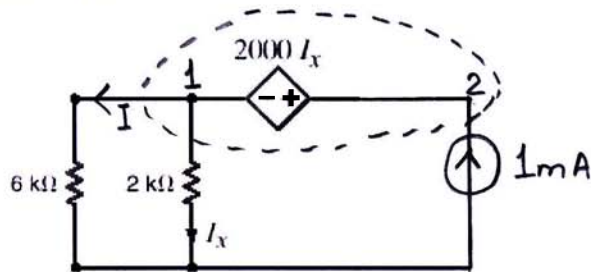

KCL at the supernode:

$$1\text{m} = \frac{V_1}{6\text{k}} + \frac{V_1}{2\text{k}}$$

$$V_1 = \frac{3}{2} \text{ V}$$

$$I_x = \frac{V_1}{2\text{k}}$$

$$V_2 - V_1 = 2000 I_x$$

$$V_2 - V_1 = 2000 \left( \frac{V_1}{2\text{k}} \right)$$

$$V_2 = 2V_1$$


$$V_2 = 2 \left( \frac{3}{2} \right)$$

$$V_2 = 3\text{V}$$

$$R = \frac{3}{1\text{m}} = 3\text{k}\Omega$$

$$R_{TH} = 4k \parallel (4k + R) = 4k \parallel 7k \\ = 2.54k\Omega$$

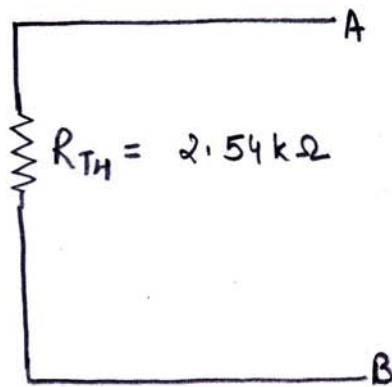Since there are no independent sources,  
 $V_{OC} = 0V$ .





5.74 Find  $I_o$  in the network in Fig. P5.74 using source transformation.



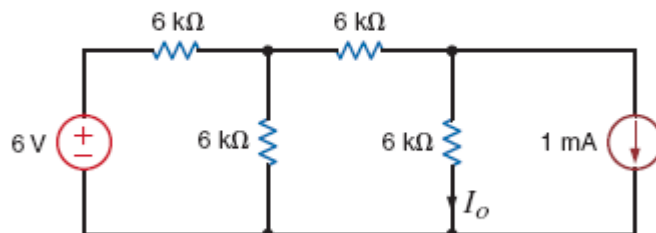
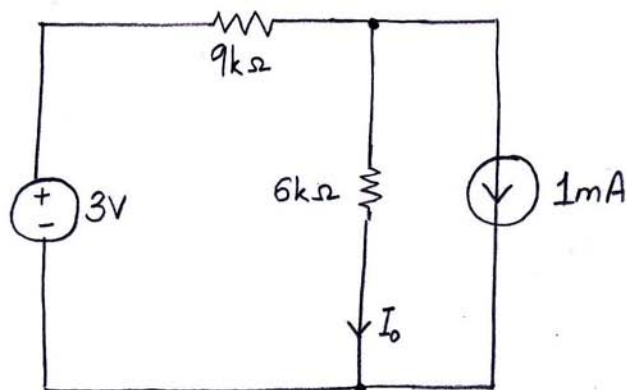
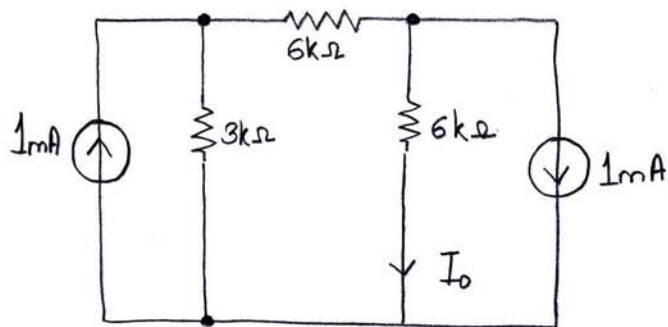


Figure P5.74


**SOLUTION:**

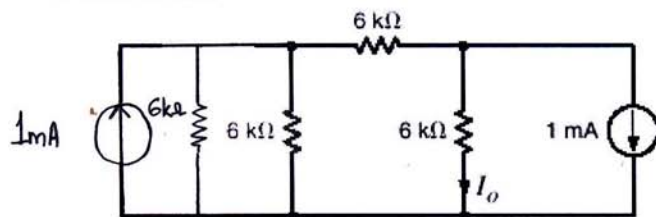

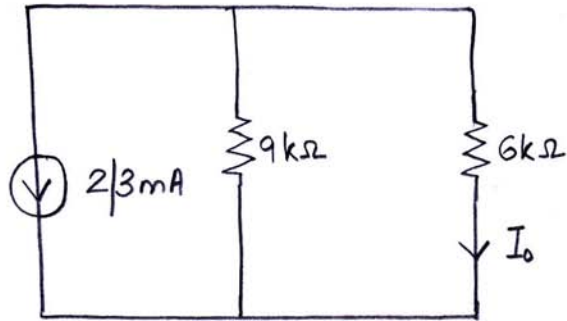





$$I_0 = \left( \frac{9 \text{ k}}{9 \text{ k} + 6 \text{ k}} \right) \left( -\frac{2}{3} \text{ m} \right) = -0.4 \text{ mA}$$

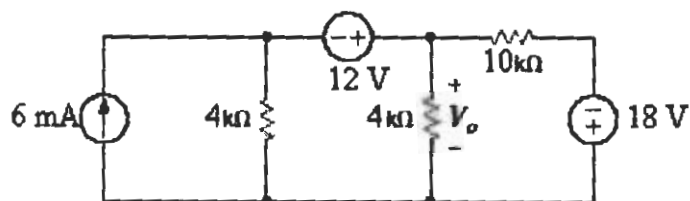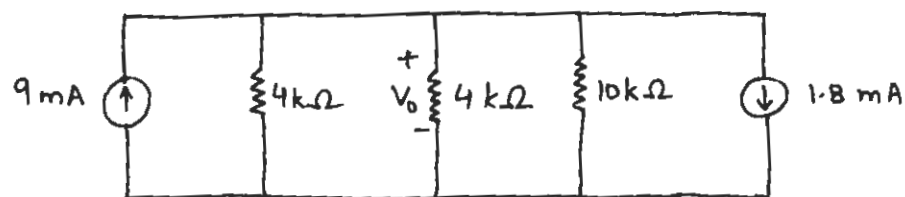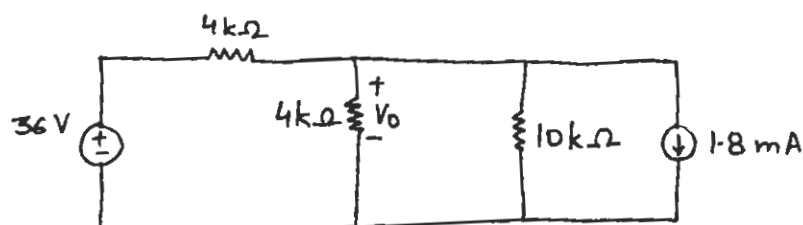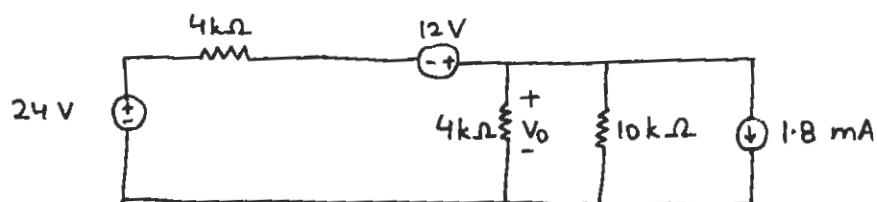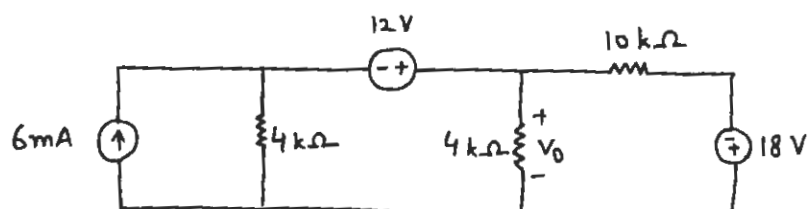5.75 Use source transformation to find  $V_o$  in the network in Fig. P5.75.

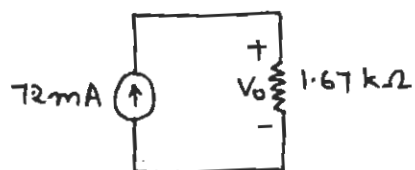


**Figure P5.75**

Solution: 5.75




$$R_{eq} = 4 \parallel 4 \parallel 10 = 1.67 \text{ k}\Omega$$




$$V_o = 12.0 \text{ V}$$

5.76 Find  $I_o$  in the network in Fig. P5.76 using source transformation.

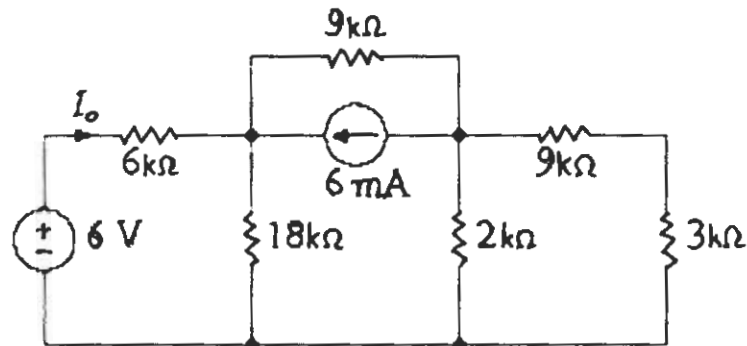


**Figure P5.76**

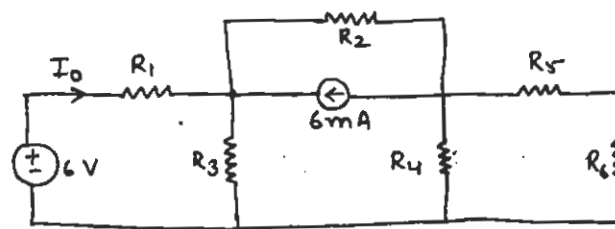
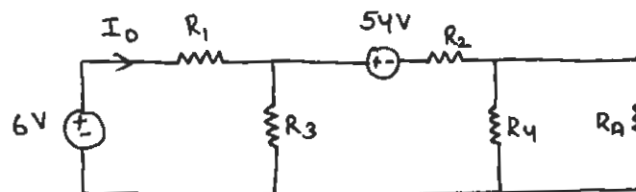
Solution: 5.76




$$\begin{aligned} R_1 &= 6\text{ k}\Omega, R_2 = 9\text{ k}\Omega, \\ R_3 &= 18\text{ k}\Omega, R_4 = 2\text{ k}\Omega, \\ R_5 &= 9\text{ k}\Omega, R_6 = 3\text{ k}\Omega \end{aligned}$$


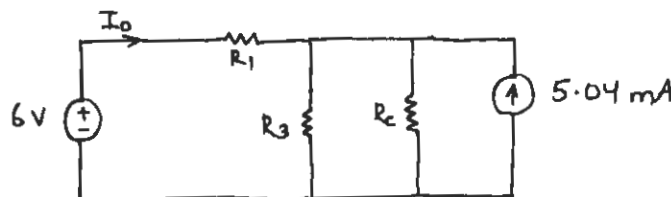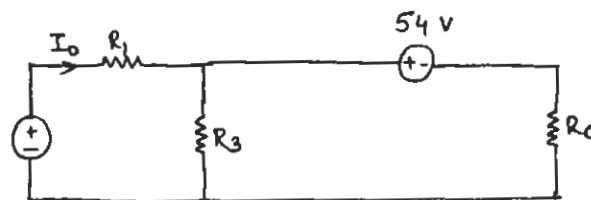
$$\begin{aligned} R_A &= R_5 + R_6 = 12\text{ k}\Omega \\ R_B &= R_4 \parallel R_A = \frac{12}{7}\text{ k}\Omega \\ R_C &= R_2 + R_B = \frac{75}{7}\text{ k}\Omega \end{aligned}$$


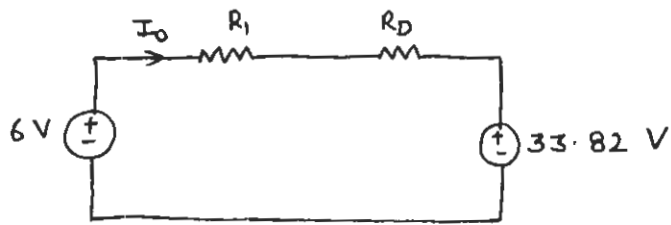
$$R_D = R_C \parallel R_3 = 6.71\text{ k}\Omega$$



$$6 = I_0(R_1 + R_D) + 33.82$$

$$I_0 = -2.19 \text{ mA}$$

5.77 Find  $V_o$  in the network in Fig. P5.77 using source transformation.



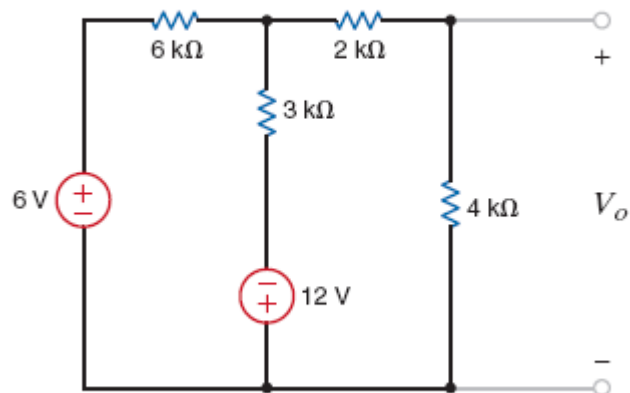


Figure P5.77

**SOLUTION:**

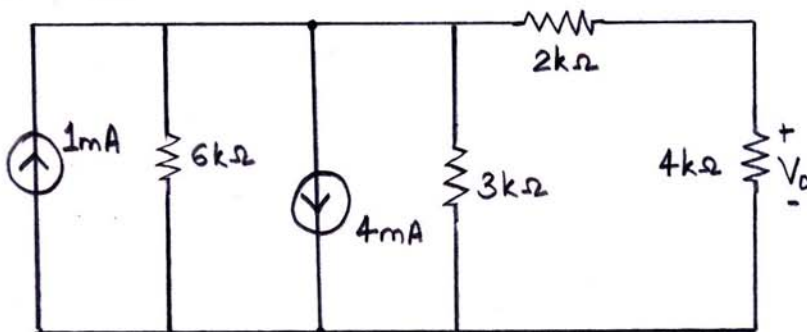


$$R' = 6k \parallel 3k = 2k\Omega$$

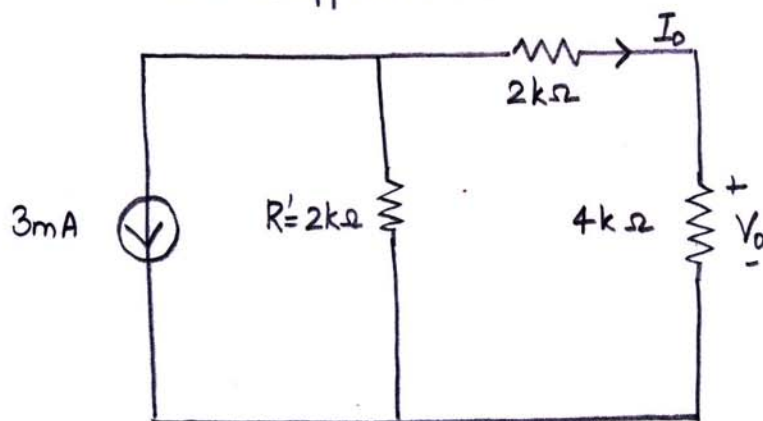

$$I_0 = \left( \frac{-2k}{2k+2k+4k} \right) (3m)$$
$$= -0.75mA$$





$$V_0 = 4k(-0.75m)$$
$$= -3V$$

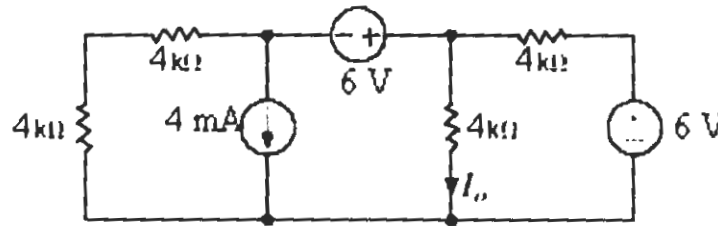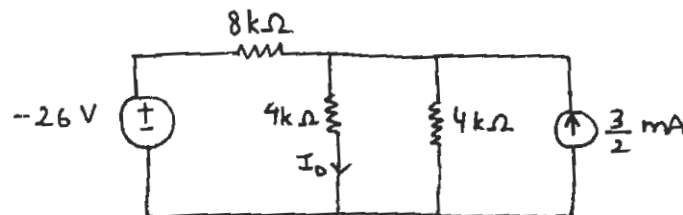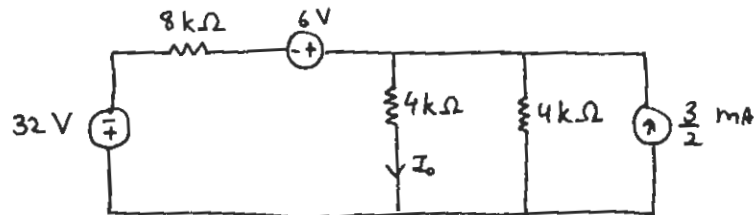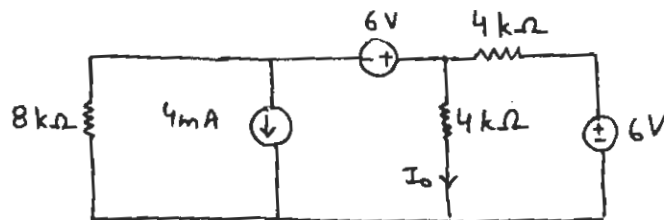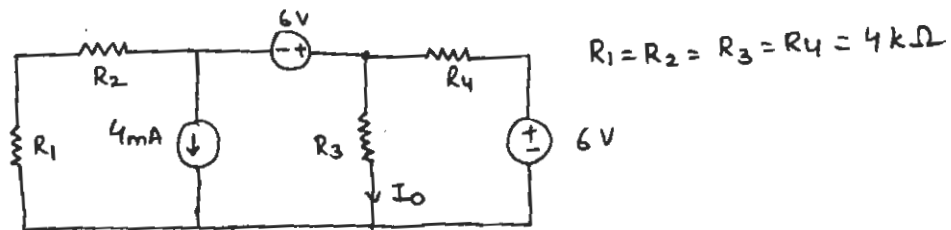5.78 Use source transformation to find  $I_o$  in the network in Fig. P5.78.


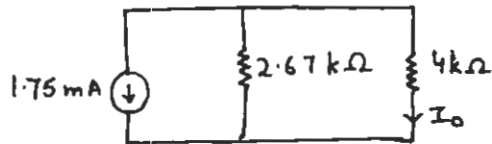


**Figure P5.78**

Solution: 5.78

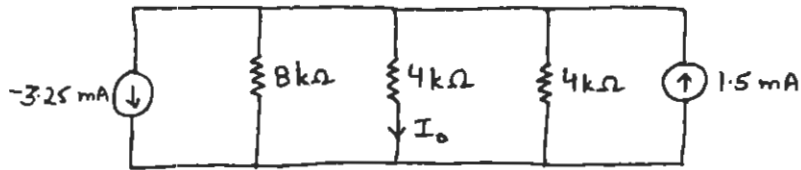





By Current Division

$$I_o = -1.75 \times 10^{-3} \left[ \frac{2.67}{6.67} \right]$$

$$I_o = -0.700 \text{ mA}$$

5.79 Find  $V_o$  in the network in Fig. P5.79 using source transformation.


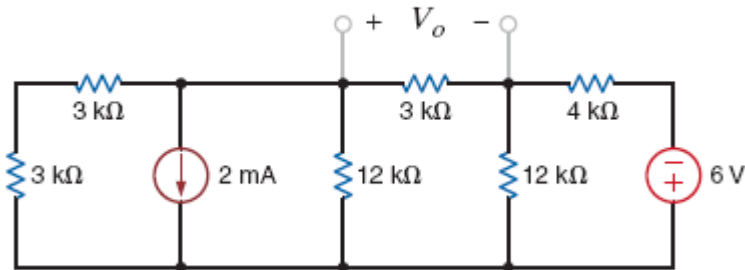



Figure P5.79


**SOLUTION:**

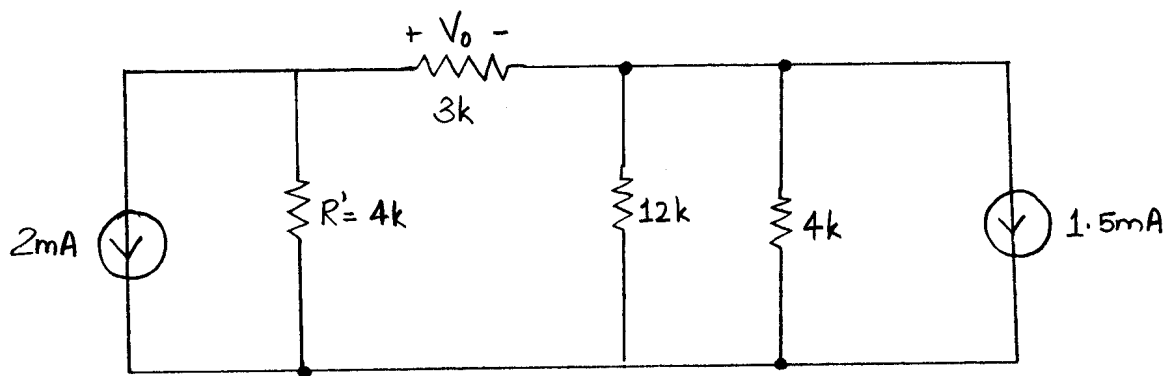

$$R' = 6k \parallel 12k = 4k\Omega$$

$$R'' = 12k \parallel 4k = 3k\Omega$$

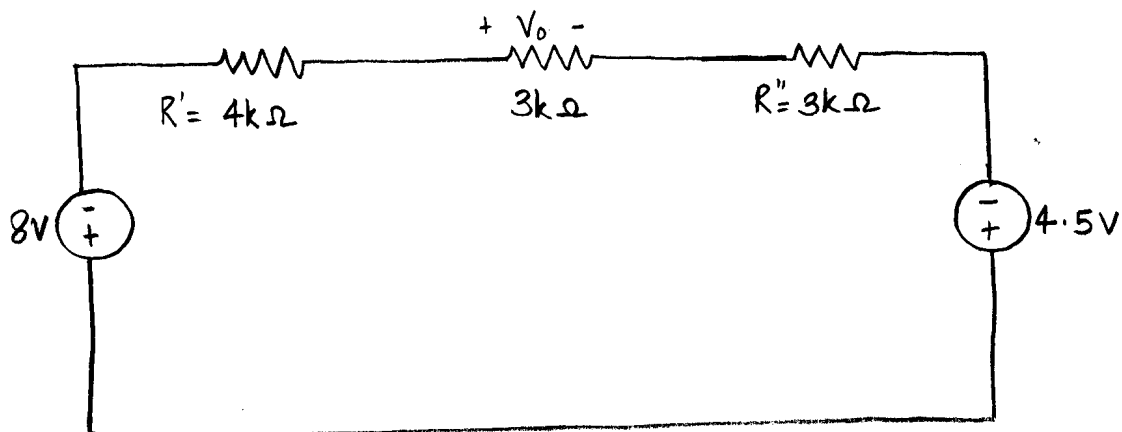

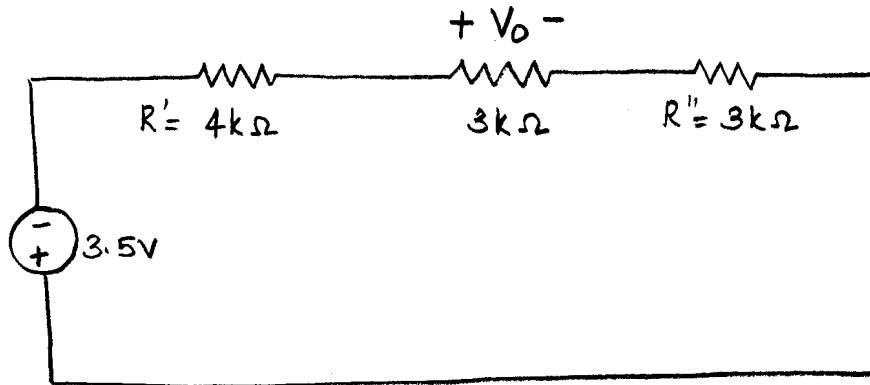

$$V_0 = \left( \frac{3k}{3k + 3k + 4k} \right) (-3.5)$$
$$= -1.05V$$

5.80 Find  $V_o$  in the network in Fig. P5.80 using source transformation.


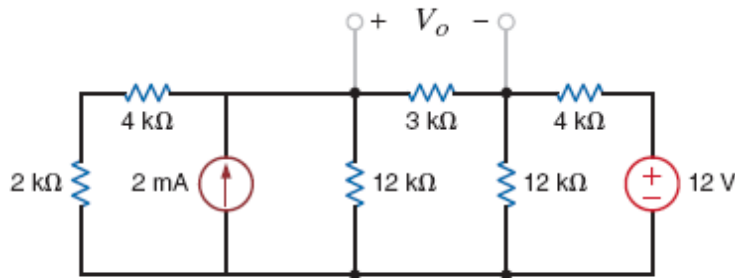




Figure P5.80

**SOLUTION:**

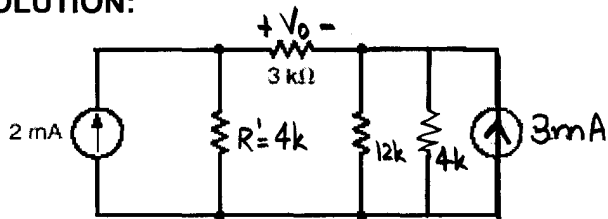


$$R' = 4k \parallel 12k = 3k\Omega$$

$$R'' = 3k \parallel 4k = 1.714k\Omega$$

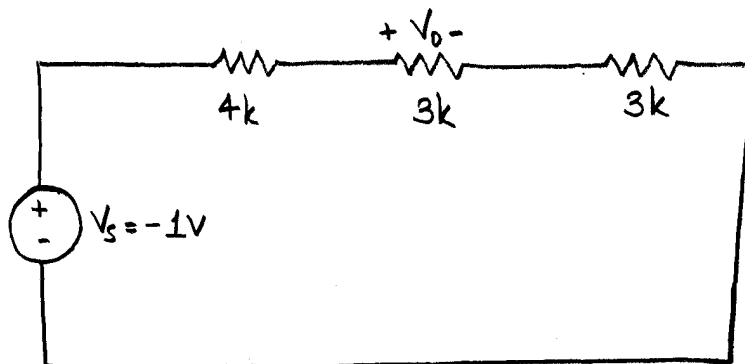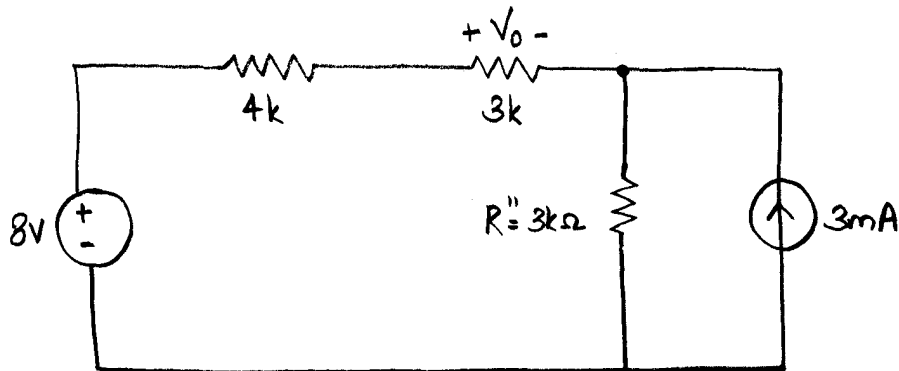



$$V_o = \left( \frac{3k}{3k + 3k + 4k} \right) (-1) = -0.3V$$

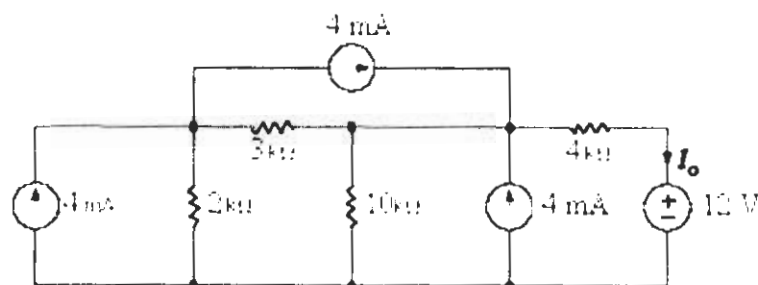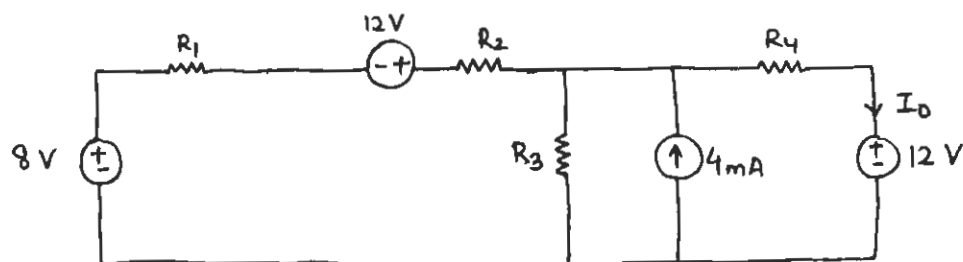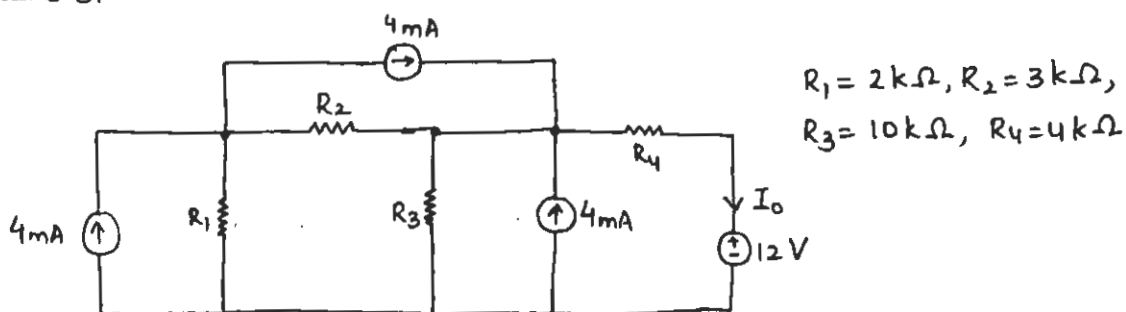5.81 Find  $I_o$  in the network in Fig. P5.81 using source transformation.


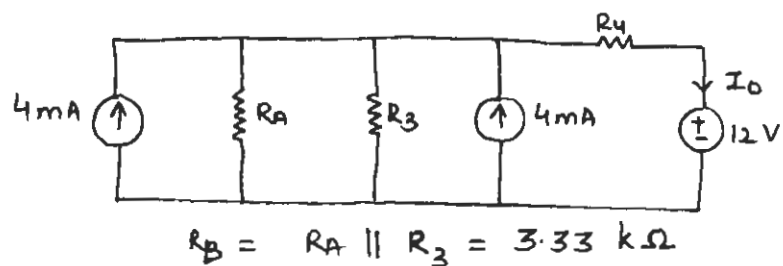




**Figure P5.81**

Solution: 5.81

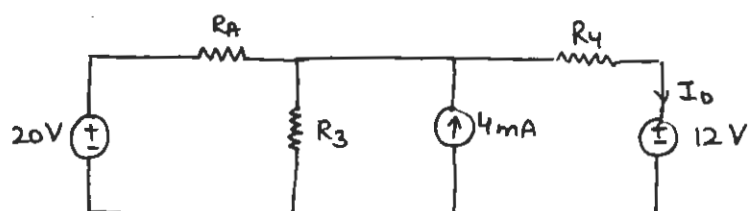

$$R_A = R_1 + R_2 = 5\text{ k}\Omega$$



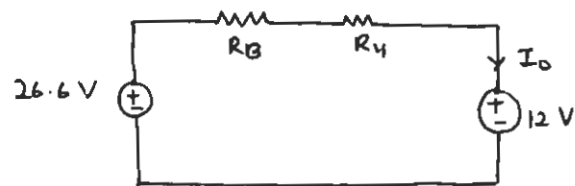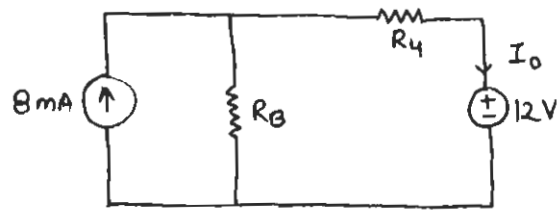

$$I_o = \frac{26.6 - 12}{R_B + R_4}$$

$$I_o = 1.99\text{ mA}$$

$$I_o = 2.00\text{ mA}$$

5.82 Find  $I_o$  in the circuit in Fig. P5.82 using source transformation.


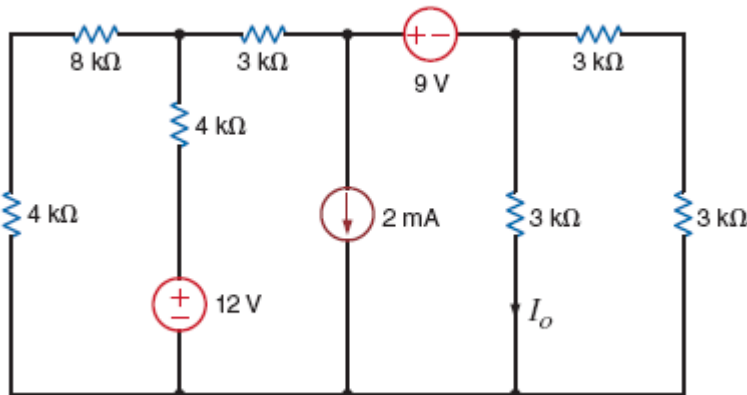



Figure P5.82



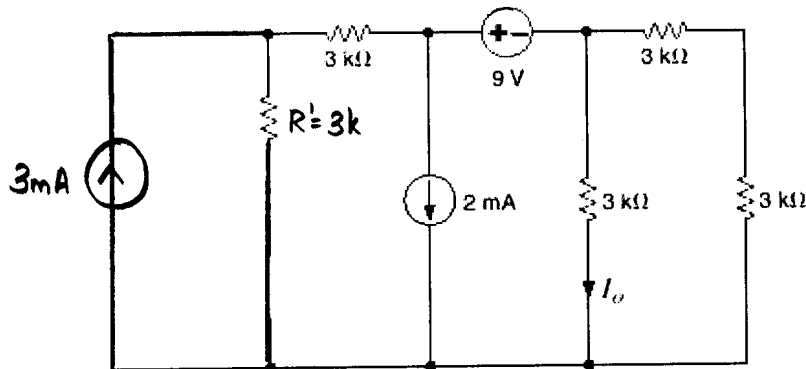
**SOLUTION:**

$$R' = (4k + 8k) \parallel 4k = 3k\Omega$$




$$R'' = 3k + 3k = 6k\Omega$$

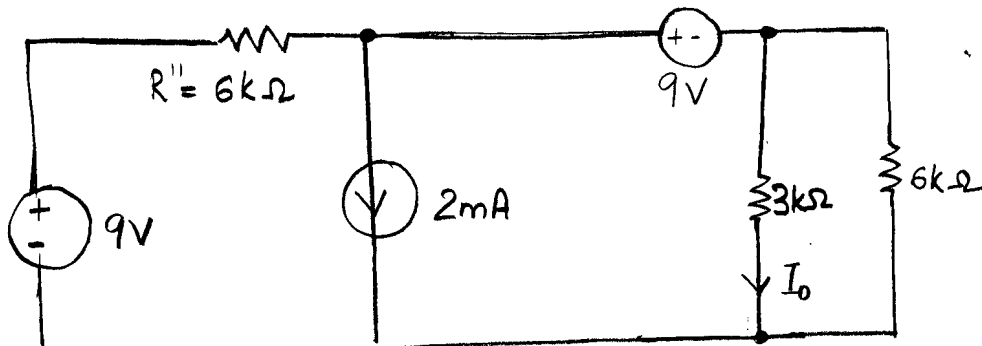

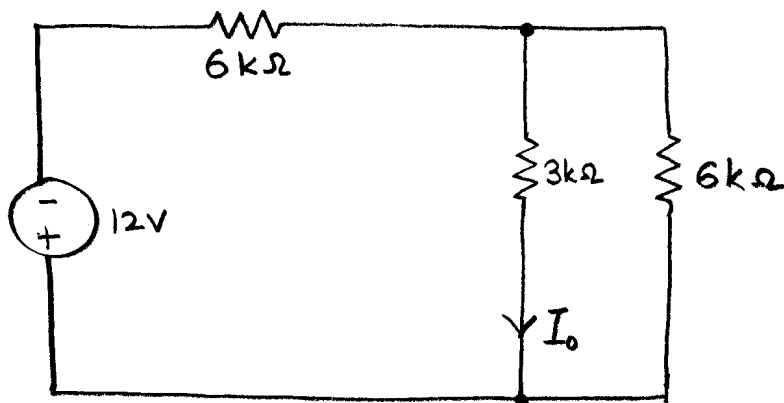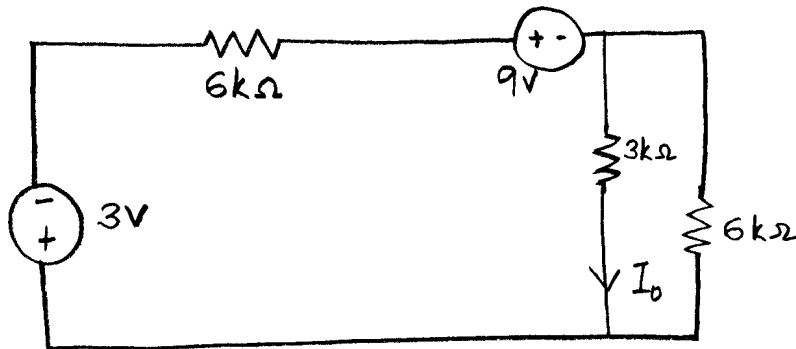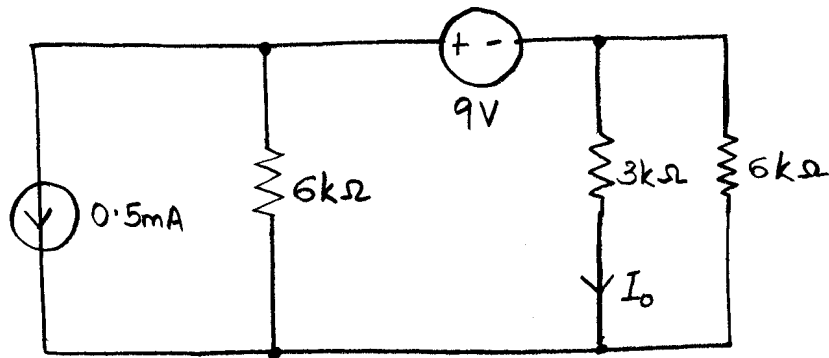


$$R = 6k \parallel 6k = 3k\Omega$$



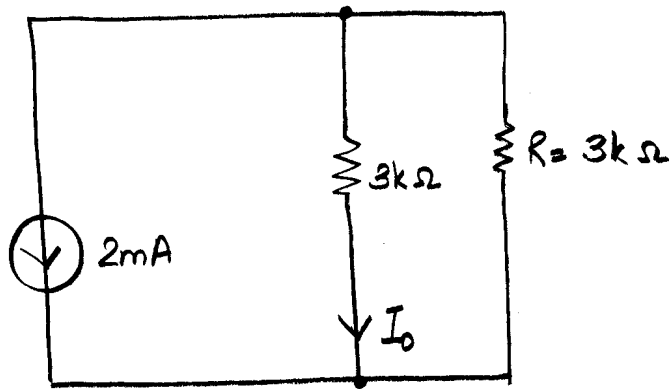




$$I_0 = \left( \frac{3k}{3k + 3k} \right) (-2m)$$
$$= -1mA$$





5.83 Find  $I_o$  in the circuit in Fig. P5.83 using source transformation.

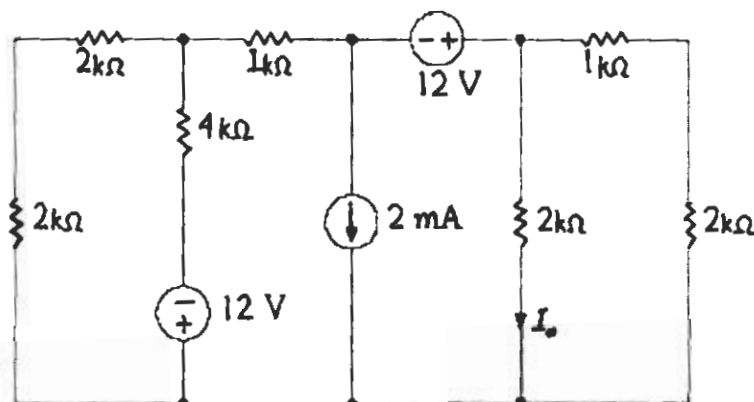

**Figure P5.83**

Solution: 5.83

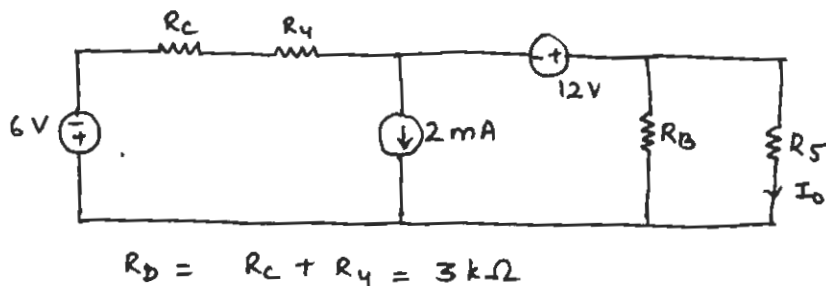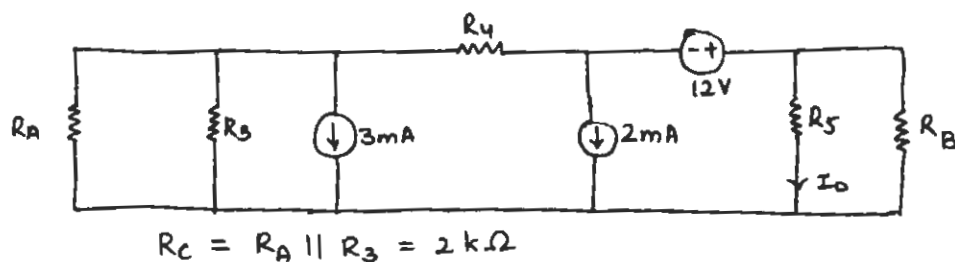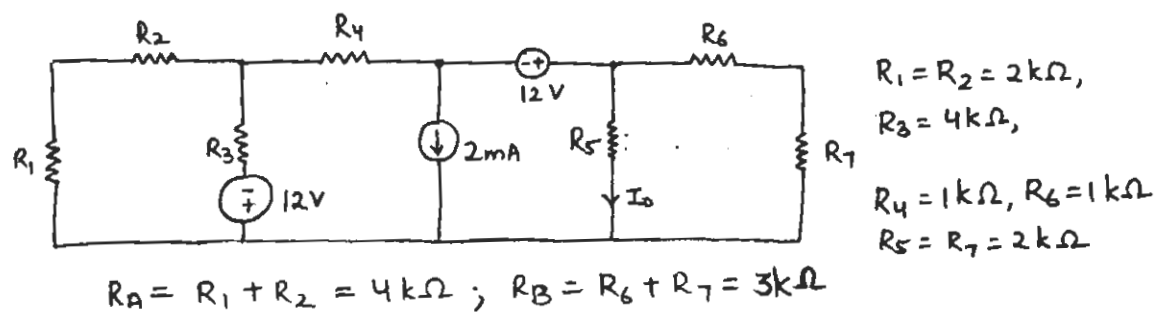

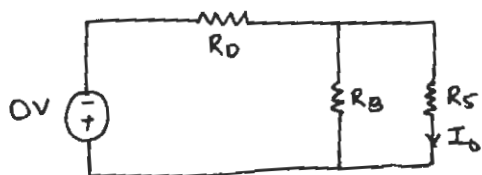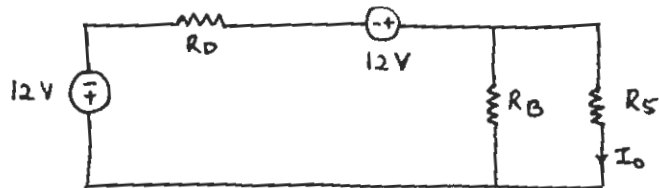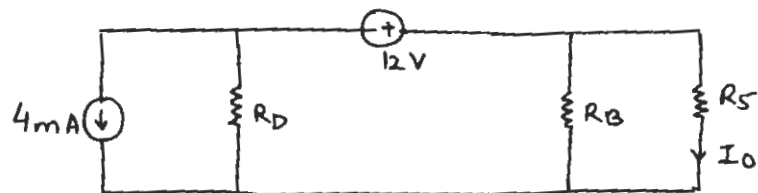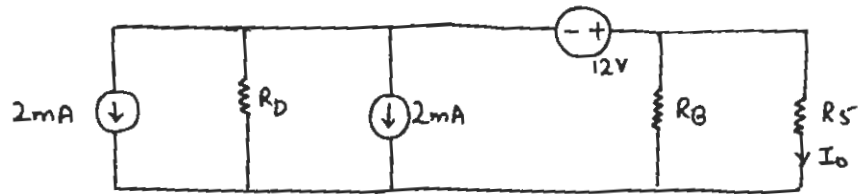

Here, Voltage = 0

$$\Rightarrow I_0 = 0A$$

5.84 Find  $I_o$  in the network in Fig. P5.84 using source transformation.



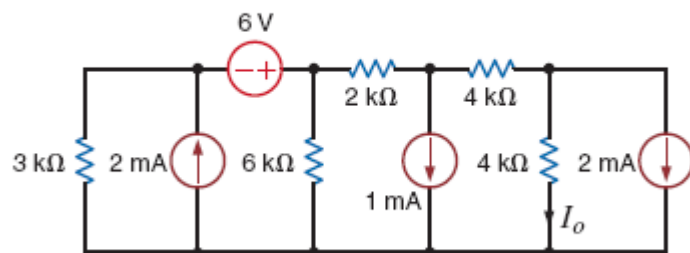
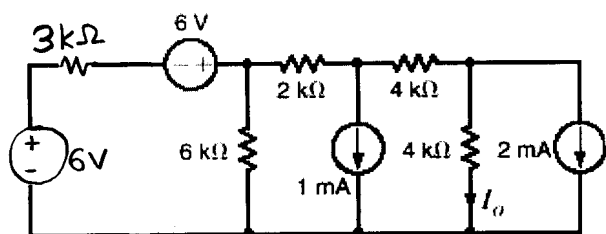



Figure P5.84

**SOLUTION:**


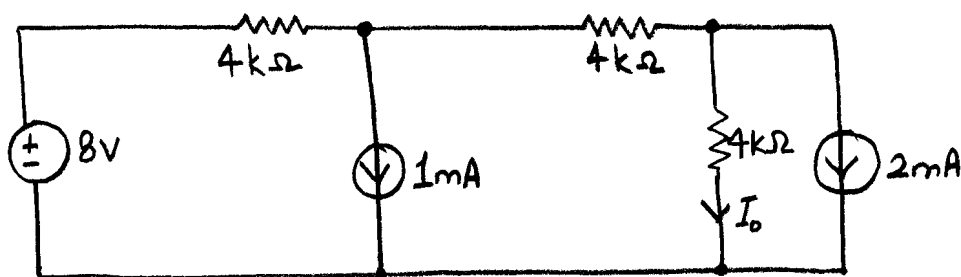


$$R' = 3k \parallel 6k = 2k\Omega$$

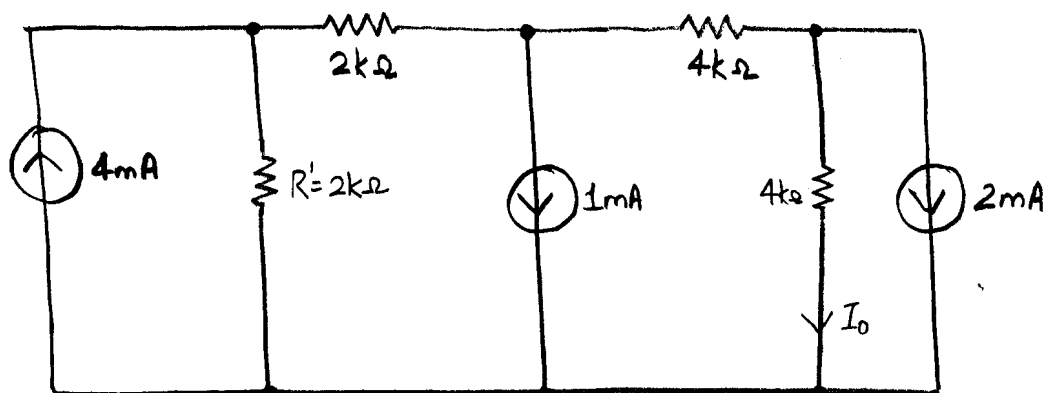

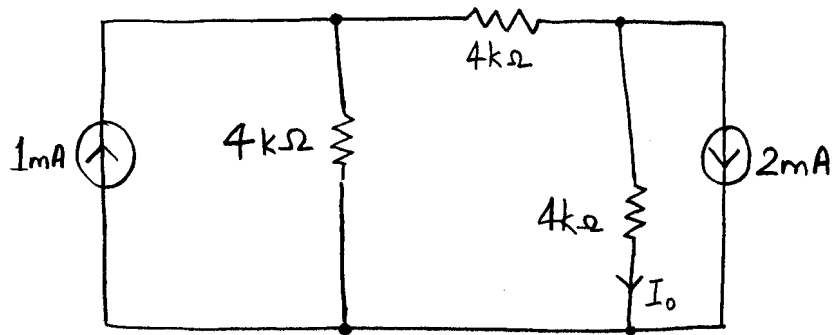

$$R'' = 4k + 4k = 8k\Omega$$

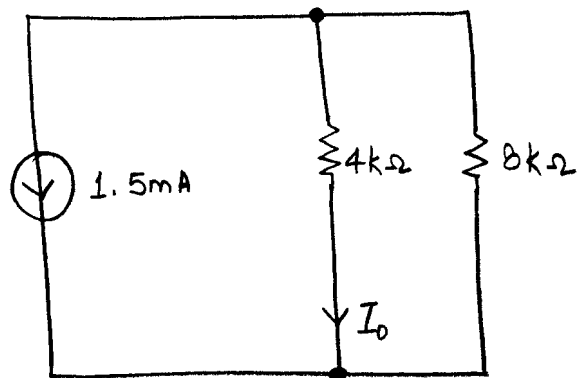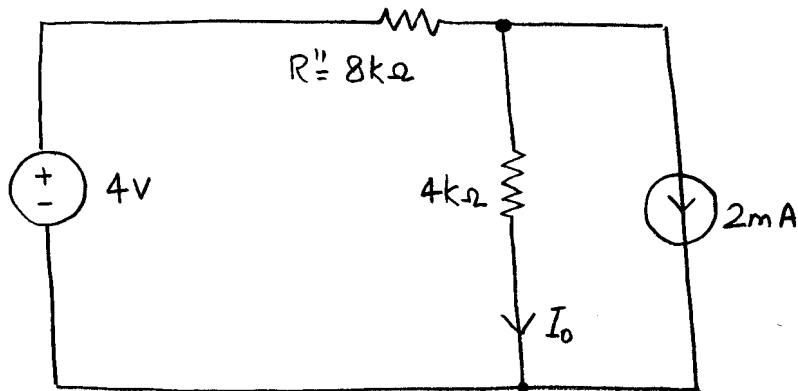

$$I_0 = \left( \frac{8k}{8k + 4k} \right) (-1.5m)$$
$$= -1mA$$

5.85 Find  $I_o$  in the network in Fig. P5.85 using source transformation.



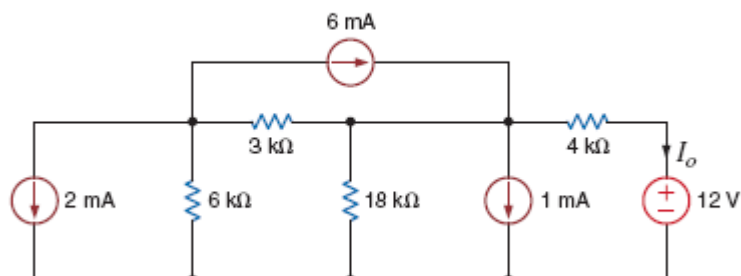
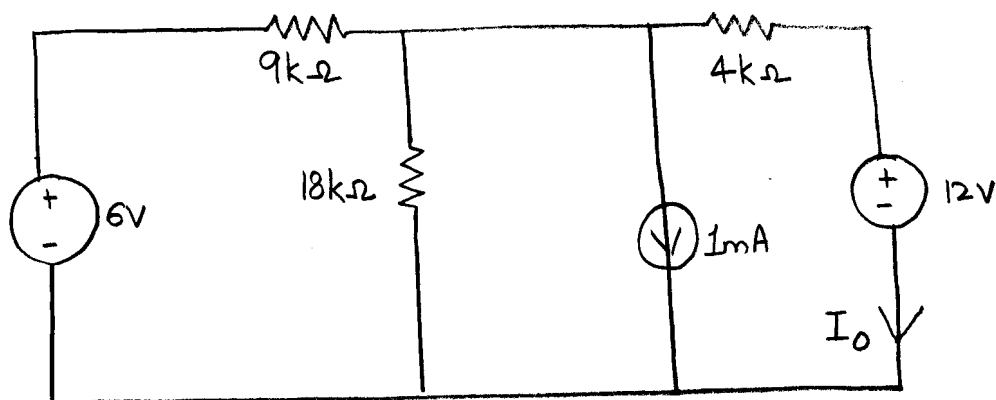




Figure P5.85

**SOLUTION:**

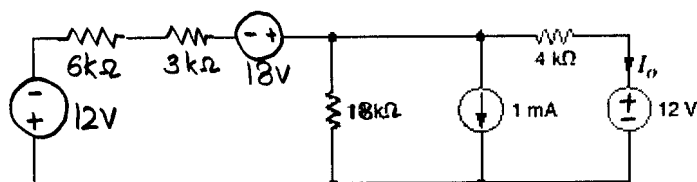

$$R' = 9k \parallel 18k = 6k\Omega$$

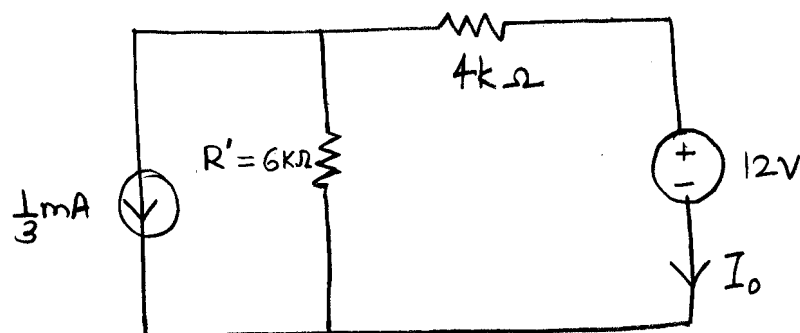

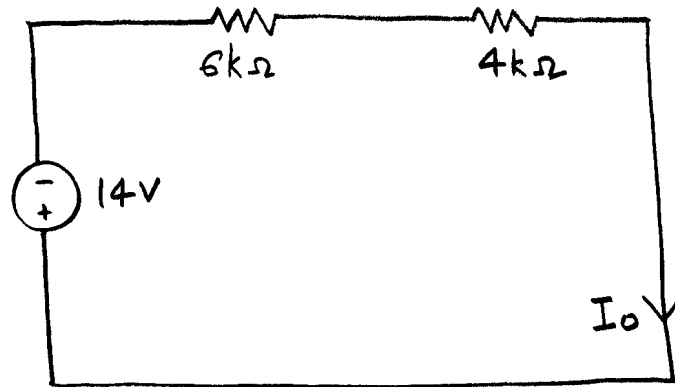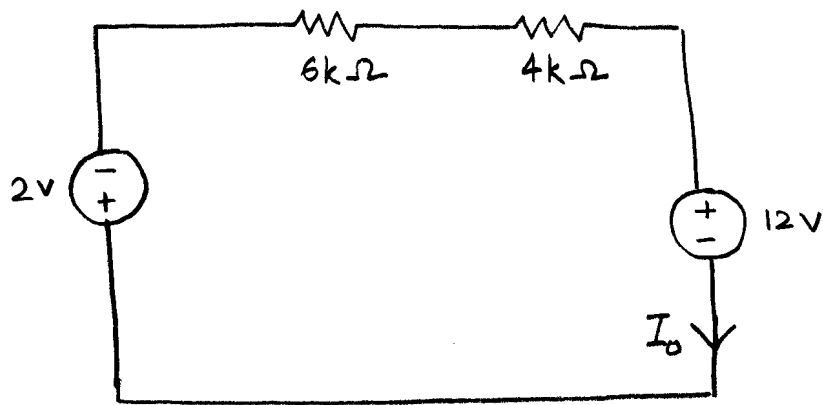

$$I_0 = \frac{-14}{10k}$$
$$= -1.4mA$$

5.86 Use source transformation to find  $I_o$  in the network in Fig. P5.86.



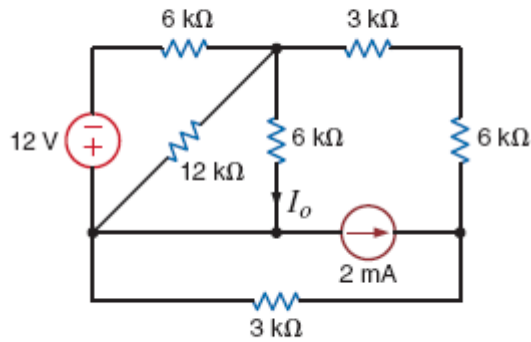


Figure P5.86


**SOLUTION:**

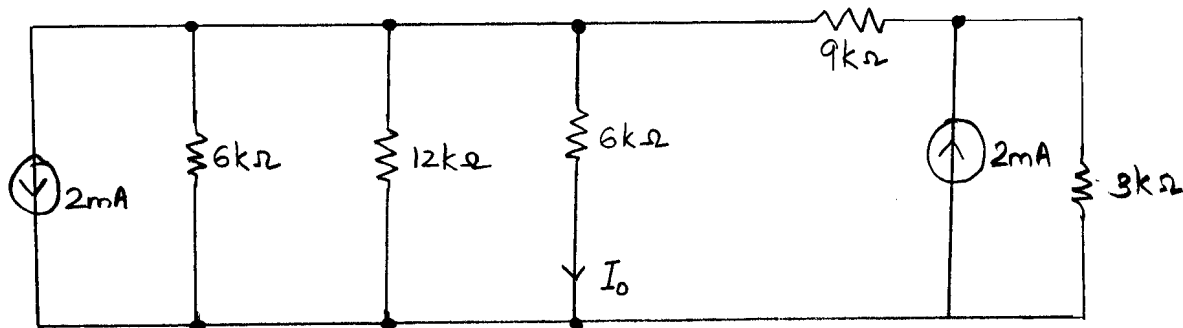


$$R' = 6k \parallel 12k = 4k\Omega$$

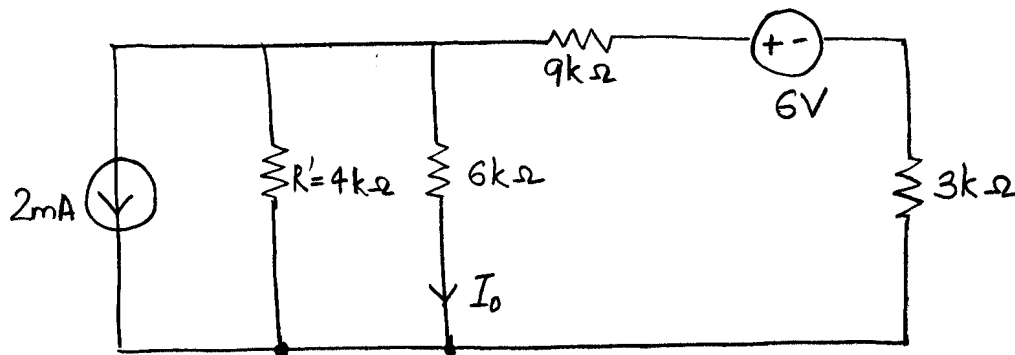



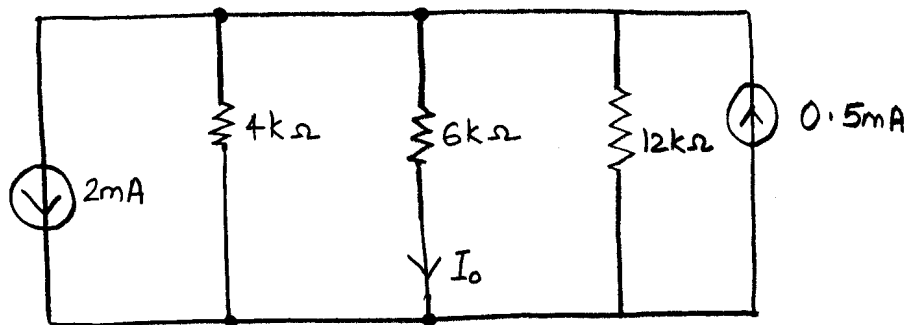


$$R'' = 4k \parallel 12k = 3k \Omega$$

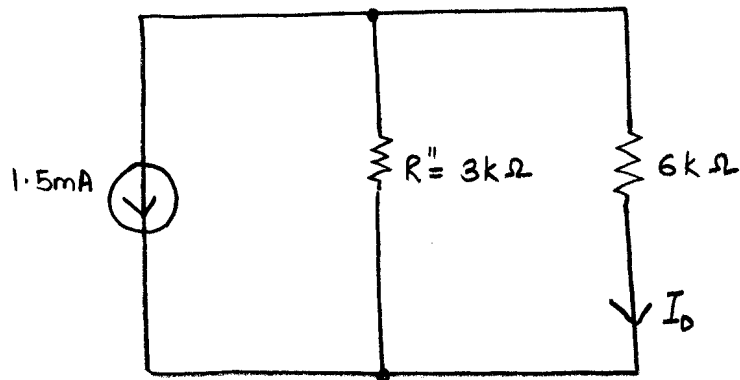

$$I_o = \left( \frac{3k}{3k+6k} \right) (-1.5m)$$


$$= -0.5mA$$

5.87 Use source transformation to find  $V_o$  in the network in Fig. P5.87.

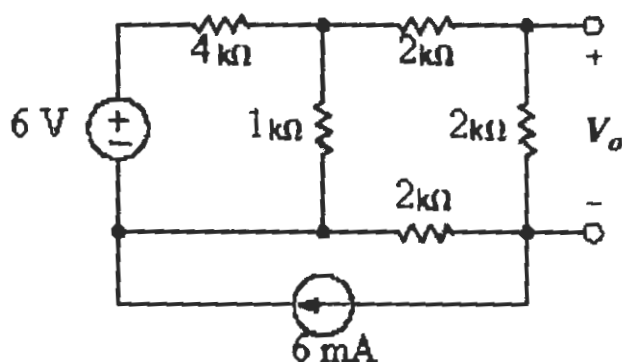


**Figure P5.87**

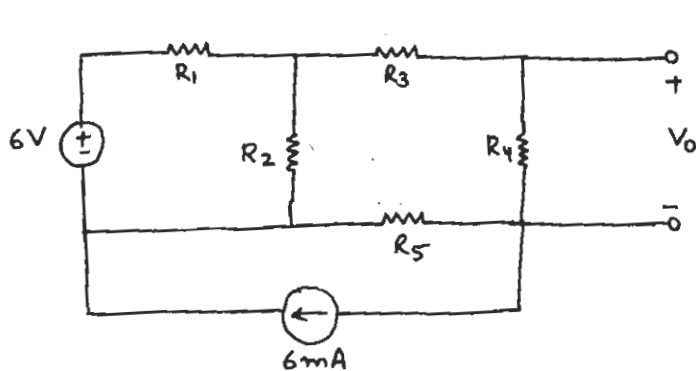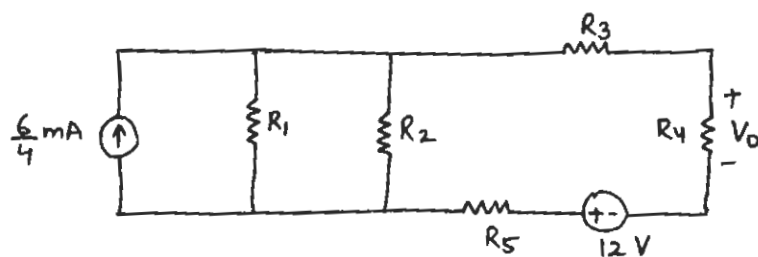
Solution: 5.87




$$R_1 = 4 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, \\ R_3 = R_4 = R_5 = 2 \text{ k}\Omega$$


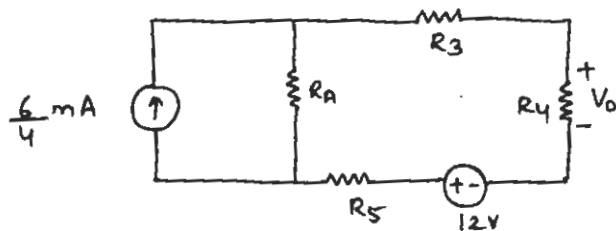
$$R_A = R_1 \parallel R_2 = \frac{4}{5} \text{ k}\Omega = 0.8 \text{ k}\Omega$$



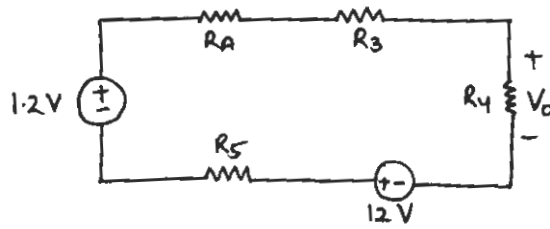

$$V_0 = 13.2 \times \frac{R_4}{R_A + R_3 + R_4 + R_5}$$

$$V_0 = 3.88 \text{ V}$$

5.88 Using source transformation, find  $I_o$  in the circuit in Fig. P5.88.



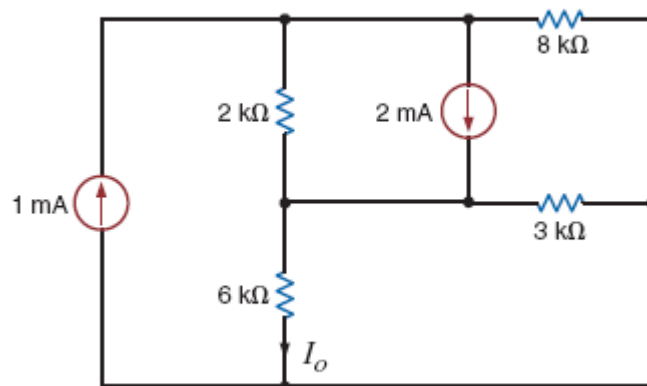
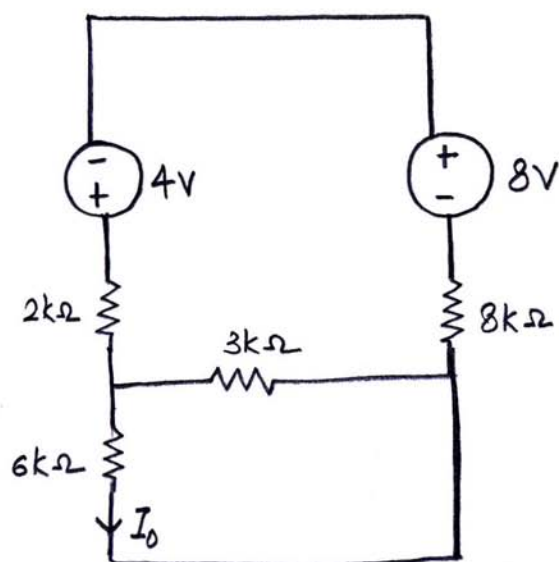
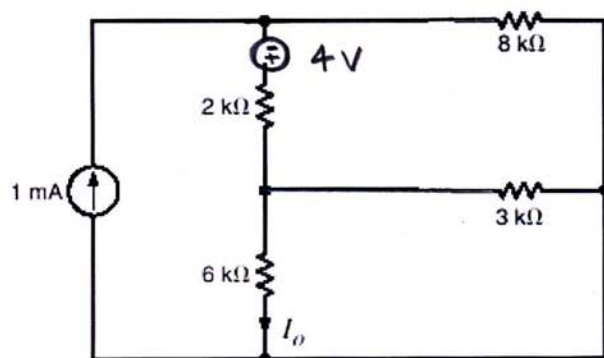


Figure P5.88


**SOLUTION:**

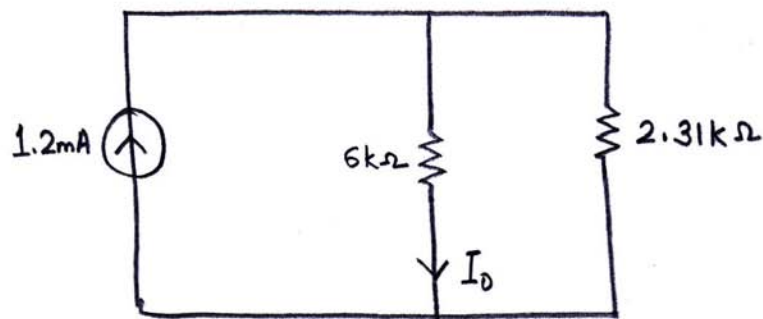

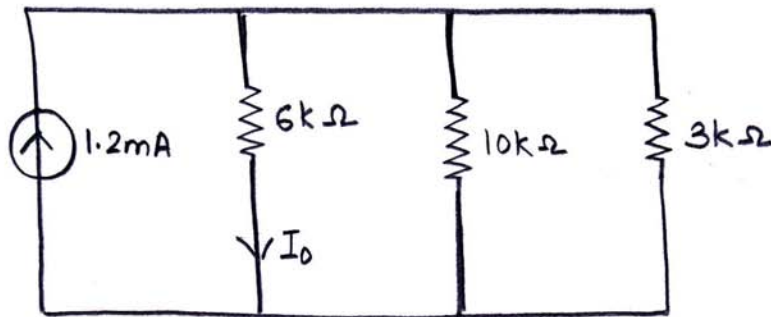


$$I_0 = \left( \frac{2.31k}{2.31k + 6k} \right) (1.2m)$$
$$= 0.333mA$$

5.89 Find  $I_o$  in the network in Fig. P5.89 using source transformation.

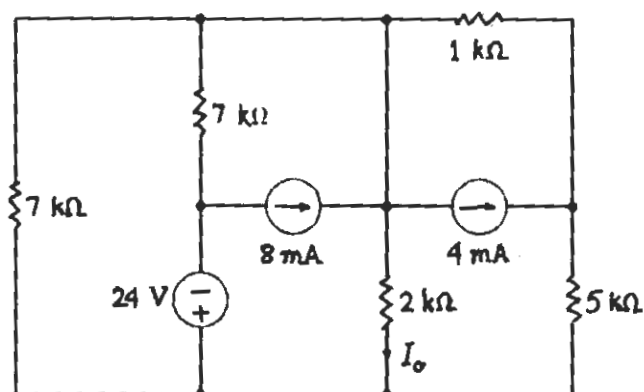



**Figure P5.89**

Solution: 5.89


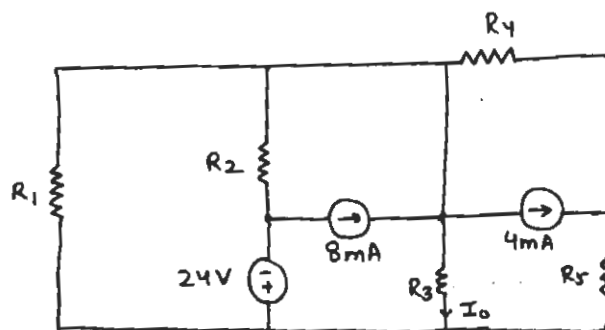


$$\begin{aligned} R_1 &= R_2 = 7 \text{ k}\Omega, \\ R_3 &= 2 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega, \\ R_5 &= 5 \text{ k}\Omega \end{aligned}$$


Rearrange circuit

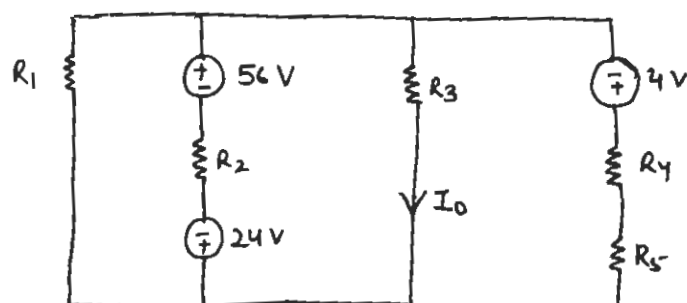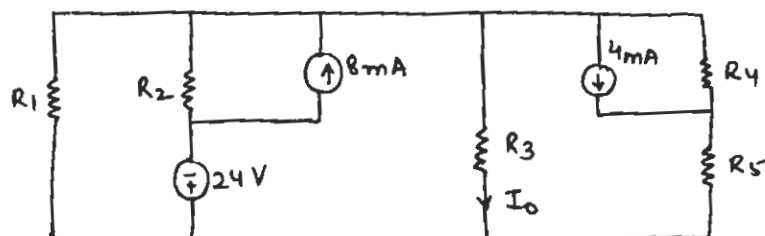

$$R_A = R_4 + R_5 = 6 \text{ k}\Omega$$

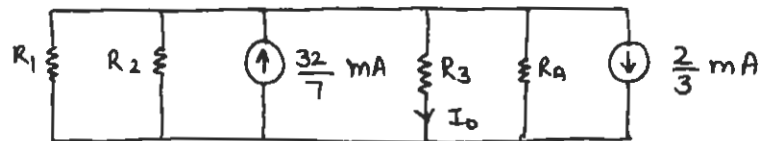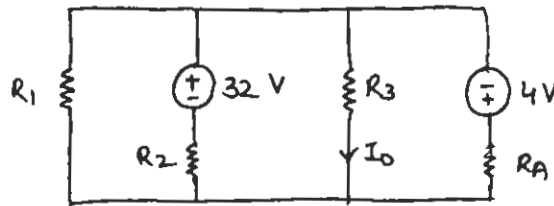
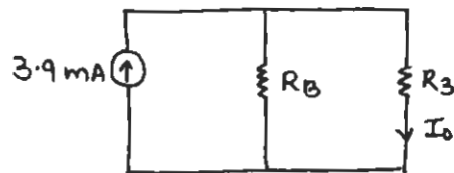
$$R_B = R_1 \parallel R_2 \parallel R_A = 2.21 \text{ k}\Omega$$



$$I_0 = 3.9 \times 10^{-3} \frac{R_B}{R_B + R_3}$$

$$I_0 = 2.05 \text{ mA}$$

5.90 Using source transformation, find  $I_o$  in the network in Fig. P5.90.




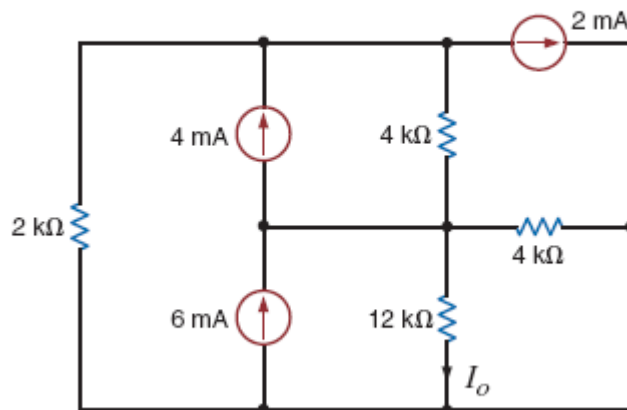
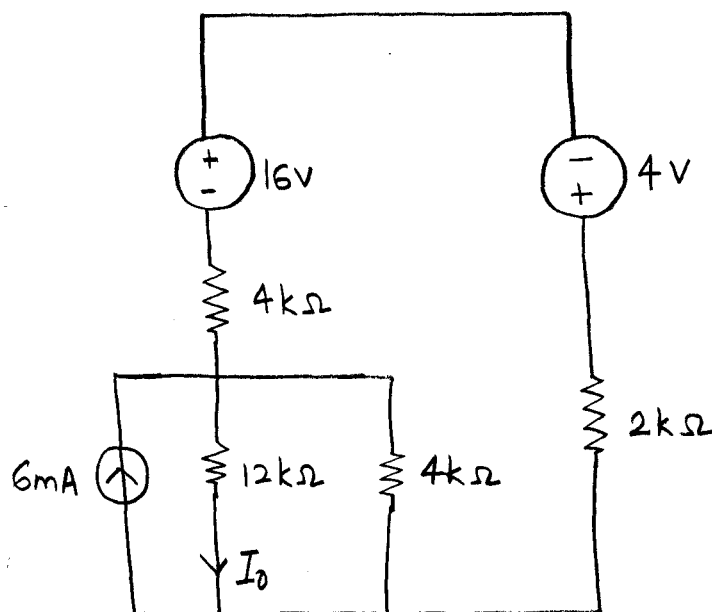


Figure P5.90

**SOLUTION:**

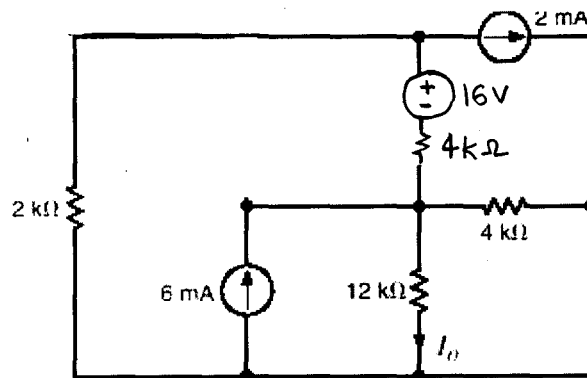

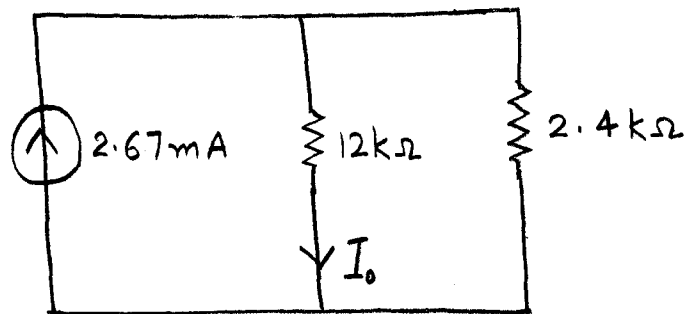


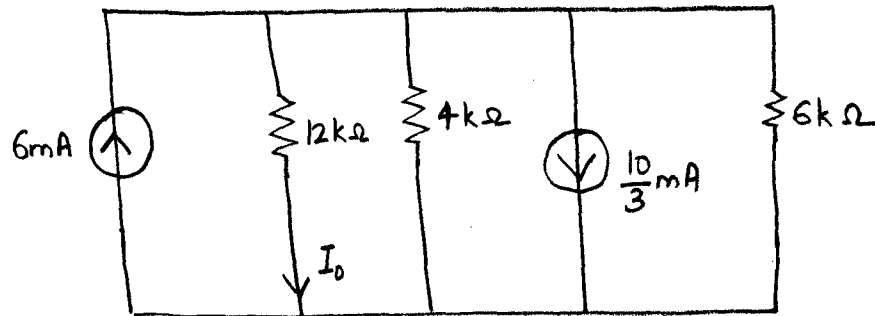

$$I_0 = \left( \frac{2.4k}{2.4k + 12k} \right) (2.667m)$$




$$= 0.444 \text{ mA}$$



5.91 Use source transformation to find  $I_o$  in the circuit in Fig. P5.91.

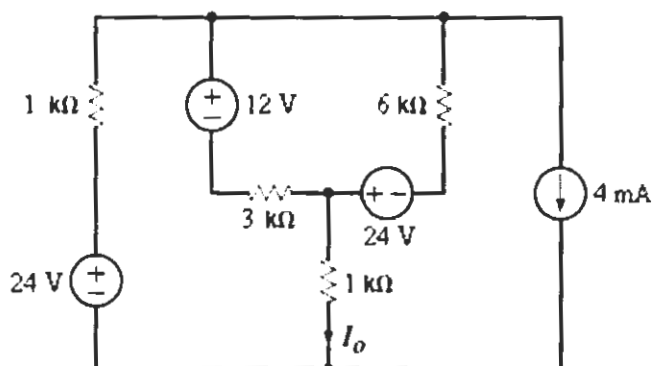

**Figure P5.91**

Solution: 5.91

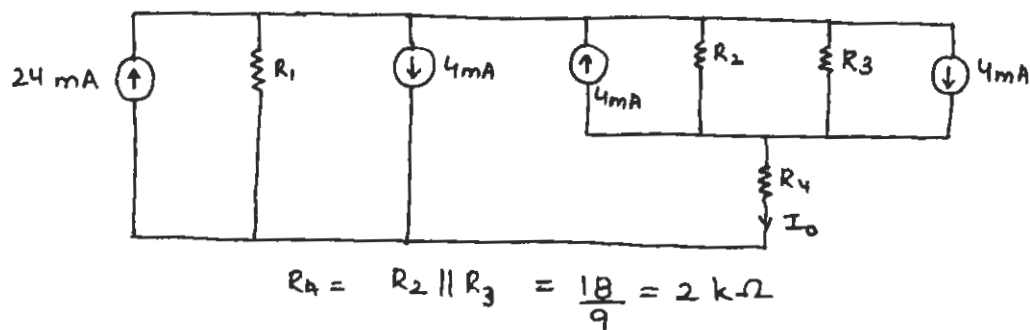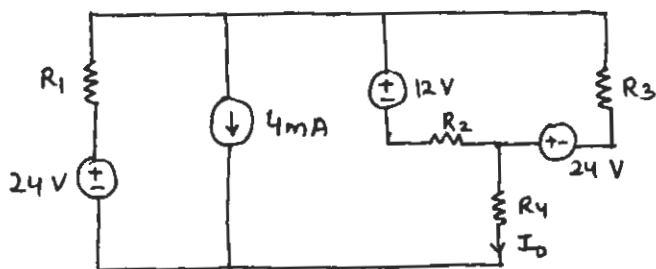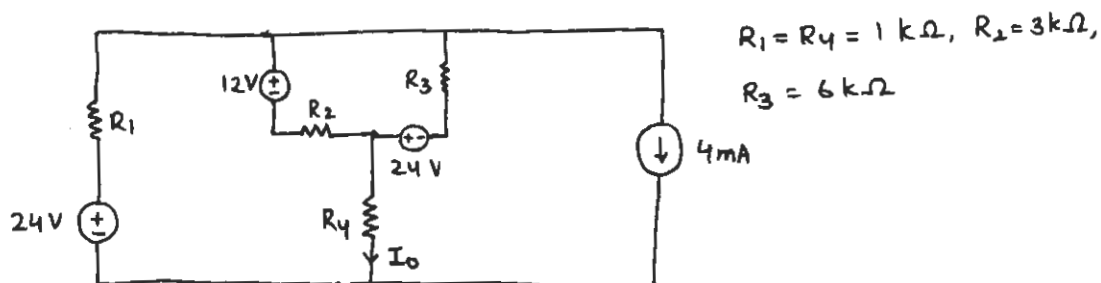

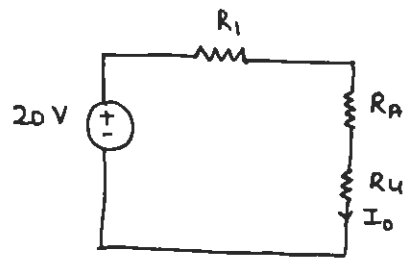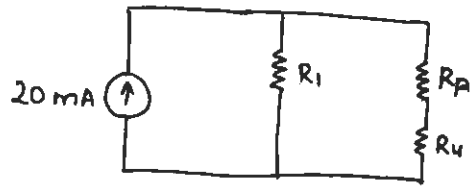


$$I_0 = \frac{20}{R_1 + R_A + R_4}$$

$$= \frac{20}{1 + 2 + 1}$$

$$= \frac{20}{4}$$


$$I_0 = 5 \text{ mA}$$

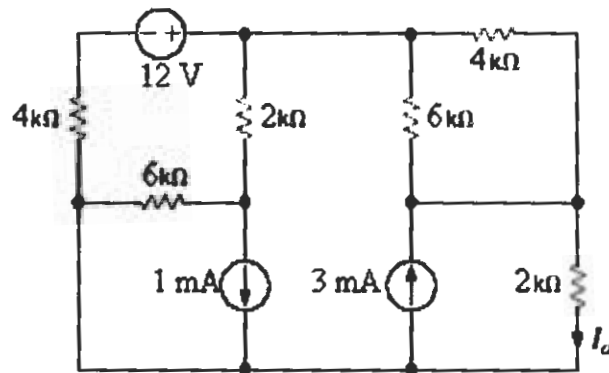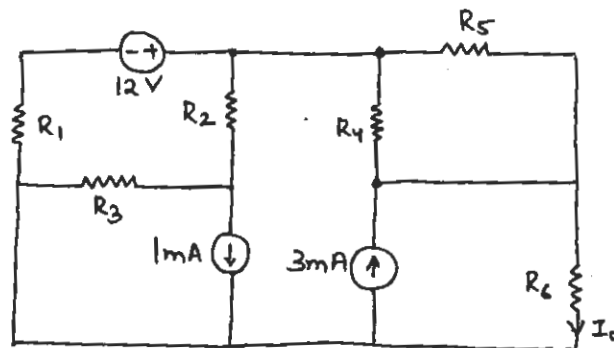5.92 Find  $I_o$  in the network in the Fig. P5.92 using source transformation.


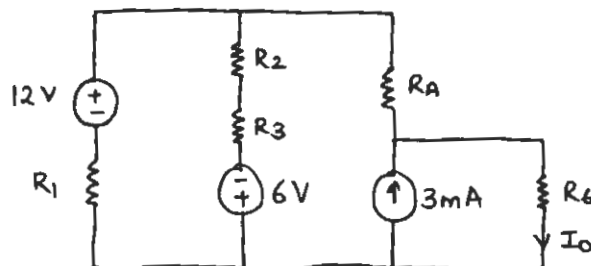


**Figure P5.92**


Solution: 5.92

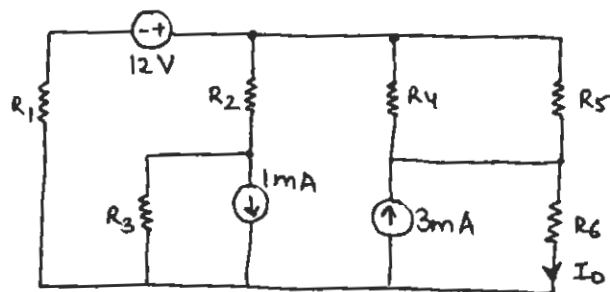



$$\begin{aligned} R_1 &= 4\text{ k}\Omega, R_2 = 2\text{ k}\Omega \\ R_3 &= R_4 = 6\text{ k}\Omega, \\ R_5 &= 4\text{ k}\Omega, R_6 = 2\text{ k}\Omega \end{aligned}$$


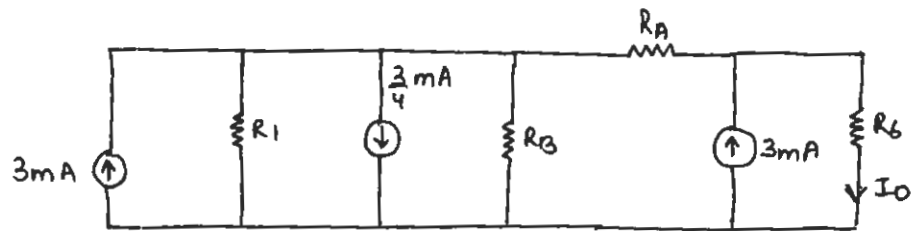
$$\begin{aligned} R_A &= R_4 \parallel R_5 \\ &= \frac{24}{10} = 2.4\text{ k}\Omega \\ R_B &= R_2 + R_3 \\ &= 2 + 6 = 8\text{ k}\Omega \end{aligned}$$



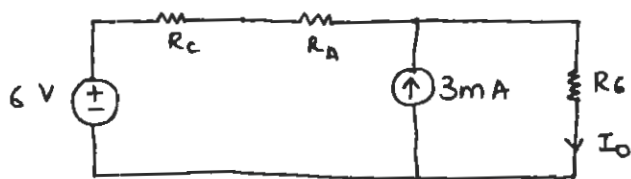
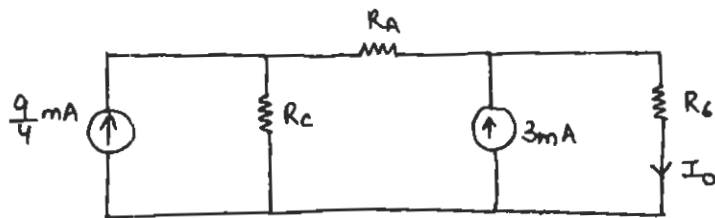
$$R_C = R_1 \parallel R_3 = 4 \parallel 8 = 2.67 \text{ k}\Omega$$



$$R_D = R_C + R_A$$

$$= \frac{32}{12} + \frac{24}{10}$$


$$= 5.07 \text{ k}\Omega$$

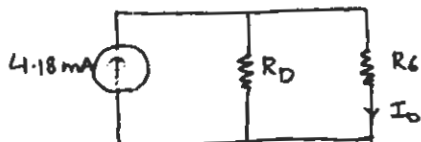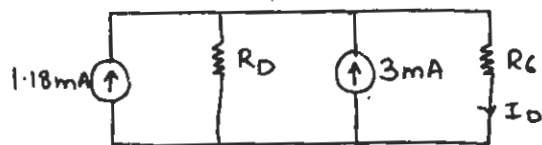

$$I_0 = \frac{4.18 \times 10^{-3} \times 5.07}{5.07 + 2}$$




$$I_0 = 3 \text{ mA}$$

5.93 Find  $I_o$  in the network in Fig. P5.93 using source transformation.

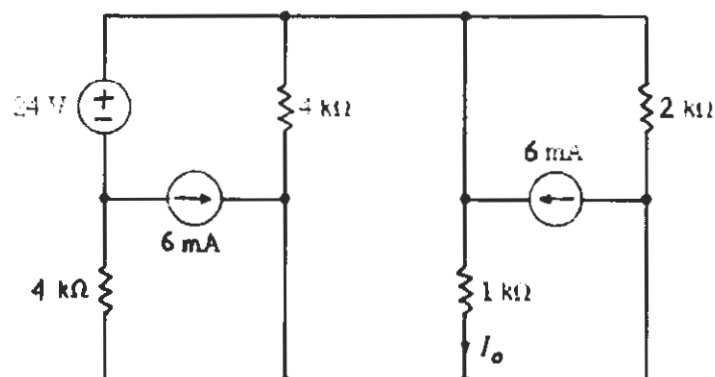


**Figure P5.93**

Solution: 5.93

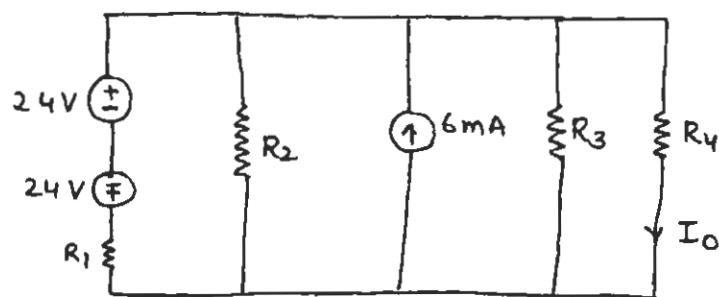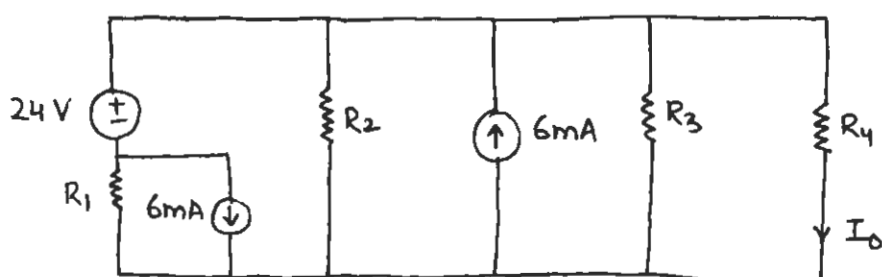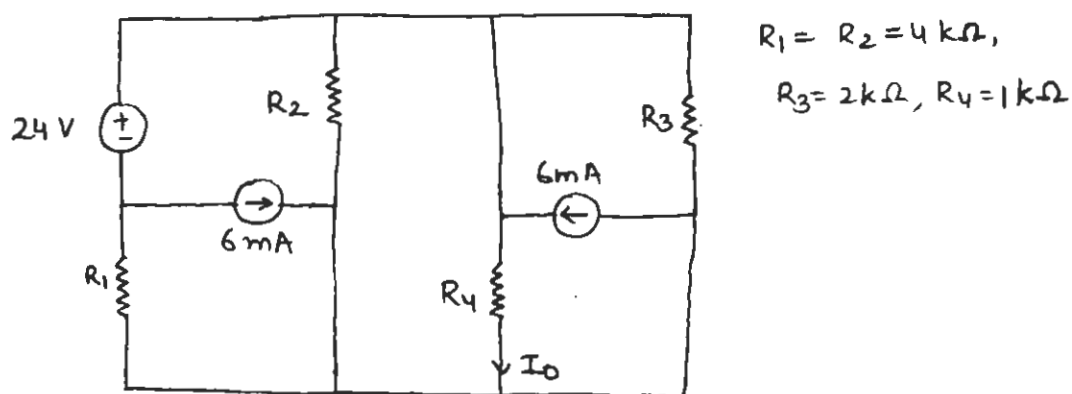

$$R_1 = 4\text{ k}\Omega, R_2 = 4\text{ k}\Omega, R_3 = 2\text{ k}\Omega$$
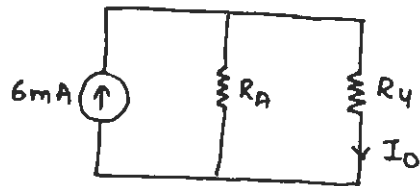
$$R_A = R_1 \parallel R_2 \parallel R_3 \\ = 1\text{ k}\Omega$$



$$I_0 = 6 \times 10^{-3} \cdot \frac{R_A}{R_A + R_4} \\ = 6 \cdot \frac{1}{2}$$

$$I_0 = 3\text{ mA}$$

5.94 Find  $R_L$  in the network in Fig. P5.94 in order to achieve maximum power transfer.


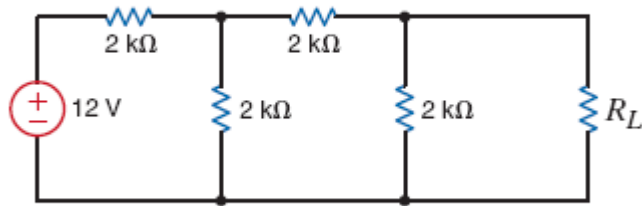


Figure P5.94

**SOLUTION:**

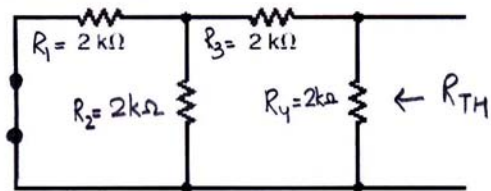

$$R_{TH} = [(R_1 || R_2) + R_3] || R_4 = 3\text{ k} || 2\text{ k} = 1.2\text{ k}\Omega$$

For maximum power transfer,  
 $R_L = R_{TH} = 1.2\text{ k}\Omega$



5.95 In the network in Fig. P5.95 find  $R_L$  for maximum power transfer and the maximum power transferred to this load.



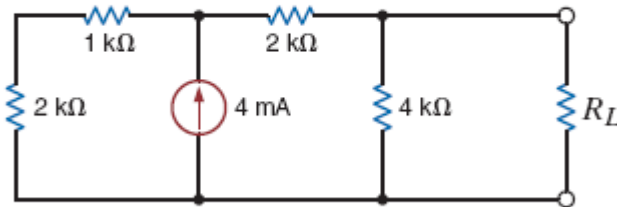
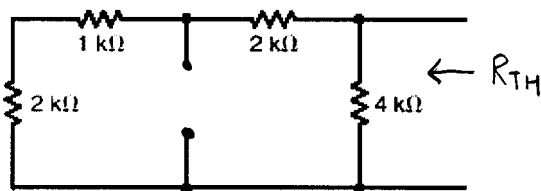


Figure P5.95

**SOLUTION:**

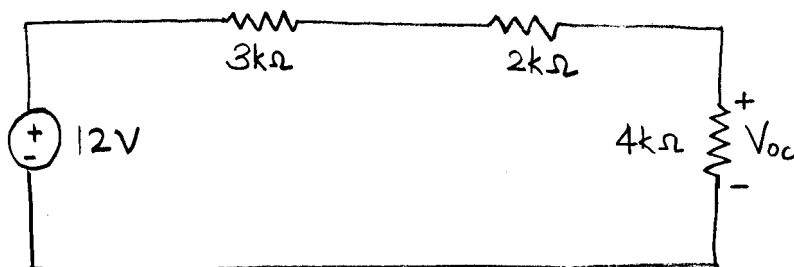

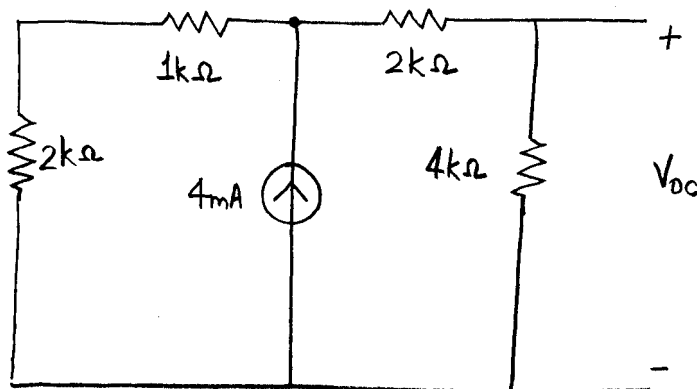
$$R_{TH} = (2k + 1k + 2k) \parallel 4k = 2.22k\Omega$$



$$V_{oc} = \left( \frac{4k}{3k + 2k + 4k} \right) (12)$$
$$= 5.33V$$

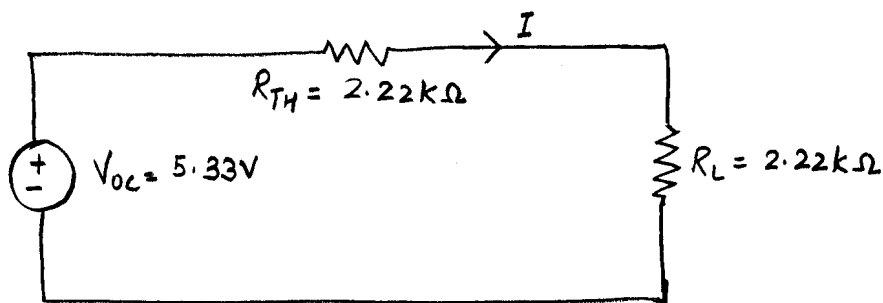
For maximum power transfer,  
 $R_L = R_{TH} = 2.22k\Omega$



$$I = \frac{5.33}{2.22k + 2.22k}$$
$$= 1.2mA$$


$$P_L = I^2 R_L = (1.2m)^2 (2.22k)$$
$$= 3.2mW$$

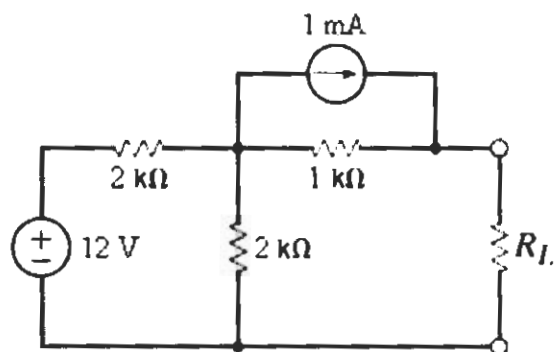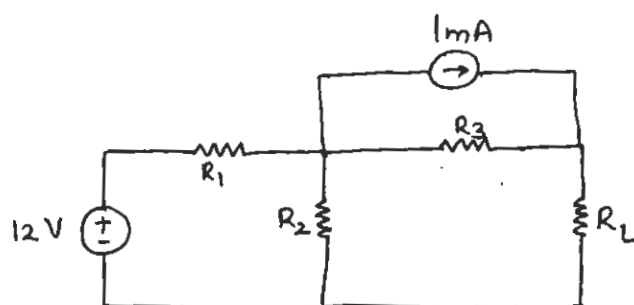**5.96** Find  $R_L$  for maximum power transfer and the maximum power that can be transferred to the load in Fig. P5.96.


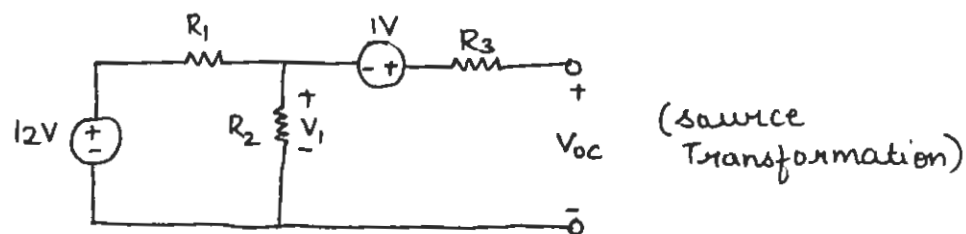


**Figure P5.96**

Solution: 5.96

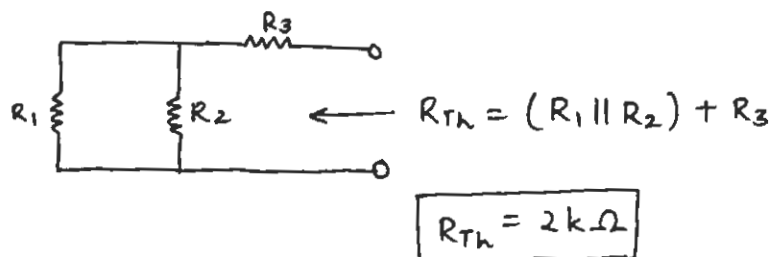


$$R_1 = R_2 = 2\text{ k}\Omega, \\ R_3 = 1\text{ k}\Omega$$



$$V_1 = 12 \cdot \frac{R_2}{R_1 + R_2} = 6\text{ V}, \quad V_{oc} = 1 + V_1$$

$$V_{oc} = 7\text{ V}$$

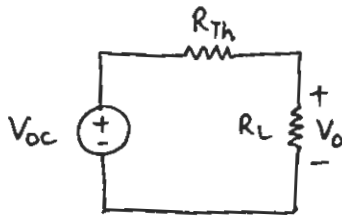

For maximum Power Transfer  $V_o = \frac{V_{oc}}{2}$   
and  $R_L = R_{Th}$

$$P_L = \frac{V_o^2}{R_L} = \frac{V_{oc}^2}{4R_{Th}}$$

$$P_L = 6.13 \text{ mW}$$

- 5.97 Find  $R_L$  for maximum power transfer and the maximum power that can be transferred to the load in the circuit in Fig. P5.97.


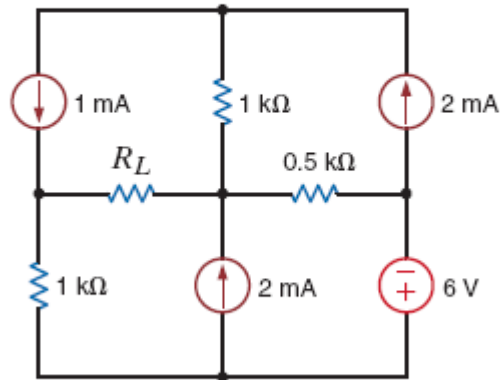


Figure P5.97

**SOLUTION:**

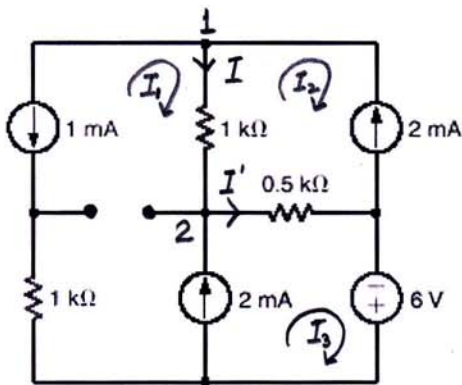

$$\text{KCL at 1: } I_1 = I + I_2$$

$$I = I_1 - I_2$$

$$I_1 = -1 \text{ mA}$$

$$I_2 = -2 \text{ mA}$$


$$\text{KCL at 2: } I + 2 \text{ m} = I'$$

$$I' = 3 \text{ mA}$$

KVL around the lower loop:


$$0 = 1 \text{ k} I_1 + V_{oc} + 0.5 \text{ k} (3 \text{ m})$$

$$V_{oc} = 5.5 \text{ V}$$

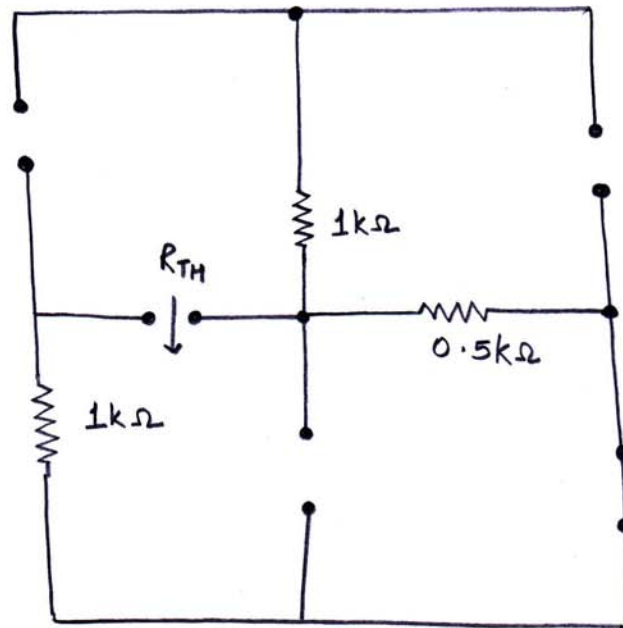

$$R_{TH} = 1.5k\Omega$$

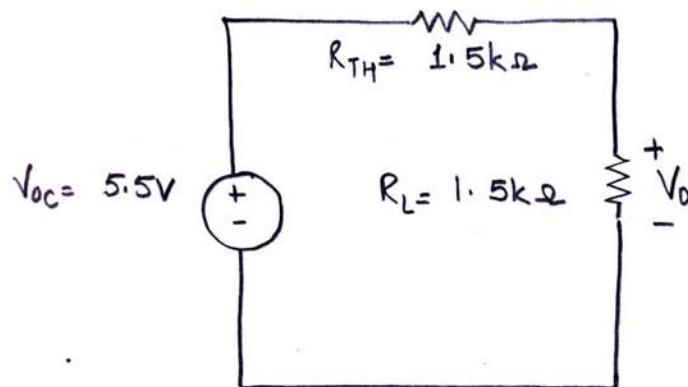for maximum power transfer,  
 $R_L = R_{TH} = 1.5k\Omega$



$$V_o = \left( \frac{1.5k}{1.5k + 1.5k} \right) (5.5) \\ = 2.75V$$

$$P_L = \frac{V_o^2}{R_L} = \frac{(2.75)^2}{1.5k} \\ = 5.04mW$$

- 5.98 Find  $R_L$  for maximum power transfer and the maximum power that can be transferred to the load in the network in Fig. P5.98.


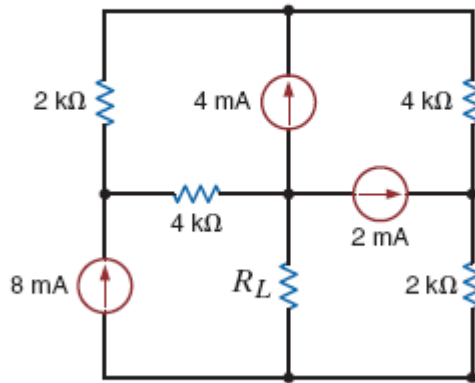


Figure P5.98

**SOLUTION:**

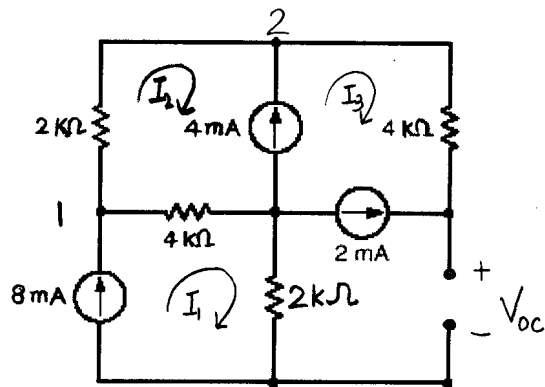

$$\text{KCL at 1: } I_2 + I = 8\text{m}$$

$$I = 8\text{m} - I_2$$

$$\text{KCL at 2: } I_2 + 4\text{m} = I_3$$

$$I_3 = -2\text{mA}$$

$$I_2 = -2\text{m} - 4\text{m} = -6\text{mA}$$

$$I_1 = 8\text{mA}$$


$$\text{KVL: } 2\text{k}I_1 + 4\text{k}I$$

$$= 2\text{k}I_2 + 4\text{k}I_3 + V_{oc}$$

$$2\text{k}(8\text{m}) + 4\text{k}(8\text{m} - I_2) = 2\text{k}(-6\text{m}) + 4\text{k}(-2\text{m}) + V_{oc}$$


$$V_{oc} = 92\text{V}$$



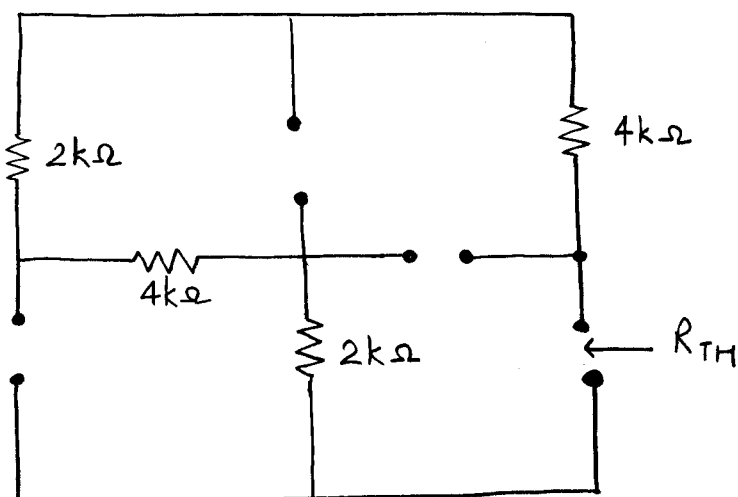

$$R_{TH} = 2k + 4k + 2k + 4k = 12k\Omega$$

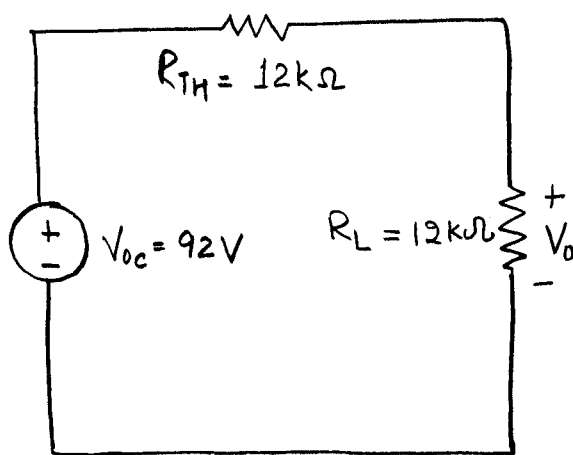For maximum power transfer,  
 $R_L = R_{TH} = 12k\Omega$



$$V_O = \left( \frac{12k}{12k + 12k} \right) (92) = 46V$$

$$P_L = \frac{V_O^2}{R_L} = \frac{(46)^2}{12k} = 176.33 \text{ mW}$$

- 5.99 Find  $R_L$  for maximum power transfer and the maximum power that can be transferred to the load in the circuit in Fig. P5.99.


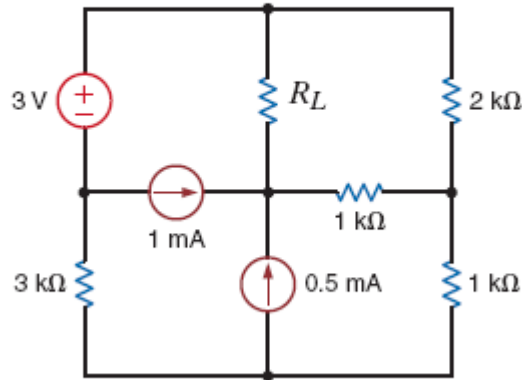


Figure P5.99

**SOLUTION:**

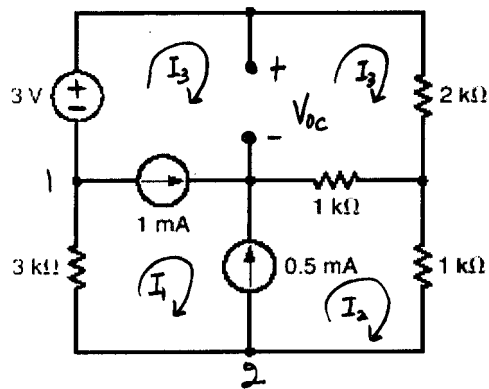

$$\text{KCL at 1: } I_1 = 1\text{m} + I_3$$

$$I_3 = I_1 - 1\text{m}$$

$$V_{oc} = 2\text{k}I_3 - 1.5\text{m}(1\text{k})$$

$$V_{oc} = 2\text{k}I_3 - 1.5$$

$$\text{KCL at 2: } I_2 = 0.5\text{m} + I_1$$

$$-I_1 + I_2 = 0.5\text{m}$$


KVL around outer loop:

$$3 = 3\text{k}I_1 + 1\text{k}I_2 + 2\text{k}I_3$$

$$3 = 3\text{k}I_1 + 1\text{k}I_2 + 2\text{k}(I_2 - 1.5\text{m})$$


$$3\text{k}I_1 + 3\text{k}I_2 = 6$$
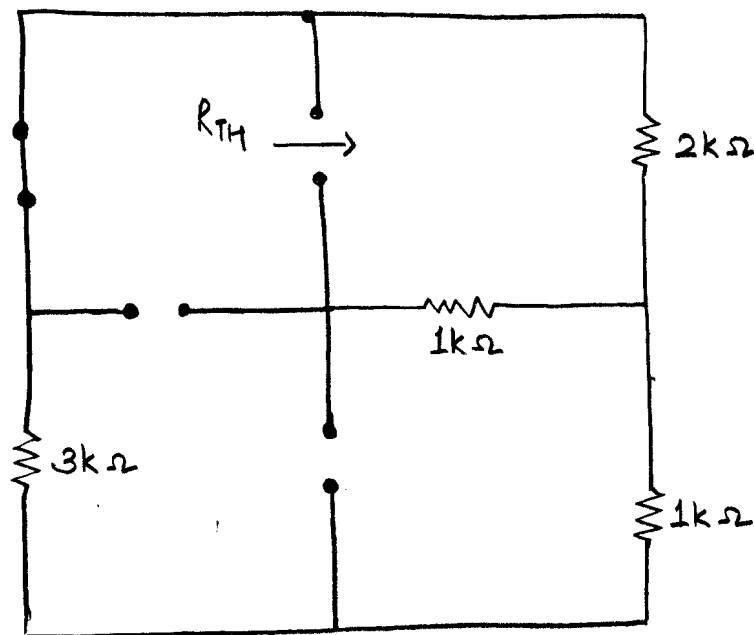
$$\begin{aligned} - I_1 + I_2 &= 0.5\text{m} \\ I_1 &= 0.75\text{mA} \\ I_2 &= 1.25\text{mA} \\ I_3 &= 0.75\text{mA} - 1\text{mA} = -0.25\text{mA} \\ V_{oc} &= 2\text{k}(-0.25\text{mA}) - 1.5 \\ &= -2\text{V} \end{aligned}$$



$$R_{TH} = [(3\text{k} + 1\text{k}) \parallel 2\text{k}] + 1\text{k} = 2.33\text{k}\Omega$$

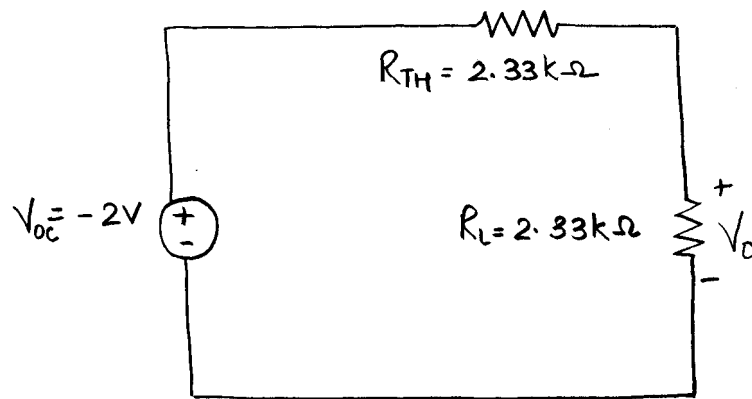
For maximum power transfer,  
 $R_L = R_{TH} = 2.33\text{k}\Omega$



$$V_o = \left( \frac{2.33k}{2.33k + 2.33k} \right) (-2) = -1V$$


$$P_L = \frac{V_o^2}{R_L} = \frac{(-1)^2}{2.33k} = 0.429mW$$

5.100 Choose  $R_L$  in Fig. P5.100 for maximum power transfer.

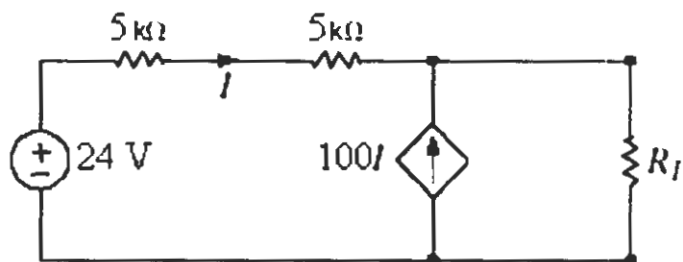

**Figure P5.100**

Solution: 5.100

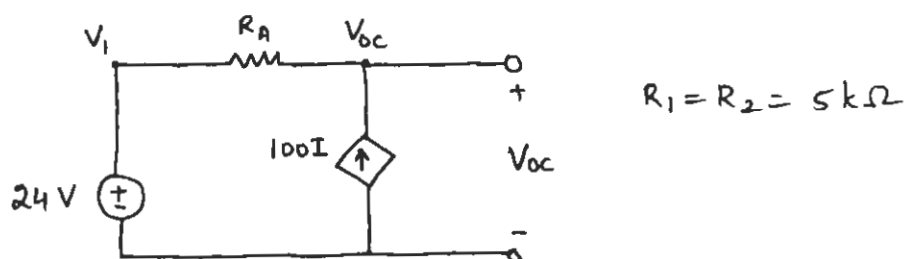

$$R_A = R_1 + R_2 = 10\text{ k}\Omega$$


$$V_1 = 24\text{ V}$$

$$\text{KCL @ } V_{OC}: \frac{V_{OC} - V_1}{R_A} - 100I = 0$$

$$\Rightarrow I - 100I = 0$$

$$\Rightarrow I = 0$$
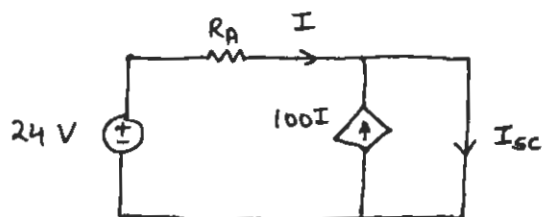
$$V_{OC} - V_1 = 0 \Rightarrow V_{OC} = V_1 = 24\text{ V}$$



$$I_{SC} = I + 100I = 101I$$

$$I = \frac{24}{10 \times 10^3} = 2.4\text{ mA}$$

$$I_{sc} = 242.4 \text{ mA}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = 99 \Omega$$

For maximum power transfer,  $R_L = 99 \Omega$

- 5.101 Find  $R_L$  for maximum power transfer and the maximum power that can be transferred to the load in Fig. P5.101.


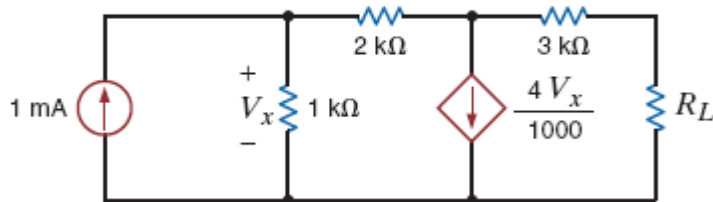


Figure P5.101

**SOLUTION:**

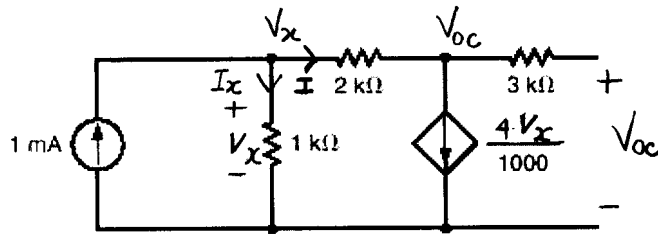

$$\text{KCL at } V_x: 1\text{m} = \frac{V_x}{1\text{k}} + \frac{V_x - V_{oc}}{2\text{k}}$$


$$3V_x - V_{oc} = 2$$

$$\text{KCL at } V_{oc}: \frac{V_x - V_{oc}}{2\text{k}} = \frac{4V_x}{1000}$$

$$7V_x + V_{oc} = 0$$

$$V_x = 0.2\text{V}$$

$$V_{oc} = -1.4\text{V}$$

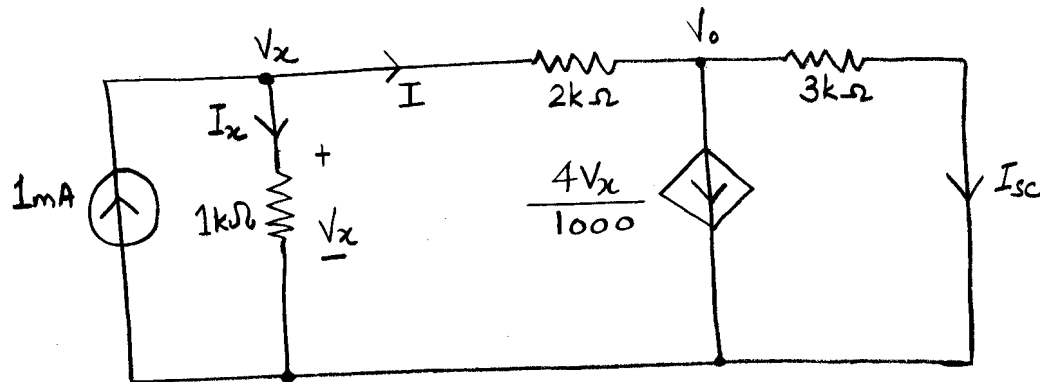

$$\text{KCL at } V_x: 1\text{m} = \frac{V_x}{1\text{k}} + \frac{V_x - V_o}{2\text{k}}$$

$$3V_x - V_o = 2$$

$$\text{KCL at } V_o: \frac{V_x - V_o}{2\text{k}} = \frac{4V_x}{1000} + \frac{V_o}{3\text{k}}$$

$$21V_x + 5V_o = 0$$


$$V_x = 0.278\text{V}$$

$$V_o = -1.167\text{V}$$

$$I_{sc} = \frac{V_o}{3\text{k}} = \frac{-1.167}{3\text{k}} = -0.389\text{mA}$$

$$R_{TH} = \frac{-1.4}{-0.389\text{m}} = 3.6\text{k}\Omega$$

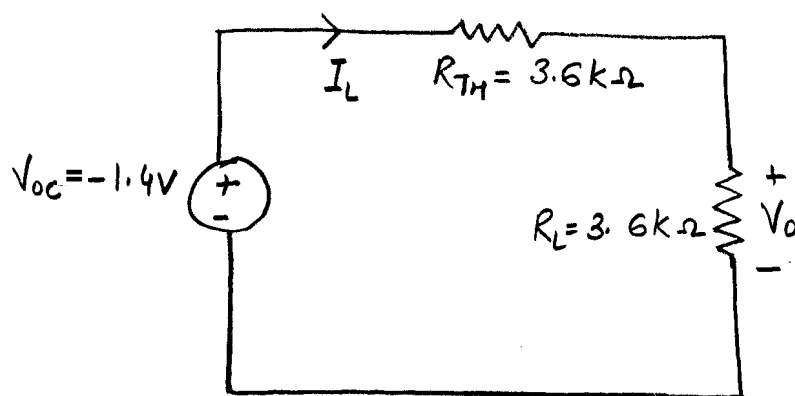For maximum power transfer,  
 $R_L = R_{TH} = 3.6\text{k}\Omega$ .





$$\begin{aligned} I_L &= \frac{-1.4}{3.6k + 3.6k} \\ &= -0.194 \text{ mA} \end{aligned}$$

$$P_L = I_L^2 R_L = (-0.194)^2 (3.6k) = 0.136 \text{ mW}$$

5.102 Find the value of  $R_L$  in the network in Fig. P5.102 for maximum power transfer.



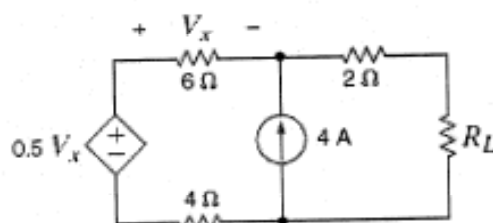


Figure P5.102


Solution: 5.102

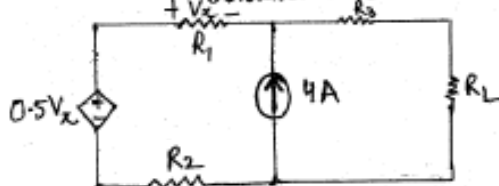
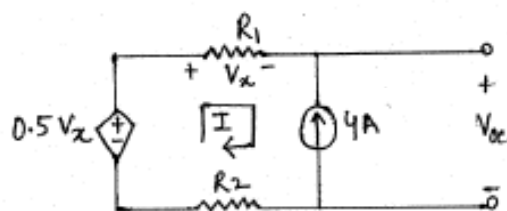
$$R_1 = 6\Omega, R_2 = 4\Omega \\ R_3 = 2\Omega$$



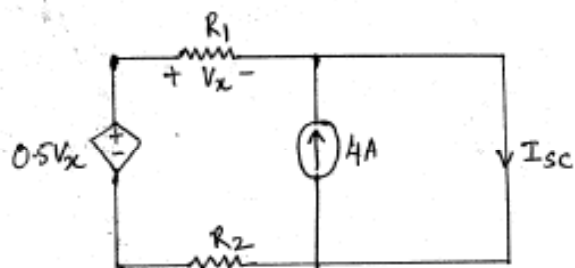
$$0.5V_x = 6I + V_{OC} + 4I \\ I = -4A, V_x = 6I = (-24) \\ -12 = -24 + V_{OC} - 16 \\ V_{OC} = 28V$$



$$0.5V_x = 6I + 4I \\ 0.5(6I) = 10I \\ I = 0A \\ \Rightarrow V_x = 0V$$
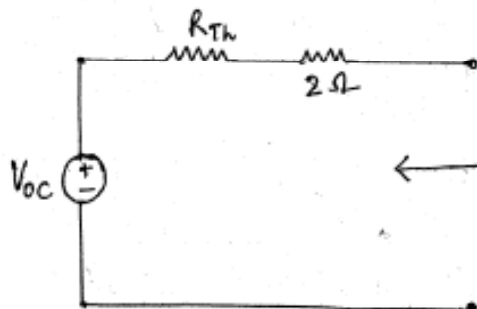
$$I_{SC} = I + 4 = 4A \\ R_{Th} = \frac{V_{OC}}{I_{SC}} = \frac{28}{4} = 7\Omega$$



$$R_{eq} = R_{Th} + 2\Omega = 9\Omega$$

For maximum power transfer  $R_L = R_{eq} = 9\Omega$

- 5.103 Find the value of  $R_L$  for maximum power transfer and the maximum power that can be transferred to  $R_L$  in the circuit of Fig. P5.103.


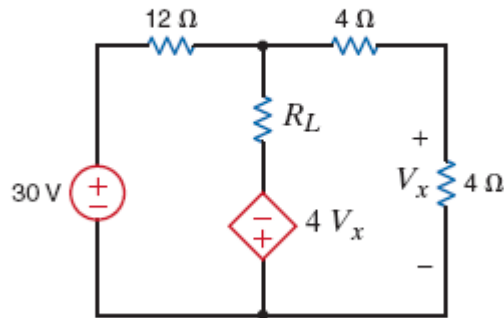


Figure P5.103

**SOLUTION:**

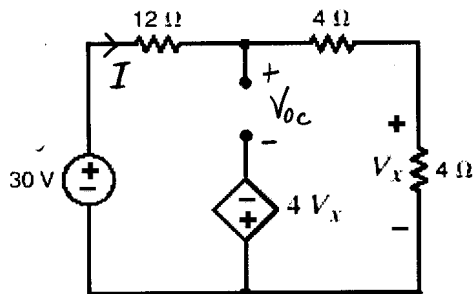


$$V_x = \left( \frac{4}{4 + 4 + 12} \right) (30) = 6V$$

$$I = \frac{30}{12 + 8} = 1.5A$$

KVL around left loop:

$$30 + 4V_x = 12I + V_{oc}$$

$$V_{oc} = 36V$$

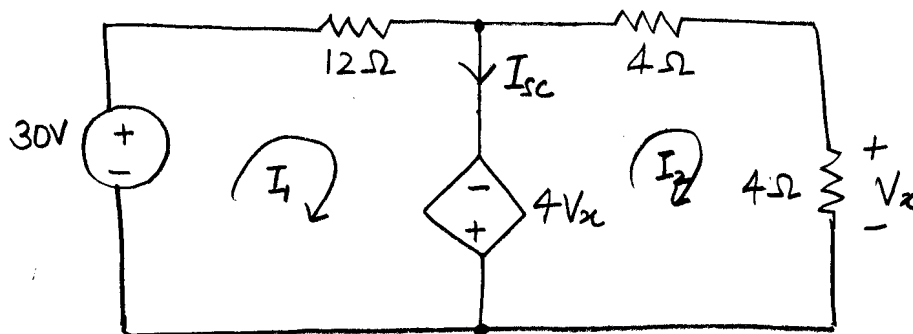

$$I_{sc} = I_1 - I_2$$
$$V_x = 4I_2$$

KVL around left loop:

$$30 + 4V_x = 12I_1$$

$$12I_1 - 16I_2 = 30$$


KVL around outer loop:

$$30 = 12I_1 + 8I_2$$

$$I_1 = 2.5A$$

$$I_2 = 0A$$

$$R_{TH} = \frac{36}{2.5} = 14.4\Omega$$

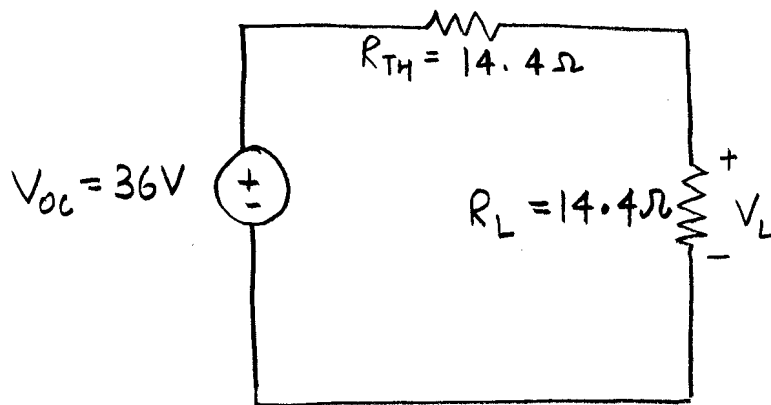

$$V_L = \left( \frac{14.4}{14.4 + 14.4} \right) (36) = 18V$$

$$P_L = \frac{V_L^2}{R_L} = \frac{(18)^2}{14.4} = 22.5W$$

- 5.104 Find the maximum power that can be transferred to  $R_L$  in the network of Fig. P5.104.


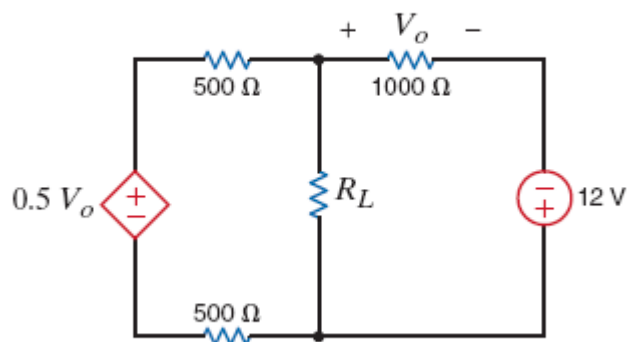


Figure P5.104

**SOLUTION:**

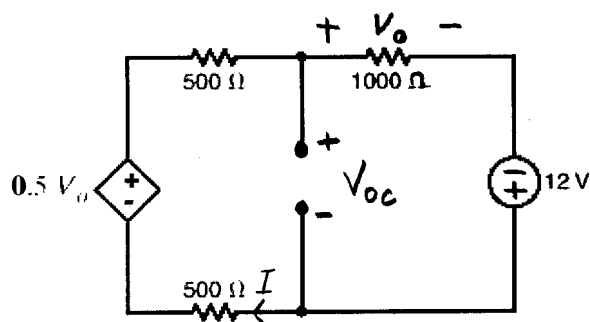


$$V_o = 1000 I$$

$$0.5 V_o + 12 = 500 I + 500 I + V_o$$

$$I = 8 \text{ mA}$$

$$V_{oc} + 12 = 1000 I$$

$$V_{oc} = -4 \text{ V}$$

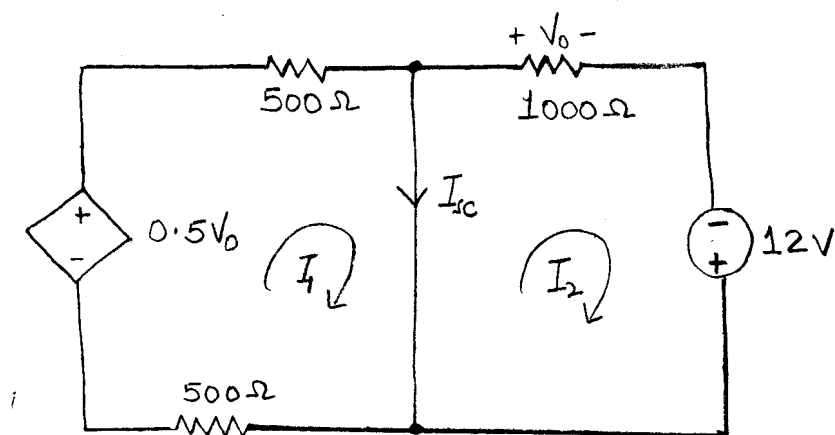

$$I_{sc} = I_1 - I_2$$

KVL around the left loop:

$$0.5V_0 = 500I_1 + 500I_1$$

$$V_0 = 2000I_1$$

KVL right loop:  $V_0 = 12V$


$$KVL \text{ right loop: } 12 = 1000I_2$$

$$I_2 = 12mA$$

$$I_1 = \frac{V_0}{2000} = \frac{12}{2000} = 6mA$$

$$I_{sc} = I_1 - I_2 = 6mA - 12mA = -6mA$$
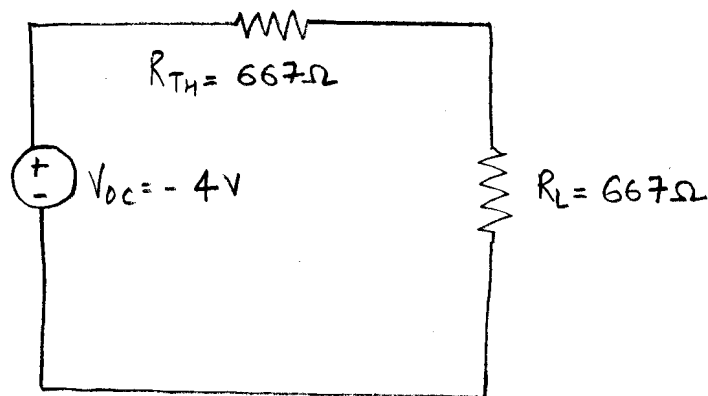
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{-4}{-6mA} = 667\Omega$$



$R_L = R_{TH} = 667\Omega$  for maximum power transfer.

$$V_L = \left( \frac{667}{667 + 667} \right) (-4) = -2V$$

$$P_L = \frac{V_L^2}{R_L} = \frac{(-2)^2}{667} = 6mW$$

- 5.105 Find the value of  $R_L$  for maximum power transfer in the circuit in Fig. P5.105.



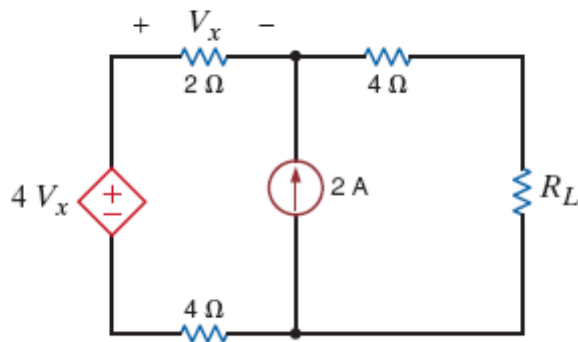


Figure P5.105


**SOLUTION:**

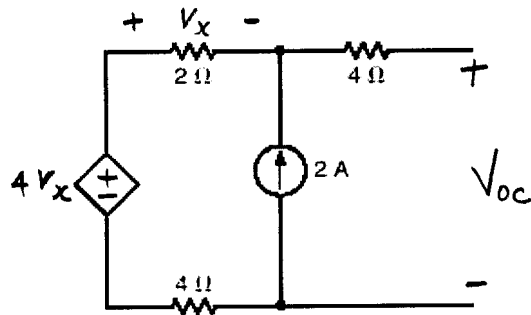
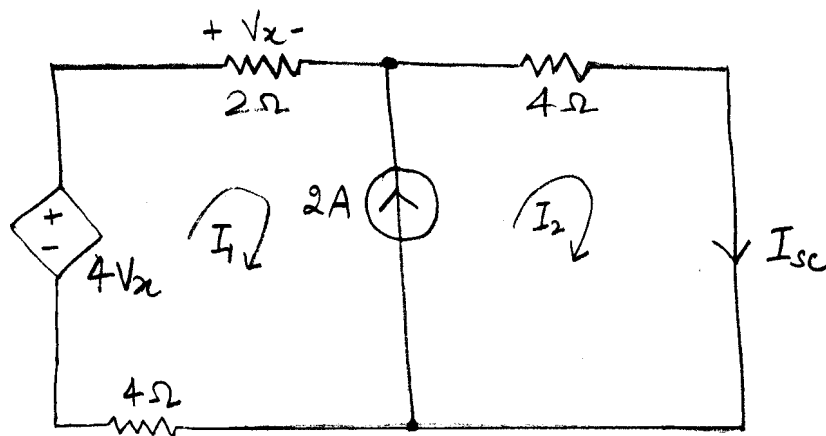
$$\begin{aligned}
 V_x &= -2(2) = -4\text{ V} \\
 V_{oc} &= 4V_x - V_x + 4(2) \\
 V_{oc} &= 4(-4) + 4 + 4(2) \\
 V_{oc} &= -4\text{ V}
 \end{aligned}$$


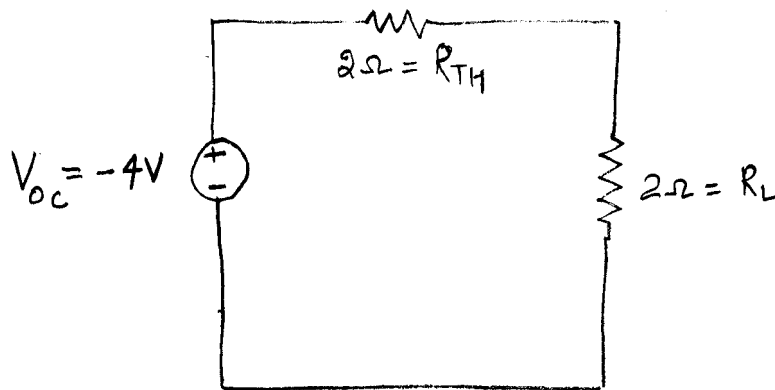
$$\begin{aligned}I_1 + 2 &= I_2 \\-I_1 + I_2 &= 2 \\4V_x &= 4I_1 + V_x + 4I_2 \\V_x &= 2I_1 \\-2I_1 + 4I_2 &= 0 \\I_1 &= -4A \\I_2 &= -2A \\I_{sc} = I_2 &= -2A\end{aligned}$$



$$R_{TH} = \frac{V_{OC}}{I_{sc}} = \frac{-4}{-2} = 2\Omega$$

$$R_L = R_{TH} = 2\Omega \text{ for maximum power transfer.}$$



- 5.106 In the network of Fig. P5.106, find the value of  $R_L$  for maximum power transfer. In addition, calculate the power dissipated in  $R_L$  under these conditions.


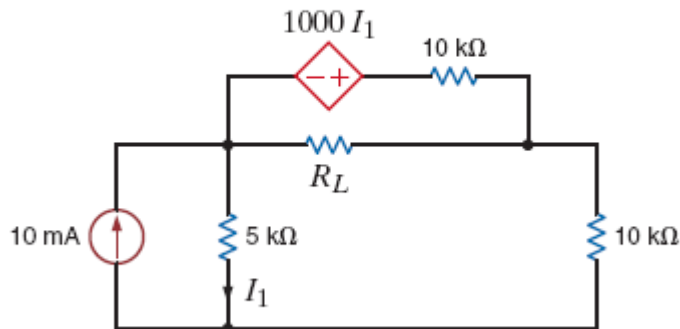


Figure P5.106

**SOLUTION:**

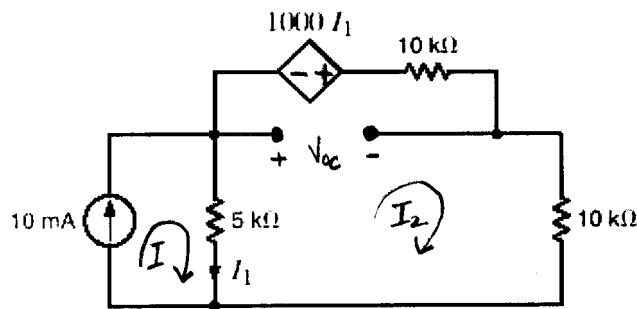

$$\text{KCL: } 10\text{m} = I_1 + I_2$$

$$1000 I_1 - 10\text{k} I_2 - 10\text{k} I_2 + 5\text{k} I_1 = 0$$


$$1000 (10\text{m} - I_2) - 20\text{k} I_2 + 5\text{k} I_1 = 0$$

$$10 - 21000 I_2 + 50 - 5000 I_2 = 0$$

$$I_2 = 2.3\text{mA}$$

$$I_1 = 7.7\text{mA}$$

$$V_{oc} = 15.5\text{V}$$

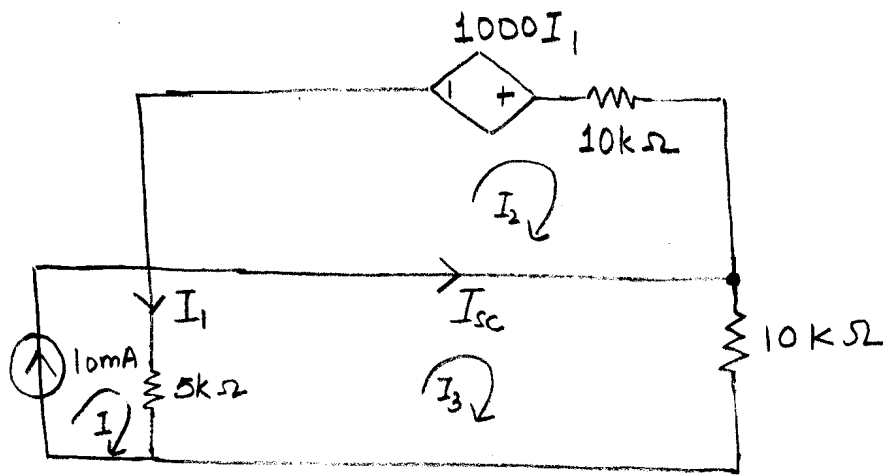

$$10\text{m} = I_1 + I_3$$

$$10\text{k}I_3 - 5\text{k}I_1 = 0$$

$$I_1 = 6.67\text{mA}$$

$$I_3 = 3.33\text{mA}$$


$$1000I_1 = -10\text{k}I_2$$

$$I_2 = 0.67\text{mA}$$

$$I_{sc} = I_3 - I_2$$

$$I_{sc} = 3.33\text{m} - 0.67\text{m} = 2.667\text{mA}$$
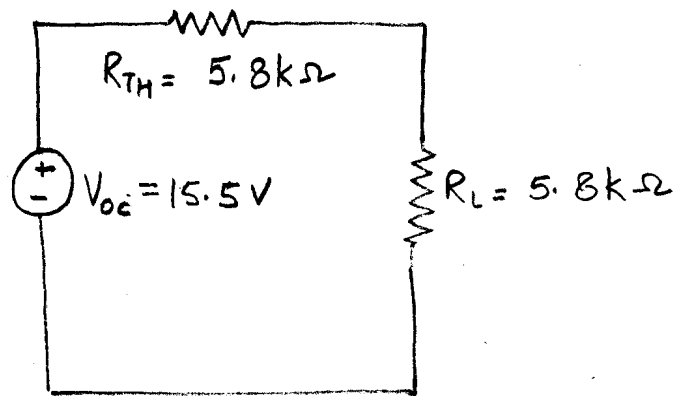
$$R_{TH} = \frac{15.5}{2.667} = 5.811\text{k}\Omega$$



$$R_L = R_{TH} = 5.8\text{ k}\Omega$$
$$\therefore V_L = 7.75\text{ V}$$

$$P_L = 10.33\text{ mW}$$

- 5.107 Calculate the maximum power that can be transferred to  $R_L$  in the circuit in Fig. P5.107.



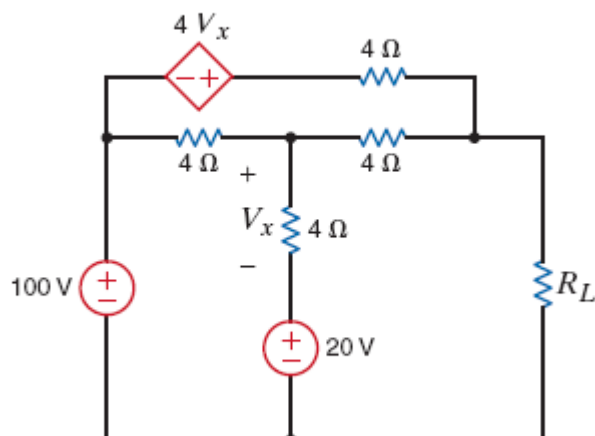


Figure P5.107

**SOLUTION:**

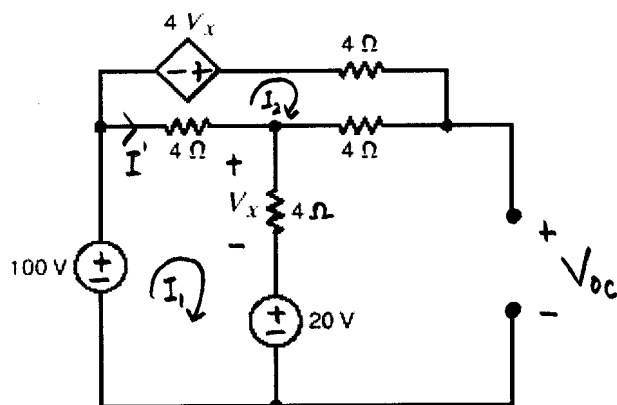

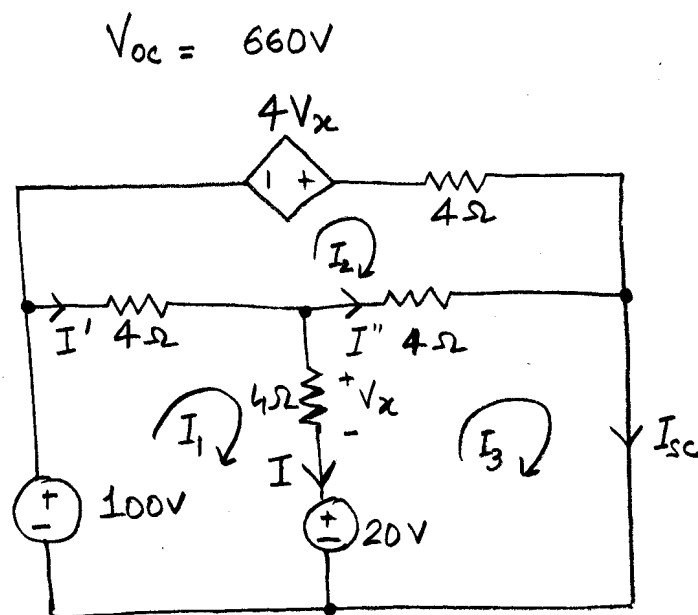
$$\begin{aligned}
 I' &= I_1 - I_2 \\
 100 &= 4I' + 4I_1 + 20 \\
 8I_1 - 4I_2 &= 80 \\
 4V_x &= 4I_2 + 4I_2 - 4I' \\
 V_x &= 4I_1 \\
 -20I_1 + 12I_2 &= 0 \\
 I_1 &= 60\text{ A} \\
 I_2 &= 100\text{ A} \\
 V_{oc} &= 20 + 4I_1 + 4I_2
 \end{aligned}$$



$$\begin{aligned} I_3 &= I_{sc} \\ I' &= I_1 - I_2 \\ I &= I_1 - I_3 \\ V_x &= 4I = 4(I_1 - I_3) \\ 100 + 4V_x &= 4I_2 \\ 16I_1 - 4I_2 - 16I_3 &= -100 \\ 100 &= 4I' + 4I + 20 \\ 8I_1 - 4I_2 - 4I_3 &= 80 \\ 100 &= 4I' + 4I'' \\ I'' &= I_3 - I_2 \\ 4I_1 - 8I_2 + 4I_3 &= 100 \\ I_1 &= 60A \\ I_2 &= 45A \\ I_3 &= 55A \\ I_{sc} &= 55A \\ R_{TH} &= \frac{660}{55} = 12\Omega \end{aligned}$$

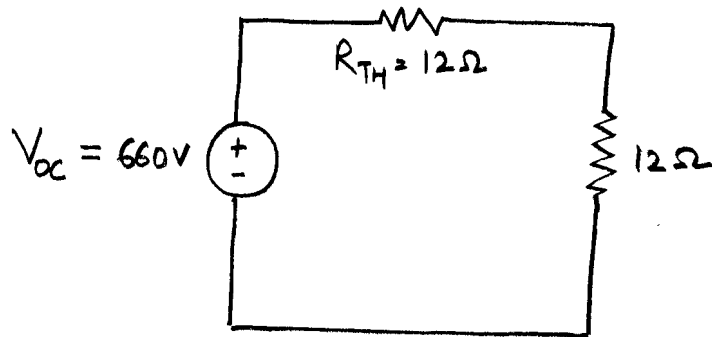
$R_L = R_{TH} = 12\ \Omega$  for maximum power transfer.



$$I_L = \frac{660}{12 + 12} = 27.5A$$


$$P_L = I_L^2 R_L = (27.5)^2 (12) = 9075W$$

**5.108** Find  $R_L$  for maximum power transfer and the maximum power that can be transferred in the network in Fig. P5.108.

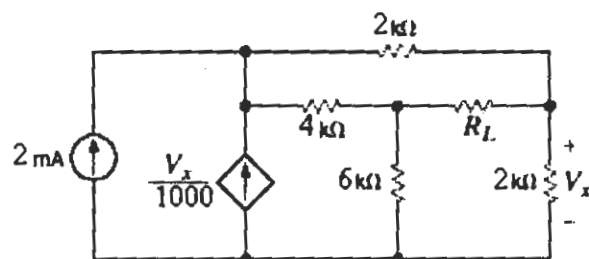


**Figure P5.108**

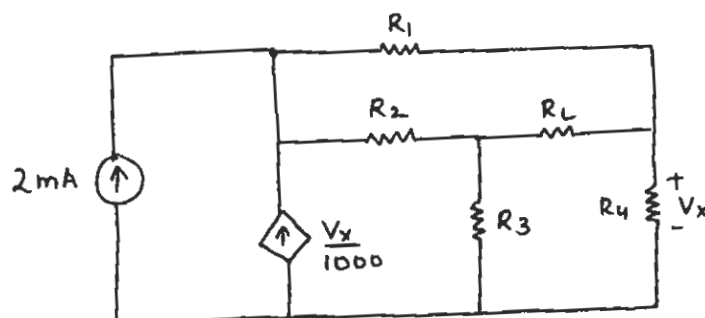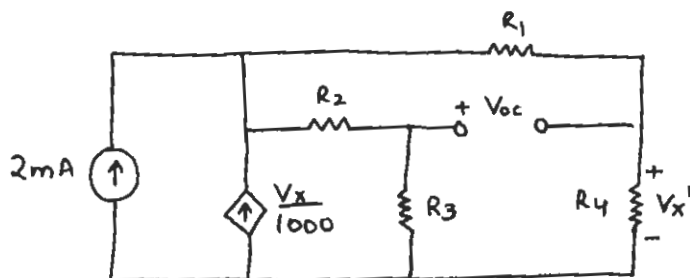Solution: 5.108



$$R_1 = R_4 = 2 \text{ k}\Omega, \quad R_2 = 4 \text{ k}\Omega, \quad R_3 = 6 \text{ k}\Omega$$



$$\text{KCL @ } V_1: -2 \times 10^{-3} - \frac{V_{x'}}{1000} + \frac{V_1}{R_2 + R_3} + \frac{V_1}{R_1 + R_4} = 0$$

$$2V_{x'} = \frac{7}{20} V_1 \quad \text{--- (1)}$$


$$\text{Also } V_{x'} = V_1 \cdot \frac{R_4}{R_1 + R_4} = \frac{V_1}{2}$$

Substituting  $V_{x'} = \frac{V_1}{2}$  in equation (1)

$$V_1 = -13.3 \text{ V} \Rightarrow V_{x'} = -6.67 \text{ V}$$

$$V_2 = V_1 \frac{R_2}{R_2 + R_3} = -8 \text{ V}$$
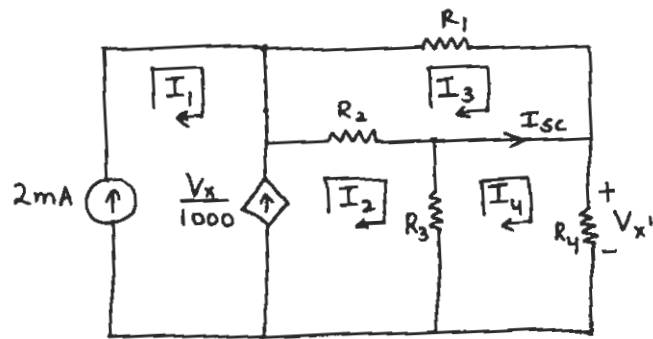
$$V_{oc} = V_2 - V_{x'} = -1.33 \text{ V} \quad \text{--- (2)}$$



$$I_1 = 2 \text{ mA} \quad V_{x''} = I_4 R_4$$

$$I_2 - I_1 = \frac{V_{x''}}{1000}$$

$$I_2 = \frac{I_4 R_4}{1000} + 2 \times 10^{-3}$$

$$\text{KVL @ } I_4: I_4(R_3 + R_4) - I_2 R_3 = 0$$


$$I_4 = -3 \text{ mA}$$

$$\text{KVL @ } I_3: I_3(R_1 + R_2) - I_2 R_2 = 0$$

$$I_3 = -2.67 \text{ mA}$$

$$I_{sc} = I_4 - I_3 = -0.333 \text{ mA}$$
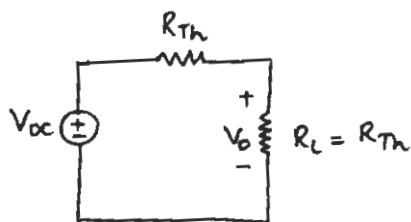
$$R_{Th} = \frac{V_{oc}}{I_{sc}} \Rightarrow R_{Th} = 4.00 \text{ k}\Omega$$



$$P_0 = \frac{V_{oc}^2}{4 R_{Th}}$$

$$P_0 = 111.4 \text{ W}$$



5.109 A cell phone antenna picks up a call. If the antenna and cell phone are modeled as shown in Fig. P5.109,

- Find  $R_{\text{cell}}$  for maximum output power.
- Determine the value of  $P_{\text{out}}$ .
- Determine the corresponding value of  $P_{\text{ant}}$ .
- Find  $V_o/V_{\text{ant}}$ .
- Determine the amount of power lost in  $R_{\text{ant}}$ .
- Calculate the efficiency  $\eta = P_{\text{out}}/P_{\text{ant}}$ .
- Determine the value of  $R_{\text{cell}}$  such that the efficiency is 90%.
- Given the change in (g), what is the new value of  $P_{\text{ant}}$ ?
- Given the change in (g), what is the new value of  $P_{\text{out}}$ ?
- Comment on the results obtained in (i) and (b).


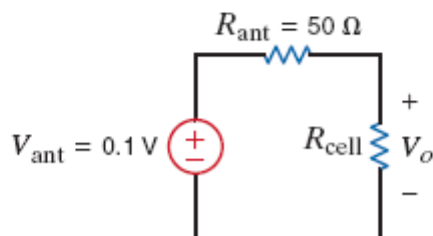


Figure P5.109

**SOLUTION:**

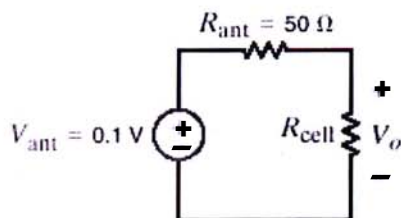

$$a) R_{\text{cell}} = R_{\text{ant}} = 50 \Omega$$

$$b) V_o = \left( \frac{50}{50+50} \right) (0.1) = 50 \text{ mV}$$

$$P_{\text{out}} = \frac{V_o^2}{R_{\text{cell}}} = \frac{(50 \text{ m})^2}{50} = 0.05 \text{ mW}$$

$$c) P_{\text{out}} = 2P_{\text{out}} = 0.1 \text{ mW}$$

$$d) V_o = \left( \frac{R_{cell}}{R_{cell} + R_{ant}} \right) (V_{ant})$$

$$\frac{V_o}{V_{ant}} = \frac{50}{50 + 50} = \frac{1}{2}$$

$$e) P_{R_{ant}} = P_{out} = 0.05 \text{ mW}$$

$$f) \eta = \frac{P_{out}}{P_{ant}} = \frac{0.05 \text{ m}}{0.1 \text{ m}} = 0.5 = 50\%$$

$$g) P_{out} = \frac{V_o^2}{R_{cell}}$$

$$P_{ant} = \frac{V_{ant}^2}{R_{cell} + R_{ant}}$$

$$\left( \frac{R_{cell}}{R_{cell} + R_{ant}} \right)^2 V_{ant}^2$$

$$\eta = \frac{\frac{R_{cell}}{V_{ant}^2}}{\frac{R_{cell} + R_{ant}}{R_{cell} + R_{ant}}} = \frac{R_{cell}}{R_{cell} + R_{ant}}$$

$$0.9 = \frac{R_{cell}}{R_{cell} + 50}$$

$$R_{cell} = 450 \Omega$$

$$h) P_{ant} = \frac{V_{ant}^2}{R_{cell} + R_{ant}} = \frac{(0.1)^2}{450 + 50} = 0.02 \text{ mW}$$

$$i) P_{out} = \eta P_{ant} = 0.9(0.02 \text{ m}) = 0.018 \text{ mW}$$

j) As  $\eta$  increases, more power is transferred. Output power decreases as  $\eta$  moves from 50%.

- 5.110 Some young engineers at the local electrical utility are debating ways to lower operating costs. They know that if they can reduce losses, they can lower operating costs. The question is whether they should design for maximum power transfer or maximum efficiency, where efficiency is defined as the ratio of customer power to power generated. Use the model in Fig. P5.110 to analyze this issue and justify your conclusions. Assume that both the generated voltage and the customer load are constant.


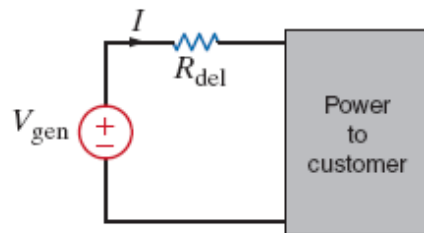


Figure P5.110

**SOLUTION:**

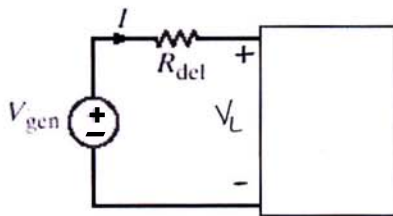

$$P_{\text{load}} = V_L I = (V_{\text{gen}} - IR_{\text{del}}) I$$

$$P_{\text{gen}} = V_{\text{gen}} I$$

$$\eta = \frac{P_{\text{load}}}{P_{\text{gen}}} = \frac{(V_{\text{gen}} - IR_{\text{del}}) I}{V_{\text{gen}} I}$$

$$\eta = \frac{V_{\text{gen}} I - I^2 R_{\text{del}}}{V_{\text{gen}} I}$$

$$\eta = 1 - \frac{IR_{\text{del}}}{V_{\text{gen}}} = 1 - kR_{\text{del}}$$

$$\text{where } k = \frac{I}{V_{\text{gen}}}$$

As  $R_{del} \rightarrow 0$ ,  $\eta \rightarrow 100\%$

If no power is lost in delivery, all of the power generated can be sold.

5.111 Using PSPICE, find  $I_o$  in the network in Fig. P5.111.



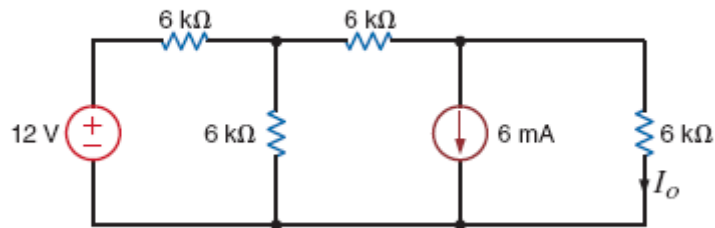



Figure P5.111

**SOLUTION:**

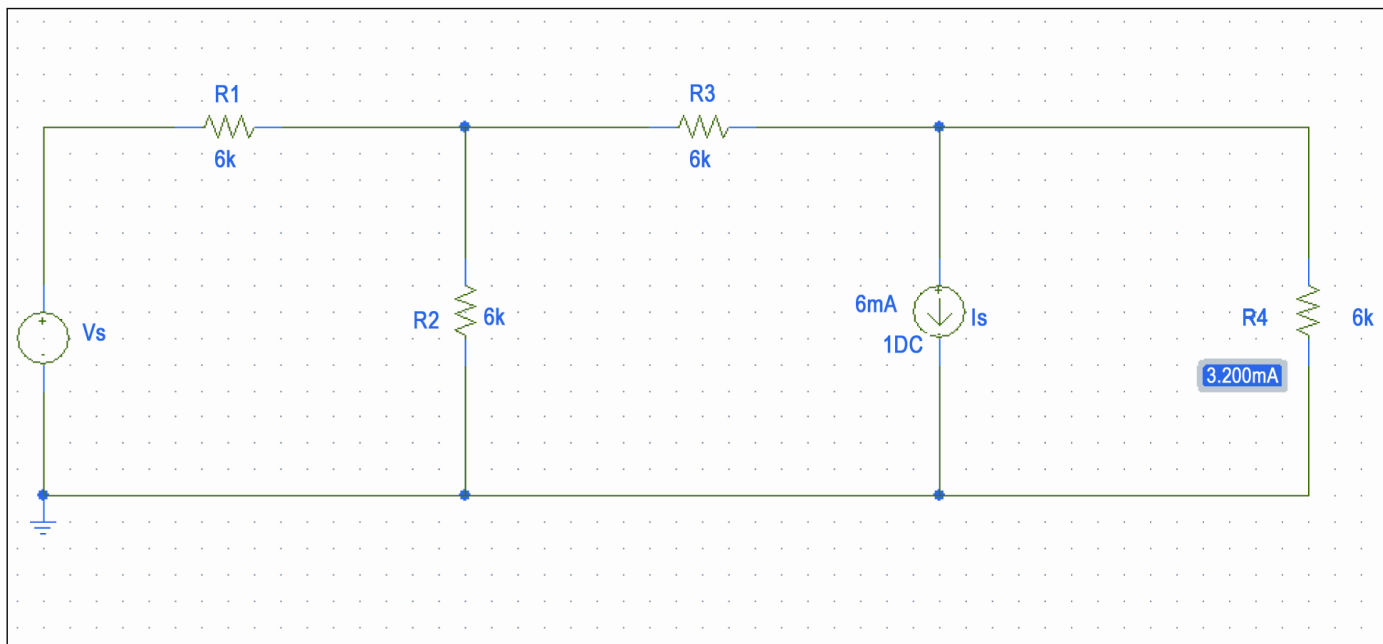

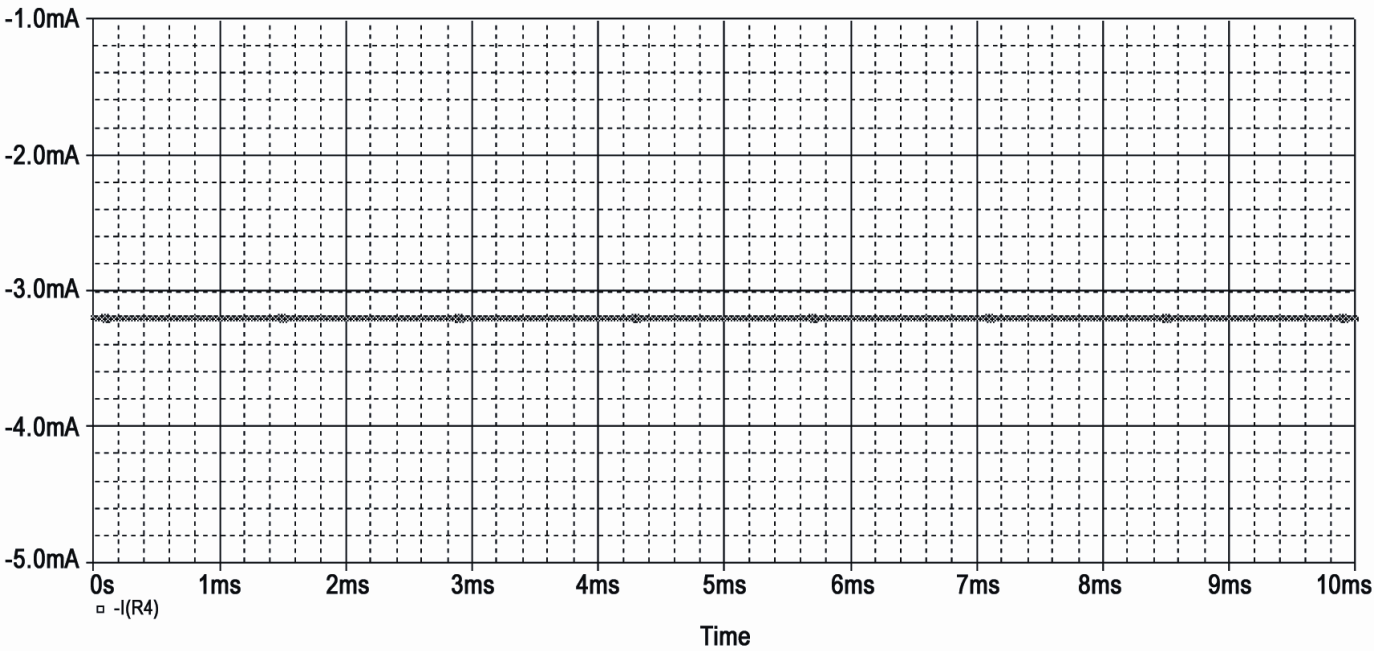


5.112 Find  $V_o$  in the network in Fig. P5.112 using PSPICE.

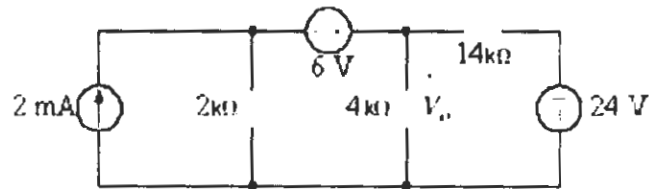

**Figure P5.112**

Solution: 5-112

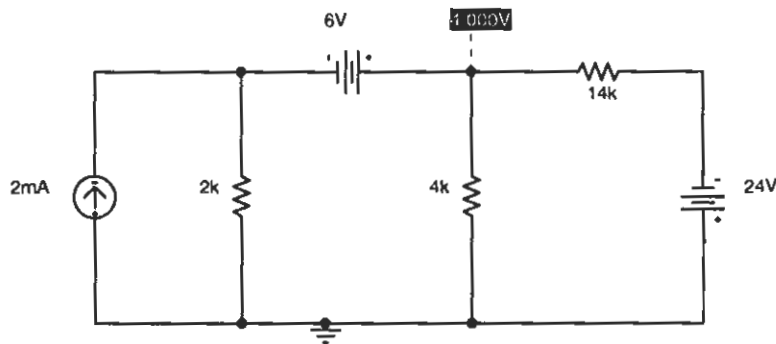

5.113 Using PSPICE, find  $I_o$  in the circuit in Fig. P5.113.



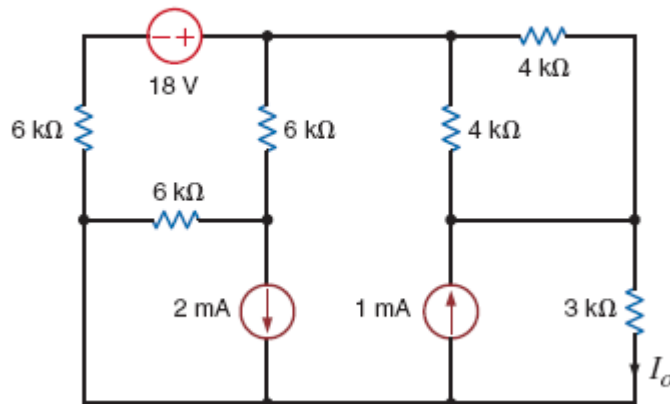


Figure P5.113


**SOLUTION:**

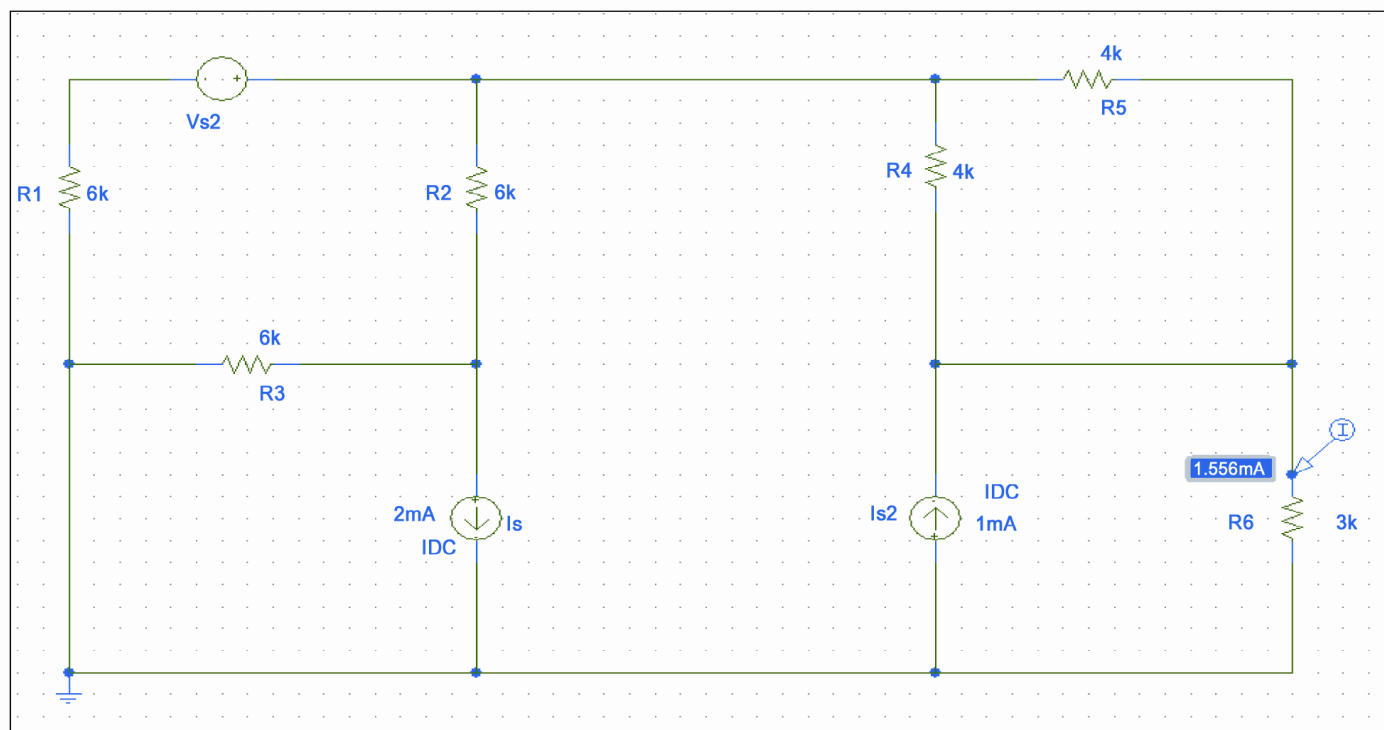

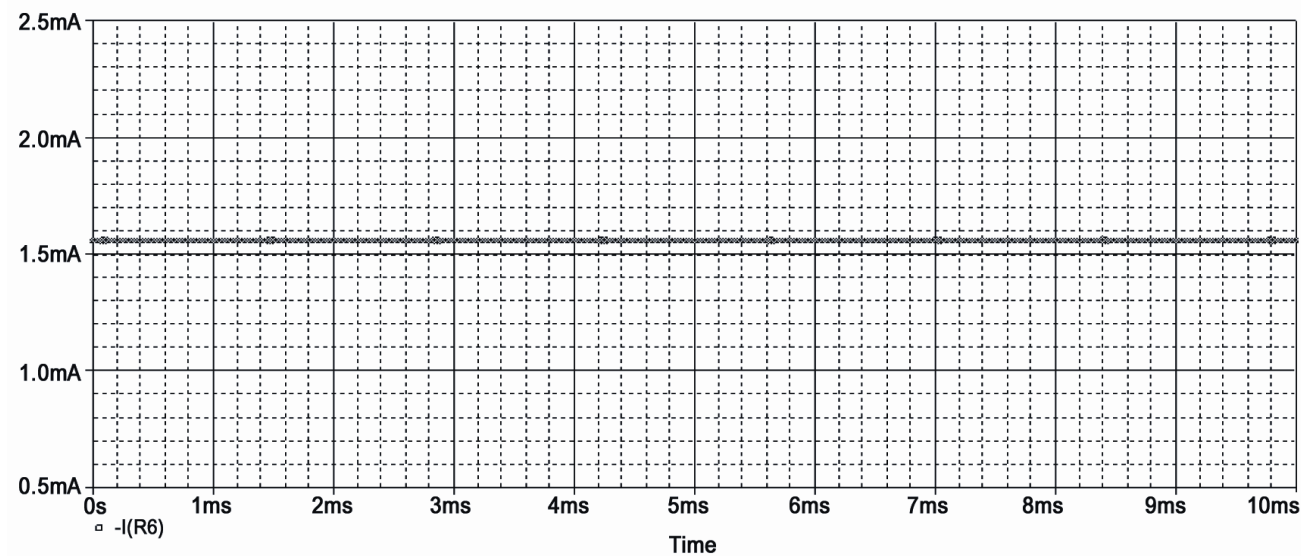




5.114 Find  $V_o$  in the network in Fig. P5.114 using PSPICE.

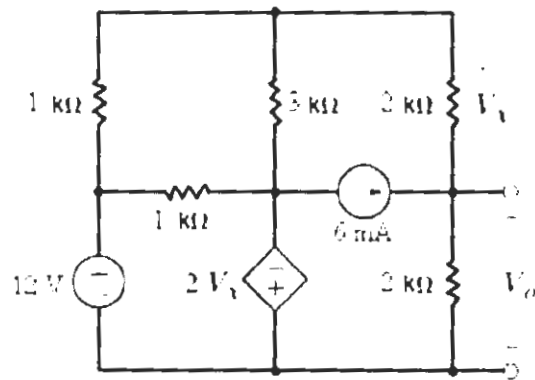

**Figure P5.114**

Solution: 5.114

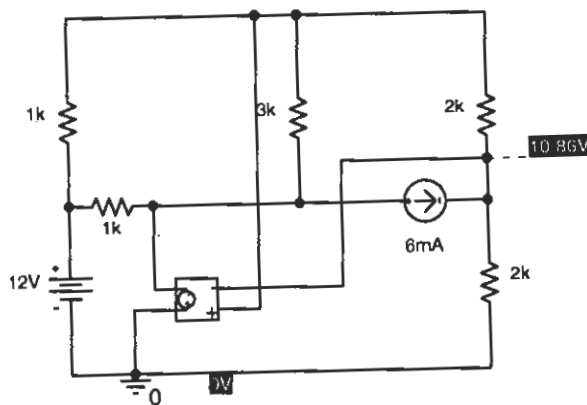

**5FE-1** Determine the maximum power than can be delivered to the load  $R_L$  in the network in Fig. 5PFE-1.

- a. 2 mW
- b. 10 mW
- c. 4 mW
- d. 8 mW


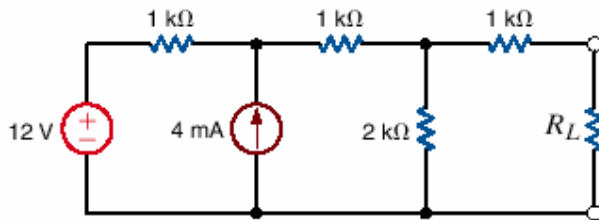


Figure 5PFE-1

**SOLUTION:**

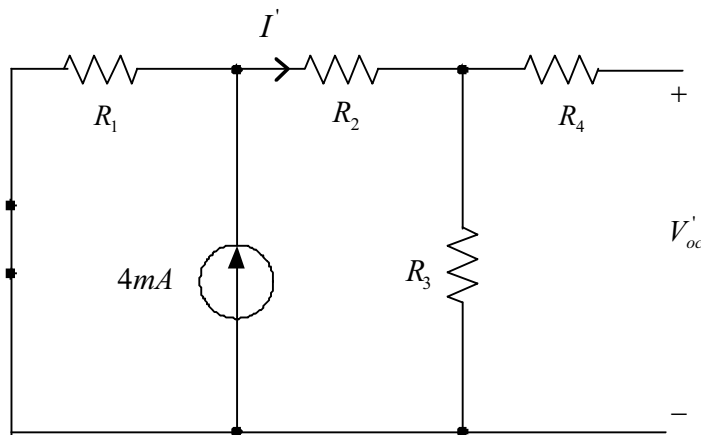

The correct answer is *d*.


Use superposition.

$$I' = \left( \frac{R_1}{R_1 + R_2 + R_3} \right) (4m)$$

$$I' = \left( \frac{1k}{1k + 1k + 2k} \right) (4m) = 1mA$$

$$V'_{oc} = I' R_3 = (1m)(2k)$$

$$V'_{oc} = 2V$$

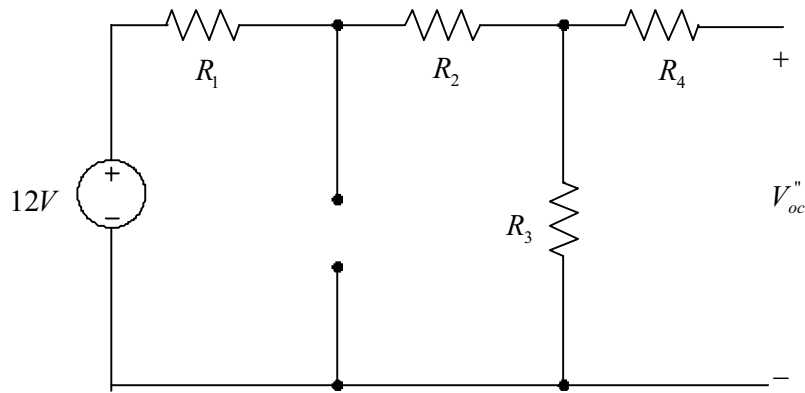


$$V''_{oc} = \left( \frac{R_3}{R_1 + R_2 + R_3} \right) (12)$$

$$V''_{oc} = \left( \frac{2k}{1k + 1k + 2k} \right) (12)$$


$$V''_{oc} = 6V$$
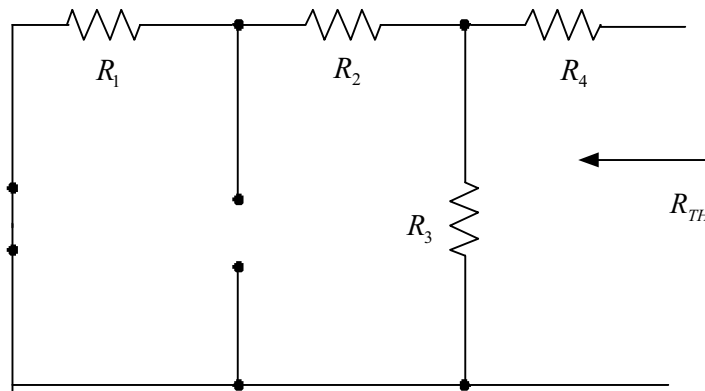
$$V_{oc} = V'_{oc} + V''_{oc} = 2 + 6 = 8V$$



$$R_{TH} = [(R_1 + R_2) \parallel R_3] + R_4$$
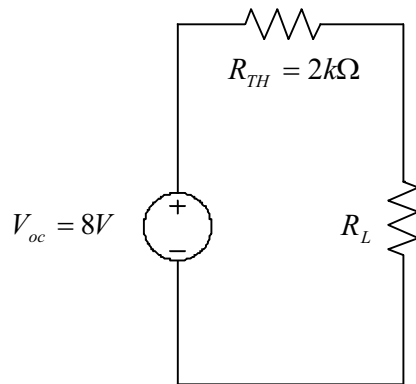
$$R_{TH} = \frac{2k(2k)}{2k + 2k} + 1k = 2k\Omega$$



$$P_{L_{\max}} = I_L^2 R_L$$

$$R_L = R_{TH} \text{ for maximum power.}$$

$$P_{L_{\max}} = \left( \frac{V_{oc}}{2R_{TH}} \right)^2 R_{TH}$$

$$P_{L_{\max}} = \frac{V_{oc}^2}{4R_{TH}} = \frac{8^2}{4(2k)} = 8mW$$

**5FE-2** Find the value of the load  $R_L$  in the network in Fig. 5PFE-2 that will achieve maximum power transfer, and determine that value of the maximum power.

- a. 22.5 mW
- b. 80.4 mW
- c. 64.3 mW
- d. 121.5 mW


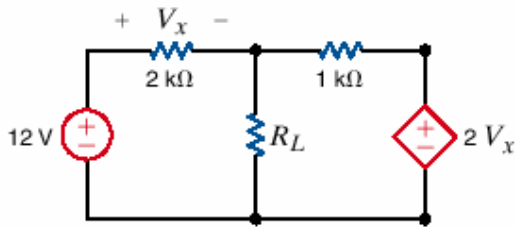


Figure 5PFE-2

**SOLUTION:**

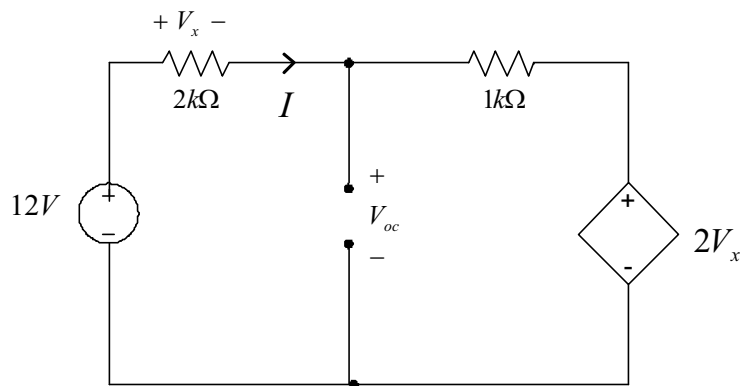

The correct answer is *c*.

$$12 = 2kI + 1kI + 2V_x$$

$$V_x = I(2k)$$


$$12 = 2kI + 1kI + 2(2kI)$$

$$I = \frac{12}{7} \text{ mA}$$

$$12 = 2kI + V_{oc}$$

$$12 = 2k\left(\frac{12}{7} \text{ mA}\right) + V_{oc}$$

$$V_{oc} = 8.57 \text{ V}$$

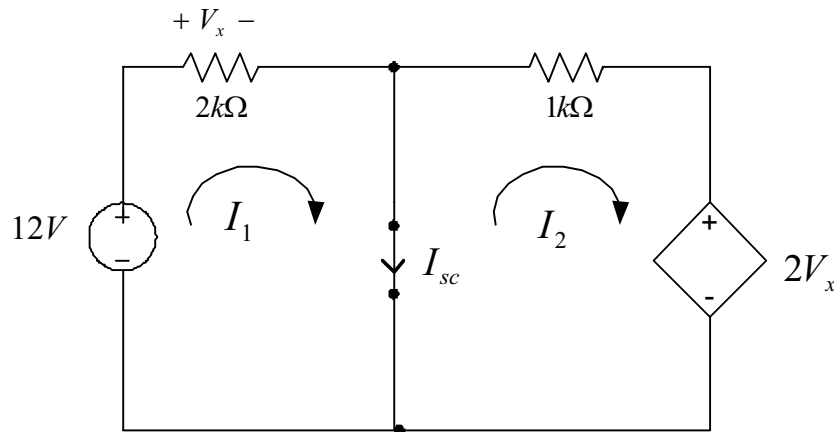

$$I_1 = \left( \frac{12}{2k} \right) = 6mA$$

$$1kI_2 + 2V_x = 0$$

$$1kI_2 + 2(2kI_1) = 0$$


$$I_2 = -24mA$$

$$I_1 = I_2 + I_{sc}$$

$$I_{sc} = 6mA - (-24mA) = 30mA$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{8.57}{30mA} = 285.7\Omega$$
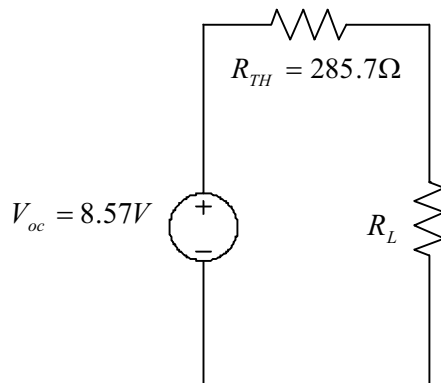
$$R_L = R_{TH} \text{ for maximum power.}$$



$$P_{L_{max}} = \frac{V_{oc}^2}{4R_{TH}} = \frac{(8.57)^2}{4(285.7)} = 64.3mW$$

**5FE-3** Find the value of  $R_L$  in the network in Fig. 5PFE-3 for maximum power transfer to this load.

- a.  $12.92 \, \Omega$
- b.  $8.22 \, \Omega$
- c.  $6.78 \, \Omega$
- d.  $10.53 \, \Omega$


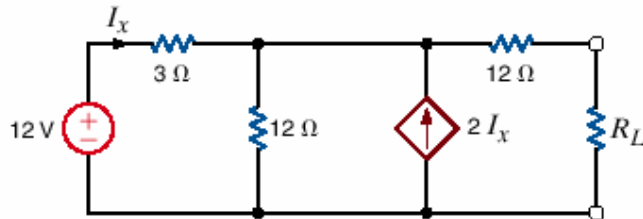


Figure 5PFE-3

**SOLUTION:**

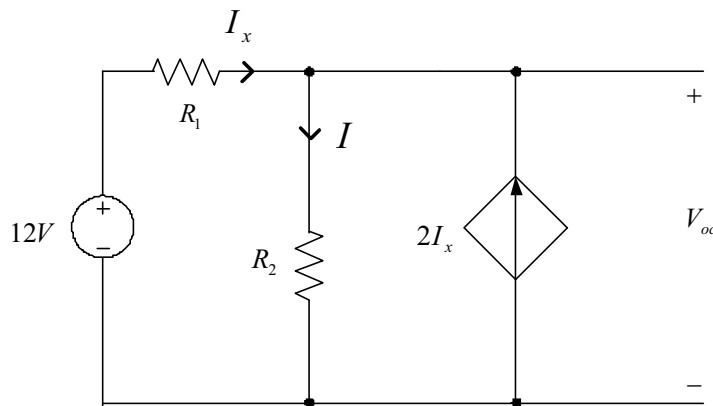

The correct answer is *a*.

$$I = I_x + 2I_x$$

$$I = 3I_x$$


$$12 = 3I_x + 12I$$

$$12 = 3I_x + 12(3I_x)$$

$$I_x = \frac{4}{13} \text{ A}$$
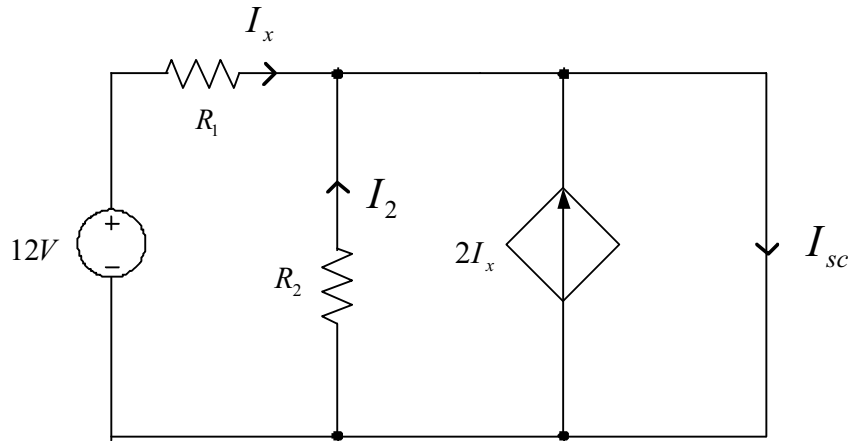
$$V_{oc} = 12I = 12(3I_x) = 12(3)\left(\frac{4}{13}\right) = 11.08 \text{ V}$$





$$I_{sc} = I_x + I_2 + 2I_x = 3I_x + I_2$$

$$I_2 = 0A$$


$$I_{sc} = 3I_x$$

$$12 = 3I_x$$

$$I_x = 4A$$

$$I_{sc} = 3(4) = 12A$$
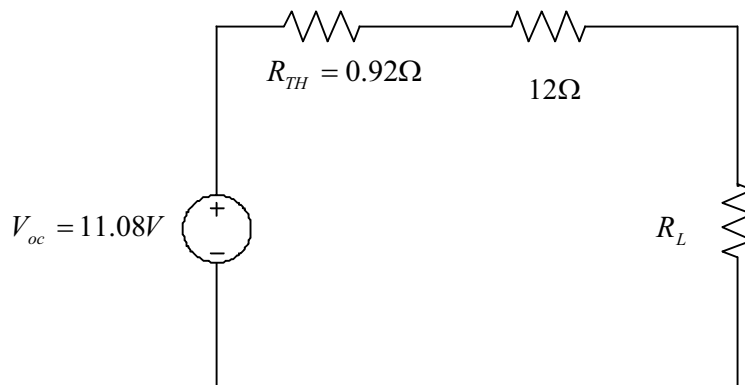
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{11.08}{12} = 0.92\Omega$$



$$R_L = 0.92 + 12 = 12.92\Omega$$

$$R_L = 12.92\Omega \text{ for maximum power transfer.}$$

**5FE-4** What is the current  $I$  in Fig. 5PFE-4?

- a. 8 A
- b. -4 A
- c. 0 A
- d. 4 A


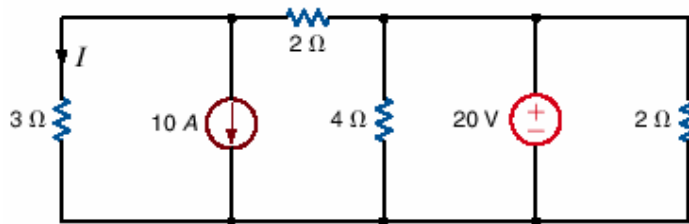


Figure 5PFE-4


**SOLUTION:**

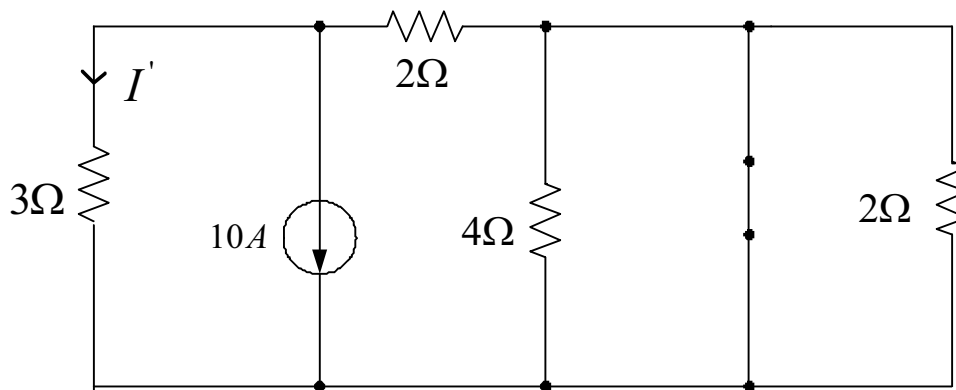

The correct answer is *c*.

Use superposition.
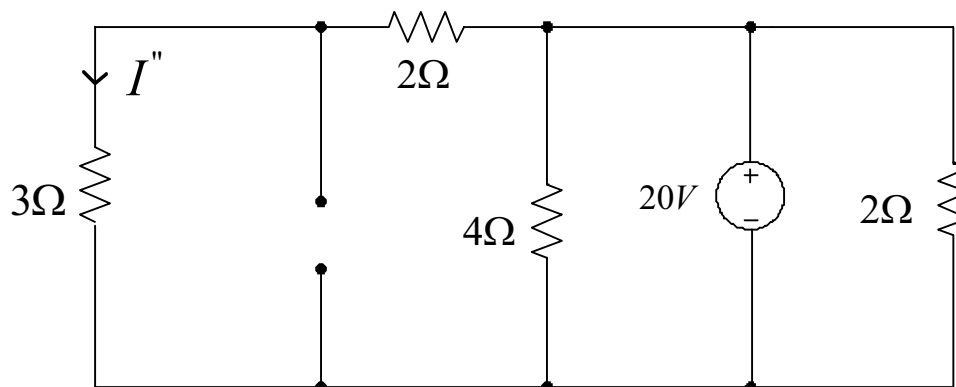
$$I' = \left( \frac{2}{2+3} \right) (-10) = -4A$$



$$I'' = \frac{20}{5} = 4A$$

$$I = I' + I''$$

$$I = -4 + 4$$

$$I = 0A$$

**5FE-5** What is the open circuit voltage  $V_{oc}$  at terminals a and b of the circuit in Fig. 5PFE-5?

- a. 8 V
- b. 12 V
- c. 4 V
- d. 10 V


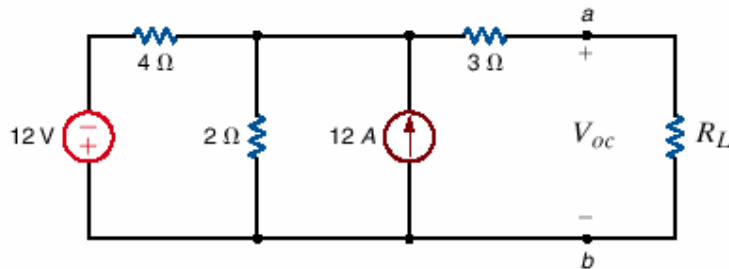


Figure 5PFE-5

**SOLUTION:**


Use superposition.

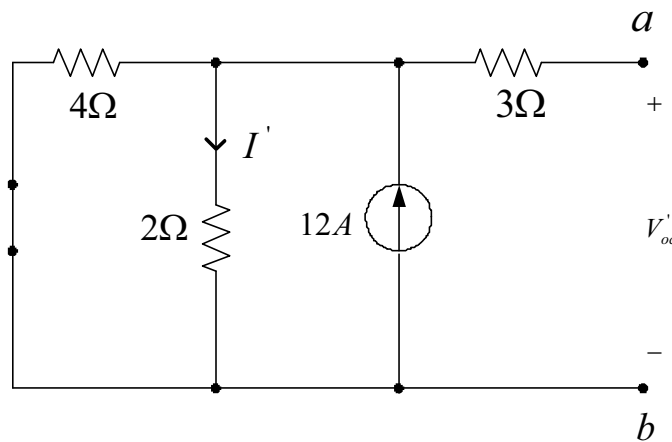

The correct answer is *b*.

$$I' = \left( \frac{4}{2+4} \right) (12) = 8A$$

$$V'_{oc} = I'(2) = 8(2) = 16V$$

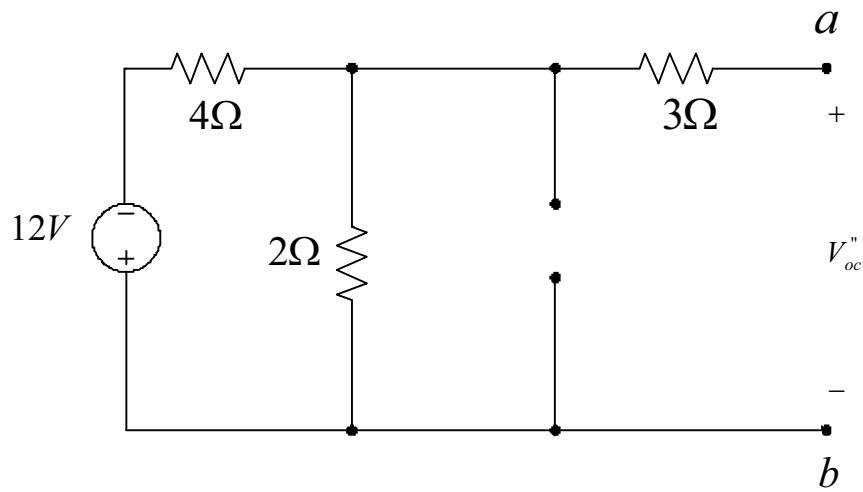

$$V''_{oc} = \left( \frac{2}{2+4} \right) (-12) = -4V$$

$$V_{oc} = 16 - 4 = 12V$$

6.1 A 12- $\mu\text{F}$  capacitor has an accumulated charge of 480  $\mu\text{C}$ .  
Determine the voltage across the capacitor.

---

**SOLUTION:**

$$C = \frac{Q}{V}$$

$$V = \frac{Q}{C}$$

$$V = \frac{480\mu}{12\mu}$$

$$V = 40V$$

6.2 A capacitor has an accumulated charge of  $600 \mu\text{C}$  with 5 V across it. What is the value of capacitance?

---

**SOLUTION:**

$$C = \frac{Q}{V}$$

$$C = \frac{600 \mu}{5}$$

$$C = 120 \mu\text{F}$$

6.3 A 25- $\mu$ F capacitor initially charged to  $-10$  V is charged by a constant current of  $2.5$   $\mu$ A. Find the voltage across the capacitor after  $2\frac{1}{2}$  min.

**SOLUTION:**

$$V(t) = \frac{1}{C} \int_0^t i(t) dt + V(0)$$

$$V(t) = \frac{1}{25\mu} \int_0^{150} 2.5\mu dt - 10$$

$$V(t) = \frac{2.5\mu}{25\mu} [150] - 10$$

$$V(t) = 5\text{ V}$$



- 6.4 A capacitor is charged by a constant current of 2 mA and results in a voltage increase of 12 V in a 10-s interval. What is the value of the capacitance?

---

**SOLUTION:**

$$v(t_2) - v(t_1) = \frac{1}{C} \int_{t_1}^{t_2} i(t) dt$$

$$v(t_2) - v(t_1) = \frac{1}{C} [I(t_2 - t_1)]$$

$$12 = \frac{I}{C} (10)$$

$$C = \frac{2 \times 10^{-3} (10)}{12}$$

$$C = 1.67 \text{ mF}$$

- 6.5 The current in a  $100\text{-}\mu\text{F}$  capacitor is shown in Fig. P6.5. Determine the waveform for the voltage across the capacitor if it is initially uncharged.

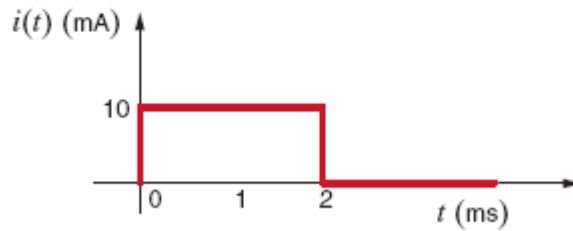


Figure P6.5

**SOLUTION:**

$$t_1 = 2\text{ms}$$

$$V = \frac{1}{C} \int i dt + V_0$$

$$t < 0, \quad i = 0, \quad \text{and} \quad V = 0$$

$$0 \leq t < t_1, \quad i = 10\text{mA}, \quad \text{and}$$

$$V = \frac{1}{100\mu} \int_0^{2\text{m}} 10\text{m} dt$$

$$V = \frac{10\text{m}}{100\mu} \left[ t \right]_0^{2\text{m}} = 100t \text{ V}$$

$$t \geq t_1$$

$$V = \frac{1}{C} \int 0 dt + 100(2\text{m})$$

$$V = 0.2 \text{ V}$$

$$v(t) = \begin{cases} 0 \text{ V} & , t < 0 \\ 100t \text{ V} & , 0 \leq t < t_1 \\ 0.2 \text{ V} & , t \geq t_1 \end{cases}$$

6.6 The voltage across a  $50\text{-}\mu\text{F}$  capacitor is shown in Fig. P6.6. Determine the current waveform.

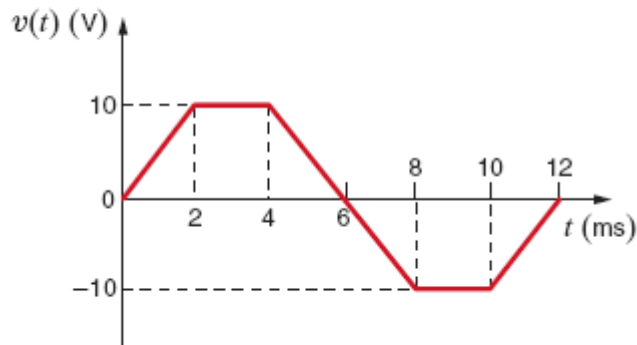


Figure P6.6

**SOLUTION:**

$$i(t) = C \frac{dv}{dt}$$

$$0 \leq t \leq 2 \text{ ms}$$

$$i(t) = 50 \mu [5000]$$

$$i(t) = 250 \text{ mA}$$

$$\text{for } 2 \text{ ms} \leq t \leq 4 \text{ ms}$$

$$i(t) = 0 \text{ A}$$

$$\text{for } 4 \text{ ms} \leq t \leq 8 \text{ ms}$$

$$i(t) = 50 \mu [-5000]$$

$$i(t) = -250 \text{ mA}$$

$$\text{for } 8 \text{ ms} \leq t \leq 10 \text{ ms}$$

$$i(t) = 0 \text{ A}$$

$$\text{for } 10\text{ms} \leq t \leq 12\text{ms}$$
$$i(t) = 50\mu [5000]$$

$$i(t) = 250\text{mA}$$

$$\text{for } i(t) = 250\text{mA}$$

$$\text{for } t > 12\text{ms}$$
$$i(t) = 0\text{A}$$

$$i(t) = \begin{cases} 250 \\ 0 \\ -250 \\ 0 \\ 250 \\ 0 \end{cases}$$

(in mA)

$$\begin{aligned} 0 &\leq t \leq 2\text{ms} \\ 2\text{ms} &\leq t \leq 4\text{ms} \\ 4\text{ms} &\leq t \leq 8\text{ms} \\ 8\text{ms} &\leq t \leq 10\text{ms} \\ 10\text{ms} &\leq t \leq 12\text{ms} \\ t &> 12\text{ms} \end{aligned}$$

- 6.7 Draw the waveform for the current in a  $12\text{-}\mu\text{F}$  capacitor when the capacitor voltage is as described in Fig. P6.7.

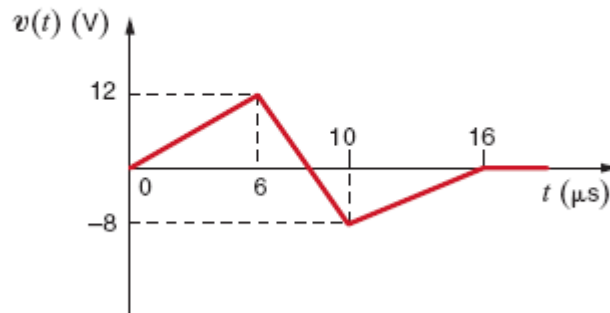


Figure P6.7

**SOLUTION:**

$$i(t) = C \frac{dv}{dt}$$

$$\text{for } 0 \leq t \leq 6\mu\text{s}$$

$$i(t) = 12\mu [2 \times 10^6]$$

$$i(t) = 24\text{A}$$

$$\text{for } 6\mu\text{s} \leq t \leq 10\mu\text{s}$$

$$i(t) = 12\mu [-5 \times 10^6]$$

$$i(t) = -60\text{A}$$

$$\text{for } 10\mu\text{s} \leq t \leq 16\mu\text{s}$$

$$i(t) = 12\mu [1.33 \times 10^6]$$


$$i(t) = 16\text{A}$$

$$\text{for } t > 16\mu\text{s}$$

$$i(t) = 0$$

$$i(t) = \begin{cases} 24 \text{ A} & 0 \leq t \leq 6 \mu\text{s} \\ -60 \text{ A} & 6 \mu\text{s} \leq t \leq 10 \mu\text{s} \\ 16 \text{ A} & 10 \mu\text{s} \leq t \leq 16 \mu\text{s} \\ 0 \text{ A} & t > 16 \mu\text{s} \end{cases}$$

$i(t)$  vs.  $t$

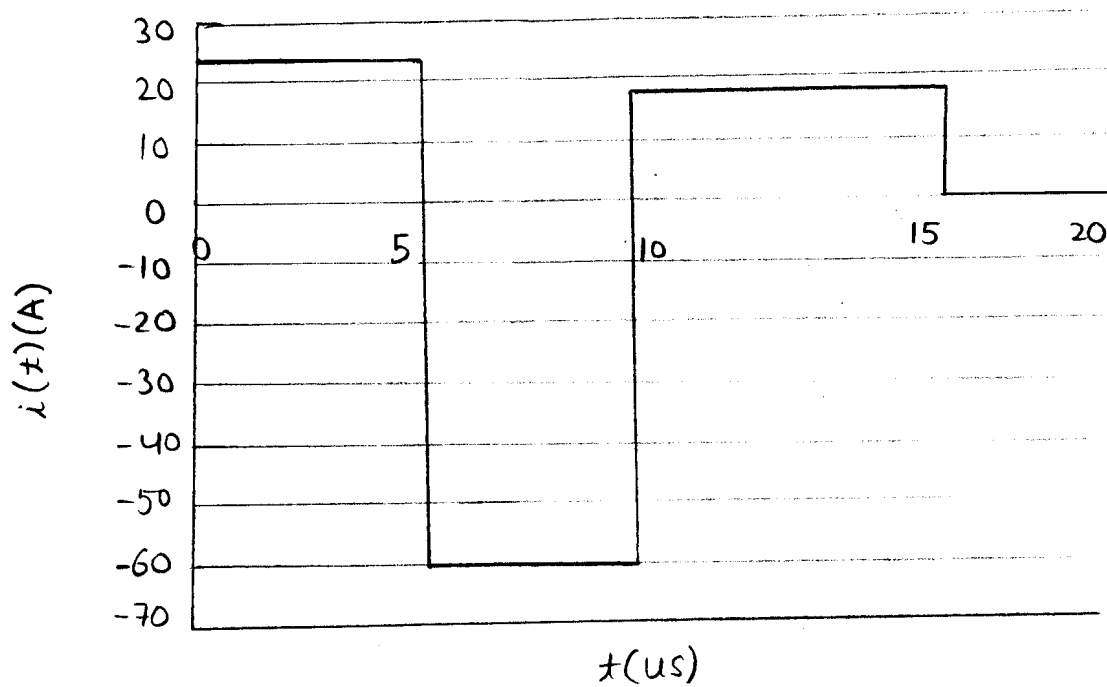

- 6.8 The voltage across a  $25\text{-}\mu\text{F}$  capacitor is shown in Fig. P6.8. Determine the current waveform.

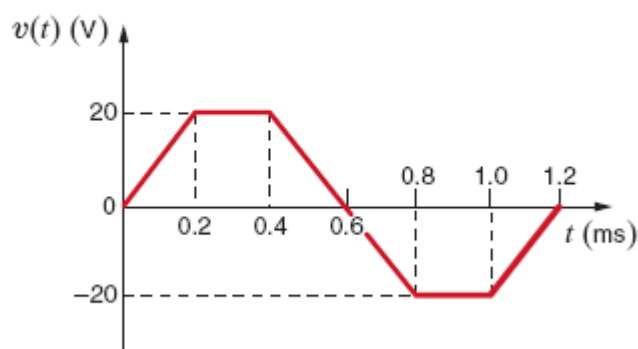


Figure P6.8

**SOLUTION:**

$$t_1 = 0.2 \text{ ms}$$

$$t_2 = 0.4 \text{ ms}$$

$$t_3 = 0.8 \text{ ms}$$

$$t_4 = 1 \text{ ms}$$

$$t_5 = 1.2 \text{ ms}$$

$$i = C \frac{dv}{dt}$$

$$t < 0, \quad v = 0, \quad \text{and} \quad i = 0$$

$$0 \leq t < t_1, \quad v = 10^5 t \text{ V}$$

$$i = 25 \mu [10^5] = 2.5 \text{ A}$$

$$t_1 \leq t < t_2, \quad v = 20 \text{ V}, \quad i = 0$$

$$t_2 \leq t < t_3, \quad v = 60 - 10^5 t \text{ V}$$



$$i = 25 \mu [-10^5] = -2.5 \text{ A}$$


$$t_3 \leq t < t_4, \quad v=0, \quad i=0$$

$$t_4 \leq t < t_5, \quad v = -120 \times 10^5 t$$

$$i = 25 \mu [10^5] = 2.5 \text{ A}$$

$$i(t) = \begin{cases} 0 & t < 0 \\ 2.5 & 0 \leq t < 0.2 \text{ ms} \\ 0 & 0.2 \text{ ms} \leq t < 0.4 \text{ ms} \\ -2.5 & 0.4 \text{ ms} \leq t < 0.8 \text{ ms} \\ 0 & 0.8 \text{ ms} \leq t < 1 \text{ ms} \\ 2.5 & 1 \text{ ms} \leq t < 1.2 \text{ ms} \\ 0 & t \geq 1.2 \text{ ms} \end{cases}$$

6.9 The voltage across a 1-F capacitor is given by the waveform in the Fig. P6.9. Find the waveform for the current in the capacitor.

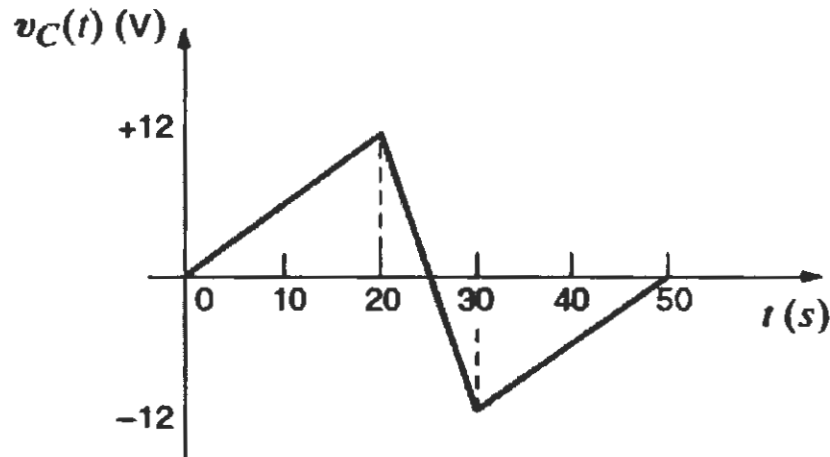

**Figure P6.9**

**Solution:** 6.9

$$i = C \frac{dv}{dt}, \quad t_1 = 20\text{s}, \quad t_2 = 30\text{s}, \quad t_3 = 50\text{s}$$

$$t < 0 \quad v = 0, \quad \frac{dv}{dt} = 0, \quad i = 0$$

$$0 \leq t < t_1 \quad \text{At } t = 20\text{s}, \quad dv = 12\text{V}, \quad dt = 20\text{s}$$

$$\frac{dv}{dt} = \frac{12}{20} = 0.6 \text{ V/s}, \quad i = 0.6 \text{ A}$$

$$t_1 \leq t < t_2 \quad \text{At } t = 30\text{s}, \quad dv = -12 - 12 = -24 \text{ V}, \quad dt = 30 - 20 = 10\text{s}$$

$$\frac{dv}{dt} = \frac{-24}{10} = -2.4 \text{ V/s}, \quad i = -2.4 \text{ A}$$


$$t_2 \leq t \leq t_3 \quad \text{At } t=50\text{ s}, dv = -12\text{ V}, dt = 20\text{ s}$$

$$\frac{dv}{dt} = \frac{-12}{20} = 0.6\text{ V/s}, i = 0.6\text{ A}$$


$$t \geq t_3 \quad v=0, \frac{dv}{dt} = 0, i=0$$

$$i(t) = \begin{cases} 0\text{ A} & t < 0 \\ 0.6\text{ A} & 0 \leq t < 20\text{ s} \\ -2.4\text{ A} & 20\text{ s} \leq t < 30\text{ s} \\ 0.6\text{ A} & 30\text{ s} \leq t < 50\text{ s} \\ 0\text{ A} & t \geq 50\text{ s} \end{cases}$$

Therefore current waveform is

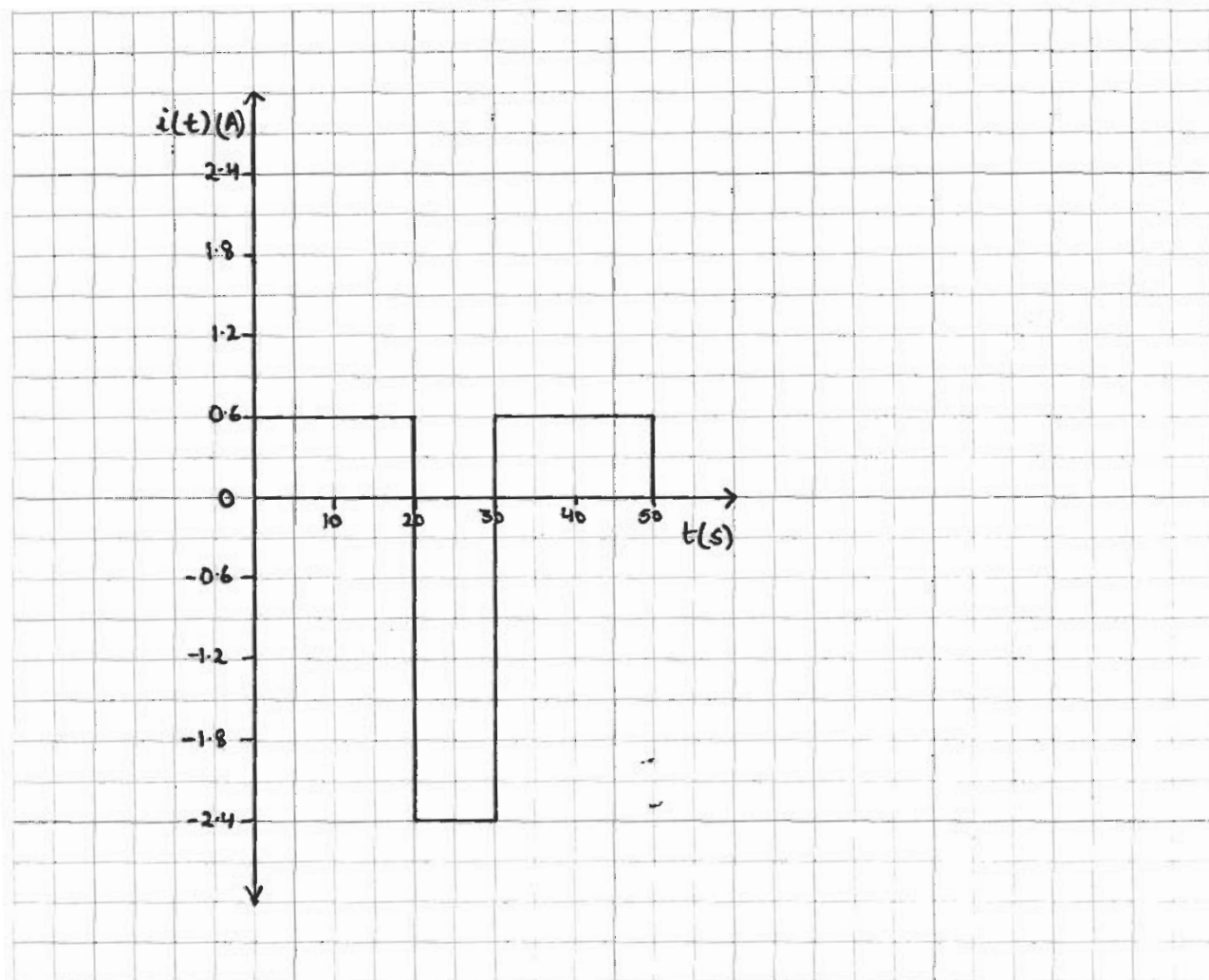

**6.10** The Voltage across a  $1\text{-}\mu\text{F}$  capacitor is given by the waveform in the Fig. P6.10. Compute the current waveform.

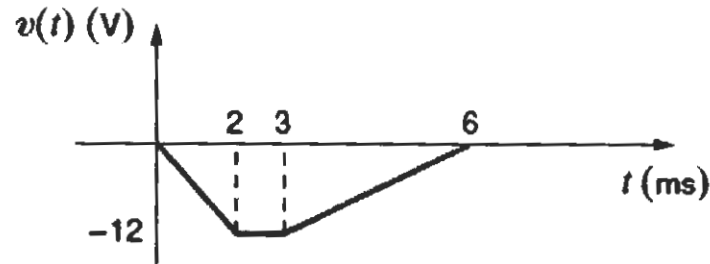

**Figure P6.10**

**Solution:** 6.10

$$t_1 = 2\text{ ms}, t_2 = 3\text{ ms}, t_3 = 6\text{ ms} \quad i = C \frac{dv}{dt}$$

$$t < 0, v = 0, \frac{dv}{dt} = 0, i = 0$$


$$0 \leq t < t_1, \frac{dv}{dt} = \frac{-12}{2} = -6 \text{ V/ms}, i = -6 \text{ mA}$$

$$t_1 \leq t < t_2, \frac{dv}{dt} = 0, i = 0 \text{ mA}$$

$$t_2 \leq t < t_3, \frac{dv}{dt} = \frac{12}{3} = 4 \text{ V/ms}, i = 4 \text{ mA}$$

$$t \geq t_3, \frac{dv}{dt} = 0, i = 0$$
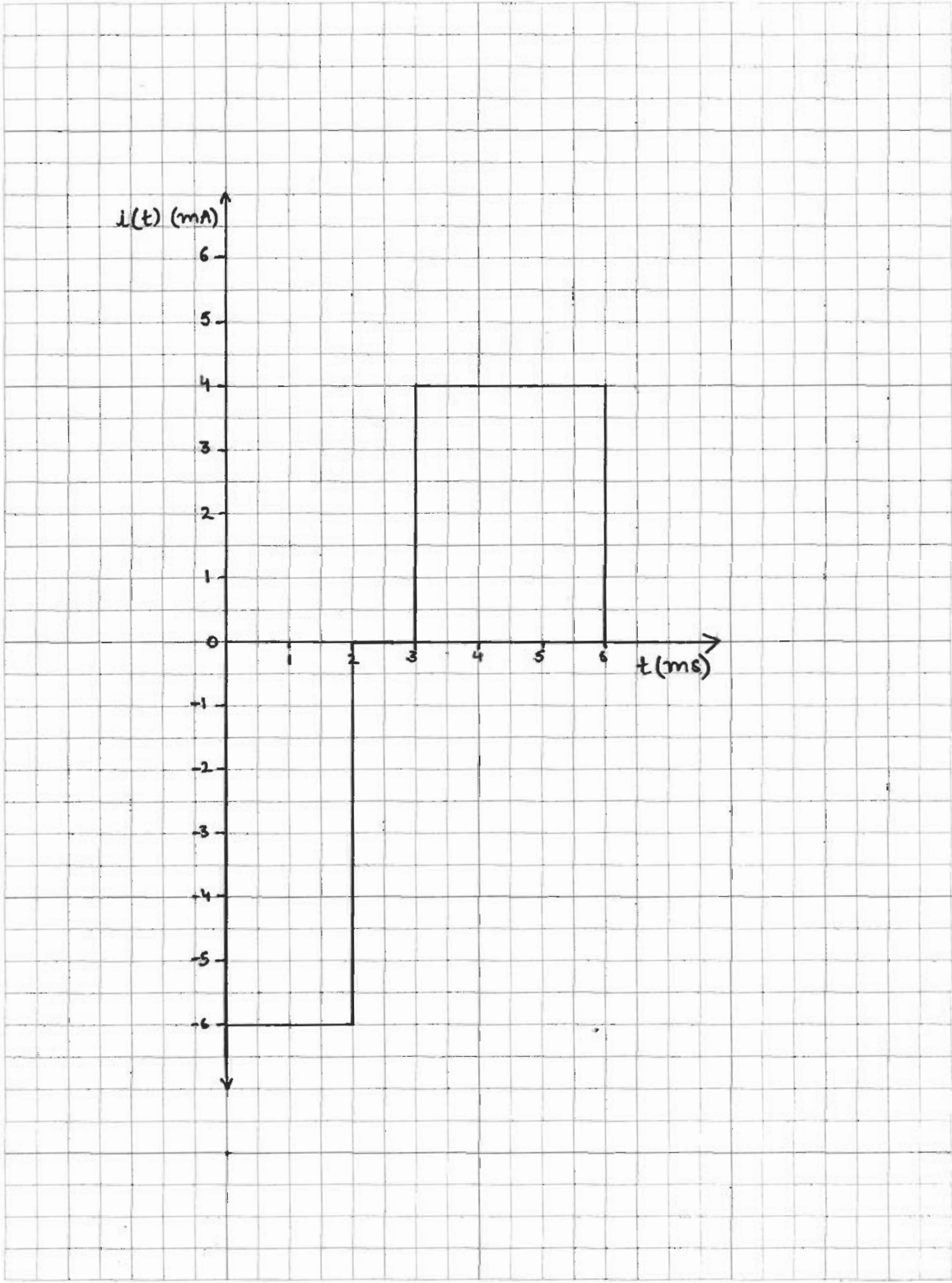
$$\therefore i(t) = \begin{cases} 0 \text{ mA} & t < 0 \text{ ms} \\ -6 \text{ mA} & 0 \text{ ms} \leq t < 2 \text{ ms} \\ 0 \text{ mA} & 2 \text{ ms} \leq t < 3 \text{ ms} \\ 4 \text{ mA} & 3 \text{ ms} \leq t < 6 \text{ ms} \\ 0 \text{ mA} & t \geq 6 \text{ ms} \end{cases}$$



- 6.11 Draw the waveform for the current in a  $24\text{-}\mu\text{F}$  capacitor when the capacitor voltage is as described in Fig. P6.11.

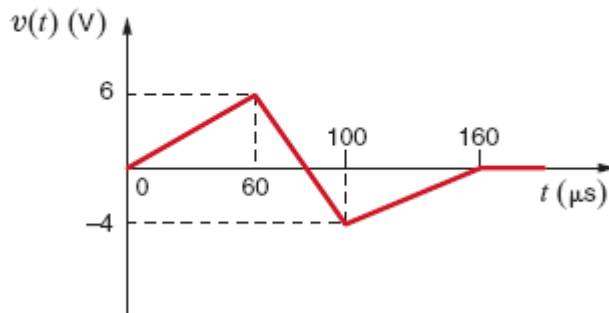


Figure P6.11

**SOLUTION:**

$$t < 0, \quad v = 0, \quad i = 0$$

$$0 \leq t < 60\mu\text{s}, \quad v = 10^5 t \text{ V}$$

$$i = C \frac{dv}{dt}$$

$$i = (24\mu)(10^5)$$

$$i = 2.4\text{ A}$$

$$60\mu\text{s} \leq t < 100\mu\text{s}, \quad v = 21 - 2.5 \times 10^5 t \text{ V}$$

$$i = (24\mu)(-2.5 \times 10^5)$$

$$i = -6\text{ A}$$

$$100\mu\text{s} \leq t < 160\mu\text{s}, \quad v = \frac{-32}{3} + \frac{10^6}{15} t \text{ V}$$

$$i = 24\mu \left[ \frac{10^6}{15} \right]$$

$$i = 1.6\text{ A}$$

$$t \geq 160 \mu\text{s}, v=0, i=0$$

$$i(t) = \begin{cases} 0 \\ 2.4\text{A} \\ -2.4\text{A} \\ 1.6\text{A} \\ 0 \end{cases}$$

$$t < 0$$

$$0 \leq t < 60 \mu\text{s}$$

$$60 \mu\text{s} \leq t < 100 \mu\text{s}$$

$$100 \mu\text{s} \leq t < 160 \mu\text{s}$$

$$t \geq 160 \mu\text{s}$$

6.12 The voltage across a  $10\text{-}\mu\text{F}$  capacitor is given by the waveform in Fig. P6.12. Plot the waveform for the capacitor current.

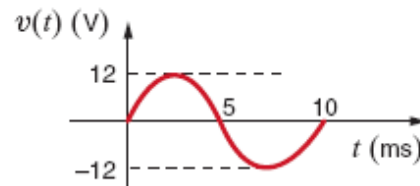


Figure P6.12

**SOLUTION:**

$$i = C \frac{dv}{dt}$$


$$v(t) = 12 \sin \omega t, \quad T = 10 \text{ ms}$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{10 \text{ ms}}$$

$$\omega = 200\pi \text{ rad/s}$$


$$i(t) = (10 \mu)(12)(\omega) \cos \omega t$$

$$i(t) = 75.4 \cos \omega t \text{ mA}$$

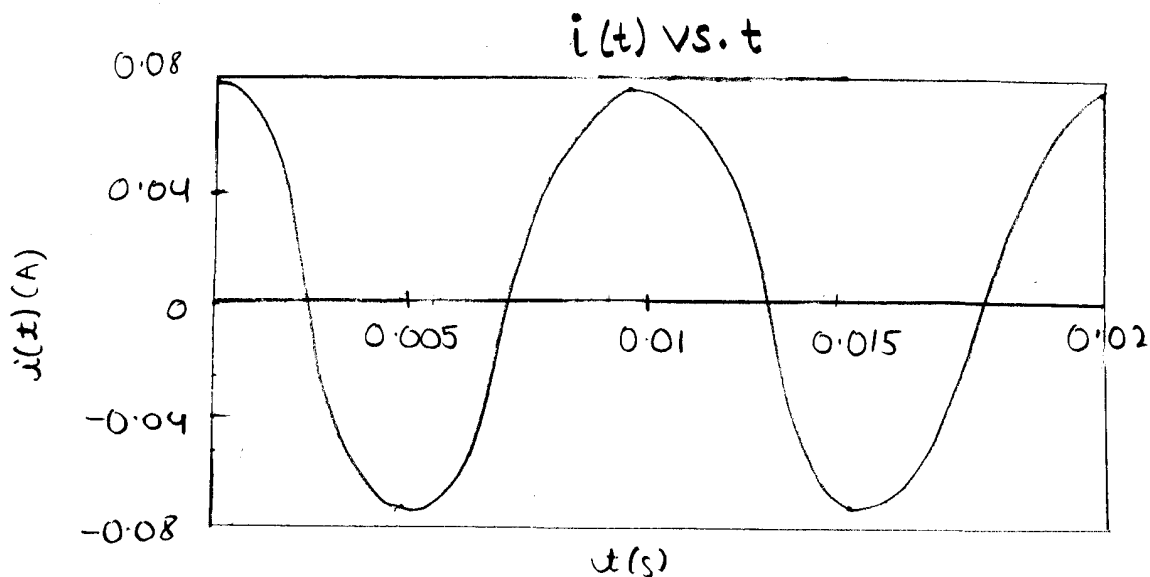




**6.13** The waveform for the current in a  $26\text{-}\mu\text{F}$  capacitor is shown in the Fig. P6.13. Determine the waveform for the capacitor voltage.

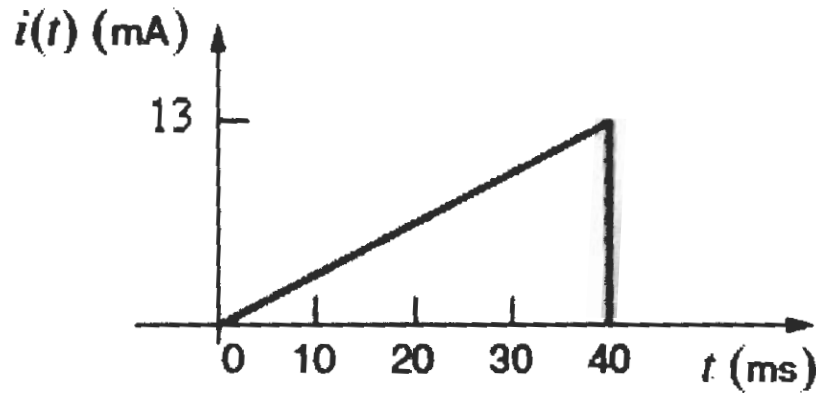


**Figure P6.13**

**Solution:** 6.13

$$\begin{aligned}
 t_1 &= 40 \text{ ms} & V &= \frac{1}{C} \int i dt + V_0 \\
 t < 0, & i(t) = 0, & V &= 0 \\
 0 \leq t < t_1, & i(t) = \frac{13}{40} t = 0.325 t, & V &= 6250 t^2 \text{ V} \\
 t \geq t_1, & i(t) = 0, & V &= 6250 (40 \times 10^{-3})^2 + 0 = 10 \text{ V} \\
 \therefore V(t) &= \begin{cases} 0 \text{ V} & t < 0 \text{ ms} \\ 6250 t^2 \text{ V} & 0 \leq t < 40 \text{ ms} \\ 10 \text{ V} & t \geq 40 \text{ ms} \end{cases}
 \end{aligned}$$

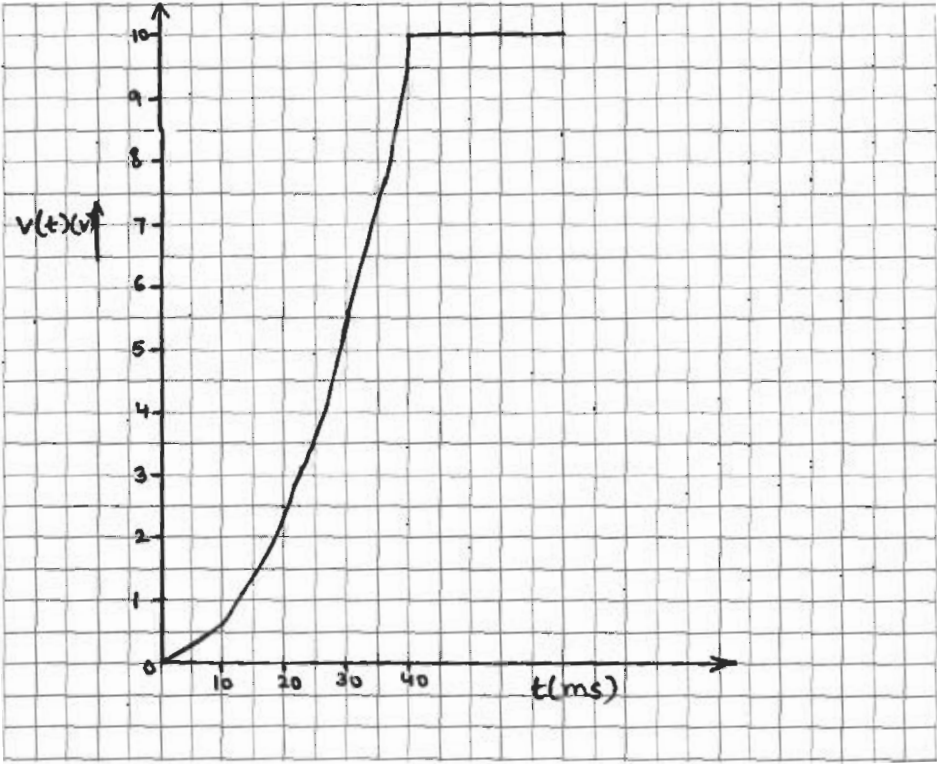

**6.14** The waveform for the current in a 50- $\mu\text{F}$  initially uncharged capacitor is shown in the Fig. P6.14. Determine the waveform for the capacitor's voltage.

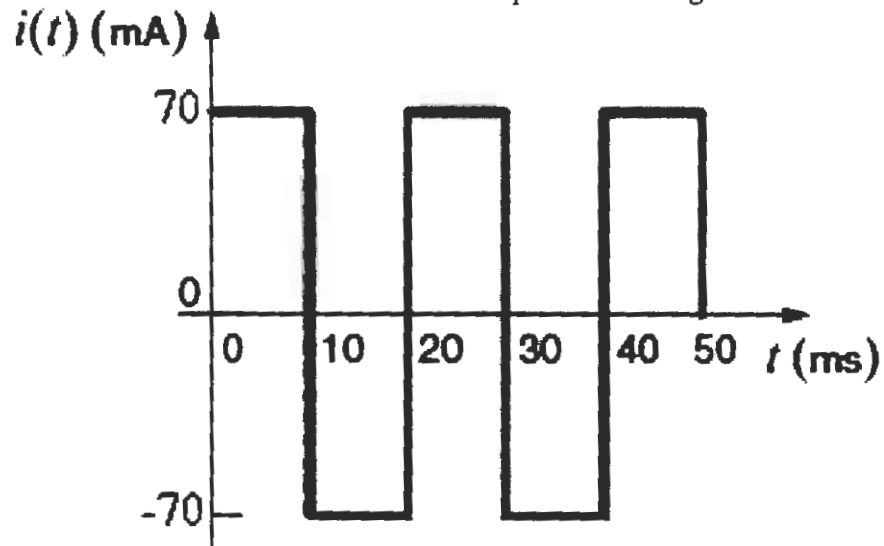

**Figure P6.14**

Solution: 6.14

$$v(t) = \frac{1}{C} \int i \, dt$$

For  $t < 0$ ,  $v(t) = 0$

For  $0 \leq t < 10 \text{ ms}$

$$\begin{aligned} v(t) &= \frac{1}{50 \times 10^{-6}} \int_0^t (70 \times 10^{-3}) \, dt \\ &= 1400t \text{ V} \end{aligned}$$

For  $10 \leq t < 20 \text{ ms}$

$$\begin{aligned} v(t) &= V_0 + \frac{1}{C} \int_{10}^t i(t) dt \\ &= 14 + \frac{1}{50 \times 10^{-6}} (-70 \times 10^{-3}) t - \frac{1}{50 \times 10^{-6}} (-70 \times 10^{-3}) \times 10 \times 10^{-3} \\ &= 28 - 1400t \text{ V} \end{aligned}$$

For  $20 \leq t < 30 \text{ ms}$

$$\begin{aligned} v(t) &= 28 + 1400t - 56 \\ &= -28 + 1400t \text{ V} \end{aligned}$$

For  $30 \leq t < 40 \text{ ms}$

$$\begin{aligned} v(t) &= -28 + 42 + 42 - 1400t \text{ V} \\ &= 56 - 1400t \text{ V} \end{aligned}$$

For  $40 \leq t < 50 \text{ ms}$

$$\begin{aligned} v(t) &= 56 - 56 - 56 + 1400t \\ &= -56 + 1400t \text{ V} \end{aligned}$$

For  $t > 50 \text{ ms}$

$$v(t) = 0 \text{ V}$$

$$v(t) = \begin{cases} 0 \text{ V} & t < 0 \\ 1400t \text{ V} & 0 \leq t < 10 \text{ ms} \\ 28 - 1400t \text{ V} & 10 \leq t < 20 \text{ ms} \\ -28 + 1400t \text{ V} & 20 \leq t < 30 \text{ ms} \\ 56 - 1400t \text{ V} & 30 \leq t < 40 \text{ ms} \\ -56 + 1400t \text{ V} & 40 \leq t < 50 \text{ ms} \\ 0 \text{ V} & t > 50 \text{ ms} \end{cases}$$

- 6.15 The waveform for the current flowing through the  $10\text{-}\mu\text{F}$  capacitor in Fig. P6.15a is shown in Fig. P6.15b. If  $v_c(t=0) = 1\text{ V}$ , determine  $v_c(t)$  at  $t = 1\text{ ms}$ ,  $3\text{ ms}$ ,  $4\text{ ms}$ , and  $5\text{ ms}$ .

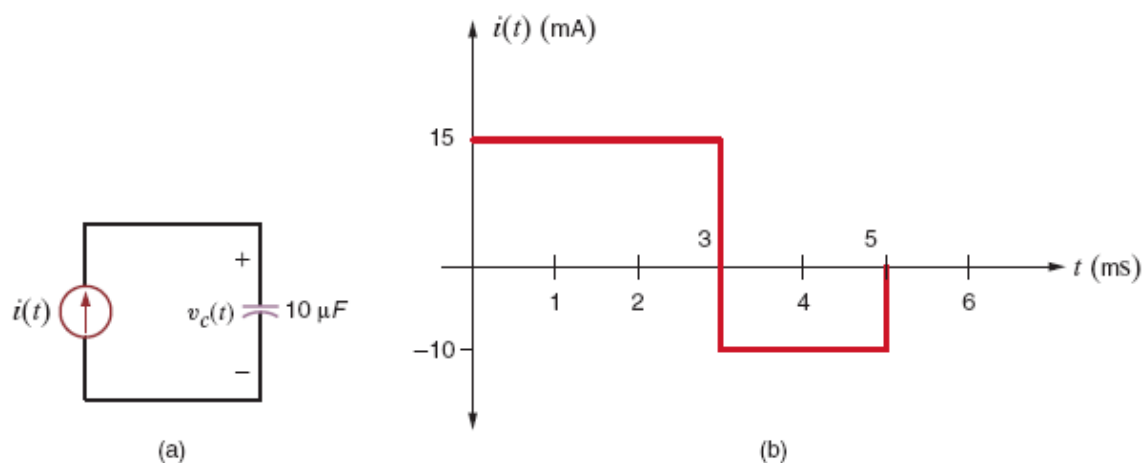


Figure P6.15

**SOLUTION:**

$$V_c(0) = 1\text{ V}$$

$$V_c(t) = V_c(t_0) + \frac{1}{C} \int_{t_0}^t i(t) dt$$

$$V_c(1\text{ ms}) = V_c(0) + \frac{1}{C} \int_0^{1\text{ ms}} (15\text{ m}) dt$$

$$V_c(1\text{ ms}) = 1 + \frac{1}{10\mu} \int_0^{1\text{ ms}} (15\text{ m}) dt$$

$$V_c(1\text{ ms}) = 1 + 100 \times 10^3 (15 \times 10^{-3}) [t]_0^{1\text{ ms}}$$

$$V_c(1\text{ ms}) = 1 + 1500t$$

$$V_c(1\text{ ms}) = 1 + 1500(1\text{ ms})$$

$$V_c(1\text{ ms}) = 2.5\text{ V}$$

$$V_C(3\text{ms}) = V_C(1\text{ms}) + \frac{1}{10\mu} \int_{1\text{m}}^t 15\text{m} dt$$

$$V_C(3\text{ms}) = 2.5 + 100 \times 10^3 (15 \times 10^{-3}) [t]_{1\text{m}}^t$$

$$V_C(3\text{ms}) = 2.5 + 1500 [t - 1\text{m}]$$

$$V_C(3\text{ms}) = 2.5 + 1500 [3\text{m} - 1\text{m}]$$

$$V_C(3\text{ms}) = 5.5 \text{ V}$$

$$V_C(4\text{ms}) = V_C(3\text{m}) + \frac{1}{10\mu} \int_{3\text{m}}^t -10\text{m} dt$$

$$V_C(4\text{ms}) = 5.5 + 100 \times 10^3 (-10 \times 10^{-3}) [t]_{3\text{m}}^t$$

$$V_C(4\text{ms}) = 5.5 - 1000 [t - 3\text{m}]$$

$$V_C(4\text{ms}) = 5.5 - 1000 [4\text{m} - 3\text{m}]$$

$$V_C(4\text{ms}) = 4.5 \text{ V}$$

$$V_C(5\text{ms}) = V_C(4\text{m}) + \frac{1}{10\mu} \int_{4\text{m}}^t -10\text{m} dt$$

$$V_C(5\text{ms}) = 4.5 + 100 \times 10^3 (-10 \times 10^{-3}) [t]_{4\text{m}}^t$$

$$\begin{aligned}V_c(5\text{ms}) &= 4.5 - 1000[t - 4\text{m}] \\&= 4.5 - 1000[5\text{m} - 4\text{m}]\end{aligned}$$

$$V_c(5\text{ms}) = 3.5\text{ V}$$

- 6.16 If  $v_c(t = 2 \text{ s}) = 10 \text{ V}$  in the circuit in Fig. P6.16, find the energy stored in the capacitor and the power supplied by the source at  $t = 6 \text{ s}$ .

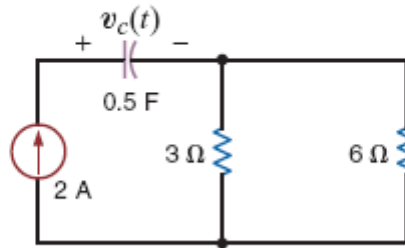
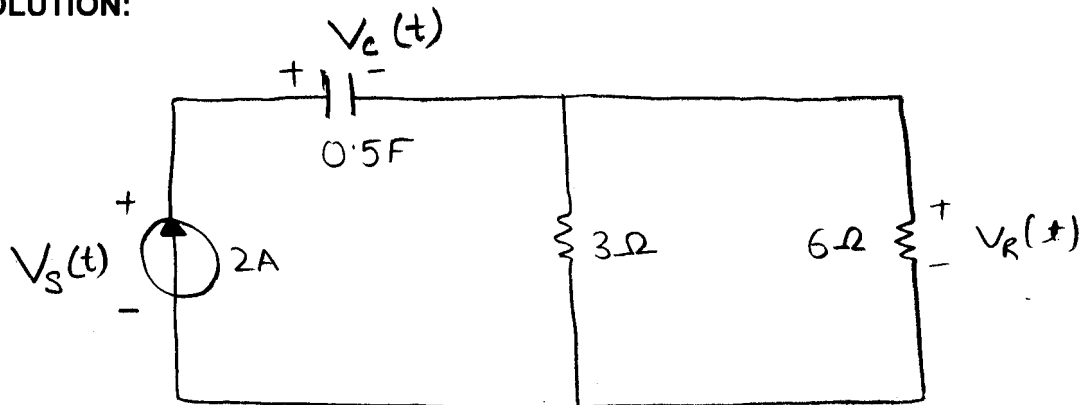


Figure P6.16

**SOLUTION:**

$$V_C(t_2) = \frac{1}{C} \int_{t_1}^{t_2} i_C(t) dt + v_C(2)$$

$$V_C(t_2) = 2 \int_2^6 2 dt + 10$$

$$V_C(t_2) = 2 [2t]_2^6 + 10$$

$$V_C(t_2) = 2 [2(6) - 2(2)] + 10$$

$$V_C(t_2) = 26 \text{ V}$$



$$W_C(t_2) = \frac{1}{2} C [v_C(t_2)]^2$$

$$W_C(t_2) = \frac{1}{2} \left( \frac{1}{2} \right) [26]^2$$

$$W_C(t_2) = 169 \text{ J}$$

$$V_R(t_2) = i(t_2) \left[ \frac{3(6)}{3+6} \right] = 2 \left[ \frac{18}{9} \right]$$

$$V_R(t_2) = 4 \text{ V}$$

$$V_S(t_2) = v_C(t_2) + v_R(t_2)$$

$$V_S(t_2) = 26 + 4$$

$$V_S(t_2) = 30 \text{ V}$$

$$P_S(t_2) = V_S(t_2) i_S(t_2)$$

$$P_S(t_2) = 30(2)$$

$$P_S(t_2) = 60 \text{ W}$$

**6.17** The current in an inductor changes from 0 to 50 mA in 2 ms and induces a voltage of 50 mV. What is the value of the inductor?

---

**Solution:** 6.17

$$V = L \frac{di}{dt} \Rightarrow V = L \frac{\Delta i}{\Delta t} \quad \Delta i = 50 \text{ mA}, \Delta t = 2 \text{ ms},$$
$$V = 50 \text{ mV}$$

$$L = V \frac{\Delta t}{\Delta i}$$

$$\boxed{L = 2 \text{ mH}}$$

- 6.18 The current in a 100-mH inductor is  $i(t) = 2 \sin 377t$  A. Find (a) the voltage across the inductor and (b) the expression for the energy stored in the element.

---

**SOLUTION:**

$$\begin{aligned} \text{(a)} \quad v(t) &= L \frac{di(t)}{dt} \\ v(t) &= 0.1(2)(377) \cos 377t \\ v(t) &= 75.4 \cos 377t \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad w(t) &= \frac{1}{2} Li^2(t) \\ w(t) &= \frac{1}{2} (0.1) [2 \sin 377t]^2 \\ w(t) &= 0.2 \sin^2 377t \text{ J} \end{aligned}$$

**6.19** If the current  $i(t) = 2.0t$  A flows through a 4-H inductor, find the energy stored at  $t = 3$ s.

**Solution:** 6.19

$$W(t) = \frac{1}{2} L [i(t)]^2$$

$$W(3) = \frac{1}{2} \times 4 \times [2 \times 3]^2$$

$$= 72 \text{ J}$$

$$W(3) = 72 \text{ J}$$

6.20 The current in a 25-mH inductor is given by the expressions

$$i(t) = 0 \quad t < 0$$

$$i(t) = 10(1 - e^{-t}) \text{ mA} \quad t > 0$$

Find (a) the voltage across the inductor and (b) the expression for the energy stored in it.

**SOLUTION:**

*Assumption:  $i(t) = 10(1 - e^{-t})$*

$$(a) \quad v(t) = L \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} = \begin{cases} 0 & , t < 0 \\ 10e^{-t} & , t > 0 \end{cases}$$

$$v(t) = \begin{cases} 0 & , t < 0 \\ 250e^{-t} \text{ } \mu\text{V} & , t > 0 \end{cases}$$

$$(b) \quad w(t) = \frac{1}{2} L i^2(t)$$

$$w(t) = \begin{cases} 0 \text{ J} & , t < 0 \\ 1.25 (1 - e^{-t})^2 \text{ } \mu\text{J} & , t > 0 \end{cases}$$

**6.21** The current in a 25-mH inductor is given by the expressions

$$i(t) = 0 \quad t < 0$$

$$i(t) = 14(1 - e^{-t}) \text{ mA} \quad t > 0$$

Find

(a) the voltage across the inductor and

(b) the energy stored in it after 1 s.

---

**Solution:** 6-21

$$(a) \quad v = L \frac{di}{dt}$$

$$v = \begin{cases} 0 \text{ V} & t < 0 \\ 350 e^{-t} \text{ } \mu\text{V} & t > 0 \end{cases}$$

$$(b) \quad w(t) = \frac{1}{2} L i^2(t)$$

$$w(1) = 0.979 \text{ } \mu\text{J}$$

6.22 The current in 50-mH inductor is specified as follows.

$$\begin{aligned} i(t) &= 0 & t < 0 \\ i(t) &= 2te^{-4t} \text{ A} & t > 0 \end{aligned}$$

Find (a) the voltage across the inductor, (b) the time at which the current is a maximum, and (c) the time at which the voltage is a minimum.

**SOLUTION:**

$$\begin{aligned} i(t) &= 0 \text{ A} & t < 0 \\ i(t) &= 2te^{-4t} \text{ A} & , t > 0 \end{aligned}$$

$$(a) \quad v_L(t) = L \frac{di(t)}{dt}$$

$$v_L(t) = 50 \text{ m} \left[ 2t(-4)e^{-4t} + e^{-4t}(2) \right]$$

$$v_L(t) = -0.4te^{-4t} + 0.1e^{-4t}$$

$$v_L(t) = 0.1e^{-4t}(1-4t) \text{ V}$$

$$v_L(t) = 0 \text{ V} \quad , t < 0$$

$$v_L(t) = 0.1e^{-4t}(1-4t) \text{ V} \quad , t > 0$$

(b) The time when  $i(t)$  is maximum is found when

$$\frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} = 2e^{-4t} - 8te^{-4t}$$

$$2e^{-4t} - 8te^{-4t} = 0$$

$$8te^{-4t} = 2e^{-4t}$$

$$t = 0.25 \text{ s}$$

$$(c) \quad v_L(t) = 0.1e^{-4t}(1-4t) \text{ V}$$

$$v_L(t) = 0.1e^{-4t} - 0.4te^{-4t}$$

$$\frac{dv_L(t)}{dt} = -4(0.1)e^{-4t} - 0.4(-4)te^{-4t} - 0.4e^{-4t}$$

$$-0.4e^{-4t} + 1.6te^{-4t} - 0.4e^{-4t} = \frac{dv_L(t)}{dt}$$

$$-0.8e^{-4t} + 1.6te^{-4t} = \frac{dv_L(t)}{dt}$$


$$= 0$$

$$0.8e^{-4t} = 1.6te^{-4t}$$

$$\text{or } t = 1/2$$



**6.23** The voltage across a 4-H inductor is given by the waveform shown in the Fig. P6.23. Find the waveform for the current in the inductor.

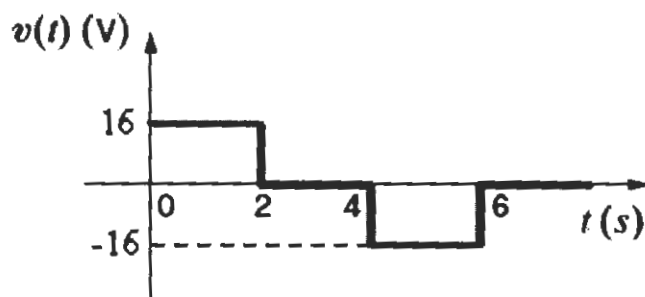

**Figure P6.23**

Solution: 6-23

$$i(t) = \frac{1}{L} \int v(t) dt$$

$$L = 4 \text{ H}$$

For  $t < 0$ ,  $i(t) = 0$  since  $v(t) = 0$

For  $0 \leq t < 2 \text{ s}$

$$i(t) = \frac{1}{4} \int_0^t 16 dt = 4t \text{ A}$$

For  $2 \leq t < 4 \text{ s}$

$$\begin{aligned} i(t) &= i_0 + \frac{1}{4} \int_2^4 v(t) dt \\ &= (4 \times 2) \text{ A} + 0 \quad (\because v(t) = 0 \text{ in the interval}) \\ &= 8 \text{ A} \end{aligned}$$

For  $4 \leq t < 6 \text{ s}$

$$i(t) = 8 + \frac{1}{4} \int_4^t (-16) dt$$

$$= 8 - 4t - (-4) \times 4$$

$$= 24 - 4t \text{ A}$$

For  $t > 6 \text{ s}$

$$i(t) = 0 \text{ A}$$

$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \text{ s} \\ 4t \text{ A} & 0 \leq t < 2 \text{ s} \\ 8 \text{ A} & 2 \leq t < 4 \text{ s} \\ 24 - 4t \text{ A} & 4 \leq t < 6 \text{ s} \\ 0 \text{ A} & t > 6 \text{ s} \end{cases}$$

- 6.24 The voltage across a 4-H inductor is given by the waveform shown in Fig. P6.24. Find the waveform for the current in the inductor.  $v(t) = 0, t < 0$ .

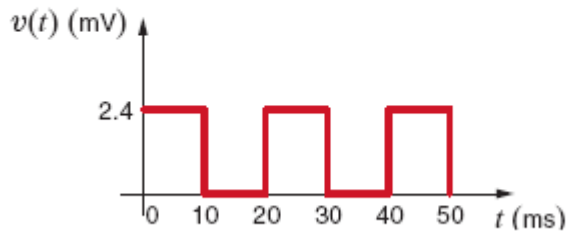


Figure P6.24

**SOLUTION:**

$$i(t) = \frac{1}{L} \int v(t) dt$$

$v(t)$  is constant across the time spans,  
and  $i(t)$  can be written as:

$$i(t) = \frac{V}{L} t + I_0$$

$$\text{for } t < 0, i(t) = 0$$

$$\text{for } 0 \leq t \leq 10 \text{ ms}$$

$$i(t) = \frac{2.4 \text{ mV}}{4} t$$

$$i(t) = 600 t \text{ } \mu\text{A}$$

$$\text{for } 10 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$i(t) = 0 + (600)(10 \text{ m})$$

$$i(t) = 6 \text{ } \mu\text{A}$$

for  $20\text{ms} \leq t \leq 30\text{ms}$

$$i(t) = \frac{2.4\text{m}}{4} t - 6 = 600t - 6 \mu\text{A}$$

for  $30\text{ms} \leq t \leq 40\text{ms}$

$$i(t) = 12 \mu\text{A}$$

for  $40\text{ms} \leq t \leq 50\text{ms}$

$$i(t) = -12 + 600t \mu\text{A}$$

for  $t \geq 50\text{ms}$

$$i(t) = 18 \mu\text{A}$$

$$i(t) = \begin{cases} 0 & t < 0 \\ 600t \mu\text{A} & 0 \leq t \leq 10\text{ms} \\ 6 \mu\text{A} & 10\text{ms} \leq t \leq 20\text{ms} \\ -6 + 600t \mu\text{A} & 20\text{ms} \leq t \leq 30\text{ms} \\ 12 \mu\text{A} & 30\text{ms} \leq t \leq 40\text{ms} \\ -12 + 600t \mu\text{A} & 40\text{ms} \leq t \leq 50\text{ms} \\ 18 \mu\text{A} & t \geq 50\text{ms} \end{cases}$$

- 6.25 The voltage across a 10-mH inductor is shown in Fig. P6.25. Determine the waveform for the inductor current.

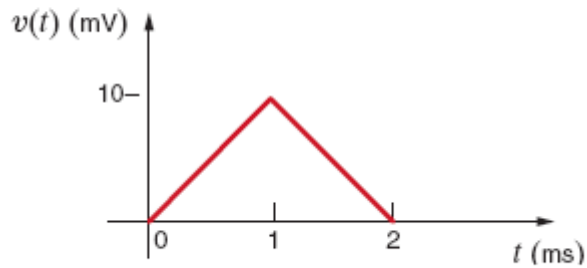


Figure P6.25

**SOLUTION:**

For  $0 \leq t \leq 1 \text{ ms}$

$$v_L(t) = 10t \text{ mV}$$

$$i_L(t) = \frac{1}{L} \int v_L(t) dt$$

$$i_L(t) = 100 \int 10t dt$$


$$i_L(t) = 500 t^2 \text{ mA}$$

for  $1 \text{ ms} \leq t \leq 2 \text{ ms}$

$$v_L(t) = -10t + 20$$

$$i_L(t) = 100 \int (-10t + 20) dt$$

$$i_L(t) = -500 t^2 + 2000t \text{ mA}$$

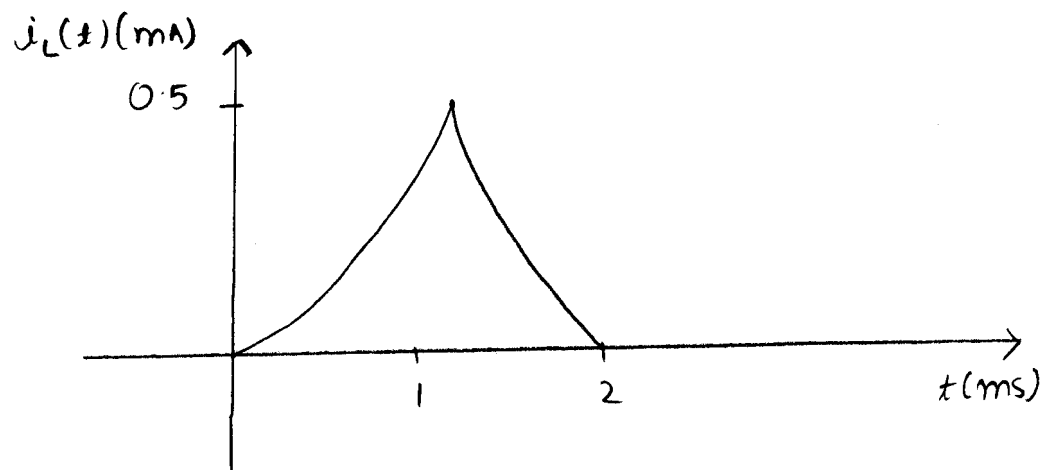

- 6.26 The current in a 10-mH inductor is shown in Fig. P6.26. Determine the waveform for the voltage across the inductor.

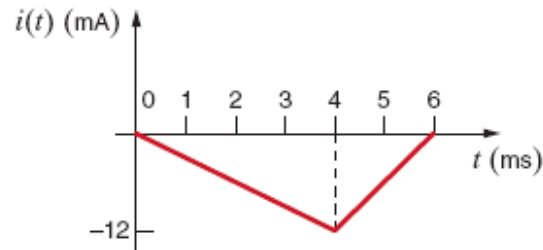


Figure P6.26

**SOLUTION:**

$$v(t) = L \frac{di(t)}{dt}$$

$$\text{for } t < 0, \quad v(t) = 0$$

$$\text{for } 0 < t \leq 4 \text{ ms} \\ v(t) = 10 \text{ m} \left[ \frac{-12 \text{ m}}{4 \text{ m}} \right] = -30 \text{ mV}$$

$$\text{for } 4 \text{ ms} < t \leq 6 \text{ ms}$$


$$v(t) = 10 \text{ m} \left[ \frac{12 \text{ m}}{2 \text{ m}} \right] = 60 \text{ mV}$$

$$\text{for } t > 6 \text{ ms} \\ v(t) = 0$$

$$v(t) = \begin{cases} 0 \\ -30 \text{ mV} \\ 60 \text{ mV} \\ 0 \end{cases}$$

$$\begin{aligned} &t < 0 \\ &0 < t \leq 4 \text{ ms} \\ &4 \text{ ms} < t \leq 6 \text{ ms} \\ &t > 6 \text{ ms} \end{aligned}$$

6.27 The current in a 50-mH inductor is given in the Fig. P6.27. Find the inductor voltage.

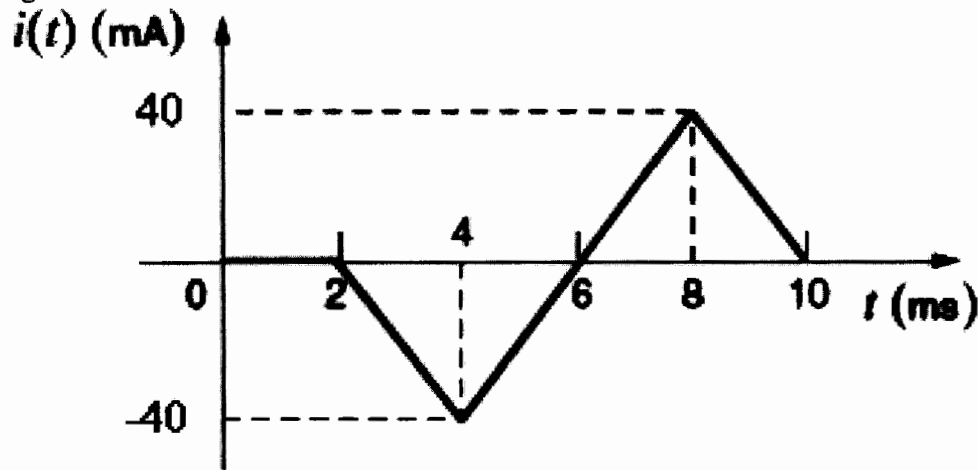

**Figure P6.27**


**Solution:** 6.27

$$V = L \frac{di}{dt}$$


$$\frac{di}{dt} = \begin{cases} 0 & 0 \leq t < 2 \\ -20 \text{ A/s} & 2 \leq t < 4 \\ 20 \text{ A/s} & 4 \leq t < 8 \\ -20 \text{ A/s} & 8 \leq t < 10 \end{cases}$$
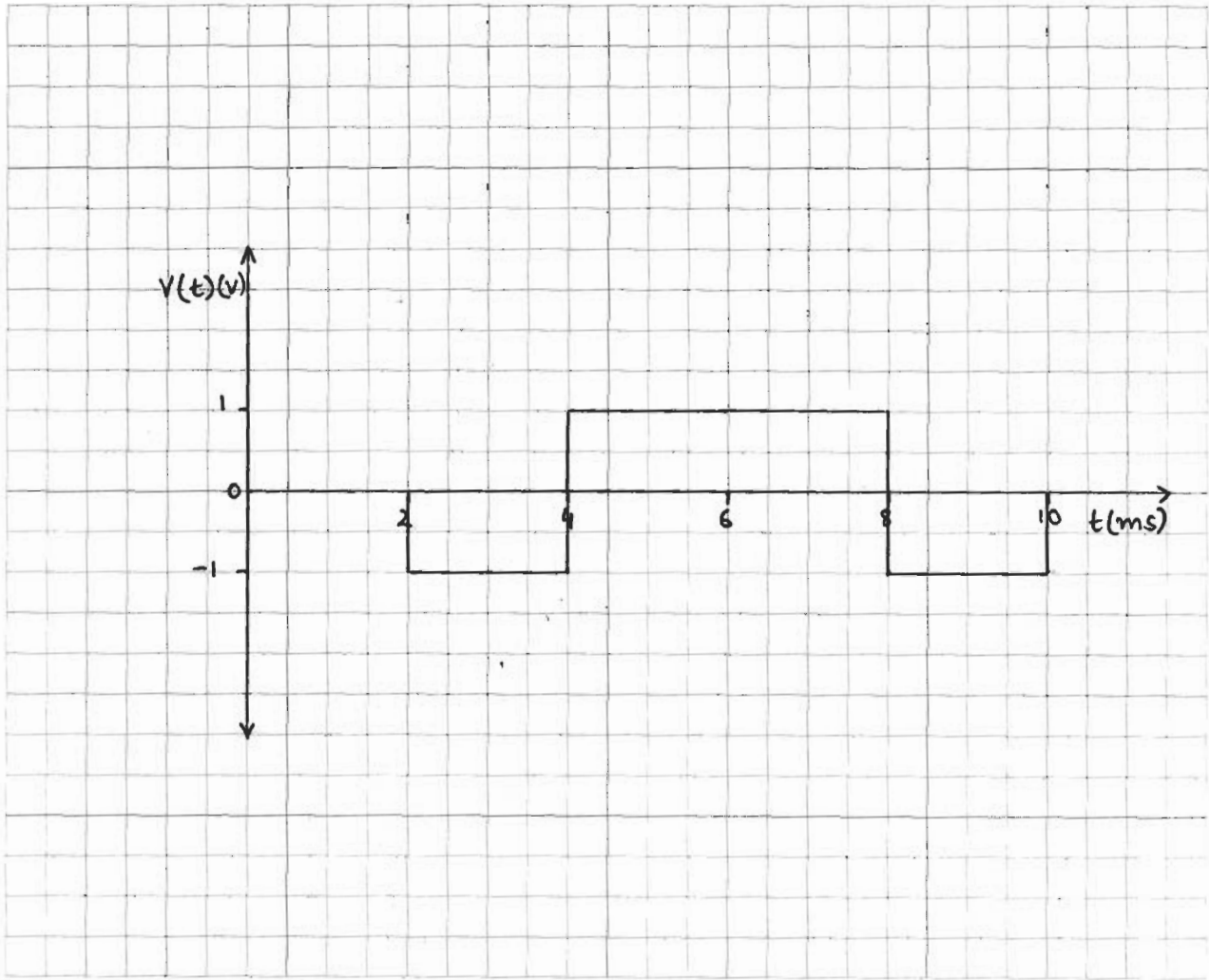
$$V = \begin{cases} 0 & 0 \leq t < 2 \\ -1 \text{ V} & 2 \leq t < 4 \\ 1 \text{ V} & 4 \leq t < 8 \\ -1 \text{ V} & 8 \leq t < 10 \end{cases}$$





**6.28** The current in a 70-mH inductor is shown in the Fig. P6.28. Find the voltage across the inductor.

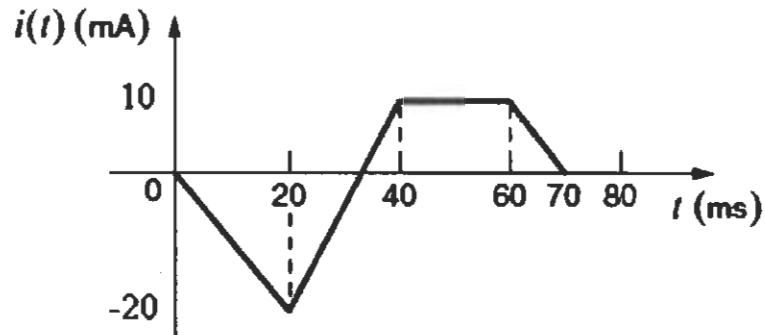


**Figure P6.28**

Solution: 6.28

$$v = L \frac{di}{dt}$$

$$\frac{di}{dt} = \begin{cases} 0 & t < 0 \\ -1 \text{ A/s} & 0 \leq t < 20 \\ 1.5 \text{ A/s} & 20 \leq t < 40 \\ 0 \text{ A/s} & 40 \leq t < 60 \\ -1 \text{ A/s} & 60 \leq t < 70 \end{cases}$$
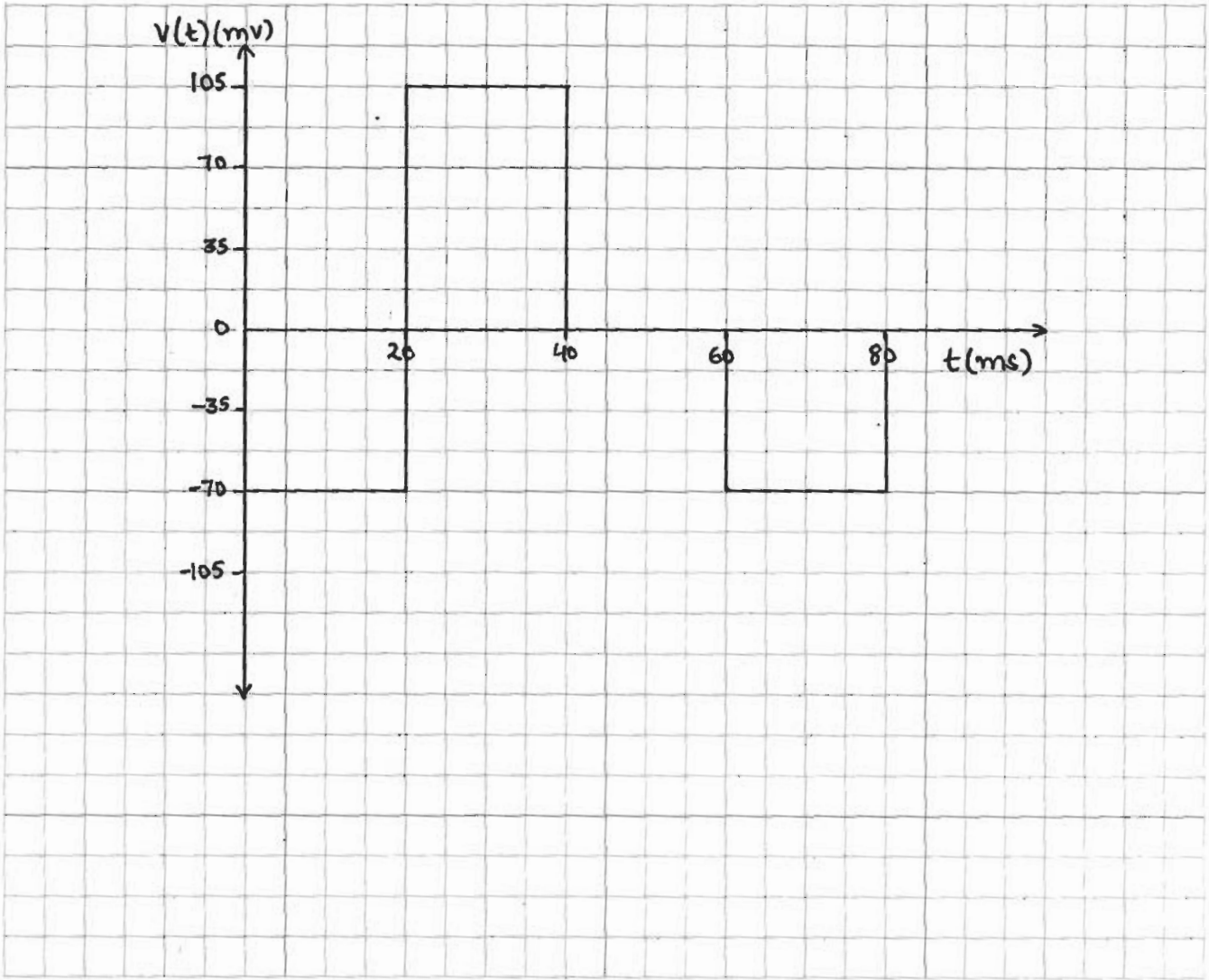
$$v = \begin{cases} 0 \text{ mV} & t \leq 0 \\ -70 \text{ mV} & 0 \text{ ms} \leq t < 20 \text{ ms} \\ 105 \text{ mV} & 20 \text{ ms} \leq t < 40 \text{ ms} \\ 0 \text{ mV} & 40 \text{ ms} \leq t < 60 \text{ ms} \\ -70 \text{ mV} & 60 \text{ ms} \leq t < 70 \text{ ms} \\ 0 \text{ mV} & t > 70 \text{ ms} \end{cases}$$



- 6.29 Draw the waveform for the voltage across a 24-mH inductor when the inductor current is given by the waveform shown in Fig. P6.29.

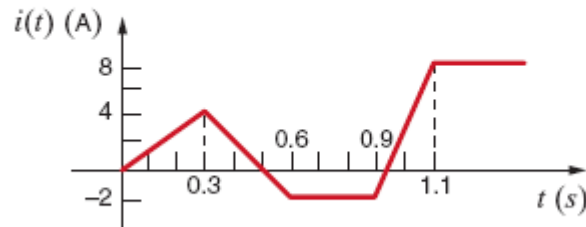


Figure P6.29

**SOLUTION:**

$$v(t) = L \frac{di(t)}{dt}$$

$$\text{for } t \leq 0, \quad v(t) = 0$$

$$\text{for } 0 \leq t \leq 0.3 \text{ s}$$

$$v(t) = 24 \text{ m} \left[ \frac{40}{3} \right]$$

$$v(t) = 320 \text{ mV}$$

$$\text{for } 0.3 \text{ s} < t \leq 0.6 \text{ s}$$

$$v(t) = 24 \text{ m} [-20]$$

$$v(t) = -480 \text{ mV}$$

$$\text{for } 0.6 \text{ s} < t \leq 0.9 \text{ s}$$


$$v(t) = 0$$

$$\begin{aligned} \text{for } 0.9\text{ s} < t \leq 1.1\text{ s} \\ V(t) &= 24\text{ m [50]} \\ V(t) &= 1200\text{ mV} \end{aligned}$$


$$\begin{aligned} \text{for } t > 1.1\text{ s} \\ V(t) &= 0 \end{aligned}$$

$$V(t) = \begin{cases} 0 \\ 320\text{ mV} \\ -480\text{ mV} \\ 0 \\ 1200\text{ mV} \\ 0 \end{cases}$$
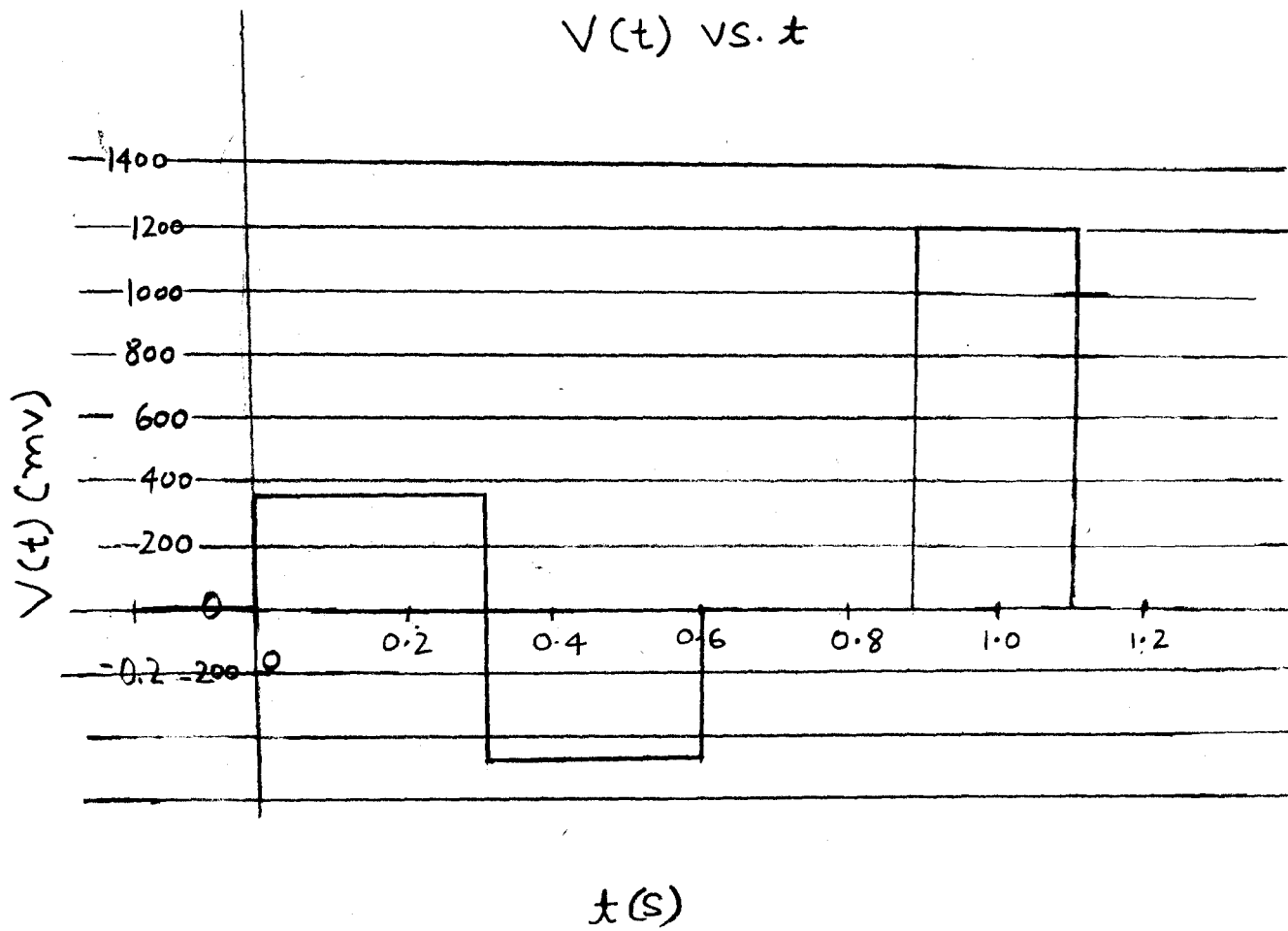
$$\begin{aligned} t &\leq 0 \\ 0 < t &\leq 0.3\text{ s} \\ 0.3\text{ s} < t &\leq 0.6\text{ s} \\ 0.6\text{ s} < t &\leq 0.9\text{ s} \\ 0.9\text{ s} < t &\leq 1.1\text{ s} \\ t &> 1.1\text{ s} \end{aligned}$$



**6.30** The current in a 29-mH inductor is given by the waveform in the Fig. P6.30. Find the waveform for the voltage across the inductor.

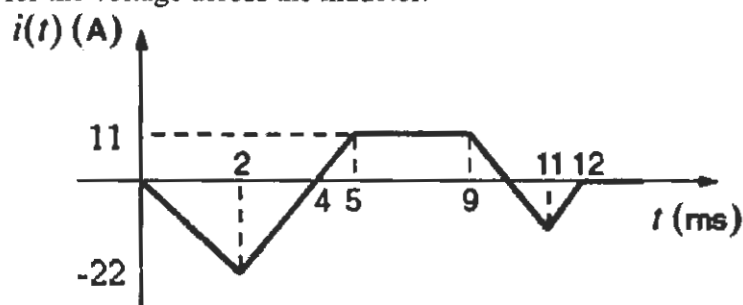


**Figure P6.30**

**Solution:** 6.30

$$V = L \frac{di}{dt}$$

$$\frac{di}{dt} = \begin{cases} 0 \text{ A/s} & t < 0 \text{ ms} \\ -11 \times 10^3 \text{ A/s} & 0 \leq t < 2 \text{ ms} \\ 11 \times 10^3 \text{ A/s} & 2 \text{ ms} \leq t < 5 \text{ ms} \\ 0 \text{ A/s} & 5 \text{ ms} \leq t < 9 \text{ ms} \\ -11 \times 10^3 \text{ A/s} & 9 \text{ ms} \leq t < 11 \text{ ms} \\ 11 \times 10^3 \text{ A/s} & 11 \text{ ms} \leq t < 12 \text{ ms} \\ 0 \text{ A/s} & t \geq 12 \text{ ms} \end{cases}$$
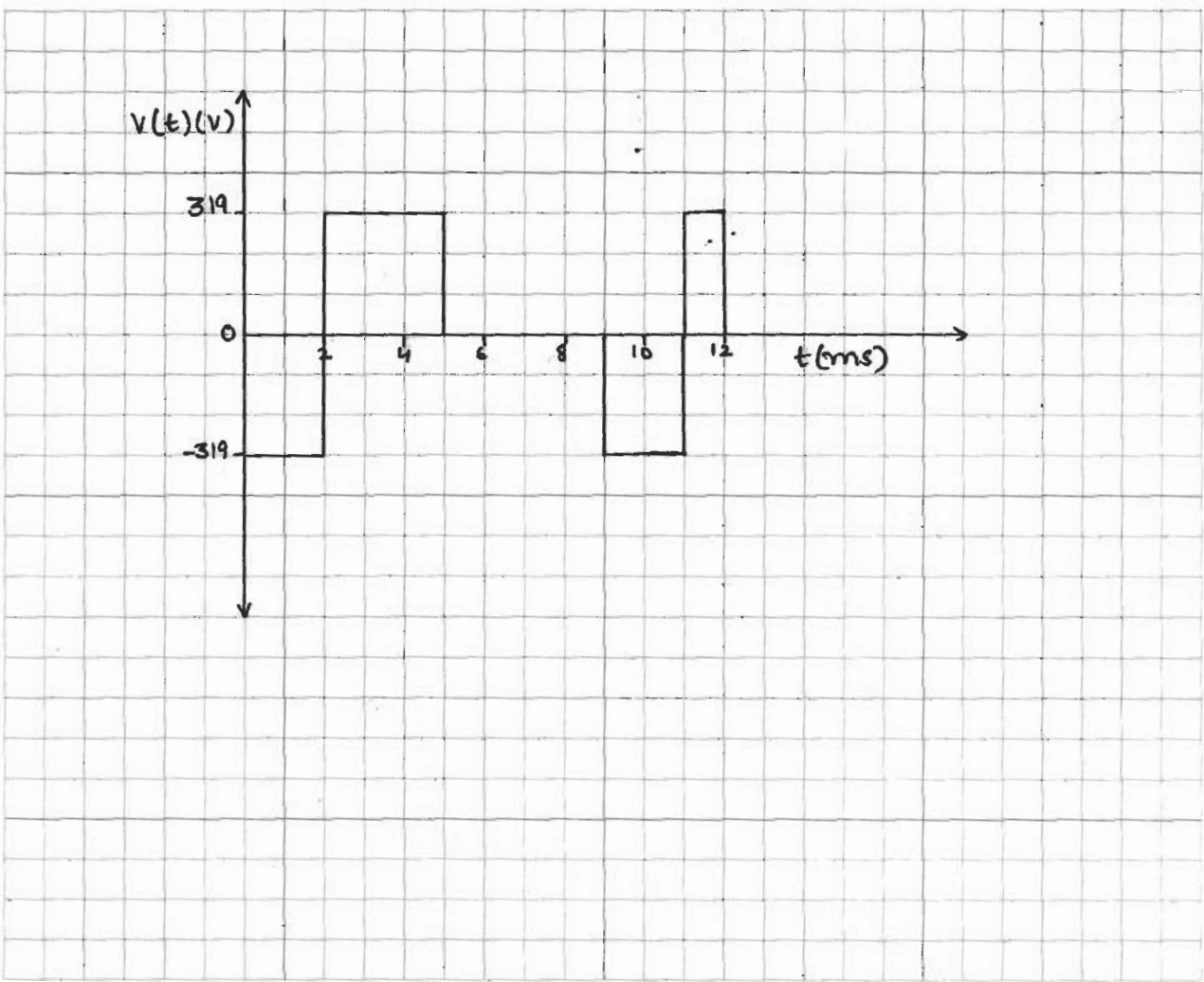
$$L = \begin{cases} 0 \text{ V} & t < 0 \text{ ms} \\ -319 \text{ V} & 0 \leq t < 2 \text{ ms} \\ 319 \text{ V} & 2 \text{ ms} \leq t < 5 \text{ ms} \\ 0 \text{ V} & 5 \text{ ms} \leq t < 9 \text{ ms} \\ -319 \text{ V} & 9 \text{ ms} \leq t < 11 \text{ ms} \\ 319 \text{ V} & 11 \text{ ms} \leq t < 12 \text{ ms} \\ 0 \text{ V} & t \geq 12 \text{ ms} \end{cases}$$





- 6.31 The current in a 4-mH inductor is given by the waveform in Fig. P6.31. Plot the voltage across the inductor.

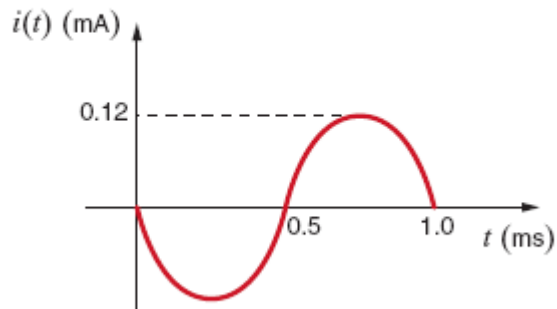


Figure P6.31

**SOLUTION:**

$$i(t) = -120 \sin \omega t \text{ } \mu\text{A}$$

$$\omega = \frac{2\pi}{T}$$

$$T = 1 \text{ ms}$$


$$\omega = 2000\pi \text{ rad/s}$$

$$i(t) = -120 \sin 2000\pi t \text{ } \mu\text{A}$$

$$v(t) = L \frac{di(t)}{dt}$$

$$v(t) = 4 \text{ m} [-120 \mu (2000\pi) \cos 2000\pi t]$$
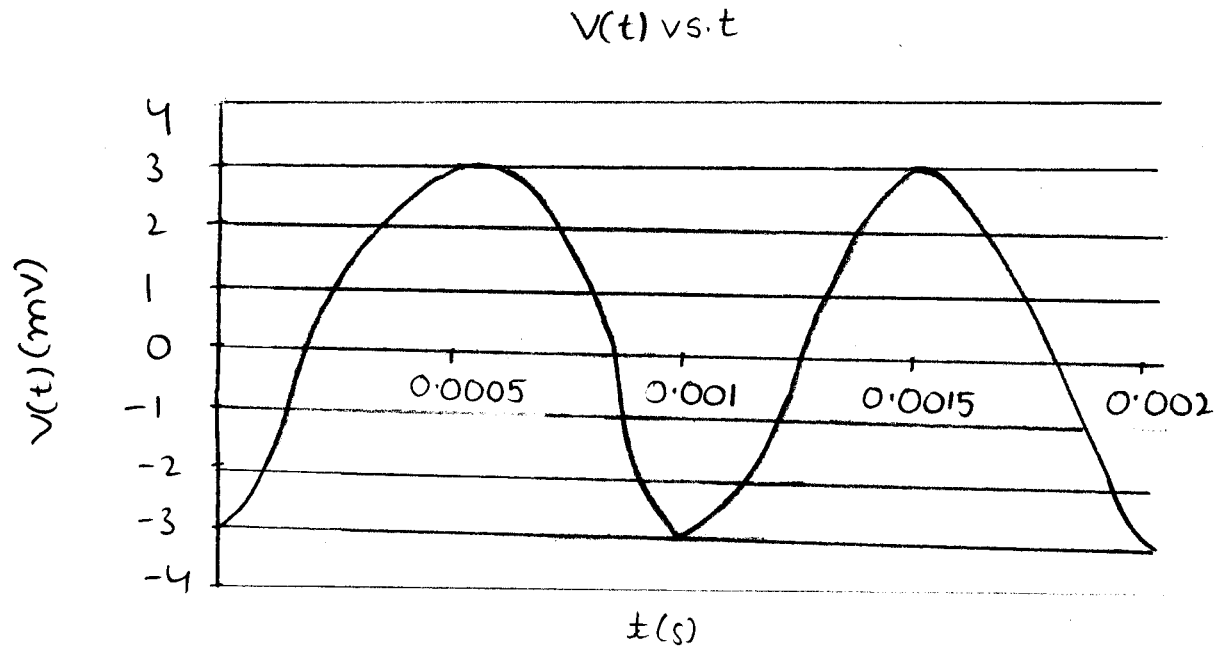
$$v(t) = -3.02 \cos 2000\pi t \text{ mV}$$



- 6.32 The waveform for the current in the 2-H inductor shown in Fig. P6.32a is given in Fig. P6.32b. Determine the following quantities (a) the energy stored in the inductor at  $t = 1.5$  ms, (b) the energy stored in the inductor at  $t = 7.5$  ms, (c)  $v_L(t) = 1.5$  ms, (d)  $v_L(t)$  at  $t = 6.25$  ms, and (e)  $v_L(t)$  at  $t = 2.75$  ms.

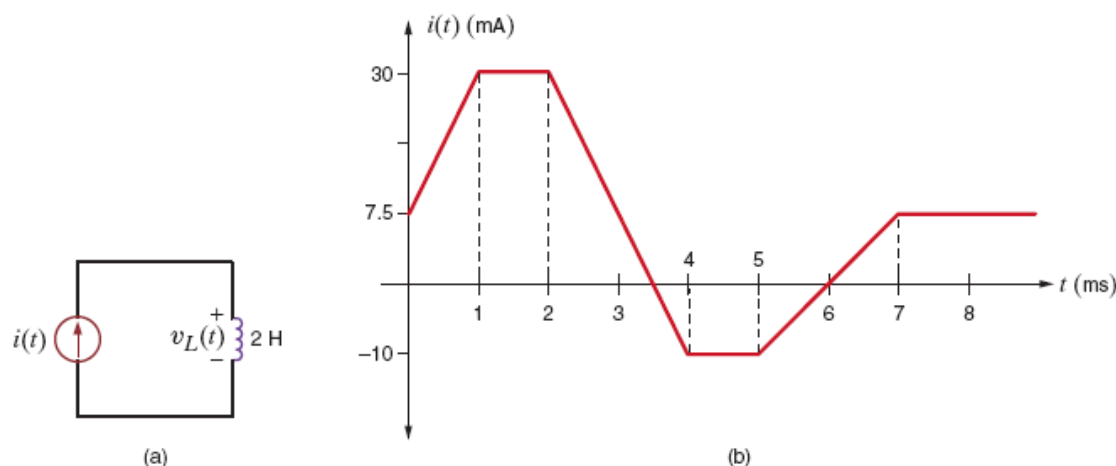


Figure P6.32

**SOLUTION:**

$$(a) \quad w(t) = \frac{1}{2} L i^2(t)$$

$$w(1.5 \text{ ms}) = \frac{1}{2} (2) (30 \times 10^{-3})^2$$

$$w(1.5 \text{ ms}) = 0.9 \text{ mJ}$$

$$(b) \quad w(t) = \frac{1}{2} L i^2(t)$$

$$w(7.5 \text{ ms}) = \frac{1}{2} (2) (7.5 \times 10^{-3})^2$$

$$w(7.5 \text{ ms}) = 56.25 \text{ } \mu\text{J}$$

$$(c) \quad v_L(t) = L \frac{di(t)}{dt}$$

$$i(t) = 30 \text{ mA in the interval of interest}$$

$$V_L(t) = 2[0]$$

$$V_L(t) = 0V$$

$$V_L(1.5ms) = 0V$$

$$(d) \quad V_L(t) = L \frac{di(t)}{dt}$$

$$m = \frac{-10 \times 10^{-3} - 10 \times 10^{-3}}{5 \times 10^{-3} - 7 \times 10^{-3}} = 10$$

$$i(t) = mt + B$$

$$i(t) = 10t + 60$$

A in the interval  
of interest

$$V_L(t) = 2[10]$$

$$V_L(t) = 20V$$

$$V_L(6.25ms) = 20V$$

$$(e) \quad V_L(t) = L \frac{di(t)}{dt}$$

$$m = \frac{-10 \times 10^{-3} - 30 \times 10^{-3}}{4 \times 10^{-3} - 2 \times 10^{-3}} = -20$$

$$\begin{aligned}i(t) &= -20t + B \\30 \times 10^{-3} &= -20(2 \times 10^{-3}) + B \\B &= 0.07\end{aligned}$$

$$i(t) = -20t + 0.07 \text{ A in the interval of interest}$$

$$v_L(t) = 2[-20]$$

$$v_L(t) = -40\text{V}$$

$$v_L(2.75 \text{ ms}) = -40\text{V}$$

6.33 Find the possible capacitance range of the following capacitors.

(a)  $0.0068 \mu\text{F}$  with a tolerance of 10%.

(b)  $120 \text{ pF}$  with a tolerance of 20%.

(c)  $39 \mu\text{F}$  with a tolerance of 20%.

---

**SOLUTION:**

(a)  $C = 0.0068 \mu\text{F}$  with 10% tolerance

Range:

$$61.2 \text{ nF} \leq C \leq 74.8 \text{ nF}$$

$$61.2 \text{ n} \leq C \leq 74.8 \text{ n}$$

(b)  $C = 120 \text{ pF}$  with 20% tolerance

Range:

$$96 \text{ pF} \leq C \leq 144 \text{ pF}$$

(c)  $C = 39 \mu\text{F}$  with 20% tolerance

Range:

$$31.2 \mu\text{F} \leq C \leq 46.8 \mu\text{F}$$

**6.34** Find the possible inductance range of the following inductors.

(a) 50 mH with a tolerance of 10%.

(b) 8 nH with a tolerance of 5%.

(c) 63  $\mu$ H with a tolerance of 10%.

---


**Solution:** 6.34

$$(a) \quad L = 50 \text{ mH} \pm 10\%, \quad 45 \text{ mH} \leq L \leq 55 \text{ mH}$$


$$(b) \quad L = 8 \text{ nH} \pm 5\%, \quad 7.6 \text{ nH} \leq L \leq 8.4 \text{ nH}$$

$$(c) \quad L = 63 \mu\text{H} \pm 10\%, \quad 56.7 \mu\text{H} \leq L \leq 69.3 \mu\text{H}$$

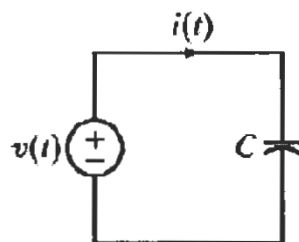6.35 The capacitor in Fig. P6.35 (a) is 53 nF with a tolerance of 10%. Given the voltage waveform in Fig. P6.35 (b), find the current  $i(t)$  for the minimum and maximum capacitor values.



(a)

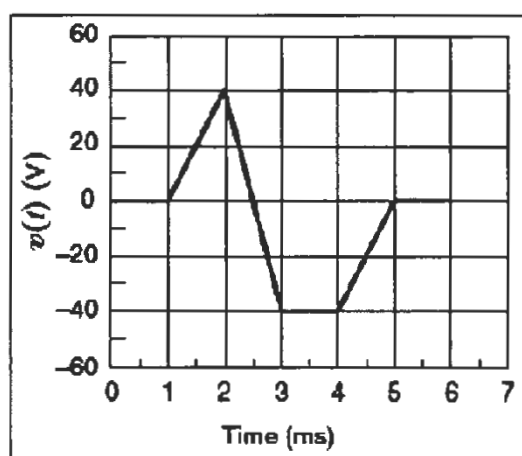

(b)

**Figure P6.35**

**Solution:** 6.35

$$i(t) = C \frac{dv}{dt}$$

$\frac{dv}{dt} =$	0 V/s	$0 \leq t < 1$
	$4 \times 10^4$ V/s	$1 \leq t < 2$
	$-8 \times 10^4$ V/s	$2 \leq t < 3$
	0 V/s	$3 \leq t < 4$
	$4 \times 10^4$ V/s	$4 \leq t < 5$
	0 V/s	$5 \leq t < 6$


$$C_{\max} = 53 + 5.3 = 58.3 \text{ nF}$$

$$C_{\min} = 53 - 5.3 = 47.7 \text{ nF}$$



$$i(t) [\text{mA}] = \begin{cases} 0 \text{ mA} & 0 \leq t < 15 \\ 2.33 \text{ mA} & 15 \leq t < 25 \\ -4.66 \text{ mA} & 25 \leq t < 35 \\ 0 \text{ mA} & 35 \leq t < 45 \\ 2.33 \text{ mA} & 45 \leq t < 55 \\ 0 \text{ mA} & 55 \leq t < 65 \end{cases}$$
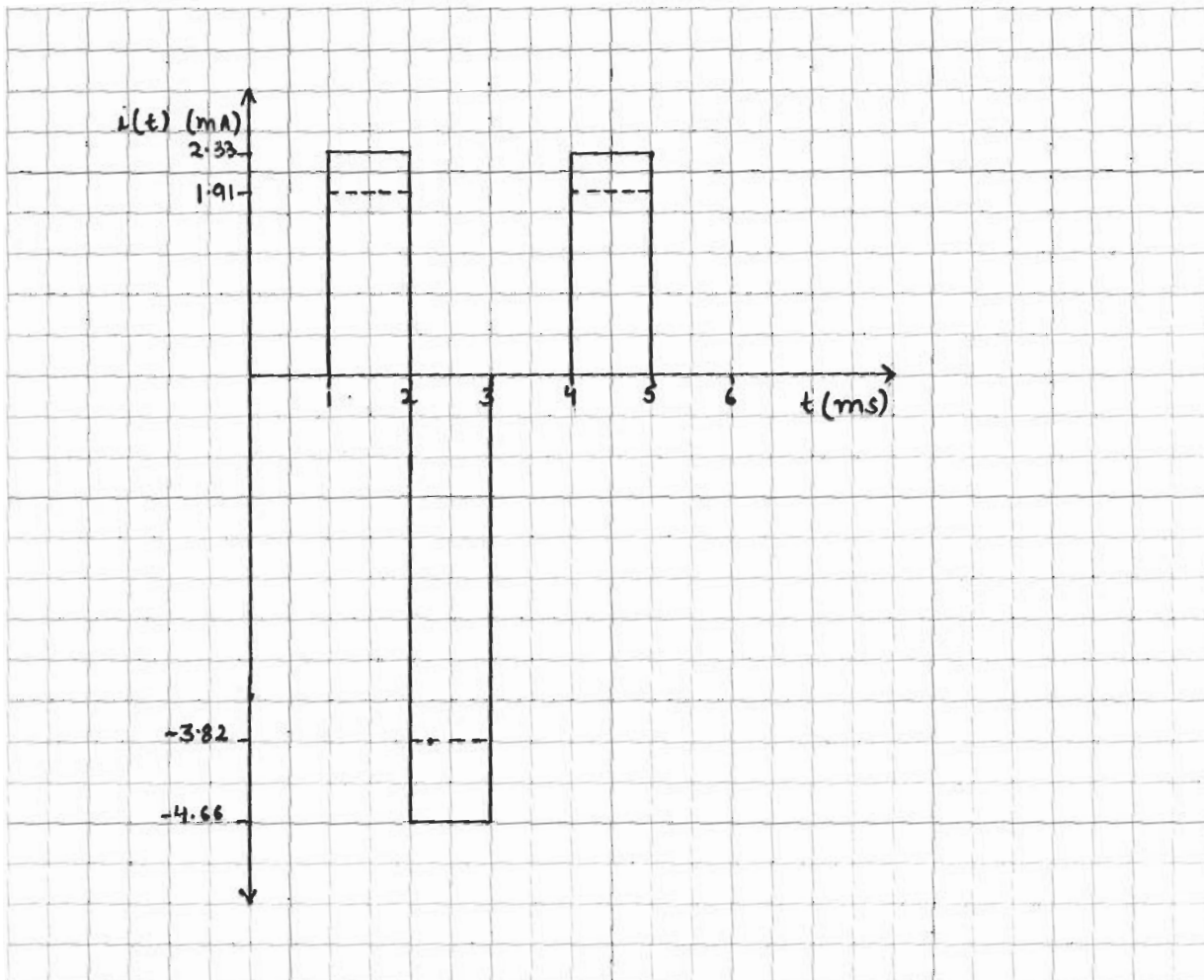
$$i(t) [\text{mA}] = \begin{cases} 0 \text{ mA} & 0 \leq t < 15 \\ 1.91 \text{ mA} & 15 \leq t < 25 \\ -3.82 \text{ mA} & 25 \leq t < 35 \\ 0 \text{ mA} & 35 \leq t < 45 \\ 1.91 \text{ mA} & 45 \leq t < 55 \\ 0 \text{ mA} & 55 \leq t < 65 \end{cases}$$



6.36 Given the capacitors in Fig. 6.36 are  $C_1 = 2.0 \mu\text{F}$  with a tolerance of 2% and  $C_2 = 2.0 \mu\text{F}$  with a tolerance of 20%, find the following.

- The nominal value of  $C_{eq}$ .
- The minimum and maximum possible values of  $C_{eq}$ .
- The percent errors of the minimum and maximum values.

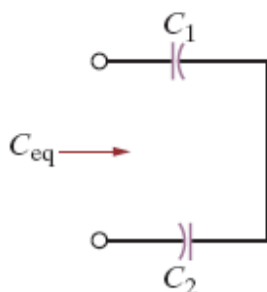


Figure P6.36

**SOLUTION:**

$$(a) \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = \frac{(2 \times 10^{-6})(2 \times 10^{-6})}{2 \times 10^{-6} + 2 \times 10^{-6}}$$

$$C_{eq} = 1 \mu\text{F}$$

$$(b) \quad C_{max} = \frac{C_{1max} + C_{2max}}{C_{1max} + C_{2max}}$$

$$C_{max} = \frac{(2.04 \times 10^{-6})(2.4 \times 10^{-6})}{2.04 \times 10^{-6} + 2.4 \times 10^{-6}}$$

$$C_{\max} = 1.1 \mu\text{F}$$

$$C_{\min} = \frac{C_{1\min} C_{2\min}}{C_{1\min} + C_{2\min}}$$

$$C_{\min} = \frac{(1.96 \times 10^{-6})(1.6 \times 10^{-6})}{(1.96 \times 10^{-6}) + 1.6 \times 10^{-6}}$$

$$C_{\min} = 0.881 \mu\text{F}$$

$$(C) \quad + \% \text{ error} = \frac{C_{\max} - C_{eq}}{C_{eq}}$$

$$+ \% \text{ error} = \frac{1.1 \times 10^{-6} - 1 \times 10^{-6}}{1 \times 10^{-6}}$$


$$+ \% \text{ error} = 10\%$$

$$- \% \text{ error} = \frac{C_{\min} - C_{eq}}{C_{eq}}$$


$$- \% \text{ error} = \frac{0.881 \times 10^{-6} - 1 \times 10^{-6}}{1 \times 10^{-6}}$$

$$- \% \text{ error} = -11.9\%$$

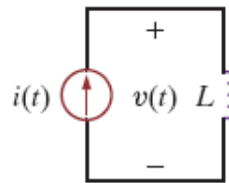- 6.37 The inductor in Fig. P6.37a is  $4.7 \mu\text{H}$  with a tolerance of 20%. Given the current waveform in Fig. P6.37b, graph the voltage  $v(t)$  for the minimum and maximum inductor values.



(a)

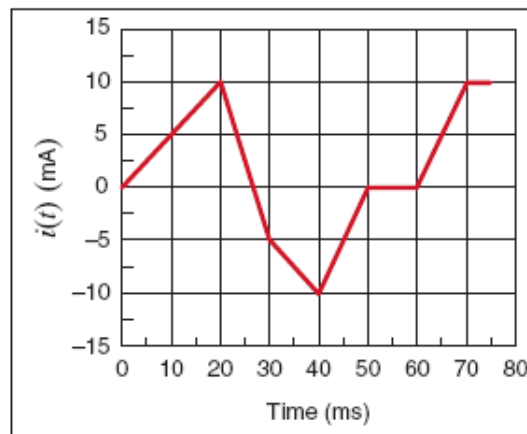

(b)

Figure P6.37

**SOLUTION:**

$$v(t) = L \frac{di(t)}{dt}$$

$$\text{for } 0 \leq t < 20\text{ms}$$

$$v_{\max}(t) = (1.2)(4.7\mu)(\frac{1}{2}) = 2.82\mu\text{V}$$

$$v_{\min}(t) = (0.8)(4.7\mu)(\frac{1}{2}) = 1.88\mu\text{V}$$

$$\text{for } 20\text{ms} \leq t \leq 30\text{ms}$$

$$v_{\max}(t) = (1.2)(4.7\mu)(-1.5) = -8.46\mu\text{V}$$

$$v_{\min}(t) = (0.8)(4.7\mu)(-1.5) = -5.46\mu\text{V}$$

for  $30\text{ms} \leq t \leq 40\text{ms}$

$$V_{\max}(t) = (1.2)(4.7\mu)(0.5) = -2.82\mu\text{V}$$

$$V_{\min}(t) = (0.8)(4.7\mu)(-0.5) = -1.88\mu\text{V}$$

for  $40\text{ms} \leq t \leq 50\text{ms}$

$$V_{\max}(t) = (1.2)(4.7\mu)(1) = 5.64\mu\text{V}$$

$$V_{\min}(t) = (0.8)(4.7\mu)(1) = 3.76\mu\text{V}$$

for  $50\text{ms} \leq t < 60\text{ms}$

$$V(t) = 0\text{V}$$


for  $60\text{ms} \leq t \leq 70\text{ms}$

$$V_{\max}(t) = (1.2)(4.7\mu)(1) = 5.64\mu\text{V}$$

$$V_{\min}(t) = (0.8)(4.7\mu)(1) = 3.76\mu\text{V}$$

for  $t > 70\text{ms}$

$$V(t) = 0\text{V}$$

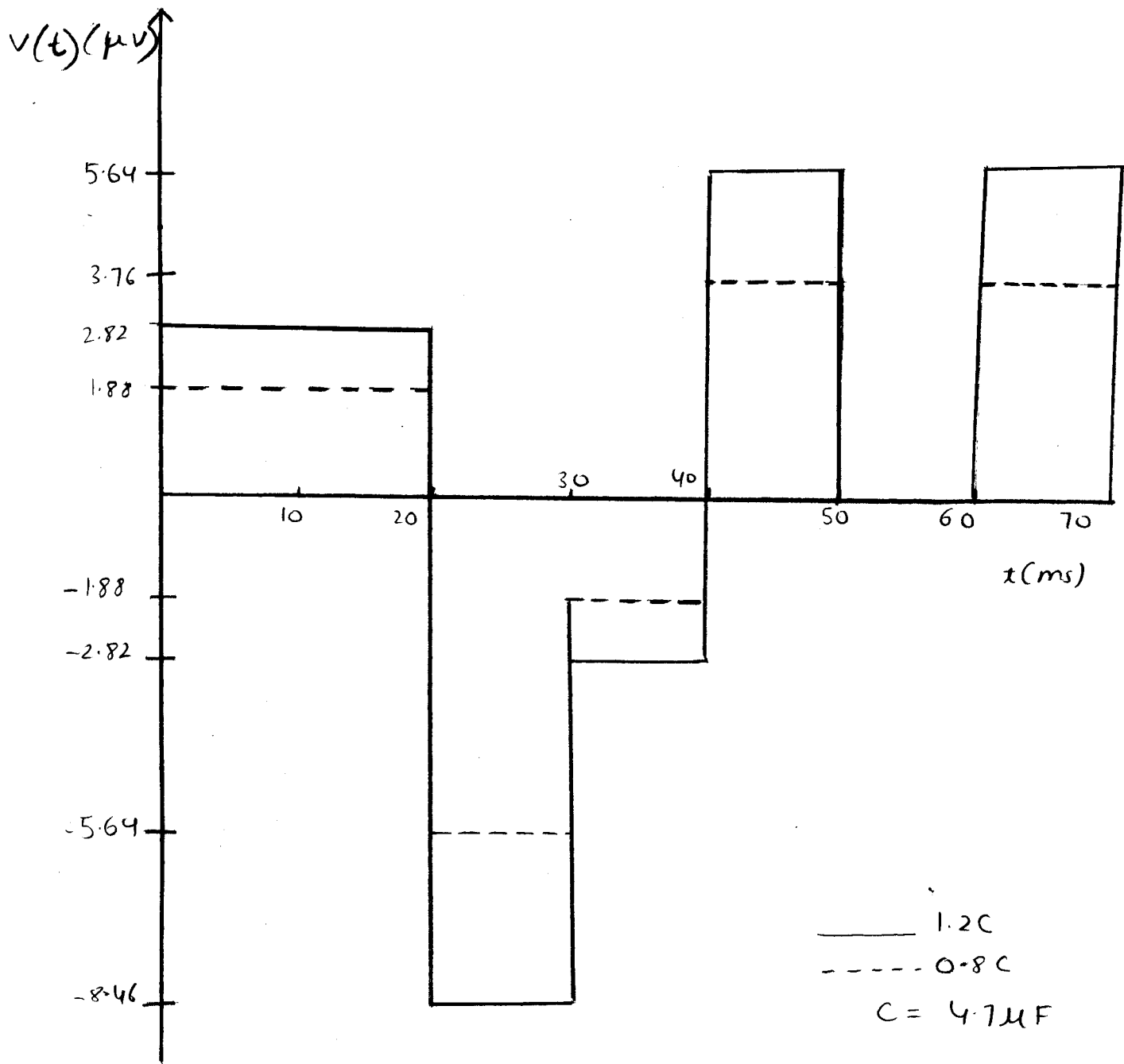

- 6.38 If the total energy stored in the circuit in Fig. P6.38 is 80 mJ, what is the value of  $L$ ?


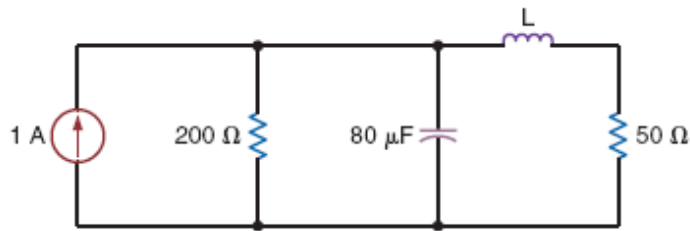


Figure P6.38


**SOLUTION:**

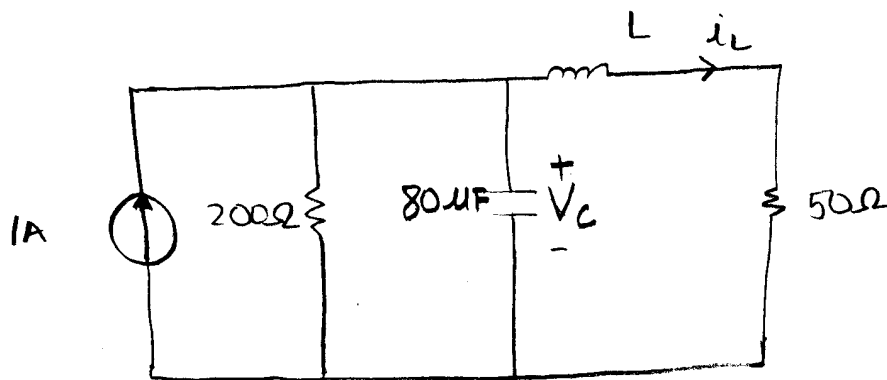

$$i_C = C \frac{dV_C}{dt} = 0, \quad V_C \text{ is a constant}$$

$$V_L = L \frac{di_L}{dt} = 0, \quad i_L \text{ is a constant}$$

Redraw the circuit as:

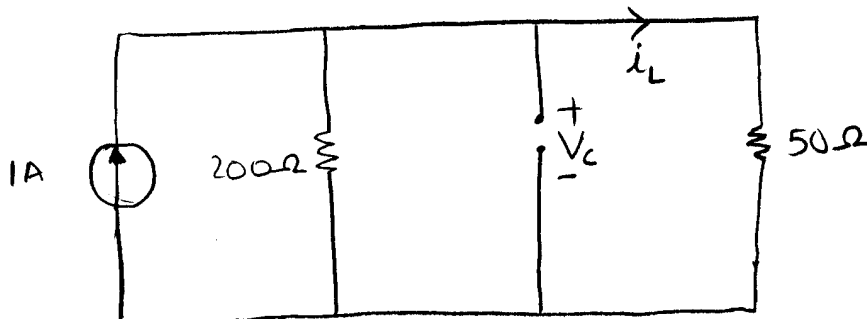

$$R_{eq} = 200 \parallel 50 = \frac{200(50)}{200+50}$$

$$R_{eq} = 40 \Omega$$

$$V_C = (1)(40) \quad V_C = 40V$$
$$W_C = \frac{1}{2} C V_C^2$$

$$W_C = \frac{1}{2} (80 \mu) (40)^2$$
$$W_C = 64 mJ$$

$$i_L = \left( \frac{200}{200+50} \right) (1)$$

$$i_L = 0.8 A$$

$$W_L = \frac{1}{2} L i_L^2$$

$$L = \frac{2 W_L}{i_L^2}$$

$$W_{total} = W_L + W_C$$

$$W_L = 80 mJ - 64 mJ$$


$$W_L = 16 mJ$$

$$L = \frac{2(16 mJ)}{(0.8)^2}$$

$$L = 50 mH$$




**6.39** Find the value of  $C$  if the energy stored in the capacitor in Fig. P6.39 equals the energy stored in the inductor.

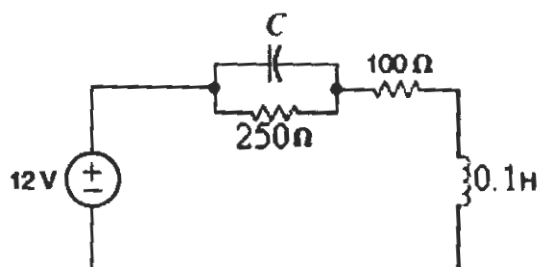

**Figure P6.39**


**Solution:** 6.39

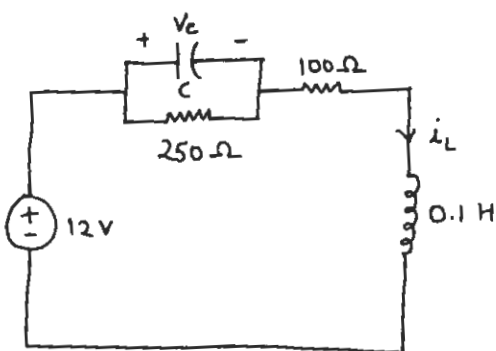

Since voltage source is constant,  $V_C$  and  $i_L$  are constant.

$$i_C = C \frac{dV_C}{dt} = 0 \text{ and}$$

$$V_L = L \frac{di_L}{dt} = 0$$

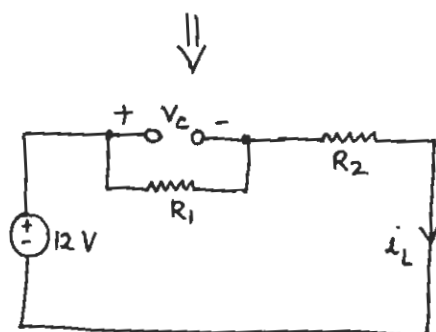


$$i_L = \frac{12}{R_1 + R_2} = 34.29 \text{ mA}$$

$$V_C = \frac{12 R_1}{R_1 + R_2} = 8.57 \text{ V}$$

$$W_C = \frac{1}{2} C V_C^2 = W_L = \frac{1}{2} L i_L^2 \Rightarrow C = L \left( \frac{i_L}{V_C} \right)^2$$


$$C = 1.60 \mu\text{F}$$

**6.40** Given the network in Fig. P6.40, find (a) the power dissipated in the  $3\text{-}\Omega$  resistor and (b) the energy stored in the capacitor.

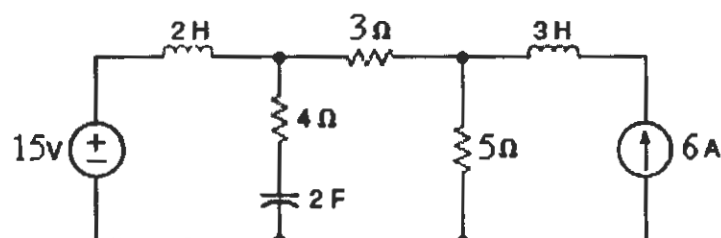

**Figure P6.40**

**Solution:** 6.40

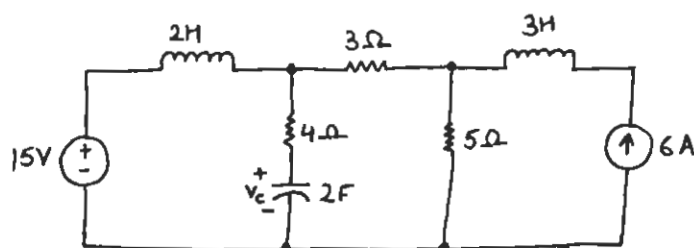

Since all sources are constant, all voltages and current are constant

$$V_L = L \frac{di_L}{dt} = 0 \quad \text{and}$$

$$i_C = C \frac{dV_C}{dt} = 0$$

$$P_{R_2} = R_2 i_R^2, \quad W_C = \frac{1}{2} C V_C^2$$


By superposition

$$i_R = 15 \left[ \frac{1}{R_2 + R_3} \right] - 6 \left[ \frac{R_3}{R_2 + R_3} \right]$$

$$= -1.875 \text{ A}$$

$$P_{R_2} = 10.54 \text{ W}$$


$$W_C = 225 \text{ J}$$

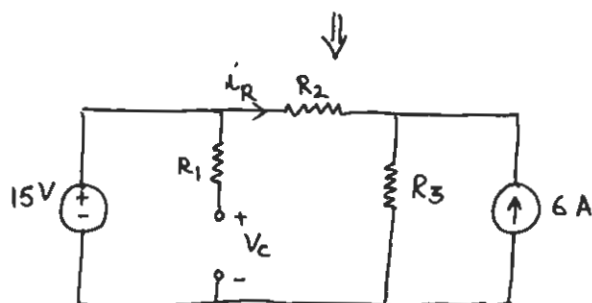


6.41 What values of capacitance can be obtained by interconnecting a  $4\text{-}\mu\text{F}$  capacitor, a  $6\text{-}\mu\text{F}$  capacitor, and a  $12\text{-}\mu\text{F}$  capacitor?

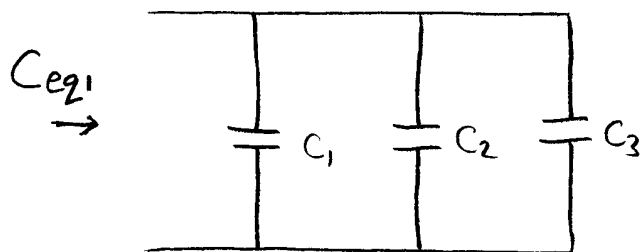**SOLUTION:**

$$C_1 = 4\text{ }\mu\text{F}, C_2 = 6\text{ }\mu\text{F}, \text{ and } C_3 = 12\text{ }\mu\text{F}$$



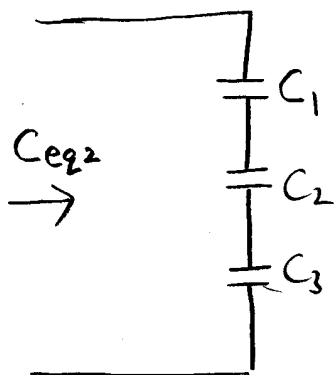
$$C_{eq1} = C_1 + C_2 + C_3 = 4\mu + 6\mu + 12\mu = 22\mu\text{F}$$



$$C_{eq2} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$


$$C_{eq2} = \frac{1}{\frac{1}{4\mu} + \frac{1}{6\mu} + \frac{1}{12\mu}}$$

$$C_{eq2} = 2\text{ }\mu\text{F}$$

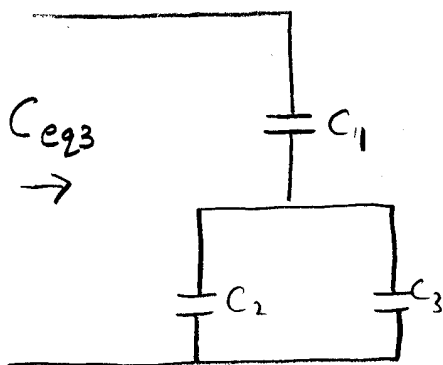


$$C_{eq3} = \frac{(C_2 + C_3) C_1}{C_1 + C_2 + C_3}$$

$$C_{eq3} = 3.27\text{ }\mu\text{F}$$

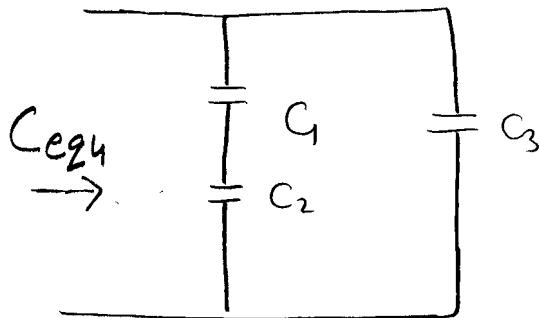


$$C_{eq4} = C_3 + \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq4} = 14.4 \mu F$$

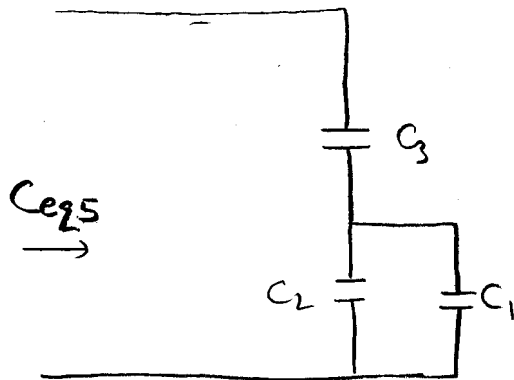


$$C_{eq5} = \frac{(C_1 + C_2)(C_3)}{C_1 + C_2 + C_3}$$

$$C_{eq5} = 5.45 \mu F$$

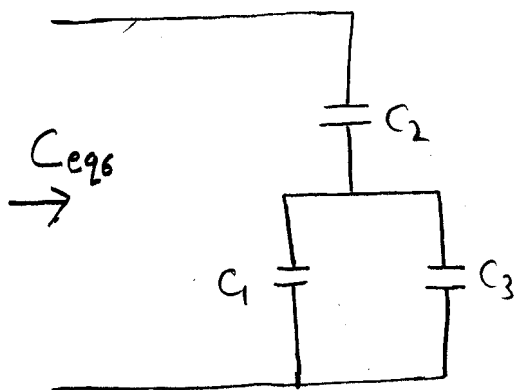


$$C_{eq6} = \frac{(C_1 + C_3)(C_2)}{C_1 + C_2 + C_3}$$

$$C_{eq6} = 4.36 \mu F$$

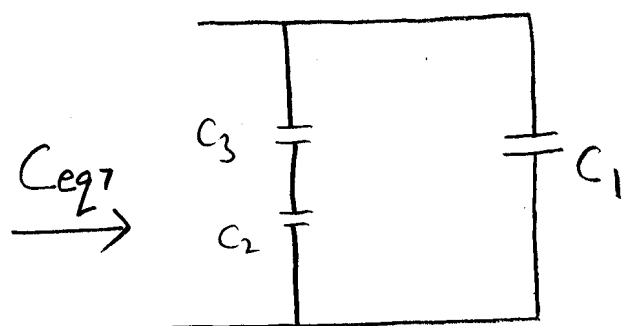

$$C_{eq7} = \frac{C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

$$C_{eq7} = 8 \mu F$$

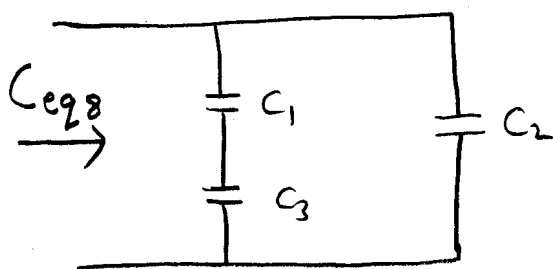

$$C_{eq8} = \frac{C_2(C_1 + C_3)}{C_1 + C_2 + C_3}$$

$$C_{eq8} = 9 \mu F$$

Capacitance values possible:

$$C_{eq1} = 22 \mu F$$

$$C_{eq2} = 2 \mu F$$

$$C_{eq3} = 3.27 \mu F$$

$$C_{eq4} = 14.4 \mu F$$

$$C_{eq5} = 5.45 \mu F$$

$$C_{eq6} = 4.36 \mu F$$

$$C_{eq7} = 8 \mu F$$


$$C_{eq8} = 9 \mu F$$

- 6.42 Given four  $2\text{-}\mu\text{F}$  capacitors, find the maximum value and minimum value that can be obtained by interconnecting the capacitors in series/parallel combinations.

**SOLUTION:**

$$C_1 = C_2 = C_3 = C_4 = 2\text{ }\mu\text{F}$$


Minimum when all connected in series:

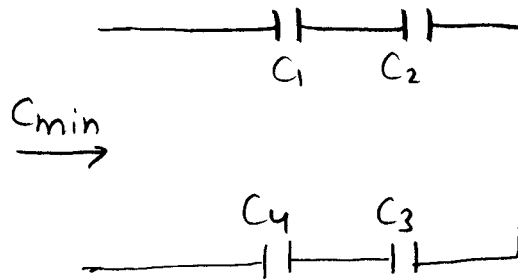

$$C_{\min} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}}$$

$$C_{\min} = 0.5\text{ }\mu\text{F}$$

Maximum when all connected in parallel:

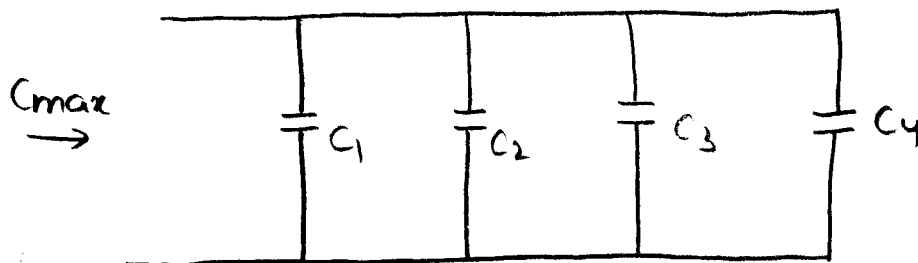


$$C_{\max} = C_1 + C_2 + C_3 + C_4$$

$$C_{\max} = 8 \mu F$$

6.43 Given a 4-, 12-, and 16- $\mu\text{F}$  capacitor, can they be interconnected to obtain an equivalent 8- $\mu\text{F}$  capacitor?

**Solution:** 6.43

Yes

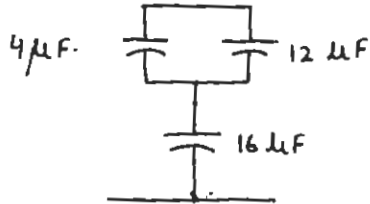


$$C_{eq} = \frac{(4 \times 10^{-6} + 12 \times 10^{-6}) 16 \times 10^{-6}}{(4 \times 10^{-6} + 12 \times 10^{-6}) + 16 \times 10^{-6}}$$
$$= 8 \mu\text{F}$$



6.44 Determine the values of inductance that can be obtained by interconnecting a 4-mH inductor, a 6-mH inductor, and a 12-mH inductor.

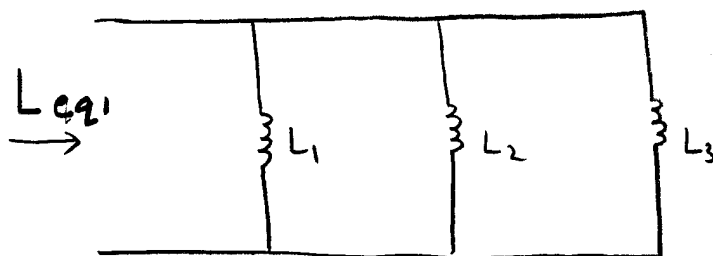
**SOLUTION:**

$$L_1 = 4\text{mH}, L_2 = 6\text{mH}, \text{ and } L_3 = 12\text{mH}$$




$$Leq1 = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$

$$Leq1 = 2\text{mH}$$

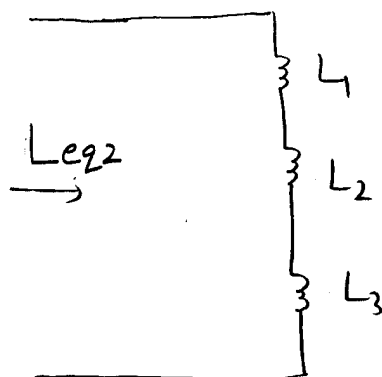


$$Leq2 = L_1 + L_2 + L_3$$

$$Leq2 = 22\text{mH}$$

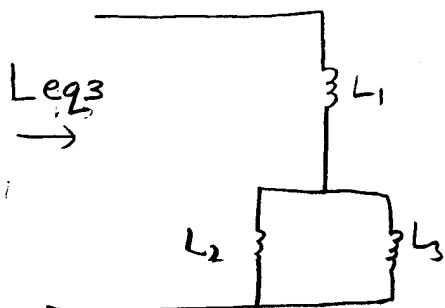

$$Leq3 = \frac{L_2 L_3}{L_2 + L_3} + L_1$$


$$Leq3 = 8\text{mH}$$

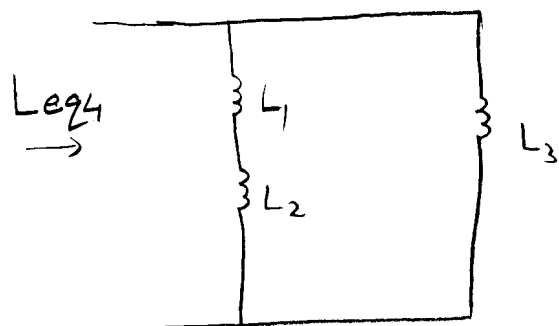

$$Leq4 = (L_1 + L_2) \parallel L_3$$

$$Leq4 = \frac{(L_1 + L_2)(L_3)}{L_1 + L_2 + L_3}$$


$$Leq4 = 5.45 \text{ mH}$$

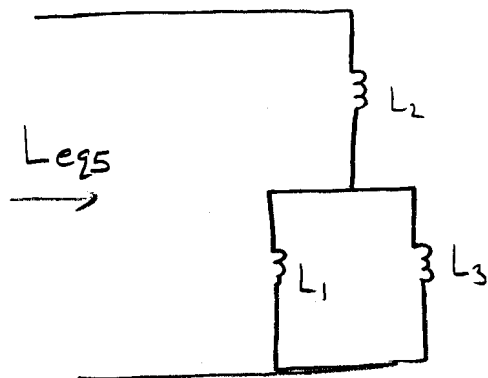

$$Leq5 = (L_1 \parallel L_3) + L_2$$

$$Leq5 = \frac{L_1 L_3}{L_1 + L_3} + L_2$$


$$Leq5 = 14.4 \text{ mH}$$

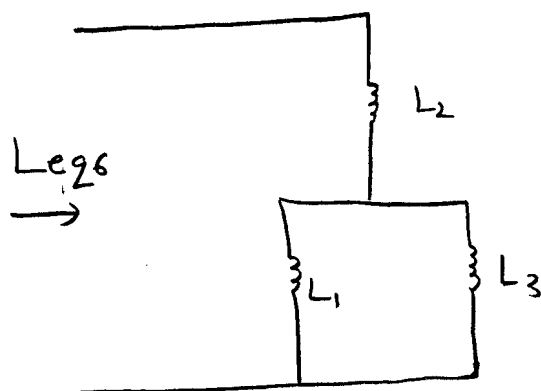


$$Leq6 = (L_1 \parallel L_3) + L_2$$

$$Leq6 = \frac{L_1 L_3}{L_1 + L_3} + L_2$$

$$Leq6 = 9 \text{ mH}$$

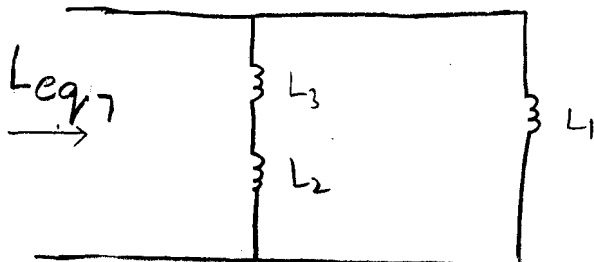
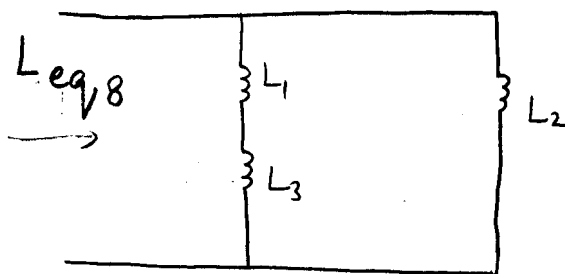
$$Leq_7 = \frac{(L_2 + L_3)L_1}{L_1 + L_2 + L_3} = 3.27 \text{ mH}$$



$$Leq_8 = \frac{(L_1 + L_3)L_2}{L_1 + L_2 + L_3} = 4.36 \text{ mH}$$

Inductance values possible:


$$\begin{aligned} Leq_1 &= 2 \text{ mH} \\ Leq_2 &= 22 \text{ mH} \\ Leq_3 &= 8 \text{ mH} \\ Leq_4 &= 5.45 \text{ mH} \end{aligned}$$

$$\begin{aligned} Leq_5 &= 14.4 \text{ mH} \\ Leq_6 &= 9 \text{ mH} \\ Leq_7 &= 3.27 \text{ mH} \\ Leq_8 &= 4.36 \text{ mH} \end{aligned}$$

- 6.45 Given four 4-mH inductors, determine the maximum and minimum values of inductance that can be obtained by interconnecting the inductors in series/parallel combinations.


**SOLUTION:**

$$L_1 = L_2 = L_3 = L_4 = 4\text{ mH}$$

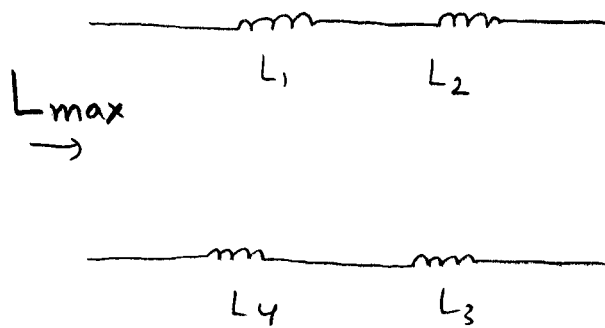

$$L_{\max} = L_1 + L_2 + L_3 + L_4$$

$$L_{\max} = 16\text{ mH}$$

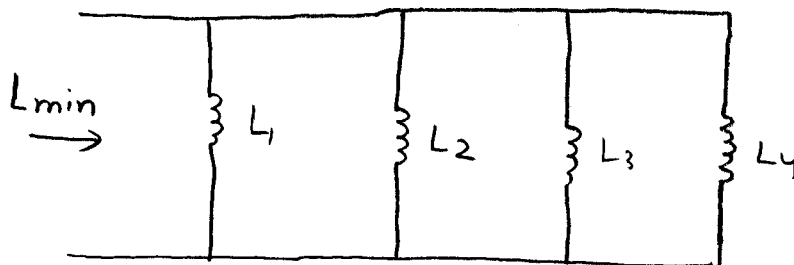


$$L_{\min} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}}$$

$$L_{\min} = 1\text{ mH}$$

6.46 Given a 6-, 9- and 18-mH inductor, can they be interconnected to obtain an equivalent 12-mH inductor?

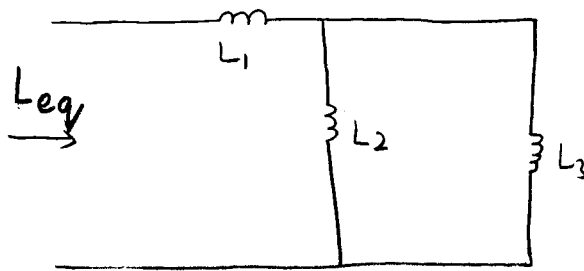**SOLUTION:**

$$L_1 = 6 \text{ mH}, L_2 = 9 \text{ mH}, \text{ and } L_3 = 18 \text{ mH}$$
$$L_{eq} = 12 \text{ mH}$$




$$L_{eq} = (L_2 \parallel L_3) + L_1$$

$$L_{eq} = \frac{L_2 L_3}{L_2 + L_3} + L_1$$


$$L_{eq} = 12 \text{ mH}$$

6.47 Find the total capacitance  $C_T$  of the network shown in the Fig. P6.47 below.

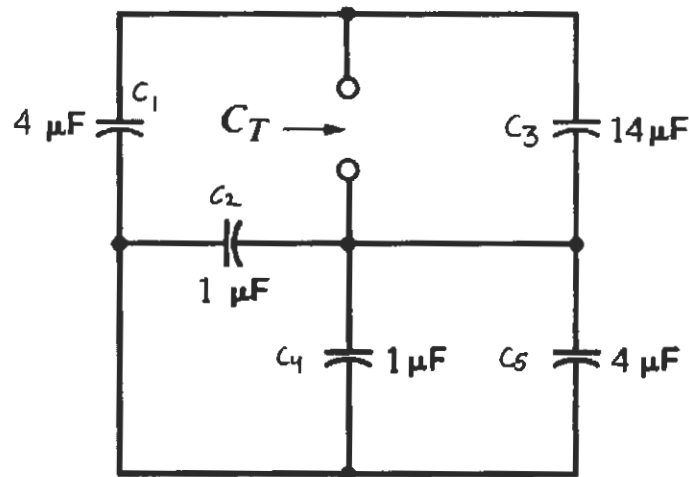

**Figure P6.47**

**Solution:** 6.47

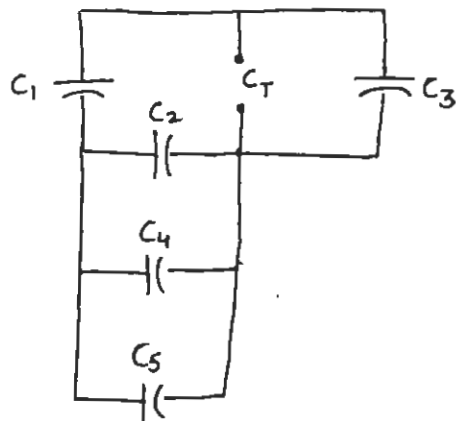

$$C_x = C_2 + C_4 + C_5$$


$$= 6 \mu F$$

$$C_T = C_3 + \frac{C_1 C_x}{C_1 + C_x}$$

$$= \left[ 14 + \frac{4 \times 6}{4 + 6} \right] \mu F$$


$$C_T = 16.4 \mu F$$

6.48 Find the total capacitance  $C_T$  of the network in Fig. P6.48.

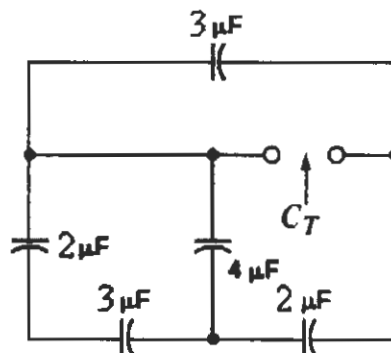

**Figure P6.48**

**Solution:** 6.48

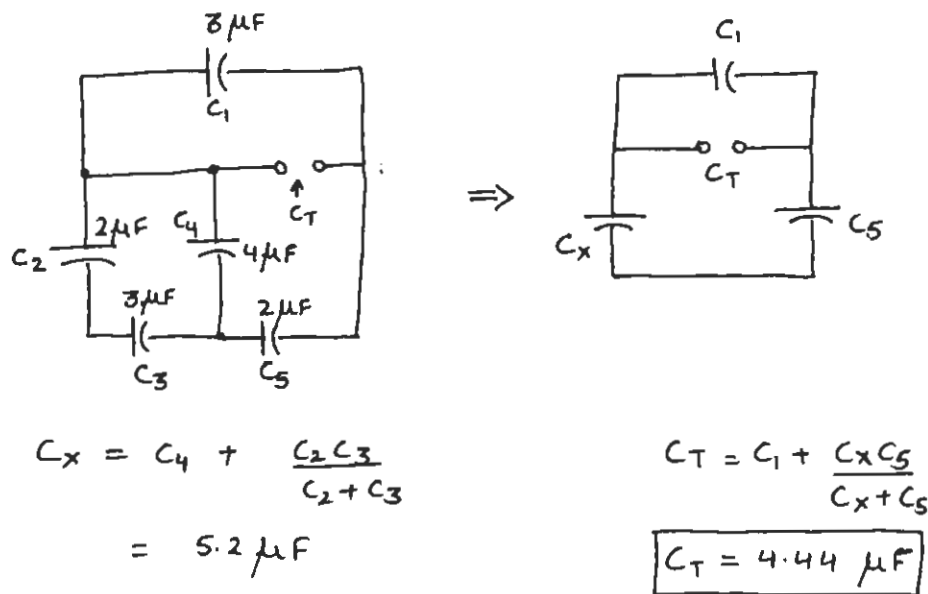

6.49 Find the total capacitance  $C_T$  shown in the network in Fig. P6.49.


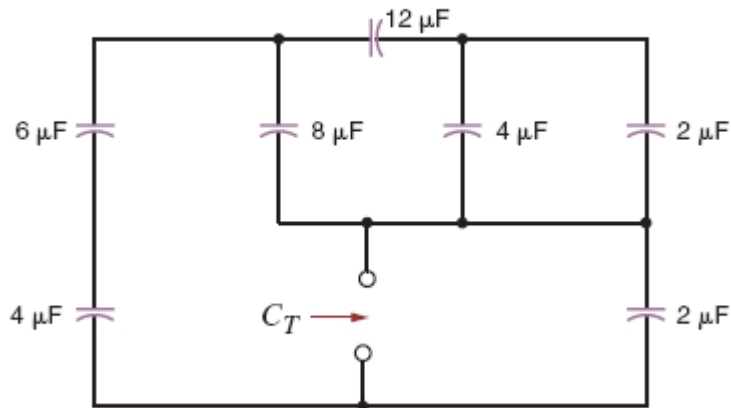


Figure P6.49

**SOLUTION:**

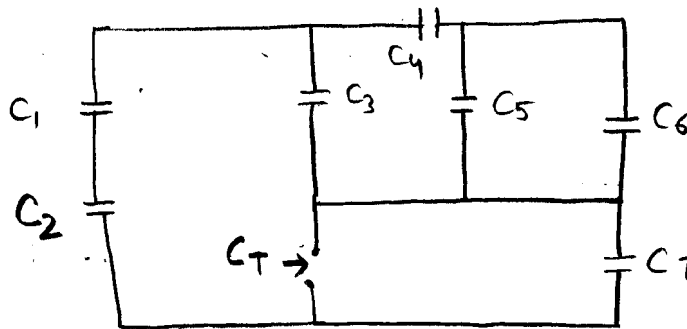

$$C_1 = 6\mu\text{F}, C_2 = 4\mu\text{F}, C_3 = 8\mu\text{F}, \\ C_4 = 12\mu\text{F}, C_5 = 4\mu\text{F}, C_6 = 2\mu\text{F}, \\ \text{and } C_7 = 2\mu\text{F}$$


$$C' = \frac{(C_5 + C_6)(C_4)}{C_4 + C_5 + C_6} + C_3$$

$$C' = \frac{(4\mu + 2\mu)(12\mu)}{12\mu + 4\mu + 2\mu} + 8\mu$$

$$C' = 12\mu\text{F}$$



Redraw:

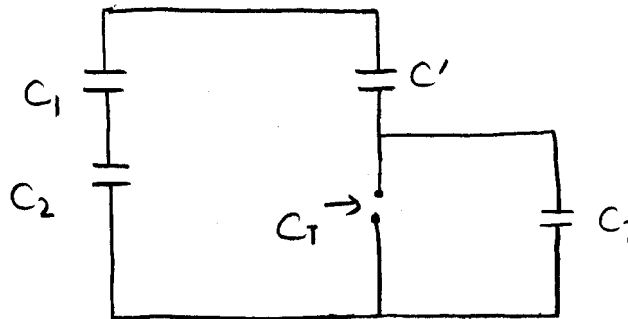

$$\frac{1}{C''} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C'}$$

$$\frac{1}{C''} = \frac{1}{6\mu} + \frac{1}{4\mu} + \frac{1}{12\mu}$$

$$\frac{1}{C''} = 500,000$$

$$C'' = 2\mu F$$

$$C_T = C'' + C_7 = 2\mu + 2\mu$$

$$C_T = 4\mu F$$

- 6.50 Compute the equivalent capacitance of the network in Fig. P6.50 if all the capacitors are  $4\ \mu\text{F}$ .


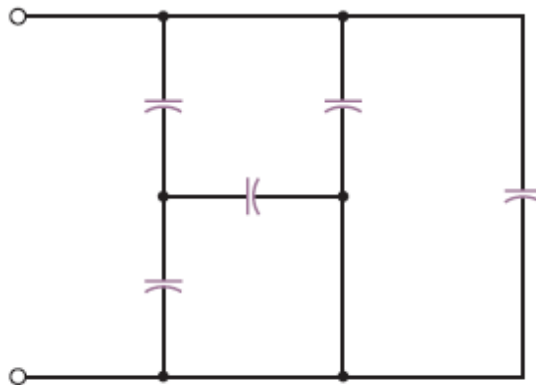



Figure P6.50

**SOLUTION:**

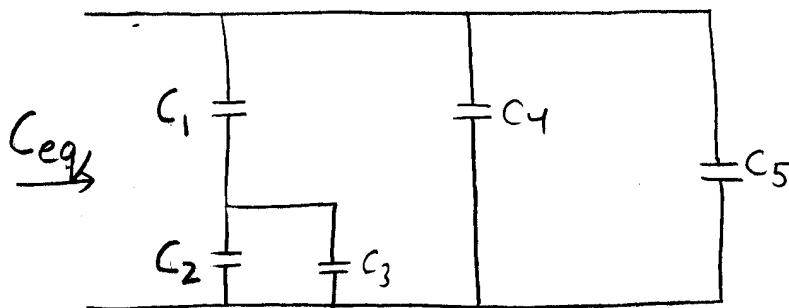

$$C_1 = C_2 = C_3 = C_4 = C_5 = 4\ \mu\text{F}$$

$$C' = C_2 + C_3 = 8\ \mu\text{F}$$

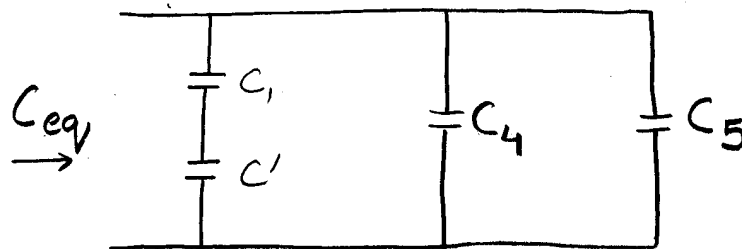

$$C'' = \frac{C_1 C'}{C_1 + C'} = 2.67\ \mu\text{F}$$

$$C_{eq} = C'' + C_4 + C_5$$

$$C_{eq} = 10.67 \mu F$$

6.51 Find  $C_T$  in the network in Fig. P6.51 if (a) the switch is open and (b) the switch is closed.


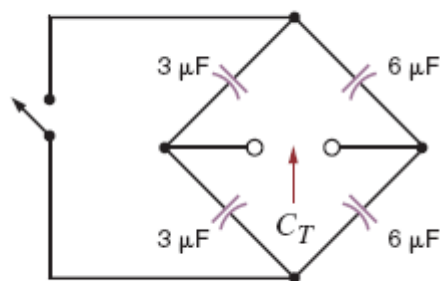
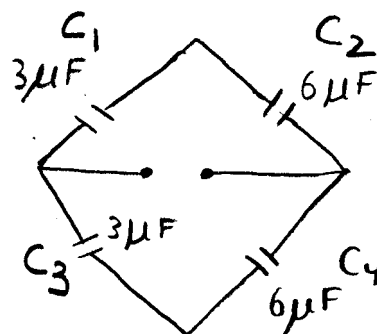


Figure P6.51

**SOLUTION:**


(a) switch open:

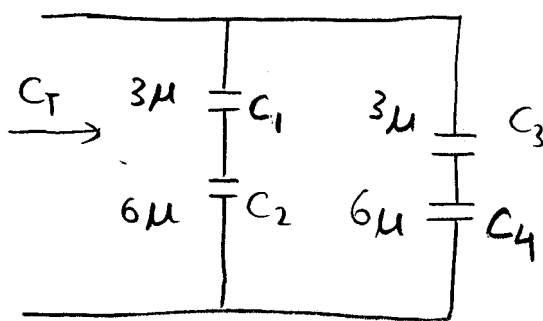


$$C' = \frac{6(3)}{6+3} = 2\mu F$$

$$C'' = 2\mu F$$

$$C_T = C' + C'' = 4\mu F$$

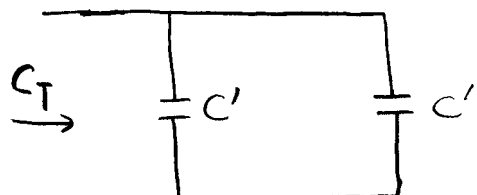


(b) Switch closed:

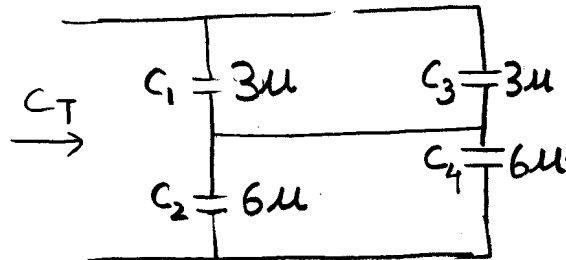

$$C' = C_1 + C_3 = 6\mu F$$


$$C'' = C_2 + C_4 = 12\mu F$$

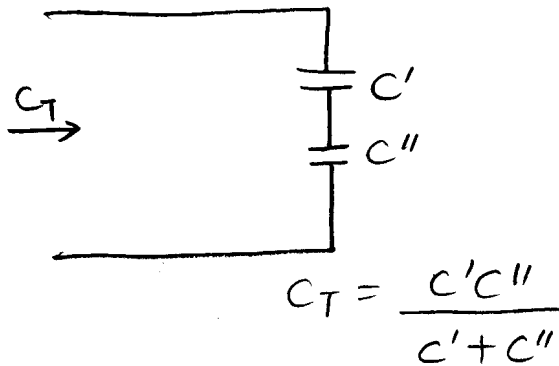

$$C_T = \frac{C' C''}{C' + C''}$$


$$C_T = 4\mu F$$


6.52 In the network in the Fig. P6.52 below, find the capacitance  $C_T$  if  
(a) the switch is open and  
(b) the switch is closed.

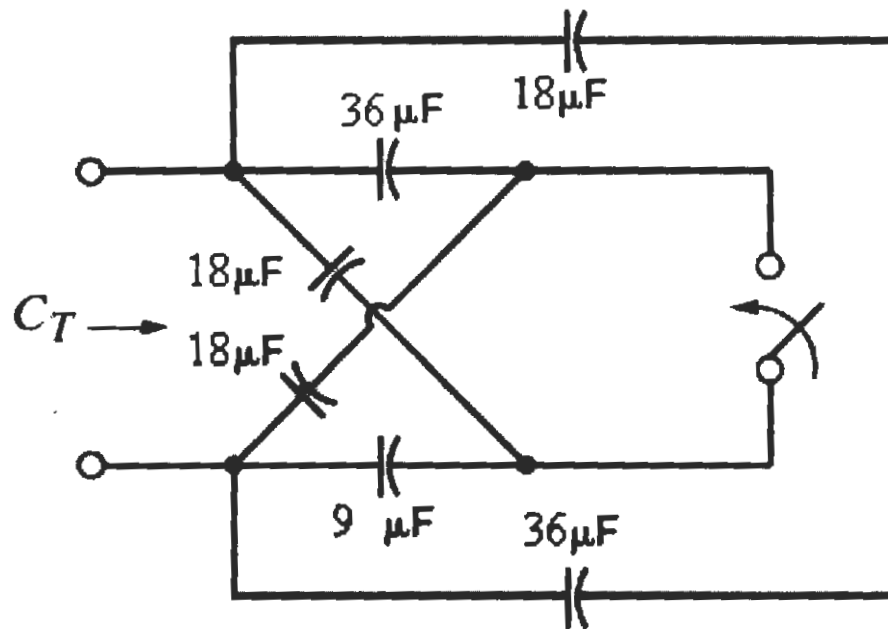

**Figure P6.52**


**Solution:** 6.52

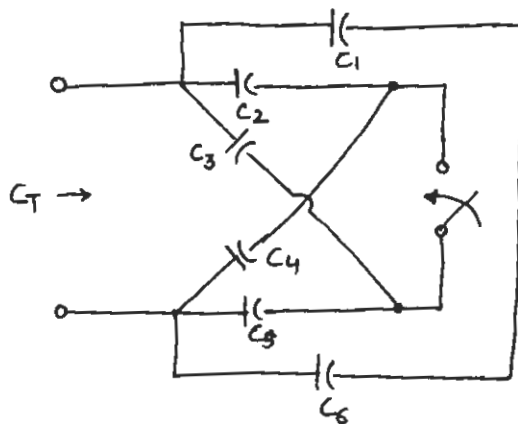

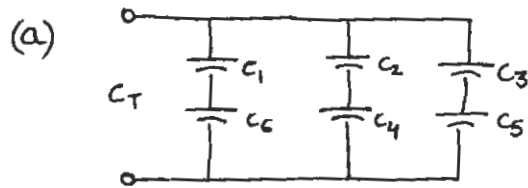

$$C_T = \frac{C_1 C_6}{C_1 + C_6} + \frac{C_2 C_4}{C_2 + C_4} + \frac{C_3 C_5}{C_3 + C_5}$$

$$C_T = 30 \mu F$$

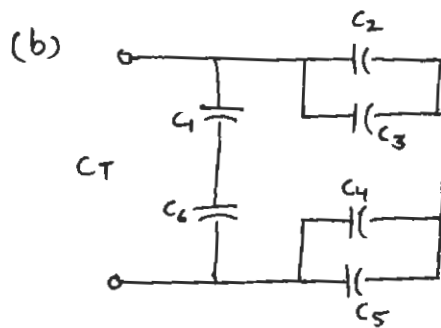

$$C_x = \frac{(C_2 + C_3)(C_4 + C_5)}{C_2 + C_3 + C_4 + C_5}$$

$$= 18 \mu F$$

$$C_T = C_x + \frac{C_1 C_6}{C_1 + C_6}$$

$$C_T = 30 \mu F$$

- 6.53 Select the value of  $C$  to produce the desired total capacitance of  $C_T = 10 \mu\text{F}$  in the circuit in Fig. P6.53.


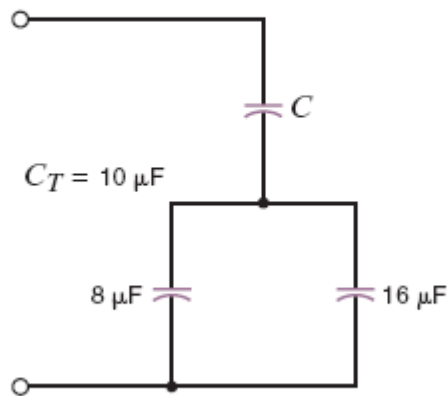


Figure P6.53

**SOLUTION:**

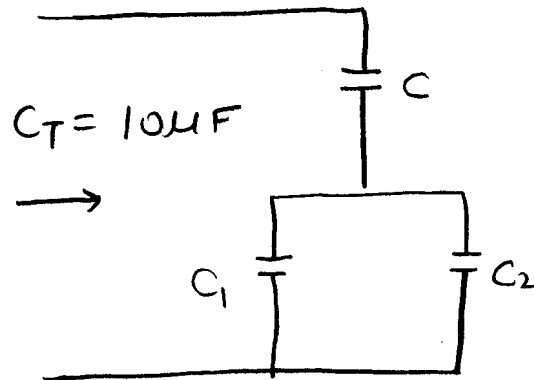

$$C_1 = 8 \mu\text{F} \text{ and } C_2 = 16 \mu\text{F}$$

$$C_T = \frac{(C_1 + C_2)(C)}{C_1 + C_2 + C}$$

$$C_T(C_1 + C_2) + CC_T = (C_1 + C_2)C$$

$$C[C_1 + C_2 - C_T] = C_T(C_1 + C_2)$$



$$C = \frac{C_T(C_1 + C_2)}{C_1 + C_2 - C_T}$$

$$C = \frac{10\mu(8\mu + 16\mu)}{8\mu + 16\mu - 10\mu}$$

$$C = 17.14\mu F$$

- 6.54 Select the value of  $C$  to produce the desired total capacitance of  $C_T = 1\ \mu\text{F}$  in the circuit in Fig. P6.54.

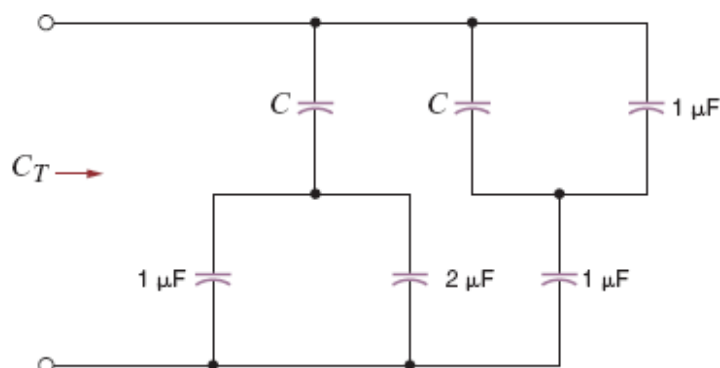
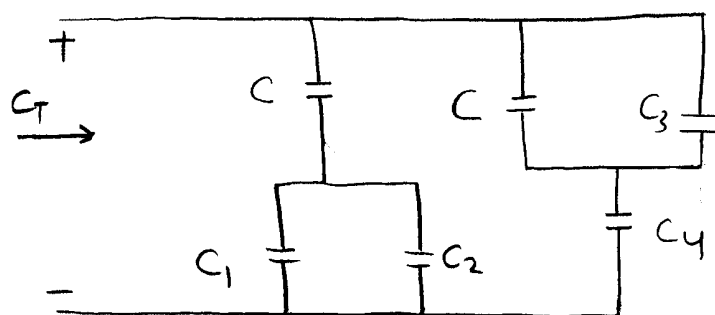


Figure P6.54

**SOLUTION:**

$$C_1 = 1\ \mu\text{F}, C_2 = 2\ \mu\text{F}, C_3 = 1\ \mu\text{F}, C_4 = 1\ \mu\text{F}$$

$$C_x = \frac{(C + C_3)(C_4)}{C + C_3 + C_4}$$

$$C_y = \frac{(C_1 + C_2)(C)}{C + C_1 + C_2}$$

$$C_T = C_x + C_y$$

$$C_T = \frac{(C + C_3)(C_4)}{C + C_3 + C_4} + \frac{(C_1 + C_2)(C)}{C + C_1 + C_2}$$

$$1\mu = \frac{(C+1\mu)(1\mu)}{C+1\mu+1\mu} + \frac{(1\mu+2\mu)(C)}{C+1\mu+2\mu}$$

$$1\mu = \frac{(C+1\mu)(1\mu)}{C+2\mu} + \frac{(3\mu)(C)}{C+3\mu}$$

$$1 = \frac{C+1}{C+2} + \frac{3C}{C+3}$$

Note:  $C$  is in  $\mu F$

$$C+2 = C+1 + \frac{3C(C+2)}{C+3}$$

$$(C+2)(C+3) = (C+1)(C+3) + 3C(C+2)$$

$$C^2 + 5C + 6 = C^2 + 4C + 3 + 3C^2 + 6C$$


$$3C^2 + 5C - 3 = 0$$

$$C = \frac{-5 \pm \sqrt{25 - 4(3)(-3)}}{2(3)}$$

$$C = \frac{-5 \pm 7.81}{6}$$


$$C = 468 \text{ nF}$$

6.55 The two capacitors in Figure were charged and then connected as shown in Fig. P6.55. Determine (a) the equivalent capacitance, (b) the initial voltage at the terminals, and (c) the total energy stored in the network.

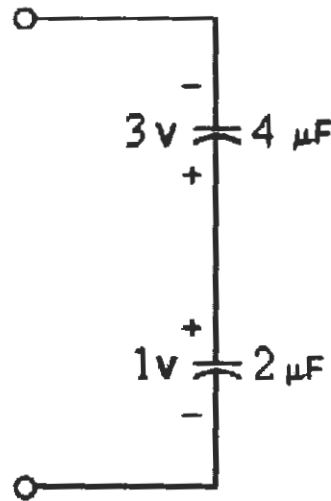

**Figure P6.55**

**Solution:** 6.55

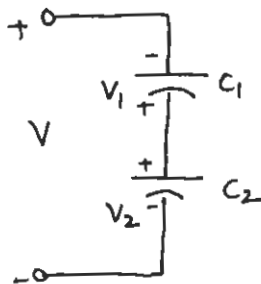

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = 1.33 \mu F$$


$$V = -3 + 1 = -2 V$$

$$V = -2 V$$

$$W = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

$$W = 19 \mu J$$

6.56 The two capacitors shown in Fig. P6.56 have been connected for some time and have reached their present values, Find  $V_o$ .

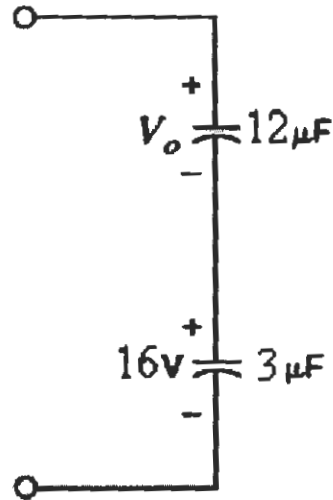

**Figure P6.56**


**Solution:** 6.56

Identical charge on each capacitor.

$$Q = CV = (3 \times 10^{-6})(16) = (12 \times 10^{-6}) V_o$$


$$\Rightarrow \boxed{V_o = 4.0 \text{ V}}$$

6.57 The three capacitors shown Fig. P6.57 have been connected for some time and have reached their present values. Find (a)  $V_1$  and (b)  $V_2$ .

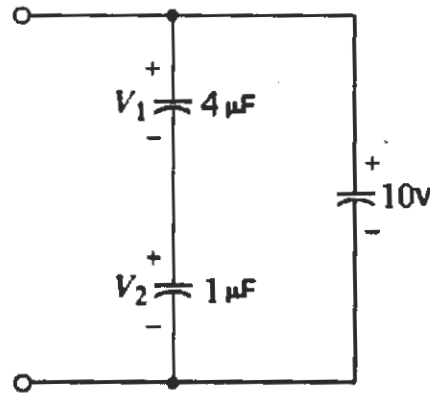

**Figure P6.57**

**Solution:** 6.57

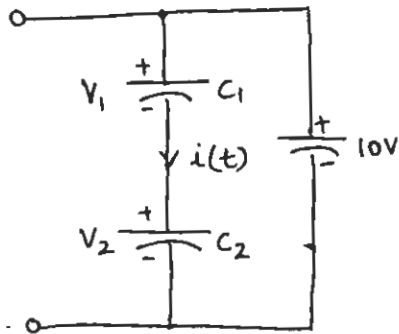

$$C_1 = 4\mu\text{F}, \quad C_2 = 1\mu\text{F}$$

$$V_1 = \frac{1}{C_1} \int i dt \quad V_2 = \frac{1}{C_2} \int i dt$$

$$\frac{V_1}{V_2} = \frac{C_2}{C_1} = \frac{1}{4}$$

$$V_1 + V_2 = 10\text{V}$$

$$\boxed{V_1 = 2\text{V}}$$

$$\boxed{V_2 = 8\text{V}}$$

6.58 Determine the inductance at terminals  $A$ - $B$  in the network in Fig. 6.58.


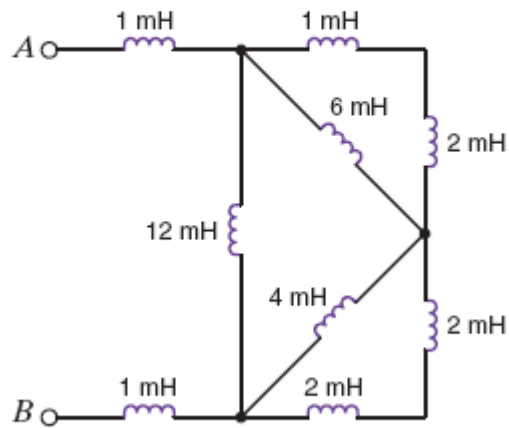


Figure P6.58

**SOLUTION:**

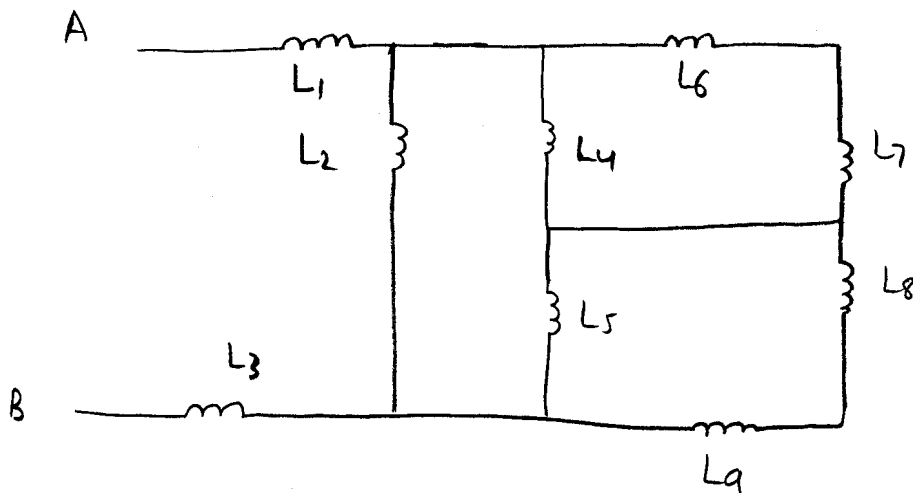

$$L_1 = L_3 = L_6 = 1 \text{ mH}$$

$$L_2 = 12 \text{ mH}$$

$$L_4 = 6 \text{ mH}, L_5 = 4 \text{ mH}$$

$$L_7 = L_8 = L_9 = 2 \text{ mH}$$

$$L_a = L_6 + L_7 = 3 \text{ mH}$$

$$L_b = \frac{L_4 L_a}{L_4 + L_a} = 2 \text{ mH}$$

$$L_c = L_8 + L_9 = 4 \text{ mH}$$

$$L_d = \frac{L_c L_5}{L_c + L_5} = 2 \text{ mH}$$

$$L_e = \frac{L_2 (L_b + L_d)}{L_2 + L_b + L_d}$$


$$L_e = 3 \text{ mH}$$

$$L_{AB} = L_1 + L_3 + L_e$$

$$L_{AB} = 5 \text{ mH}$$




6.59 Determine the inductance at terminals  $A$ - $B$  in the network in Fig P6.59.

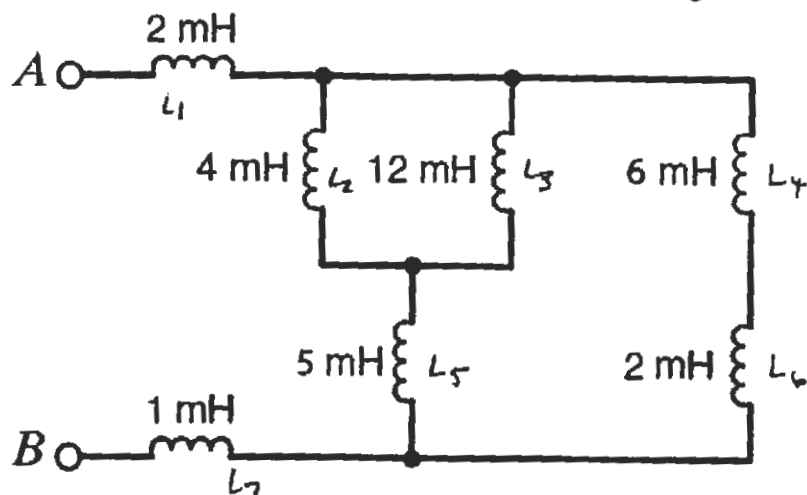

**Figure P6.59**

**Solution:** 6.59

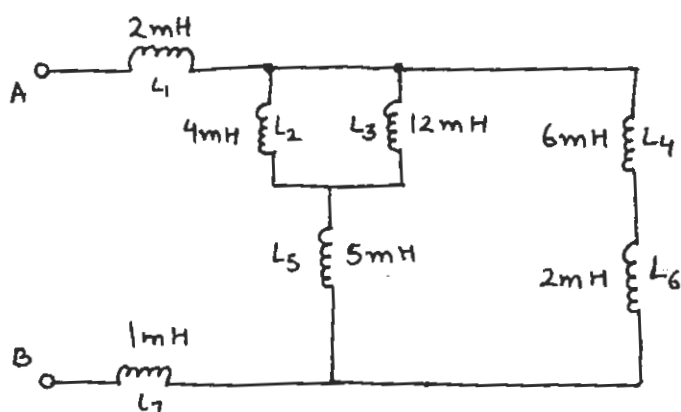

$$L_x = L_5 + \frac{L_2 L_3}{L_2 + L_3}$$

$$= 8 \text{ mH}$$

$$L_y = L_4 + L_6$$

$$= 8 \text{ mH}$$

$$L_{AB} = L_1 + L_7 + \frac{L_x L_y}{L_x + L_y}$$

$$\boxed{L_{AB} = 9 \text{ mH}}$$

6.60 Find the total inductance at the terminals of the network in Fig. P6.60.


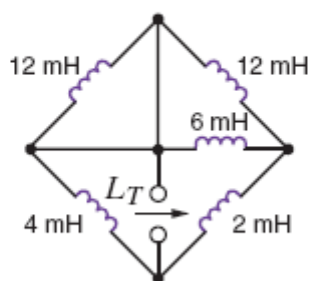


Figure P6.60

**SOLUTION:**

Redraw circuit:

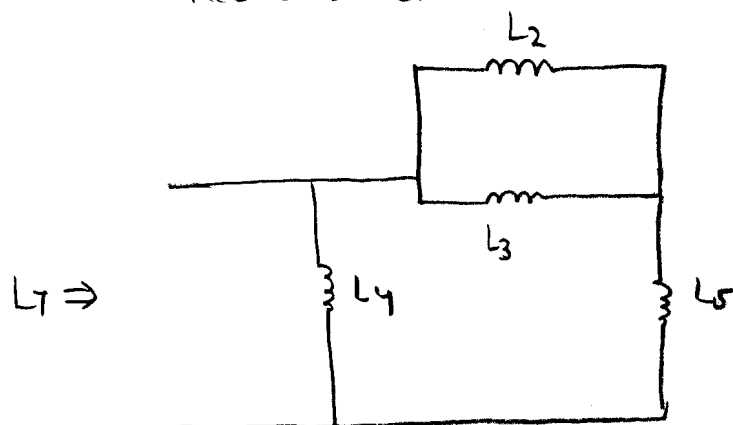

$$L_2 = 12 \text{ mH}, L_3 = 6 \text{ mH}, L_4 = 4 \text{ mH}, \text{ and } L_5 = 2 \text{ mH}$$

note:  $L_1 = 12 \text{ mH}$  was shorted.

$$L_T = [(L_2 || L_3) + L_5] || L_4$$

$$L_T = [(12 \text{ m} || 6 \text{ m}) + 2 \text{ m}] || 4 \text{ m}$$

$$L_T = \left[ \frac{12 \text{ m}(6 \text{ m})}{12 \text{ m} + 6 \text{ m}} + 2 \text{ m} \right] || 4 \text{ m}$$

$$L_T = 6\text{m} \parallel 4\text{m}$$

$$L_T = 2.4\text{mH}$$

- 6.61 Compute the equivalent inductance of the network in Fig. P6.61 if all inductors are 4 mH.



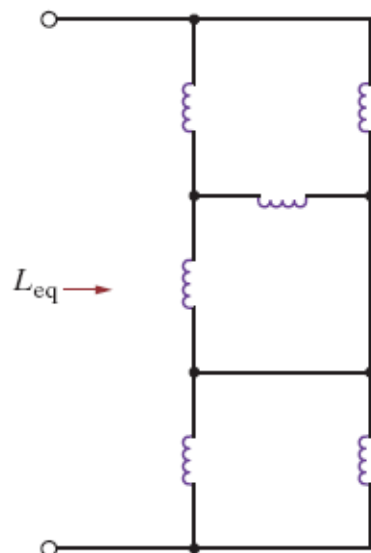
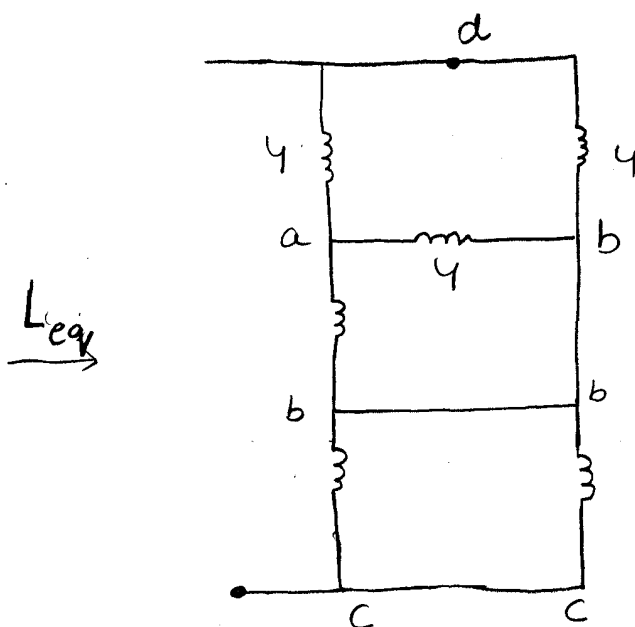


Figure P6.61

**SOLUTION:**

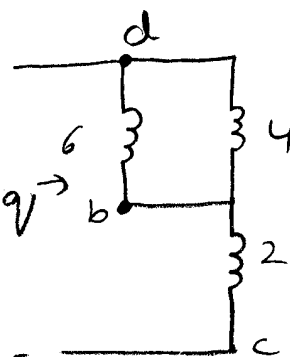

Redrawing

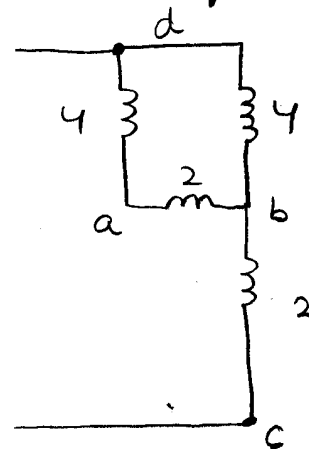

$$L_a = \frac{L_1 L_2}{L_1 + L_2} = 2 \text{ mH}$$

$$L_b = \frac{L_3 L_4}{L_3 + L_4} = 2 \text{ mH}$$

$$L_{eq} = [(6 \parallel 4) + 2] \text{ mH}$$

$$L_{eq} = \frac{6(4)}{2} + 2$$

$$= 4.4 \text{ mH}$$

**6.62** Find  $L_T$  in the network in Fig. P6.62 (a) with the switch open and (b) with the switch closed. All inductors are 12 mH.


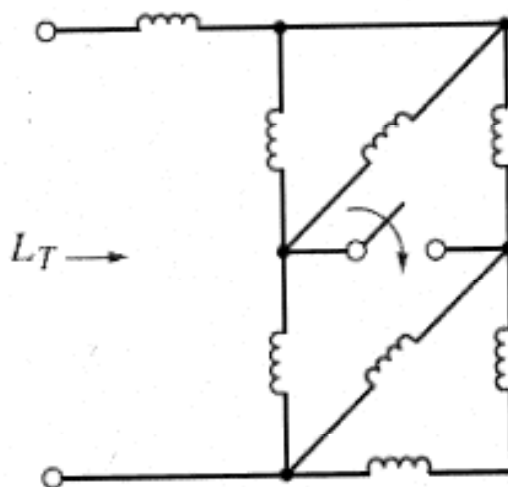


Figure P6.62

Solution: 6.62

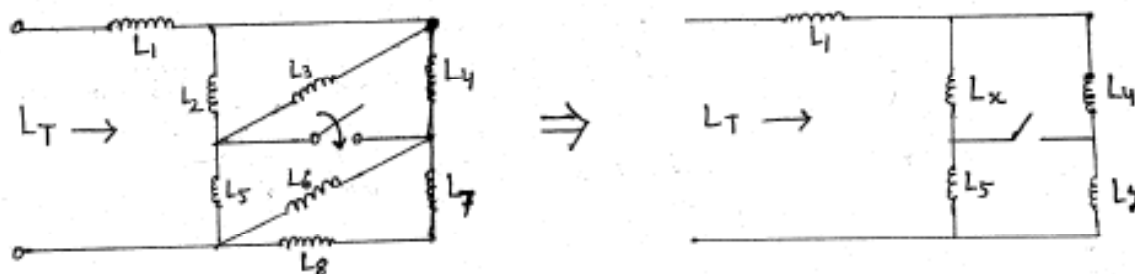

$$L_x = \frac{L_2 L_3}{L_2 + L_3} = 6 \text{ mH}$$

$$L_y = \frac{L_6 (L_7 + L_8)}{L_6 + L_7 + L_8} = 8 \text{ mH}$$


$$(a) \quad L_T = L_1 + \frac{(L_x + L_5)(L_4 + L_7)}{L_x + L_5 + L_4 + L_7} = 21.47 \text{ mH}$$

$$\boxed{L_T = 21.5 \text{ mH}}$$

$$(b) \quad L_T = L_1 + \frac{L_x L_4}{L_x + L_4} + \frac{L_5 L_7}{L_5 + L_7} = 20.8 \text{ mH}$$



$$\boxed{L_T = 20.8 \text{ mH}}$$

6.63 Given the network shown in Fig. P6.63, find (a) the equivalent inductance at terminals  $A$ - $B$  with terminals  $C$ - $D$  short circuited, and (b) the equivalent inductance at terminals  $C$ - $D$  with terminals  $A$ - $B$  open circuited.

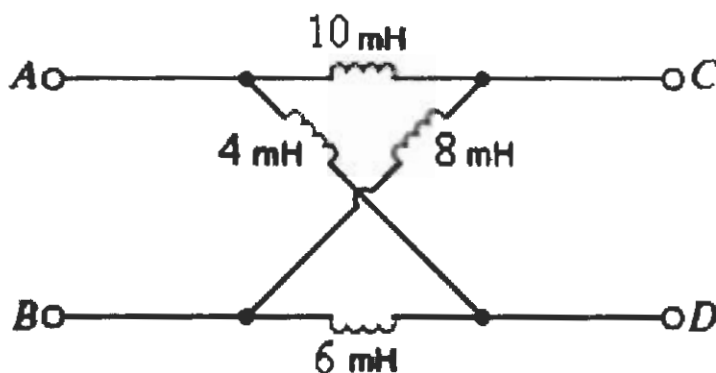


**Figure P6.63**

**Solution:** 6.63

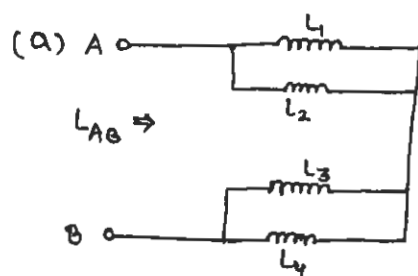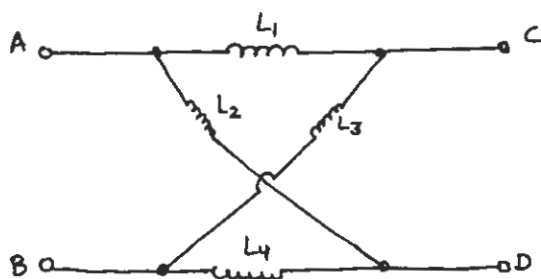

$$L_{AB} = \frac{L_1 L_2}{L_1 + L_2} + \frac{L_3 L_4}{L_3 + L_4}$$


$$L_{AB} = 6.29 \text{ mH}$$

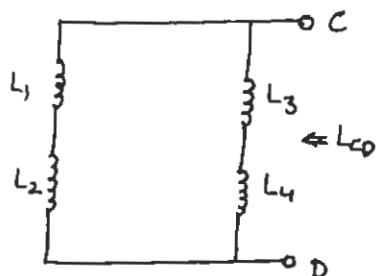

$$L_{CD} = \frac{(L_1 + L_2)(L_3 + L_4)}{L_1 + L_2 + L_3 + L_4}$$


$$L_{CD} = 7 \text{ mH}$$

**6.64** Find the value of  $L$  in the network in Fig. P6.64 so that the total inductance  $L_T$  will be 2.25 mH.

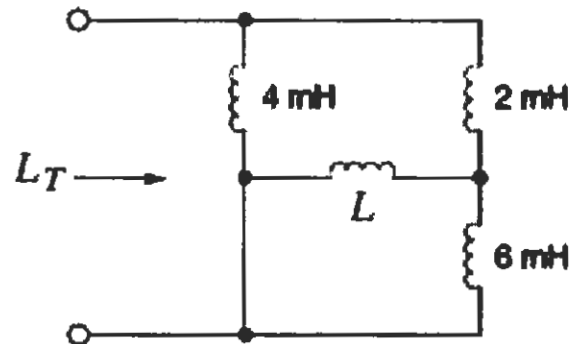

**Figure P6.64**

**Solution:** 6.64

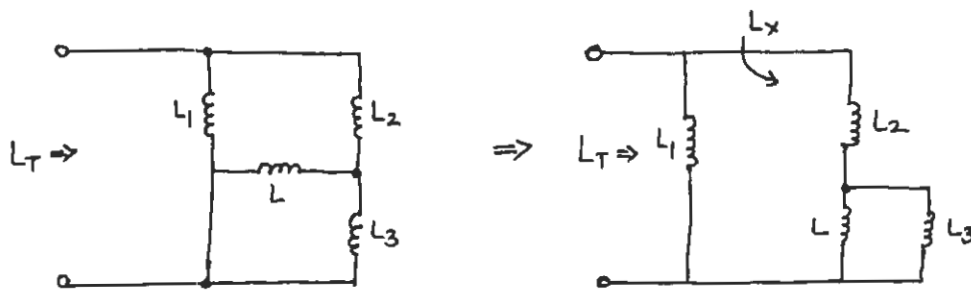

$$L_x = L_2 + \frac{L L_3}{L + L_3} = 2 + \frac{6L}{6 + L} \text{ mH}$$

$$L_T = \frac{L_1 L_x}{L_1 + L_x} = 2.25 \text{ mH} \Rightarrow \boxed{L = 6.60 \text{ mH}}$$



6.65 Find the value of  $L$  in the network in Fig. P6.65 so that the value of  $L_T$  will be 2 mH.


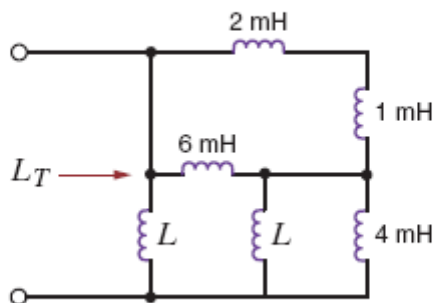


Figure P6.65

**SOLUTION:**

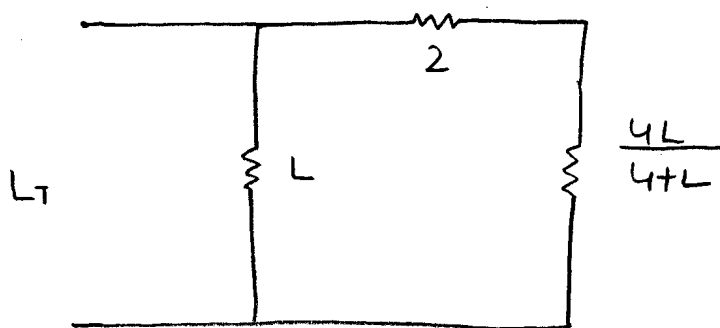

$$L_T = \left( 2 + \frac{4L}{4+L} \right) \parallel L$$

$$L_T = \frac{\left( 2 + \frac{4L}{4+L} \right) L}{L + 2 + \frac{4L}{4+L}}$$

$$L_T = \frac{2L + \frac{4L^2}{4+L}}{\frac{L(4+L) + 2(4+L) + 4L}{4+L}}$$

$$L_T = \frac{2L(4+L) + 4L^2}{4+L} = \frac{4L + L^2 + 8 + 2L + 4L}{4+L}$$

$$L_T = \frac{8L + 2L^2 + 4L^2}{8L + L^2 + 8 + 2L}$$

$$L_T = \frac{6L^2 + 8L}{L^2 + 10L + 8}$$

$$L_T = \frac{6L^2 + 8L}{L^2 + 10L + 8}$$

$$6L^2 + 8L = 2L^2 + 20L + 16$$

$$4L^2 - 12L - 16 = 0$$

$$L^2 - 3L - 4 = 0$$


$$(L-4)(L+1) = 0$$

$$L = 4, \quad L = -1$$

$$L = 4 \text{ mH}$$

6.66 A 20-mH inductor and a 12-mH inductor are connected in series with a 1-A current source. Find (a) the equivalent inductance and (b) the total energy stored.

**SOLUTION:**

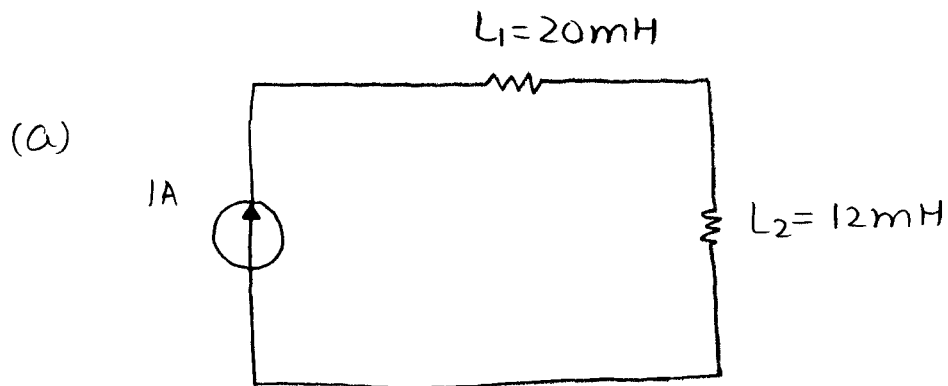

$$L_{eq} = L_1 + L_2 = 20\text{m} + 12\text{m}$$

$$L_{eq} = 32\text{mH}$$

(b)

$$W_{total} = W_1 + W_2$$

$$W_{total} = \frac{1}{2} L_1 I^2 + \frac{1}{2} L_2 I^2$$

$$W_{total} = \frac{1}{2} (20\text{m}) (1)^2 + \frac{1}{2} (12\text{m}) (1)^2$$

$$W_{total} = 16\text{mJ}$$

6.67 For the network in Fig. P6.67,  $v_S(t) = 120 \cos 377t$  V.  
Find  $v_O(t)$ .


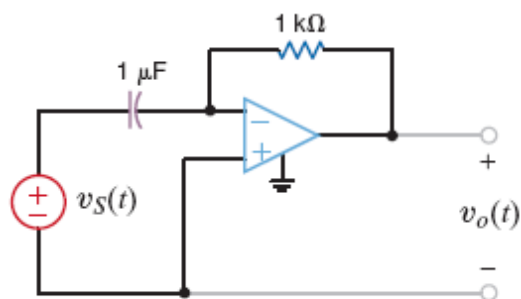


Figure P6.67

**SOLUTION:**

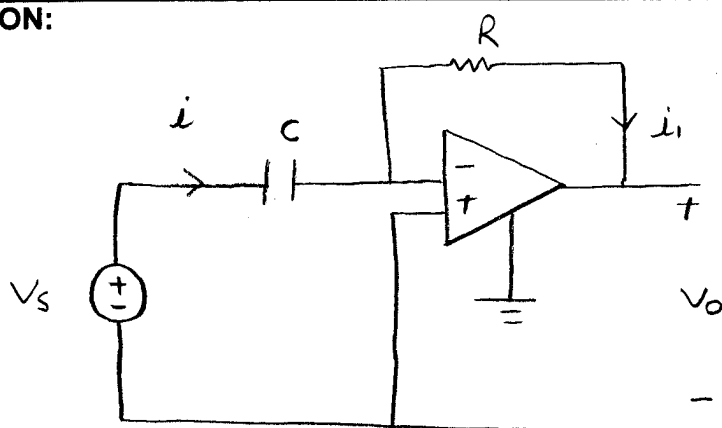

$$C = 1 \mu\text{F} \quad \text{and} \quad R = 1 \text{ k}\Omega$$

$$V_S(t) = 120 \cos 377t \text{ V}$$

$$i = i_1 \quad (\text{ideal op-amp})$$

$$C \frac{dV_S}{dt} = -\frac{V_O}{R}$$

$$V_O = -RC \frac{dV_S}{dt}$$

$$V_O = -(1\text{K})(1\mu) [-120(377) \cos 377t]$$

$$V_o(t) = 45.24 \sin 377 t \text{ V}$$

6.68 For the network in Fig. P6.68 choose  $C$  such that

$$v_o = -10 \int v_s dt.$$


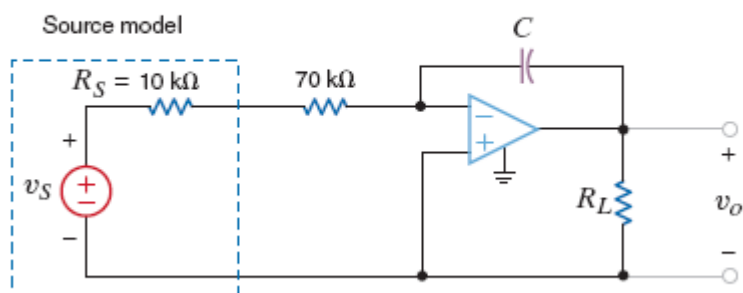


Figure P6.68

**SOLUTION:**

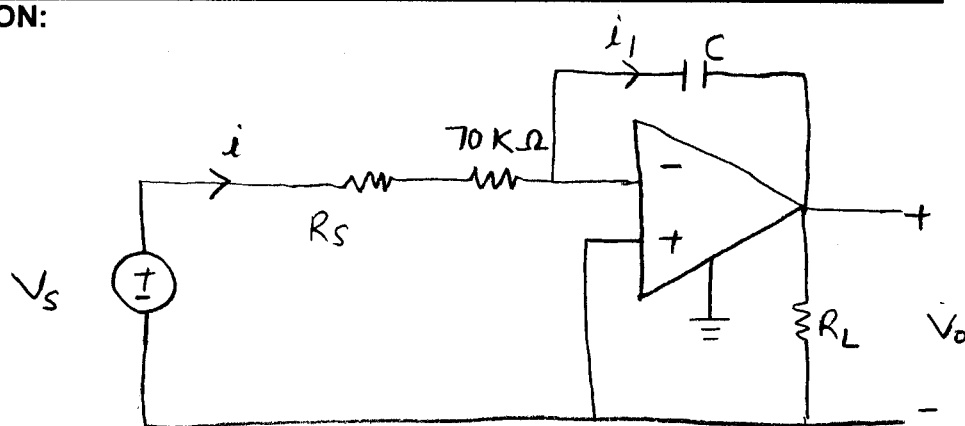

$$V_o = -10 \int v_s dt$$

$$R_s = 10 \text{ k}\Omega$$

$$R_{eq} = R_s + 70 \text{ k}\Omega = 10 \text{ k}\Omega + 70 \text{ k}\Omega$$

$$R_{eq} = 80 \text{ k}\Omega$$


$$i = i_1 \quad (\text{ideal op-amp})$$

$$\frac{V_s - 0}{R_{eq}} = -C \frac{dV_o}{dt}$$

$$V_o = -\frac{1}{R_{eq}C} \int V_s dt$$


$$R_{eq}C = \frac{1}{10}$$
$$C = 1.25 \mu F$$

**6.69** For the network in the Fig. P6.69 below,  $v_{s_1}(t) = 80 \cos 324t$  V and  $v_{s_2}(t) = 40 \cos 324t$  V. Find  $v_o(t)$ .

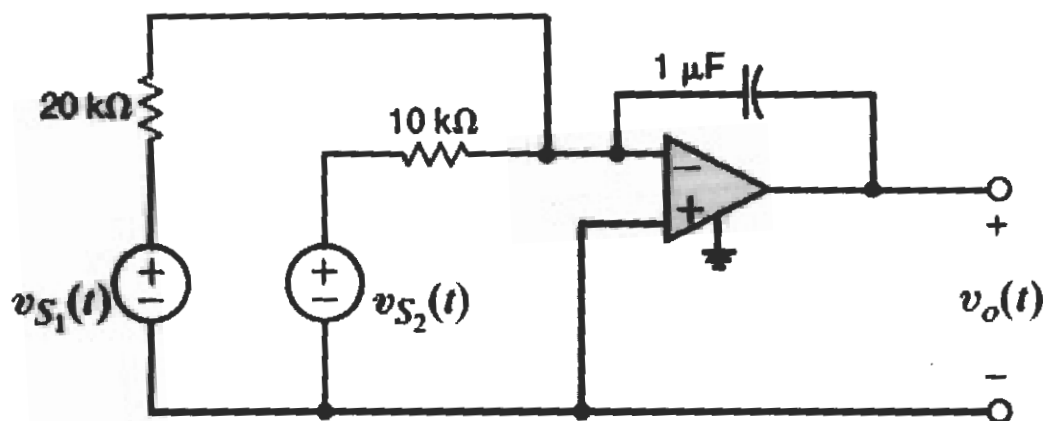

**Figure P6.69**

**Solution:** 6.69

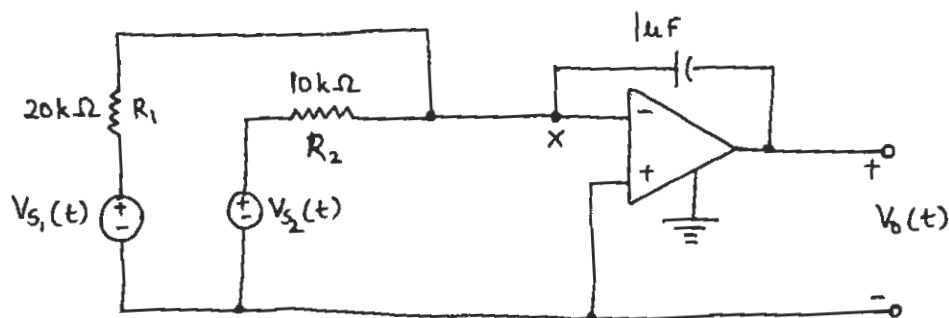


$$\frac{V_{s_1}}{R_1} + \frac{V_{s_2}}{R_2} = -C \frac{dV_o}{dt}$$

$$\therefore V_o(t) = -\frac{1}{C} \int \left( \frac{V_{s_1}}{R_1} + \frac{V_{s_2}}{R_2} \right) dt$$

$$V_o(t) = -24.7 \sin 324t \text{ V}$$




**6.70** The circuit shown in the Fig. P6.70 below is known as a “Deboo” integrator. Express the output voltage in terms of the input voltage and circuit parameters.

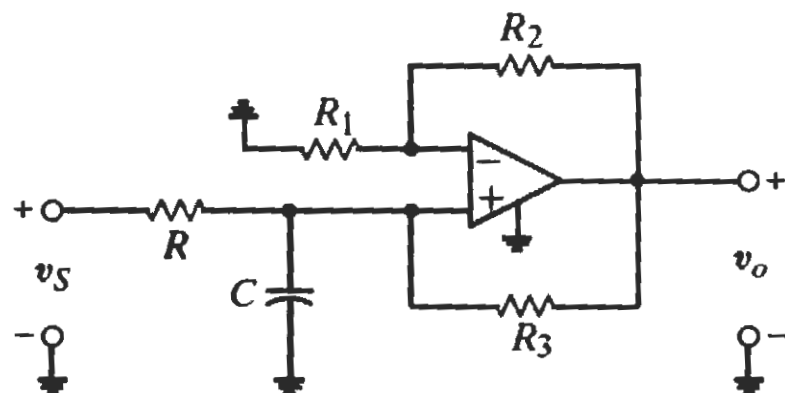

**Figure P6.70**

**Solution:** 6.70

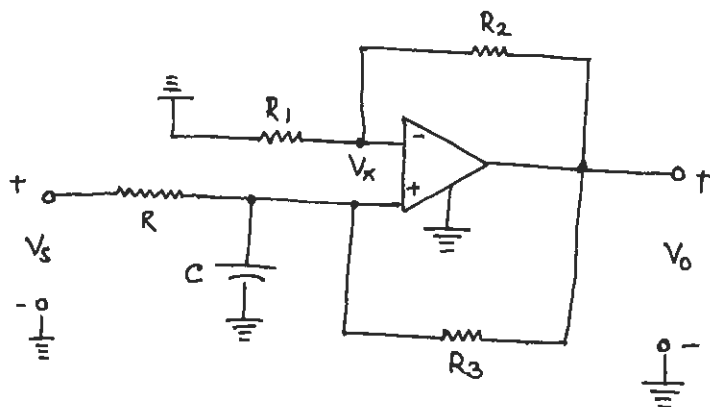

$$V_x = V_o \frac{R_1}{R_1 + R_2} = \alpha V_o$$

$$\frac{V_s - V_x}{R} = C \frac{dV_x}{dt} + \frac{V_x - V_o}{R_3}$$

$$\Rightarrow V_s = \frac{R_1 R C}{R_1 + R_2} \frac{dV_o}{dt} + \frac{V_o R_1}{(R_1 + R_2)} \left( \frac{R}{R_3} + 1 \right) - \frac{V_o R}{R_3}$$

$$V_o = \left( \frac{R_1 + R_2}{R_1} \right) \frac{1}{RC} \int \left\{ V_s(t) + \left[ \frac{R}{R_3} - \frac{R_1(R + R_3)}{(R_1 + R_2)R_3} \right] V_o \right\} dt$$

6.71 An integrator is required that has the following performance


$$V_o = 10^6 \int V_s dt$$

where the capacitor values must be greater than 10 nF and the resistor values must be greater than 10 k $\Omega$ .

(a) If  $\pm 20$  V supplies are used, what are the maximum and minimum values of  $V_o$ ?

(b) Suppose  $V_s = 1$  V. What is the rate of changes of  $V_o$ ?

**Solution:** 6.71

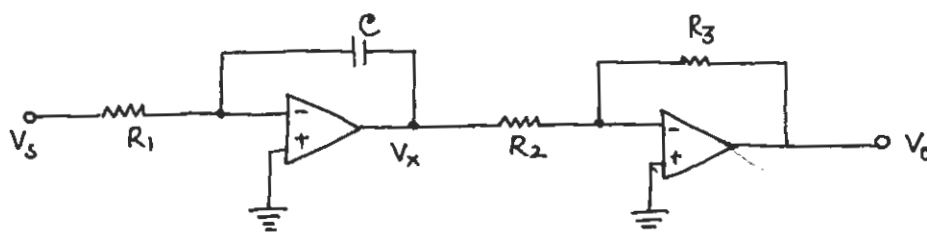

$$V_x = -\frac{1}{R_1 C} \int V_s dt \quad V_o = -\frac{R_3}{R_2} V_x$$

$$V_o = \frac{R_3}{C R_1 R_2} \int V_s dt$$

Arbitrarily select :  $C = 20$  nF,  $R_1 = 20$  k $\Omega$ ,  $R_2 = 20$  k $\Omega$

$$R_3 = 8$$
 M $\Omega$

(a)  $V_o$  cannot exceed the supplies and it is limited to  $\pm 20$  V

$$V_{o \text{ max}} = 20 \text{ V}$$

$$V_{o \text{ min}} = -20 \text{ V}$$

(b)  $V_s = 1$  V

$$V_o(t) = 10^6 \int dt$$

$$= 10^6 t$$

$$\frac{dV_o}{dt} = 10^6 \text{ V/s}$$

- 6.72 A driverless automobile is under development. One critical issue is braking, particularly at red lights. It is decided that the braking effort should depend on distance to the light (if you're close, you better stop now) and speed (if you're going fast, you'll need more brakes). The resulting design equation is

$$\text{braking effort} = K_1 \left[ \frac{dx(t)}{dt} \right] + K_2 x(t)$$

where  $x$ , the distance from the vehicle to the intersection, is measured by a sensor whose output is proportional to  $x$ ,  $v_{\text{sense}} = \alpha x$ . Use superposition to show that the circuit in Fig. P6.72 can produce the braking effort signal.


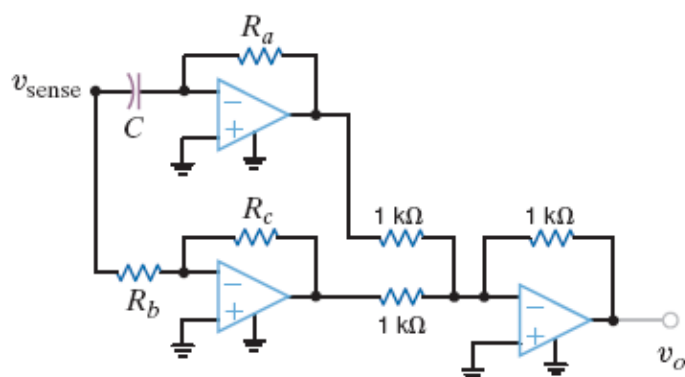


Figure P6.72

**SOLUTION:**

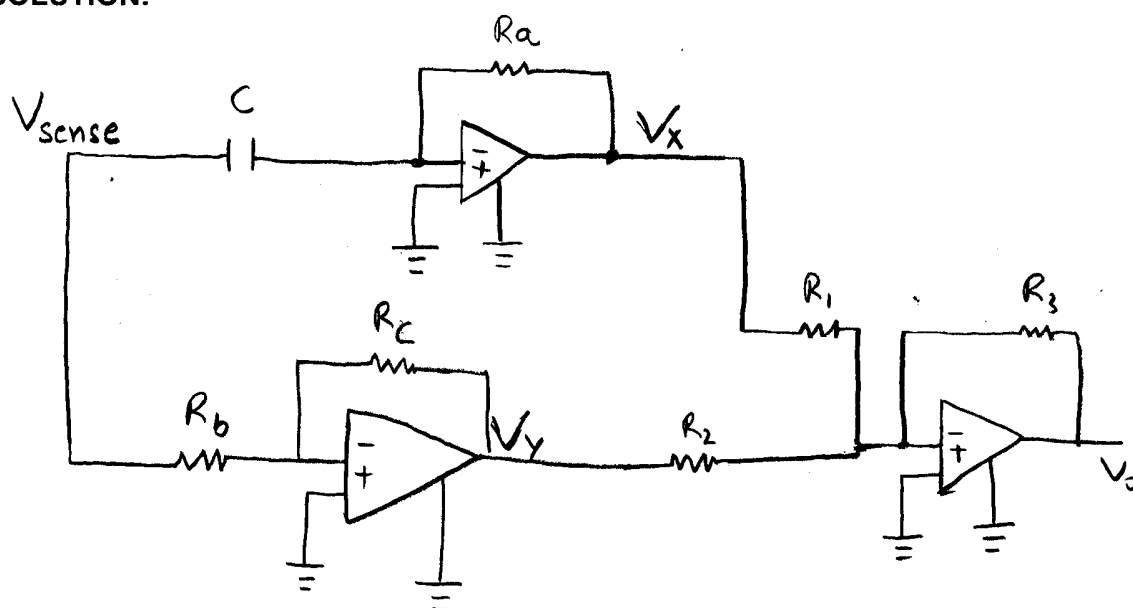

$$V_x = -R_a C \frac{dV_{\text{sense}}}{dt}$$

$$V_y = -\frac{R_c}{R_b} V_{\text{sense}}$$

$$V_o = \frac{-R_3}{R_1} V_x - \frac{R_3}{R_2} V_y$$


$$V_o = \alpha \frac{R_3 R_a C}{R_1} \frac{dx}{dt} + \frac{R_3}{R_2} \frac{R_c}{R_b} \alpha x$$

$$K_1 = \frac{\alpha R_3 R_a C}{R_1}$$


$$K_2 = \frac{R_3 R_c}{R_2 R_b}$$

**6FE-1** Given three capacitors with values  $2\text{-}\mu\text{F}$ ,  $4\text{-}\mu\text{F}$ , and  $6\text{-}\mu\text{F}$ , can the capacitors be interconnected so that the combination is an equivalent  $3\text{-}\mu\text{F}$  capacitor?

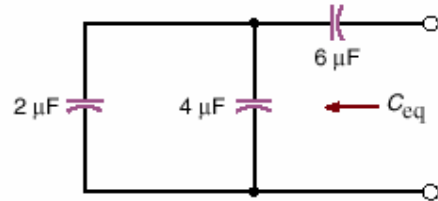
a. Yes. The capacitors should be connected as shown.



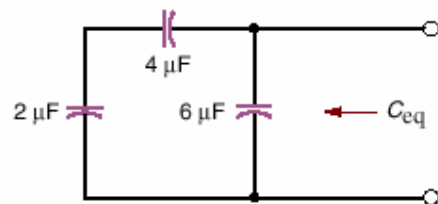b. Yes. The capacitors should be connected as shown.



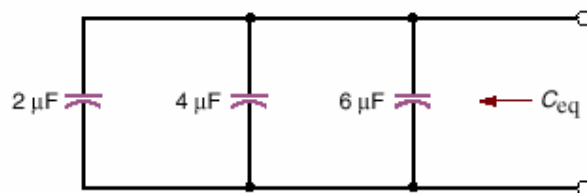c. Yes. The capacitors should be connected as shown.




d. No. An equivalent capacitance of  $3\text{-}\mu\text{F}$  is not possible with the given capacitors.
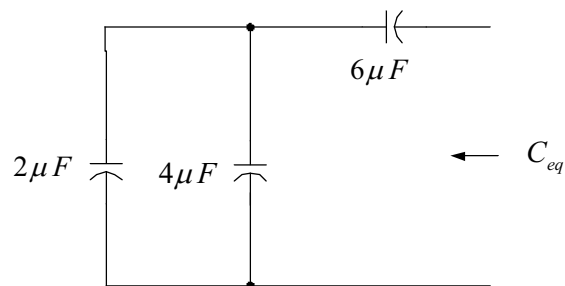
### SOLUTION:

The correct answer is *a*.

Yes. The capacitors should be connected as shown.



$$C_{eq} = \frac{6\mu(6\mu)}{6\mu + 6\mu} = 3\mu F$$

**6FE-2** The current pulse shown in Fig. 6PFE-2 is applied to a 1- $\mu\text{F}$  capacitor. What is the energy stored in the electric field of the capacitor?

a.  $w(t) = \begin{cases} 0 \text{ J}, t \leq 0 \\ 10 \times 10^6 t^2 \text{ J}, 0 < t \leq 1 \mu\text{s} \\ 10 \mu\text{J}, t > 1 \mu\text{s} \end{cases}$

b.  $w(t) = \begin{cases} 0 \text{ J}, t \leq 0 \\ 6 \times 10^6 t \text{ J}, 0 < t \leq 1 \mu\text{s} \\ 6 \mu\text{J}, t > 1 \mu\text{s} \end{cases}$

c.  $w(t) = \begin{cases} 0 \text{ J}, t \leq 0 \\ 18 \times 10^6 t^2 \text{ J}, 0 < t \leq 1 \mu\text{s} \\ 18 \mu\text{J}, t > 1 \mu\text{s} \end{cases}$

d.  $w(t) = \begin{cases} 0 \text{ J}, t \leq 0 \\ 30 \times 10^6 t \text{ J}, 0 < t \leq 1 \mu\text{s} \\ 30 \mu\text{J}, t > 1 \mu\text{s} \end{cases}$

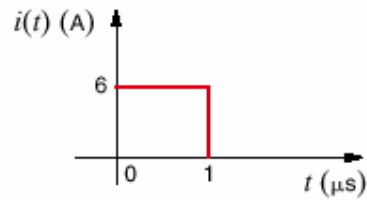


Figure 6PFE-2

### SOLUTION:

The correct answer is *c*.

$$q(t) = \int i(t) dt$$

$$q(t) = \begin{cases} 0 \text{ C}, t \leq 0 \\ 6t \text{ C}, 0 < t \leq 1 \mu\text{s} \\ 6 \mu\text{C}, t > 1 \mu\text{s} \end{cases}$$

$$v(t) = \frac{q(t)}{C}$$


$$v(t) = \begin{cases} 0 \text{ V}, t \leq 0 \\ 6 \times 10^6 t \text{ V}, 0 < t \leq 1 \mu\text{s} \\ 6 \text{ V}, t > 1 \mu\text{s} \end{cases}$$

$$w(t) = \frac{1}{2} C v^2(t)$$

$$w(t) = \begin{cases} 0 \text{ J}, t \leq 0 \\ 18 \times 10^6 t^2 \text{ J}, 0 < t \leq 1 \mu\text{s} \\ 18 \mu\text{J}, t > 1 \mu\text{s} \end{cases}$$

**6FE-3** The two capacitors shown in Fig. 6FE-3 have been connected for some time and have reached their present values. Determine the unknown capacitor  $C_x$ .

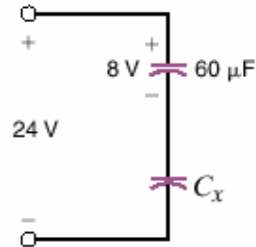- a.  $20\ \mu F$
- b.  $30\ \mu F$
- c.  $10\ \mu F$
- d.  $90\ \mu F$



---

**SOLUTION:**

The correct answer is *b*.

The voltage across the unknown capacitor  $C_x$  is (using KVL):

$$24 = 8 + V_x$$

$$V_x = 16V$$

$$q = C v$$

The capacitors are connected in series and the charge is the same.

$$q = 60\mu (8) = 480\mu C$$

$$C_x = \frac{q}{v} = \frac{480\mu}{16} = 30\mu F$$

**6FE-4** What is the equivalent inductance of the network in Fig. 6PFE-4?

- a. 9.5 mH      b. 2.5 mH  
c. 6.5 mH      d. 3.5 mH


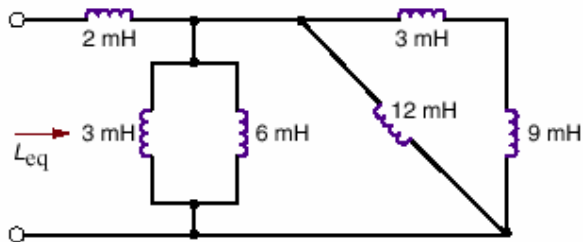


Figure 6PFE-4

**SOLUTION:**

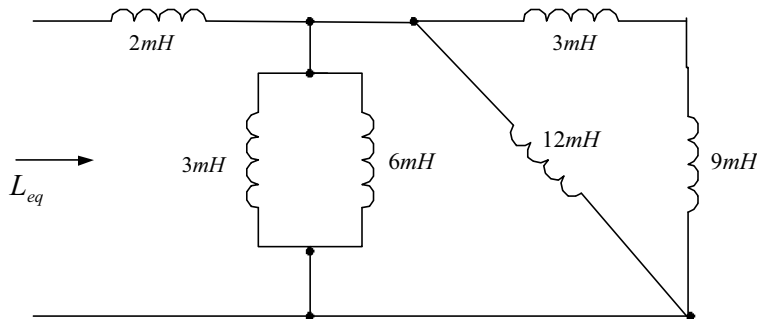

The correct answer is *d*.

$$L_{eq} = [ \{ [(3m + 9m) \parallel 12m] \parallel 6m \} \parallel 3m ] + 2m$$

$$L_{eq} = [ \{ [(12m) \parallel 12m] \parallel 6m \} \parallel 3m ] + 2m$$

$$L_{eq} = [ \{ 6m \parallel 6m \} \parallel 3m ] + 2m$$

$$L_{eq} = [ 3m \parallel 3m ] + 2m$$

$$L_{eq} = 1.5m + 2m$$

$$L_{eq} = 3.5mH$$



**6FE-5** The current source in the circuit in Fig. 6PFE-5 has the following operating characteristics:

$$i(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ 20te^{-2t} \text{ A}, & t > 0 \end{cases}$$

What is the voltage across the 10-mH inductor expressed as a function of time?

- a.  $v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ 0.2e^{-2t} - 4te^{-2t} \text{ V}, & t > 0 \end{cases}$
- b.  $v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ 2e^{-2t} + 4te^{-2t} \text{ V}, & t > 0 \end{cases}$
- c.  $v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ -0.2te^{-2t} + 0.4e^{-2t} \text{ V}, & t > 0 \end{cases}$
- d.  $v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ -2te^{-2t} \text{ V}, & t > 0 \end{cases}$

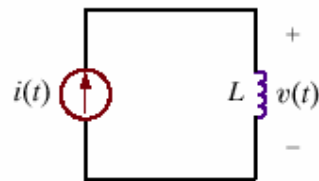


Figure 6PFE-5

### SOLUTION:

The correct answer is *a*.

$$v(t) = L \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} = 20te^{-2t}(-2) + 20e^{-2t} = 20e^{-2t} - 40te^{-2t}$$

$$v(t) = 10m[20e^{-2t} - 40te^{-2t}]$$

$$v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ 0.2e^{-2t} - 0.4te^{-2t} \text{ V}, & t > 0 \end{cases}$$

### 7.3

[Add/View Comments](#)

For  $t = 0^-$ , the circuit is in steady state therefore the inductor acts as a short circuit,  
The initial current through the inductor is found as shown in Fig (a),

$$\therefore i_L(0^-) = \frac{12}{6}$$

$$i_L(0^-) = 2A$$


$$i_L(0^+) = 2A \quad (\because i_L(0^+) = i_L(0^-))$$

www.zeallsoft.com

#### Step 1

[Add/View Comments](#)

For  $t \leq 0^-$  the circuit is

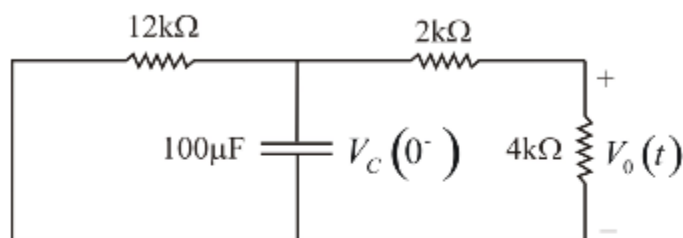

#### Step 2


[Add/View Comments](#)

Since there is no source

$$V_C(0^-) = 0V$$

$$V_0(0^-) = 0V$$

For  $t \geq 0^+$ , the circuit becomes

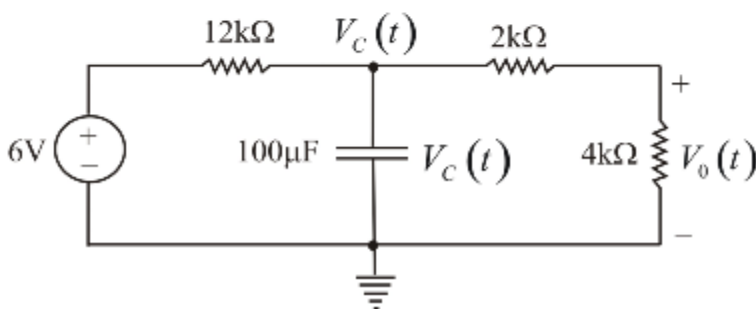

myUET

We Feel Your Feelings

www.myUET.net.tc

www.zeallsoft.com

Add/View Comments

Now writing the KCL equation at the top node,

$$\frac{V_C(t) - 6}{12k} + (100\mu) \frac{dV_C(t)}{dt} + \frac{V_C(t)}{(2k + 4k)} = 0$$

$$(100\mu) \frac{dV_C(t)}{dt} + V_C(t) \left[ \frac{1}{12k} + \frac{1}{6k} \right] = \frac{6}{12k}$$

$$\frac{dV_C(t)}{dt} + V_C(t) \left[ \frac{1}{(4k)(100\mu)} \right] = \frac{1}{(2k)(100\mu)}$$

$$\frac{dV_C(t)}{dt} + 2.5V_C(t) = 5$$

www.zeallsoft.com

Add/View Comments

The solution to this equation is of the form

$$V_C(t) = k_1 + k_2 e^{-t/\tau}$$

Substituting this we have

$$\frac{-k_2}{\tau} e^{-t/\tau} + (k_1 + k_2 e^{-t/\tau}) 2.5 = 5$$

Comparing on both sides

$$2.5k_1 = 5$$

$$k_1 = 2,$$

$$-\frac{1}{\tau} + 2.5 = 0$$

$$\tau = \frac{1}{2.5}$$

$$\tau = 0.4$$

Therefore the solution is

$$V_C(t) = 2 + k_2 e^{-t/0.4}$$

$$\text{At } t = 0^-, V_C(0^-) = 0$$

$$\text{Hence } 0 = 2 + k_2$$


$$k_2 = -2$$

$$\text{Hence } V_C(t) = 2(1 - e^{-2.5t}) \text{ V}$$

By voltage division

$$\begin{aligned} V_0(t) &= V_C(t) \left[ \frac{4k}{4k + 2k} \right] \\ &= \frac{4}{6} \times 2(1 - e^{-2.5t}) \end{aligned}$$
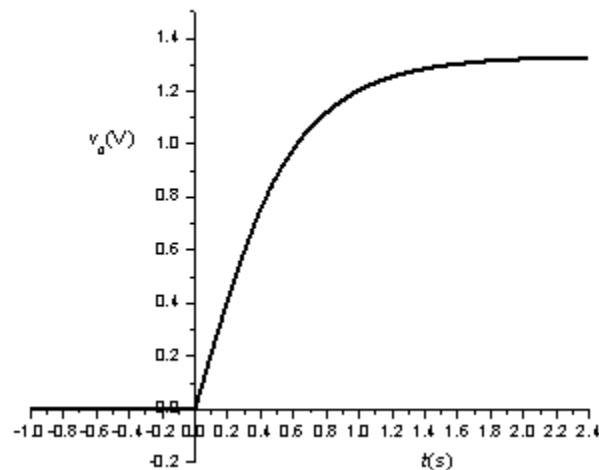
$$\boxed{V_0(t) = \frac{4}{3} (1 - e^{-2.5t}) \text{ V}}$$




www.zeallsoft.com

Step 1

Add/View Comments

For  $t < 0^-$  the circuit is

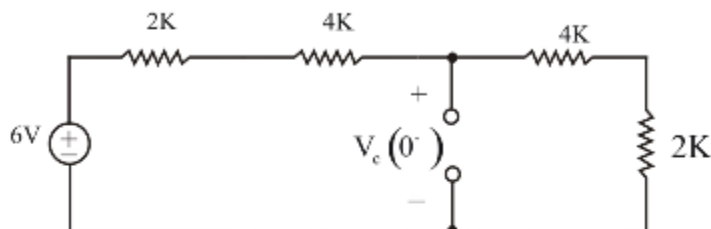

Step 2

Add/View Comments


By voltage division

$$V_c(0^-) = 6V \cdot \frac{4k}{4k + 2k}$$

#### 7.4

$$V_c(0^-) = 3V$$

For  $t > 0^+$  the circuit is

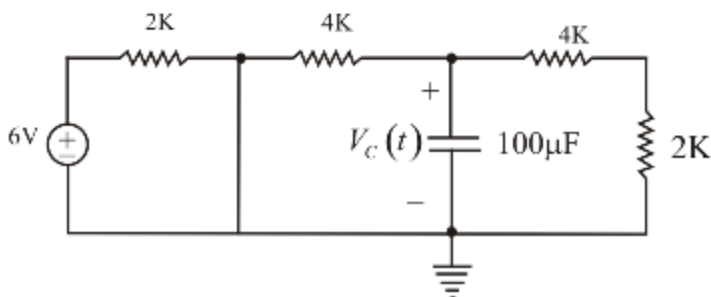

www.zeallsoft.com

Step 3

Add/View Comments

Due to the short circuit the left part is not there. So writing KCL equation at the top node,

$$(100\mu) \frac{dV_c(t)}{dt} + \frac{V_c(t)}{4k} + \frac{V_c(t)}{(4k + 2k)} = 0$$

$$100\mu \frac{dV_c(t)}{dt} + V_c(t) \left[ \frac{1}{4k} + \frac{1}{6k} \right] = 0$$

$$\frac{dV_c(t)}{dt} + V_c(t) \frac{1}{(2.4k)(100\mu)} = 0$$

$$\frac{dV_c(t)}{dt} + \frac{25}{6} V_c(t) = 0$$

myUET

We Feel Your Feelings

www.myUET.net.tc

www.zeallsoft.com

Step 4

Add/View Comments (1)

The solution for this differential equation is of the form

$$V_C(t) = k_2 e^{-t/\tau}$$

Therefore substituting we get

$$-\frac{k_2}{\tau} e^{-t/\tau} + \frac{25}{6} k_2 e^{-t/\tau} = 0$$

Comparing we get

$$-\frac{1}{\tau} + \frac{25}{6} = 0$$

$$\tau = \frac{6}{25}$$

Step 5

Add/View Comments

### 7.5

Hence  $V_C(t) = k_2 e^{-t/\tau}$

At  $t = 0^-$ ,  $V_C(0^-) = 3V$

$$3 = k_2$$


Hence the solution is of the form

$$V_C(t) = 3e^{-\frac{25}{6}t} V$$

www.zeallsoft.com


Step 6

Add/View Comments

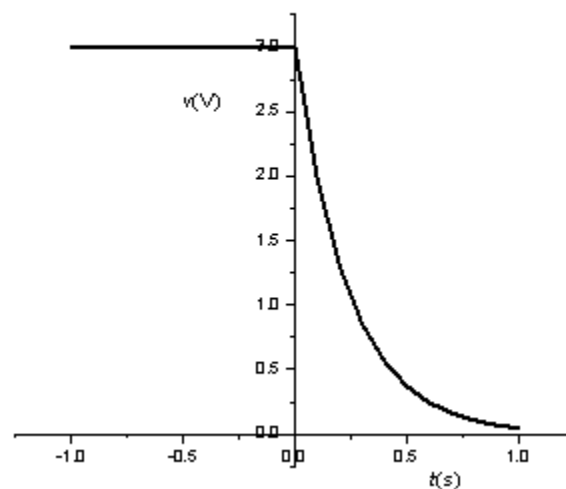


www.zeallsoft.com

Add/View Comments

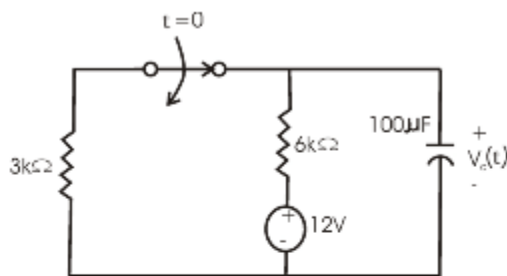

At  $t = 0^-$

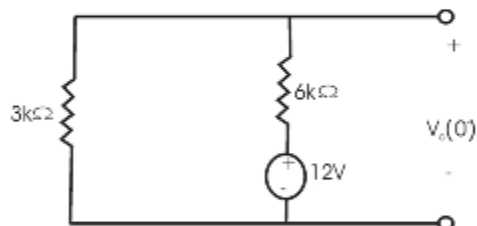

### Step 2

Add/View Comments


$$V_c(0^-) = \frac{12 \times 3K}{3K + 6K} = 4V$$

$$V_c(0^-) = V_c(0^+) = 4V$$

At  $t > 0$

www.zeallsoft.com

Add/View Comments

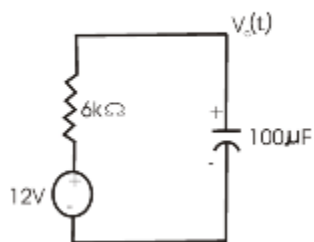

By applying nodal analysis

$$\frac{V_c - 12}{6K} + C \frac{dV_c(t)}{dt} = 0$$

$$\frac{V_c}{6K} - 2m + 100\mu \frac{dV_c(t)}{dt} = 0$$

$$\frac{dV_c(t)}{dt} + \frac{V_c(t)}{0.6} = 20 \quad \text{--- (1)}$$

$$\frac{dx(t)}{dt} + \frac{x(t)}{T} = A \quad \text{--- (2)}$$

The solution above (2) equation is

$$x(t) = AT + K_2 e^{\frac{-t}{T}}$$

By comparing equation (1) and (2)

$$x(t) = V_c(t)$$

$$A = 20$$

$$T = 0.6$$

$$\Rightarrow V_c(t) = 20(0.6) + K_2 e^{\frac{-t}{0.6}}$$

$$\Rightarrow V_c(t) = K_2 e^{\frac{-t}{0.6}} + 12$$

At  $t = 0^+$

$$V_c(0^+) = K_2 + 12$$

$$\Rightarrow 4 = K_2 + 12$$

$$\Rightarrow K_2 = -8$$

$$\boxed{V(t) = 12 - 8e^{\frac{-t}{0.6}} \quad v}$$



We Feel Your Feelings


www.myUET.net.tc



## 7.6

[Add/View Comments](#)

For  $t < 0^-$  the circuit is

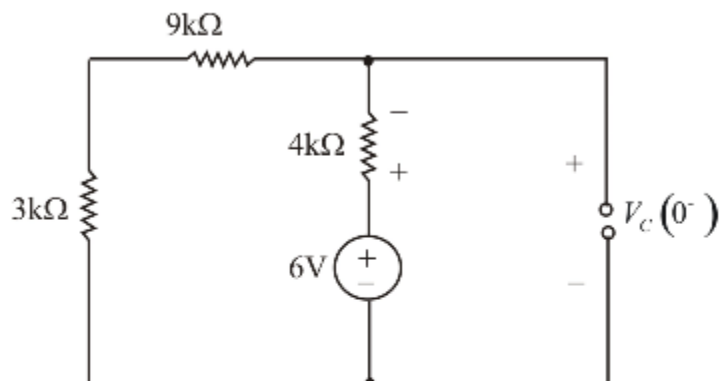

### Step 2

[Add/View Comments](#)

By voltage division voltage across  $4k\Omega$ ,

$$\begin{aligned} V_{4k\Omega} &= 6 \times \left( \frac{4k}{4k + 9k + 3k} \right) \\ &= \frac{6}{4} \\ &= \frac{3}{2} \text{ V} \\ &= 1.5 \text{ V} \end{aligned}$$

$$\text{Hence } V_c(0^-) = 6 - 1.5$$


$$V_c(0^-) = 4.5 \text{ V}$$

www.zeallsoft.com

Step 3

Add/View Comments

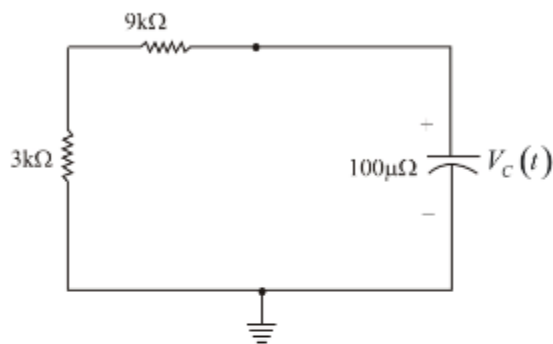At  $t = 0$  the switch is open hence the circuit is



Step 4

Add/View Comments

Writing KCL equation at the top node.

$$(100\mu) \frac{dV_C(t)}{dt} + \frac{V_C(t)}{(9k + 3k)} = 0$$

$$\frac{dV_C(t)}{dt} + V_C(t) \left[ \frac{1}{(12k)(100\mu)} \right] = 0$$

$$\frac{dV_C(t)}{dt} + \frac{5}{6} V_C(t) = 0$$

www.zeallsoft.com

Step 5

Add/View Comments

The solution for this differential equation is of the form

$$V_C(t) = k_2 e^{-t/\tau}$$

Substituting we get

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + \frac{5}{6} k_2 e^{-t/\tau} = 0$$

Comparing we get

$$-\frac{1}{\tau} + \frac{5}{6} = 0$$

$$\tau = \frac{6}{5}$$

Step 6

Add/View Comments

Hence the solution is

$$V_C(t) = k_2 e^{-t/(6/5)}$$

$$\text{At } t = 0, V_C(0^-) = 4.5 \text{ V}$$


$$\text{Hence } 4.5 = k_2$$

$$\text{Therefore } V_C(t) = 4.5 e^{-\frac{5}{6}t} \text{ V}$$

www.zeallsoft.com

Step 7


Add/View Comments

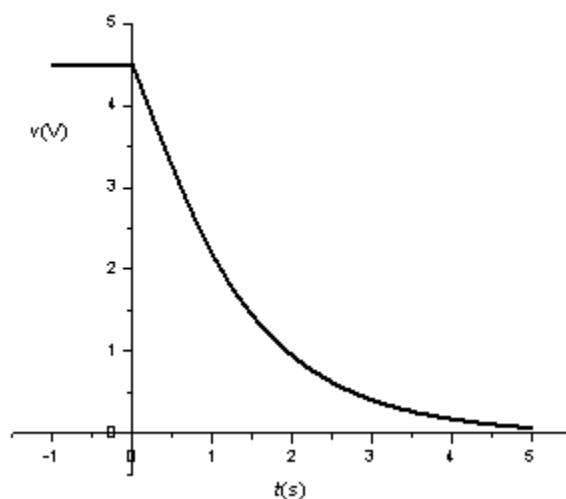

## 7.7

Add/View Comments

For  $t < 0^-$  the circuit is

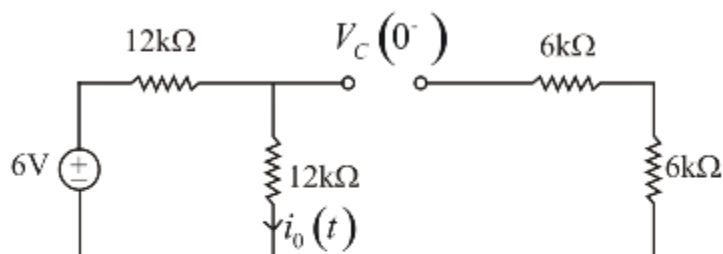

### Step 2

Add/View Comments

$$i_0(t) = \frac{6}{24k}$$

$$= \frac{1}{4} \text{ mA}$$


Since capacitor acts as a open circuit, no current flows through the  $6k\Omega$ ,  
Hence the voltage across the  $12k\Omega$  is

$$V_{12k\Omega} = (12k) \left( \frac{1}{4} \right) \text{ m}$$

$$= 3V$$

$$\text{Hence } V_C(0^-) = 3V$$


At  $t > 0^+$  the circuit is

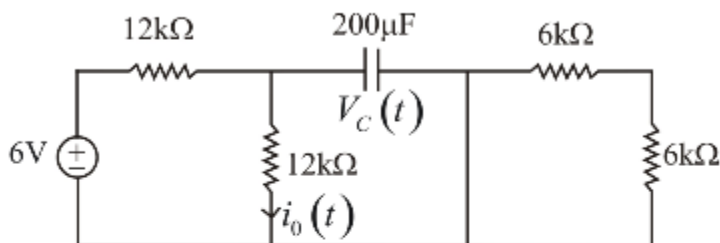
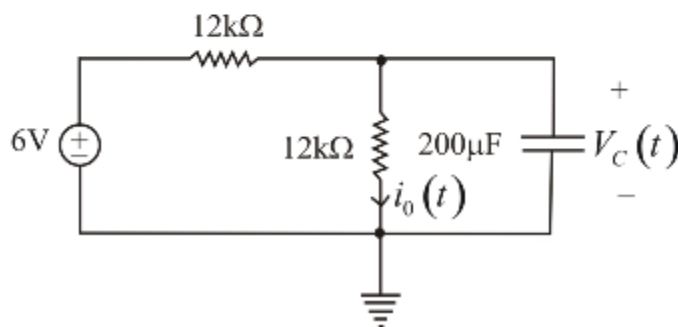
#### Step 4

Add/View Comments

Since there is a short circuit on the right side, the circuit diagram can be transformed as,



myUET

We Feel Your Feelings

www.myUET.net.tc

### Step 5

Writing KCL equation at the top node.

$$(200\mu) \frac{dV_C(t)}{dt} + \frac{V_C(t)}{12k} + \frac{V_C(t) - 6}{12k} = 0$$

$$\frac{dV_C(t)}{dt} + \frac{V_C(t)}{(6k)(200\mu)} = \frac{6}{(12k)(200\mu)}$$

$$\frac{dV_C(t)}{dt} + \frac{5}{6} V_C(t) = 2.5$$

### Step 6

The solution for the differential equation is of the form

$$V_C(t) = k_1 + k_2 e^{-t/\tau}$$

Substituting we get

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + \frac{5}{6} k_1 + \frac{5}{6} k_2 e^{-t/\tau} = 2.5$$

Comparing we get

$$k_1 = \frac{6 \times 2.5}{5}$$

$$k_1 = 3$$

$$-\frac{1}{\tau} = \frac{5}{6}$$

$$\tau = \frac{6}{5}$$

$$V_C(t) = 3 + k_2 e^{-t/\left(\frac{6}{5}\right)}$$

$$\text{At } t = 0^-, V_C(0^-) = 3V$$

Therefore

$$3 = 3 + k_2$$

$$k_2 = 0$$


$$\text{Hence } V_C(t) = 3V$$

$$\begin{aligned} \text{Therefore } i_0(t) &= \frac{V_C(t)}{12k} \\ &= \frac{3}{12k} \end{aligned}$$

$$i_0(t) = \frac{1}{4} \text{ mA}$$

www.zeallsoft.com has been challenged - view comments for detail


Add/View Comments (1)

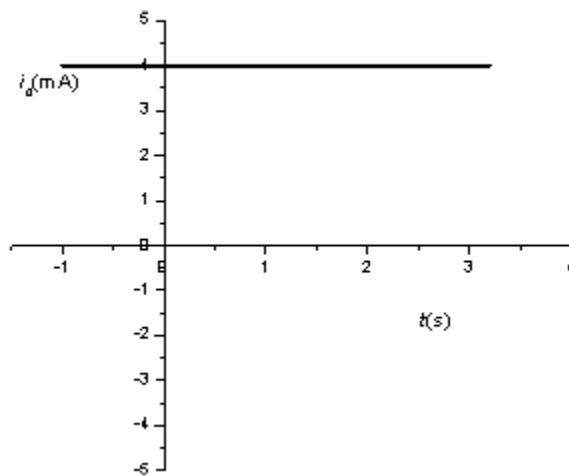

## 7.8

[Add/View Comments](#)

For  $t < 0^-$  the circuit is

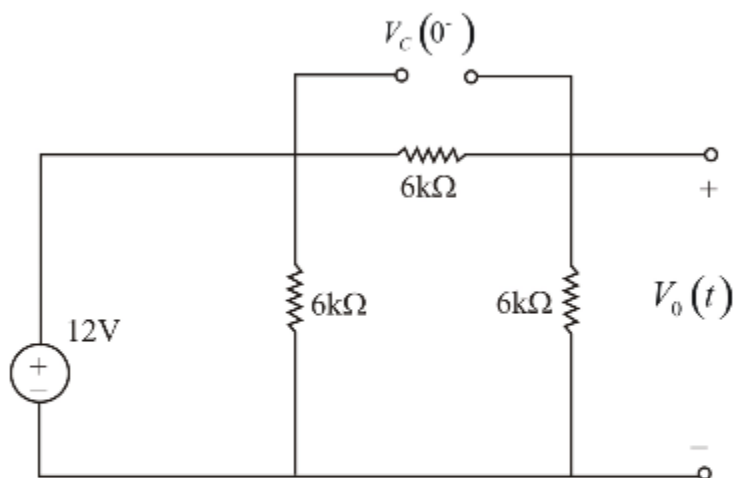

### Step 2

[Add/View Comments](#)

By voltage division


$$V_c(0^-) = 12 \times \frac{6k}{6k + 6k}$$

$$V_c(0^-) = 6V,$$

www.zeallsoft.com

[Add/View Comments](#)

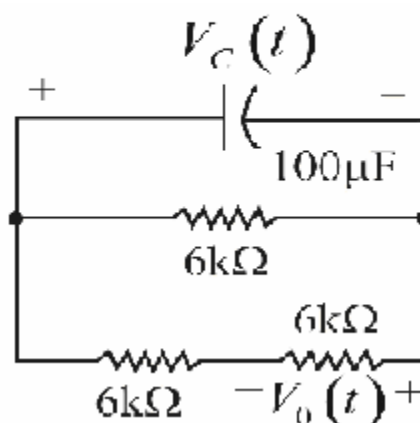For  $t = 0$ , the switch is opened, hence the circuit is





www.zeallsoft.com

Step 4

Add/View Comments

Writing KCL equation,

$$(100\mu) \frac{dV_c(t)}{dt} + \frac{V_c(t)}{6k} + \frac{V_c(t)}{(6k+6k)} = 0$$

$$(100\mu) \frac{dV_c(t)}{dt} + \frac{V_c(t)}{4k} = 0$$

$$\frac{dV_c(t)}{dt} + 2.5V_c(t) = 0$$

www.zeallsoft.com

Step 5

Add/View Comments

The solution for the differential equation is of the form,

$$V_c(t) = k_2 e^{-t/\tau}$$

Substituting we get

$$\frac{1}{\tau} k_2 e^{-t/\tau} + 2.5 k_2 e^{-t/\tau} = 0$$

$$-\frac{1}{\tau} + 2.5 = 0$$

$$\tau = \frac{1}{2.5}$$

www.zeallsoft.com

Step 6

Add/View Comments

Hence at  $t = 0^-$ ,  $V_c(0^-) = 6 \text{ V}$

$$6 = k_2$$

Therefore  $V_c(t) = 6 e^{-2.5t} \text{ V}$

$$\text{Hence, } V_0(t) = -V_c(t) \left[ \frac{6k}{6k+6k} \right]$$

$$= -6 e^{-2.5t} \left[ \frac{1}{2} \right]$$

$$V_0(t) = -3 e^{-2.5t} \text{ V}$$




We Feel Your Feelings

www.myUET.net.tc


www.zeallsoft.com

Add/View Comments

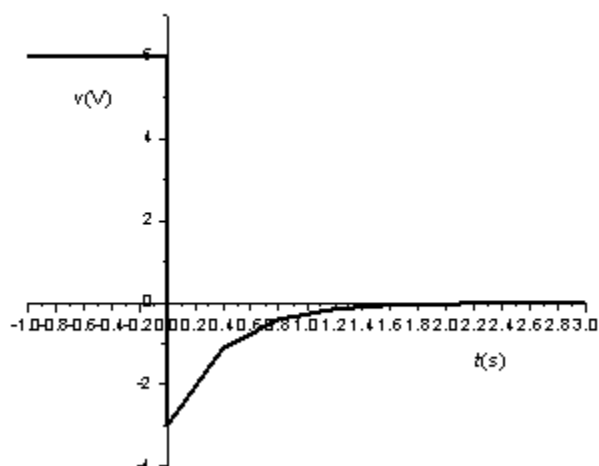


## 7.9

Add/View Comments

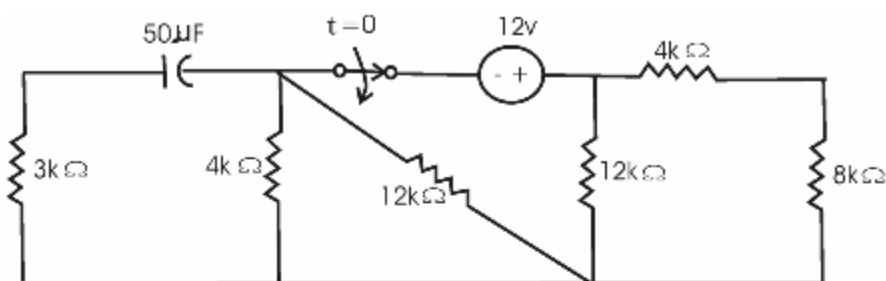

## Step 2

Add/View Comments

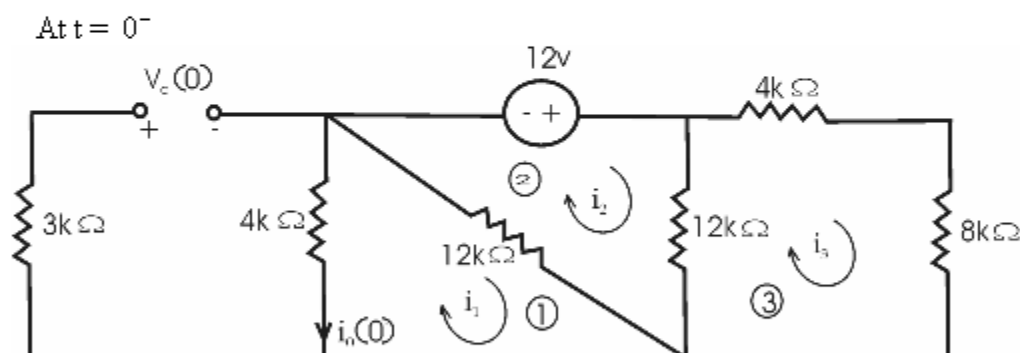

## Step 3

Add/View Comments

By applying KVL to the loop (2)

$$-12 + 12i_2 - 12i_3 + 12i_2 - 12i_1 = 0$$

$$-12i_1 + 24i_2 - 12i_3 = 12 \rightarrow (1)$$

By applying KVL to the loop (1)

$$4i_1 + 12i_1 - 12i_2 = 0$$

$$16i_1 - 12i_2 = 0 \quad \rightarrow (2)$$

Step 5

By applying KVL to the loop (3)

$$4i_3 + 8i_3 + 12i_3 - 12i_2 = 0$$

$$\Rightarrow -12i_2 + 24i_3 = 0 \quad \rightarrow (3)$$

Step 6

$$i_1 = 1 \text{ mA},$$

$$i_2 = 1.333 \text{ mA},$$

$$i_3 = 0.667 \text{ mA}$$

$$\Rightarrow i_0(0) = -1 \text{ mA}$$

$$V_c(0^-) = 4 \text{ K} \times 1\text{m} = 4 \text{ V}$$


$$\Rightarrow V_c(0^-) = V_c(0^+) = 4 \text{ V}$$

www.zeallsoft.com

Step 7

Add/View Comments

at  $t > 0$

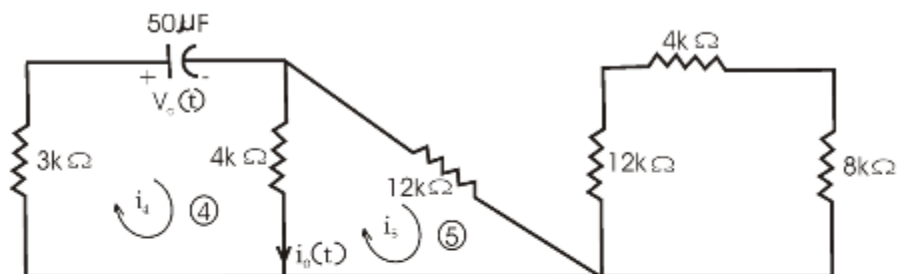

Step 8

Add/View Comments

By applying KVL to the loop (1) we get

$$3i_4 + V_c(t) + 4i_4 - 4i_5 = 0$$

$$7i_4 - 4i_5 + V_c(t) = 0 \quad \rightarrow (1)$$

Step 9

Add/View Comments

By applying KVL to the loop (2) we get

$$12i_5 + 4i_5 - 4i_4 = 0$$

$$-4i_4 + 16i_5 = 0$$

$$4i_4 = 16i_5$$

$$\Rightarrow i_5 = \frac{4}{16}i_4 \quad \rightarrow (2)$$

www.zeallsoft.com

Add/View Comments

Step 10

By substituting equation (2) in equation (1)

$$(7k)i_4 - (4k)\left(\frac{4}{16}\right)i_4 + V_c(t) = 0$$

$$(6k)i_4 + V_c(t) = 0 \rightarrow (3)$$

$$\text{But } i_4 = 50\mu \frac{dV_c(t)}{dt}$$

$$\Rightarrow 6K \times 50\mu \frac{dV_c(t)}{dt} + V_c(t) = 0$$

$$\Rightarrow \frac{dV_c(t)}{dt} + \frac{V_c(t)}{0.3} = 0$$

$$\Rightarrow V_c(t) = K_2 e^{\frac{-t}{0.3}} \text{ Volt}$$

Step 11

Add/View Comments

At  $t = 0^+$

$$V_c(0^+) = K_2$$

$$K_2 = 4$$

$$\Rightarrow V_c(t) = 4 e^{\frac{-t}{0.3}} \text{ volt}$$

www.zeallsoft.com

Step 12

Add/View Comments

$$i_o(t) = i_1 - i_2$$

$$\text{and } i_1 = 50 \mu \frac{d}{dt} \left( 4 e^{\frac{-t}{0.3}} \right) \quad \because i_1 = C \frac{dV_c}{dt}$$

$$\Rightarrow i_1 = 50 \mu \times 4 \left( -\frac{1}{0.3} \right) e^{\frac{-t}{0.3}}$$

$$\Rightarrow i_1 = -0.666 e^{\frac{-t}{0.3}} \text{ mA}$$

$$i_2 = \frac{4}{16} \times \left( -0.666 e^{\frac{-t}{0.3}} \right)$$

$$i_2 = -0.1667 e^{\frac{-t}{0.3}} \text{ mA}$$


$$\Rightarrow i_o(t) = \left( -0.666 e^{\frac{-t}{0.3}} + 0.1667 e^{\frac{-t}{0.3}} \right) \text{ mA}$$

$$\text{for } t > 0 \Rightarrow i_o(t) = -0.5 e^{\frac{-t}{0.3}} \text{ mA}$$

www.zeallsoft.com

Step 13


Add/View Comments

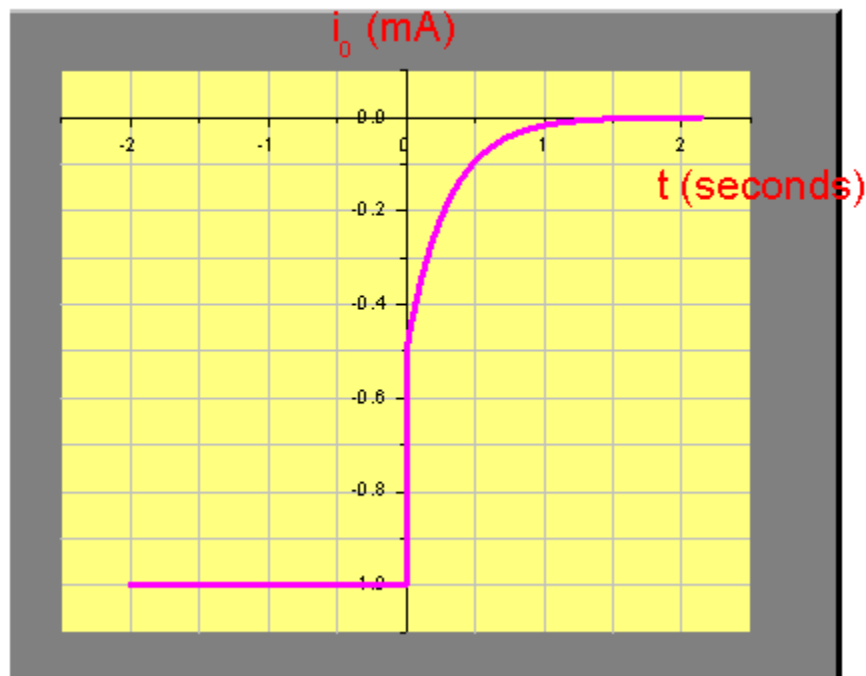

## 7.10

Add/View Comments

For  $t = 0^-$ , the circuit is

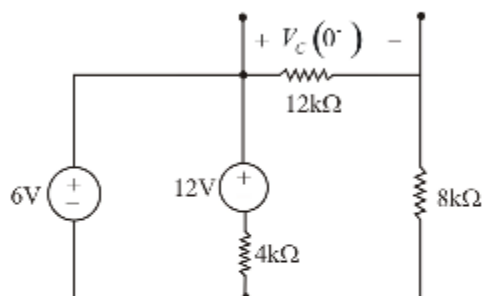

### Step 2

Add/View Comments (2)

By voltage division

$$V_c(0^-) = 6 \left( \frac{12k}{12k + 8k} \right)$$

$$V_c(0^-) = \frac{18}{5} \text{ V}$$


myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Create your own webpage, Completely Free

The circuit for  $t > 0$  is

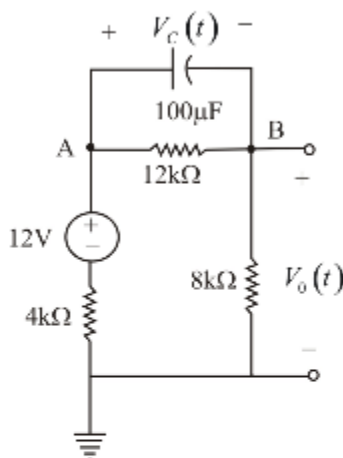

#### Step 4

Add/View Comments

Writing KCL equation at node A.

$$(100\mu) \frac{dV_C(t)}{dt} + \frac{V_C(t)}{12k} + \frac{V_C(t) - 12}{12k} = 0$$

$$\frac{dV_C(t)}{dt} + \frac{V_C(t)}{100\mu} \left[ \frac{1}{12k} + \frac{1}{12k} \right] - \frac{12}{(12k)(100\mu)} = 0$$

$$\frac{dV_C(t)}{dt} + V_C(t) \left( \frac{10}{6} \right) - 10 = 0$$

Add/View Comments

The solution for this differential equation is of the form  $V_C(t) = k_1 + k_2 e^{-t/\tau}$

Substituting this we get,

$$-\frac{1}{\tau} k_2 e^{-\frac{t}{\tau}} + \frac{10}{6} k_1 + \frac{10}{6} k_2 e^{-\frac{t}{\tau}} - 10 = 0$$

Comparing we get

$$\frac{10}{6} k_1 = 10$$

$$k_1 = 6$$

$$-\frac{1}{\tau} + \frac{10}{6} = 0$$

$$\tau = \frac{6}{10} s$$



www.zeallsoft.com

Add/View Comments

Hence the solution is,

$$V_C(t) = 6 + k_2 e^{-\frac{10}{6}t} \text{ V}$$

From initial conditions at  $t = 0^-$

$$V_C(0^-) = V_C(0^+) = \frac{18}{5} \text{ V}$$

$$\frac{18}{5} = 6 + k_2$$

$$k_2 = \frac{18}{5} - 6$$

$$= \frac{18 - 30}{5}$$

$$k_2 = -\frac{12}{5}$$

www.zeallsoft.com

Add/View Comments

Therefore the solution is

$$V_C(t) = 6 - \frac{12}{5} e^{-\frac{10}{6}t} \text{ V}$$

$$\begin{aligned} \text{Hence: } V_0(t) &= -(V_C(t) - 12) \left[ \frac{8k}{8k + 4k} \right] \\ &= - \left[ 6 - \frac{12}{5} e^{-\frac{10}{6}t} - 12 \right] \left[ \frac{2}{3} \right] \\ &= \left[ 6 + \frac{12}{5} e^{-\frac{10}{6}t} \right] \left[ \frac{2}{3} \right] \end{aligned}$$

$$V_0(t) = 4 + 1.6 e^{-\frac{10}{6}t} \text{ V}$$




We Feel Your Feelings

www.myUET.net.tc

[www.zeallsoft.com](http://www.zeallsoft.com)

Step 8

[Add/View Comments](#)

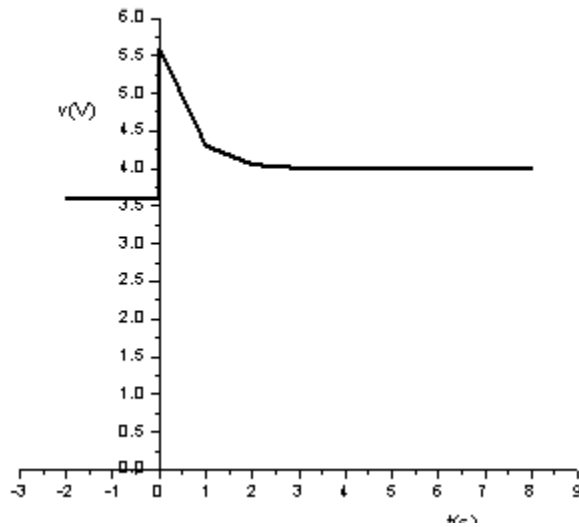


7.11

Step 1

[Add/View Comments](#)

For  $t < 0^-$ , the circuit is

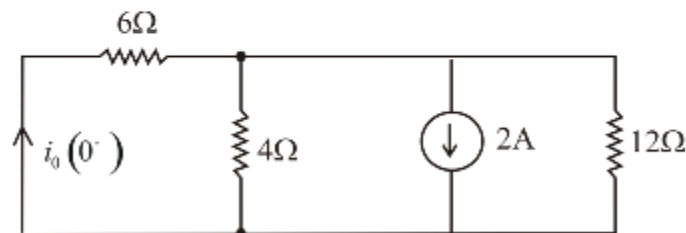

www.zeallsoft.com

Step 2

Add/View Comments


By current division

$$i_0(0^-) = 2 \times \frac{(4 \parallel 12)}{(6 + [4 \parallel 12])}$$

$$= 2 \times \frac{3}{6 + 3}$$

$$i_0(0^-) = \frac{2}{3} \text{ A}$$

For  $t > 0^+$ , the circuit is

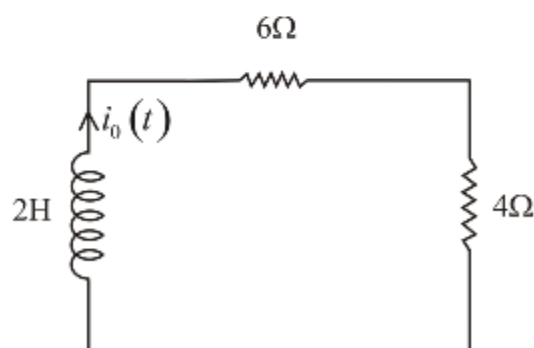

www.zeallsoft.com

Step 3

Add/View Comments

Writing KVL equation across the loop

$$2 \frac{d}{dt} i_0(t) + (6 + 4) i_0(t) = 0$$

$$\frac{d}{dt} i_0(t) + 5 i_0(t) = 0$$

The solution for this differential equation is of the form

$$i_0(t) = k_2 e^{-t/\tau}$$

Substituting

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + 5 k_2 e^{-t/\tau} = 0$$

Comparing

$$-\frac{1}{\tau} + 5 = 0$$

$$\tau = \frac{1}{5}$$

Hence the solution is

$$i_0(t) = k_2 e^{-t/\left(\frac{1}{3}\right)}$$


at  $t = 0^-$ ,  $i_0(0^-) = \frac{2}{3} \text{ A}$

$$\frac{2}{3} = k_2$$

Hence the solution is

$$i_0(t) = \frac{2}{3} e^{-3t} \text{ A}$$

### Step 5

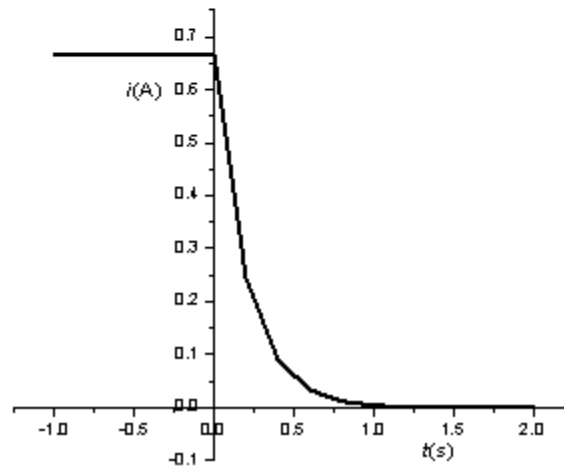


## 7.12

### Step 1

[Add/View Comments](#)

For  $t < 0^-$ , the circuit is

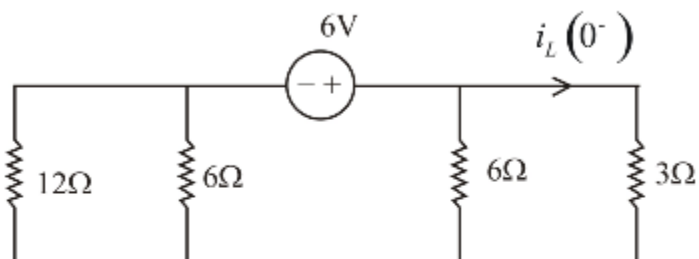


### Step 2


[Add/View Comments](#)

The resistors  $12\Omega$ ,  $6\Omega$  are in parallel
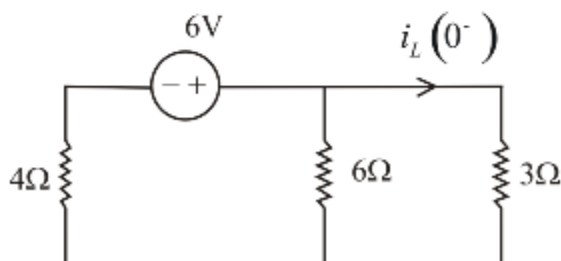
$$R_{eq} = \frac{12 \times 6}{12 + 6} = 4\Omega$$



By source transformation technique

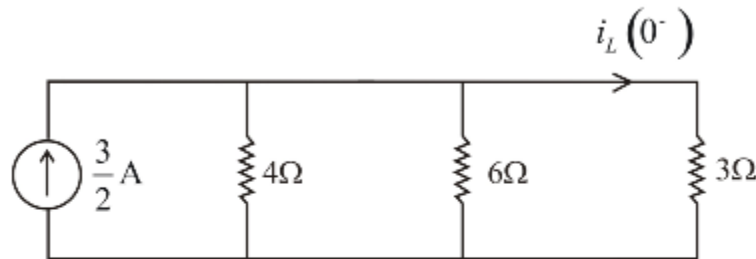

Step 4

By current division we get

$$\begin{aligned} i_L(0^-) &= \frac{3}{2} \left[ \frac{4 \parallel 6}{3 + (4 \parallel 6)} \right] \\ &= \frac{3}{2} \left[ \frac{\frac{12}{5}}{3 + \frac{12}{5}} \right] \\ &= \frac{3}{2} \times \frac{12}{27} \\ i_L(0^-) &= \frac{2}{3} \text{ A} \end{aligned}$$




We Feel Your Feelings

[www.myUET.net.tc](http://www.myUET.net.tc)

www.zeallsoft.com

Add/View Comments

For  $t > 0^+$  the circuit is,

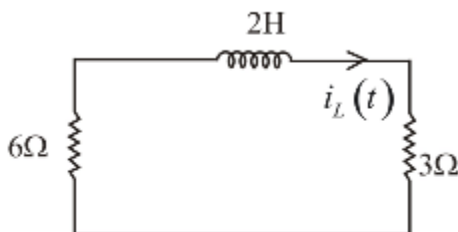

### Step 6

Add/View Comments

Writing KVL equation around the loop

$$2 \frac{d}{dt} i_L(t) + (6+3) i_L(t) = 0$$

$$\frac{d}{dt} i_L(t) + \frac{9}{2} i_L(t) = 0$$

The solution for this differential equation is of the form

$$i_L(t) = k_2 e^{-t/\tau}$$

www.zeallsoft.com

### Step 7

Add/View Comments

Substituting we get

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + \frac{9}{2} k_2 e^{-t/\tau} = 0$$

$$-\frac{1}{\tau} + \frac{9}{2} = 0$$

$$\tau = \frac{2}{9}$$

Therefore the solution is


$$i_L(t) = k_2 e^{-t/(2/9)}$$

$$\text{at } t = 0^-, i_L(0^-) = \frac{2}{3} \text{ A}$$

$$\frac{2}{3} = k_2$$

Therefore the solution is

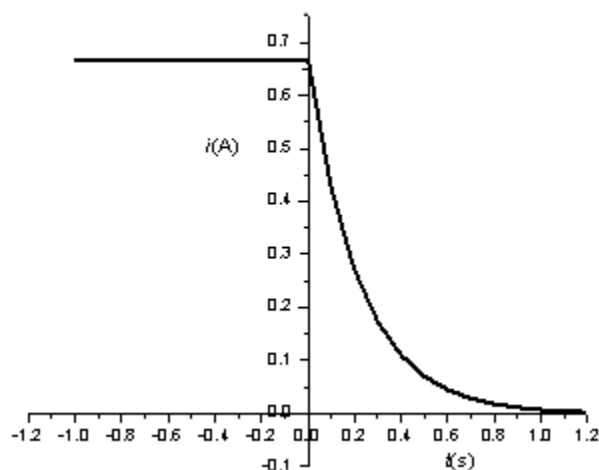
$$i_L(t) = \frac{2}{3} e^{-\frac{9}{2}t} \text{ A}$$



### 7.13

Add/View Comments

For  $t < 0^-$ , the circuit is,

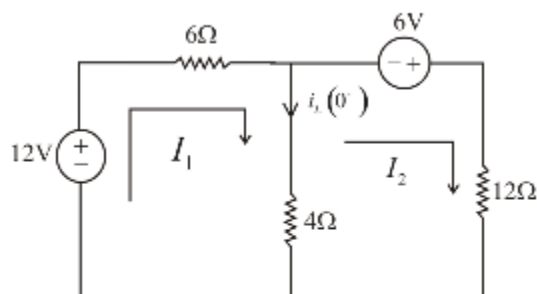

#### Step 2

Add/View Comments

By mesh analysis

$$-12 + 6I_1 + 4(I_1 - I_2) = 0$$

$$-6 + 12I_2 + 4(I_2 - I_1) = 0$$

$$10I_1 - 4I_2 - 12 = 0 \quad \text{..... (i)}$$

$$-4I_1 + 16I_2 - 6 = 0 \quad \text{..... (ii)}$$

Solving equations (i) and (ii) we get

$$I_1 = \frac{3}{2} \text{ A}$$

$$I_2 = \frac{3}{4} \text{ A}$$

myUET

We Feel Your Feelings

www.myUET.net.tc



www.zeallsoft.com

Step 3

Add/View Comments


$$\begin{aligned}\text{Hence } I_L(0^-) &= I_1 - I_2 \\ &= \frac{3}{2} - \frac{3}{4} \\ I_L(0^-) &= \frac{3}{4} \text{ A}\end{aligned}$$

www.zeallsoft.com

Step 4

Add/View Comments

For  $t = 0$ , the circuit is

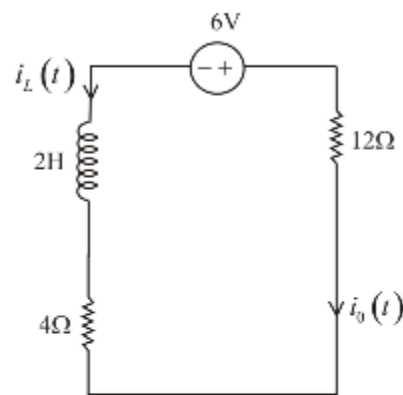

Step 5

Add/View Comments

$$6 + 2 \frac{d}{dt} i_L(t) + (4 + 12) i_L(t) = 0$$

$$\frac{d}{dt} i_L(t) + 8 i_L(t) = -3$$

The solution for this differential equation is of the form

$$i_L(t) = k_1 + k_2 e^{-t/\tau}$$

Substituting we get

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + 8 k_1 + 8 k_2 e^{-t/\tau} = -3$$

Comparing

$$8k_1 = -3$$

$$k_1 = -\frac{3}{8}$$

$$-\frac{1}{\tau} + 8 = 0$$

$$\tau = \frac{1}{8}$$

Step 7

The solution is

$$i_L(t) = -\frac{3}{8} + k_2 e^{-t/(1/8)}$$

$$\text{at } t = 0^- \quad i_L(0^-) = \frac{3}{4}$$

$$\frac{3}{4} = \frac{-3}{8} + k_2$$

$$k_2 = \frac{3}{4} + \frac{3}{8}$$

$$k_2 = \frac{9}{8}$$



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Get Solutions of All Engineering Subjects

www.zeallsoft.com

Add/View Comments

$$i_L(t) = -\frac{3}{8} + \frac{9}{8} e^{-8t} \text{ A}$$


From the circuit

$$i_0(t) = -i_L(t)$$

$$i_0(t) = \frac{3}{8} - \frac{9}{8} e^{-8t} \text{ A}$$

Step 9

Add/View Comments

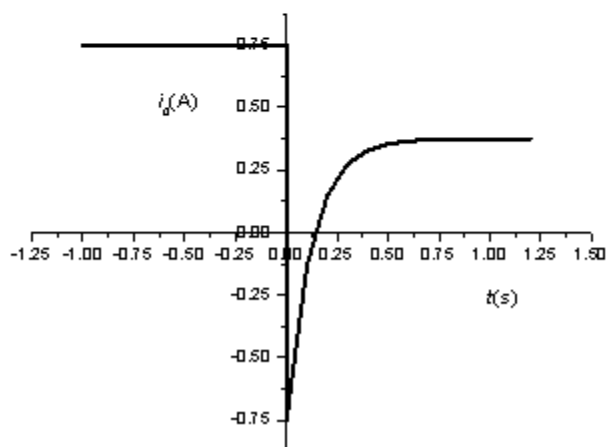

myUET

Connecting UETians Together


[www.myUET.net.tc](http://www.myUET.net.tc)

Get Solutions of All Engineering Subjects

## 7.14

[Add/View Comments](#)

For  $t = 0^-$ , the circuit is

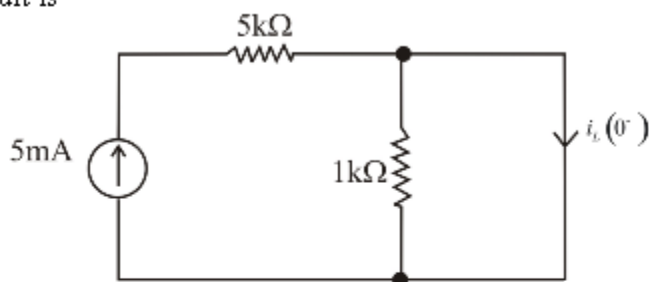


### Step 2

[Add/View Comments](#)

Since inductor acts as a short circuit for a steady state, no current flows through  $1k\Omega$  and towards the right part

Hence  $i_L(0^-) = 5mA$

For  $t > 0$ , the circuit is

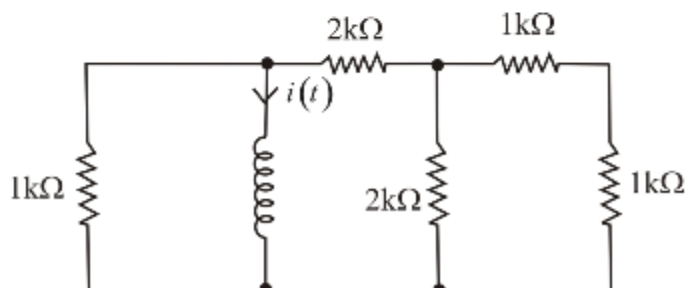

www.zeallsoft.com

### Step 3

[Add/View Comments](#)

Reducing the network from the right side

$$R_{eq} = [(1k + 1k) \parallel 2k] + 2k$$


$$= [2k \parallel 2k] + 2k$$

$$= 1k + 2k$$


$$= 3k\Omega$$

### Step 4

[Add/View Comments](#)

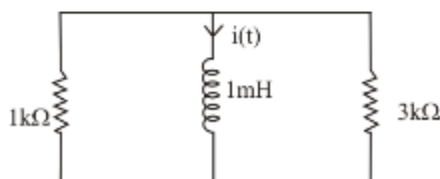
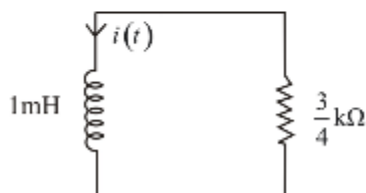
$$\begin{aligned}\text{Now } R_{eq} &= \frac{1k \times 3k}{1k + 3k} \\ &= \frac{3}{4} k\Omega\end{aligned}$$



Writing KVL equation across the loop

$$1m \frac{d}{dt} i(t) + i(t) \frac{3}{4} k = 0$$

$$\frac{d}{dt} i(t) + i(t) \frac{3}{4} M = 0$$

The solution for this differential equation is of the form

$$i(t) = k_2 e^{-t/\tau}$$

Substituting we get

$$-\frac{1}{\tau} k_2 e^{-t/\tau} + \frac{3}{4} M k_2 e^{-t/\tau} = 0$$

$$-\frac{1}{\tau} + \frac{3}{4} M = 0$$

$$\tau = \frac{4}{3} \mu s$$



We Feel Your Feelings

www.myUET.net.tc

www.zeallsoft.com

Add/View Comments

Hence  $i(t) = K_2 e^{-t/\left(\frac{4}{3}\mu s\right)}$  A

Using initial conditions  $i_L(0^-) = i_L(0^+) = 5\text{mA}$


$5\text{mA} = K_2$

Therefore

$$i(t) = 5e^{-t/\left(\frac{4}{3}\mu\right)} \text{ mA}$$

Step 8


Add/View Comments

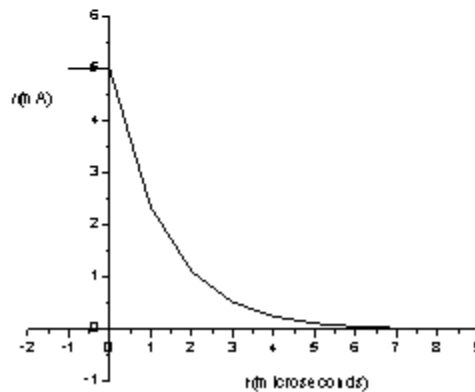

## 7.15

Add/View Comments

The given circuit is,

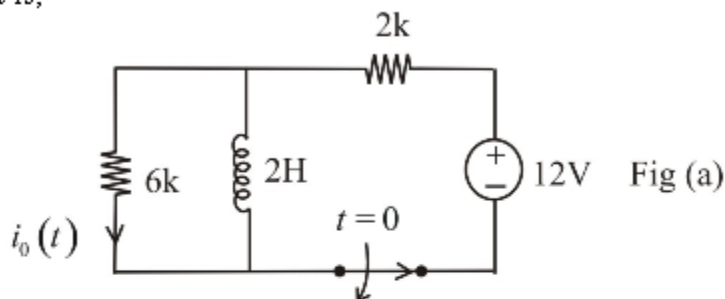


Step 1:  $i_0(t)$  is of the form  $K_1 + K_2 e^{\frac{-t}{\tau}}$ .
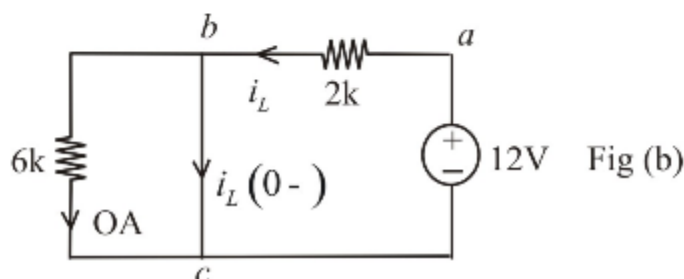
### Step 2

Add/View Comments

Step 2: At  $t = 0^-$ , circuit is as shown in Fig (b), the circuit is in steady state prior to time  $t = 0$  therefore the inductor acts as short circuit,



www.zeallsoft.com

Add/View Comments

The initial current through the inductor is calculated from the above circuit as,

$\therefore V_{ac} = 0V$ , Therefore current in  $6k\Omega$  is  $0A$

$$\therefore i_L(0^-) = \frac{12}{2k}$$

$$i_L(0^-) = 6 \text{ mA}$$



www.zeallsoft.com

Step 4

Add/View Comments

Step 3: Fig (c) is the new circuit valid only at  $t = 0+$ ,

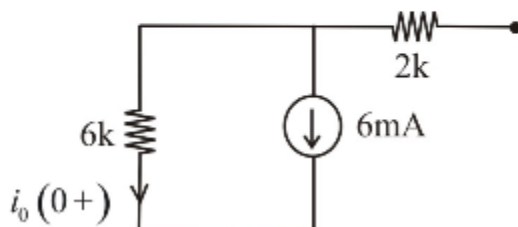


Fig (c)

www.zeallsoft.com

Step 5

Add/View Comments

The value of the current source that replaces the inductor is,

$$i_L(0-) = i_L(0+)$$

$$i_L(0+) = 6\text{mA}$$

$$\text{Hence, } i_0(0+) = -6\text{mA}$$

#### Step 6

Add/View Comments

Step 4: The equivalent circuit, valid for  $t > 5\tau$ , is shown in Fig (d)

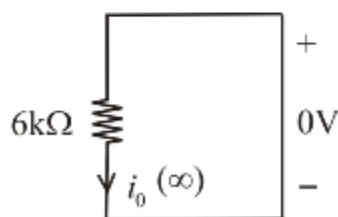


Fig (d)

$$\therefore i_0(\infty) = 0 \text{ mA}$$

myUET


Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians



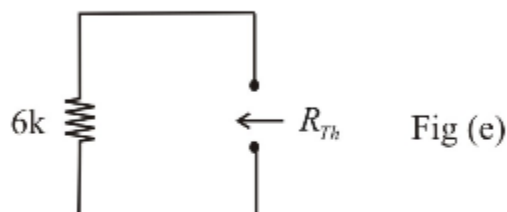Step 5: The Thevenin equivalent resistance  $R_{Th}$  as seen into the open circuit terminals of the inductor,



## 7.16

### Step 8

Therefore the time constant is,

$$\tau = \frac{2}{6k}$$

$$\tau = \frac{1}{3} \text{ ms}$$

$$\text{Step 6: } K_1 = i_0(\infty) = 0$$

$$K_2 = i_0(0+) - i_0(\infty)$$

$$K_2 = -6 \text{ mA}$$

$$\therefore i_0(t) = -6e^{\frac{-t}{\left(\frac{1}{3} \text{ ms}\right)}} \text{ mA}$$


$$i_0(t) = -6e^{-3000t} \text{ mA}$$

www.zeallsoft.com

Add/View Comments

Step1.  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

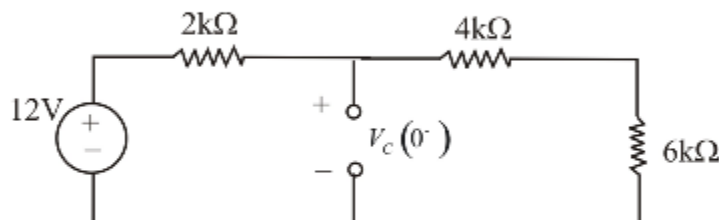Step2. The initial voltage across the capacitor  $V_c(0^-)$  at  $t = 0^-$  is calculated from the circuit.



## Step 2

Add/View Comments

By Voltage division


$$V_c(0^-) = 12 \times \frac{(4k + 6k)}{(2k + 4k + 6k)}$$

$$V_c(0^-) = 10V$$

www.zeallsoft.com

Add/View Comments

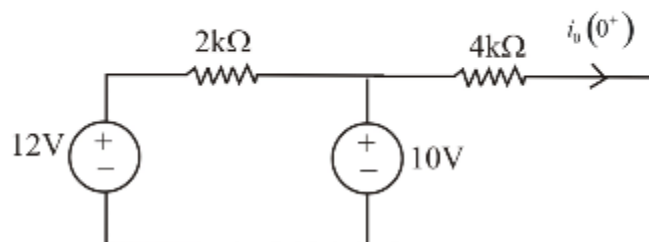Step 3. The new circuit for  $t = 0^+$  is



www.zeallsoft.com

Add/View Comments

In the second mesh


$$i_0(0^+) = \frac{10}{4k}$$

$$i_0(0^+) = 2.5mA$$

www.zeallsoft.com

Add/View Comments

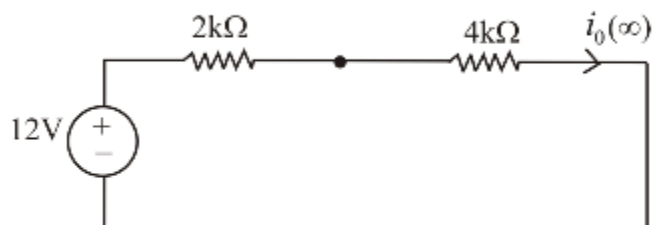Step 4. The equivalent circuit valid for  $t > 5\tau$



Step 6

Add/View Comments


$$i_o(\infty) = \frac{12}{2k + 4k}$$

$$i_o(\infty) = 2\text{mA}$$

www.zeallsoft.com

Add/View Comments

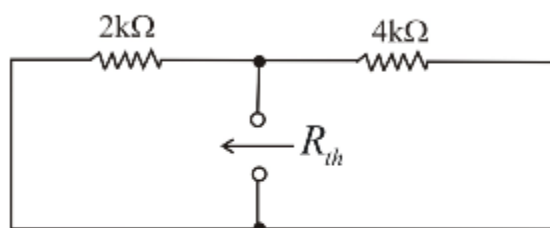Step 5. The Thevenin equivalent resistance, obtained by looking into the open circuit terminals of the capacitor.



Step 8

Add/View Comments

$$R_{th} = \frac{2k \times 4k}{2k + 4k}$$

$$= \frac{8}{6}k\Omega$$

$$R_{th} = \frac{4}{3}k\Omega$$

Therefore, the circuit time constant is

$$\tau = R_{th} C$$

$$= \left(\frac{4}{3}k\right) (200 \times 10^{-6})$$

$$\tau = 0.267s$$

## 7.17

[Add/View Comments](#)

Step 6.  $k_1 = i_0(\infty)$

$$= 2 \text{ mA}$$

$$k_2 = i_0(0^+) - i_0(\infty)$$

$$= 2.5 - 2$$

$$k_2 = 0.5 \text{ mA}$$

Therefore the solution is


$$i_0(t) = 2 + 0.5e^{-t/0.27} \text{ mA}$$

www.zeallsoft.com

## Step 1

[Add/View Comments](#)

The given circuit is,


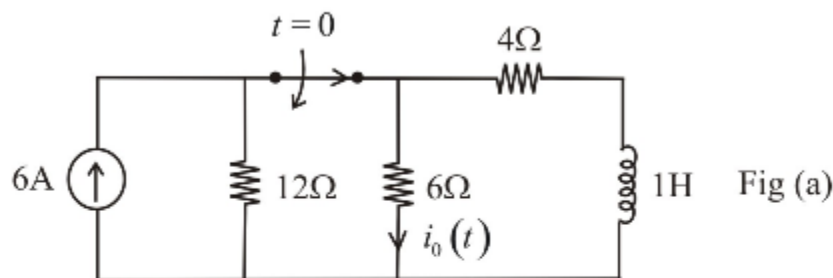


Step 1:  $i_0(t)$  is of the form  $K_1 + K_2e^{\frac{-t}{\tau}}$ .
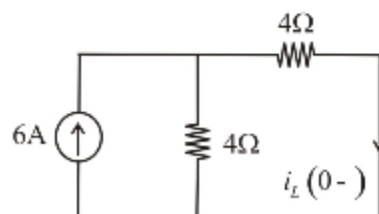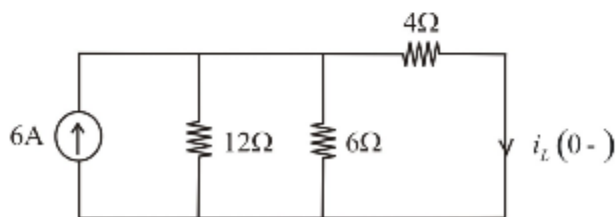
## Step 2

[Add/View Comments](#)

Step 2: At  $t = 0^-$ , circuit is as shown in Fig (b), the circuit is in steady state prior to time  $t = 0$  therefore the inductor acts as short circuit,



$12\Omega$  and  $6\Omega$  are in parallel, hence replaced as in Fig (c)

$$R_{eq} = \frac{12 \times 6}{12 + 6}$$

$$R_{eq} = 4\Omega$$

The initial current through the inductor is calculated from Fig (c),

$$i_L(0-) = 6 \times \frac{4}{4 + 4}$$

$$i_L(0-) = 3 \text{ A}$$

#### Step 4

Add/View Comments

Step 3: Fig (d) is the new circuit valid only at  $t = 0+$ ,

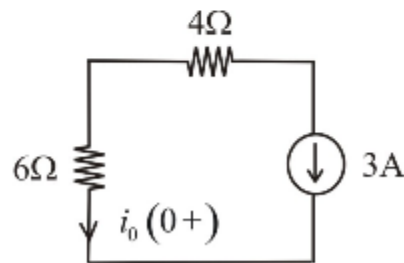


Fig (d)

The value of the current source that replaces the inductor is,

$$i_L(0-) = i_L(0+)$$

$$i_L(0+) = 3\text{A}$$

$$\text{Hence, } i_0(0+) = -3\text{A}$$

#### Step 6

Add/View Comments

Step 4: The equivalent circuit, valid for  $t > 5\tau$ , is shown in Fig (e)


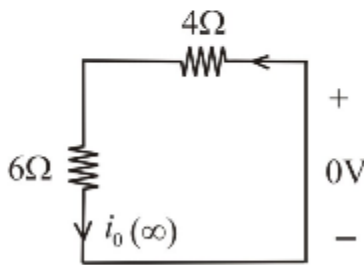


Fig (e)

$$\therefore i_0(\infty) = 0\text{ A}$$

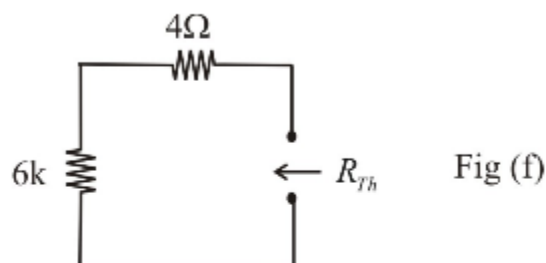Step 5: The Thevenin equivalent resistance  $R_{Th}$  as seen into the open circuit terminals of the inductor



$$R_{Th} = 6 + 4$$

$$R_{Th} = 10\Omega$$

### Step 8

Add/View Comments

Therefore the time constant is,

$$\tau = \frac{L}{R_{Th}}$$

$$\tau = \frac{1}{10}$$

$$\tau = 0.1s$$

Step 6:  $K_1 = i_0(\infty)$

$$K_1 = 0$$

$$K_2 = i_0(0+) - i_0(\infty)$$

$$K_2 = -3A$$

$$i_0(t) = -3e^{-\frac{t}{0.1}} A$$

$$i_0(t) = -3e^{-10t} A$$



We Feel Your Feelings

www.myUET.net.tc

## 7.18

### Step 1

[Add/View Comments](#)


Step 1:  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

### Step 2

[Add/View Comments](#)

Step 2: The initial current through the inductor is obtained from the circuit at  $t = 0^-$
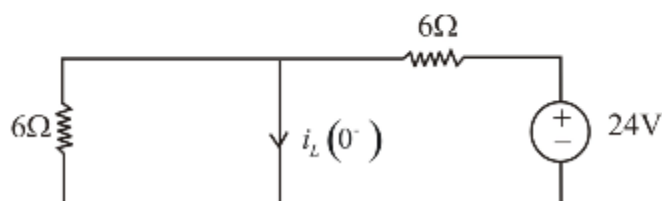
$$\begin{aligned} i_L(0^-) &= \frac{24}{6} \\ &= 4\text{A} \end{aligned}$$



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians




[www.zeallsoft.com](http://www.zeallsoft.com)

Step 3

[Add/View Comments](#)

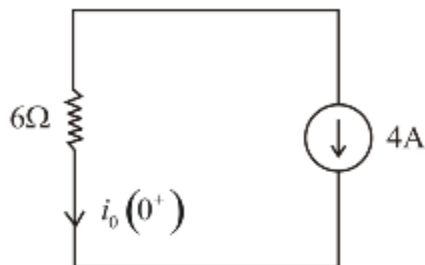Step 3: The new valid circuit for  $t = 0^+$  is




$$i_0(0^+) = -4A$$

Step 4

[Add/View Comments](#)

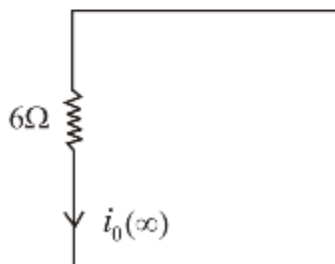Step 4: The equivalent circuit for  $t > 5\tau$



$$i_0(\infty) = 0A$$

myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians


## 7.19

Add/View Comments

Step 1.  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

Step 2. The initial voltage across the capacitor is calculated from

$t = 0^-$  The current is

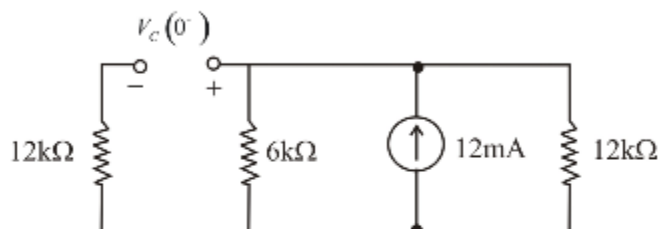

## Step 2

Add/View Comments

Since the capacitor acts as a open circuit, there is no current through  $12k\Omega$

Therefore the voltage across capacitor is the voltage across  $6k\Omega$

$$i_{6k\Omega} = (12\text{m}) \frac{12k}{(12k + 6k)}$$

$$= 12 \times \frac{2}{3}$$

$$= 8\text{mA}$$

$$V_{6k\Omega} = (6k)(8\text{m})$$

$$= 48\text{V}$$

$$\text{Hence } V_c(0^-) = 48\text{V}$$




Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

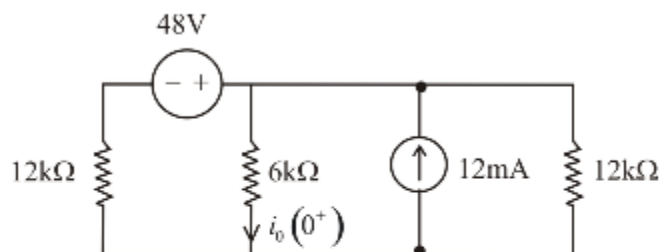Step3. The new circuit valid for  $t = 0^+$  is



#### Step 4

Add/View Comments

Therefore

$$\begin{aligned} i_0(0^+) &= \frac{48}{(6k + 12k)} \\ &= \frac{48}{18k} \\ i_0(0^+) &= \frac{8}{3} \text{ mA} \end{aligned}$$



We Feel Your Feelings

www.myUET.net.tc

Step 4. The equivalent circuit, valid for  $t > 5\tau$




Since there is no source

$$i_0(\infty) = 0 \text{ mA}$$
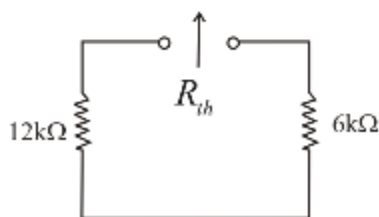
### Step 6

Add/View Comments

Step 5. The Thevenin equivalent resistance, obtained by looking into the open circuit terminals of the capacitor.



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

$$R_{th} = 12k + 6k$$

$$R_{th} = 18k\Omega$$

Therefore, the circuit time constant is

$$\tau = R_{th} C$$

$$= 18 \times 10^3 \times 200 \times 10^{-6}$$

$$= 3.6s$$

#### Step 8

Add/View Comments

Step 6.

$$k_1 = i_0(\alpha)$$

$$= 0mA$$

$$k_2 = i_0(0^+) - i_0(\alpha)$$

$$= \frac{8}{3} - 0$$

$$= \frac{8}{3} mA$$

Therefore the solution is


$$i_0(t) = \frac{8}{3} e^{-t/3.6} mA$$

7.21

[Add/View Comments](#)

Step1.  $i_0(t)$  is of the form of  $k_1 + k_2 e^{-t/\tau}$

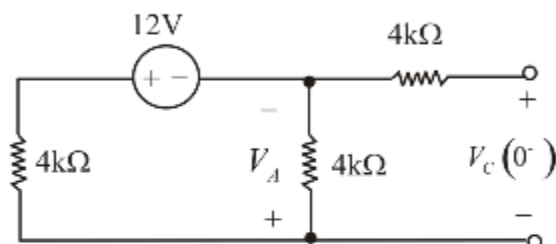Step2. The initial voltage across the capacitor  $V_C(0^-)$  is calculated from



**Step 2** has been challenged - view comments for detail

[Add/View Comments \(1\)](#)

Since there is no current through  $4k\Omega$  due to open circuit

Hence  $V_C(0^-) = -V_A$

The voltage across  $4k\Omega$  is by voltage division

$$V_A = (12) \left[ \frac{4k}{4k + 4k} \right]$$

$$= 6V$$

Hence  $V_C(0^-) = -6V$




Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

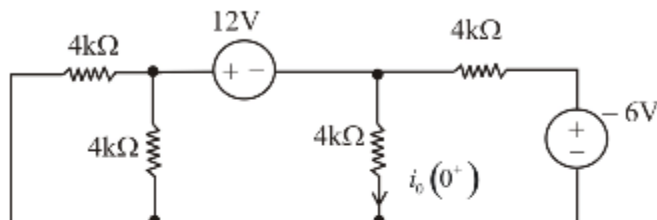Step 3. The new valid circuit at  $t = 0^+$  is




#### Step 4

Add/View Comments

Since  $4k\Omega$  and  $4k\Omega$  are in parallel

$$R_{eq} = \frac{4k \times 4k}{4k + 4k}$$

$$R_{eq} = 2k\Omega$$

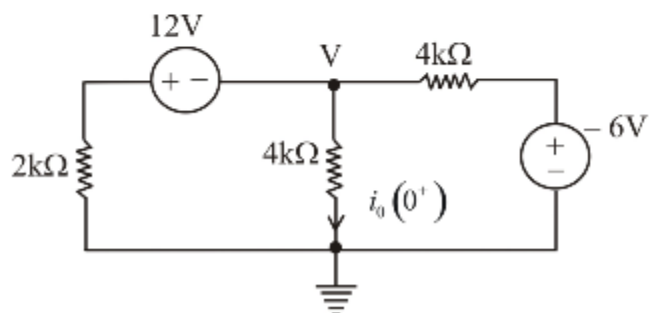

www.zeallsoft.com

Step 5

Add/View Comments

Writing KCL equation at the top node

$$\frac{V - (-12)}{2k} + \frac{V}{4k} + \frac{V - (-6)}{4k} = 0$$

$$\frac{V + 12}{2k} + \frac{V}{4k} + \frac{V + 6}{4k} = 0$$

$$2V + 24 + V + V + 6 = 0$$

$$4V = -30$$

$$V = \frac{-15}{2} \text{ V}$$


Step 6

Add/View Comments

$$\begin{aligned} \text{Hence } i_0(0^+) &= \frac{V}{4k} \\ &= \frac{-15}{2 \times 4k} \\ i_0(0^+) &= \frac{-15}{8} \text{ mA} \end{aligned}$$



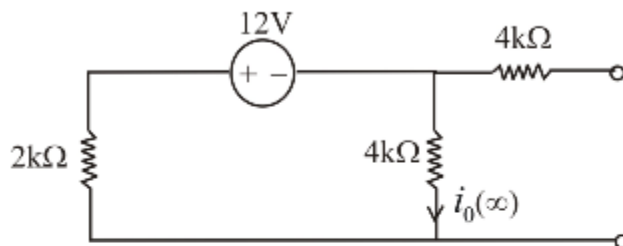Step 4. The equivalent circuit for  $t > 5\tau$




$$i_0(\infty) = \frac{-12}{2k + 6k}$$

$$i_0(\infty) = -2\text{mA}$$
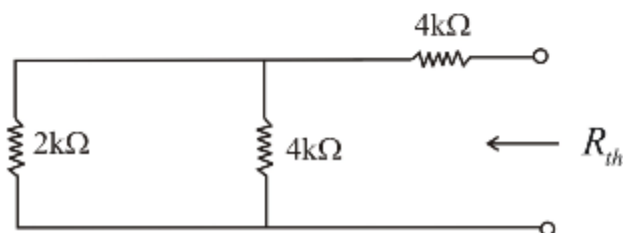
### Step 8

Add/View Comments

Step 5. The Thevenin equivalent circuit is found by



myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Get your own webpage created, Just For Free!

$$R_{th} = 4k\Omega + (2k\parallel 4k)$$

$$= 4k + \frac{4}{3}k$$

$$R_{th} = \frac{16}{3}k\Omega$$

Therefore, the circuit time constant is

$$\tau = R_{th} C$$

$$= \frac{16}{3} \times 10^3 \times 200 \times 10^{-6}$$

$$= 1.067s$$

### Step 10

$$\text{Step 6. } k_1 = i_0(\infty)$$

$$= -2mA$$

$$k_2 = i_0(0^+) - i_0(\infty)$$

$$= \frac{-15}{8} + 2$$

$$= \frac{1}{8}mA$$

Therefore the solution is

$$i_0(t) = -2 + \frac{1}{8}e^{-t/1.067} \text{ mA}$$



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Get solutions of all Engineering Subjects!

7.23


[Add/View Comments](#)

Step 1:  $V_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

Step 2

[Add/View Comments](#)

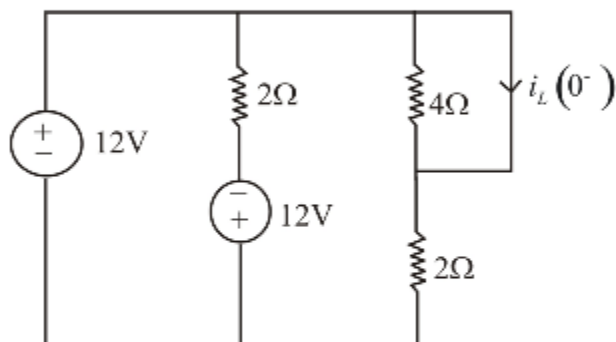Step 2: The initial current through the inductor  $i_L(0^-)$  is



Connecting UETians Together


[www.myUET.net.tc](http://www.myUET.net.tc)

We Feel Your Feelings!

www.zeallsoft.com

Add/View Comments (1)

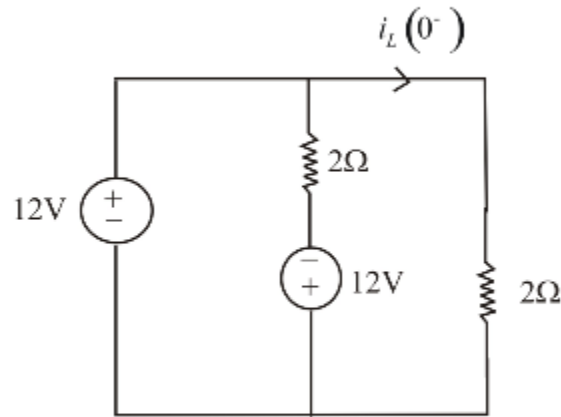Since  $4\Omega$  is in parallel with a short circuit.




$$i_L(0^-) = \frac{12}{2} = 6A$$

www.zeallsoft.com

Add/View Comments

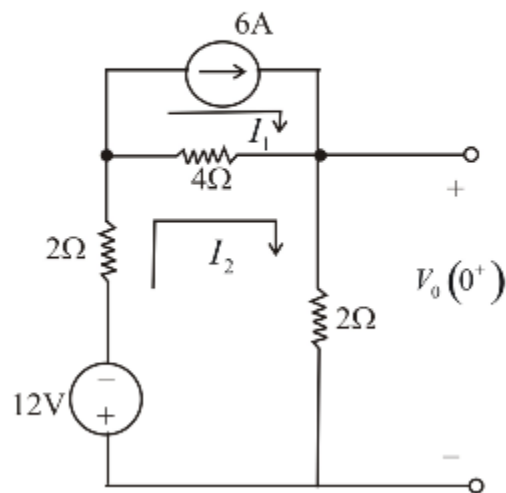Step 3: The new valid circuit at  $t = 0^+$  is



[www.zeallsoft.com](http://www.zeallsoft.com)

[Add/View Comments](#)

Now by mesh analysis

$$I_1 = 6A$$

KVL in the second mesh gives

$$12 + 2I_2 + 4(I_2 - I_1) + 2I_2 = 0$$

$$8I_2 - 24 + 12 = 0$$

$$8I_2 = 12$$

$$I_2 = \frac{12}{8}A$$

$$I_2 = \frac{3}{2}A$$


$$\text{Hence } V_0(0^+) = \frac{3}{2} \times 2$$

$$V_0(0^+) = 3V$$

[www.zeallsoft.com](http://www.zeallsoft.com)

[Add/View Comments](#)

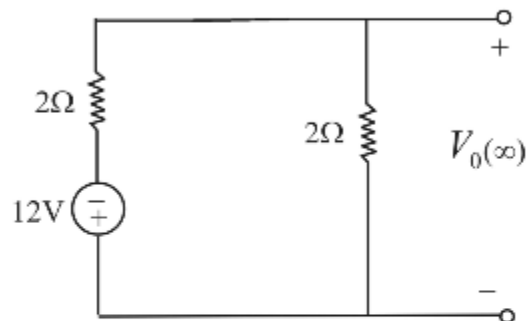Step 4: The equivalent circuit for  $t > 5\tau$



**Step 7**

[Add/View Comments](#)


Now by voltage division

$$V_0(\infty) = -12 \times \frac{2}{2+2}$$

$$= -12 \times \frac{2}{4}$$

$$V_0(\infty) = -6V$$

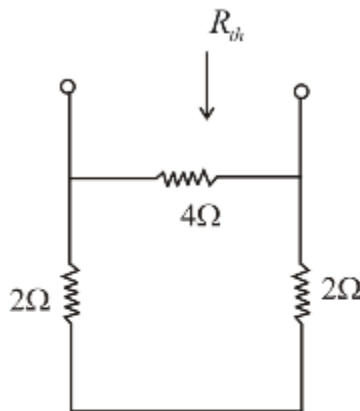Step 5: The Thevenin equivalent resistance is found



### Step 9

Add/View Comments

$$R_{th} = 4 \parallel (2 + 2)$$

$$= 4 \parallel 4$$

$$R_{th} = 2\Omega$$

Therefore circuit time constant is,

$$\tau = \frac{L}{R_{th}}$$

$$= \frac{\left(\frac{1}{3}\right)}{2}$$

$$= \frac{1}{6}$$

Add/View Comments

Step 6:  $k_1 = V_0(\infty)$

$$= -6V$$

$$k_2 = V_0(0^+) - V_0(\infty)$$

$$= 3 - (-6)$$

$$= 9V$$

Therefore the solution is

$$V_0(t) = -6 + 9e^{-t/0.167} V$$

7.25


[Add/View Comments](#)

Step 1:  $V_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

> Step 2

[Add/View Comments](#)

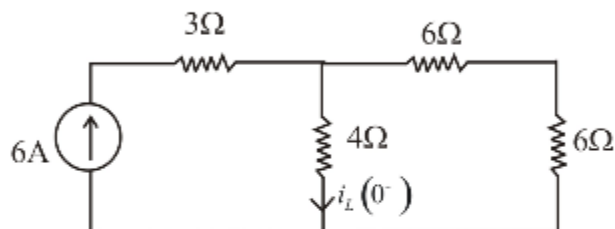Step 2: The initial current through the inductor  $i_L(0^-)$  is given by




> Step 3

[Add/View Comments](#)

By current division

$$\begin{aligned} i_L(0^-) &= 6 \times \left[ \frac{6+6}{4+6+6} \right] \\ &= 6 \times \frac{12}{16} \\ i_L(0^-) &= \frac{9}{2} \text{ A} \end{aligned}$$

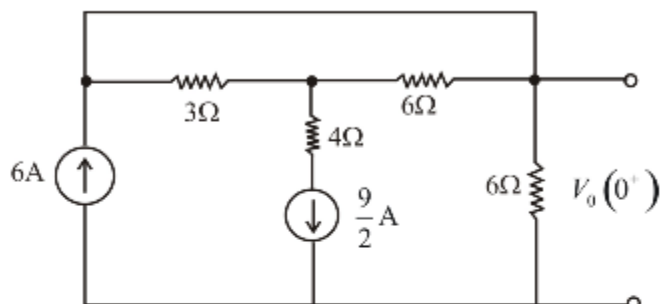
Step 3: The new valid circuit at  $t = 0^+$  s



Step 5

AddView Comments

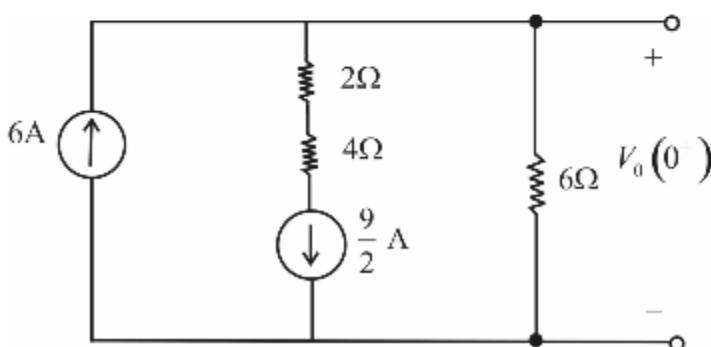We see that  $3\Omega$  and  $6\Omega$  are in parallel.  $R_{eq} = 2\Omega$



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

We Feel Your Feelings!



www.zeallsoft.com

Add/View Comments


Current through  $6\Omega$  is,  $i_{6\Omega} = 6 - \frac{9}{2}$   
 $= \frac{3}{2} \text{ A}$

Hence  $V_0(0^+) = (6)\left(\frac{3}{2}\right)$   
 $V_0(0^+) = 9 \text{ V}$
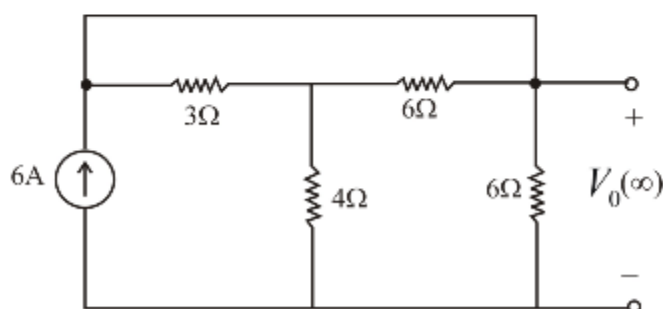
### Step 7

Add/View Comments

Step 4: The equivalent circuit for  $t > 5\tau$




myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

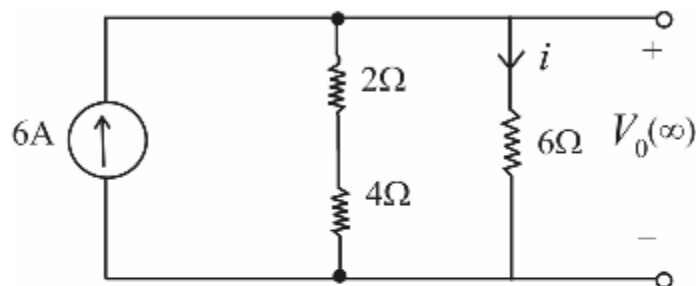Since resistors  $3\Omega$  and  $6\Omega$  are in parallel,  $R_{eq} = 2\Omega$



### Step 9

Add/View Comments

Current through  $6\Omega$  by current division


$$i = 6 \left[ \frac{6}{6+2+4} \right]$$

$$= 3A$$

Therefore  $V_0(\infty) = 6(3)$

$$V_0(\infty) = 18V$$

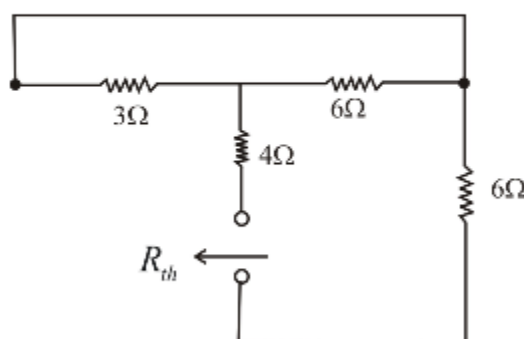Step 5: The thevenin equivalent resistance for the circuit



We Feel Your Feelings

www.myUET.net.tc

$$\begin{aligned} R_{th} &= 4 + 6 + (3 \parallel 6) \\ &= 4 + 6 + \left( \frac{3 \times 6}{3 + 6} \right) \\ R_{th} &= 4 + 6 + 2 \\ &= 12 \Omega \end{aligned}$$

Therefore circuit time constant is

$$\begin{aligned} \tau &= \frac{L}{R_{th}} \\ &= \frac{2}{12} \\ &= \frac{1}{6} \\ \tau &= 0.167 \text{ s} \end{aligned}$$

$$\begin{aligned} \text{Step 6: } k_1 &= V_0(\infty) \\ &= 18 \text{ V} \\ k_2 &= V_0(0^+) - V_0(\infty) \\ &= 9 - 18 \\ &= -9 \text{ V} \end{aligned}$$

Therefore the solution is

$$\begin{aligned} V_0(t) &= 18 - 9e^{-\frac{t}{0.167}} \text{ V} \\ \boxed{V_0(t) &= 18 - 9e^{-6t} \text{ V}} \end{aligned}$$

myUET

Connecting UETians Together


[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

7.26

[Add/View Comments](#)


At  $t = 0^-$

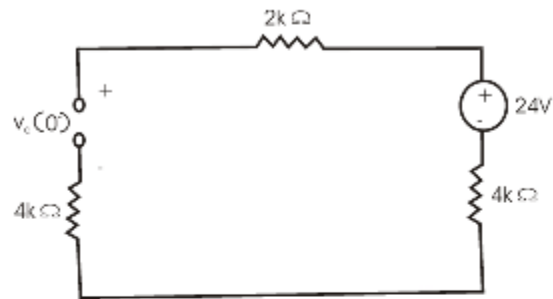

$$V_c(0^-) = 24\text{ V}$$

$$V_c(0^+) = 24\text{ V}$$

At  $t = 0^+$

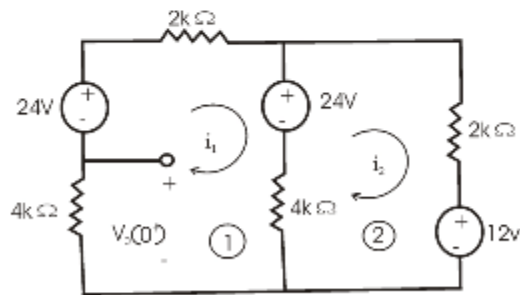

www.zeallsoft.com

Add/View Comments

By applying KVL to the loop (1)

$$2K i_1 + 24 + 4K i_1 - 4K i_2 + 4K i_1 - 24 = 0$$

$$\Rightarrow 10K i_1 - 4K i_2 = 0 \rightarrow (1)$$

By applying KVL to loop (2)

$$2K i_2 + 12 + 4K i_2 - 4K i_1 - 24 = 0$$

$$\Rightarrow 4K i_1 - 6K i_2 = 12 \rightarrow (2)$$

By solving equation (1) & (2) we get

$$i_1 = 1.1 \text{ mA},$$

$$i_2 = 2.727 \text{ mA},$$


$$V_0(0^+) = -i_1 \times 4K$$

$$= -1.1\text{mA} \times 4K$$

$$V_0(0^+) = -4.4 \text{ V}$$


$$\text{At } t = \infty$$

www.zeallsoft.com

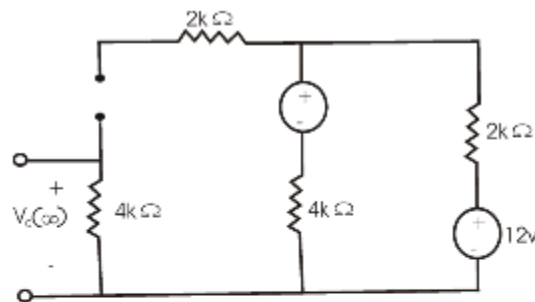

$$V_0(\infty) = 0$$

To find  $R_{th}$

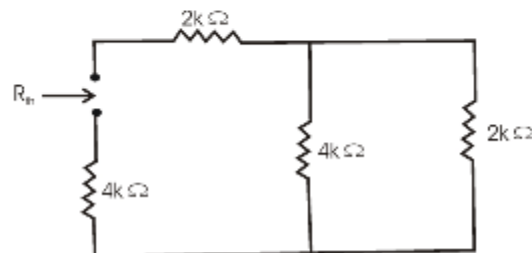

www.zeallsoft.com has been challenged - view comments for detail

Add/View Comments (1)

$$\begin{aligned}
 &4\text{ K}\Omega \parallel 2\text{ K}\Omega \\
 &= 1.333\text{ K}\Omega \\
 &2\text{ K}\Omega, 1.333\text{ K}\Omega \text{ and } 4\text{ K}\Omega \text{ are in series} \\
 &\therefore R_{th} = 7.333\text{ K}\Omega \\
 &T = R_{th} C \\
 &= 7.333\text{ K} \times 50\mu \\
 &\Rightarrow T = 0.3667\text{ sec} \\
 &\therefore V_c(t) = V_c(\infty) + V_c(0^+) - V_c(\infty) e^{\frac{-t}{T}} \text{ V} \\
 &\boxed{V_c(t) = 4.4 e^{\frac{-t}{0.3667}} \text{ V}} \quad \text{Ans.}
 \end{aligned}$$

7.27


Add/View Comments

Step 1.  $V_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

Step 2

Add/View Comments

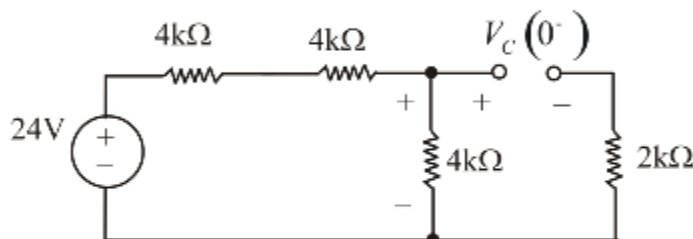Step 2. The initial voltage across the capacitor  $V_c(0^-)$  at  $t = 0^-$  is calculated from circuit.



Step 3

Add/View Comments

The voltage across  $4\text{ k}\Omega$  is,

$$\begin{aligned}
 V_{4k\Omega} &= 24 \times \frac{4k}{4k + 4k + 4k} \\
 &= 8\text{ V}
 \end{aligned}$$


Hence  $V_c(0^-) = V_{4k\Omega}$

$$V_c(0^-) = 8\text{ V}$$

www.zeallsoft.com

Add/View Comments

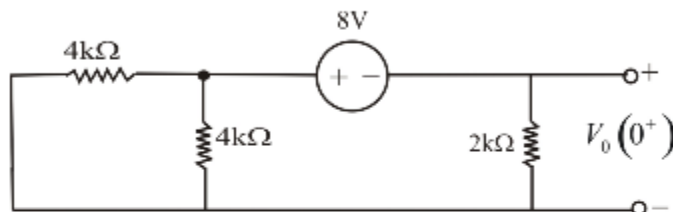Step 3. The new valid circuit for  $t = 0^+$  is



#### Step 5

Add/View Comments


$V_o(0^+)$  by voltage division

$$\begin{aligned} V_o(0^+) &= (-8) \left( \frac{2k}{2k + (4k || 4k)} \right) \\ &= (-8) \left( \frac{2k}{2k + 2k} \right) \\ V_o(0^+) &= -4V \end{aligned}$$

www.zeallsoft.com

Add/View Comments

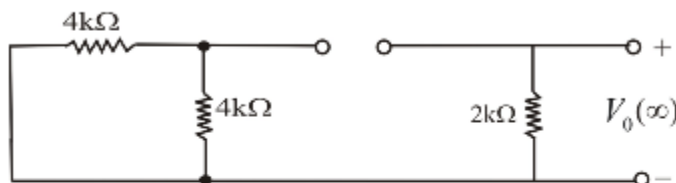Step 4. The equivalent circuit for  $t > 5\tau$




$$V_o(\infty) = 0V$$
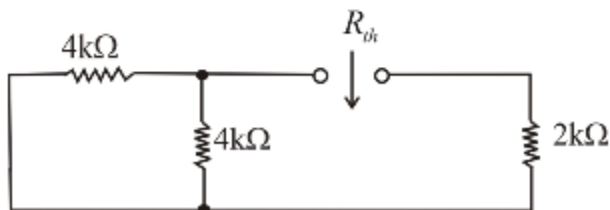
#### Step 7

Add/View Comments

Step 5. The thevenin equivalent resistance is calculated from



www.zeallsoft.com

Add/View Comments

$$R_{th} = 2k + (4k || 4k) \\ = 2k + 2k$$

$$R_{th} = 4k\Omega$$

Therefore, the circuit time constant is

$$\tau = R_{th} C \\ = (4 \times 10^3) (200 \times 10^{-6}) \\ \tau = 0.8s$$

### Step 9

Add/View Comments

$$\text{Step 6. } k_1 = V_0(\infty) \\ = 0V$$

$$k_2 = V_0(0^+) - V_0(\infty) \\ = -4 - 0 \\ = -4V$$

Therefore the solution is

$$V_0(t) = -4e^{-t/0.8} V$$



7.28


[Add/View Comments](#)

Step1.  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

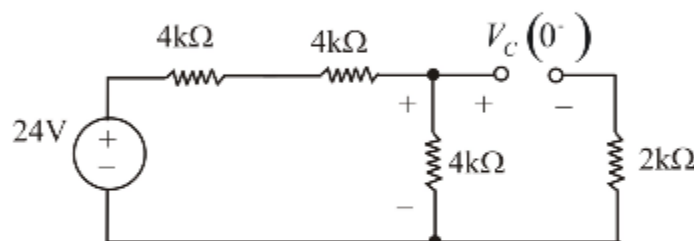**Step 2**

[Add/View Comments](#)

Step2. The initial voltage across the capacitor  $V_C(0^-)$  at  $t = 0^-$  is calculated from the circuit.



**Step 3**


[Add/View Comments](#)

Since there is a open circuit due to capacitor, no current flows through the  $2k\Omega$  and hence the voltage across the capacitors is same as the voltage across  $4k\Omega$   
By voltage division,

$$V_C(0^-) = 24 \times \frac{4k}{(4k + 4k + 4k)}$$


$$V_C(0^-) = 8V$$

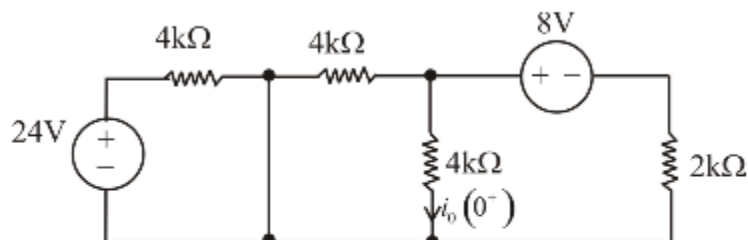Step3. The new circuit valid from  $t = 0^+$  is



### Step 5

Modified as,

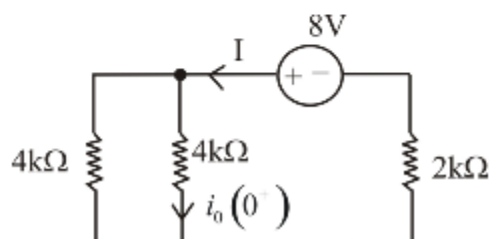

The total current  $I$  is given by

$$I = \frac{8}{2k + (4 \parallel 4)k}$$

$$= \frac{8}{(2 + 2)k}$$

$$= 2\text{mA}$$

By current division


$$i_0(0^+) = 2\text{mA} \times \frac{4k}{4k + 4k}$$

$$i_0(0^+) = 1\text{mA}$$
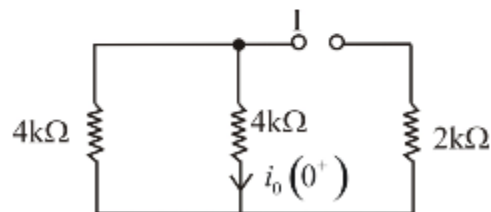
#### Step 7

[Add/View Comments](#)

Step 4. The equivalent circuit for  $t > 5\tau$




$$i_0(\infty) = 0\text{mA}$$

www.zeallsoft.com

Add/View Comments

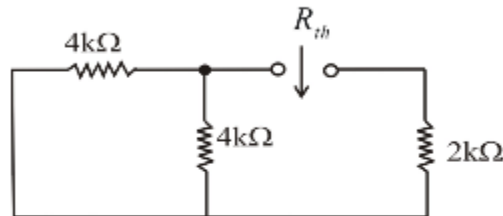Step 5. The Thevenin equivalent resistance is obtained from



### Step 9

Add/View Comments

$$R_{th} = 2k + 4k || 4k$$

$$= 2k + 2k$$

$$R_{th} = 4k\Omega$$

Therefore the circuit time constant is,

$$\tau = R_{th} C$$

$$= (4 \times 10^3) (200 \times 10^{-6})$$

$$\tau = 0.8s$$

www.zeallsoft.com

Add/View Comments

Step 6.  $k_1 = i_0(\infty)$

$$= 0mA$$

$$k_2 = i_0(0^+) - i_0(\infty)$$

$$= 1 - 0$$

$$= 1mA$$

Therefore the solution is,

$$i_0(t) = 1e^{-t/0.8} \text{ mA}$$

7.29


[Add/View Comments](#)

Step 1:  $V_0(t)$  is of the form  $k_1 + k_2 e^{-\frac{t}{\tau}}$

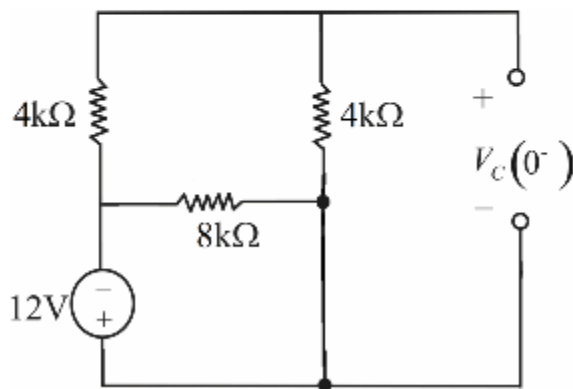**Step 2**

[Add/View Comments](#)

Step 2: The initial voltage across the capacitor is obtained from the circuit.




www.zeallsoft.com

**Step 3**

[Add/View Comments](#)

Redrawing the circuit carefully

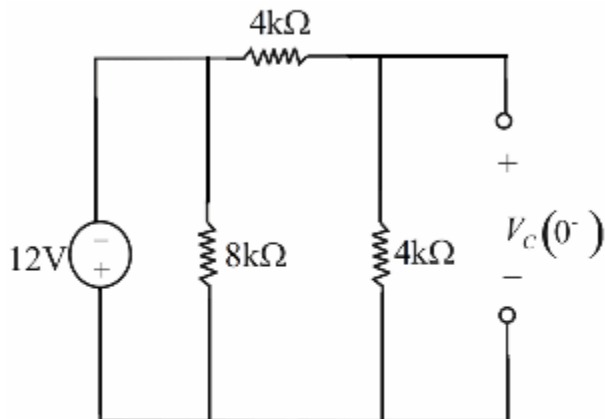

**Step 4**

[Add/View Comments](#)


Therefore by voltage division

$$V_C(0^-) = -12 \times \frac{4k}{4k + 4k}$$

$$= -12 \times \frac{4}{8}$$

$$V_C(0^-) = -6V$$

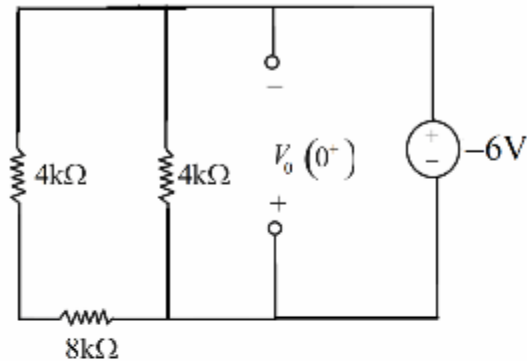Step 3: the new valid circuit at  $t = 0^+$  is




Therefore  $V_o(0^+) = 6\text{V}$
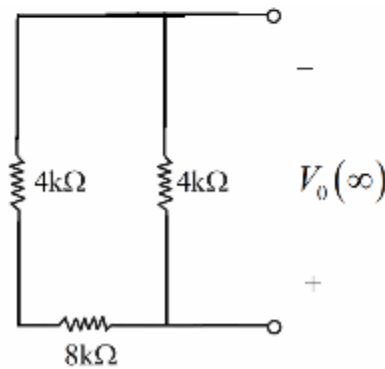
### Step 6


Add/View Comments

Step 4: The equivalent circuit for  $t > 5\tau$



Therefore  $V_o(\infty) = 0\text{V}$

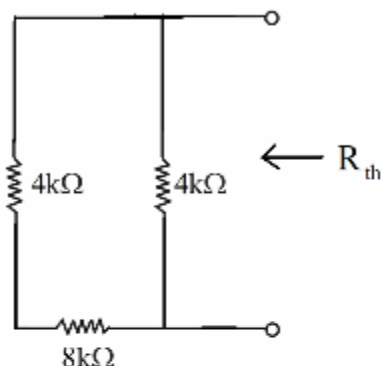Step 5: The Thevenin equivalent resistance is obtained by



### Step 8

Add/View Comments

$$\begin{aligned}
 R_{th} &= 4k \parallel (4k + 8k) \\
 &= 4k \parallel (12k) \\
 &= \frac{4k \times 12k}{4k + 12k} \\
 &= \frac{48k}{16} \\
 R_{th} &= 3 \text{ k}\Omega
 \end{aligned}$$

Therefore circuit time constant is

$$\begin{aligned}\tau &= R_{\text{th}} C \\ &= (3 \times 10^3) (50 \times 10^{-6}) \\ &= 0.15 \text{ s}\end{aligned}$$

### Step 10

Add/View Comments

$$\begin{aligned}\text{Step 6: } k_1 &= V_0(\infty) \\ &= 0 \text{ V} \\ k_2 &= V_0(0^+) - V_0(\infty) \\ &= 6 - 0 \\ &= 6 \text{ V}\end{aligned}$$

Therefore the solution is

$$V_0(t) = 6e^{-\frac{t}{0.15}} \text{ V}$$

$$V_0(t) = 6e^{-6.67t} \text{ V}$$


31

### 7.31

Add/View Comments


Step 1.  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

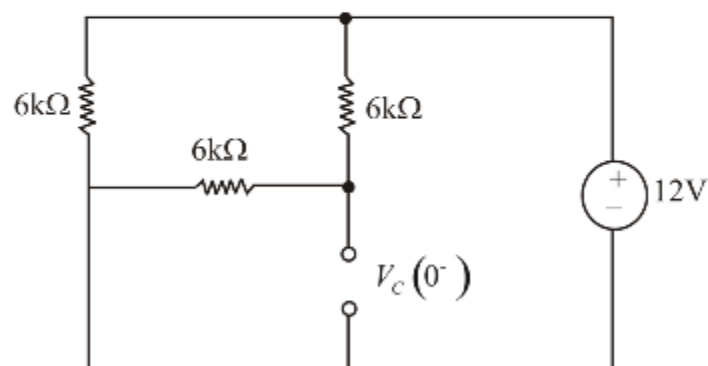Step 2. The initial voltage across the capacitor  $V_C(0^-)$  is obtained from the circuit.





The Circuit can be drawn as

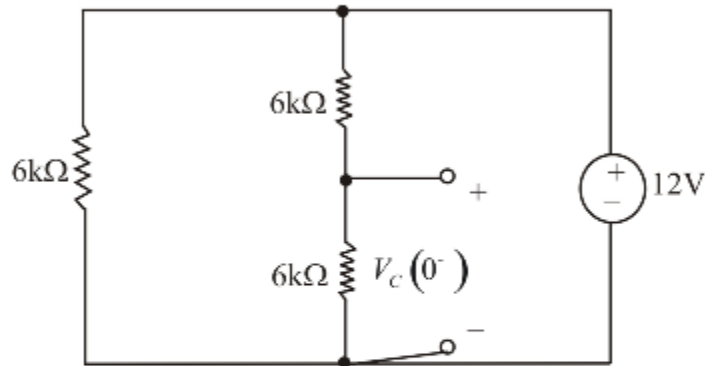

### Step 3


[Add/View Comments](#)

By voltage division

$$V_c(0^-) = \frac{6k}{(6k + 6k)}$$

$$V_c(0^-) = 6V$$

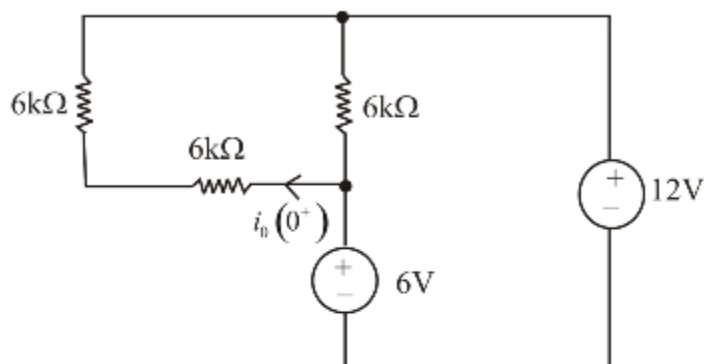
Step 3. The new valid circuit for  $t = 0^+$  is



Step 5

Add/View Comments

The circuit can be drawn as

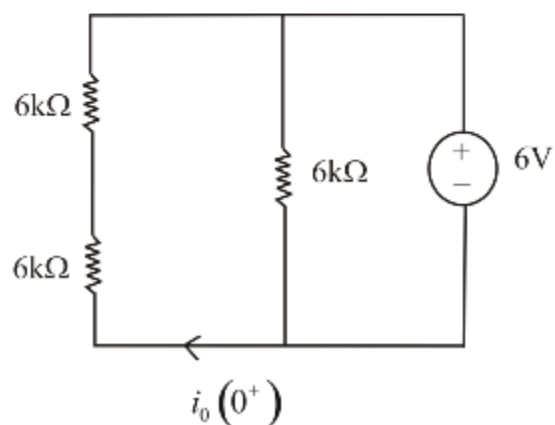

www.zeallsoft.com


Add/View Comments

$$\begin{aligned} \text{By } i_0(0^+) &= \frac{-6}{6k + 6k} \\ &= \frac{-6}{12k} \\ i_0(0^+) &= -\frac{1}{2} \text{ mA} \end{aligned}$$
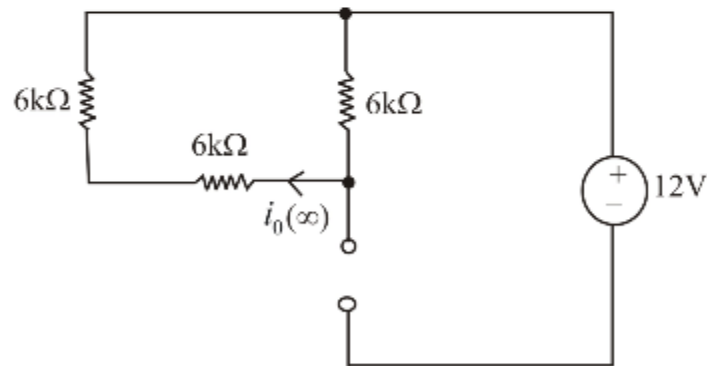
### Step 7

Add/View Comments

Step 4. The equivalent circuit for  $t > 5\tau$




$$i_0(\infty) = 0 \text{ mA}$$

www.zeallsoft.com

Add/View Comments

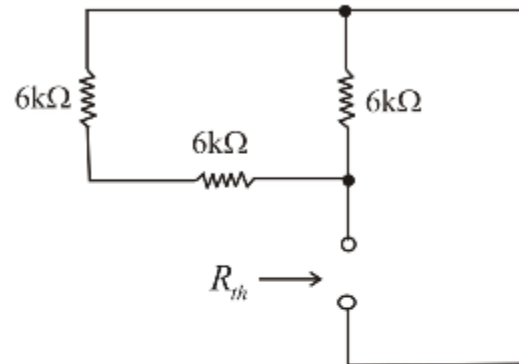Step 5. The Thevenin equivalent can be found by



Step 9

Add/View Comments

$$R_{th} = (6k \parallel (6k + 6))$$

$$= (6k \parallel 12k)$$

$$R_{th} = \frac{6 \times 12}{6 + 12}$$

$$R_{th} = 4k\Omega$$

Therefore, the circuit time constant is

$$\tau = R_{th} C$$

$$= 4 \times 10^3 \times 50 \times 10^{-6}$$

$$= 0.2s$$

www.zeallsoft.com

Add/View Comments

Step 6.  $k_1 = i_0(\infty)$

$$= 0 \text{ mA}$$

$$k_2 = i_0(0^+) - i_0(\infty)$$

$$= -\frac{1}{2} - 0$$

$$= -\frac{1}{2} \text{ mA}$$

Hence the solution is

$$i_0(t) = -\frac{1}{2} e^{-t/0.2} \text{ mA}$$

7.32


[Add/View Comments](#)

Step 1:  $i_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

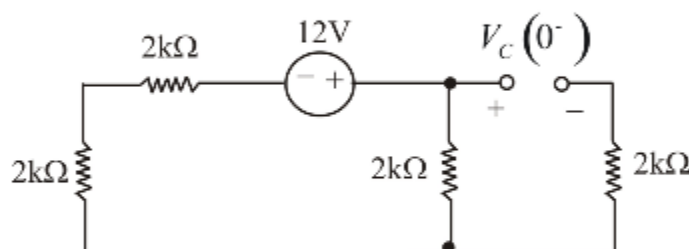**Step 2**

[Add/View Comments](#)

Step 2: the initial voltage across the capacitor is found by



**Step 3**

[Add/View Comments](#)

By voltage division


$$V_C(0^-) = 12 \times \frac{2k}{2k + 2k + 2k}$$

$$V_C(0^-) = 4V$$

www.zeallsoft.com

[Add/View Comments](#)

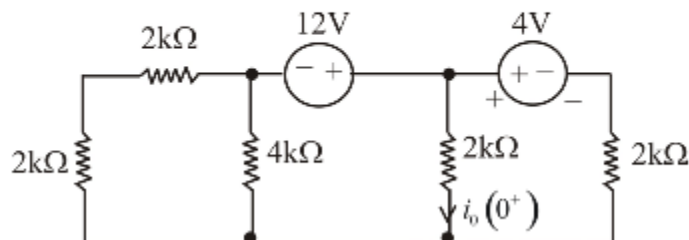
Step 3: The new valid circuit at  $t = 0^+$  is



Since the resistor  $2k\Omega$  and  $2k\Omega$  are in series and this combination in parallel with  $4k\Omega$

$$\begin{aligned} R_{eq} &= (2k + 2k) \parallel 4k \\ &= 4k \parallel 4k \\ &= 2k\Omega \end{aligned}$$

Step 6

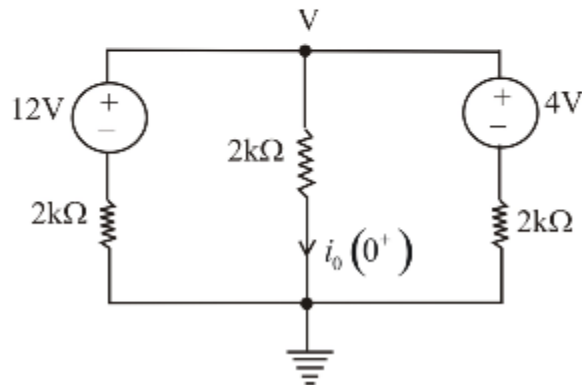

www.zeallsoft.com

[Add/View Comments](#)

Writing KCL equation at the top node,

$$\frac{V-12}{2k} + \frac{V}{2k} + \frac{V-4}{2k} = 0$$

$$3V - 16 = 0$$

$$V = \frac{16}{3} \text{ V}$$

$$i_0(0^+) = \frac{V}{2k}$$


$$= \frac{\left(\frac{16}{3}\right)}{2k}$$

$$i_0(0^+) = \frac{8}{3} \text{ mA}$$
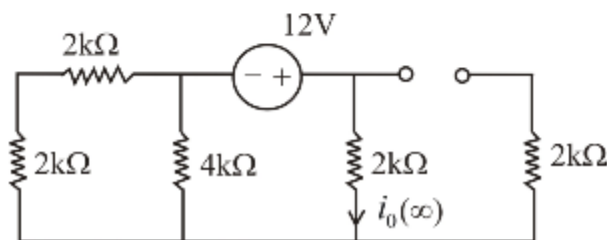
#### Step 8

[Add/View Comments](#)

Step 4: The equivalent circuit for  $t > 5\tau$



www.zeallsoft.com

[Add/View Comments](#)

$$i_0(\infty) = \frac{12}{2k + (4k \parallel (2k + 2k))}$$

$$= \frac{12}{2k(4k \parallel 4k)}$$


$$= \frac{12}{2k + 2k}$$

$$i_0(\infty) = 3 \text{ mA}$$
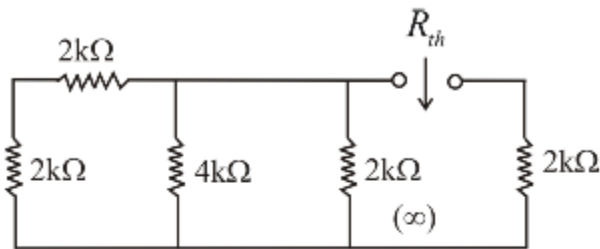
#### Step 10

[Add/View Comments](#)

Step 5: The Thevenin equivalent resistance can be found by looking into the open circuited terminals of the capacitor



### Step 12

[Add/View Comments](#)

$$\begin{aligned} R_{th} &= 2k + \left\{ 2k \parallel \left[ 4k \parallel (2k + 2k) \right] \right\} \\ &= 2k + \left\{ 2k \parallel [4k \parallel 4k] \right\} \\ &= 2k + \left\{ 2k \parallel 2k \right\} \\ &= 2k + 1k \end{aligned}$$

$$R_{th} = 3k\Omega$$

Therefore, the circuit time constant is

$$\begin{aligned} \tau &= R_{th} C \\ &= (3 \times 10^3)(200 \times 10^{-6}) \\ \tau &= 0.6s \end{aligned}$$

$$\begin{aligned} \text{Step 6: } k_1 &= i_0(\infty) \\ &= 3\text{mA} \\ k_2 &= i_0(0^+) - i_0(\infty) \\ &= \frac{8}{3} - 3 \\ &= -\frac{1}{3} \text{mA} \end{aligned}$$

Therefore the solution is

$$i_0(t) = 3 - \frac{1}{3} e^{-t/0.6} \text{ mA}$$



7.33


[Add/View Comments](#)

Step 1:  $V_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

Step 2

[Add/View Comments](#)

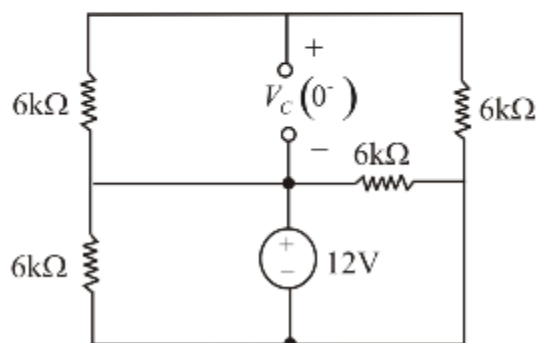Step 2: The initial voltage across the capacitor is obtained from the circuit.




www.zeallsoft.com

Step 3

[Add/View Comments](#)

Redrawing the circuit carefully

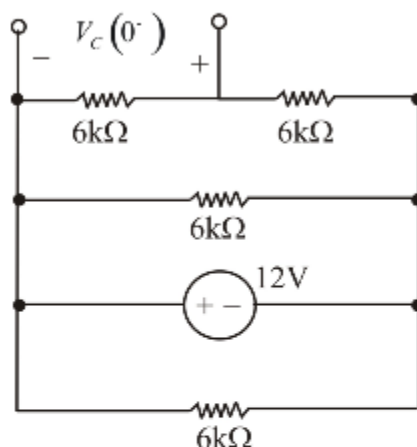

Step 4

[Add/View Comments](#)

Therefore by voltage division

$$V_c(0^-) = -12 \times \frac{6k}{6k + 6k}$$

$$= -12 \times \frac{6}{12}$$


$$V_c(0^-) = -6V$$

myUET

Give Suggestions at:

www.myUET.net.tc

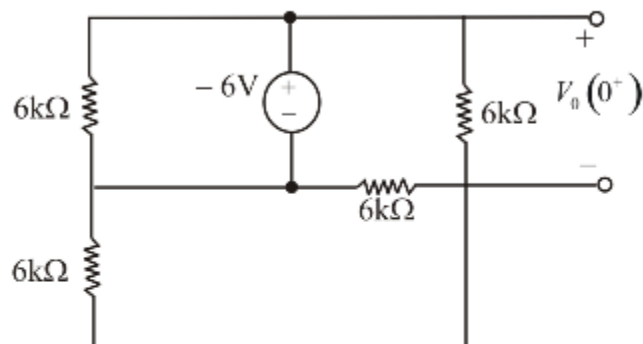
Step 3: the new valid circuit at  $t = 0^+$  is



### Step 6

Add/View Comments

The circuit can be redrawn as

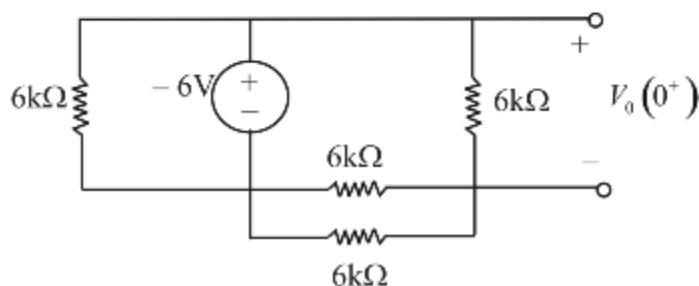

Give Suggestions at:

www.myUET.net.tc

By voltage division


$$\begin{aligned} V_0(0^+) &= -6 \left[ \frac{6k}{6k + (6k \parallel 6k)} \right] \\ &= -6 \left[ \frac{6k}{6k + 3k} \right] \\ &= -6 \left[ \frac{6}{9} \right] \end{aligned}$$

$$V_0(0^+) = -4V$$
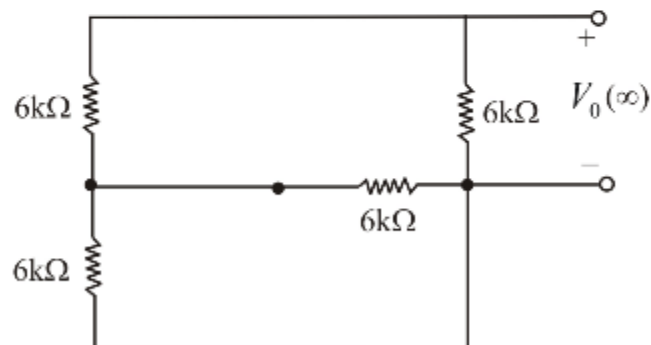
#### Step 8

Add/View Comments

Step 4: The equivalent circuit for  $t > 5\tau$




$$V_0(\infty) = 0V$$

www.zeallsoft.com

Step 9

Add/View Comments

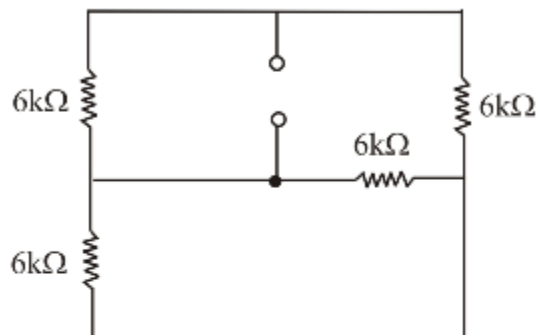
Step 5: The Thevenin equivalent resistance is obtained by



Step 10

Add/View Comments

The circuit can be redrawn as.

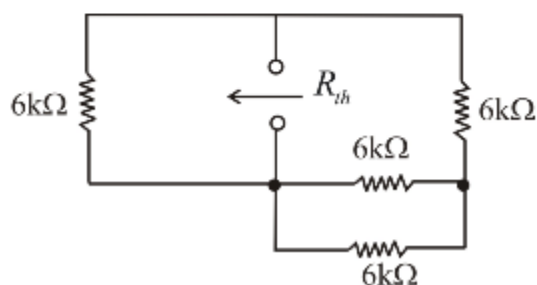

myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

www.zeallsoft.com

 Add/View Comments

$$\begin{aligned} R_{th} &= 6 \parallel (6 + (6 \parallel 6)) \\ &= 6 \parallel (6 + 3) \\ &= 6 \parallel 9 \\ &= \frac{6 \times 9}{6 + 9} \\ &= \frac{6 \times 9}{15} \\ R_{th} &= \frac{18}{5} \text{ k}\Omega \end{aligned}$$

#### Step 12

 Add/View Comments

Therefore circuit time constant is

$$\begin{aligned} \tau &= R_{th} C \\ &= \left( \frac{18}{5} \times 10^3 \right) (50 \times 10^{-6}) \\ &= 0.180 \text{ s} \end{aligned}$$

www.zeallsoft.com

 Add/View Comments

$$\begin{aligned} \text{Step 6: } k_1 &= V_0(\infty) \\ &= 0 \text{ V} \\ k_2 &= V_0(0^+) - V_0(\infty) \\ &= -4 - 0 \\ &= -4 \text{ V} \end{aligned}$$

Therefore the solution is

$$\boxed{V_0(t) = -4e^{-t/0.18} \text{ V}}$$

7.34


[Add/View Comments](#)

Step 1:  $i_0(t)$  is in the form  $k_1 + k_2 e^{-t/\tau}$

Step 2

[Add/View Comments](#)

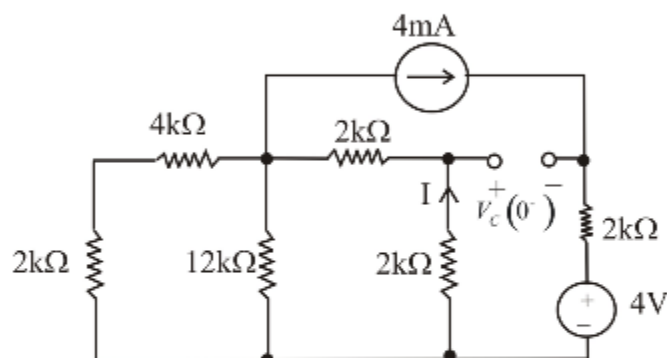Step 2: The initial voltage across the capacitor can be found by



myUET

Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

Resistor  $4k\Omega$ ,  $2k\Omega$  are in series and this in parallel with  $12k\Omega$

$$\begin{aligned} R_{eq} &= 12k \parallel (4k + 2k) \\ &= 12k \parallel 6k \\ &= \frac{12 \times 6}{12 + 6} \end{aligned}$$

$$R_{eq} = 4k\Omega$$

By current division,

$$I = (4m) \left[ \frac{4k}{4k + 2k + 2k} \right]$$

$$I = 2mA$$


And hence KVL across the loop

$$(2m)(2k) + V_C(0^-) + (2k)(4m) + 4 = 0$$

$$4 + V_C(0^-) + 8 + 4 = 0$$

$$V_C(0^-) = -16V$$

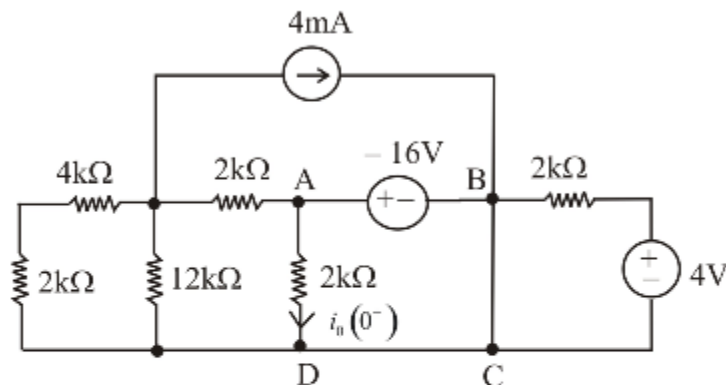Step 3: The new valid circuit for  $t = 0^+$  is



### Step 5


In the closed loop BADC applying KVL

$$-(-16) + 2k i_0(0^+) = 0$$

$$i_0(0^+) = \frac{-16}{2k}$$

$$i_0(0^+) = -8mA$$

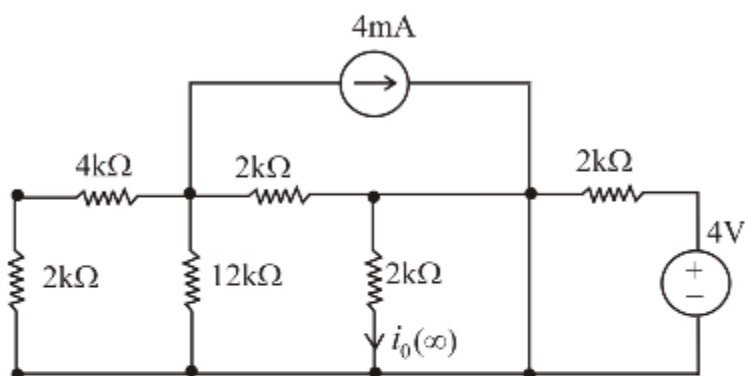Step 4: The equivalent circuit for  $t > 5\tau$



Step 7

Add/View Comments

$$i_0(\infty) = (-4\text{mA}) \left[ \frac{4\text{k}}{4\text{k} + 4\text{k}} \right]$$

$$i_0(\infty) = -2\text{mA}$$

Since the resistors 4k, 2k are in series and this in parallel with 12kΩ.


$$R_{eq} = 12\text{k} \parallel (4\text{k} + 2\text{k})$$

$$= 12\text{k} \parallel 6\text{k}$$

$$R_{eq} = 4\text{k}\Omega$$



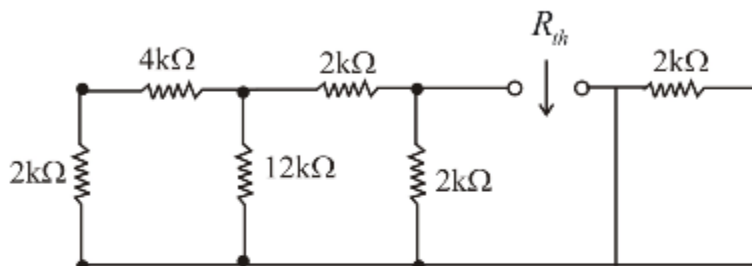Step 5: The Thevenin resistance can be found by



Step 9

[Add/View Comments](#)

$$\begin{aligned}
 R_{th} &= \left\{ \left[ (4k + 2k) \parallel 12k \right] + 2k \right\} \parallel 2k \\
 &= \left\{ [6k \parallel 12k] + 2k \right\} \parallel 2k \\
 &= \{ 4k \parallel 2k \} \parallel 2k \\
 &= 6k \parallel 2k \\
 &= \frac{6 \times 2}{6 + 2} k \\
 &= \frac{12}{8} k \\
 R_{th} &= \frac{3}{2} k\Omega
 \end{aligned}$$



Give Suggestions at:

[www.myUET.net.tc](http://www.myUET.net.tc)

Therefore, the circuit time constant is

$$\begin{aligned}\tau &= R_{\text{eq}} C \\ &= \frac{3}{2} \times 10^3 \times 100 \times 10^{-6} \\ \tau &= 0.15 \text{ s}\end{aligned}$$

#### Step 11

Add/View Comments

$$\begin{aligned}\text{Step 6: } k_1 &= i_0(\infty) \\ &= -2 \text{ mA} \\ k_2 &= i_0(0^+) - i_0(\infty) \\ &= -8 + 2 \\ &= -6 \text{ mA}\end{aligned}$$

Therefore the solution is

$$i_0(t) = -2 - 6e^{-t/0.15} \text{ mA}$$

7.35


[Add/View Comments](#)

Step 1:  $V_0(t)$  is of the form  $k_1 + k_2 e^{-t/\tau}$

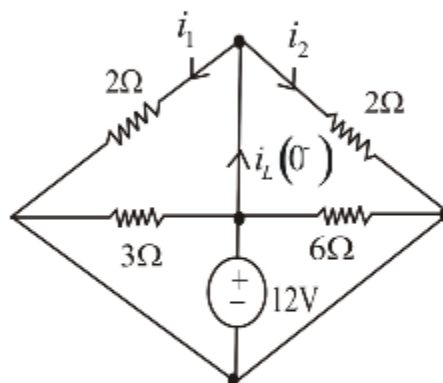**Step 2**

[Add/View Comments](#)

Step 2: The initial current through the inductor  $i_L(0^-)$  is found by



**Step 3**

[Add/View Comments](#)

Observe carefully, we see that the voltage across each element is the same i.e. 12V, due to the short circuited inductor KCL at the top node gives.

$$\begin{aligned} i_L(0^-) &= i_1 + i_2 \\ &= \frac{12}{2} + \frac{12}{2} \\ &= 6 + 6 \end{aligned}$$

$$i_L(0^-) = 12\text{A}$$




Give Suggestions at:

www.myUET.net.tc

www.zeallsoft.com has been challenged - view comments for detail

Add/View Comments (1)

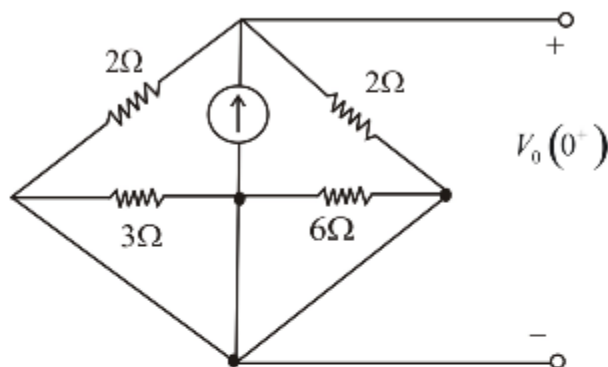
Step 3: The new valid circuit at  $t = 0^+$



### Step 5

Add/View Comments

This circuit can be redrawn as

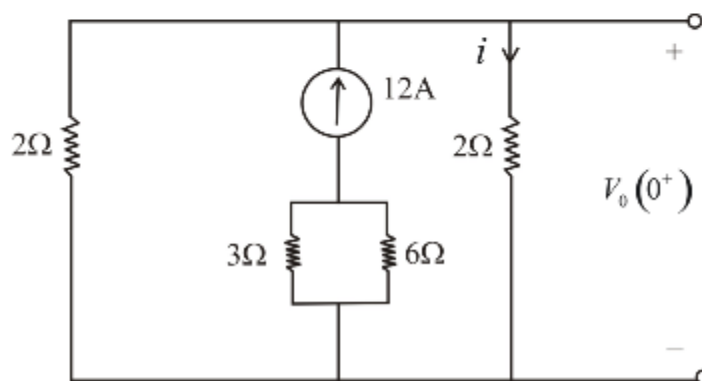

www.zeallsoft.com

Add/View Comments

By current division, current through  $2\Omega$  is

$$i = 12 \times \frac{2}{2+2} = 6A$$

Therefore  $V_o(0^+) = (6)(2)$

$$V_o(0^+) = 12V$$

myUET

Give Suggestions at:


www.myUET.net.tc

www.zeallsoft.com

Step 7

Add/View Comments

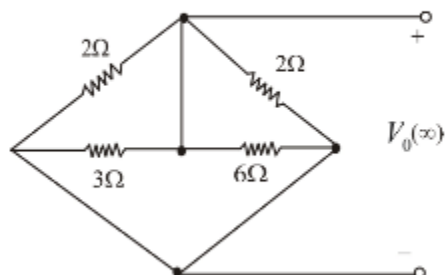Step 4: The equivalent circuit at  $t = 5\tau$




$$V_0(\infty) = 0V$$

www.zeallsoft.com

Step 5

Add/View Comments

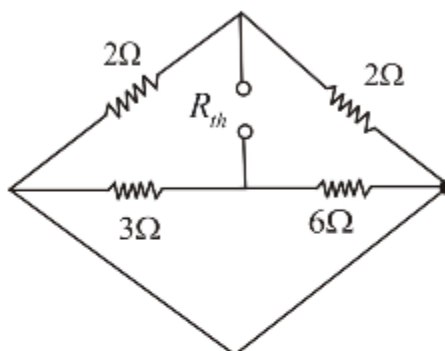
Step 5: The thevenin equivalent resistance is found by



Step 9

Add/View Comments

This circuit is redrawn as

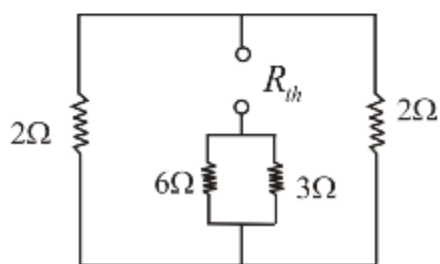

[www.zeallsoft.com](http://www.zeallsoft.com)

[Add/View Comments](#)

$$R_{th} = (6 \parallel 3) + (2 \parallel 2)$$

$$= 2 + 1$$

$$R_{th} = 3\Omega$$

Therefore circuit time constant is

$$\tau = \frac{L}{R_{th}}$$

$$= \frac{2}{3}$$

$$\tau = 0.67s$$

#### Step 11

[Add/View Comments](#)

$$\text{Step 6: } k_1 = V_0(\infty)$$

$$= 0$$

$$k_2 = V_0(0^+) - V_0(\infty)$$

$$= 12 - 0$$

$$= 12$$

Therefore the solution is


$$V_0(t) = 12e^{-t/0.67} \text{ V}$$



Give Suggestions at:

[www.myUET.net.tc](http://www.myUET.net.tc)

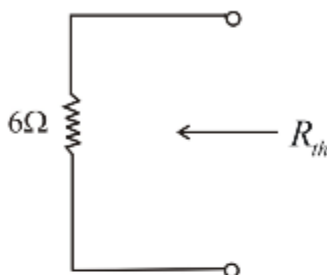Step 5: The Thevenin equivalent resistance is obtained from



$$R_{th} = 6\Omega$$

### Step 6

Add/View Comments

Therefore the circuit time constant is,

$$\begin{aligned}\tau &= \frac{L}{R_{th}} \\ &= \frac{2}{6} \\ &= \frac{1}{3} s \\ &= 0.33s\end{aligned}$$



Connecting UETians Together

[www.myUET.net.tc](http://www.myUET.net.tc)

Online Community of UETians

**8.6** Calculate the current in the resistor in Fig. P8.6 if the voltage input is

(a)  $v_1(t) = 10 \cos(377t + 180^\circ) \text{ V}$ .

(b)  $v_2(t) = 12 \sin(377t + 45^\circ) \text{ V}$ .

Give the answers in both the time and frequency domains.

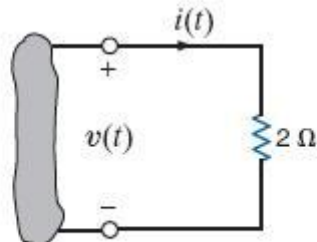



Figure P8.6

Download any solution manual for free

All Departments, All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**SOLUTION:**

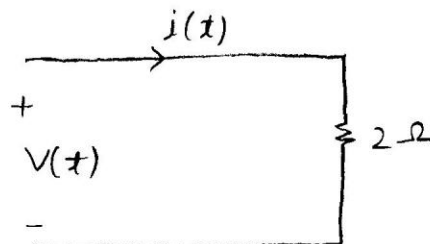

CREATE YOUR OWN WEB  
PAGE

VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

(a)  $v_1(t) = 10 \cos(377t + 180^\circ) \text{ V}$

$$i(t) = \frac{10}{2} \cos(377t + 180^\circ)$$

$$i(t) = 5 \cos(377t + 180^\circ) \text{ A}$$

$$\bar{I} = 5 \angle 180^\circ \text{ A}$$

(b)  $v_2(t) = 12 \sin(377t + 45^\circ) \text{ V}$

$$v_2(t) = 12 \cos(377t - 45^\circ) \text{ V}$$

$$i(t) = 6 \cos(377t - 45^\circ) \text{ A}$$

$$\bar{I} = 6 \angle -45^\circ \text{ A}$$



**8.7** Calculate the current in the capacitor shown in Fig. P8.7 if the voltage input is

(a)  $v_1(t) = 10 \cos(377t - 30^\circ) \text{ V}$

(b)  $v_2(t) = 5 \sin(377t + 60^\circ) \text{ V}$

Give the answers in both the time and frequency domains.

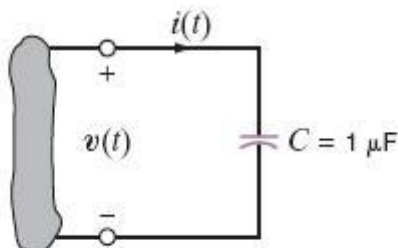



Figure P8.7

Download any solution manual for free

All Departments, All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**SOLUTION:**

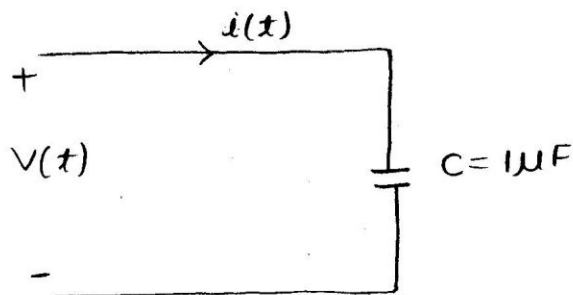

(a)  $v_1(t) = 10 \cos(377t - 30^\circ) \text{ V}$

$$i(t) = C \frac{dv_1(t)}{dt}$$

$$\frac{dv_1(t)}{dt} = -3770 \sin(377t - 30^\circ)$$

$$i(t) = (1 \times 10^{-6}) (-3770 \sin(377t - 30^\circ))$$

$$i(t) = -3.77 \sin(377t - 30^\circ) \text{ mA}$$

$$i(t) = 3.77 \sin(377t + 150^\circ) \text{ mA}$$

$$i(t) = 3.77 \cos(377t + 60^\circ) \text{ mA}$$

$$\bar{I} = 3.77 \angle 60^\circ \text{ mA}$$

$$\begin{aligned} (b) \quad v_2(t) &= 5 \sin(377t + 60^\circ) \text{ V} \\ v_2(t) &= 5 \cos(377t - 30^\circ) \text{ V} \\ i(t) &= C \frac{dv_2(t)}{dt} \end{aligned}$$

$$\frac{dv_2(t)}{dt} = -1885 \sin(377t - 30^\circ)$$

$$i(t) = (1 \times 10^{-6}) (-1885 \sin(377t - 30^\circ))$$

$$i(t) = -1.89 \sin(377t - 30^\circ) \text{ mA}$$

$$i(t) = 1.89 \sin(377t + 150^\circ) \text{ mA}$$

$$i(t) = 1.89 \cos(377t + 60^\circ) \text{ mA}$$

$$\bar{I} = 1.89 \angle 60^\circ \text{ mA}$$

Download any solution manual for free

All Departments, All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

Simpopdf Merge and Split Unregistered Version - <http://www.simpopdf.com>

**8.11** Find the frequency-domain impedance,  $\bar{Z}$ , as shown in Fig. P8.11.


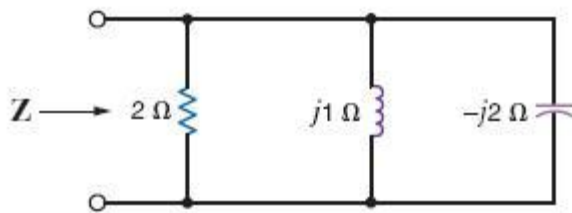


Figure P8.11

CREATE YOUR OWN WEB  
PAGE  
VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

**SOLUTION:**

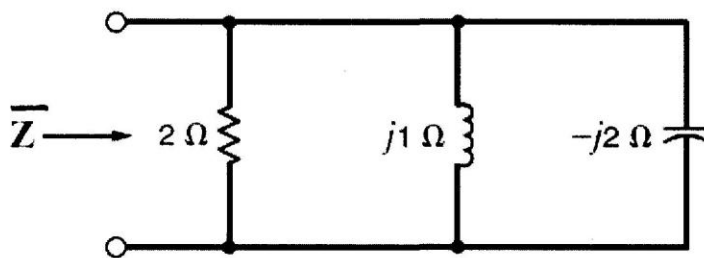

$$\bar{Z} = [-j2 \parallel j1] \parallel 2$$

$$\bar{Z} = \left[ \frac{-j2(j1)}{-j2 + j1} \right] \parallel 2$$

$$\bar{Z} = \frac{(2 \angle 90^\circ)(2 \angle 0^\circ)}{2 \angle 90^\circ + 2 \angle 0^\circ}$$

$$\bar{Z} = 1.414 \angle 45^\circ \Omega$$

Download any solution manual for free

All Departments, All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**8.12** Find the impedance,  $Z$ , shown in Fig. P8.12 at a frequency of 60 Hz.


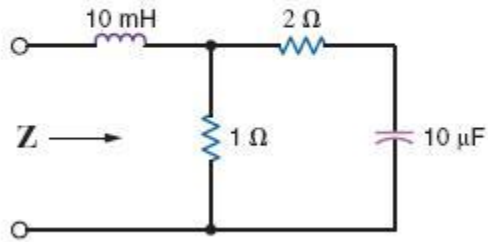



Figure P8.12

**SOLUTION:**

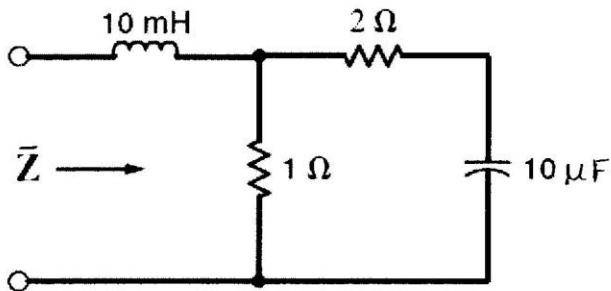

$$\bar{Z}_L = j(377)(10\text{m}) = j3.77\Omega$$
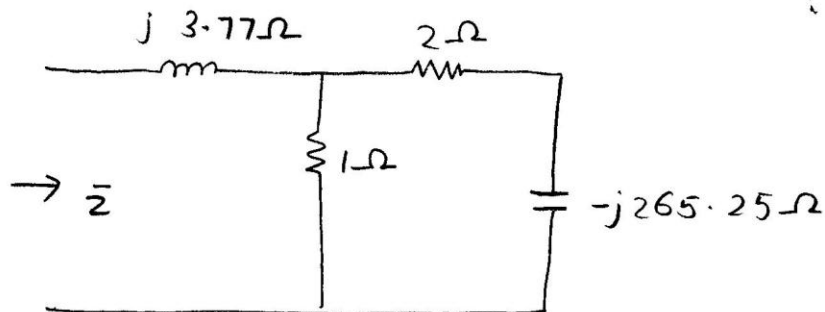
$$\bar{Z}_C = \frac{1}{j(377)(10\mu)} = -j265.25\Omega$$



$$\bar{Z} = [1 \parallel 2 - j265.25] + j3.77$$

$$\bar{Z} = \frac{1(2 - j265.25)}{1 + 2 - j265.25} + j3.77$$

$$\bar{Z} = 1 + j3.77 \Omega$$

[www.myUET.net.tc](http://www.myUET.net.tc)

Request a solution Now

And

Get it within one week

Absolutely free

*"We Feel Your Feelings..!"*

- 8.25** Find the frequency at which the circuit shown in Fig. P8.25 is purely resistive.


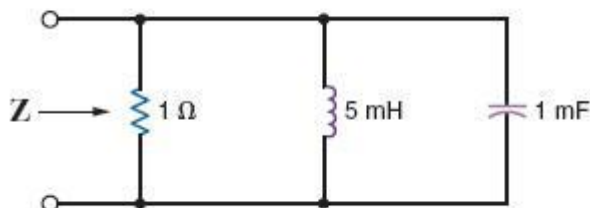


Figure P8.25

**SOLUTION:**

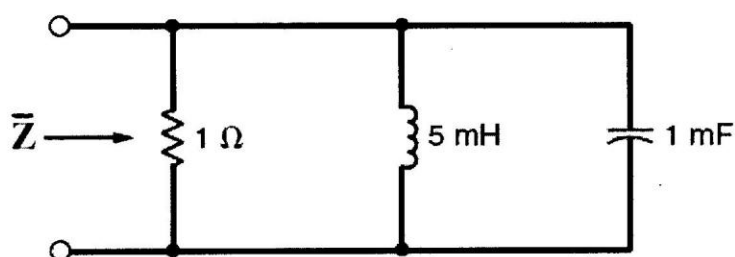

$$\bar{Z} = R_{eq}^Y$$

$$eq =$$

$$= \frac{1}{R} + \frac{1}{\bar{Z}_L} + \frac{1}{\bar{Z}_C}$$

$$\frac{1}{\omega L} = \omega C$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5m(1m)}} = 447.21 \text{ rad/s}$$

$$F = \frac{\omega}{2\pi} = \frac{447.21}{2\pi}$$

$$F = 71.2 \text{ Hz}$$

[www.myUET.net.tc](http://www.myUET.net.tc)

Request a solution Now

And

Get it within one week

Absolutely free

*“We Feel Your Feelings..!”*

- 8.29** Draw the frequency-domain network and calculate  $i(t)$  in the circuit shown in Fig. P8.29 if  $v_s(t)$  is  $15 \sin(10000t)$  V. Also, using a phasor diagram, show that  $v_C(t) + v_R(t) = v_s(t)$ .


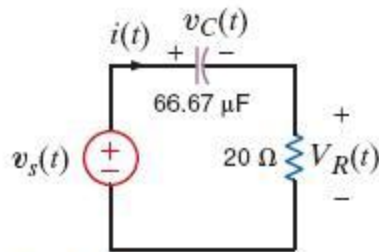


Figure P8.29

**SOLUTION:**

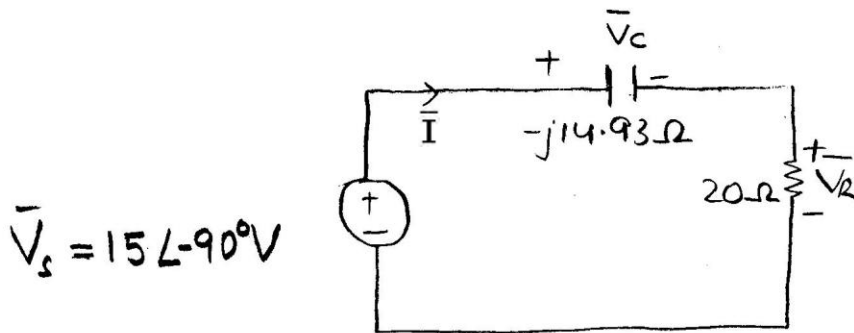

$$\bar{Z}_C = \frac{1}{j(10000)(66.67 \mu)}$$

$$\bar{Z}_C = -j14.93 \Omega$$

$$V_s(t) = 15 \sin 10000t \text{ V}$$

$$V_s(t) = 15 \cos(10000t - 90^\circ) \text{ V}$$

$$\bar{V}_s = 15 \angle -90^\circ \text{ V}$$

$$\bar{I} = \frac{15 \angle -90^\circ}{20 - j14.93}$$



$$\bar{I} = 0.6 \angle 53.26^\circ \text{ A}$$


$$i(t) = 0.6 \cos(1000t - 53.26^\circ) \text{ A}$$

$$\bar{V}_C = (0.6 \angle -53.26^\circ) (-j14.93)$$

$$\bar{V}_C = 8.96 \angle -143.26^\circ \text{ V}$$

$$\bar{V}_R = (0.6 \angle -53.26^\circ) (20)$$
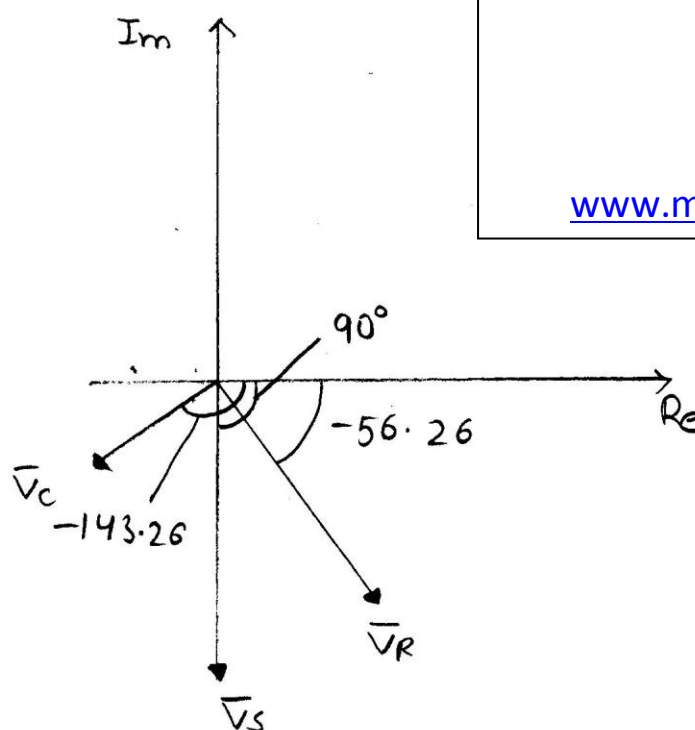
$$\bar{V}_R = 12 \angle -53.26^\circ \text{ V}$$



CREATE YOUR OWN WEB  
PAGE  
VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

- 8.33** If  $v_s(t) = 20 \cos 5t$  volts, find  $v_o(t)$  in the network in Fig. P8.33.

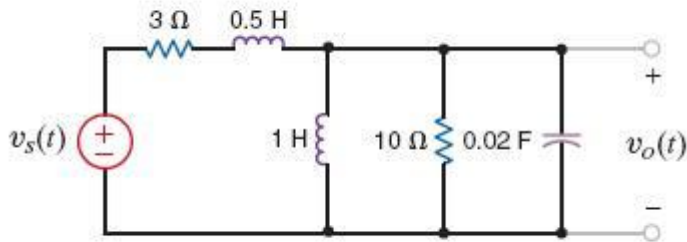



Figure P8.33

**SOLUTION:**

$$\bar{Z}_{L_1} = j5(0.5) = j2.5 \Omega$$

$$\bar{Z}_{L_2} = j(5)(1) = j5 \Omega$$
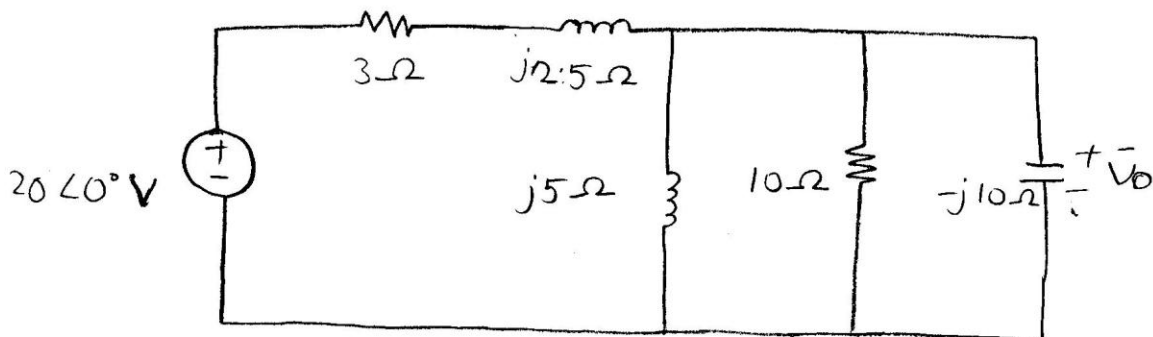
$$\bar{Z}_C = \frac{1}{j(5)(0.02)} = -j10 \Omega$$



$$\bar{Z}_1 = (-j10 \parallel 10) \parallel j5$$

$$\bar{Z}_1 = \left[ \frac{-j10(10)}{10 - j10} \right] \parallel j5$$

$$\bar{Z}_1 = 7.07 \angle +45^\circ \Omega$$

$$\bar{V}_o = \left( \frac{7.07 \angle +45^\circ}{7.07 \angle +45^\circ + 3 + j2.5} \right) (20 \angle 0^\circ)$$

$$\bar{V}_o = 12.9 \angle 1.85^\circ \text{ V}$$

$$v_o(t) = 12.9 \cos(5t + 1.85^\circ) \text{ V}$$

[www.myUET.net.tc](http://www.myUET.net.tc)

Request a solution Now

And

Get it within one week

Absoluteley free

*"We Feel Your Feelings..!"*

8.35 Find  $v(t)$  in the network in Fig. P8.35.


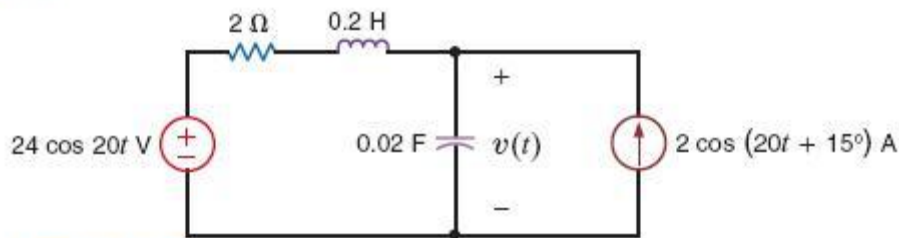
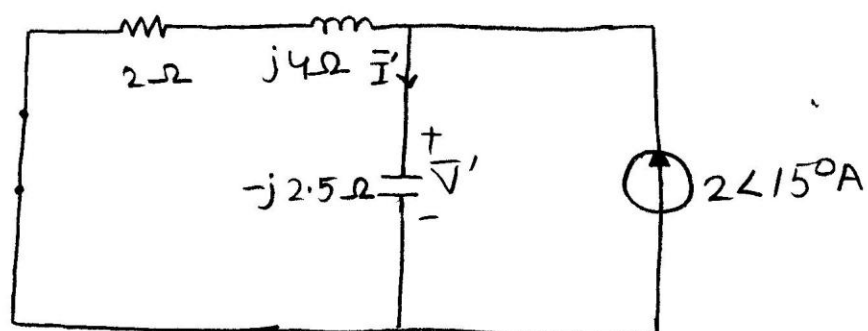


Figure P8.35

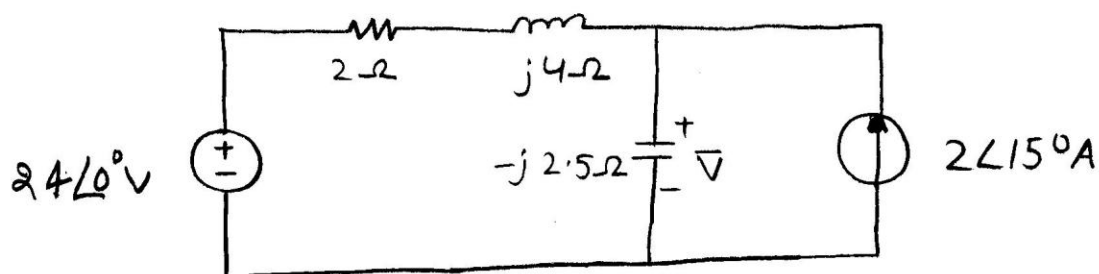**SOLUTION:**

$$\bar{Z}_L = j(20)(0.2) = j4\Omega$$


$$\bar{Z}_C = \frac{1}{j(20)(0.02)} = -j2.5\Omega$$



$$\bar{I}' = \left( \frac{2 + j4}{2 + j4 - j2.5} \right) (2 \angle 15^\circ)$$

$$\bar{V}' = (3.58 \angle 41.57^\circ) (-j2.5)$$
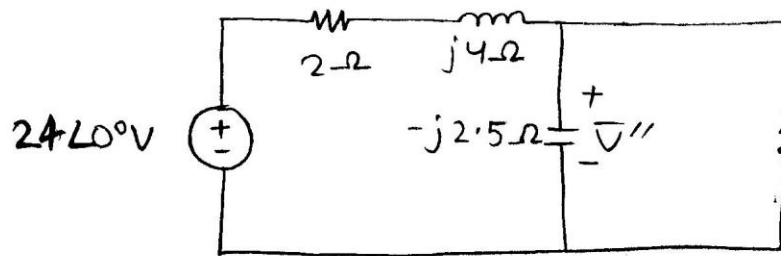
$$\bar{V}' = 8.94 \angle -48.43^\circ \text{ V}$$



$$\bar{V}'' = \left( \frac{-j2.5}{-j2.5 + j4 + 2} \right) (24\angle 0^\circ)$$

$$\bar{V}'' = 24 \angle -126.87^\circ \text{ V}$$

$$\bar{V} = \bar{V}' + \bar{V}'' = 8.94 \angle -48.43^\circ + 24 \angle -126.87^\circ$$

$$\bar{V} = 27.24 \angle -108.1^\circ \text{ V}$$

$$v(t) = 27.24 \cos(20t - 108.1^\circ) \text{ V}$$

**8.38** Find  $i_1(t)$  and  $i_2(t)$  in the circuit in Fig. P8.38.

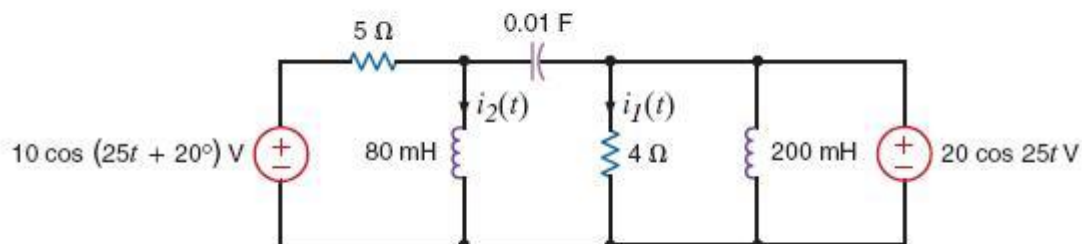




Figure P8.38

**SOLUTION:**


$$\bar{Z}_{L_1} = j(25)(80\text{m}) = j2\Omega$$

$$\bar{Z}_{L_2} = j(25)(200\text{m}) = j5\Omega$$
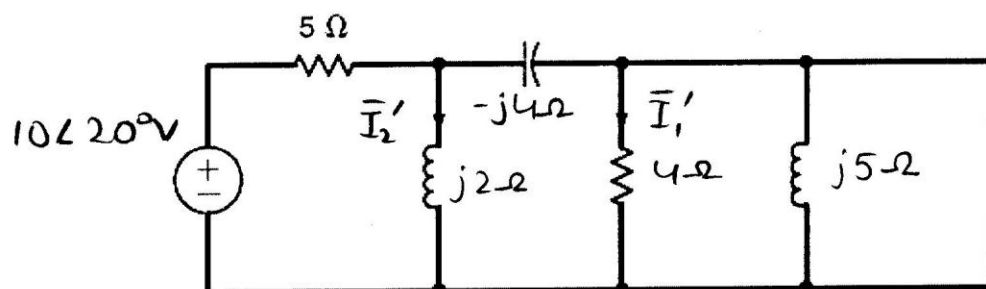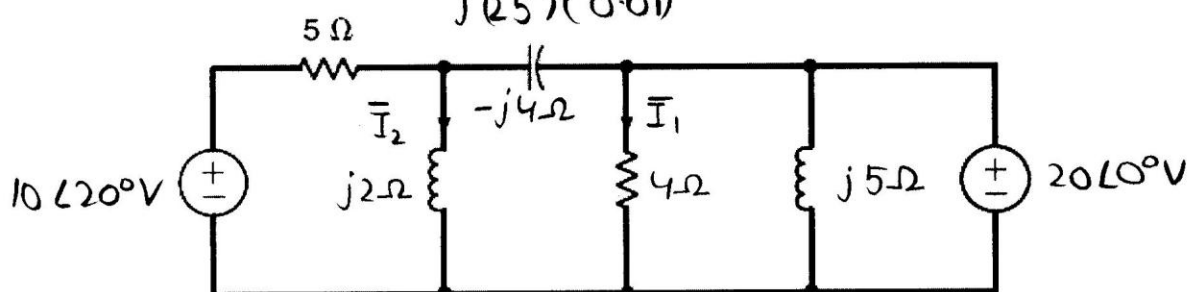
$$\bar{Z}_C = \frac{1}{j(25)(0.01)} = -j4\Omega$$



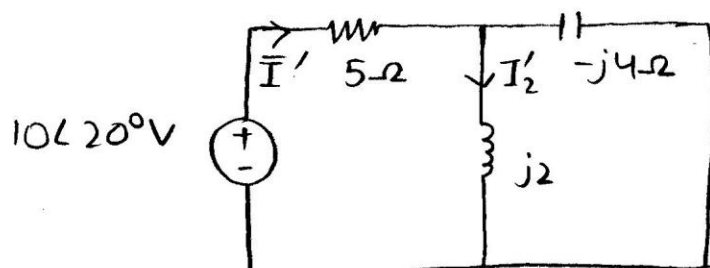
$\bar{I}_1' = 0\text{A}$ , short across  $4\Omega$ .



$$\bar{I}' = \frac{10 \angle 20^\circ}{(j2 \parallel -j4) + 5} = 1.56 \angle -18.66^\circ \text{ A}$$

$$\bar{I}_2' = \left( \frac{-j4}{-j4 + j2} \right) (1.56 \angle -18.66^\circ)$$
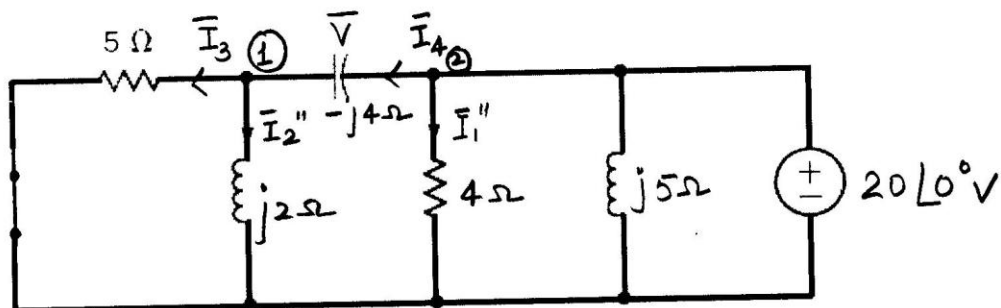
$$\bar{I}_2' = 3.12 \angle -18.66^\circ \text{ A}$$



$$\bar{I}_1'' = 20 \angle 0^\circ = 5 \angle 0^\circ \text{ A}$$

$$\text{KCL at (1): } \bar{I}_2'' + \bar{I}_3 = \bar{I}_4$$

$$\frac{\bar{V}_1}{j2} + \frac{\bar{V}_1}{5} = \frac{\bar{V}_2 - \bar{V}_1}{-j4}$$

$$10\bar{V}_1 + j4\bar{V}_1 = -5\bar{V}_2 + 5\bar{V}_1$$

$$(5 + j4)\bar{V}_1 + 5\bar{V}_2 = 0$$

$$\bar{V}_2 = 20 \angle 0^\circ \text{ V}$$

$$\bar{V}_1 = \frac{-5(20 \angle 0^\circ)}{5 + j4}$$

$$\bar{V}_1 = 15.62 \angle 141.34^\circ \text{ V}$$

$$\bar{I}_2'' = \frac{\bar{V}_1}{j2} = \frac{15.62 \angle 141.34^\circ}{j2}$$

$$\bar{I}_2'' = 7.81 \angle 51.34^\circ \text{ A}$$

$$\bar{I}_1 = \bar{I}_1' + \bar{I}_1'' = 0 + 5 \angle 0^\circ$$

$$\bar{I}_1 = 5 \angle 0^\circ \text{ A}$$

$$i_1(t) = 5 \cos 25t \text{ A}$$

$$\bar{I}_2 = \bar{I}_2' + \bar{I}_2'' = 3.12 \angle -18.66^\circ + 7.81 \angle 51.34^\circ$$

$$\bar{I}_2 = 9.35 \angle 33.1^\circ \text{ A}$$

$$i_2(t) = 9.35 \cos(25t + 33.1^\circ) \text{ A}$$

[www.myUET.net.tc](http://www.myUET.net.tc)

Request a solution Now

And

Get it within one week

Absolute free

*"We Feel Your Feelings..!"*



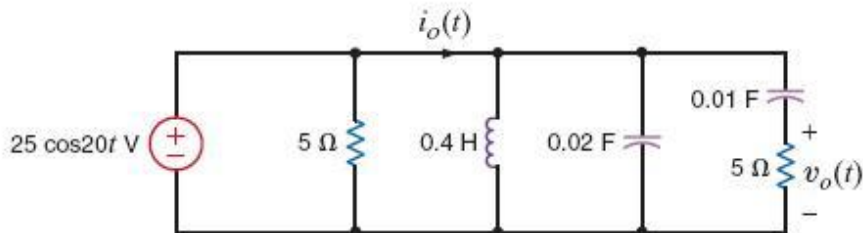
**8.39** Find  $v_o(t)$  and  $i_o(t)$  in the network in Fig. P8.39.


Figure P8.39

**SOLUTION:**

$$\bar{Z}_L = j(20)(0.4) = j8\Omega$$

$$\bar{Z}_{c1} = \frac{1}{j(20)(0.02)} = -j2.5\Omega$$
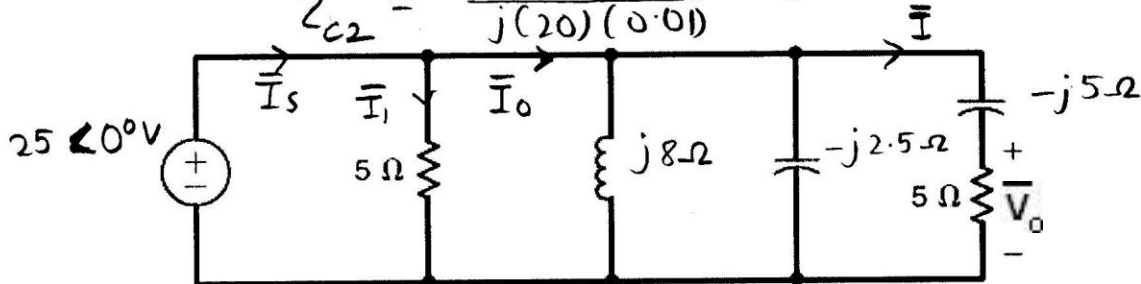
$$\bar{Z}_{c2} = \frac{1}{j(20)(0.01)} = -j5\Omega$$



$$\bar{I} = \frac{25\angle 0^\circ}{5 - j5} = 3.54\angle 45^\circ \text{ A}$$

$$\bar{V}_o = (3.54\angle 45^\circ)(5)$$

$$\bar{V}_o = 17.68\angle 45^\circ \text{ V}$$

$$v_o(t) = 17.68 \cos(20t + 45^\circ) \text{ V}$$

$$\bar{I}_1 = \frac{25\angle 0^\circ}{5} = 5\angle 0^\circ \text{ A}$$

$$\bar{Z}_{eq} = [(5 - j5) \parallel -j2.5] \parallel j8 \parallel 5$$

$$\bar{Z}_{eq} = \left[ \frac{(5-j5)(-j2.5)}{5-j5-j2.5} \right] \parallel j8 \parallel 15$$

$$\bar{Z}_{eq} = (1.96 \angle -78.7^\circ \parallel j8) \parallel 15$$

$$\bar{Z}_{eq} = 2.57 \angle -75.08^\circ \parallel 15$$

$$\bar{Z}_{eq} = 2.08 \angle -51.4^\circ \Omega$$

$$\bar{I}_s = \frac{25 \angle 0^\circ}{2.08 \angle -51.4^\circ} = 12.02 \angle 51.4^\circ \text{ A}$$

$$\text{KCL: } \bar{I}_s = \bar{I}_1 + \bar{I}_0$$

$$\bar{I}_0 = \bar{I}_s - \bar{I}_1$$

$$\bar{I}_0 = 12.02 \angle 51.4^\circ - 5 \angle 0^\circ$$

$$\bar{I}_0 = 9.72 \angle 75.1^\circ \text{ A}$$

$$i_o(t) = 9.72 \cos(20t + 75.1^\circ) \text{ A}$$

**8.43** Find the voltage  $V$  shown in Fig. P8.43.


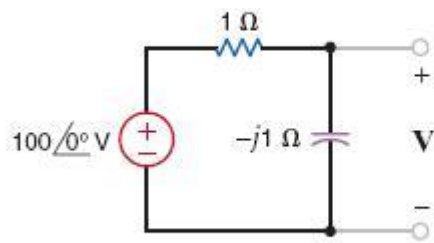


Figure P8.43

**SOLUTION:**

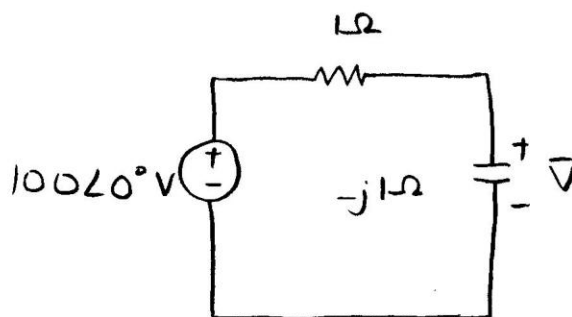

$$\bar{V} = \left( \frac{-j1}{1-j1} \right) (100\angle 0^\circ)$$

$$\bar{V} = 70.71 \angle -45^\circ \text{ V}$$

Download any solution manual for free

All Departments , All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**8.45** Find the frequency-domain current  $\mathbf{I}$ , as shown in Fig. P8.45.


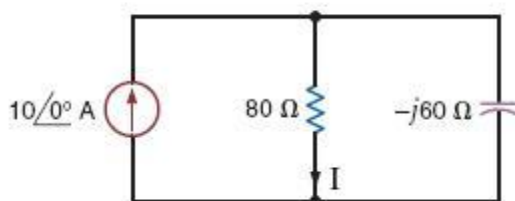


Figure P8.45

**SOLUTION:**

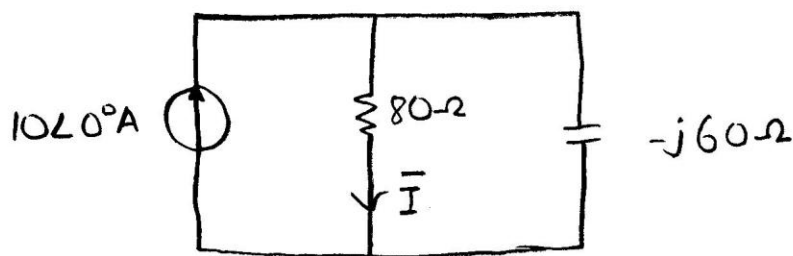

$$\bar{\mathbf{I}} = \left( \frac{-j60}{80 - j60} \right) (10\angle 0^\circ)$$

$$\bar{\mathbf{I}} = 6\angle -53.13^\circ \text{ A}$$

Download any solution manual for free

All Departments , All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**8.46** Find the frequency-domain voltage  $V_o$ , as shown in Fig. P8.46.


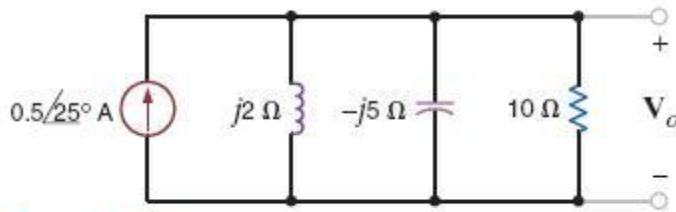


Figure P8.46

**SOLUTION:**

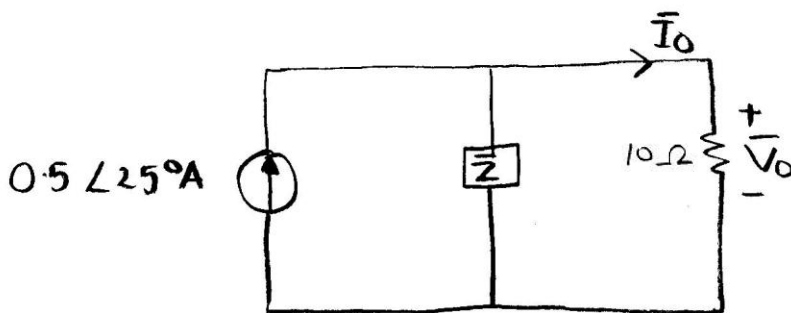

$$\bar{Z} = j2 \parallel -j5 = \frac{j2(-j5)}{-j5 + j2}$$

$$\bar{Z} = 3.33 \angle 90^\circ \Omega$$

$$\bar{I}_0 = \left( \frac{3.33 \angle 90^\circ}{3.33 \angle 90^\circ + 10} \right) (0.5 \angle 25^\circ)$$

$$\bar{I}_0 = 0.158 \angle 96.58^\circ \text{ A}$$

$$\bar{V}_o = 10 (0.158 \angle 96.58^\circ)$$

$$\bar{V}_o = 1.58 \angle 96.58^\circ \text{ V}$$

**8.50** Find the frequency-domain voltage  $V_o$ , as shown in Fig. P8.50.


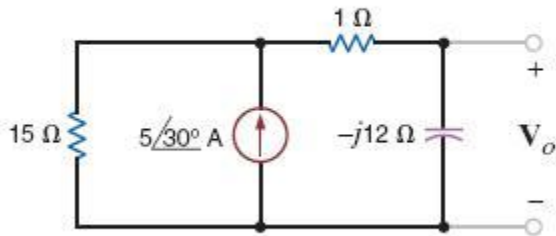


Figure P8.50

**SOLUTION:**

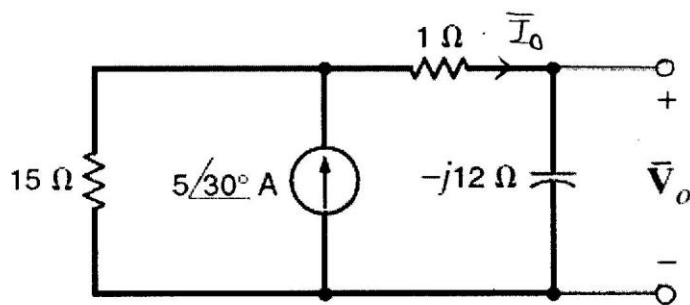

$$\bar{I}_0 = \left( \frac{15}{15 + 1 - j12} \right) (5 \angle 30^\circ)$$

$$\bar{I}_0 = 3.75 \angle 66.87^\circ \text{ A}$$

$$\bar{V}_o = (3.75 \angle 66.87^\circ) (-j12)$$

$$\bar{V}_o = 45 \angle -23.13^\circ \text{ V}$$

Download any solution manual for free

All Departments, All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)

**8.54** Given the network in Fig. P8.54, determine the value of  $V_o$  if  $V_s = 24\angle 0^\circ \text{ V}$ .


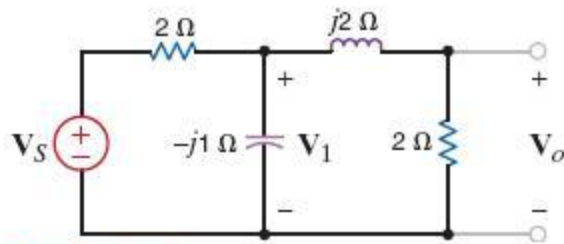
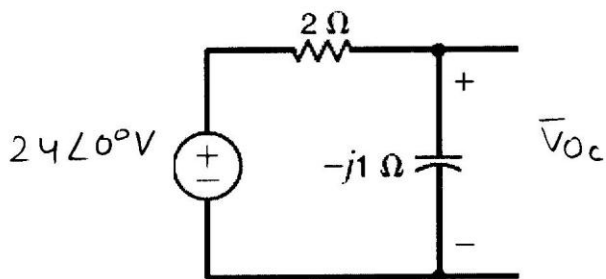


Figure P8.54

**SOLUTION:**

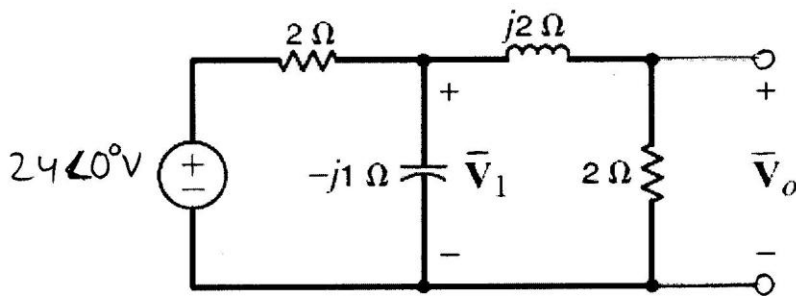


Download any solution manual for free

All Departments , All Subjects

[www.myUET.net.tc](http://www.myUET.net.tc)


$$\bar{V}_{oc} = \left( \frac{-j1}{2-j1} \right) (24\angle 0^\circ)$$
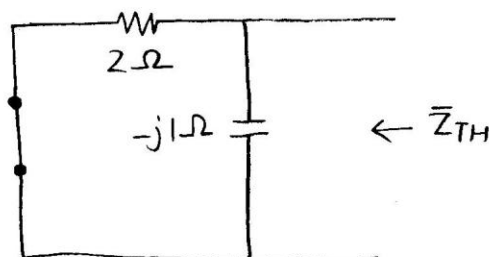
$$\bar{V}_{oc} = 10.73 \angle -63.43^\circ \text{ V}$$



$$\bar{Z}_{TH} = 2/1-j1 = \frac{2(-j1)}{2-j1}$$
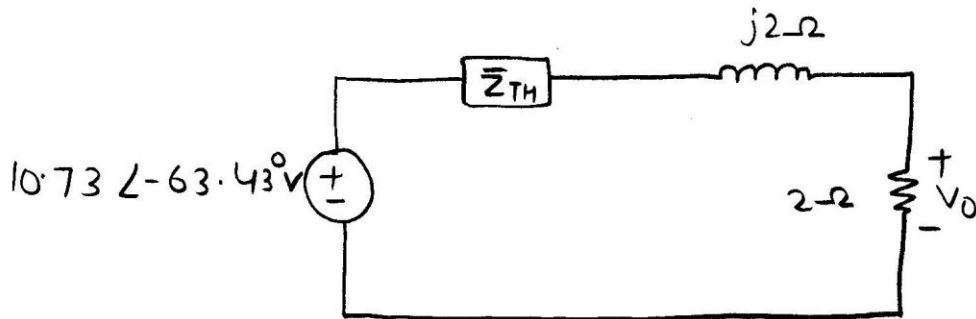
$$\bar{Z}_{TH} = 0.89 \angle -63.43^\circ \Omega$$



$$\bar{V}_0 = \left( \frac{2}{2+j2 + 0.89 \angle -63.43^\circ} \right) (10.73 \angle -63.43^\circ)$$

$$\bar{V}_0 = 8 \angle -90.1^\circ \text{V}$$

**www.myUET.net.to**



**8.62** In the network in Fig. P8.62  $I_o = 4 \angle 0^\circ$  A, find  $I_x$ .


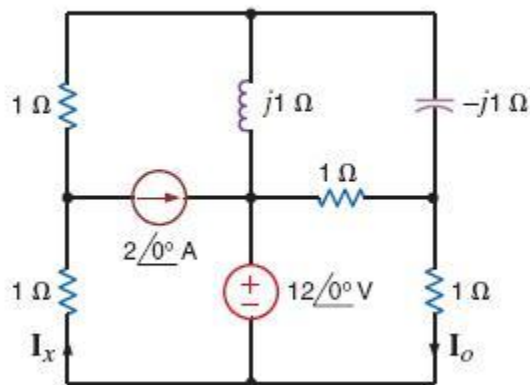


Figure P8.62

**SOLUTION:**

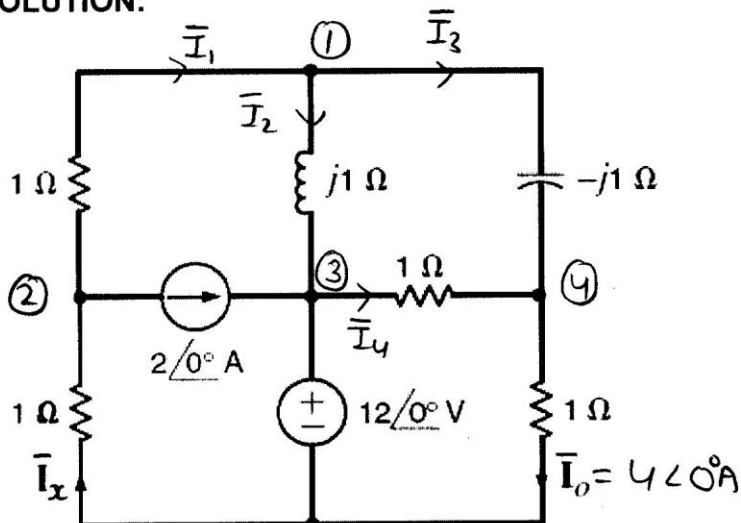

$$\text{KCL at } ① : \bar{I}_1 = \bar{I}_2 + \bar{I}_3$$

$$\frac{\bar{V}_2 - \bar{V}_1}{1} = \frac{\bar{V}_1 - \bar{V}_3}{j1} = \frac{\bar{V}_1 - \bar{V}_4}{-j1}$$

$$j1(\bar{V}_2 - \bar{V}_1) = \bar{V}_1 - \bar{V}_3 - \bar{V}_1 + \bar{V}_4$$

$$-j1\bar{V}_1 + j1\bar{V}_2 + \bar{V}_3 - \bar{V}_4 = 0$$

$$\text{KCL at } \textcircled{2} : \bar{I}_1 + 2\angle 0^\circ = \bar{I}_x$$

$$\frac{\bar{V}_2 - \bar{V}_1}{1} + 2\angle 0^\circ = \frac{-\bar{V}_2}{1}$$

$$\bar{V}_2 - \bar{V}_1 + 2\angle 0^\circ = -\bar{V}_2$$

$$\bar{V}_1 - 2\bar{V}_2 = 2\angle 0^\circ$$

$$\text{KCL at } \textcircled{4} : \bar{I}_3 + \bar{I}_4 = \bar{I}_0$$

$$\frac{\bar{V}_1 - \bar{V}_4}{j1} + \frac{\bar{V}_3 - \bar{V}_4}{1} = \frac{\bar{V}_4}{1}$$

$$\bar{V}_1 - \bar{V}_4 - j1(\bar{V}_3 - \bar{V}_4) = -j1\bar{V}_4$$

$$\bar{V}_1 - j1\bar{V}_3 + (-1 + j2)\bar{V}_4 = 0$$

$$\bar{V}_4 = 1(\angle 4\angle 0^\circ) = 4\angle 0^\circ \text{ V}$$

$$\bar{V}_1 + (-1 + j2)\bar{V}_4 = 12\angle 90^\circ$$

$$\bar{V}_1 = 12\angle 90^\circ - 4\angle 0^\circ (-1 + j2)$$

$$\bar{V}_1 = 5.66 \angle 45^\circ \text{ V}$$

$$\bar{V}_1 - 2\bar{V}_2 = 2\angle 0^\circ$$

$$\bar{V}_2 = \frac{5.66 \angle 45^\circ - 2 \angle 0^\circ}{2}$$

$$\bar{V}_2 = 2.24 \angle 63.43^\circ \text{ V}$$

$$\bar{I}_x = -1 (2.24 \angle 63.43^\circ)$$

$$\bar{I}_x = 2.24 \angle -116.57^\circ \text{ A}$$

**8.66** Using nodal analysis, find  $I_o$  in the circuit in Fig. P8.66.


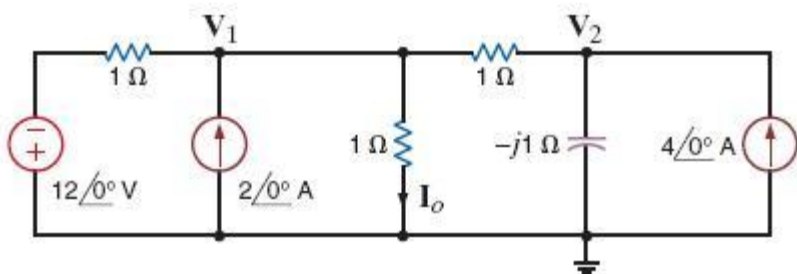


Figure P8.66

**SOLUTION:**

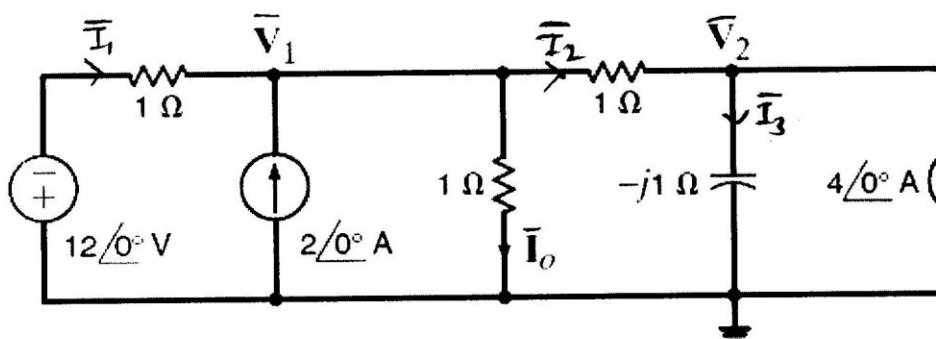

$$\text{KCL at } \textcircled{1} : \bar{I}_1 + 2\angle 0^\circ = \bar{I}_o + \bar{I}_2$$

$$\frac{-12\angle 0^\circ - \bar{V}_1}{1} + 2\angle 0^\circ = \frac{\bar{V}_1}{1} + \frac{\bar{V}_1 - \bar{V}_2}{1}$$

$$-12\angle 0^\circ - \bar{V}_1 + 2\angle 0^\circ = \bar{V}_1 + \bar{V}_1 - \bar{V}_2$$

$$3\bar{V}_1 - \bar{V}_2 = 10\angle 180^\circ$$

$$\text{KCL at } \textcircled{2} : \bar{I}_2 + 4\angle 0^\circ = \bar{I}_3$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + 4\angle 0^\circ = \frac{\bar{V}_2}{-j1}$$

$$-j1(\bar{V}_1 - \bar{V}_2) - j1(4\angle 0^\circ) = \bar{V}_2$$

$$-j1\bar{V}_1 + (-1+j1)\bar{V}_2 = 4\angle 90^\circ$$

$$3\bar{V}_1 - \bar{V}_2 = 10\angle 180^\circ$$

$$-j1\bar{V}_1 + (-1+j1)\bar{V}_2 = 4\angle 90^\circ$$

$$\bar{V}_1 = 3.23\angle -177.3^\circ \text{ V}$$

$$\bar{V}_2 = 0.55\angle -56.3^\circ \text{ V}$$

$$\bar{I}_0 = \frac{\bar{V}_1}{1}$$

$$\bar{I}_0 = \frac{3.23\angle -177.3^\circ}{1}$$

$$\bar{I}_0 = 3.23\angle -177.3^\circ \text{ A}$$

**8.68** Find  $V_o$  in the network in Fig. P8.68 using nodal analysis.


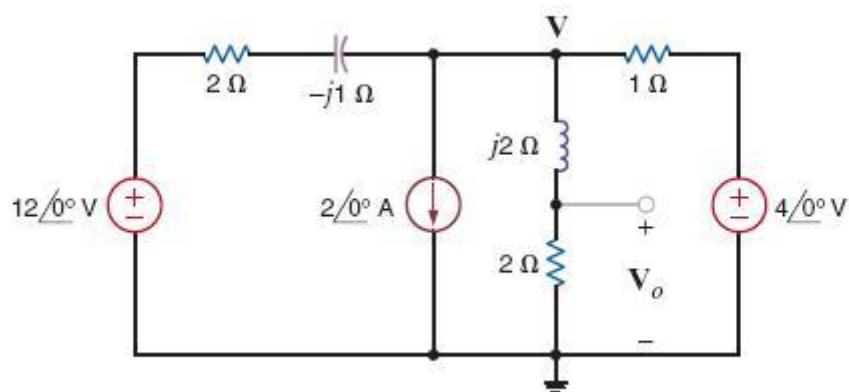


Figure P8.68

**SOLUTION:**

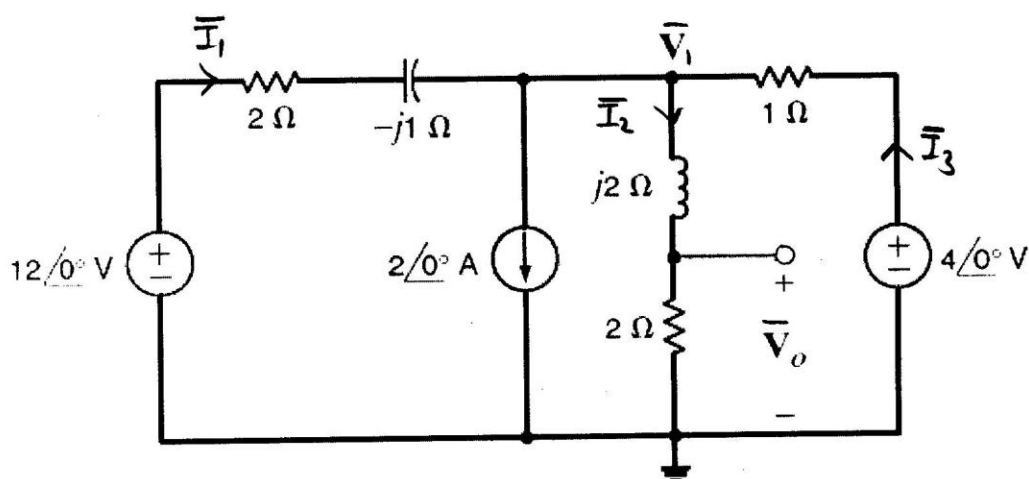

$$\text{KCL at } \textcircled{1}: \bar{I}_1 + \bar{I}_3 = 2\angle 0^\circ + \bar{I}_2$$

$$\frac{12\angle 0^\circ - \bar{V}_1}{2 - j1} + \frac{4\angle 0^\circ - \bar{V}_1}{1} = 2\angle 0^\circ + \frac{\bar{V}_1}{2 + j2}$$

$$\frac{\bar{V}_1}{2 + j2} + \frac{\bar{V}_1}{2 - j1} + \bar{V}_1 = \frac{12\angle 0^\circ}{2 - j1} + 4\angle 0^\circ - 2\angle 0^\circ$$

$$\bar{V}_1 = \frac{7.21 \angle 19.44^\circ}{1.65 \angle -1.74^\circ}$$

$$\bar{V}_1 = 4.37 \angle 21.2^\circ \text{ V}$$

$$\bar{I}_2 = \frac{\bar{V}_1}{2+j2} = \frac{4.37 \angle 21.2^\circ}{2+j2}$$

$$\bar{I}_2 = 1.55 \angle -23.8^\circ \text{ A}$$

$$\bar{V}_0 = 2(1.55 \angle -23.8^\circ)$$

$$\bar{V}_0 = 3.1 \angle -23.8^\circ \text{ V}$$

**8.71** Use nodal analysis to find  $V_o$  in the circuit in Fig. P8.71.


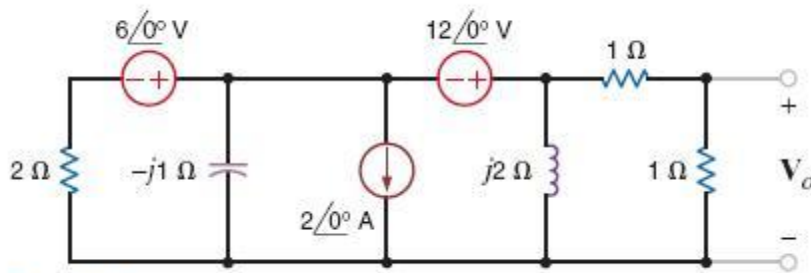


Figure P8.71

**SOLUTION:**

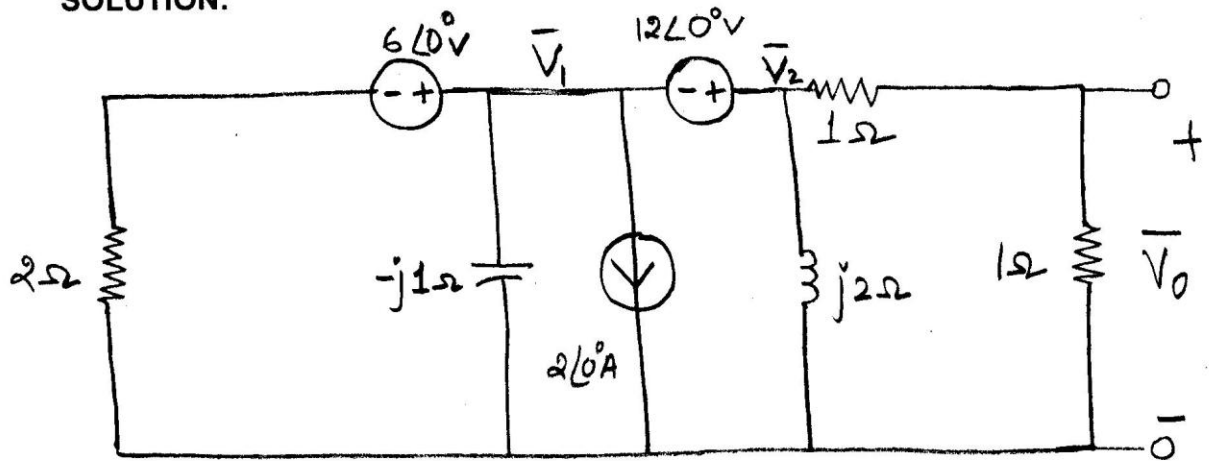

$$(\bar{V}_1 - 6)/2 + \bar{V}_1/(-j) + 2 = \bar{V}_2/(j2) + \bar{V}_2/(2)$$

$$\Rightarrow \bar{V}_1 \times (j-2) - 2j = \bar{V}_2 \times (1+j) \quad \text{eq 1}$$

$$\bar{V}_1 = \bar{V}_2 - 12 \quad \text{eq 2}$$

$$\bar{V}_o = \bar{V}_2/(2) \quad \text{eq 3}$$

upon solving these

$$\bar{V}_2 = 8 - (14/3)j$$

$$\text{hence } \bar{V}_o = \bar{V}_2/(2) = 4 - j(7/3) = 4.6 \angle -30.25^\circ$$



**8.77** Use mesh analysis to find  $V_o$  in the circuit shown in Fig. P8.77.


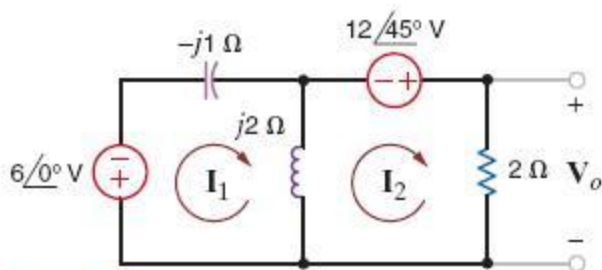


Figure P8.77

**SOLUTION:**

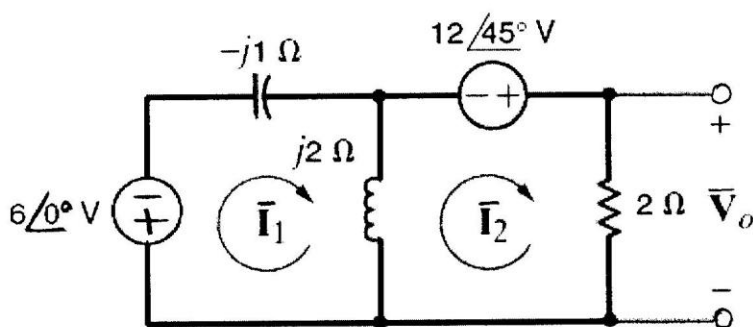

$$\bar{I}_1 = \bar{I} + \bar{I}_2$$

$$\bar{I} = \bar{I}_1 - \bar{I}_2$$

$$\text{KVL left loop: } 6\angle 0^\circ - j1\bar{I}_1 + j2\bar{I} = 0$$

$$j1\bar{I}_1 - j2(\bar{I}_1 - \bar{I}_2) = 6\angle 0^\circ$$

$$\boxed{-j1\bar{I}_1 + j2\bar{I}_2 = 6\angle 0^\circ}$$

KVL right loop:

$$2\bar{I}_2 - j2\bar{I} = 12\angle 45^\circ$$

$$-j2(\bar{I}_1 - \bar{I}_2) + 2\bar{I}_2 = 12\angle 45^\circ$$

$$\boxed{-j2\bar{I}_1 + (2+j2)\bar{I}_2 = 12\angle 45^\circ}$$

$$-j1\bar{I}_1 + j2\bar{I}_2 = 6\angle 0^\circ$$

$$-j2\bar{I}_1 + (2+j2)\bar{I}_2 = 12\angle 45^\circ$$

$$\bar{I}_1 = 10.39 \angle 125.26^\circ \text{ A}$$

$$\bar{I}_2 = 3.25 \angle 157.5^\circ \text{ A}$$

$$\bar{V}_o = 2(3.25 \angle 157.5^\circ)$$

$$\bar{V}_o = 6.5 \angle 157.5^\circ$$

[www.myUET.net.tc](http://www.myUET.net.tc)

CREATE YOUR OWN WEB  
PAGE  
VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

**8.82** Using loop analysis, determine  $V_o$  in the network in Fig. P8.82.


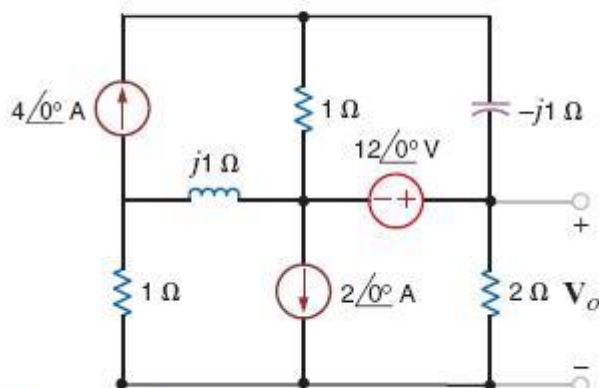


Figure P8.82

**SOLUTION:**

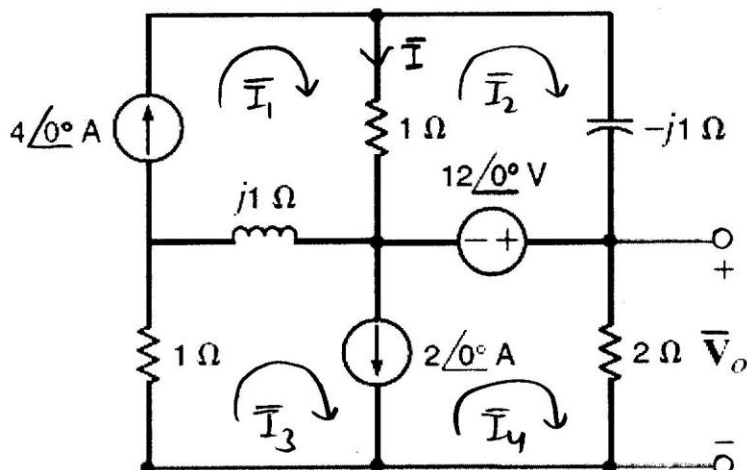

$$\begin{aligned} \text{KCL: } \bar{I}_1 &= \bar{I} + \bar{I}_2 \\ \bar{I} &= \bar{I}_1 - \bar{I}_2 \end{aligned}$$

$$\begin{aligned} \text{KCL: } \bar{I}_3 &= \bar{I}' + \bar{I}_1 \\ \bar{I}' &= \bar{I}_3 - \bar{I}_1 \end{aligned}$$

$$\text{KVL: } 12\angle 0^\circ + 1(-\bar{I}) - j1(\bar{I}_2) = 0$$

$$-(\bar{I}_1 - \bar{I}_2) - j1\bar{I}_2 = 12\angle 180^\circ$$

$$-\bar{I}_1 + (1-j1) \bar{I}_2 = 12 \angle 180^\circ$$

$$\bar{I}_1 = 4 \angle 0^\circ \text{ A}$$

$$(1-j1) \bar{I}_2 = 12 \angle 180^\circ + 4 \angle 0^\circ$$

$$\bar{I}_2 = 5.66 \angle -135^\circ \text{ A}$$

$$\text{KVL: } 1(-\bar{I}_1) - j1\bar{I}_2 + 2\bar{I}_4 + 1(\bar{I}_3) + j1\bar{I}' = 0$$

$$-(\bar{I}_1 - \bar{I}_2) - j1\bar{I}_2 + 2\bar{I}_4 + \bar{I}_3 + j1(\bar{I}_3 - \bar{I}_1) = 0$$

$$(-1-j1) \bar{I}_1 + (1-j1) \bar{I}_2 + (1+j1) \bar{I}_3 + 2\bar{I}_4 = 0$$

$$(-1-j1) (4 \angle 0^\circ) + (1-j1) (5.66 \angle -135^\circ) + (1+j1) \bar{I}_3 + 2\bar{I}_4 = 0$$

$$(1+j1) \bar{I}_3 + 2\bar{I}_4 = 12.65 \angle 18.43^\circ$$

$$\text{KCL: } \bar{I}_4 + 2 \angle 0^\circ = \bar{I}_3$$

$$\bar{I}_3 - \bar{I}_4 = 2 \angle 0^\circ$$

$$(1+j1) \bar{I}_3 + 2\bar{I}_4 = 12.65 \angle 18.43^\circ$$

$$\bar{I}_3 - \bar{I}_4 = 2 \angle 0^\circ$$

$$\bar{I}_3 = 5.22 \angle -4.4^\circ \text{ A}$$

$$\bar{I}_4 = 3.23 \angle -7.13^\circ \text{ A}$$

$$\bar{V}_o = 2\bar{I}_1 = 2(3.23 \angle -7.13^\circ)$$

$$\bar{V}_o = 6.46 \angle -7.13^\circ \text{ V}$$

**W  
W  
W  
.  
m  
y  
U  
E  
T  
.  
n  
e  
t  
.  
t  
c**

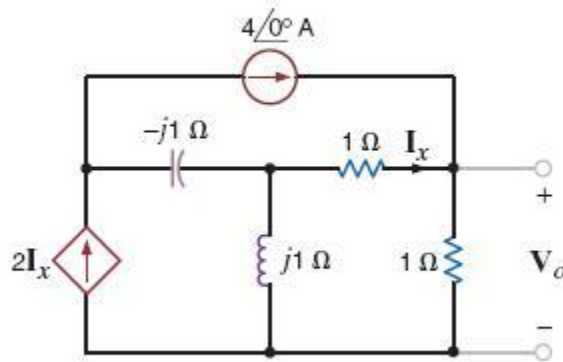
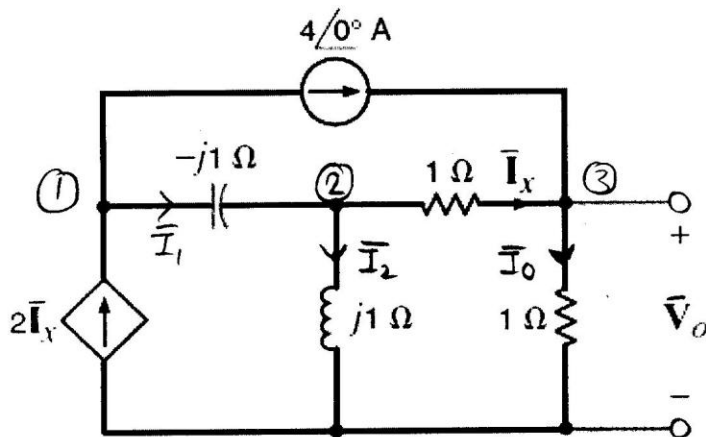
**8.87** Find  $V_o$  in the network in Fig. P8.87.

Figure P8.87

CREATE YOUR OWN WEB  
PAGE

VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

**SOLUTION:**

$$\text{KCL at } ① : 2\bar{I}_x = 4\angle 0^\circ + \bar{I}_1$$

$$\bar{I}_x = \frac{\bar{V}_2 - \bar{V}_3}{1}$$

$$2 \left[ \frac{\bar{V}_2 - \bar{V}_3}{1} \right] = 4\angle 0^\circ + \frac{\bar{V}_1 - \bar{V}_2}{-j1}$$

$$-j2 [\bar{V}_2 - \bar{V}_3] = -j1 (4\angle 0^\circ) + \bar{V}_1 - \bar{V}_2$$

$$\bar{V}_1 + (-1 + j2) \bar{V}_2 - j2 \bar{V}_3 = j1 (4\angle 0^\circ)$$

$$\text{KCL at } \textcircled{2}: \bar{I}_1 = \bar{I}_x + \bar{I}_2$$

$$\frac{\bar{V}_1 - \bar{V}_2}{-j1} = \frac{\bar{V}_2 - \bar{V}_3}{1} + \frac{\bar{V}_2}{j1}$$

$$\bar{V}_1 - \bar{V}_2 = -j1(\bar{V}_2 - \bar{V}_3) - \bar{V}_2$$

$$\bar{V}_1 + j1\bar{V}_2 - j1\bar{V}_3 = 0$$

$$\text{KCL at } \textcircled{3}: \bar{I}_x + 4\angle 0^\circ = \bar{I}_0$$

$$\frac{\bar{V}_2 - \bar{V}_3}{1} + 4\angle 0^\circ = \frac{\bar{V}_3}{1}$$

$$\bar{V}_2 - 2\bar{V}_3 = 4\angle 180^\circ$$

$$\bar{V}_1 + (-1 + j2)\bar{V}_2 - j2\bar{V}_3 = 4\angle 90^\circ$$

$$\bar{V}_1 + j1\bar{V}_2 - j1\bar{V}_3 = 0$$

$$\bar{V}_2 - 2\bar{V}_3 = 4\angle 180^\circ$$

$$\bar{V}_1 = 2.53 \angle 161.57^\circ \text{ V}$$

$$\bar{V}_2 = 5.37 \angle -63.43^\circ \text{ V}$$

$$\bar{V}_3 = 4 \angle -36.87^\circ \text{ V}$$

$$\bar{V}_0 = \bar{V}_3$$

$$\bar{V}_0 = 4 \angle -36.87^\circ \text{ V}$$

www.mynetc.cc

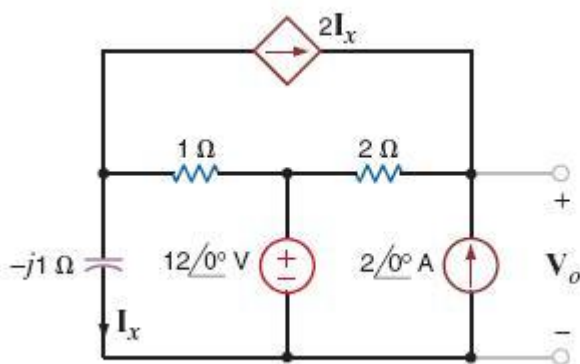
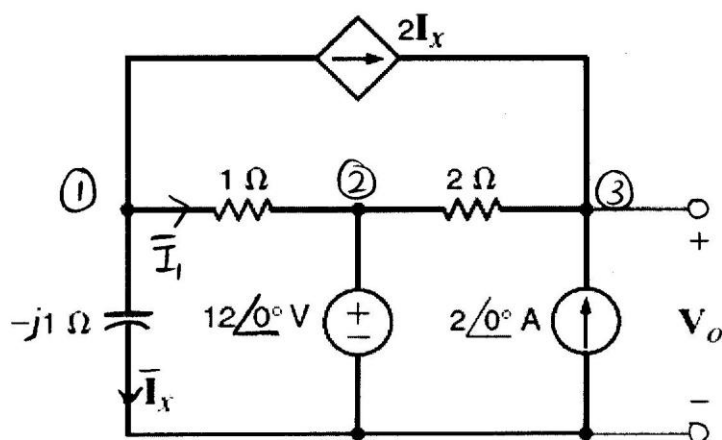
**8.88** Find  $V_o$  in the circuit in Fig. P8.88.

Figure P8.88

**SOLUTION:**

$$\text{KCL at } \textcircled{1}: \quad 2\bar{I}_x + \bar{I}_1 + \bar{I}_x = 0$$

$$\bar{I}_x = \frac{\bar{V}_1}{-j1}$$

$$2\left[\frac{\bar{V}_1}{-j1}\right] + \frac{\bar{V}_1 - \bar{V}_2}{1} + \frac{\bar{V}_1}{-j1} = 0$$

$$2\bar{V}_1 - j1(\bar{V}_1 - \bar{V}_2) + \bar{V}_1 = 0$$

$$(3 - j1)\bar{V}_1 + j1\bar{V}_2 = 0$$



$$\bar{V}_2 = 12 \angle 0^\circ \text{ V}$$

$$(3 - j1)\bar{V}_1 + j1(12 \angle 0^\circ) = 0$$

$$\bar{V}_1 = 3.8 \angle 71.6^\circ \text{ V}$$

$$\text{KCL at } \textcircled{3}: \bar{I}_2 + 2\bar{I}_x + 2 \angle 0^\circ = 0$$

$$\frac{\bar{V}_2 - \bar{V}_3}{2} + 2 \left[ \frac{\bar{V}_1}{-j1} \right] + 2 \angle 0^\circ = 0$$

$$\frac{12 \angle 0^\circ - \bar{V}_3}{2} + 2 \left[ \frac{3.8 \angle -71.6^\circ}{-j1} \right] + 2 \angle 0^\circ = 0$$

$$\bar{V}_3 = 30.8 \angle 8.96^\circ \text{ V}$$

$$\bar{V}_o = \bar{V}_3$$

$$\bar{V}_3 = 30.8 \angle 8.96^\circ \text{ V}$$

**8.100** Use Thévenin's theorem to find  $V_o$  in the network in Fig. P8.100.



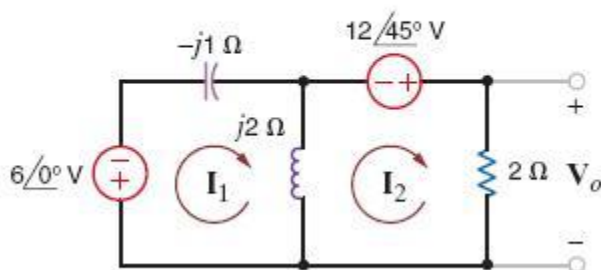


Figure P8.100

**SOLUTION:**

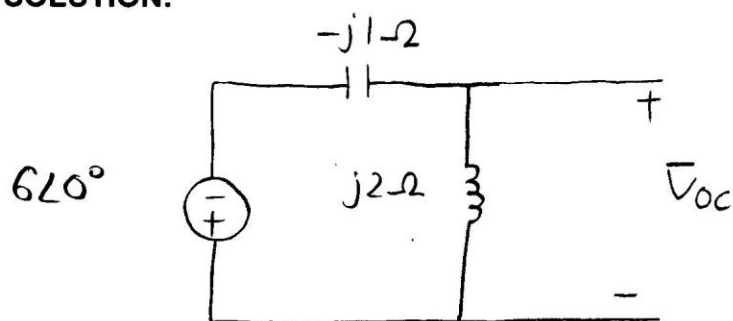

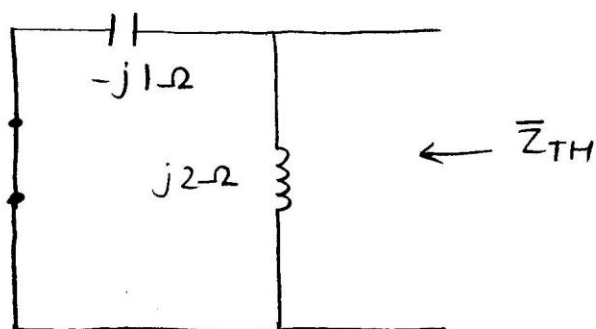
$$\bar{V}_{OC} = \left( \frac{j2}{-j1 + j2} \right) (-6\angle 0^\circ) = 12\angle 180^\circ \text{ V}$$



$$\bar{Z}_{TH} = j2 \parallel -j1 = \frac{j2(-j1)}{j2 - j1}$$
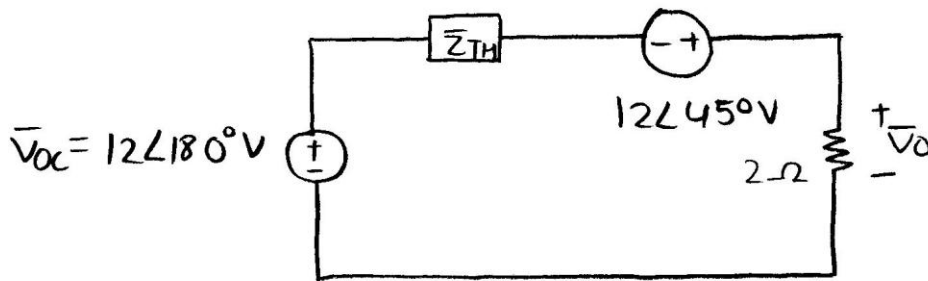
$$\bar{Z}_{TH} = 2\angle -90^\circ \Omega$$



$$\bar{V}_0 = \left( \frac{2}{2 + 2\angle -90^\circ} \right) (12\angle 180^\circ + 12\angle 45^\circ)$$

$$\bar{V}_0 = 6.5 \angle 157.5^\circ \text{ V}$$

CREATE YOUR OWN WEB  
PAGE

VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

**W  
W  
W  
-  
m  
y  
U  
E  
T  
-  
n  
e  
t  
-  
t  
c**

**8.101** Find  $V_o$  in Fig. P8.101 using Thévenin's theorem.


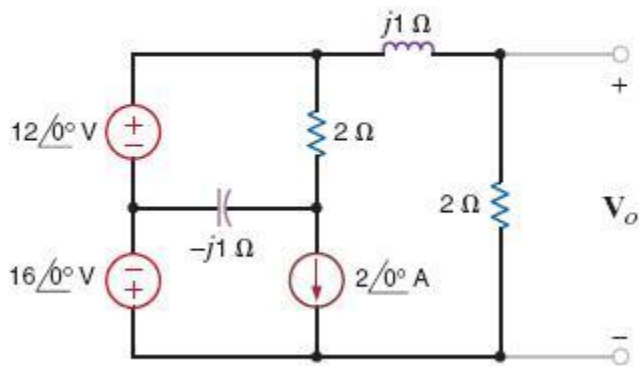


Figure P8.101

**SOLUTION:**

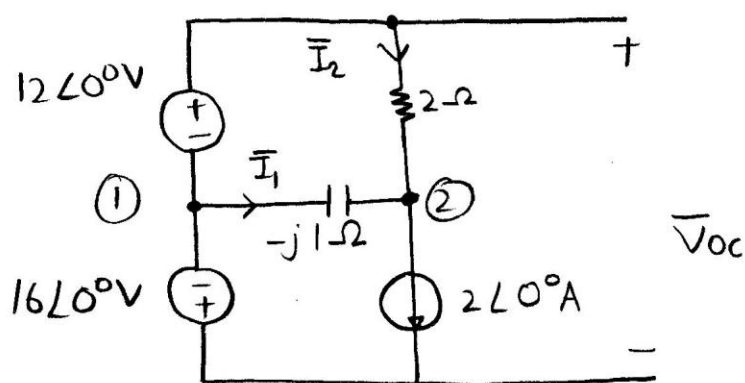

$$\text{KCL at } ②: \bar{I}_1 + \bar{I}_2 = 2\angle 0^\circ$$

$$\frac{\bar{V}_1 - \bar{V}_2}{-j1} + \frac{\bar{V}_{oc} - \bar{V}_2}{2} = 2\angle 0^\circ$$



$$\frac{\bar{V}_1}{-j1} + \left( \frac{1}{j1} - \frac{1}{2} \right) \bar{V}_2 + \frac{\bar{V}_{oc}}{2} = 2\angle 0^\circ$$

$$\bar{V}_1 = -16\angle 0^\circ \text{ V}$$

$$\bar{V}_{oc} - \bar{V}_1 = 12\angle 0^\circ$$

$$\bar{V}_{oc} = 12\angle 0^\circ + 16\angle 180^\circ$$
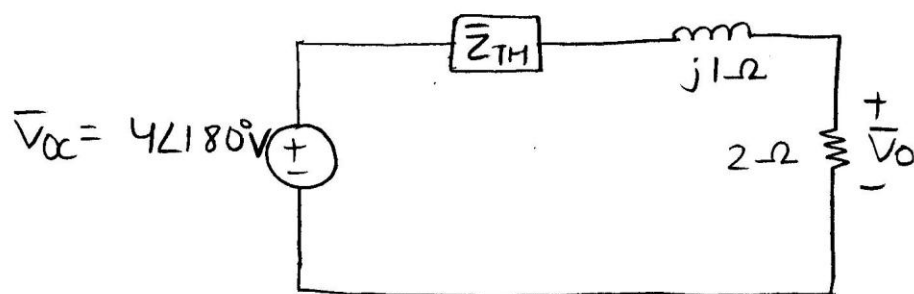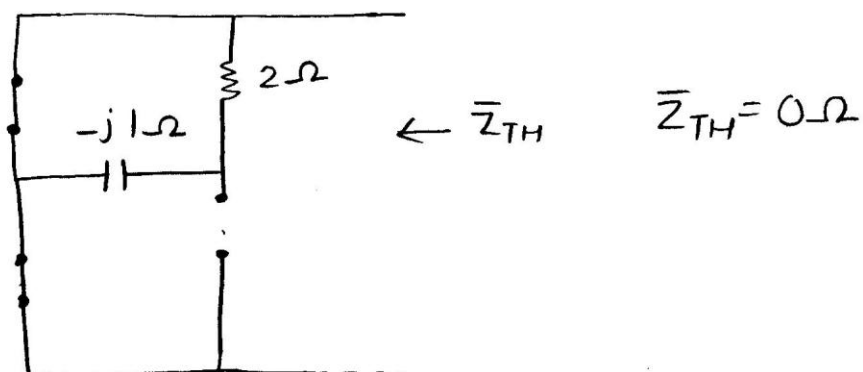
$$\bar{V}_{oc} = 4\angle 180^\circ \text{ V}$$



$$\bar{V}_o = \left( \frac{2}{2 + j1 + 0} \right) (4\angle 180^\circ)$$

$$\bar{V}_o = 3.6\angle 153.4^\circ \text{ V}$$

**8.107** Find  $V_o$  in the network in Fig. P8.107 using Thévenin's theorem.


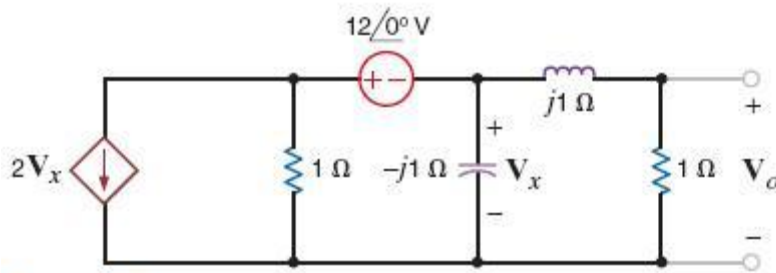


Figure P8.107

**SOLUTION:**

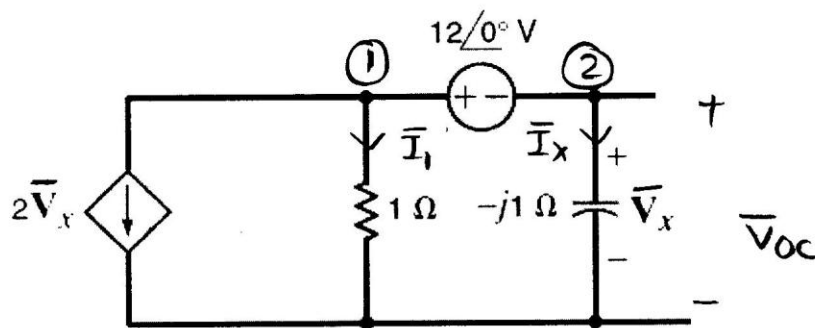

KCL at reference node:

$$2\bar{V}_x + \bar{I}_1 + \bar{I}_x = 0$$

$$\bar{V}_x = \bar{V}_2$$

$$2\bar{V}_2 + \frac{\bar{V}_1}{1} + \frac{\bar{V}_2}{-j1} = 0$$

$$-j2\bar{V}_2 - j1\bar{V}_1 + \bar{V}_2 = 0$$

$$-j1\bar{V}_1 + (1-j2)\bar{V}_2 = 0$$

$$\bar{V}_1 - \bar{V}_2 = 12\angle 0^\circ$$


$$\bar{V}_1 = 8.49 \angle 8.13^\circ \text{ V}$$

$$\bar{V}_2 = 3.8 \angle 161.57^\circ \text{ V}$$

$$\bar{V}_{oc} = \bar{V}_2$$

$$\bar{V}_{oc} = 3.8 \angle 161.57^\circ \text{ V}$$

$$12 \angle 0^\circ \text{ V}$$

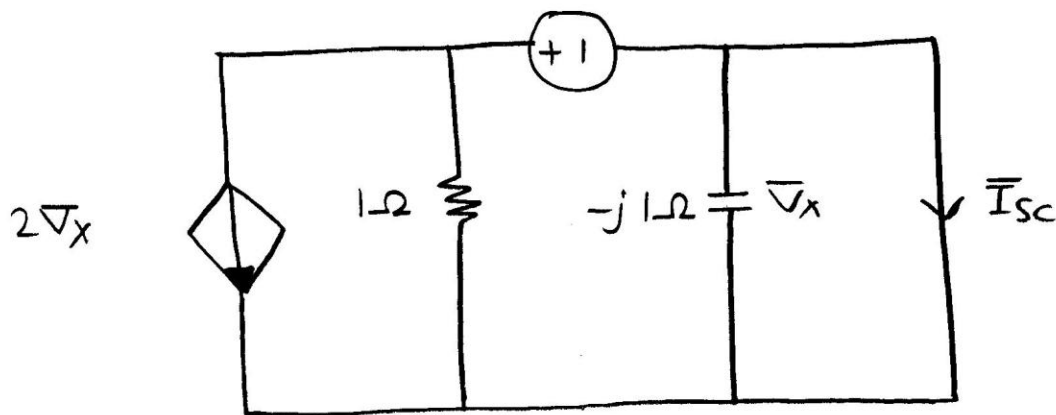


$$\bar{V}_x = 0 \text{ V}$$

$$\frac{12 \angle 0^\circ}{1} + \bar{I}_{sc} = 0$$

$$\bar{I}_{sc} = 12 \angle 180^\circ \text{ A}$$

$$\bar{Z}_{TH} = \frac{\bar{V}_{oc}}{\bar{I}_{sc}} = \frac{3.8 \angle 161.57^\circ}{12 \angle 180^\circ}$$
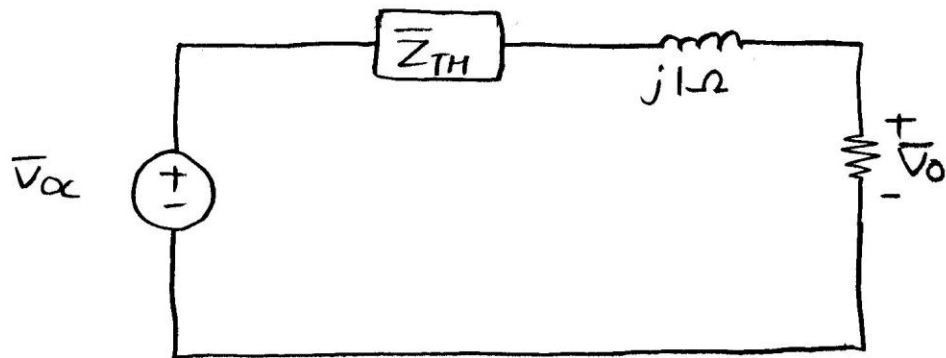
$$\bar{Z}_{TH} = 0.32 \angle -18.43^\circ \Omega$$



$$\bar{V}_0 = \left( \frac{1}{1 + j1 + 0.32 \angle -18.43^\circ} \right) (3.8 \angle 161.57^\circ)$$

$$\bar{V}_0 = 2.4 \angle 127^\circ \text{ V}$$

Create your own web page

Sign Up to

[www.myUET.net.tc](http://www.myUET.net.tc)



**8.108** Find the Thévenin's equivalent for the network in Fig. P8.108 at terminals A-B.

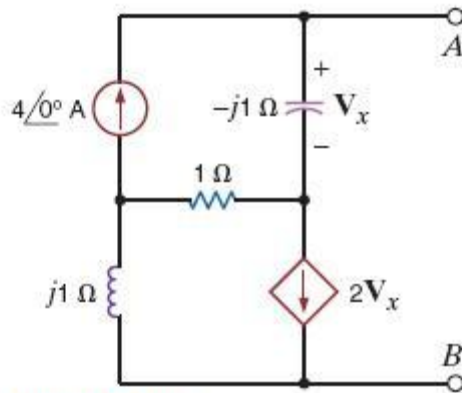



Figure P8.108

CREATE YOUR OWN WEB  
PAGE

VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

**SOLUTION:**

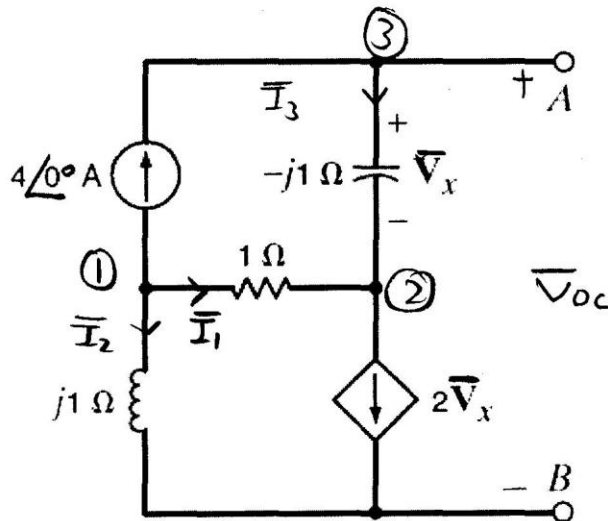

$$\text{KCL at } ① : 4\angle 0^\circ + \bar{I}_1 + \bar{I}_2 = 0$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + \frac{\bar{V}_1}{j1} = -4\angle 0^\circ$$

$$j1(\bar{V}_1 - \bar{V}_2) + \bar{V}_1 = j1(-4\angle 0^\circ)$$

$$(1 + j1)\bar{V}_1 - j1\bar{V}_2 = 4\angle -90^\circ$$

$$\text{KCL at } ② : \bar{I}_3 + \bar{I}_1 = 2\bar{V}_x$$

$$\bar{V}_x = \bar{V}_{oc} - \bar{V}_2$$

$$\frac{\bar{V}_{oc} - \bar{V}_2}{-j1} + \frac{\bar{V}_1 - \bar{V}_2}{1} = 2[\bar{V}_{oc} - \bar{V}_2]$$

$$\bar{V}_{oc} - \bar{V}_2 - j1(\bar{V}_1 - \bar{V}_2) = -j2[\bar{V}_{oc} - \bar{V}_2]$$

$$-j1\bar{V}_1 + (-1-j1)\bar{V}_2 + (1+j2)\bar{V}_{oc} = 0$$

$$\text{KCL at } \textcircled{3}: \bar{I}_3 = 4\angle 0^\circ$$

$$\frac{\bar{V}_{oc} - \bar{V}_2}{-j1} = 4\angle 0^\circ$$

$$-\bar{V}_2 + \bar{V}_{oc} = 4\angle -90^\circ$$

$$(1+j1)\bar{V}_1 - j1\bar{V}_2 = 4\angle -90^\circ$$


$$-j1\bar{V}_1 + (-1-j1)\bar{V}_2 + (1+j2)\bar{V}_{oc} = 0$$

$$-\bar{V}_2 + \bar{V}_{oc} = 4\angle -90^\circ$$

$$\bar{V}_1 = 8\angle 180^\circ \text{ V}$$

$$\bar{V}_2 = 8.94\angle 116.6^\circ \text{ V}$$
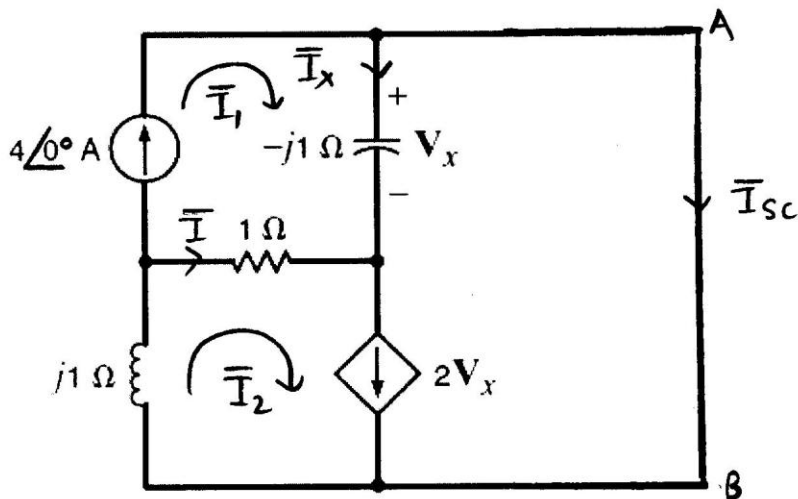
$$\bar{V}_{oc} = 5.66\angle 135^\circ \text{ V}$$



$$\text{KCL: } \bar{I}_2 = \bar{I} + \bar{I}_1$$

$$\bar{I} = \bar{I}_2 - \bar{I}_1$$

$$\text{KCL: } 4\angle 0^\circ = \bar{I}_x + \bar{I}_{sc}$$

$$\bar{I}_x = 4\angle 0^\circ - \bar{I}_{sc}$$

$$\text{KVL: } 1(\bar{I}) - j1(-\bar{I}_x) + j1(\bar{I}_2) = 0$$

$$\bar{I}_2 - \bar{I}_1 + j1(4\angle 0^\circ - \bar{I}_{sc}) + j1\bar{I}_2 = 0$$

$$-\bar{I}_1 + (1+j1)\bar{I}_2 - j1\bar{I}_{sc} = 4\angle -90^\circ$$

$$\text{KCL: } 2\bar{V}_x + \bar{I}_{sc} = \bar{I}_2$$

$$\bar{V}_x = -j1(4\angle 0^\circ - \bar{I}_{sc})$$

$$-j2(4\angle 0^\circ - \bar{I}_{sc}) + \bar{I}_{sc} = \bar{I}_2$$

$$-\bar{I}_2 + (1+j2) \bar{I}_{sc} = 8 \angle 90^\circ$$

$$\bar{I}_1 = 4 \angle 0^\circ \text{ A}$$

$$(1+j1) \bar{I}_2 - j1 \bar{I}_{sc} = 5.66 \angle -45^\circ$$


$$-\bar{I}_2 + (1+j2) \bar{I}_{sc} = 8 \angle 90^\circ$$

$$\bar{I}_2 = 2.53 \angle 71.6^\circ \text{ A}$$

$$\bar{I}_{sc} = 2.53 \angle 18.43^\circ \text{ A}$$

$$\bar{Z}_{TH} = \frac{\bar{V}_{oc}}{\bar{I}_{sc}} = \frac{5.66 \angle 135^\circ}{2.53 \angle 18.43^\circ}$$
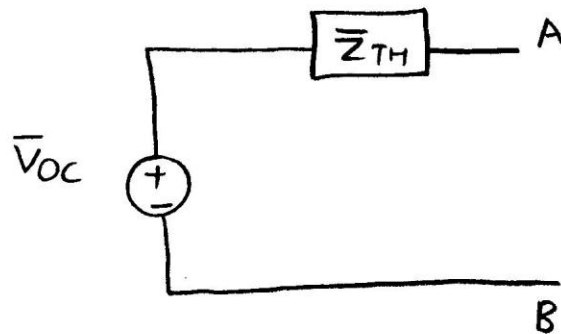
$$\bar{Z}_{TH} = 2.24 \angle 116.57^\circ \Omega$$



**8.114** Calculate the Thévenin equivalent impedance  $Z_{Th}$  in the circuit shown in Fig. P8.114.


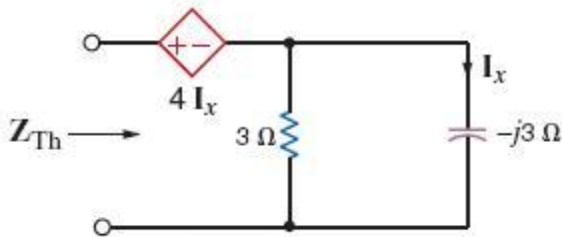


Figure P8.114

**SOLUTION:**

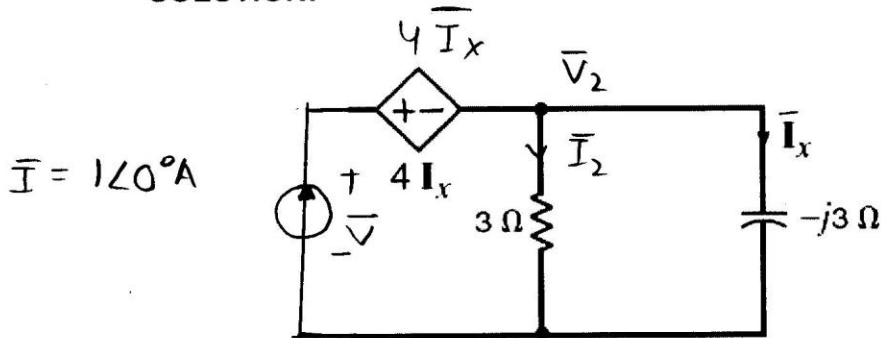

$$\text{KCL at } \textcircled{2} : 1 \angle 0^\circ = \bar{I}_2 + \bar{I}_x$$

$$\frac{\bar{V}_2}{3} + \frac{\bar{V}_2}{-j3} = 1 \angle 0^\circ$$

$$-j1\bar{V}_2 + \bar{V}_2 = -j3(1 \angle 0^\circ)$$

$$\bar{V}_2(1 - j1) = 3 \angle -90^\circ$$

$$\bar{V}_2 = 2.12 \angle -45^\circ \text{ V}$$

$$\bar{I}_2 = \frac{\bar{V}_2}{3} = \frac{2.12 \angle -45^\circ}{3} = 0.707 \angle -45^\circ \text{ A}$$

$$\bar{I}_x = \frac{\bar{V}_2}{-j3} = \frac{2.12 \angle -45^\circ}{-j3} = 0.707 \angle 45^\circ \text{ A}$$

$$\text{KVL: } \bar{V} = 4\bar{I}_x + 3\bar{I}_2$$

$$\bar{V} = 4(0.707 \angle 45^\circ) + 3(7.07 \angle -45^\circ)$$

$$\bar{V} = 3.54 \angle 8.13^\circ \text{ V}$$

$$\bar{Z}_{TH} = \frac{\bar{V}}{\bar{I}} = \frac{3.54 \angle 8.13^\circ}{1 \angle 0^\circ}$$

$$\bar{Z}_{TH} = 3.54 \angle 8.13^\circ \Omega$$

**8.115** Find the Thévenin equivalent for the network in Fig. P8.115 at terminals A-B.


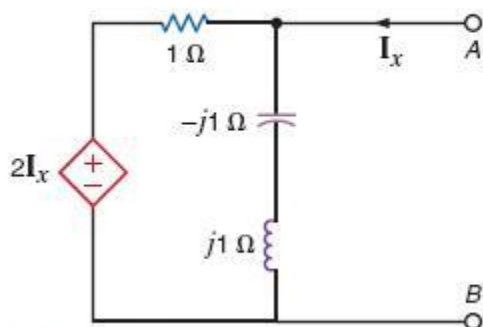


Figure P8.115

**SOLUTION:**

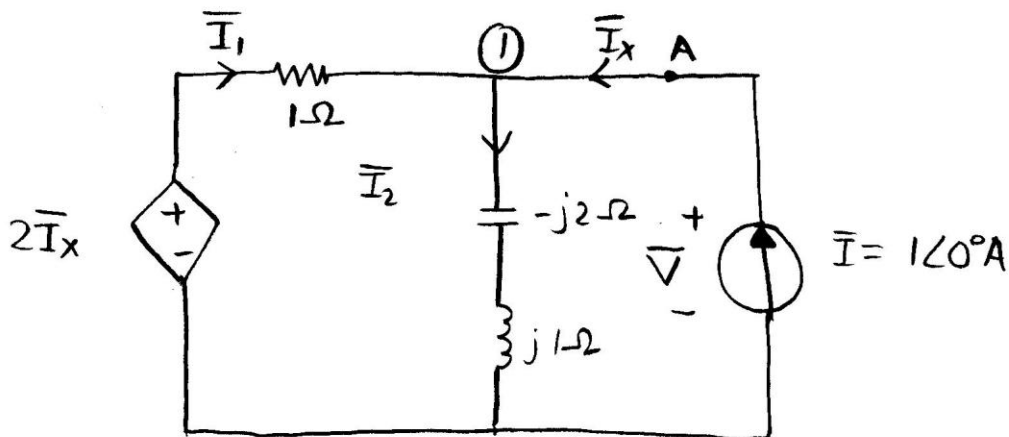

$$\bar{I}_x = \bar{I} = 1 \angle 0^\circ \text{ A}$$

$$\text{KCL at } \textcircled{1}: \bar{I}_1 + \bar{I}_x = \bar{I}_2$$

$$\frac{2\bar{I}_x - \bar{V}_1}{1} + 1 \angle 0^\circ = \frac{\bar{V}_1}{-j1}$$

$$-j1 [2(1 \angle 0^\circ) - \bar{V}_1] - j1 (1 \angle 0^\circ) = \bar{V}_1$$

$$\bar{V}_1 (1-j1) = -j1(2) (\angle 0^\circ) - j1 (\angle 0^\circ)$$

$$\bar{V}_1 = 2.12 \angle -45^\circ \text{ V}$$

$$\bar{V} = \bar{V}_1 = 2.12 \angle -45^\circ \text{ V}$$

$$\bar{Z}_{eq} = \frac{\bar{V}}{\bar{I}} = \frac{2.12 \angle -45^\circ}{1 \angle 0^\circ}$$

$$\bar{Z}_{eq} = 2.12 \angle -45^\circ \Omega$$

$$\bar{Z}_{eq} = 1.5 - j1.5 \Omega$$

Create your own web page

Sign Up to

[www.myUET.net.tc](http://www.myUET.net.tc)



**8.123** Use both a nodal analysis and a loop analysis, each in conjunction with MATLAB, to find  $I_o$  in the network in Fig. P8.123.


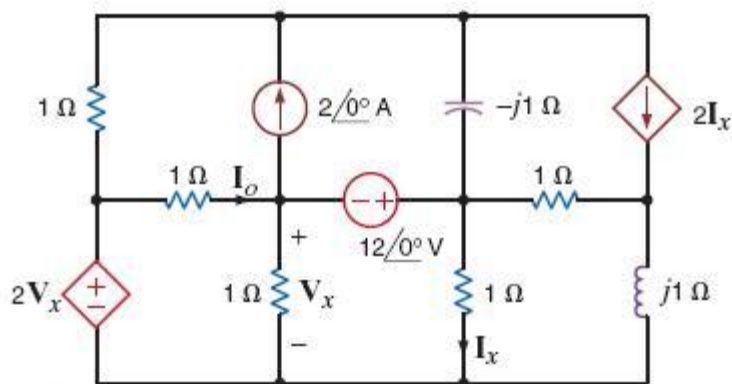


Figure P8.123

**SOLUTION:**

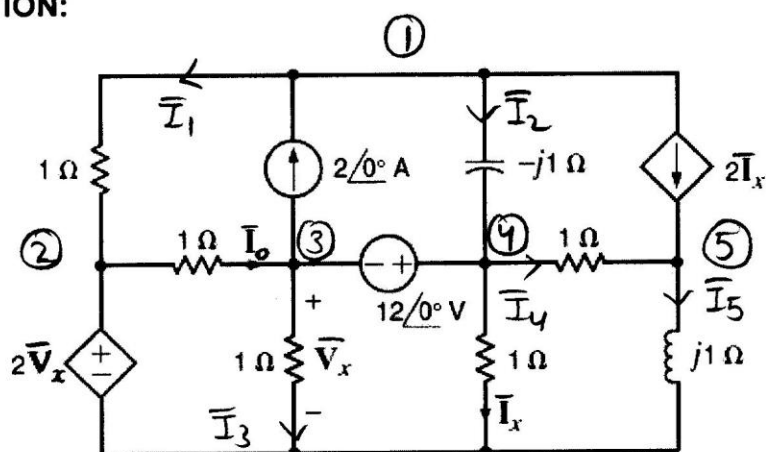

$$\text{KCL at } \textcircled{1}: \bar{I}_1 + \bar{I}_2 + 2\bar{I}_x = 2\angle 0^\circ$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + \frac{\bar{V}_1 - \bar{V}_4}{-j1} + 2 \left[ \frac{\bar{V}_4}{1} \right] = 2\angle 0^\circ$$

$$-j1(\bar{V}_1 - \bar{V}_2) + \bar{V}_1 - \bar{V}_4 - j2\bar{V}_4 = -j1(2\angle 0^\circ)$$

$$(1 - j1)\bar{V}_1 + j1\bar{V}_2 + (-1 - j2)\bar{V}_4 = 2\angle -90^\circ$$

$$\text{KCL at } \textcircled{5}: \bar{I}_4 + 2\bar{I}_x = \bar{I}_5$$

$$\frac{\bar{V}_4 - \bar{V}_5}{1} + 2 \left[ \frac{\bar{V}_4}{1} \right] = \frac{\bar{V}_5}{j1}$$

$$j1(\bar{v}_4 - \bar{v}_5) + j2\bar{v}_4 = \bar{v}_5$$

$$j3\bar{v}_4 + (-1-j1)\bar{v}_5 = 0$$

KCL at supernode:

$$\bar{I}_0 + \bar{I}_2 = 2\angle 0^\circ + \bar{I}_4 + \bar{I}_x + \bar{I}_3$$

$$\frac{\bar{v}_2 - \bar{v}_3}{1} + \frac{\bar{v}_4 - \bar{v}_5}{-j1} = 2\angle 0^\circ + \frac{\bar{v}_4 - \bar{v}_5}{1} + \frac{\bar{v}_4}{1} + \frac{\bar{v}_3}{1}$$

$$-j1(\bar{v}_2 - \bar{v}_3) + \bar{v}_1 - \bar{v}_4 = 2\angle 0^\circ(-j1) - j1(\bar{v}_4 - \bar{v}_5) - j1\bar{v}_4 - j1\bar{v}_3$$

$$\boxed{\bar{v}_1 - j1\bar{v}_2 + j2\bar{v}_3 + (-1+j2)\bar{v}_4 - j1\bar{v}_5 = 2\angle -90^\circ}$$

$$\bar{v}_2 = 2\bar{v}_x$$

$$\bar{v}_2 = 2[\bar{v}_3]$$

$$\bar{v}_2 - 2\bar{v}_3 = 0$$

$$-\bar{v}_3 + \bar{v}_4 = 12\angle 0^\circ$$

$$(1-j1)\bar{v}_1 + j1\bar{v}_2 + (-1-j2)\bar{v}_4 = 2\angle -90^\circ$$

$$j3\bar{v}_4 + (-1-j1)\bar{v}_5 = 0$$

$$\bar{v}_2 - 2\bar{v}_3 = 0$$

$$-\bar{V}_3 + \bar{V}_4 = 12 \angle 0^\circ$$

$$\bar{V}_1 - j1\bar{V}_2 + j2\bar{V}_3 + (-1+j2)\bar{V}_4 - j1\bar{V}_5 = 2 \angle -90^\circ$$

$$\bar{V}_1 = 7.11 \angle 140.7^\circ \text{ V}$$

$$\bar{V}_2 = 35.38 \angle -137.3^\circ \text{ V}$$

$$\bar{V}_3 = 17.7 \angle -137.3^\circ \text{ V}$$

$$\bar{V}_4 = 12.04 \angle -94.8^\circ \text{ V}$$

$$\bar{V}_5 = 25.54 \angle -49.8^\circ \text{ V}$$


$$\bar{I}_0 = \frac{\bar{V}_2 - \bar{V}_3}{1}$$

$$= \frac{35.38 \angle -137.3^\circ - 17.7 \angle -137.3^\circ}{1}$$

$$I_0 = 17.7 \angle -137.3^\circ \text{ A}$$

CREATE YOUR OWN WEB  
PAGE  
VISIT

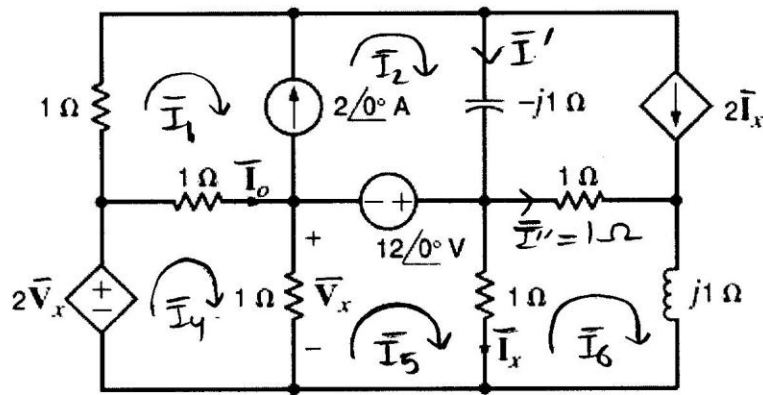[www.myUET.net.tc](http://www.myUET.net.tc)



$$\text{KCL: } \bar{I}_5 + \bar{I} = \bar{I}_4$$

$$\bar{I} = \bar{I}_4 - \bar{I}_5$$

$$\text{KCL: } \bar{I}_3 + \bar{I}'' = \bar{I}_6$$

$$\bar{I}'' = \bar{I}_6 - \bar{I}_3$$

$$\text{KCL: } \bar{I}_4 = \bar{I}_1 + \bar{I}_0$$

$$\bar{I}_0 = \bar{I}_4 - \bar{I}_1$$

$$\text{KCL: } \bar{I}_2 = \bar{I}' + \bar{I}_3$$

$$\bar{I}' = \bar{I}_2 - \bar{I}_3$$

$$\text{KCL: } \bar{I}_x + \bar{I}_6 = \bar{I}_5$$

$$\bar{I}_x = \bar{I}_5 - \bar{I}_6$$

$$\text{KVL: } 1(\bar{I}_0) + 1(\bar{I}) = 2\bar{V}_x$$

$$\bar{V}_x = \bar{I}(1) = \bar{I}_4 - \bar{I}_5$$

$$\bar{I}_4 - \bar{I}_1 + \bar{I}_4 - \bar{I}_5 = 2(\bar{I}_4 - \bar{I}_5)$$

$$\boxed{-\bar{I}_1 + \bar{I}_5 = 0}$$

$$\text{KVL: } 1(-1) + 1(\bar{I}_x) = 12 \angle 0^\circ$$

$$-(\bar{I}_4 - \bar{I}_5) + \bar{I}_5 - \bar{I}_6 = 12 \angle 0^\circ$$

$$\boxed{-\bar{I}_4 + 2\bar{I}_5 - \bar{I}_6 = 12 \angle 0^\circ}$$

$$\text{KVL: } 1(\bar{I}'') + j1(\bar{I}_6) + 1(-\bar{I}_x) = 0$$

$$\bar{I}_6 - \bar{I}_3 + j1\bar{I}_6 - (\bar{I}_5 - \bar{I}_6) = 0$$

$$\boxed{-\bar{I}_3 - \bar{I}_5 + (2 + j1)\bar{I}_6 = 0}$$

$$\text{KCL: } \bar{I}_1 + 2 \angle 0^\circ = \bar{I}_2$$

$$\boxed{\bar{I}_1 - \bar{I}_2 = -2 \angle 0^\circ}$$

$$\bar{I}_3 = 2\bar{I}_x$$

$$\bar{I}_3 = 2(\bar{I}_5 - \bar{I}_6)$$

$$\boxed{\bar{I}_3 - 2\bar{I}_5 + 2\bar{I}_6 = 0}$$

W  
W  
W  
-  
m  
y  
U  
E  
T  
-  
n  
e  
t  
-  
t  
c

$$\text{KVL: } 1(\bar{I}_1) - j1\bar{I}' + 12\angle 0^\circ + 1(-\bar{I}_0) = 0$$

$$\bar{I} - j1(\bar{I}_2 - \bar{I}_3) + 12\angle 0^\circ - \bar{I}_4 + \bar{I}_1 = 0$$

$$\boxed{2\bar{I}_1 - j1\bar{I}_2 + j1\bar{I}_3 - \bar{I}_4 = -12\angle 0^\circ}$$

$$-\bar{I}_1 + \bar{I}_5 = 0$$

$$-\bar{I}_4 + 2\bar{I}_5 - \bar{I}_6 = 12\angle 0^\circ$$

$$-\bar{I}_3 - \bar{I}_5 + (2+j1)\bar{I}_6 = 0$$

$$\bar{I}_1 - \bar{I}_2 = -2\angle 0^\circ$$

$$\bar{I}_3 - 2\bar{I}_5 + 2\bar{I}_6 = 0$$

$$2\bar{I}_1 - j1\bar{I}_2 + j1\bar{I}_3 - \bar{I}_4 = -12\angle 0^\circ$$

$$\bar{I}_1 = 35.11 \angle -125.73^\circ \text{ A}$$

$$\bar{I}_2 = 34 \angle -123^\circ \text{ A}$$

$$\bar{I}_3 = 24.1 \angle -94.8^\circ \text{ A}$$

$$\bar{I}_4 = 52.56 \angle -129.6^\circ \text{ A}$$

$$\bar{I}_5 = 35.11 \angle -125.73^\circ \text{ A}$$

$$\bar{I}_6 = 25.54 \angle -139.8^\circ \text{ A}$$

CREATE YOUR OWN WEB  
PAGE  
VISIT

[www.myUET.net.tc](http://www.myUET.net.tc)

$$\bar{I}_0 = \bar{I}_4 - \bar{I}_1$$

$$\bar{I}_0 = 52.56 \angle -129.6^\circ - 35.11 \angle -125.73^\circ$$

$$\bar{I}_0 = 17.7 \angle -137.3^\circ \text{ A}$$

MATLAB solution:

$$Y = \begin{bmatrix} 1-i & i & 0 & -1-2i & 0 & 0 & 0 & 3i & -1-i & 0 & 1-2 & 0 & 0 & 0 & -1 & 1 & 0 & 1-i & 2i \\ & & & & & & & & & & & & & & & & & -1+2i & -1 \end{bmatrix}$$

$$I = [-2i; 0; 0; 12; -2i; ]$$

$$V = \text{inv}(Y) * I$$

$$I_0 = V(2) - V(3) / 1$$

% Answer:

Y =

Columns 1 through 3

$$1.0000 - 1.0000i \quad 0 + 1.0000i \quad 0$$

$$0 \quad 0 \quad 0$$

$$0 \quad 1.0000 \quad -2.0000$$

$$0 \quad 0 \quad -1.0000$$

$$1.0000 \quad 0 - 1.0000i \quad 0 + 2.0000i$$

Columns 4 through 5

$$-1.0000 - 2.0000i \quad 0$$

$$0 + 3.0000i \quad -1.0000 - 1.0000i$$

$$0 \quad 0$$

$$1.0000 \quad 0$$

$$-1.0000 + 2.0000i \quad 0 - 1.0000i$$



$$I =$$

$$0 - 2.0000i$$

$$0$$

$$0$$

$$12.0000$$

$$0 - 2.0000i$$

$$V =$$

$$-5.5000 + 4.5000i$$

$$-26.0000 - 24.0000i$$

$$-13.0000 - 12.0000i$$

$$-1.0000 - 12.0000i$$

$$16.5000 - 19.5000i$$

$$I_0 =$$

$$-13.0000 - 12.0000i$$

**W  
W  
W  
-  
m  
y  
U  
E  
T  
-  
n  
e  
t  
-  
t  
c**



- 8.126** The network in Fig. P8.126 operates at  $f = 60$  Hz.  
Use PSpice to find the voltage  $V_o$ .


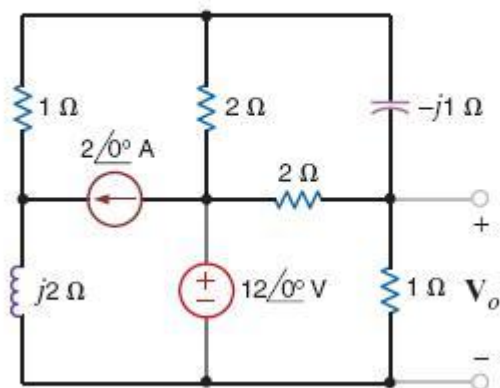


Figure P8.126

**SOLUTION:**

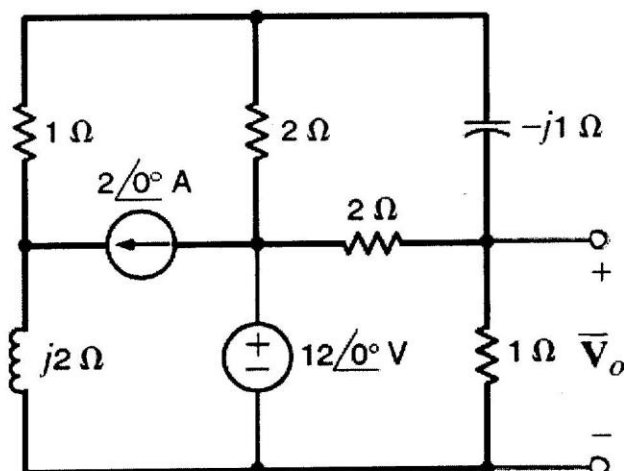

$$F = 60 \text{ Hz} \quad , \quad \omega = 377 \text{ rad/s}$$


$$\bar{Z}_L = j\omega L$$

$$L = \frac{\bar{Z}_L}{j\omega} = \frac{j2}{j(377)} = 5.3 \text{ mH}$$

$$\bar{Z}_C = \frac{1}{j\omega C}$$

$$C = \frac{1}{j\omega \bar{Z}_C} = \frac{1}{j(377)(-j1)}$$

$$C = 2.65 \text{ mF}$$

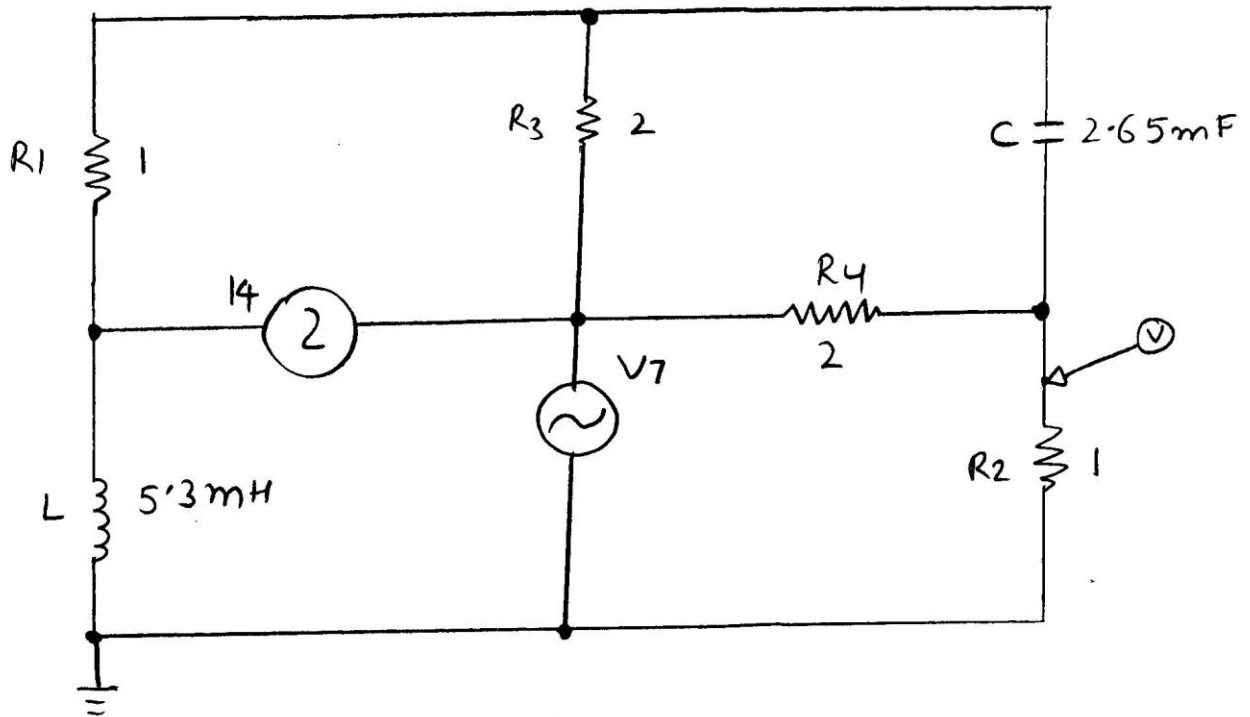

PSPICE Schematic Diagram

\*\*\*\* AC ANALYSIS

\*\*\*\*\*

FREQ VM(\$N\_0004) VP(\$N\_0004)

6.000E+01 4.368E+00 1.018E+01

WE NEED YOUR FEED BACK

[www.myUET.net.tc](http://www.myUET.net.tc)